



PHYSICS

BOOKS - NCERT PHYSICS (ENGLISH)

CURRENT ELECTRICITY

Mcqs

1. Consider a current carrying wire (current I)
in the shape of a circle

A. source of emf

B. electric field produced by charges
accumulated on the surface of wire


C. the charges just behind a given segment
of wire which push them just the right
way by repulsion

D. The charges ahead.

Answer: B



Watch Video Solution

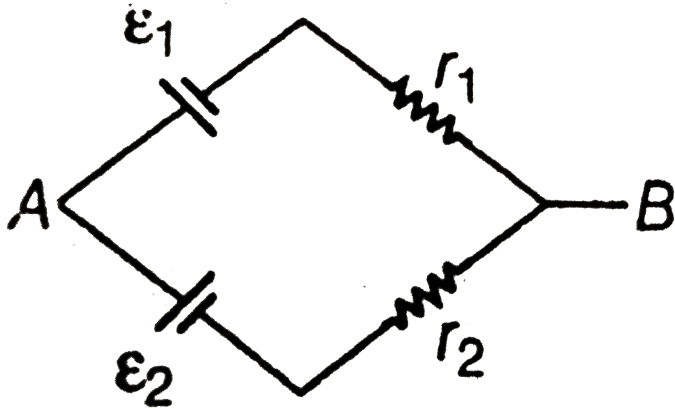

2.

Two batteries of emf ϵ_1 and ϵ_2 ($\epsilon_2 > \epsilon_1$) and internal resistance r_1 and r_2 respectively are connected in parallel as shown in figure.

A. The equivalent emf ϵ_{eq} of the two cells is

between ϵ_1 and ϵ_2 , i.e., $\epsilon_1 < \epsilon_{eq} < \epsilon_2$

B. the equivalent emf ϵ_{eq} is smaller than ϵ_1

C. The ε_{eq} is given by $\varepsilon_{eq} = \varepsilon_1 + \varepsilon_2$ always.

D. ε_{eq} is independent of internal resistance

r_1 and r_2 .

Answer: A



Watch Video Solution

3. A resistance R is to be measured using a meter bridge. Student chooses the standard resistance S to be 100Ω . He finds the null point at $l_1 = 2.9cm$. He is told to attempt to

improve the accuracy. Which of the following is a useful way?

A. He should measure I_1 more accurately

B. He should change S to 1000Ω and repeat the experiment

C. He should change S to 3Ω and repeat the experiment.

D. He should give up hope of a more accurate measurement with a meter bridge

Answer: C



Watch Video Solution

4. Two cells of emfs approximately 5V and 10V are to be accurately compared using a potentiometer of length 400 cm.

A. The battery that runs the potentiometer should have voltage of 8 V

B. The battery of potentiometer can have a voltage of 15 V and R adjusted so that

the potential drop across the wire slightly exceeds 10 V

C. The first portion of 50 cm of wire itself should have a potential drop of 10V

D. Potentiometer is usually used for comparing resistances and not voltages.

Answer: B



Watch Video Solution

5. A metal rod of the length 10cm and a rectangular cross-section of 1 cm x $\frac{1}{2}$ cm is connected to a battery across opposite faces.

The resistance will be

A. maximum when the battery is connected

across $1\text{cm} \times \frac{1}{2}\text{cm}$ faces

B. maximum when the battery is connected

across $10\text{cm} \times 1\text{cm}$ faces

C. maximum when the battery is connected

across $10\text{cm} \times \frac{1}{2}\text{cm}$ faces.

D. Same irrespective of the three faces.

Answer: A



Watch Video Solution

6. Which of the following characteristics of electrons determines the current in a conductor?

A. Drift velocity along

B. Thermal velocity alone

C. Both drift velocity and thermal velocity

D. Neither drift nor thermal velocity.

Answer: A



Watch Video Solution

Mcqs More Than One Options

1. Kirchoff's junction rule is a reflection of

A. conservation of current density vector.

B. conservation of charge

C. the fact that the momentum with which a charged particle approaches a junction is unchanged (as a vector) as the charged particle leaves the junction

D. The fact that there is no accumulation of charges at a junction.

Answer: B::D



Watch Video Solution


2. Consider a simple circuit shown in Fig.

2(ET).2. stands for a variable resistance R' . R'

can vary from R_0 to infinity. r is internal

resistance of the battery

$$(r \ll R \ll lR_0)$$

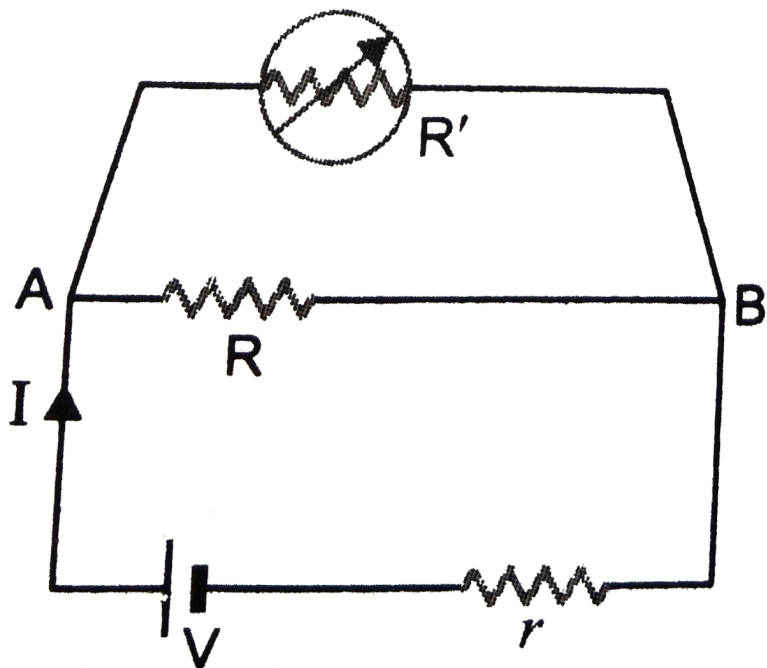

A. Potential drop across AB is nearly constant as R' is varied

B. Current through R' is nearly a constant as R' is varied

C. Current I depends sensitively on R'

D. $I \geq \frac{V}{r + R}$ always.

Answer: A::D



Watch Video Solution

3. Temperature dependence of resistivity $\rho(T)$ of semiconductors, insulators and metals is significantly based on the following factors:

A. Numbr of charge carriers can change with temperature T

B. time interval between two successie collisions can depend of T

C. length of material can be a function of T


D. mass of carriers is a function of T.

Answer: A::B



Watch Video Solution

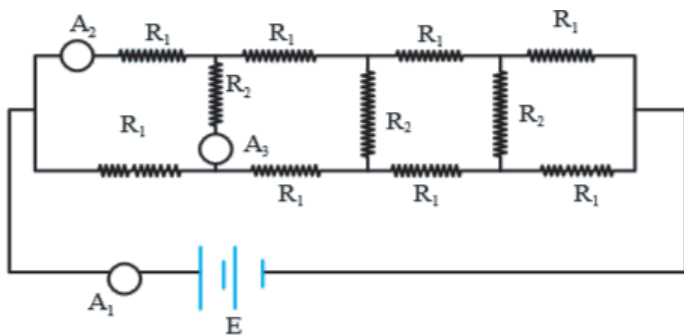4. In the given circuit, $R_1 = 10\Omega$ $R_2 = 6\Omega$ and $E = 10V$, then correct statement is



A. The errors of measurement of two students are the same

B. Errors of measurement do depend on the accuracy with which R_2 and R_1 can be measured

C. If the student uses large values of R_2 and R_1 the currents through the arms will be feeble. This will make determination of null point accurately more difficult.

D. Whatstone bridge is a very accurate instrument and has no errors of


measurement.

Answer: B::C



Watch Video Solution

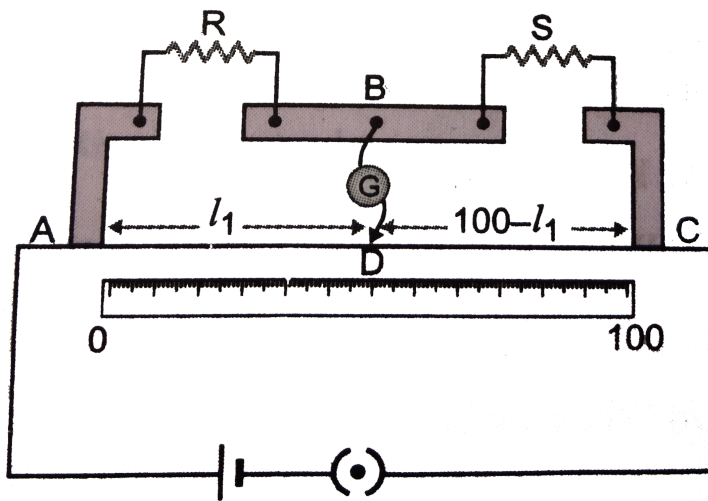5. In a meter bridge the point D is a neutral point (Fig. 2(EP).4).



A. The meter bridge can have no other neutral. A point for this set of resistances

B. When the jockey contacts a point on meter wire left of D, currents flows to B

from the wire.

C. When the jockey contacts a point on the metre wire to the right of D, current flows from B to the wire through galvanometer.

D. When R is increased the neutral point shifts to left.

Answer: A::C



Watch Video Solution

Very Short Answer Type Question

1. Is the motion of a charge across junction momentum conserving ? Why or why not ?



[Watch Video Solution](#)

2. The relaxation time τ is nearly independent of applied electric field E whereas it changes significantly with temperature T . First fact is (in part) responsible for Ohm's law whereas

the second fact leads to variation of p with temperature. Elaborate why ?



[Watch Video Solution](#)

3. What are the advantages of the null-point method in a Wheatstone bridge ? What additional measurements would be required to calculate R_{unknown} by any other method ?



[Watch Video Solution](#)

4. What are the advantages of using thick metallic strips to join wires in a potentiometer ?



[Watch Video Solution](#)

5. For wiring in the home, one uses Cu wires or Al wires. What considerations are involved in this ?



[Watch Video Solution](#)

6. Why are alloys used for making standard resistance coils?



[Watch Video Solution](#)

7. Power P is to be delivered to a device via transmission cables having resistance R_c . If V is the voltage across R and I the current through it, find the power wasted and how can it be reduced.




[Watch Video Solution](#)

8. AB is a potentiometer wire Fig. If the value of R is increased, in which direction will the balance point J shift ?



Watch Video Solution

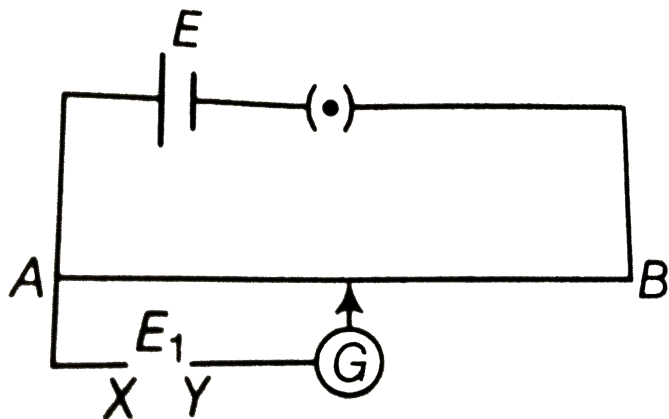

9.

While doing an experiment with

potentiometer (figure) it was found that the deflection is one sided and (i) the deflection decreased while moving from one end A of the wire, to the end R, (ii) the deflection increased, while the jockey was moved towards the end D.

(i). Which terminal positive or negative of the cell E_1 is connected at X in case (i) and how is

E_1 , related to E?

(ii). Which terminal of the cell E_1 is connected at X in case (1 in 1)?



Watch Video Solution

10. A cell of emf E and internal resistance r is connected across an external resistance R . Plot a graph showing the variation of $P.D.$ across R , versus ' R '.



Watch Video Solution

11. First a set of n equal resistors of R each are connected in series to a battery of emf E and internal resistance R . A current I is observed to flow. Then, the n resistors are connected in

parallel to the same battery. It is observed that the current is increased 10 times. What is 'n'?



[Watch Video Solution](#)

12. Let there be n resistors $R_1 \dots R_n$ with

$$R_{\max} = \max (R_1 \dots R_n) \quad \text{and}$$

$$R_{\min} = \min \{R_1 \dots R_n\}. \text{ Show that when}$$

they are connected in parallel the resultant

resistance $R_p = R_{\min}$ and when they are



connected in series, the resultant resistance

$R_s > R_{\max}$. Interpret the result physically.




Watch Video Solution

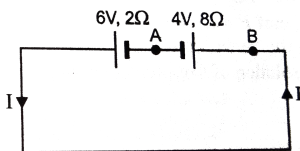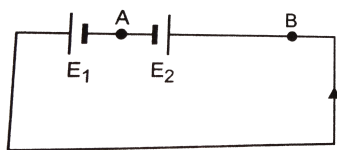13. The circuit in Fig. shows two cells connected in opposition to each other. Cell E_1 is of emf $6V$ and internal resistance 2Ω , the cell E_2 is of emf $4V$ and internal resistance 8Ω . Find the potential difference between the points A and B .



Watch Video Solution

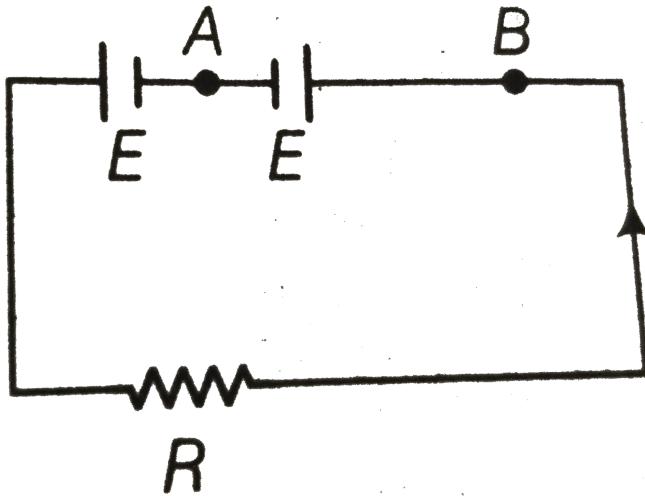

14.

Two cells of same emf E but internal resistance r_1 and r_2 are connected in series to an external resistor R (figure). What should be the value of R so that the potential difference across the terminals of the first cell becomes zero?



Watch Video Solution

15. Two conductors are made of the same material and have the same length. Conductor A is a solid wire of diameter 1mm . Conductor B is a hollow tube of outer diameter 2mm and inner diameter 1mm . Find the ratio of resistance R_A to R_B .



[Watch Video Solution](#)


16. Suppose there is a circuit consist of only resistance and batteries , suppose one is to double (or increase it to in n-times)all voltage and all resistances , show that currents are unaltered



Watch Video Solution

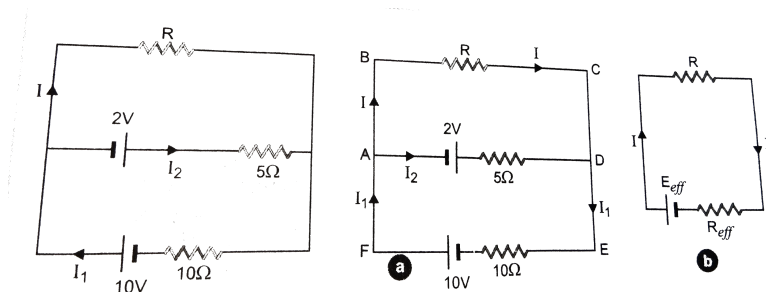17. Two cells of voltage $10V$ and $2V$ and internal resistance 10Ω and 5Ω respectively , are connected in parallel with the position and

of $10V$ battery connected to negative pole of $2V$ battery Find the effected voltage and effected resistance of the combination



Watch Video Solution

18. A room AC run for 5 hour at a voltage of $220V$ The wiring of the room constant of C_u of $1mm$ ratio and a length of $10m$

consumption per day is 10 commercial unit

What fraction of it goes in the joule heated in

wire? What would happen if the wiring is

made of aluminum of the same distances?

$$[\rho_{cu} = 1.7 \times 10^{-8} \Omega, \rho_{Al} = 2.7 \times 10^{-8} \Omega m]$$



[View Text Solution](#)


19. In an experiment with a potentiometer,

$V_B = 10V$. R is adjusted to be 50Ω (see figure)

. A student wanting to measure voltage E_1 of


a battery (approx. 8V) finds no null point.He

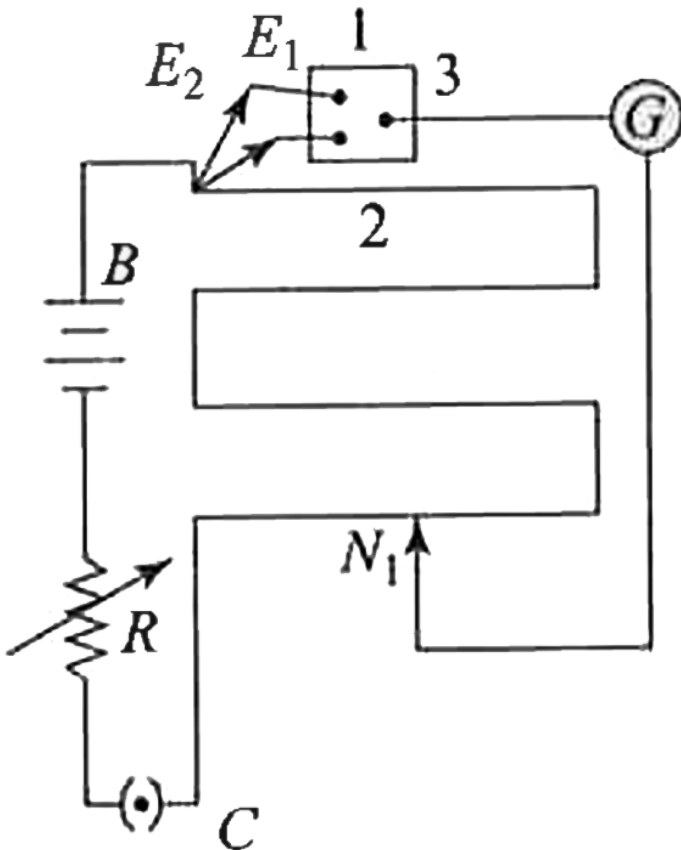then diminishes R to 10Ω and is able to locate the null point on the last (4th) segment of the potentiometer. Find the resistance of the potentiometer wire and potential drop per unit length across the wire in the second case.





Watch Video Solution

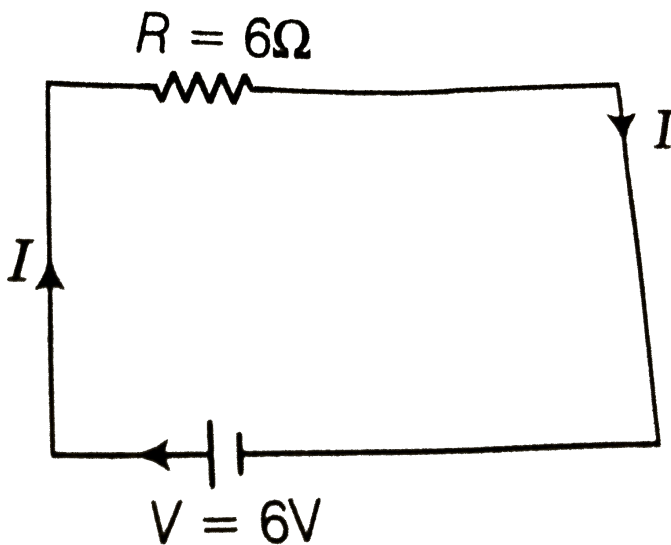

20.

(a). Consider circuit in figure. How much energy is absorbed by electrons from the initial state of no current (ignore thermal motion) to the state of drift velocity?

(b). Electrons give up energy at the rate of

RI^2 per second to the thermal energy. what time scale would number associate with energy in problem (a)? n =number of electron/volume = $10^{29} / m^3$. Length of circuit = $10cm$, cross-section= $A=(1mm)^2$.



Watch Video Solution