



PHYSICS

BOOKS - JEEVITH PUBLICATIONS

PHYSICS (KANNADA ENGLISH)

ALTERNATING CURRENT

One Marks Questions With Answers

1. What is meant by alternating current?



Watch Video Solution

2. Mention any one advantage of ac over dc.



[Watch Video Solution](#)

3. What is the phase relation between voltage and current in a resistor connected to an ac voltage?



[Watch Video Solution](#)

4. Give an expression for the average value of a time function $F(t)$ over a complete time period.



[Watch Video Solution](#)

5. What is the value of $\langle \cos 2\omega t \rangle$ over a complete period?



[Watch Video Solution](#)

6. Give the average value of $\sin^2 \omega t$ ($\langle \sin^2 \omega t \rangle$).



[Watch Video Solution](#)

7. Give the expression for average power dissipated in a resistor over a complete as cycle.



[Watch Video Solution](#)

8. What will be the instantaneous power dissipation in the resistor connected to ac?



[Watch Video Solution](#)

9. Draw voltage and current waveform in a pure resistor connected to ac



[Watch Video Solution](#)

10. Mention the average value of ac over one complete ac cycle



Watch Video Solution

11. Relate v_{rms} and v_{peak} values of ac.



Watch Video Solution

12. Relate v_{rms} and v_{ave} over one half of an ac cycle.



[Watch Video Solution](#)

13. Will there be any energy loss in the case of a pure inductor or a pure capacitor connected in ac circuits?



[Watch Video Solution](#)

14. What is a low pass filter?



[Watch Video Solution](#)

15. What is the value of inductive reactance of a pure inductor connected to DC?



Watch Video Solution

16. Why is that a pure inductor not used to control DC?



Watch Video Solution

17. What is meant by a high pass filter?





[Watch Video Solution](#)

18. What is the value of capacitive reactance connected to DC?



[Watch Video Solution](#)

19. Give the expression for wattless component of current in a pure inductor or capacitor.



[Watch Video Solution](#)

20. Mention the power factor of a pure inductor or a capacitor.



Watch Video Solution

21. What is the value of power factor of a pure resistor?



Watch Video Solution

22. How does current in a pure resistor vary in terms of phase diagram with the voltage across it?



Watch Video Solution

23. How does current in a pure capacitor vary in terms of phase angle with the voltage across it?



Watch Video Solution

24. What does an ac voltmeter or an ac ammeter in an ac circuit measure?



[Watch Video Solution](#)

25. What does a DC voltmeter measure when connected across a load resistor in an ac circuit?



[Watch Video Solution](#)

26. Can a capacitor of suitable capacitance replace a choke coil in an ac circuit?



Watch Video Solution

27. (a) For circuits used for transporting electric power, a low power factor implies large power loss in transmission. Explain.

(b) Power factor can often be improved by the use of a capacitor of appropriate capacitance in the circuit. Explain.





[Watch Video Solution](#)

28. A choke coil is connected in series with a lamp and the combination across a dc supply. What happens to the intensity of light if an iron core is used in the coil?



[Watch Video Solution](#)

29. If ac supply is used and an iron core is introduced in a coil connected in series with

the bulb, then what happens to the intensity of the bulb?



[Watch Video Solution](#)

30. Write the expression for the electromagnetic energy of an electrical system.



[View Text Solution](#)

31. Give the differential equation for an LC oscillator in the absence of an ac source and resistor.



Watch Video Solution

32. What is an alternating emf?



Watch Video Solution

33. What is an AC waveform?



[Watch Video Solution](#)

34. Define the period of an AC.



[Watch Video Solution](#)

35. Define the frequency of an Ac.



[Watch Video Solution](#)

36. Define the peak value of an AC.



[Watch Video Solution](#)

37. Define the mean value of an AC.



[Watch Video Solution](#)

38. Define the rms value of an AC.



[Watch Video Solution](#)

39. Give one method of generating a sinusoidal AC.



Watch Video Solution

40. Define instantaneous value of AC.



Watch Video Solution

41. Define inductive reactance. On what factors does it depend?



Watch Video Solution

42. Define capacitive reactance. On what factors does it depend?



Watch Video Solution

43. Define impedance of an AC circuit.



Watch Video Solution

44. Write the formula for the impedance of a series LCR circuit.



Watch Video Solution

45. What is the phase relation between current and voltage in a series LCR circuit in which $X_L < X_C$?



Watch Video Solution

46. What is the power factor of a series LCR circuit in which $X_L > X_C$?



View Text Solution

47. Under what condition will the current through a series LCR circuit be in phase with voltage?



Watch Video Solution

48. What is a choke?



Watch Video Solution

49. What is a transformer?



Watch Video Solution

50. When is a transformer said to be ideal?



Watch Video Solution

51. What is wattless current?



Watch Video Solution

52. What is a step up transformer?



Watch Video Solution

53. What is a step down transformer?



Watch Video Solution

Two Marks Questions With Answers

1. Draw a phasor diagram for the ac circuit comprising of a pure resistor.



[Watch Video Solution](#)

2. Draw phasor diagram for the ac circuit comprising of a pure inductor.



[Watch Video Solution](#)

3. Draw phasor diagram for the ac circuit comprising of a pure capacitor.



[Watch Video Solution](#)

4. Draw phasor diagram for a RLC series circuit connected to ac voltage source.



[Watch Video Solution](#)

5. Based on what principle does a transformer work? Explain.



[Watch Video Solution](#)

6. Define 'Q' factor and sharpness of resonant curve.



[Watch Video Solution](#)

7. What is the relation between rms and average values of a sinusoidal A.C. voltage?



[Watch Video Solution](#)

8. Give the differential equation for an LC oscillator.



[Watch Video Solution](#)

9. Give the expression for the instantaneous energy stored in a capacitor along with the meaning of the symbols used.



[Watch Video Solution](#)

10. Give the expression for the instantaneous energy stored in an inductor along with the meaning of the symbols used.



Watch Video Solution

11. If $V = V_m \sin \omega t$ represents instantaneous voltage connected across a resistor of resistance 'R' then write the expression for the instantaneous current in it.



Watch Video Solution

12. Write the equation for a sinusoidal AC voltage. Give meaning of the symbols used.



[Watch Video Solution](#)

Three Marks Questions With Answers

1. Draw current v/s frequency curve for a series RLC circuit and explain the different portions of the curve.



[Watch Video Solution](#)

2. Distinguish between a pure inductor and a pure resistor.



[Watch Video Solution](#)

3. Distinguish between HF chokes and LF chokes.



[Watch Video Solution](#)

4. Define inductive reactance. On what factors does it depend?



Watch Video Solution

5. Define capacitive reactance. On what factors does it depend?



Watch Video Solution

6. Define the term power factor. What is the value of power factor for a pure resistor, pure inductor and pure capacitor?



[Watch Video Solution](#)

7. What are the uses of an induction coil?



[Watch Video Solution](#)

8. Distinguish between DC and AC.



[Watch Video Solution](#)

9. Show that the sum of electrostatic energy and magnetic energy in an LC oscillator equals

$$\frac{q_0^2}{2C}$$



[Watch Video Solution](#)

10. Give an expression for an ac driven series RLC circuit.



[Watch Video Solution](#)

11. S.T. average power over a complete cycle in a pure inductor connected to ac is zero.



[Watch Video Solution](#)

Five Marks Questions With Answers

1. Show that the current in a pure resistor is in phase with the ac voltage across it and hence S.T. average power dissipation in a resistor is $i^2 R$ where I is r.m.s value of ac.



[Watch Video Solution](#)

2. Show that voltage in an inductor leads the current by $\pi / 2$ rad for a pure inductor



[Watch Video Solution](#)

3. S.T. the voltage across a pure capacitor lags the current by 90° or $\frac{\pi}{2}$ rad.



[Watch Video Solution](#)

4. Obtain an expression for the impedance of a series LCR circuit. (using phasor diagram method).



[Watch Video Solution](#)

5. Give the expression for the impedance of an LCR circuit and obtain the expression for the resonant frequency. What is the power factor of the resonant circuit?



[Watch Video Solution](#)

6. Explain the advantage and disadvantages of AC over DC.



[Watch Video Solution](#)

7. Obtain an expression for the average power supplied to a series RLC circuit. Discuss the average power when the series RLC circuit behaves as a pure resistive, inductive or capacitive circuit.



[Watch Video Solution](#)

8. S.T an LC oscillator executes SHM and hence obtain an expression for the angular frequency of oscillation.



Watch Video Solution

9. Write a note a transformers.



Watch Video Solution

10. Give the qualitative explanation of the action of an LC oscillator in the absence of any external ac voltage source. Assume that the capacitor is charged initially.



Watch Video Solution

11. Obtain an expression for quality factor of series RLC circuit connected to ac source.



Watch Video Solution

12. Give analytical solution to a series RLC circuit connected to ac.



[Watch Video Solution](#)

Numericals With Solutions

1. A 220 AC voltage source is connected across a pure inductor of inductance 0.5 H. Find the current through the inductor, if the frequency of the source is

100 Hz



[Watch Video Solution](#)

2. A 220 AC voltage source is connected across a pure inductor of inductance 0.5 H. Find the current through the inductor, if the frequency of the source is

150 kHz



[Watch Video Solution](#)

3. A 220 AC voltage source is connected across a pure inductor of inductance 0.5 H. Find the current through the inductor, if the frequency of the source is 50Hz What is the power lost in the inductor?



[Watch Video Solution](#)

4. If a coil is to have a reactance of 16Ω for a frequency 2 kHz, then what must be its

inductance? What will be its reactance at 10 Hz?



[Watch Video Solution](#)

5. A pair of adjacent coils have a mutual inductance of 0.25 H. If the current in the primary changes from zero to 2A in 0.05 s., then find the average induced emf in the secondary?



[Watch Video Solution](#)

6. A sinusoidal current is represented by the equation $I = 2 \sin 100\pi t$. Calculate

Period



[Watch Video Solution](#)

7. A sinusoidal current is represented by the equation $I = 2 \sin 100\pi t$. Calculate

RMS value



[Watch Video Solution](#)

8. A sinusoidal current is represented by the equation $I = 2 \sin 100\pi t$. Calculate

Current at $t = \frac{1}{16}$ s.



[Watch Video Solution](#)

9. A sinusoidal current is represented by the equation $I = I_0 \sin 100\pi t$. Calculate

Time required by the current to change its value from zero to the RMS value.



[Watch Video Solution](#)

10. An A.C. Source of 250 V, 50 Hz is connected to a circuit consisting of an electric lamp rated 100 W, 50 V and a capacitor in series. What should be value of the capacitance of the capacitor to make the lamp work at the rated value?



Watch Video Solution

11. A coil of resistance 100Ω , an inductor of 0.5 H and a capacitor of $15\mu F$ are connected in

series with a $200V - 50Hz$ AC source.

Calculate the current in the circuit.



[Watch Video Solution](#)

12. In the circuit as show in figure, find the impedance of the circuit. What is the phase angle between voltage and current? (given

$$V_{rms} = 220V, f = 50Hz)$$



[View Text Solution](#)

13. A 100Ω resistor is connected to a 220 V, 50 Hz ac supply

What is the rms value of the current in the circuit?



Watch Video Solution

14. A 100Ω resistor is connected to a 220 V, 50 Hz ac supply

What is the net power consumed over a full cycle?



Watch Video Solution

15. A 44 mH inductor is connected to a 220 V, 50Hz ac supply. Determine the r.m.s value and peak value of the current in the circuit.



Watch Video Solution

16. A $60\mu F$ capacitor is connected to a 110V, 60Hz, ac supply. Determine the r.m.s value of a current in the circuit.



Watch Video Solution

17. Obtain the resonant frequency ω_r of a series LCR circuit with $L = 2.0 \text{ H}$, $C = 32\mu\text{F}$, and $R = 10\Omega$. What is the Q - value of this circuit?



[Watch Video Solution](#)

18. A charged $30\mu\text{F}$ capacitor is connected in series to a 27mH inductor. What is the angular frequency of free oscillations of the circuit?



 [Watch Video Solution](#)

19. A series LCR circuit with $R = 20\Omega$, $L = 1.5H$, and $C = 35\mu F$ is connected to a variable frequency 200 V ac supply. When the frequency of the supply equals the natural frequency of the circuit, what is the average power transferred to the circuit in one complete cycle?



[Watch Video Solution](#)

20. A coil of inductance 0.50 H , and resistance 100Ω is connected to a 240V , 50Hz ac supply

What is the maximum current in the coil?



Watch Video Solution

21. A coil of inductance 0.50 H , and resistance 100Ω is connected to a 240V , 50Hz ac supply

What is the time lag between the voltage maximum and the current maximum?



Watch Video Solution

22. A 100×10^{-6} capacitor is series with a 40Ω resistance is connected to a 110 V, 60 Hz supply.

What is the maximum current in the circuit?



Watch Video Solution

23. A 100×10^{-6} capacitor is series with a 40Ω resistance is connected to a 110 V, 60 Hz supply.

What is the time lag between current maximum and the voltage maximum?



[Watch Video Solution](#)

24. A circuit containing an inductor of 80mH inductance and a capacitor of $60\mu\text{F}$ capacitance in series, is connected to a 230V , 50Hz supply. The resistance of the circuit is negligible.

Obtain the current amplitude and r.m.s value.



[Watch Video Solution](#)

25. A circuit containing an inductor of 80mH inductance and a capacitor of $60\mu\text{F}$ capacitance in series, is connected to a 230V , 50Hz supply. The resistance of the circuit is negligible.

Obtain the r.m.s values of potential drop across each element.



Watch Video Solution

26. A circuit containing an inductor of 80mH inductance and a capacitor of $60\mu\text{F}$ capacitance in series, is connected to a 230V , 50Hz supply. The resistance of the circuit is negligible.

What is the average power transferred to the inductor?



Watch Video Solution

27. A circuit containing an inductor of 80mH inductance and a capacitor of $60\mu\text{F}$ capacitance in series, is connected to a 230V , 50Hz supply. The resistance of the circuit is negligible.

What is the average power transferred to the capacitor?



[Watch Video Solution](#)

28. A circuit containing an inductor of 80mH inductance and a capacitor of $60\mu\text{F}$ capacitance in series, is connected to a 230V , 50Hz supply. The resistance of the circuit is negligible.

What is the total average power absorbed by the circuit (averaged over one complete cycle)?



Watch Video Solution

29. A power transmission line feeds input power at 2300V to a step down transformer with its primary windings having 4000 turns. What should be the number of turns in the secondary in order to get the output power at 230V? For an efficiency of 0.70, calculate the rms value of the primary current when rms value of the secondary current is 5A.



Watch Video Solution

30. At a hydroelectric power plant, the water pressure head is at a height of 300 m and the water flow available is $100\text{m}^3\text{s}^{-1}$. If the turbine generator efficiency is 60%, estimate the electric power available from the plant ($g = 9.8\text{ms}^{-2}$).



Watch Video Solution

31. A series LRC circuit comprising of an inductor of inductance 3H, a resistor of

resistance 7.4Ω and a capacitor of capacitance $27\mu F$. When connected to an a.c source, the circuit resonates at a particular frequency. Calculate angular resonant frequency and quality factor of the resonant circuit.



[Watch Video Solution](#)

32. A sinusoidal voltage of peak value $283V$ and frequency $50Hz$ is applied to a series LCR circuit in which

$R = 3\Omega$, $L = 25.48mH$ and $C = 786\mu F$.

Find: Impedance of the circuit.



[Watch Video Solution](#)

33. A sinusoidal voltage of peak value 283V and frequency 50Hz is applied to a series LCR circuit in which

$R = 3\Omega$, $L = 25.48mH$ and $C = 786\mu F$.

The phase difference between the voltage across the source and the current.



[Watch Video Solution](#)

34. A sinusoidal voltage of peak value 283V and frequency 50Hz is applied to a series LCR circuit in which

$$R = 3\Omega, L = 25.48mH \text{ and } C = 786\mu F.$$

The power factor.



Watch Video Solution