



PHYSICS

BOOKS - JEEVITH PUBLICATIONS

PHYSICS (KANNADA ENGLISH)

CURRENT ELECTRICITY

One Mark Questions And Answers

1. What constitutes an electric current?



Watch Video Solution

2. What is the net flow of charge at the given cross section of a conductor?



[Watch Video Solution](#)

3. Define electric current.



[Watch Video Solution](#)

4. Mention the S.I. unit of current.



[Watch Video Solution](#)

5. What is the direction of conventional current?



[Watch Video Solution](#)

6. What is the direction of flow of electrons in a conductor?



[Watch Video Solution](#)

7. Define 'drift velocity' of free electrons .



[Watch Video Solution](#)

8. Define relaxation time or mean free time.



[Watch Video Solution](#)

9. Define electron mobility.



[Watch Video Solution](#)

10. What is the order of relaxation time?



Watch Video Solution

11. Mention the SIU of electron mobility.



Watch Video Solution

12. How does drift velocity depend on electric current?



Watch Video Solution

13. What is the average electron thermal velocity at room temperature?



Watch Video Solution

14. What is the order of drift velocity of electrons?



Watch Video Solution

15. State Ohm's law.



Watch Video Solution

16. Define electrical resistance.



Watch Video Solution

17. Mention the SIU of electrical resistance.



Watch Video Solution

18. Define the unit one ohm.



Watch Video Solution

19. How does the resistance of a conductor depend on its length?



Watch Video Solution

20. How does electrical resistance depend on the area of cross-section of a conductor?



[Watch Video Solution](#)

21. Define electrical conductance?



[Watch Video Solution](#)

22. Mention the SI units of electrical conductance?



[Watch Video Solution](#)

23. What is ohmic device? Give one example.



Watch Video Solution

24. What is ohmic device? Give one example.



Watch Video Solution

25. A graph of electric current along the y-axis and potential difference along the x-axis gives

a straight line passing through the origin.

What does the slope determine?



Watch Video Solution

26. What are non ohmic devices?



Watch Video Solution

27. Write the dimensional formula for electrical resistance?



Watch Video Solution

28. Define resistivity.



Watch Video Solution

29. Mention the SIU of resistivity.



Watch Video Solution

30. Write the dimensional formula for resistivity.



Watch Video Solution

31. What is meant by electrical conductivity?



Watch Video Solution

32. Mention the SI unit of electrical conductivity.



Watch Video Solution

33. Write the equivalent mathematical form for Ohm's law.



Watch Video Solution

34. Express the range of resistivity of conductors.



Watch Video Solution

35. What is the range of resistivity of semiconductors?



Watch Video Solution

36. What is the range of resistivity of insulators?



Watch Video Solution

37. Show variation of resistivity of copper as a function of temperature in a graph.



Watch Video Solution

38. Draw a graph of resistivity of nichrome as a function of absolute temperature.




Watch Video Solution

39. Plot a graph of resistivity of a semiconductor as a function of absolute temperature.



Watch Video Solution

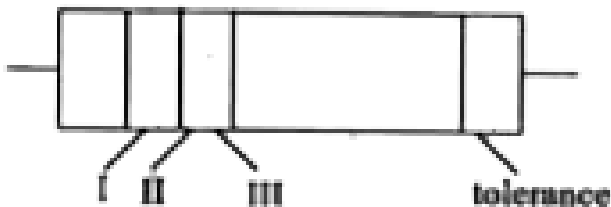40. The first three colour bands are Red, Red, Orange. What will be the value of resistance of the resistor?





[Watch Video Solution](#)

41. Define temperature coefficient of resistance of a conductor. Give the expression for temperature coefficient.



[Watch Video Solution](#)

42. What is meant by 'Critical temperature'?



[Watch Video Solution](#)

43. What are super conductors?



Watch Video Solution

44. A carbon resistor is marked Red, Red, Red, Gold. What is the value of its resistance?



Watch Video Solution

45. Compare R_s with R_p for 'n' identical resistors connected in series and parallel

combinations.



Watch Video Solution

46. Define EMF of a cell.



Watch Video Solution

47. What amount of energy is derived from a cell by a capacitor, to charge it completely?



Watch Video Solution

48. Define internal resistance of a cell.



Watch Video Solution

49. Define one volt of emf



Watch Video Solution

50. What happens to the effective resistance when two resistors are connected in series?



Watch Video Solution

51. Two resistors are connected in parallel.
What will happen to its equivalent resistance?



Watch Video Solution

52. Define effective resistance of a number of resistors connected in a series or parallel combination



Watch Video Solution

53. Obtain an expression for equivalent resistance of two resistors connected in parallel.



Watch Video Solution

54. What is the reciprocal of resistance called?



Watch Video Solution

55. What is the reciprocal of resistivity called?





[Watch Video Solution](#)

56. Why is that the terminal potential difference is always less than the e.m.f. of a cell?



[Watch Video Solution](#)

57. What is the unit of e.m.f.?




[Watch Video Solution](#)

58. Give the colour code for $10\Omega \pm 10\%$ tolerance resistor.



Watch Video Solution

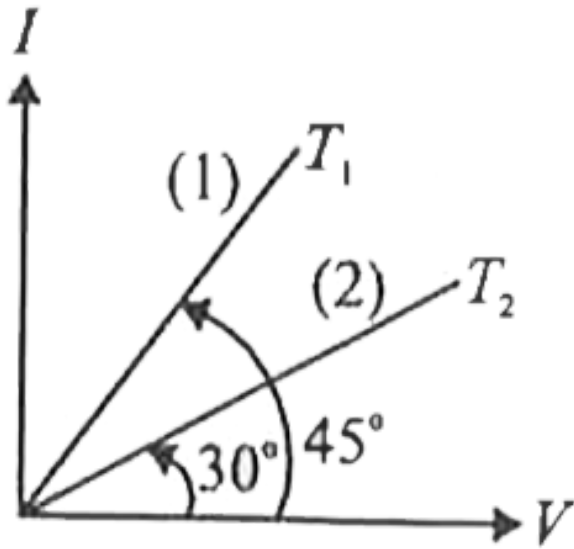59. In the following graph, say whether $T_1 > T_2$ or not.



[Watch Video Solution](#)

60. How does resistivity depend on number density of electrons?



[Watch Video Solution](#)

61. The length of a conductor is increased two folds. What will happen to the resistivity of the material?



Watch Video Solution

62. Why are Manganin and Constantan used in making resistance coils?



Watch Video Solution

63. Define the term current density.



Watch Video Solution

64. What is an electrical network?



Watch Video Solution

65. What is a node?



Watch Video Solution

66. What is a mesh or loop?



Watch Video Solution

67. What principle is involved in Kirchhoff's first law?



Watch Video Solution

68. What is the significance of Kirchhoff's voltage law?



Watch Video Solution

69. Can Kirchoff's laws be applied to AC circuits?



Watch Video Solution

70. What is the principle of a metre bridge?



Watch Video Solution

71. Write the balanced condition of Wheatstone's network.



[Watch Video Solution](#)

72. Why are the connections between the resistors in a meter bridge made of thick copper strips ?



[Watch Video Solution](#)

73. What is generally connected in the right gap of a metre bridge?



Watch Video Solution

74. If the galvanometer in the Wheatstone's network is removed under the balanced condition, then say whether the network is still balanced or not.



Watch Video Solution

75. In a balanced Wheatstone's network, galvanometer and cell are interchanged. Will the network be still balanced?



Watch Video Solution

76. In a balanced Wheatstone's network, the galvanometer resistance is increased by 20Ω . What happens to the balance of the network?



Watch Video Solution

77. At what point of a closed circuit, conservation of charge is valid?



Watch Video Solution

78. Name the instrument which can measure the emf of a cell and its internal resistance accurately.



Watch Video Solution

79. Name the physical quantity which gives the rate of flow of charge per unit area normal to the flow?



Watch Video Solution

80. Name any one device that works based on balanced condition of the Wheatstone's bridge or network.



Watch Video Solution

81. What will be the resistance of a semiconductor near absolute zero.



Watch Video Solution

82. What will be the resistance of a conductor near absolute zero?



Watch Video Solution

83. A resistor draws energy from a battery.

Where does this energy come from?



Watch Video Solution

84. What are semiconductors?



Watch Video Solution

85. What is meant by electrical grounding or earthing?



[Watch Video Solution](#)

86. What is Super conductivity?



[Watch Video Solution](#)

Two Mark Questions And Answers

1. Mention any two effects of current.



[Watch Video Solution](#)

2. Mention any two factors on which the internal resistance of the cell depends.



Watch Video Solution

3. Mention the unit of current density. Say whether current density is a scalar or a vector physical quantity.



Watch Video Solution

4. Write the dimensional formula for voltage



[Watch Video Solution](#)

5. Write the dimensional formula for resistivity.



[Watch Video Solution](#)

6. State Kirchhoff's laws of Electrical network.



[Watch Video Solution](#)

7. P, Q, S, R are four resistances arranged in a cyclic order in a Wheatstone's network. Under a balanced condition, what will be the potential difference between the junction of P and Q and R and S?



[Watch Video Solution](#)

8. What are electrical conductors? Give an example.



Watch Video Solution

9. What are insulators? Give an example.



Watch Video Solution

10. Two bulbs $110\text{ V} / 10\text{ W}$ and $110\text{ V} / 40\text{ W}$ are connected in series and across a 110 V . Which

of these will glow brighter? Explain why.



Watch Video Solution

11. Two heaters rated $220\text{ V} / 1\text{ kW}$ and $220\text{ V} / 3\text{ kW}$ are connected in parallel across a 220V source. Which of these will heat up faster? Explain why.



Watch Video Solution

12. If $E_1, E_2, E_3 \dots E_n$ represent emfs of a number of cells of internal resistances $r_1, r_2, \dots r_n$ then mention their equivalent emf and internal resistance when these are connected in series.




Watch Video Solution

13. If a number of cells are connected in parallel then write their equivalent emf and internal resistance.



 Watch Video Solution

14. In the network shown below, find I.

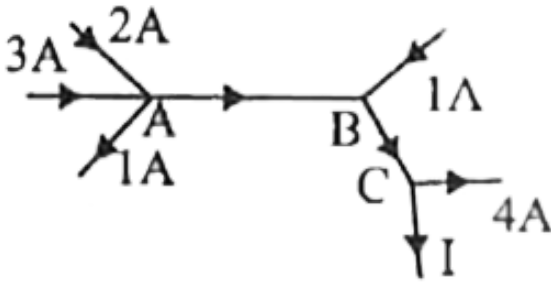

 Watch Video Solution

15. What is a potentiometer?

 Watch Video Solution

16. Give the formula to determine internal resistance of a cell using a potentiometer.



Watch Video Solution

17. How does the emf of a cell depend on the balancing length obtained in a potentiometer? Give the expression for ratio of emfs in terms of balancing lengths.



Watch Video Solution

18. Give the expression for power wasted in connecting wires.



Watch Video Solution

19. Give any two practical limitations of Ohm's law.



Watch Video Solution

Three Mark Questions And Answers

1. A uniform wire of resistance 9Ω is bent to form an equilateral triangle. What is the effective resistance between any two corners of the triangle.



[Watch Video Solution](#)

2. State and explain ohm's law



[Watch Video Solution](#)

3. Define temperature coefficient of resistance of a conductor. Give the expression for temperature coefficient.



Watch Video Solution

4. Derive the expression for current in a simple circuit based on Ohm's law.



Watch Video Solution

5. If 10Ω is unplugged from a standard resistance box and $33\frac{1}{3}$ cm is the balancing length obtained in the metre bridge, then calculate the resistance of the wire.



[Watch Video Solution](#)

6. Four resistors of resistances 2Ω , 4Ω , 6Ω and 2Ω are connected in a cyclic order of a Wheatstone's network. What resistance

should be connected with 2Ω in the arm AD so as to balance the network?



Watch Video Solution

7. Four resistors 4Ω , 8Ω , 18Ω and 6Ω are connected in a cyclic order to form a Wheatstone's network. How and what value of resistance should be connected in the 18Ω branch to balance the network?



Watch Video Solution

8. Write a note on Wheatstone's network.



[View Text Solution](#)

9. If two parallel resistors P and R of Wheatstone's network, are short circuited, then find the equivalent resistance of the circuit, when $G = S = Q = 10\Omega$.



[Watch Video Solution](#)

10. Show that $j = \sigma E$ where symbols have their usual meanings.



[Watch Video Solution](#)

11. Distinguish between Current and Current density.



[Watch Video Solution](#)

Five Mark Questions And Answers

1. Derive an expression for electrical conductivity.



Watch Video Solution

2. State the laws of resistance of a conductor. Define specific resistance of material of a conductor. Mention the SI unit of specific resistance.



Watch Video Solution

3. Write a note on the variation of resistance of a metallic conductor with temperature.



[Watch Video Solution](#)

4. Obtain an expression for equivalent resistance of two resistors connected in a series combination.



[Watch Video Solution](#)

5. Obtain an expression for equivalent resistance of two resistors connected in parallel.



[Watch Video Solution](#)


6. Obtain an expression for the equivalent emf and internal resistance of two cells connected in parallel.



[Watch Video Solution](#)

Numerical Problems And Answers

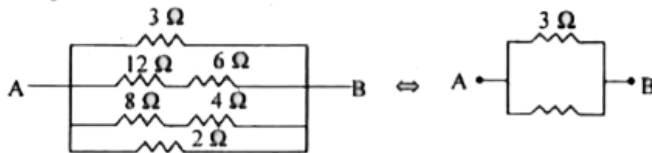
1. In the given circuit, calculate the effective resistance between A and B.



[Watch Video Solution](#)


2. In the given circuit, calculate the current through the circuit when connected with $12V$

supply.

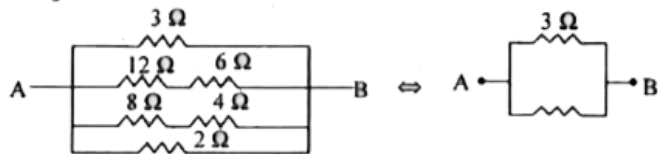

 [Watch Video Solution](#)

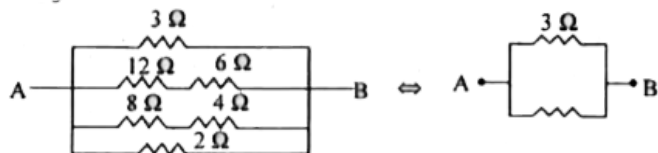3. In the given circuit, calculate the current through $3\ \Omega$ resistor, when circuit is connected to 12V battery.




 [Watch Video Solution](#)

4. A battery of internal resistance 3Ω is connected to 20Ω resistor and the potential difference across the resistor is 10V . If another resistor 30Ω is connected in series with the first resistor and battery is again connected to the combination, then calculate the e.m.f and terminal potential difference across the combination..




Watch Video Solution

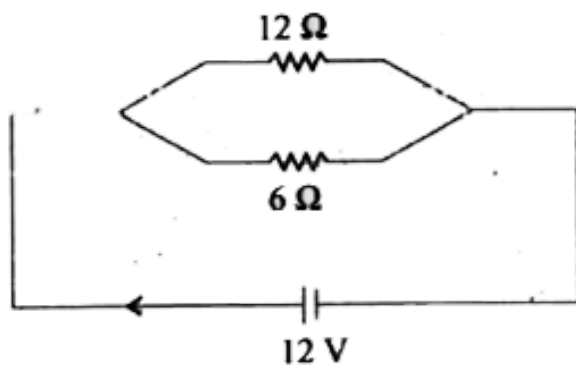5. A network of resistors is connected to a 12V battery as shown in the figure. Calculate the equivalent resistance of the network.



[Watch Video Solution](#)

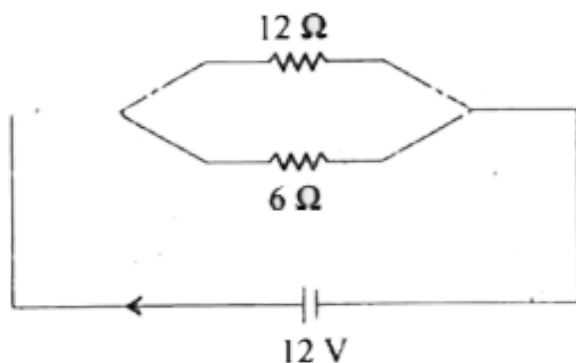6. A network of resistors is connected to a 12V battery as shown in the figure. Obtain current in 12Ω and 6Ω resistors.



[Watch Video Solution](#)

7. Two cells of emf 2V and 4V and internal resistance 1Ω and 2Ω respectively are connected in parallel so as to send the current in the same direction through an external resistance of 10Ω . Find the potential difference across 10Ω resistor.



Watch Video Solution

8. Which two resistors are connected in series with a cell of emf 2V and negligible internal

resistance, a current of $(2/5)\text{A}$ flows in the circuit. When the resistances are in parallel, the main current is $(5/3)\text{A}$. Calculate the resistances.



[Watch Video Solution](#)

9. Two resistors of resistances 2Ω and 4Ω are connected in parallel. Two more resistors 3Ω and 6Ω are also connected in parallel. These two combinations are in series with a battery

of emf 5 V and internal resistance 0.7Ω .

Calculate current through the 6Ω resistor.



[Watch Video Solution](#)

10. Three equal resistors connected in series across a source of emf of negligible internal resistance together dissipate 10 W of power.

What would be the power dissipated if the resistors are connected in parallel across the same source of e.m.f.



[Watch Video Solution](#)

11. A copper wire has 3×10^{22} free electrons in 0.021m length. The drift velocity of electrons is found to be $2 \times 10^{-5}\text{ms}^{-1}$.

How large a current will flow through the wire?



Watch Video Solution

12. A copper wire has 3×10^{22} free electrons in 0.021 m length. The drift velocity of electrons is found to be $2 \times 10^{-5}\text{ms}^{-1}$.

How many electrons would pass through a given cross-section of the wire in one second?



[Watch Video Solution](#)

13. A cube of side $0.05m$ of a material of conductor is drawn into a wire of thickness $0.20mm$. If the specific resistance of the wire is $10^{-6}\Omega m$ then calculate the resistance of the wire.



[Watch Video Solution](#)

14. If the number density of electrons in a conductor is 3×10^{28} and thickness of the conductor is 5 mm, then calculate the current in that conductor for a drift velocity of $2 \times 10^{-4} \text{ms}^{-1}$. If the voltage applied is 500V, then calculate relaxation time. Given specific charge of electron = $1.76 \times 10^{11} \text{ C kg}^{-1}$, length of the conductor = 10 m



Watch Video Solution

15. Two resistors 10Ω and 25Ω are connected in series and the combination is connected across a 25 V source of negligible internal resistance. A voltmeter of resistance 25Ω is connected across the 10Ω resistor. Find the reading in the voltmeter. If another voltmeter of a very large resistance replaces the voltmeter, then find the reading of voltmeter.



Watch Video Solution

16. Four resistors of resistances 2Ω , 1Ω , 3Ω , 4Ω are arranged in a cyclic order to form a Wheatstone's network ABCD. The junctions B and D are connected to a galvanometer of resistance 2Ω . A current of 0.1 A enters the junction 'A'. Calculate the current in the galvanometer.



Watch Video Solution

17. ABCD forms the four arms of a Wheatstone's network. The arms AB, BC, CD, DA are of 10Ω , 15Ω , 25Ω and 20Ω respectively. The junctions B and D are connected to the ends of galvanometer of resistance 25Ω . If the source voltage is $5V$, $r = 0$, then calculate the current in the galvanometer. Assume the branch currents across AB, BC, CD, DA and BD as i_1 , i_3 , $-i_4$, $-i_2$, and i_g respectively.



[Watch Video Solution](#)

18. A battery of emf $10V$ and internal resistance 3Ω is connected to a resistor. If the current in the circuit is $0.5A$, what is the resistance of the resistor? What is the terminal voltage of the battery when the circuit is closed?



Watch Video Solution

19. Three resistors 2Ω , 4Ω and 5Ω are connected in parallel. What is the total resistance of the combination?



[Watch Video Solution](#)

20. Three resistors 2Ω , 4Ω and 5Ω are connected in parallel. If the combination is connected to a battery of emf $20V$ and negligible internal resistance, determine the current through each resistor and the total current drawn from the battery.



[Watch Video Solution](#)

21. A negligibly small current is passed through a wire of length 15m, uniform cross - section $6.0 \times 10^{-7} m^2$ and its resistance is measured to be 5.0Ω . What is the resistivity of the material at the temperature of the experiment?



[Watch Video Solution](#)

22. A heating element using nichrome connected to a 230V supply draws an initial

current of 3.2A which settles after a few seconds to a steady value of 2.8A. What is the steady temperature of the heating -element, if the room temperature is 27.0°C ? Temperature coefficient of resistance of nichrome averaged over the temperature range involved is $1.70 \times 10^{-4}^{\circ}\text{C}^{-1}$.



[Watch Video Solution](#)

23. The number density of free electrons in a copper conductor is estimated as

$8.5 \times 10^{28} m^{-3}$. How long does an electron take to drift from one end of a wire 3.0m long to its other end? The area of cross-section of the wire is $2.0 \times 10^{-6} m^2$ and it is carrying a current of 3.0A.



[Watch Video Solution](#)

24. The earth's surface has-a negative surface charge density of $10^{-9} Cm^{-2}$. The potential difference of 400kV between the top of the atmosphere and the surface results in a

current of only 1800A over the entire globe. If there were no mechanism of sustaining atmospheric electric field, how much time would be required to neutralize the earth's surface charge? Take radius of earth $= 6.37 \times 10^6$ m.



Watch Video Solution

25. Six lead - acid type of secondary cells each of emf 2.0V and internal resistance 0.015Ω are joined in series to provide supply to a

resistance of 8.5Ω . What is the current drawn from the supply and its terminal voltage?



[Watch Video Solution](#)

26. A secondary cell after long use has an emf of 1.9V and large internal resistance of $380\ \Omega$.


What maximum current can be drawn from the cell? Could the cell drive the starting motor of a car?



[Watch Video Solution](#)

27. The figure shows a potentiometer circuit for comparison of two resistances. The balance point with a standard resistor $R = 10.0\Omega$ is found to be 58.3cm, while that the unknown resistance 'X' is 68.5 cm. Determine the value of x. What might you do if you failed to find a balance point with the

given cell of emf ε ?

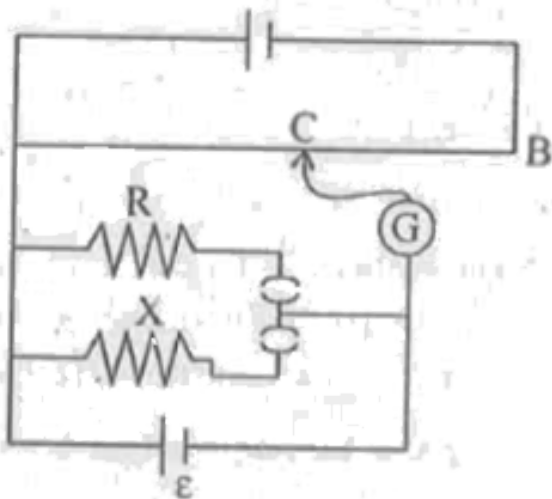

[Watch Video Solution](#)

28. A battery of internal resistance 3Ω is connected to 20Ω resistor and the potential difference across the resistor is 10V. If another


resistor 30Ω is connected in series with the first resistor and battery is again connected to the combination, then calculate the e.m.f and terminal potential difference across the combination..



[Watch Video Solution](#)

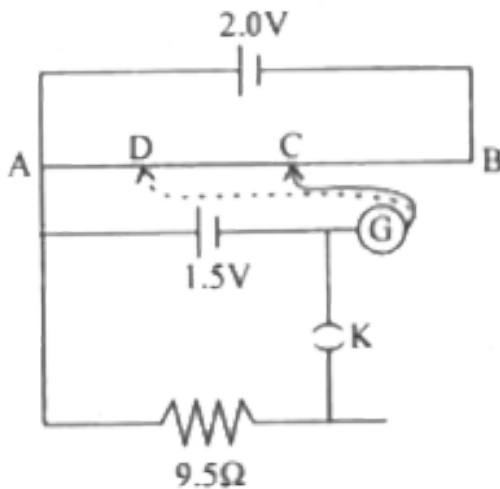29. The figure shows a 2.0V potentiometer used for the determination of internal resistance of a 1.5V cell. The balance point of the cell in open circuit is 76.3 cm. When a

resistor of 9.5Ω is used in the external circuit of the cell, the balance point shifts to 64.8 cm length of the potentiometer wire. Determine the internal resistance of the cell.



[Watch Video Solution](#)