



PHYSICS

BOOKS - VGS BRILLIANT PHYSICS (TELUGU ENGLISH)

ELECTRIC CURRENT

Review Of Your Previous Knowledge

1. What do you mean by electric current ?



Watch Video Solution

2. What do you mean by electric current ?



Watch Video Solution

3. which type of charge (Positive or negative) flows through an electric wire when it is connected in an electric circuit ?



[View Text Solution](#)

4. Is there any evidence for the motion of charge in daily life situations ?



[View Text Solution](#)

Conceptual Understanding

1. Explain the lorentz - Drude theory.



[Watch Video Solution](#)

2. Explain the Lorentz - Drude theory.



Watch Video Solution

3. How does a battery work? Explain.



Watch Video Solution

4. Write the difference between potential difference and emf.



View Text Solution

5. What do you mean by electric shock? Explain how it takes place.



Watch Video Solution

6. Derive $R = \frac{\rho l}{A}$.



[View Text Solution](#)

7. Derive a formula that shows the relation between resistance length and area of cross section of a conductor.



[View Text Solution](#)

8. What is the relationship between length of a conductor and its resistance ? Write the experimental procedure to verify that relationship.



[Watch Video Solution](#)

9. State Kirchhoff's law for an electrical network. Using these laws deduce the conditions for balance in a wheatstone bridge.



Watch Video Solution

10. What is the of 1 KWH in joules ?



View Text Solution

11. What happens when this current (overloading) increases greatly to the household circuit ?



Watch Video Solution

12. Deduce the expression for the equivalent resistance of there resistor connected in series.

 [View Text Solution](#)

13. Derive $R = R_1 + R_2 + R_3$.

 [View Text Solution](#)

14. Explain the expression for the equivalent resistance of three resistors which are connected in series.\

 [Watch Video Solution](#)

15. The second end of a first resistor is connected to first end of second resistor. Then how are the resistors connected ? Derive the for the resultant resistance of this connection.

 [Watch Video Solution](#)

16. Derive an expression for the effective resistance when three resistors are connected in (i) series (ii) parallel.



[Watch Video Solution](#)

17. Derive $\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$. (Resistors in parallel)



[Watch Video Solution](#)

18. Derive an expression for the effective resistance when three resistors are connected in (i) series (ii) parallel.



[Watch Video Solution](#)

19. Derive an expression for the effective resistance when three resistors are connected in (i) series (ii) parallel.



[Watch Video Solution](#)

20. Silver is a better conductor of electricity than copper. Why do we use copper wire for conduction of electricity ?



[View Text Solution](#)

21. Two bulbs have ratings 100 W, 220 V and 60 W, 220 V. Which one has the greater resistance ?



[View Text Solution](#)

22. Why don't we use series arrangement of electrical appliances like bulb, television, fan and others in domestic circuits ?



[View Text Solution](#)

23. A wire of length 1 m and radius 0.1 mn has a resistance of 100Ω .

Find the resistivity of the material.



[Watch Video Solution](#)

24. Express the units ohm in terms in terms of volt and ampere.



[Watch Video Solution](#)

25. What is a conductor of electricity ?



[View Text Solution](#)

26. What is non-conductor ?



[View Text Solution](#)

27. Define potential difference and give an expression to it.

 [Watch Video Solution](#)

28. State Ohm's law.

 [View Text Solution](#)

29. What are the limitations of Ohm's law ?

 [Watch Video Solution](#)

30. What is resistor ?

 [View Text Solution](#)

31. Define electric circuit.



View Text Solution

32. State Kirchhoff's Junction Law.



View Text Solution

33. State Kirchhoff's Loop law.



View Text Solution

34. Define electric power.



Watch Video Solution

35. What do you say that two or more resistance are conneted in series ?



Watch Video Solution

36. When do you say that two or more resistors are connected in series ?



View Text Solution

37. When do you say that two or more resistors are connected in parallel?



View Text Solution

38. What is lattice ?

 [Watch Video Solution](#)

39. What is the drift speed of electrons ?

 [Watch Video Solution](#)

40. Is the voltmeter connected in series or parallel in circuit ? Why ?

 [Watch Video Solution](#)

41. State the use of Ammeter. How to connect the Ammeter in electric circuit ?

 [Watch Video Solution](#)

42. The home appliance like Fridge ,T.V, Computer are connected in series or parallel ? Why ?



Watch Video Solution

43. Why are copper wires used as connecting wires ?



View Text Solution

44. Name two special characteristics of fuse wire.



Watch Video Solution

45. Name two special characteristics of heating coil.



View Text Solution

46. What is Resistance ? What are the SI Units of Resistance ?



View Text Solution

47. When a potential difference 30V is applied across a resistors, it draws a current of 3A. If 20V is applied across the same resistor, what will be the current ?



Watch Video Solution

48. Is Ohm's law universally applicable for all conducting elements? If not, give examples of elements which do not obey Ohm's law.



Watch Video Solution

49. Give reasons for using lead in making fuses.

 [View Text Solution](#)

50. Define electric current and give an expression to it.

 [View Text Solution](#)

51. What is drift speed ?

 [View Text Solution](#)

52. Define emf.

 [View Text Solution](#)

53. What are the factors affecting the resistance of a material ?

 [Watch Video Solution](#)

54. Calculate the drift speed of electrons in copper wire carrying a current of 1A and cross sectional area $10^{-6}m^2$.



View Text Solution

55. How can we decide the direction of electric current in a conductor ?



View Text Solution

56. A student says "Potential difference and emf are same. Justify your answer.



View Text Solution

57. Define Ohmic and non-ohmic conductors and give two examples each of them.



Watch Video Solution

58. Derive an expression to find drift velocity of electrons.



Watch Video Solution

59. Derive $V_d = \frac{1}{nqA}$.



Watch Video Solution

60. Derive an expression to find the work done by the electric force to move free charges in specified directions.



Watch Video Solution

61. Derive an expression for the electric potential due to a point charge.



Watch Video Solution

62. Derive an expression to measure of a battery.



Watch Video Solution

63. How do you appreciate a multimeter ?



Watch Video Solution

64. Deduce an expression to measure electric power.



View Text Solution

65. Derive $P = I^2 R$.



[View Text Solution](#)

66. Find electric current draw (figure) from the battery of emf 12V.



[View Text Solution](#)

Application To Daily Life Concern To Biodiversity

1. How can you appreciate the role of a small fuse in house wiring circuit in preventing damage to various electrical appliance connected in the circuit ?



[Watch Video Solution](#)

2. We can save the household wiring and devices by using fuses.

Write any four points by appreciating the role of fuse.

 [Watch Video Solution](#)

3. Observe the circuit and answer the questions given below.

Are resistors C and D in series ?



 [View Text Solution](#)

4. Observe the circuit and answer the questions given below.

Are resistors A and B in series ?



 [View Text Solution](#)

5. Observe the circuit and answer the questions given below.

Is the battery in series with any resistors ?



View Text Solution

6. What is the potential drop across the resistors C ?



View Text Solution

7. Observe the circuit and answer the questions given below.

What is the total emf in the circuit if the potential drop across resistor A is 6V ?



View Text Solution

8. A house has three tube lights, two fans and a Television. Each tube light draws 40W. The fan draws 80W and the Television draws 60W. On the average all the tube lights are kept on for five hours, two fans for 12 hours and the television for five hours every day. Find the cost of electric energy used in 30 days at the of Rs. 3.00 per KWH.

 **Watch Video Solution**

9. Which device is used to measure the current in your pump sets ?

 **Watch Video Solution**

10. The current resistance of bodies of Karthik and Hemanth are $10,000\Omega$ and $1,00,000\Omega$ respectively. If they touch a current wire with 240 V, who may experience more effect by an electrical shock ?

 **Watch Video Solution**

11. What is the use of a multimeter ?



Watch Video Solution

12. A bulb is marked 60 W and 120 V. How much current does pass through it ?



Watch Video Solution

13. Which instrument is used to measure electric current ?



View Text Solution

14. What are uses of semi conductors ?



Watch Video Solution

15. Which instrument is used to measure potential difference or emf ?



[View Text Solution](#)

16. Shekhar was observed a bulb and asked some questions to you.

Those are

What is the material of the filament ?



[View Text Solution](#)

17. Shekhar was observed a bulb and asked some questions to you.

Those are

Why does it used as a filament ?



[View Text Solution](#)

18. 12 V, 9 V and 12 V bulbs are connected in series. What is the potential difference of their combination ?



[View Text Solution](#)

19. 

What is the value of 'x' ?



[View Text Solution](#)

20. Jhansi has been using the given devices in her house. Calculate the current bill for one month @ 5/ – per unit.

1. 100 W TV for 12 hrs.

2. 80 W two fans for 10 hrs

3. 11 W four LED bulbs for 12 hrs.



[View Text Solution](#)

21. Find the resistance of a bulb, on which 60W and 120 V is marked.



[View Text Solution](#)

22. Two wires have equal area of cross section. One is copper and other is Aluminium have the same resistance. Find Which one is longer.



[View Text Solution](#)

23. Find which has greater resistance, 1 KW heater or a 100 W tungsten bulb, both marked for 230 V.



[View Text Solution](#)

24. A circuit is shown in the picture. The current passing through A is



What is the potential difference between A and B ?



[View Text Solution](#)

25. A circuit is shown in the picture. The current passing through A is



What is the equivalent resistance between A and B ?



[View Text Solution](#)

26. What do you mean by short circuit ?



[Watch Video Solution](#)

27. A household uses the following electric appliances.

- i. Refrigerator of rating 400 W each for ten hours each day.
- ii. Two electric fans of rating 80 W each for 12 hours each day.
- iii. Six electric tubes of rating 18 W each for 6 hours each day.

Calculate the electric bill of the household in a month if the cost per unit electric energy is Rs 3.00.



View Text Solution

28. From the adjacent figure

- i. Find the potential at D.
- ii. Find the current passes through AD, DB and DC.



View Text Solution

29. 

Calculate the equivalent resistance.



[View Text Solution](#)

30. 

Calculate the equivalent resistance.



[View Text Solution](#)

31. 

Calculate the equivalent resistance.



[View Text Solution](#)

32. How do you connect the resistance of 6Ω , 3Ω and 1Ω to get $R_{eff} = 3\Omega$.



[Watch Video Solution](#)

33. some metals are given

Classify them into insulators and semi conductors.



[View Text Solution](#)

34. some metals are given

What material do you observe in (i) a bulb, (ii) a soldering unit, (iii) an iron box, (iv) a diode.



[View Text Solution](#)

35. some metals are given

To protect from an electrical shock which material is generally used to cover over a tool ?



View Text Solution

36. some metals are given

Which metals did you observe in your house electrical is wiring ?



View Text Solution

37. 0.5 amp current is passing through the 3 bulbs with 4Ω , 12Ω and 8Ω resistances and they are connected in series ? Find the voltage of the combination.



[View Text Solution](#)

Fill In The Blanks

1. The kilowatt hour is the of



[Watch Video Solution](#)

2. A thick wire has Resistance than a thin wire.



[Watch Video Solution](#)

3. A unknown circuit drwas a current of 2 A from a 12 V battery. Its equilatent resitance is



[Watch Video Solution](#)

4. The SI unit of potential difference is



Watch Video Solution

5. The SI unit of currents is



Watch Video Solution

6. Three resistors of values 2Ω , 4Ω , 6Ω are connected in series. The equivalent resistance of combination of resistors is



Watch Video Solution

7. Three resistors of values 2Ω , 4Ω , 6Ω are connected in parallel. The equivalent resistance of combination of resistors is



Watch Video Solution

8. The power delivered by a battery of emf, 10 V is 10 W. Then current delivered by the battery is



Watch Video Solution

Multiple Choice Questions

1. A uniform wire of resistance 50Ω is cut into five equal parts. These parts are now connected in parallel in parallel. Then equivalent resistance of the combination is

A. 2Ω

B. 12Ω

C. 250Ω

D. 6250Ω

Answer: A



View Text Solution

2. A charge is moved from a point A to a point B. The work done to move unit charge during this process is called

- A. potential at A
- B. potential at B
- C. potential difference between A and B
- D. current from A to B

Answer: C



Watch Video Solution

3. joule/coulomb is the same as

A. 1 - watt

B. 1 - volt

C. 1 - ampere

D. 1 - ohm

Answer: B



Watch Video Solution

4. The current in the wire depends

A. only on the potential difference applied

B. only on the resistance of the wire

C. on potential difference and resistance

D. none of them

Answer: C



[Watch Video Solution](#)

5. A. In series connection, the same current flows through each element.

B. In parallel connection, the same potential difference gets applied across each element.

Which is/are correct ?

A. both a and b are correct

B. a is correct but b is wrong

C. a is wrong but b is correct

D. both a and b are wrong

Answer: A



[Watch Video Solution](#)

6. A. In series connection, the same current flows through each element.

B. In parallel connection, the same potential difference gets applied across each element.

Which is/are correct ?

A. both a and b are correct

B. a is correct but b is wrong

C. a is wrong but b is correct

D. both a and b are wrong

Answer: A



Watch Video Solution

Try These

1. Write an activity to show the relation between temperature and Resistance.



View Text Solution

2. Why do we use fuse in household circuit ?



Watch Video Solution

3. Suppose that you have three resistance each of value 30Ω . How many resistor can you obtain by various combinations of these three resistors ? Draw diagrams in support of your predictions.



Watch Video Solution

4. Draw a circuit diagram for a circuit in which two resistors A and B are connected in series with a battery and voltmeter is connected to measure the potential difference across the resistor A.



[Watch Video Solution](#)

5. In the below figure, the potential at A is when the potential at B is zero.



[View Text Solution](#)

6. If the resistance of your body is 100000Ω , what would be the current that flow in your body when you touch the terminals of a 12V battery ?



[Watch Video Solution](#)

7. A uniform wire of resistance 100Ω is melted and recast into of length double that of the origina. What would be the resistance of the wire formed ?



[Watch Video Solution](#)

Think And Discuss

1. What do you mean by short circuit ?



[Watch Video Solution](#)

2. Why does a short circuit damage electric wiring and devices connected to it ?



[Watch Video Solution](#)

Questions Given In The Lesson 1 Mark Questions

1. Does motion of charge always lead to electric current ?

 [Watch Video Solution](#)

2. Take a bulb, a battery, a switch and few insulated copper wires to the terminals of the battery through the bulb and switch. Now switch on the circuit and observe the bulb. What do you notice ?

 [View Text Solution](#)

3. Can you predict the reason for the bulb not glowing in situations 2 and 3 ?

 [View Text Solution](#)

4. Why do all materials not act as conductors ?



Watch Video Solution

5. How does a conductor transfer energy from source to bulb ?



Watch Video Solution

6. What happens to the motions of electrons when the ends of the conductor are connected to the battery ?



Watch Video Solution

7. Why do electrons move in specified direction ?



Watch Video Solution

8. In which direction do the electrons move ?



Watch Video Solution

9. Do the electrons accelerate continuously ?



Watch Video Solution

10. Do they move with a constant speed ?



Watch Video Solution

11. How can we decide the direction of electric current ?



Watch Video Solution

12. How can we measure electric current ?



View Text Solution

13. Where do the electrons get energy for their motion from ?



View Text Solution

14. Can you find the work done by the electric force ?



View Text Solution

15. What is the work done by the electric force on unit charge ?



View Text Solution

16. what is the direction of electric current in terms of potential difference ?



View Text Solution

17. Do positive charges move in a conductor ? Can you give an example of this ?



View Text Solution

18. How does a battery maintain a constant potential difference between its terminals ?



Watch Video Solution

19. Why does the battery discharge when its positive and negative terminals are connected through a conductor ?



Watch Video Solution

20. What happens when the battery is conneted in a circuit ?



View Text Solution

21. How can we measure potential difference or emf ?



View Text Solution

22. Is there any relation between emf of battery and drift speed of electrons in the conductor connected to a battery ?



Watch Video Solution

23. Can you guess the reason wh the ratio of V and I in case of LED is not constant ?



Watch Video Solution

24. Do all materials obey Ohm's law ?



Watch Video Solution

25. What is resitance ?



Watch Video Solution

26. Is the value of resistance same for all materials ?



Watch Video Solution

27. Is there any application of Ohm's law in daily life ?



Watch Video Solution

28. What cause electric shock in the human body ?



Watch Video Solution

29. Do you know the voltage of mains that we use in our household circuits ?



Watch Video Solution

30. What happens to the resistance of a conductor if we increase its length ?



[View Text Solution](#)

31. Does the thickness of a conductor influence its resistance ?



[View Text Solution](#)

32. How are electric devices connected in circuits ?



[Watch Video Solution](#)

33. When bulbs are connected (resistors) in series, What do you notice ?



[Watch Video Solution](#)

34. What do you notice when bulbs (resotors) are connected in series to the current ?



Watch Video Solution

35. What do you mean by equivalent resistance resitance ?



Watch Video Solution

36. What happens when the one of the resistor in series breaks down ?



Watch Video Solution

37. Can you guess in what way household wiring has been done ?



Watch Video Solution

38. How much current is drawn from the battery if the resistors are connected in parallel ? Is it equal to individual currents drawn by resistors ?



Watch Video Solution

39. How could the sign convention be take ?



Watch Video Solution

40. You might have heard the sentences like "this month we have consumed 100 units of current". What does 'unit' mean ?



View Text Solution

41. A bulb is marked 60 W and 120 V. What do the values indicate ?



View Text Solution

42. A bulb is marked 60 W and 120 V. What do the values indicate ?



View Text Solution

43. What is the energy lost by the charge in 1 sec. ?



View Text Solution

44. What do you mean by overload ?



View Text Solution

45. Why does it (overloading) cause damage to electric appliances ?



View Text Solution

46. What happens when this current (overloading) increases greatly to the household circuit ?



Watch Video Solution

47. How can we prevent damage due to overloading ?



Watch Video Solution

Questions Given In The Lesson 2 Mark Questions

1. Why does a bulb glow immediately when we switch on ?



[View Text Solution](#)

2. Can we classify the materials based on Ohm's law ?



[Watch Video Solution](#)

3. What happens to our body if touch live wire of 240 V ?



[Watch Video Solution](#)

4. Why doesn't a bird get a shock when it stands on a high voltage wire ?



[View Text Solution](#)

1. Which one has free electrons ?



View Text Solution

2. Who proposed that conductors like metals a large number of the free electrons while the positive ions are fixed in their location ?



Watch Video Solution

3. What is the vauue of net charge moving along a conductor through any cross section, when the conductor is in open circuit ?



Watch Video Solution

4. Which are respsible for transfer of energy from battery to bulb ?



Watch Video Solution

5. What is called the ordered motion of electrons in a conductor ?



Watch Video Solution

6. Write a formula for electric current in the terms of charge (Q) and (t).



View Text Solution

7. What is the SI units of electric current ?



Watch Video Solution

8. What makes the electrons move in specific direction when the ends of the conductor are connected to the terminals of a battery ?



Watch Video Solution

9. Which physical quantit is measured in amperes ?



View Text Solution

10. How is the directions of electric field and moment of free electrons ?



View Text Solution

11. Write a formula for electric current in terms of drift speed of electrons.



Watch Video Solution

12. What is the magnitude of electric charge ?



View Text Solution

13. What is the drift speed of electrons ?



Watch Video Solution

14. Which apparatus do you use to measure current in your lab ?



Watch Video Solution

15. State the use of Ammeter. How to connect the Ammeter in electric circuit ?



Watch Video Solution

16. If F_e is force exerted by electric field on a free charge and ' l ' is distance moved by the free charge, what is work done by the electric force on a free charge ?



Watch Video Solution

17. What do you call the work done by the electric force on unit positive charge to move it ?



Watch Video Solution

18. What is the direction of electrons in a circuit ?



View Text Solution

19. What are the parts of battery ?

 [View Text Solution](#)

20. In battery, which one helps to move the ions in a specific direction ?

 [View Text Solution](#)

21. Match it.

- 1)Positively charged plate (a)anode
2)Negatively charged plate (b)*cathode*

 [View Text Solution](#)

22. On which factor the amount of charge accumulated on the plate depends in a battery ?

 [View Text Solution](#)

23. What do you call the work done by the chemical force to move unit positive charge from negative terminal to positive terminal of the battery ?



[Watch Video Solution](#)

24. emf of a battery $= \frac{W}{q}$, what is 'W' ?



[View Text Solution](#)

25. How can you measure potential difference or emf /



[Watch Video Solution](#)

26.

Potential difference \times Current : Electrical Power : : Power \times Time : ?

 [Watch Video Solution](#)

27. What is the law, $\frac{V}{I} = \text{constant}$ For a conductor ?

 [View Text Solution](#)

28. Which device do you use in lab to change electric current ?

 [Watch Video Solution](#)

29. The algebraic sum of the increases and decreases in P.D across various components of closed circuit loop must be

- a. one
- b. zero
- c. constant

 [Watch Video Solution](#)

30. Draw a graph to show the relation between current (I) and voltage (V) for conductors ?



[View Text Solution](#)

31. How is $\frac{V}{I}$ for semi conductors ?



[Watch Video Solution](#)

32. 

Which type of electrical device is used in the experiment ?



[View Text Solution](#)

33. What is SI units of resistance of a metal ?



[View Text Solution](#)



[Watch Video Solution](#)

34. A device passes 1 ampere current at 1 volt of potential difference.

What is the resistance of the device ?



[Watch Video Solution](#)

35. Do all materials obey Ohm's law ?



[Watch Video Solution](#)

36. Give example to ohmic material.



[Watch Video Solution](#)

37. What type of material LED ?





[View Text Solution](#)

38. According to Ohm's Law many types of materials are there ?



[View Text Solution](#)

39. For what materials Ohm's law is not applicable ?



[View Text Solution](#)

40. Which one obstructs the motion of electrons in a conductor ?



[Watch Video Solution](#)

41. What is the property of a conductor which is defined as the obstruction to the motion of the elections in a conductor ?





[Watch Video Solution](#)

42. How do we call the material which offers resistance ?



[View Text Solution](#)

43. What is the range of resistance of the human body, generally ?



[Watch Video Solution](#)

44. What will happen to resistance of a human body when current flow for a longer time ?



[Watch Video Solution](#)

45. What cause electric shock in the human body ?

- A. effect of current
- B. effect of potential difference
- C. effect of resistance of the body
- D. combined effect of a, b, c

Answer: d



Watch Video Solution

46. Which device do you use to measure current, voltage and resistance?



View Text Solution

47. Which of the following materials do you select to show that the resistance of a conductor depends on the material of the conductor?

1. Manganin wires of different lengths with the same cross section areas.
2. Manganin wires of equal lengths but different cross sectional areas.
3. Different copper, nichrome, manganin wires of the length and same cross sectional areas.



[Watch Video Solution](#)

48. What is the relation between resistance (R), resistivity(ρ), length(l) and area of cross section (A) of a conductor ?



[Watch Video Solution](#)

49. What is SI unit of resistivity ?



[Watch Video Solution](#)

50. What is conductivity ?



Watch Video Solution

51. Resistivity : ρ : ? : (σ)

Fill it by suitable word.



Watch Video Solution

52. A : Copper is used for making electric wires.

R : Metal with low resistivity behave as good conductors.

A. A and 'R' are correct and 'R' is correct explanation of 'A'

B. A and 'R' are correct but 'R' is not correct explanation of 'A'

C. A is correct but 'R' is incorrect

D. A is incorrect but 'R' is correct

Answer: a

 [Watch Video Solution](#)

53. Guess the material which is used in electrical devices and its resistivity and melting point are high.

 [Watch Video Solution](#)

54. What is the value of melting point of tungsten ?

 [View Text Solution](#)

55. What is the range of resistance of insulators ?

 [Watch Video Solution](#)

56. Give examples to Alloys.



[View Text Solution](#)

57. Name two heating elements.



[View Text Solution](#)

58. Material – $\rho(\Omega - m)$

$$A = 1.59 \times 10^{-8}$$

$$B = 4.60 \times 10^1$$

$$C = 1.00 \times 10^{13}$$

Which material is used integrated ciucuits ?



[Watch Video Solution](#)

59. 

V_1, V_2, V_3 are voltages, what is resultant voltage (V) ?



[View Text Solution](#)

60. If you connect three resistor R_1, R_2 and R_3 in series as shown in the figure, what is the resistance ?



[View Text Solution](#)

61. "The sum of individual resistance is equal to their equivalent resistance". How are resistors connected in the circuit ?



[View Text Solution](#)

62. How do household electrical appliances connect in circuit ?

 [Watch Video Solution](#)

63. Two resistors R_1 and R_2 are connected in parallel. What is equivalent resistance ?

 [Watch Video Solution](#)

64. How is the resistance of a combination when compared to the resistance of each resistor ?

 [View Text Solution](#)

65. Write the Kirchhoff's laws.

 [View Text Solution](#)

66. Which law states that there is no accumulation of electric charges at any junction in a circuit ?



Watch Video Solution

67. 

Find the resultant potential difference in the circuit ?



View Text Solution

68. Write a formula for electric power.



Watch Video Solution

69. $AC : P = VI :: DC : P = ?$



[Watch Video Solution](#)

70. How much resistance can be offered by a bulb, which is marked 60W and 120V ?



[Watch Video Solution](#)

71. What is a bigger unit of power ?



[View Text Solution](#)

72. We are using 'units's for measuring current. What does one unit equal ?



[View Text Solution](#)

73. How many Joules are equal to one kilo Watt Hour (1KWH) ?



View Text Solution

74. How can we prevent damage due to overloading ?



Watch Video Solution

75. 100W - 1 fan - 12 hours

9W - 5 LED bulbs - 10 hrs

Calculate power consumption.



Watch Video Solution

76. What are the units of household electrical energy ?



View Text Solution

77. Which of the following has high resistance ?

- A. thick wire
- B. thin wire
- C. length wire
- D. short wire

Answer: b and c



View Text Solution

78. Find the equivalent resistance of a device which draw 2A of current at 12V.



View Text Solution

79. Three resistors of values 2Ω , 4Ω and 6Ω are connected in series.

Find the equivalent resistance of combination.



[View Text Solution](#)

80. Three resistors of values 2Ω , 4Ω and 6Ω are connected in parallel. Find the equivalent resistance of combination.



[View Text Solution](#)

81. The power delivered by a battery of emf, 10 is 10W. Find the current delivered by the battery.



[View Text Solution](#)

82. A uniform wire of resistance 50Ω is cut into five equal parts. These parts now connected in parallel. Find the equivalent

resistance of the combination.



[View Text Solution](#)

83. A. In series connection, the same current flows through each element.

B. In parallel connection, the same potential difference gets applied across each element.

Which is/are correct ?



[Watch Video Solution](#)

Section II 1 Mark Questions

1. 

Find the quantity of current in the above circuit.



[View Text Solution](#)

2. 

Three resistance A, B and C are connected as shown in the figure. Each of them dissipates energy to a maximum of 18 W. Find the maximum current that can flow through the three resistors.



[View Text Solution](#)

3. What happens if we use a fuse made up of same wire which is used to make the electric circuit ?



[Watch Video Solution](#)

4. Draw the electric circuit with the help of a Battery, Voltmeter, Ammeter, Resistance and connecting wires.



[View Text Solution](#)

5. Write any two differences between ohmic and non - ohmic conductors.



View Text Solution

6. What happens, if the household electric appliance are connected in series ?



Watch Video Solution

Asking Questions And Making Hypothesis

1. Why do we consider tungsten as a suitable material for making the filament of a bulb ?



Watch Video Solution

2. Why do we consider tungsten as a suitable material for making the filament of a bulb ?



Watch Video Solution

3. Are the headlights of a car connected in series or Parallel ? Why ?



Watch Video Solution

4. Why should we connect electric appliances in parallel in a household circuit ? What happens If they are connected in series ?



Watch Video Solution

5. What happens to the free electrons when the conductor are connected to the battery ?

 [Watch Video Solution](#)

6. The direction of electric current (I) is opposite to flow of charge'. Guess the charge. Why ?

 [Watch Video Solution](#)

7. There is a force 'x' . Direction of 'x' is opposite to the direction of electrical force : predict x.

 [Watch Video Solution](#)

8. Predict the condition of a battery if $F_e = F_e$?

 [Watch Video Solution](#)

9. Predict the final outcome in the given experiment.



View Text Solution

10. What will happen if a bird touches both line and neutral wires of 240volts ?



Watch Video Solution

11. What will if the electrical home appliances are conneted in a series ? Is it suggestible for home ?



Watch Video Solution

12. Guess the reason for the given situation, not glowing of D, E, F.



View Text Solution

13. The equivalent resistance of three equal resistor is 1.5Ω . The resistance of a single resistor is more than 1.5Ω How would the resistors connected ? Guess without doing the sum.



Watch Video Solution

14. What will happen if a fuse contains a wire with high melting point ?



Watch Video Solution

15. Goutham was switched a circuit with a bulb, battery, a switch and wire wire. But it did not glow. Predict the reasons.



Watch Video Solution

16. What will happen if a uniform electric field is setup throughout the conductor ?



Watch Video Solution

17. Rithvik does not understand the concep 'drift speed'. To make understand the concept prepare some questions.



Watch Video Solution

18. In a lab activity to show that V/I is constant, it was noticed that V/I is not constant. Guess the reasons.

 [Watch Video Solution](#)

19. Akshay saw the specification of a bulb as 60 W and 120 V, on the surface of the bulb. She got many doubts in her mind. What would be those doubts ?

 [Watch Video Solution](#)

20. Sangeetha often confused the current and potential differences. Ravi explained the terms by asking some questions. What would be those questions ?

 [View Text Solution](#)

1. State Ohm's law. Suggest an experiment to verify it and explain the procedure.



Watch Video Solution

2. How do you prove experimentally the ratio V / I is a constant for a given conductor ?



Watch Video Solution

3. What are the material required to make a simple circuit ?



View Text Solution

4. In lab, how do you connect an ammeter to the circuit ?

 [Watch Video Solution](#)

5. How do you connect a volt meter to the circuit ?

 [View Text Solution](#)

6. What is the conclusion in the Ohm's law experiment ?

 [View Text Solution](#)

Communication Through Drawing Model Making

1. Draw the shape of V - I graph for a conductor.

 [Watch Video Solution](#)

2. Draw the shape of V - I graph for semi conductor.



Watch Video Solution

3. Draw the symbols of the following.

Battery



View Text Solution

4. Draw the symbols of the following.

Resistace



View Text Solution

5. Draw the symbols of the following.

Ammeter



[View Text Solution](#)

6. Draw the symbols of the following.

Voltmeter



[View Text Solution](#)

7. Draw the symbols of the following.

Key



[View Text Solution](#)

8. Draw the symbols of the following.

Rheostat



[View Text Solution](#)

9. Draw the symbol of a fuse.



[View Text Solution](#)

10. Draw the symbol of a resistor.



[View Text Solution](#)

11. Draw a simple circuit with an ammeter, a voltmeter, a resistors, a key and a battery.



[View Text Solution](#)

12. Draw a circuit diagram to verify the Ohm's Law.



Watch Video Solution

13. Draw V-I graph of Ohmic and non-ohmic conductors.



Watch Video Solution

14. Draw a circuit diagram with a cell, an electric bulb, an ammeter and plug key.



Watch Video Solution

15. 

Identify the wrongly connected device/s in the given figure.

[View Text Solution](#)

16. Draw a simple junction with I_1 , I_4 and I_5 (into the junction) and I_2 , $I(3)$ (leaving the junction).

[Watch Video Solution](#)

17. Draw a circuit as mentioned below

- i. Total number of resistance are 4. They are 5Ω , 2Ω , 4Ω and 6Ω
- ii. 5Ω and 6Ω are in parallel
- iii. 4Ω and 6Ω are in parallel
- iv. 5Ω and 2Ω are in series
- v. 2Ω and 4Ω are in series

[View Text Solution](#)

18. Draw a loop ACDBA as $-V_2 + I_2 R_1 - I_1 R_1 + V_1 = 0$.



[View Text Solution](#)

19. In an experiment to verify Ohm's Law from the values given below.

Draw a graph of 'I' versus 'V'. Show that the graph the graph conforms Ohm's Law and find the resistance of the resistor.



[View Text Solution](#)

20. Identify the defects in the circuit. Redraw it.



[View Text Solution](#)

21. R_1 , R_2 and R_3 resistors are connected in parallel in a circuit with a battery voltmeters and ammeters.

Draw the circuit for the given situation.



[View Text Solution](#)

22. Draw a parallel connection of the given devices.

1. Fan (4A)
2. Bulb (2A)
3. Fridge (8A)
4. TV (6A)
5. Fuse (fuse (20A)
6. Heater



[Watch Video Solution](#)

1. Is there any application of Ohm's Law in daily life ?



View Text Solution

2. Which one saves the electrical devices from overloading ?



Watch Video Solution

3. How do you appreciate a multimeter ?



Watch Video Solution

4. Write some of insulators and appreciate them.



View Text Solution

5. How do you appreciate the scientist Ohm for his contribution to electrical field ?



[Watch Video Solution](#)

Section Iii 2 Marks Questions

1. Observe the graph of potential difference (V) drawn between two ends of a conductor and current (I) passing through it. Answer the following questions :

Which law is used to explain the graph ? State it.



[View Text Solution](#)

2. Observe the graph of potential difference (V) drawn between two ends of a conductor and current (I) passing through it. Answer the following questions :

What is the resistance of the conductor ?



 [View Text Solution](#)

3. Draw the experimental set-up to verify V/I is constant for a conductor.

 [Watch Video Solution](#)

4. A house has 3 tube-lights of 20 watts each. On the all the tube-light are kept on for five hours. Find the energy consumed in 30 days.





Watch Video Solution

Experimentation And Field Investigation

1. What are the material required to show that the V/I is a constant for a conductor ?



Watch Video Solution

2. Describe the activity with the help of diagram to establish the relationship between Current (I) flowing in a conductor and potential difference (V) maintained across its ends.



Watch Video Solution

3. Show that the semi conductor do not obey Ohm's Law.



Watch Video Solution

Information Skills And Projects

1. Take a battery and measure the potential difference. Make a circuit and measure the potential difference when the battery is connected in the circuit. Is there any difference in potential difference of battery?



Watch Video Solution

2. Measure the resistance of a bulb (filament) in open circuit with a multi-meter. Make a circuit with elements such as bulb, battery of 12V and key in series. Close the key. Then again measure the resistance of the same bulb (filament) for every 30 seconds. Record the observation in a proper table. What can you conclude from the above results?

 [Watch Video Solution](#)

3. $P = V^2 / R$ is given. What the relation between 'P' and 'V' , P and R ?

 [Watch Video Solution](#)

4. i. Water vapour, ii. Silicon, iii. Zinc, iv. Germanium.

Which of the above substances obey the Ohm's law ?

 [Watch Video Solution](#)

5. i. Water vapour, ii. Silicon, iii. Zinc, iv. Germanium.

For which of the above substance / s the V / I graph is non-linear ?

 [Watch Video Solution](#)

6. 

When does occur loss of muscle control ?



[View Text Solution](#)

7. 

What is the effect if a body with $24,000\Omega$ touches an electrical wire with 240 volts ?



[View Text Solution](#)

8. $R = \frac{\rho l}{A}$

What is ρ ?



[View Text Solution](#)

9. $R = \frac{\rho l}{A}$

On what does the resistance of a metal depend ?



[View Text Solution](#)

10. 

Where do you place aluminium in the above table ?



[View Text Solution](#)

11. 

What is the difference between germanium and glass ?



[View Text Solution](#)

12. From the above table,

Which one does pass the electricity ?



View Text Solution

13. From the above table,

which one does not pass the electricity ?



View Text Solution

14. From the above table,

Which substance can use to make insulators ?



View Text Solution

15. From the above table,

Which material has high conductivity ?



[View Text Solution](#)

16. Resistivity of some materials are given below. (Units = $\Omega - m$)



Write any two good solid insulators.



[View Text Solution](#)

17. Resistivity of some materials are given below. (Units = $\Omega - m$)



Write any two good solid conductors.



[View Text Solution](#)

18. Resistivity of some materials are given below.(Units = $\Omega - m$)



Which one has the low melting point among the given materials ?



[View Text Solution](#)

19. Resistivity of some materials are given below.(Units = $\Omega - m$)



Silver and gold are not used in the household electrical wiring. Why ?



[View Text Solution](#)

Section Iv 4 Marks Questions

1. State Kirchoff Loop Law and explain.



[Watch Video Solution](#)

 Watch Video Solution

2. State Kirchoff Loop Law and explain.



Watch Video Solution

3. 12 V battery is connected in a circuit and to this 4W, 12W, resistors are connected in circuit from this information and the current in the circuit.



View Text Solution

4. A house has four tube-lights, three fans and a television. Each tube-light draws 40 W. The fan draws 80 w and the television draws 100 W. On an average, all the tube-lights are kept on for 5 hours, all fans for 12 hour and the television for 6 hours everyday. Find the

cost of electric energy used in 30 days at the rate of Rs. 3.00 per KWH.



[Watch Video Solution](#)

5. Observe the given circuit.

R_1 and R_2 are two resistors and $R_1 = R_2 = 4\Omega$. Emf of the battery E is 10 V.

Answer the following questions.

How are the resistance R_1 and R_2 connected in the circuit ?



[View Text Solution](#)

6. Observe the given circuit.

R_1 and R_2 are two resistors and $R_1 = R_2 = 4\Omega$. Emf of the battery E is 10 V.

Answer the following questions.

What is the potential difference of the circuit ?



[View Text Solution](#)

7. Observe the given circuit.

R_1 and R_2 are two resistors and $R_1 = R_2 = 4\Omega$. Emf of the battery E is 10 V.

Answer the following questions.

What is the effective resistance of the circuit ?



[View Text Solution](#)

8. Observe the given circuit.

R_1 and R_2 are two resistors and $R_1 = R_2 = 4\Omega$. Emf of the

battery E is 10 V.

Answer the following questions.

What is the total current drawn from the battery ?



[View Text Solution](#)

9. 

Observe the above diagram and answer the following.

Are all the resistors connected in parallel or series ?



[View Text Solution](#)

10. 

Observe the above diagram and answer the following.

What is the equivalent resistance of the combination of three resistors ?



[View Text Solution](#)

11. 

Observe the above diagram and answer the following.

In this system, which physical quantity is constant ?



[View Text Solution](#)

12. 

Observe the above diagram and answer the following.

If $R_1 = 2\Omega$, $R_2 = 3\Omega$, $R_3 = 4\Omega$, find equivalent resistance.



[View Text Solution](#)

13. What is the relationship between length of a conductor and its resistance ? Write the experimental procedure to verify that relationship.



[Watch Video Solution](#)

14. What are factors affecting the resistance of an electric conductor ? Explain any two factors.



[View Text Solution](#)

15. What is the relationship between length of a conductor and its resistance ? Write the experimental procedure to verify that relationship.



[Watch Video Solution](#)

16. In a circuit ,60V battery, three resistance $R_1 = 10\Omega$ $R_2 = 20\Omega$ and $R_3 = x\Omega$ are connected in series. If 1

ampere current flows in the circuit, find the resistance in R_3 by using Kirchhoffs loop law.



Watch Video Solution