



# PHYSICS

## BOOKS - MTG GUIDE

### CURRENT ELECTRICITY

#### Illustration Solution

1. The number density of conduction electrons in a copper conductor is  $8.5 \times 10^{28} m^{-3}$ . How long does an electron take to drift from one

end of a wire 3.0 m long to its other end ? The area of cross-section of the wire is  $2.0 \times 10^{-6} m^2$  and it is carrying a current of 3.0 A.



[Watch Video Solution](#)

2. A wire has resistance of  $10\Omega$ . If it is stretched by  $1/10$ th of its length, then its resistance is nearly



[Watch Video Solution](#)

3. Potential difference of 100 V is applied to the ends of a copper wire one metre long. Calculate the average drift velocity of the electrons ? Compare it with thermal velocity at  $27^{\circ}C$ . Consider there is one conduction electron per atom. The density of copper is  $9.0 \times 10^3 \text{ kg/m}^3$ , Atomic mass of copper is 63.5 g. Avogadro's number =  $6.0 \times 10^{23}$  per gram-mole. Conductivity of copper is  $5.81 \times 10^7 \Omega^{-1} \text{ m}^{-1}$ . Boltzmann constant =  $1.38 \times 10^{23} \text{ JK}^{-1}$ .



**Watch Video Solution**

4. A silver wire has a resistance of  $2.1\Omega$  at  $27.5^\circ C$ , and a resistance of  $2.7\Omega$  at  $100^\circ C$ , Determine the temperature coefficient of resistivity of silver.



[Watch Video Solution](#)

5. Calculate resultant resistance between the points X and Y in the circuit shown in figure.



6. Six lead-acid type of secondary cells each of emf  $2.0\text{ V}$  and internal resistance  $0.015\Omega$  are joined in series to provide a supply to a resistance of  $8.5\Omega$ . What are the current drawn from the supply and its terminal voltage ?

(b) A secondary cells after long use has an emf of  $1 - 9\text{ V}$  and a large internal resistance of  $380\Omega$ . What maximum current can be drawn

from the cell ? Could the cell drive the starting motor of a car ?



**Watch Video Solution**

7. Two identical cells of emf 1.5 V each joined in parallel provide supply to an external circuit consisting of two resistances of  $7\Omega$  each joined in parallel. A very high resistance voltmeter reads the terminal voltage of cells to be 1.4 V. Calculate the internal resistance of each cell.



[Watch Video Solution](#)

8. Calculate the current in the arm AD as shown in figure. Each resistance is of  $10\Omega$ .



[View Text Solution](#)

9. In the given circuit, it is observed that the current  $I$  is independent of the value of the resistance  $R_6$ . Then the resistance values must

satisfy.



A.  $R_1 R_2 R_5 = R_3 R_4 R_6$

B.  $\frac{1}{R_5} + \frac{1}{R_6} = \frac{1}{R_1 + R_2} + \frac{1}{R_3 + R_4}$

C.  $R_1 R_4 = R_2 R_3$

D.  $R_1 R_3 = R_2 R_4$

**Answer: C**



**View Text Solution**



**10.** In a potentiometer arrangement, a cell of emf 1.25 V gives a balance point at 35.0 cm length of the wire. If the cell is replaced by another cell and the balance point shifts to 63.0 cm, what is the emf of the second cell ?



**Watch Video Solution**

**Neet Cafe Topicwise Practice Questions**

1. The plot represents the flow of current through a wire at three different times. The ratio of charges flowing through the wire at different times is



A. 2 : 1 : 2

B. 1 : 3 : 3

C. 1 : 1 : 1

D. 2 : 3 : 4

**Answer: C**



[View Text Solution](#)

2. In a closed circuit, the current  $i$  (in ampere) at an instant of time  $t$  (in second) is given by  $i = 4 - 0.08t$ . The number of electrons flowing in 50 s through the cross-section of the conductor is

A.  $1.25 \times 10^{19}$

B.  $6.25 \times 10^{20}$

C.  $5.25 \times 10^{19}$

D.  $2.55 \times 10^{20}$

**Answer: B**



**Watch Video Solution**

**3.** Current of 4.8 amperes is flowing through a conductor. The number of electrons per second will be

A.  $10^{19}$

B.  $2 \times 10^{19}$

C.  $3 \times 10^{19}$

D.  $7 \times 10^{20}$

**Answer: C**



**Watch Video Solution**

**4.** A steady current is passing through a linear conductor of non-uniform cross-section. The net quantity of charge crossing any cross-section per second is.

- A. proportional to the area of cross-section
- B. inversely proportional to the area of cross-section
- C. independent of the area of cross-section
- D. dependent on the length of conductor

**Answer: C**



**Watch Video Solution**

5. In a certain particle accelerator, electrons emerge in pulses at the rate of 250 pulses per second. Each pulse is of duration of 200 ns and the electrons in the pulse constitute a current of 250 mA. The number of electrons delivered by the accelerator per pulse is

A.  $8.00 \times 10^{10}$

B.  $5.00 \times 10^8$

C.  $3.13 \times 10^{11}$

D.  $9.60 \times 10^{10}$

**Answer: C**



**Watch Video Solution**

6. The density of copper is  $9 \times 10^3 \text{ kgm}^{-3}$  and its atomic mass is 63.5 u. Each copper atom provides one free electron. Estimate the number of free electrons per cubic metre in copper.

A.  $10^{19}$

B.  $10^{23}$



C.  $10^{25}$

D.  $10^{29}$

**Answer: D**



**Watch Video Solution**

7. The current flowing through wire depends on time as,  $i = 3t^2 + 2t + 5$

The charge flowing through the cross - section of the wire in time  $t = 0$  to  $t = 2$  second is

A. 22 C

B. 20 C

C. 18 C

D. 5 C

**Answer: A**



**Watch Video Solution**

**8.** Ampere-hour is a unit of

A. 3600 C

B. 3600 A

C. 3600 J

D. 3600 W

**Answer: A**



**Watch Video Solution**

9. If the electric current through an electric bulb is 3.2 A, the number of electrons flow through it in 1 second is

A.  $2 \times 10^9$

B.  $2 \times 10^{19}$

C.  $3.2 \times 10^9$

D.  $1.6 \times 10^{18}$

**Answer: B**



**Watch Video Solution**

**10.** The drift velocity of free electrons in a conductor is  $v$ , when a current  $i$  is flowing in it,

If both the radius and current are doubled,  
then the drift velocity will be :

A.  $v$

B.  $\frac{v}{2}$

C.  $\frac{v}{4}$

D.  $\frac{v}{8}$

**Answer: B**



**Watch Video Solution**

**11.** Current flows through a metallic conductor whose area of cross-section increases in the direction of the current. If we move in this direction.

- A. the current will decrease
- B. the current will increase
- C. the drift velocity will increase
- D. the drift velocity will decrease

**Answer: D**



**Watch Video Solution**

12. A conductor wire having  $10^{29}$  free electrons  $/m^3$  carries a current of 20A. If the cross-section of the wire is  $1mm^2$ , then the drift velocity of electrons will be :

A.  $1.25 \times 10^{-4} ms^{-1}$

B.  $1.25 \times 10^{-3} ms^{-1}$

C.  $1.25 \times 10^{-5} ms^{-1}$

D.  $6.25 \times 10^{-3} ms^{-1}$

**Answer: B**



**Watch Video Solution**

**13.** Give relation between drift velocity and electric field.

A. current density

B. current

C. resistivity

D. mobility



**Answer: D**



**Watch Video Solution**

**14.** A nichrome wire 50 cm long and one square millimetre cross- section carries a current of 4 A when connected to a 2 V battery. The resistivity of nichrome wire in ohm metre is

A.  $1 \times 10^{-6} \Omega m$

B.  $2 \times 10^{-7} \Omega m$

C.  $4 \times 10^{-7} \Omega m$

D.  $5 \times 10^{-7} \Omega m$

**Answer: A**



**Watch Video Solution**

**15.** The masses of the three wires of copper are in the ratio 5:3:1 and their lengths are in the ratio 1:3:5. The ratio of their electrical resistances is

A. 1 : 3 : 5

B. 5 : 3 : 1

C. 1 : 15 : 25

D. 125 : 15 : 1

**Answer: D**



**Watch Video Solution**

**16.** A copper wire of resistance  $R_0$  is stretched till its length is increased to  $n$  times of its

original length. What will be its new resistance?

A.  $2R$

B.  $4R$

C.  $8R$

D.  $16R$

**Answer: B**



**Watch Video Solution**

17. A material 'B' has twice the specific resistance of 'A'. A circular wire made of 'B' has twice the diameter of a wire made of 'A'. Then for the two wires to have the same resistance, the ratio  $l_B/l_A$  of their respective lengths must be

A. 2

B. 1

C.  $\frac{1}{2}$

D.  $\frac{1}{4}$

**Answer: A**



**Watch Video Solution**

**18.** The resistance of a 10 m long wire is  $10 \Omega$ . Its length is increased by 25% by stretching the wire uniformly . The resistance of wire will change to

A.  $12.5\Omega$

B.  $14.5\Omega$

C.  $15.6\Omega$

D.  $16.6\Omega$

**Answer: C**



**Watch Video Solution**

**19.** Two wires that are made up of two different materials whose specific resistance are in the ratio  $2 : 3$ , length  $3 : 4$  and area  $4 : 5$ .

The ratio of their resistances is

A.  $6 : 5$

B. 6: 8

C. 5: 8

D. 1: 2

**Answer: C**



**Watch Video Solution**

**20.** One kg of copper is drawn into a wire of 1 mm diameter and a wire of 2 mm diameter. The resistance of the two wires will be in the ratio



A. 2: 1

B. 1: 2

C. 16: 1

D. 4: 1

**Answer: C**



**Watch Video Solution**

**21.** A wire of resistance 12 ohms per meter is bent to form a complete circle of radius 10 cm. The resistance between its two diametrically

opposite points, A and B as shown in the figure is



A.  $3\Omega$

B.  $6\pi\Omega$

C.  $6\Omega$

D.  $0.6\pi\Omega$

**Answer: D**



**View Text Solution**

22. A block has dimensions 1 cm, 2cm, 3cm  
Ratio of the maximum and minimum  
resistance between any two points of opposite  
faces of this block is

A. 9:1

B. 1:9

C. 18:1

D. 1:6

**Answer: A**



**Watch Video Solution**

**23.** A wire P has resistance of 20 ohm. Another wire Q of same material but length twice that of P has resistance of 8 ohm. If  $r$  is the radius of cross-section of P, the radius of cross-section of Q is

A.  $r$

B.  $\frac{r}{\sqrt{2}}$

C.  $r\sqrt{5}$

D.  $2r$

**Answer: C**



**View Text Solution**

**24.** Ohm's law is valid, when the temperature of the conductor is

A.  $V$  is directly proportional to  $I^3$

B. the relation between  $V$  and  $I$  is non-unique

C.  $V$  is directly proportional to  $I^2$

D. V depends on I linearly

**Answer: D**



**Watch Video Solution**

**25.** A resistance of  $2\Omega$  is to be made from a copper wire (specific resistance  $1.7 \times 10^{-8}\Omega m$ ) using a wire of length 50 cm.

The radius of the wire is

A.  $0.0116mm$

B.  $0.0367\text{mm}$

C.  $0.116\text{mm}$

D.  $0.367\text{mm}$

**Answer: B**



**Watch Video Solution**

**26.** Two copper wire of length  $l$  and  $2l$  have radii,  $r$  and  $2r$  respectively. What is the ratio of their specific resistance.?

A. 1:2

B. 2:1

C. 1:1

D. 1:3

**Answer: C**



**Watch Video Solution**

**27.** Which circuit diagram shows voltmeter V and ammeter A correctly positioned to



measure the total potential difference of the circuit and the current through each resistor?

A. 

B. 

C. 

D. 

**Answer: A**



**View Text Solution**

28. The electric field  $E$ , current density  $j$  and conductivity  $\sigma$  of a conductor are related as

A.  $\sigma = E/J$

B.  $\sigma = J/E$

C.  $\sigma = J^2 E$

D.  $\sigma = \frac{1}{JE}$

**Answer: B**



**Watch Video Solution**

29. Which of the following arrangements is correct on the basis of conductivity of materials?

A. Silver > copper > aluminium > tungsten

B. Silver > aluminium > copper > tungsten

C. Copper > silver > tungsten > aluminium

D. Silver > tungsten > copper >

aluminium

**Answer: A**



**Watch Video Solution**

**30.** The current density varies radical distance  $r$  as  $J = ar^2$ , in a cylindrical wire of radius  $R$ . The current passing through the wire between radical distance  $R/3$  and  $R/2$  is,

A.  $\frac{65\pi a R^4}{2592}$

B.  $\frac{25\pi a R^4}{72}$

C.  $\frac{65\pi a^2 R^3}{2938}$

D.  $\frac{81\pi a^2 R^4}{144}$

**Answer: A**



**Watch Video Solution**

**31.** Which of the following materials is the best conductor of electricity ?

A. Platinum

B. Gold

C. Silicon

D. Copper

**Answer: D**



**Watch Video Solution**

**32.** For which of the following dependences of drift velocity,  $v_d$  on electric field  $E$ , Ohm's law obeyed?

A.  $v_d \propto E$

B.  $v_d \propto E^2$

C.  $v_d \propto \sqrt{E}$

D.  $v_d \propto \frac{1}{E}$

**Answer: A**



**Watch Video Solution**

**33.** Current is flowing with a current density

$J = 480 \text{ Acm}^{-2}$  in a copper wire. Assuming

that each copper atom contributes one free

electron and given that

Avogadro number =  $6.0 \times 10^{23}$  atoms/mole

Density of copper =  $9.0 \text{ g/cm}^3$

Atomic weight of copper = 64 g/mole

Electronic charge =  $1.6 \times 10^{-19}$  coulomb

The drift velocity of electrons is

A. 1 mm/s

B. 2 mm/s

C. 0.5 mm/s

D. 0.36 mm/s

**Answer: D**





View Text Solution

34. The V-I graph for a conductor at temperature  $T_1$  and  $T_2$  are as shown in the figure. The term  $(T_2 - T_1)$  is proportional to



A.  $\cos 2\theta$

B.  $\sin 2\theta$

C.  $\cot 2\theta$

D.  $\tan 2\theta$

**Answer: C**



**View Text Solution**

**35.** The temperature coefficient of resistance for a wire is  $0.00125^{\circ}C^{-1}$ . At 300 K its resistance is  $1\Omega$ . The temperature at which the resistance becomes  $2\Omega$  is

A. 450 K

B. 1127 K

C. 454 K

D. 900 K

**Answer: B**



**Watch Video Solution**

**36.** The resistance of the wire in the platinum resistance thermometer at ice point is  $5\Omega$  and at steam point is  $5.25\Omega$ . When the thermometer is inserted in an unknown hot bath its resistance is found to be  $5.5\Omega$ . The temperature of the hot bath is

A.  $100^{\circ} C$

B.  $200^{\circ} C$

C.  $300^{\circ} C$

D.  $350^{\circ} C$

**Answer: B**



**Watch Video Solution**

**37. Find the true statement.**

- A. Ohm's law is applicable to all conductors of electricity
- B. In an electrolyte solution, the electric current is mainly due to the movement of electrons
- C. Specific resistance of a wire depends upon its dimension
- D. The resistance of carbon decreases with the increase of temperature

**Answer: D**



Watch Video Solution

38. The graph between resistivity and temperature, for a limited range of temperature, is a straight line for a material like

A. copper

B. nichrome

C. silicon

D. mercury

**Answer: B**



**View Text Solution**

**39.** On increasing the temperature of a conductor, its resistance increases because

A. relaxation time increases

B. electron density decreases

C. relaxation time decreases

D. relaxation time remains constant

**Answer: C**



**Watch Video Solution**

**40.** The voltage  $V$  and current  $I$  graphs for a conductor at two different temperature  $T_1$  and  $T_2$  are shown in the figure. The relation between  $T_1$  and  $T_2$  is



A.  $T_1 > T_2$

B.  $T_1 < T_2$



C.  $T_1 = T_2$

D.  $T_1 = \frac{1}{T_2}$

**Answer: A**



**View Text Solution**

**41.** Fractional increase in resistivity per unit increase in temperature is defined as

A. resistivity

B. temperature coefficient of resistivity

C. conductivity

D. drift velocity

**Answer: B**



**Watch Video Solution**

**42.** The resistance of a wire at  $20^{\circ}C$  is  $20\Omega$  and at  $500^{\circ}C$  is  $60\Omega$ . At which temperature its resistance will be  $25\Omega$ ?

A.  $160^{\circ}C$

B.  $250^{\circ}C$

C.  $100^{\circ}C$

D.  $80^{\circ}C$

**Answer: D**



**Watch Video Solution**

**43.** Nichrome or Manganin is widely used in wire bound standard resistors because of their

A. temperature independent resistivity

B. very weakly temperature dependent resistivity

C. strong dependence of resistivity with temperature

D. mechanical strength

**Answer: B**



**Watch Video Solution**

44. The tolerance level of a resistor with the colour code red, blue, orange, gold is

A.  $\pm 5\%$

B.  $\pm 10\%$

C.  $\pm 20\%$

D.  $\pm 30\%$

**Answer: A**



**Watch Video Solution**

45. What is the colour code for a resistor of resistance  $3.5k\Omega$  with 5% tolerance ?

- A. orange, green, orange and gold
- B. orange, green, orange and silver
- C. orange, green, red and silver
- D. orange, green, red and gold

**Answer: D**



**Watch Video Solution**

46. A resistor is marked with the rings coloured brown, black, green, and gold. The resistance in ohm is

A.  $1 \times 10^6 \pm 10 \%$

B.  $1 \times 10^7 \pm 5 \%$

C.  $1 \times 10^6 \pm 5 \%$

D.  $1 \times 10^5 \pm 5 \%$

**Answer: C**



**Watch Video Solution**

47. Pick out the wrong feature about carbon resistors.

A. Compact

B. Inexpensive

C. Relatively sensitive to temperature

D. Colour codes express their resistance values

**Answer: C**



**View Text Solution**



**48.** Two wires of same metal have the same length but their cross-sections are in the ratio 3 :1 . They are joined in series. The resistance of the thicker wire is  $10\Omega$  . The total resistance of the combination will be

A.  $(5/2)\Omega$

B.  $(40/3)\Omega$

C.  $40\Omega$

D.  $100\Omega$

**Answer: C**



**Watch Video Solution**

**49.** In the two circuits shown in the figure



A.  $R_{AB} = R_{CD} = (\sqrt{3} + 2)\Omega$

B.  $R_{AB} = (\sqrt{3} + 1)\Omega$

C.  $R_{CD} = (\sqrt{5} + 1)\Omega$

D.  $R_{AB} > R_{CD}$

**Answer: D**



**View Text Solution**

**50.** What is the equivalent resistance of the network shown in figure?



A.  $8\Omega$

B.  $\frac{16}{3}\Omega$

C.  $4\Omega$

D.  $\frac{16}{5}\Omega$

**Answer: B**



**View Text Solution**

51. Eight resistance each of 4 ohm are connected in the circuit as shown in figure.

The equivalent resistance between A and B is



A.  $\frac{8}{3} \Omega$

B.  $\frac{32}{3} \Omega$

C.  $\frac{32}{15} \Omega$

D.  $\frac{32}{11} \Omega$

**Answer: C**

 [View Text Solution](#)

**52.** In the circuit shown in figure, the total current supplied by the battery is



A.  $1A$

B.  $2A$

C.  $3A$

D.  $6A$

**Answer: C**



**View Text Solution**

**53.** The reading of ammeter shown in figure is



A.  $6.56 A$

B.  $3.28 A$

C. 2.18 A

D. 1.09 A

**Answer: C**



[View Text Solution](#)

**54.** Two resistances  $R_1$  and  $R_2$  provides series to parallel equivalents as  $n/1$ , then the correct relationship is

$$\text{A. } \left( \frac{R_1}{R_2} \right)^{3/2} + \left( \frac{R_2}{R_1} \right)^{3/2} = n^{3/2}$$

$$\text{B. } \left(\frac{R_1}{R_2}\right)^3 + \left(\frac{R_2}{R_1}\right)^3 = n^3$$

$$\text{C. } \left(\frac{R_1}{R_2}\right)^2 + \left(\frac{R_2}{R_1}\right)^2 = n^2$$

$$\text{D. } \left(\frac{R_1}{R_2}\right)^{1/2} + \left(\frac{R_2}{R_1}\right)^{1/2} = n^{1/2}$$

**Answer: D**



**Watch Video Solution**

**55.** Five equal resistances each of value  $R$  are connected to form a network as shown in figure. The equivalent resistance of the



network between the points A and B is



A.  $\frac{1}{2}R$

B.  $2R$

C.  $\frac{5}{8}R$

D.  $\frac{8}{5}R$

**Answer: C**



**View Text Solution**

56.  $A$  and  $B$  are two points on a uniform ring of resistance  $R$  the  $\angle ASCB = \theta$ , where  $C$  is the centre of the ring. The equivalent resistance between  $A$  and  $B$

A.  $\frac{R\theta}{2\pi}$

B.  $\frac{R(2\pi - \theta)}{4\pi}$

C.  $R\left(1 - \frac{\theta}{2\pi}\right)$

D.  $\frac{R\theta}{4\pi^2}(2\pi - \theta)$

**Answer: D**



Watch Video Solution

57. The given figure shows a network of resistance. The effective resistance between points A and B of network is



A.  $(3/2)\Omega$

B.  $6\Omega$

C.  $3\Omega$

D.  $2\Omega$

**Answer: D**



**View Text Solution**

**58.** An electric of  $5A$  is passing through a circuit containing three arrangement in parallel if the length and radius of the wires are in the ratio  $2:3:4$  and  $3:4:5$  then the ratio of current passing through wires should be

**A.  $3:6:10$**

B. 4: 9: 16

C. 9: 16: 25

D. 54: 64: 75

**Answer: D**



**Watch Video Solution**

**59.** For the circuit shown in the figure, the current in the  $4\Omega$  resistor is



A.  $0.5A$

B.  $0.25A$

C.  $1A$

D.  $1.5A$

**Answer: B**



**View Text Solution**

**60.** Fourteen identical resistors each of resistance  $R$  are connected as shown in the figure. The equivalent resistance between the

points A and B is



A.  $R$

B.  $14R$

C.  $\frac{R}{14}$

D.  $1.2R$

**Answer: D**



**View Text Solution**

61. In the circuit shown in figure, the potential difference across  $3\Omega$  is



A. 2 V

B. 4 V

C. 8 V

D. 16 V

**Answer: A**



**View Text Solution**



62. What is the potential difference between the points A and B in the circuit diagram shown in figure?



A.  $\frac{20}{3}$  volt

B.  $\frac{10}{3}$  volt

C.  $\frac{20}{\sqrt{3}}$  volt

D.  $\frac{10}{\sqrt{3}}$  volt

**Answer: A**

 [View Text Solution](#)

**63.** A uniform wire of resistance 36 ohm is bent in the form of a circle. The effective resistance across the points A and B is



A.  $5\Omega$

B.  $15\Omega$

C.  $7.2\Omega$

D.  $30\Omega$

**Answer: A**



**View Text Solution**

**64.** Three unequal resistor in parallel are equivalent to a resistance  $1\Omega$  If two of them are in the ratio 1:2 and if no resistance value is fractional the largest of the three resistance in ohm is

A. 4

B. 6

C. 5

D. 12

**Answer: B**



**Watch Video Solution**

**65.** In the figure, find the resistance between points A and B. Both the circle and the diameter are made of uniform wire of resistance  $1 \times 10^{-4}$  ohm per metre. The

length AB is 2 metre.



A.  $(2/3) \times 10^{-4} \Omega$

B.  $2\pi \times 10^{-4} \Omega$

C.  $14.56 \times 10^{-4} \Omega$

D.  $0.88 \times 10^{-4} \Omega$

**Answer: D**



**View Text Solution**

66. 

In the circuit shown, the current through the  $4\Omega$  resistor is 1 amp when the points P and M are connected to a d.c. voltage source. The potential difference between the points M and N is

A. 0.5 volt

B. 3.2 volt

C. 1.5 volt

D. 1.0 volt

**Answer: B**



**View Text Solution**

**67.** In the network shown below, the ring has zero resistance. The equivalent resistance between the points A and B is



A.  $2R$

B.  $4R$

C.  $7R$

D. 10R

**Answer: A**



**View Text Solution**

**68.** Three resistors are connected to form the sides of a triangle ABC , the resistance of the sides AB, BC and CA are 40 ohms , 60 ohms and 100 ohms respectively. The effective resistance between the points A and B in ohms will be



A. 32

B. 64

C. 50

D. 200

**Answer: A**



**Watch Video Solution**

**69.** In the given circuit the voltmeter records 5 V. The resistance of the voltmeter in ohm is



A. 200

B. 100

C. 10

D. 50

**Answer: B**



**View Text Solution**

**70.** In the circuit shown in figure, reading of voltmeter is  $V_1$  when only  $S_1$  is closed, reading of voltmeter is  $V_2$ ) when only  $S_2$  is closed and

reading of voltmeter is  $V_3$  when both  $S_1$  and  $S_2$  are closed. Then



A.  $V_3 > V_2 > V_1$

B.  $V_2 > V_1 > V_3$

C.  $V_3 > V_1 > V_2$

D.  $V_1 > V_2 > V_3$

**Answer: B**



**View Text Solution**

71. Resistors each of value  $1\Omega$  are arranged as shown in the figure. The equivalent resistance between points A and B is



A.  $\frac{1}{2}\Omega$

B.  $\frac{1}{5}\Omega$

C.  $\frac{5}{4}\Omega$

D.  $\frac{4}{5}\Omega$

**Answer: A**



**View Text Solution**

72. A potential difference of 220 V is maintained across a 12000 ohm rheostat AB as shown in figure. The voltmeter V has a resistance of 6000 ohm and point C is at one fourth of the distance from A to B. What is the reading in the voltmeter?



A. 32 V

B. 36 V

C. 40 V

D. 42 V

**Answer: C**



**View Text Solution**

**73.** Find the reading of ammeter in the given circuit?



A. 3A

B. 4A

C.  $1.5A$

D.  $6A$

**Answer: A**



**View Text Solution**

**74.** In the circuit shown in the given figure, the resistance  $R_1 R_2$  are respectively



A.  $14\Omega$  and  $40\Omega$

B.  $40\Omega$  and  $14\Omega$

C.  $40\Omega$  and  $30\Omega$

D.  $14\Omega$  and  $30\Omega$

**Answer: A**



**View Text Solution**

**75.** A letter  $A$  is constructed as a uniform wire of resistance  $1 \text{ ohm/cm}$ . The sides of the letter are  $20 \text{ cm}$  long and the cross piece in the middle is  $10 \text{ cm}$  long while the vertex angle is



$60^\circ$  the resistance of the letter between the two ends of the legs is

A.  $50.0\Omega$

B.  $26.7\Omega$

C.  $2.72\Omega$

D.  $34.0\Omega$

**Answer: B**



**Watch Video Solution**

76. Two wires of same radius having lengths  $l_1$  and  $l_2$  and resistivities  $\rho_1$  and  $\rho_2$  are connected in series. The equivalent resistivity will be

A.  $\frac{\rho_1 l_2 + \rho_2 l_1}{\rho_1 + \rho_2}$

B.  $\frac{\rho_1 l_1 + \rho_2 l_2}{l_1 + l_2}$

C.  $\frac{\rho_1 l_1 + \rho_2 l_2}{l_1 - l_2}$

D.  $\frac{\rho_1 l_2 + \rho_2 l_1}{l_1 + l_2}$

**Answer: B**



Watch Video Solution

77. You have been provided with four 400 ohm resistors each. The number of ways in which these can be combined to have different equivalent resistances is

A. seven different combinations and seven different equivalent resistances

B. eight different combinations and seven different equivalent resistances

C. nine different combinations and eight different equivalent resistances

D. ten different combinations and nine different equivalent resistances

**Answer: D**

 [View Text Solution](#)

**78.** Seven resistances each of  $20\Omega$  are connected with 2 V battery as shown in figure.

The reading of ammeter will be



A.  $\left(\frac{1}{10}\right)A$

B.  $\left(\frac{3}{10}\right)A$

C.  $\left(\frac{4}{10}\right)A$

D.  $\left(\frac{7}{10}\right)A$

**Answer: C**



**View Text Solution**

79. Two conductors have the same resistance at  $0^\circ C$  but their temperature coefficient of resistance are  $\alpha_1$  and  $\alpha_2$ . The respective temperature coefficients of their series and parallel combinations are nearly

A.  $\alpha_1 + \alpha_2$

B.  $\frac{\alpha_1 + \alpha_2}{2}$

C.  $\alpha_1 - \alpha_2$

D.  $\frac{\alpha_1 - \alpha_2}{2}$

**Answer: B**



Watch Video Solution

80. In the circuit shown, the value of



A.  $R = 15\Omega$

B.  $R = 30\Omega$

C.  $\varepsilon = 36V$

D.  $\varepsilon = 180V$

**Answer: D**



81. Thirteen resistances each of resistance  $R\omega$  are connected in the circuit as shown in the figure. The effective resistance between A and B is



A.  $2R\Omega$

B.  $\frac{4}{3}R\Omega$

C.  $\frac{2}{3}R\Omega$

D.  $R\Omega$



**Answer: C**



**View Text Solution**

**82.** In the circuit shown, when R is removed an additional resistance of  $72\Omega$  must be introduced in series with the battery in order to keep the current through  $30\Omega$  resistance unaltered. Hence R is



A.  $15\Omega$

B.  $18\Omega$

C.  $20\Omega$

D.  $21\Omega$

**Answer: C**



**View Text Solution**

**83.** In the circuit shown, the internal resistance of the cell is negligible. The steady state current in the  $2\Omega$  resistor is



A.  $0.6A$

B.  $0.9A$

C.  $1.2A$

D.  $1.5A$

**Answer: B**



**View Text Solution**

**84.** A copper wire and an iron wire, each having an area of cross-section  $A$  and lengths  $L_1$  and  $L_2$  are joined end to end. The copper

end is maintained at a potential  $V_1$  and the iron end at a lower potential  $V_2$ . If  $\sigma_1$  and  $\sigma_2$  are the conductivities of copper and iron respectively, the potential of the junction will be

- A.  $\frac{\sigma_1 V_1 + \sigma_2 V_2}{\frac{\sigma_1}{L_1} + \frac{\sigma_2}{L_2}}$
- B.  $\frac{\frac{\sigma_1 V_1}{L_1} + \frac{\sigma_2 V_2}{L_2}}{\frac{\sigma_1}{L_1} + \frac{\sigma_2}{L_2}}$
- C.  $\frac{\frac{\sigma_1}{L_1} + \frac{\sigma_2}{L_2}}{\sigma_1 V_1 + \sigma_2 V_2}$
- D.  $\frac{\sigma_1 V_1 - \sigma_2 V_2}{\frac{\sigma_1}{L_1} - \frac{\sigma_2}{L_2}}$

**Answer: B**



View Text Solution

85. The resultant resistance of the circuit between A and B is



A.  $\frac{R}{2}$

B.  $\frac{3R}{2}$

C.  $2R$

D.  $R$

**Answer: A**



[View Text Solution](#)

86. In the circuit shown below, the current that flows a to b when the switch S is closed is



A.  $-1.5A$

B.  $+1.5A$

C.  $+1.0A$

D.  $-1.0A$

**Answer: D**



View Text Solution

87. In the circuit shown below each resistance is  $R$ . The current  $I$  is



A.  $\frac{15V_0}{7R}$

B.  $\frac{7V_0}{15R}$

C.  $\frac{7V_0}{R}$

D.  $\frac{15V_0}{R}$

**Answer: A**



[View Text Solution](#)

**88.** A uniform conductor of resistance  $R$  is cut into 20 equal pieces, half of them are joined in series and the remaining half are connected in parallel. If the two combinations are joined in series, effective resistance of all the pieces is

A.  $R$

B.  $\frac{R}{2}$

C.  $\frac{101}{200}R$



D.  $\frac{201}{200}R$

**Answer: C**



**Watch Video Solution**

**89.** In the circuit shown, the current through 8 ohm is same before and after connecting  $\varepsilon$ .

The value of  $\varepsilon$  is



A. 12 V

B. 6 V

C. 4 V

D. 8 V

**Answer: C**



**View Text Solution**

**90.** Two resistors of resistances  $200k\Omega$  and  $1M\omega$  respectively form a potential divider with outer junctions maintained at potentials of  $+3V$  and  $-15V$

. Then, the potential at the junction between the resistors is

A.  $0V$

B.  $+1V$

C.  $-12V$

D.  $+12V$

**Answer: A**



**View Text Solution**

91. Three resistance  $5\Omega$ ,  $5\Omega$  and  $6\Omega$  are connected as shown in figure. If the point S divides the resistance  $6\Omega$  into two equal halves, the resistance between points P and S is



A.  $11\Omega$

B.  $8\Omega$

C.  $6\Omega$

D.  $4\Omega$

**Answer: D**



**View Text Solution**

**92.** A number of  $24\Omega$  resistors are connected as shown in the figure. Then the effective resistance between P and Q is



A.  $21.6\Omega$

B.  $24.8\Omega$

C.  $26\Omega$

D.  $36\Omega$

**Answer: B**



**View Text Solution**

**93.** The effective resistance across the points A and I is



A.  $2\Omega$

B.  $1\Omega$

C.  $0.5\Omega$

D.  $5\Omega$

**Answer: B**



**View Text Solution**

**94.** In the circuit shown in the figure, the current through  $3\Omega$  resistance is



A.  $0.5A$

B.  $0.7A$

C.  $1.0A$

D.  $1.2A$

**Answer: C**



**View Text Solution**

**95.** In the circuit shown, the current  $I_1$  and  $I_2$

are





A.  $I_1 = 1.5A, I_2 = 0.5A$

B.  $I_1 = 0.5A, I_2 = 1.5A$

C.  $I_1 = 1A, I_2 = 3A$

D.  $I_1 = 3A, I_2 = 1A$

**Answer: B**



**View Text Solution**

**96.** The reading on the ammeter in the following figure will be



A.  $0.8A$

B.  $0.6A$

C.  $0.4A$

D.  $0.2A$

**Answer: C**



**View Text Solution**

**97.** The resistance across A and B in the figure below will be



A.  $3R$

B.  $R$

C.  $\frac{R}{3}$

D.  $2R$

**Answer: C**



**View Text Solution**

**98.** The potential difference between A and B as shown in the given figure is



A.  $1V$

B.  $2V$

C.  $3V$

D.  $4V$

**Answer: A**



**View Text Solution**

**99.** The equivalent resistance between points A and B with switch S open and closed are

respectively



A.  $4\Omega$ ,  $8\Omega$

B.  $8\Omega$ ,  $4\Omega$

C.  $6\Omega$ ,  $9\Omega$

D.  $9\Omega$ ,  $6\Omega$

**Answer: B**



**View Text Solution**

**100.** How many minimum number of  $2\Omega$  resistance can be connected to have an effective resistance of  $1.5\Omega$

A. 3

B. 2

C. 6

D. 4

**Answer: C**



**Watch Video Solution**

101. A battery of emf, 10 V is connected to resistances as shown in figure. The potential difference  $V_A - V_B$  between the points A and B is



A.  $-2V$

B.  $\left(\frac{20}{11}\right)V$

C.  $2V$

D.  $5V$

**Answer: C**



[View Text Solution](#)

**102.** In the given circuit the equivalent resistance between the points A and B is



A.  $9\Omega$

B.  $11.6\Omega$

C.  $14.5\Omega$

D.  $21.2\Omega$

**Answer: B**





[View Text Solution](#)

**103.** If the ammeter in the given circuit reads 2 A, the resistance R is



A.  $1\Omega$

B.  $2\Omega$

C.  $3\Omega$

D.  $4\Omega$

**Answer: A**



[View Text Solution](#)

**104.** What current will flow through the  $2k\Omega$  resistor in the circuit shown in the figure?



- A. 3 mA
- B. 6 mA
- C. 12 mA
- D. 36 mA

**Answer: A**



[View Text Solution](#)

**105.** Figure shows a network of eight resistors, each equal to  $2\Omega$ , connected to a 3 V battery of negligible internal resistance. The current  $I$  in the circuit is



A. 0.25 A

B. 0.50 A

C. 0.75 A

D. 1.0 A

**Answer: D**



**View Text Solution**

**106.** The equivalent resistance between the terminals A and D in the following circuit is



A.  $10\Omega$

B.  $20\Omega$

C.  $5\Omega$

D.  $30\Omega$

**Answer: B**



**View Text Solution**

**107.** A metallic wire of resistance  $12\Omega$  is bent of form a square. The resistance between two diagonal points would be

A.  $12\Omega$

B.  $24\Omega$

C.  $6\Omega$


D.  $3\Omega$

**Answer: D**



**Watch Video Solution**

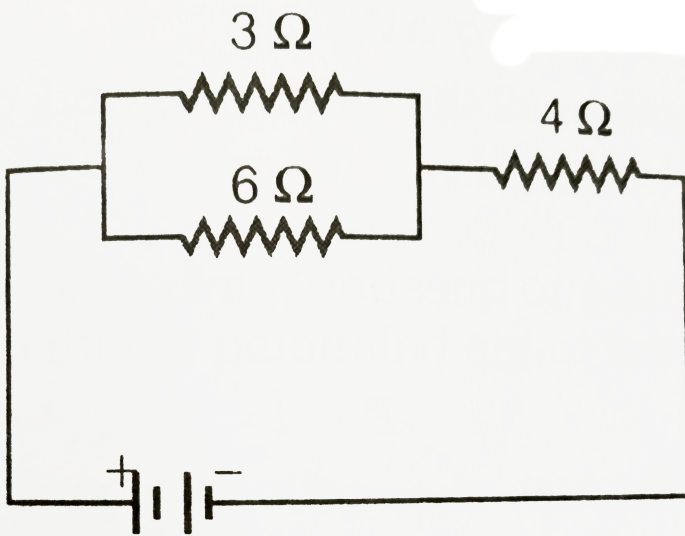**108.** Current through  $3\Omega$  resistor is  $0.8\text{A}$ , then potential drop through  $4\Omega$  resistor is



A. 9.6 V

B. 2.6 V

C. 4.8 V

D. 1.2 V

**Answer: C**



**Watch Video Solution**

**109.** Three equal resistances each of  $3\Omega$  are in series and connected to a cell of internal resistance one ohm. If these resistance are in parallel and connected to the same cell, then the ratio of the respective currents through the electric circuits in the two cases is

A.  $1/8$

B.  $1/7$

C.  $1/5$



D. 1/3

**Answer: C**



**Watch Video Solution**

**110.** The emf of the battery  $\varepsilon$  in the circuit shown in figure is 15 volt and internal resistance is 0.5 ohm. What is the current drawn from the battery?



A. 1A

B.  $2A$

C.  $3A$

D.  $4A$

**Answer: A**



**View Text Solution**

**111.** The emf of a cell is  $\varepsilon$  and its internal resistance is  $r$ . its terminals are connected to a resistance  $R$ . The potential difference between

the terminals is  $1.6V$  for  $R = 4\Omega$ , and  $1.8V$  for  $R = 9\Omega$ . Then,

A.  $\varepsilon = 1V, r = 1\Omega$

B.  $\varepsilon = 2V, r = 1\Omega$

C.  $\varepsilon = 2V, r = 2\Omega$

D.  $\varepsilon = 2.5V, r = 0.5\Omega$

**Answer: B**



**Watch Video Solution**

**112.** When a current of 2 A flows in a battery from negative to positive terminal, the potential difference across it is 12 V. If a current of 3 A flowing in the opposite direction produces a potential difference of 15 V, the emf of the battery is

A. 12.6 V

B. 13.2 V

C. 13.5 V

D. 14.0 V

**Answer: B**



**Watch Video Solution**

**113.** A battery of emf  $\varepsilon$  and internal resistance  $r$  is connected to the circuit as shown in the figure. When the key  $K_1$  is closed and  $K_2$  is open, the ideal voltmeter shows a reading of 18 V. When key  $K_2$  is closed and  $K_1$  is open, the voltmeter reading is 24 V. When  $K_1$  and  $K_2$  are both open, the voltmeter

reading is



A. 8 V

B. 12 V

C. 24 V

D. 36 V

**Answer: D**



**View Text Solution**

**114.** A battery of emf  $E$  has an internal resistance  $r$ . A variable resistance  $R$  is connected to the terminals of the battery. A current  $i$  is drawn from the battery.  $V$  is the terminal potential difference. If  $R$  alone is gradually reduced to zero, which of the following best describes  $i$  and  $V$ ?

A.  $i$  approaches zero,  $V$  approaches  $\varepsilon$

B.  $i$  approaches  $\varepsilon / r$ ,  $V$  approaches zero

C.  $i$  approaches  $\varepsilon / r$ ,  $V$  approaches  $\varepsilon$

D.  $I$  approaches infinity,  $V$  approaches  $\varepsilon$

**Answer: B**



**Watch Video Solution**

**115.** A battery of emf  $\varepsilon$  and internal resistance  $r$  sends currents  $I_1$  and  $I_2$ , when connected to external resistance  $R_1$  and  $R_2$  respectively. Find the emf and internal resistance of the battery.

A. 
$$\frac{I_1 R_2 - I_2 R_1}{I_2 - I_1}$$



B.  $\frac{I_1 R_2 + I_2 R_1}{I_1 - I_2}$

C.  $\frac{I_1 R_1 + I_2 R_2}{I_1 - I_2}$

D.  $\frac{I_1 R_1 - I_2 R_2}{I_2 - I_1}$

**Answer: D**



**Watch Video Solution**

**116.** Three resistances of magnitude 2, 3 and 5 ohm are connected in parallel to a battery of 10 volts and of negligible resistance. The

potential difference across  $3\Omega$  resistance will be

A. 10 V

B. 5 V

C. 3 V

D. 2 V

**Answer: A**



**Watch Video Solution**

**117.** A battery of emf 8 V with internal resistance  $0.5\Omega$  is being charged by a 120 V dc supply using a series resistance of  $15.5\Omega$ . The terminal voltage of the battery is

A. 20.5 V

B. 15.5 V

C. 11.5 V

D. 2.5 V

**Answer: C**



Watch Video Solution

**118.** In the given figure, the internal resistance of the cell is



A.  $2\Omega$

B.  $2.5\Omega$

C.  $1\Omega$

D.  $1.5\Omega$

**Answer: B**





**119.** A student measures the terminal potential difference ( $V$ ) of a cell (of emf  $\varepsilon$  and internal resistance  $r$ ) as a function of the current ( $I$ ) flowing through it. The slope and intercept of the graph between  $V$  and  $I$ , then respectively, equal

A.  $-r$  and  $\varepsilon$

B.  $r$  and  $-\varepsilon$

C.  $-\varepsilon$  and  $r$

D.  $\varepsilon$  and  $-r$

**Answer: A**



**Watch Video Solution**

**120.** The number of dry cells, each of e.m.f. 1.5 volt and internal resistance  $0.5\omega$  that must be joined in series with a resistance of 20 ohm so as to send a current of 0.6 ampere through the circuit is -

A. 2

B. 8

C. 10

D. 12

**Answer: C**



**Watch Video Solution**

**121.** A group of  $N$  cells whose emf varies directly with the internal resistance as per the equation  $\varepsilon_N = 1.5r_N$  are connected as shown

in the figure. The current  $I$  in the circuit is



A. 0.51 A

B. 5.1 A

C. 0.15 A

D. 1.5 A

**Answer: D**



**View Text Solution**



122. 32 cells each of emf  $3V$  are connected in series. The combination as shown and the total emf is  $84V$  How many number of cells are connected reversely?

A. 0

B. 2

C. 4

D. 8

**Answer: B**



Watch Video Solution

**123.**  $n$  identical cells, each of emf  $\varepsilon$  and internal resistance  $r$ , are joined in series to form a closed circuit. One cell is joined with reversed polarity. The potential difference across each cell, except A, is

A.  $\frac{2n\varepsilon}{n-2}$

B.  $\frac{(n-2)\varepsilon}{n}$

C.  $\frac{(n-1)\varepsilon}{n}$

D.  $\frac{2\varepsilon}{n}$

**Answer: D**



**Watch Video Solution**

**124.** Three similar cells, each of emf  $2\text{ V}$  and internal resistance  $r\Omega$  send the same current through an external resistance of  $2\Omega$ , when connected in series or in parallel. The strength of the current flowing through the external resistance is

A.  $1\text{ A}$

B.  $1.5A$

C.  $2A$

D.  $0.75A$

**Answer: D**



**View Text Solution**

**125.** What is the potential drop between points A and C in the following circuit?

Resistances  $1\Omega$  and  $2\Omega$  represent the internal

resistances of the respective cells.



A. 1.75 V

B. 2.25 V

C.  $\frac{5}{4}V$

D.  $\frac{4}{5}V$

**Answer: B**



**View Text Solution**

**126.** Two batteries of emfs 2 V and 1 V of internal resistances  $1\Omega$  and  $2\Omega$  respectively are connected in parallel. The effective emf of the combination is

A.  $\frac{3}{2}V$

B.  $\frac{5}{3}V$

C.  $\frac{3}{5}V$

D.  $2V$

**Answer: B**



Watch Video Solution

127.  $n$  equal cell having emf  $E$  and internal resistance  $r$ , are connected in series circuit of a resistance  $R$ . Same current flows in circuit either they connected in series or parallel, if:

A.  $R = nr$

B.  $R = r$

C.  $r = nR$

D.  $R = \sqrt{nr}$

**Answer: B**



**Watch Video Solution**

**128.** 4 cells each of emf 2 V and internal resistance of  $1\Omega$  are connected in parallel to a load resistor of  $2\Omega$ . Then the current through the load resistor is

A.  $2A$

B.  $1.5A$

C.  $1A$



D.  $0.888A$

**Answer: D**



**Watch Video Solution**

**129.** Four cells of identical emf  $\varepsilon$  and internal resistance  $r$  are connected in series to a variable resistor. The following graph shows the variation of terminal voltage of the combination with current. The emf of each cell

used is



A. 1.4 V

B. 5.6 V

C. 2 V

D. 1 V

**Answer: A**



**View Text Solution**

**130.** A galvanometer connected with an unknown resistor and two identical cells in series each of emf 2 V shows a current of 1 A. If the cells are connected in parallel, it shows 0.8 A. Then the internal resistance of the cell is

A.  $1\Omega$

B.  $0.5\Omega$

C.  $0.25\Omega$

D.  $0.33\Omega$

**Answer: A**



Watch Video Solution

**131.** Eels are able to generate current with biological cells called electroplaques. The electroplaques in an eel are arranged in 100 rows, each row stretching horizontally along the body of fish containing 5000 electroplaques. The arrangement is suggestively shown in the figure. Each electroplaque has an emf of 0.15 V and internal resistance of  $0.25\Omega$ . The water surrounding the eel completes a circuit between the head

and its tail. If the water surrounding it has a resistance of  $500\Omega$ , the current, an eel can produce in water is about



A. 1.5 A

B. 3.0 A

C. 15 A

D. 30 A

**Answer: A**



**View Text Solution**

132. In the given circuit voltage across resistance  $R_4$  is



A. 0.4 V

B. 0.6 V

C. 0.8 V

D. 1.0 V

**Answer: A**



**View Text Solution**

**133.** The figure shows a network of currents. The magnitude of current is shown here. The current  $I$  will be



A.  $-3A$

B.  $3A$

C.  $13A$

D.  $23A$

**Answer: D**



[View Text Solution](#)

**134.** A current of 6 A enters one corner P of an equilateral triangle PQR having 3 wires of resistances  $2\Omega$  each and leaves by the corner R. Then the currents  $I_1$  and  $I_2$  are



A. 2 A, 4 A

B. 4 A, 2 A

C. 1 A, 2 A



D. 2 A, 3 A

**Answer: A**



**View Text Solution**

**135.** Figure shows currents in a part of an electric circuit, then current  $I$  is



A. 1.7 A

B. 3.7 A

C. 1.3 A

D. 1A

**Answer: A**



**View Text Solution**

**136.** In the circuit shown, current flowing through 25 V cell is



A. 7.2 A

B.  $10A$

C.  $12A$

D.  $14.2A$

**Answer: C**

 [View Text Solution](#)

**137.** For what value of  $R$  will the current in galvanometer be zero?



A.  $1\Omega$

B.  $2\Omega$

C.  $5\Omega$

D.  $7\Omega$

**Answer: D**



**View Text Solution**

**138.** In the circuit as shown in the figure,  
current flowing through  $20\Omega$  resistor is



A.  $\frac{3}{2}A$

B.  $\frac{5}{2}A$

C.  $1A$

D.  $\frac{2}{3}A$

**Answer: A**



**View Text Solution**

**139.** The equivalent resistance between X and Y in the circuit shows is



A.  $10\Omega$

B.  $5\Omega$

C.  $7\Omega$

D.  $14\Omega$

**Answer: C**



**View Text Solution**

**140.** In the following network of 5 branches, the respective currents are  $I_1, I_2, I_3$  etc. Given that  $I_1 = -0.5A, I_4 = 1A$  and  $I_5 = 0.5A,$

the remaining currents are



A.  $I_2 = -1.5A, I_3 = 0.5A, I_6 = 0.5A$

B.  $I_2 = 1.5A, I_3 = -0.5A, I_6 = 0.5A$

C.  $I_2 = 1.5A, I_3 = 0.5A, I_6 = -0.5A$

D.  $I_2 = 1.5A, I_3 = 0.5A, I_6 = 0.5A$

**Answer: B**



**View Text Solution**

141. A circuit is as shown in the figure. Then, the current from A to B is



A.  $+ 500\text{mA}$

B.  $+ 250\text{mA}$

C.  $- 250\text{mA}$

D.  $- 500\text{mA}$

**Answer: B**



**View Text Solution**



**142.** When the switch S is closed in the circuit shown in figure, the current passing through it is



A.  $7.5A$

B.  $3.0A$

C.  $4.5A$

D.  $6.5A$

**Answer: C**



**View Text Solution**

143. In the circuit shown, the current through the  $5\Omega$  resistor is



A.  $\frac{8}{3} A$

B.  $\frac{9}{13} A$

C.  $\frac{4}{13} A$

D.  $\frac{1}{3} A$

**Answer: D**



**144.** In the part of a circuit shown in figure, the potential difference between points G and H ( $V_G - V_H$ ) will be



A. 0 V

B. 12 V

C. 7 V

D. 3 V

**Answer: C**



**View Text Solution**

**145.** In the Wheatstone's network as shown in the figure,  $P = 10\Omega$ ,  $Q = 20\Omega$ ,  $R = 15\Omega$ ,  $S = 30\Omega$  The current passing through the battery of negligible resistance is



A.  $0.36A$

B.  $0A$

C.  $0.18A$

D.  $0.72A$

**Answer: A**



**View Text Solution**

**146.** In the Wheatstone bridge as shown in the figure, in order to balance the bridge, we must have



A.  $R_1 = 3\Omega, R_2 = 3\Omega$

B.  $R_1 = 6\Omega, R_2 = 15\Omega$

C.  $R_1 = 1.5\Omega, R_2 = \text{any finite value}$

D.  $R_1 = 3\Omega, R_2 = \text{any finite value}$

**Answer: D**



**View Text Solution**

**147.** Four resistors are connected as shown in the figure. A 6 V battery of negligible resistance is connected across terminals A and

C. The potential difference across terminals B and D will be



A. 0 V

B. 1.5 V


C. 2 V

D. 3 V

**Answer: A**



**View Text Solution**

148. In a Wheatstone's network,  $P = 2\Omega$ ,  $Q = 2\Omega$ ,  $R = 2\Omega$  and  $S = 3\Omega$ . The resistance with which  $S$  is to be shunted in order that the bridge may be balanced is 

A.  $1\Omega$

B.  $2\Omega$

C.  $4\Omega$

D.  $6\Omega$

**Answer: D**



**Watch Video Solution**



**149.** Consider the following statements regarding the network shown in the figure.



(1) The equivalent resistance of the network between points A and B is independent of value of G.

(2) The equivalent resistance of the network between points A and B is  $\frac{4}{3}R$

(3) The current through G is zero.

Which of the given statements is/are true?

A. (1) alone

B. (2) alone

C. (2) and (3)

D. (1), (2) and (3)

**Answer: D**



**View Text Solution**

**150.** Five equal resistances, each of resistance  $R$ , are connected as shown in figure. A battery of  $V$  volt is connecte between A and B. The

current flowing in FC will be



A.  $\frac{3V}{R}$

B.  $\frac{V}{R}$

C.  $\frac{V}{2R}$

D.  $\frac{2V}{R}$

**Answer: C**



**View Text Solution**

**151.** What is the resistance between the points X and Y of the circuit in the figure? Assume that the resistance of each resistor is 25 ohm.



A. 100 ohm

B. 50 ohm

C. 25 ohm

D. 75 ohm

**Answer: C**



**View Text Solution**

**152.** The resistance in the four arms of a Wheatstone network in cyclic order are  $5\Omega$ ,  $2\Omega$ ,  $6\Omega$  and  $15\Omega$ . If a current of  $2.8\text{ A}$  enters the junction of  $5\Omega$  and  $15\Omega$ , then the current through  $2\Omega$  resistor is

A.  $1.5\text{ A}$

B.  $2.8\text{ A}$

C.  $0.7\text{ A}$

D.  $2.1\text{ A}$

**Answer: D**



**View Text Solution**

**153.** Six resistors each of  $10\Omega$  are connected as shown. The equivalent resistance between points X and Y is



A.  $20\Omega$

B.  $5\Omega$

C.  $\frac{25}{3}\Omega$

D.  $10\Omega$

**Answer: B**



**View Text Solution**

**154.** The resistance to be connected in parallel with  $12\Omega$  resistance in the circuit so that potential difference between B and D is zero is



A.  $6\Omega$

B.  $4\Omega$

C.  $12\Omega$

D.  $3\Omega$

**Answer: B**



**View Text Solution**

**155.** In the circuit, the value of  $I$  is



A.  $0.10A$



B.  $0.20A$

C.  $0.40A$

D.  $0.60A$

**Answer: D**



**View Text Solution**

**156.** Two resistances are connected in two gaps of a metre bridge. The balance point is 20cm from the zero end. A resistance of  $15\Omega$  is connected in series with the smaller of the

two. The null point shifts to 40cm. Then value of the smaller resistance is:

A. 3

B. 6

C. 9

D. 12

**Answer: C**



**Watch Video Solution**

157. In the shown arrangement of the experiment of the metre bridge if AC corresponding to null deflection of galvanometer is  $x$ , what will be its value if the radius of the wire AB is doubled?



A.  $x / 2$

B.  $x / 4$

C.  $4x$

D.  $x$

**Answer: D**



**View Text Solution**

**158.** With two resistance  $R_1$  and  $R_2$  ( $> R_1$ ) in the two gaps of a metre bridge the balance was found to be  $1/3$  m from the zero end. When a  $6\Omega$  resistance is connected in series with the smaller of the two resistance, the point is shifted to  $2/3$  m from the same end, then  $R_1$  and  $R_2$  are

A. 4, 2

B. 2, 4

C. both (a) and (b)

D. neither (a) nor (b)

**Answer: B**



**Watch Video Solution**

**159.** A resistance of  $2\Omega$  is connected across one gap of a metre-bridge (the length of the wire is 100 cm) and an unknown resistance,

greater than  $2\Omega$ , is connected across the other gap. When these resistances are interchanged, the balance point shifts by 20 cm. Neglecting any corrections, the unknown resistance is

A.  $3\Omega$

B.  $4\Omega$

C.  $5\Omega$

D.  $6\Omega$

**Answer: A**



**Watch Video Solution**

**160.** In a metre bridge experiment, resistance are connected as shown in the figure. The balancing length  $l_1$  is 55 cm. Now an unknown resistance  $x$  is connected in series with P and the new balancing length is found to be 75 cm.

The value of  $x$  is



A.  $\frac{54}{13} \Omega$

B.  $\frac{20}{11} \Omega$

C.  $\frac{48}{11} \Omega$

D.  $\frac{11}{48} \Omega$

**Answer: C**



**View Text Solution**

**161.** Show that the percentage error in the measurement of resistance by a metre bridge is minimum when the null point is near about the centre of the wire.

A. 0 cm



B. 20 cm

C. 50 cm

D. 100 cm

**Answer: C**



**Watch Video Solution**

**162.** A potentiometer wire of length 200 cm has a resistance of  $20\Omega$ . It is connected in series with a resistance of  $10\Omega$  and an accumulator of emf 6 V having negligible

internal resistance. A source of 2.4 V is balanced against a length  $L$  of the potentiometer wire. The value of  $L$  is



- A. 100 cm
- B. 120 cm
- C. 110 cm
- D. 140 cm

**Answer: B**



**View Text Solution**

**163.** A potentiometer wire of length 100 cm has a resistance of  $100\Omega$  it is connected in series with a resistance and a battery of emf 2 V and of negligible internal resistance. A source of emf 10 mV is balanced against a length of 40 cm of the potentiometer wire. what is the value of the external resistance?

A.  $790\Omega$

B.  $890\Omega$

C.  $990\Omega$

D.  $1090\Omega$

**Answer: A**



**Watch Video Solution**

**164.** The potential gradient long the length of a uniform wire is  $10\text{volt} / \text{meter}$ .  $B$  and  $C$  are the two points at  $30\text{cm}$  and  $60\text{cm}$  point on a meter scale fitted along the wire. The potential difference between  $B$  and  $C$  will be

A. 3 volt

B. 0.4 volt

C. 7 volt

D. 4 volt

**Answer: A**



**Watch Video Solution**

**165.** Figure shows a potentiometer using a cell C of emf 2 V and internal resistance  $0.5\Omega$  connected to a wire AB. A standard cell  $C_1$  of a constant emf of  $1.02V$  gives a balance point

at 51 cm of the wire. When  $C_1$  is replaced by a cell of emf , the balance point is obtained at 75 cm. What is the value of E?



A. 1.25 V

B. 1.5 V

C. 1.75 V

D. 2.0 V

**Answer: B**



**View Text Solution**

**166.** A potentiometer wire 10 long has a resistance of  $40\Omega$ . It is connected in series with a resistance box and a 2 v storage cell. If the potential gradient along the wire is  $0.01\frac{V}{m}$  the resistance unplugged in the box is

A.  $260\Omega$

B.  $760\Omega$

C.  $960\Omega$

D.  $1060\Omega$

**Answer: B**



**Watch Video Solution**

**167.** In a potentiometer experiment the balancing with a cell is at length 240 cm. On shunting the cell with a resistance of  $2\Omega$ , the balancing length becomes 120 cm. The internal resistance of the cell is

A.  $2\Omega$

B.  $4\Omega$



C.  $0.5\Omega$

D.  $1\Omega$

**Answer: A**



**Watch Video Solution**

**168.** A potentiometer has uniform potential gradient. The specific resistance of the material of the potentiometer wire is  $10^{-7}$  ohm-meter and the current passing through it is 0.1 ampere, cross-section of the wire is

$10^{-6}m^2$ . The potential gradient along the potentiometer wire is

A.  $10^{-4}V/m$

B.  $10^{-6}V/m$

C.  $10^{-2}V/m$

D.  $10^{-8}V/m$

**Answer: C**



**Watch Video Solution**

**169.** In a potentiometer of 10 wires, the balance point is obtained on the 7<sup>th</sup> wire. To shift the balance point to 9<sup>th</sup> wire, we should

- A. decrease resistance in the main circuit
- B. increase resistance in the main circuit
- C. decrease resistance in series with the cell whose emf is to be measured
- D. increase resistance in series with the cell whose emf is to be determined

**Answer: D**



**View Text Solution**

**170.** In a potentiometer experiment, when three cells A, B and C are connected in series, the balancing length is found to be 740 cm. If A and B are connected in series, balancing length is 440 cm and for B and C connected in series, it is 540 cm. The emf of  $E_A$ ,  $E_B$  and  $E_C$  are respectively (in volts)

A. 1, 1.2 and 1.5

B. 1, 2 and 3

C. 1.5, 2 and 3

D. 1.5, 2.5 and 3.5

**Answer: A**



**Watch Video Solution**

**171.** A cell can be balanced against  $110\text{cm}$  and  $100\text{cm}$  of potentiometer wire, respectively with and without being short circuited

through a resistance of  $10\Omega$ . Its internal resistance is

A. 2.0 ohm

B. zero

C. 1.0 ohm

D. 0.5 ohm

**Answer: C**



**Watch Video Solution**

172. The accurate measurement of emf can be obtained using.

A. multimeter

B. voltmeter

C. voltameter

D. potentiometer

**Answer: D**



**Watch Video Solution**

**173.** Two resistors whose value are in ratio 2:1 are connected in parallel with one cell. Then ratio of power dissipated is

A. 2:1

B. 4:1

C. 1:2

D. 1:1

**Answer: C**



**Watch Video Solution**



174. Two bulbs of 500W and 300W are manufactured to operate on a 220V line. If their resistances are  $R_1$  and  $R_2$  respectively then value of  $\frac{R_1}{R_2}$  is

A.  $5/3$

B.  $3/5$

C.  $25/9$

D.  $9/25$

**Answer: B**



**Watch Video Solution**

**175.** Time taken by a 836 W heater to heat one litre of water from  $10^{\circ} C \rightarrow 40^{\circ} C$  is

A. 50s

B. 100s

C. 150s

D. 200s

**Answer: C**



**Watch Video Solution**

**176.** A wire when connected to 220 V mains supply has power dissipation  $P_1$ . Now, the wire is cut into two equal pieces which are connected in parallel to same supply. Power dissipation in this case is  $P_2$ . Then,  $P_1 : P_2$  is

A. 1

B. 2

C. 3

D. 4

**Answer: D**



Watch Video Solution

177. Figure shows three resistors configurations  $R_1$ ,  $R_2$  and  $R_3$  connected to 3 V battery. If the power dissipated by the configurations  $R_1$ ,  $R_2$  and  $R_3$  is  $P_1$ ,  $P_2$  and  $P_3$  respectively, then



A.  $P_1 > P_2 > P_3$

B.  $P_1 > P_3 > P_2$

C.  $P_2 > P_1 > P_3$

$$D. P_3 > P_2 > P_1$$

**Answer: C**



**View Text Solution**

**178.** A current of 3 A flows through the  $2\Omega$  resistor shown in the circuit below. The power dissipated in the  $5\Omega$  resistor is



**A. 1 W**

B. 5 W

C. 4 W

D. 2 W

**Answer: B**



**View Text Solution**

**179.**  $n$  identical light bulbs, each designed to draw  $P$  power from a certain voltage supply, are joined in series across that supply. The total power which they will draw is

A.  $nP$

B.  $P$

C.  $\frac{P}{n}$

D.  $\frac{P}{n^2}$

**Answer: C**



**Watch Video Solution**

**180.** Consider a cylindrical element as shown in figure. Current flowing through the element is  $I$  and resistivity of material of the cylinder is  $\rho$ .

Choose the correct option out of the following.



- A. Power loss in second half is four times the power loss in first half
- B. Voltage drop in first half is twice of voltage drop in second half
- C. Current density in both halves is equal
- D. Electric field in both halves is equal

**Answer: A**





[View Text Solution](#)

**181.** An electric heating element consumes 500 W when connected to a 100 V line. If the line voltage becomes 150 V, the power consumed will be

- A. 500 W
- B. 750 W
- C. 1000 W
- D. 1125 W

**Answer: D**



**Watch Video Solution**

**182.** An electric kettle takes  $4A$  current at  $220V$ . How much time will it take to boil  $1kg$  of water from temperature  $20^{\circ}C$ ? The temperature of boiling water is  $100^{\circ}C$

A. 12.6 min

B. 4.2 min

C. 6.3 min

D. 8.4 min

**Answer: C**



**Watch Video Solution**

**183.** Five equal resistors when connected in series dissipated 5 W power. If they are connected in parallel, the power dissipated will be

A. 25 W

B. 50 W

C. 100 W

D. 125 W

**Answer: D**



**Watch Video Solution**

**184.** The total power dissipated in watts in the circuit shown in figure is



A. 40

B. 54

C. 4

D. 16

**Answer: B**



**View Text Solution**

**185.** A source of emf having internal resistance of  $6\Omega$  dissipates maximum power in a circuit consisting of three resistors  $R_1$ ,  $R_2$  and  $R_3$

as shown. Then



A.  $V = 24V, I_3 = 0.8A$

B.  $V = 6V, I_3 = 0.4A$

C.  $V = 4V, I_3 = 0.8A$

D.  $V = 24V, I_3 = 0.4A$

**Answer: A**



**View Text Solution**

**186.** Consider four circuits shown in the figure below. In which circuit power dissipated is greatest (Neglect the internal resistance of the power supply)?

A. 

B. 

C. 

D. 

**Answer: A**



Watch Video Solution

**187.** Resistances  $P$ ,  $Q$ ,  $S$  and  $R$  are arranged in a cyclic order to form a balanced Wheatstone's bridge network. The ratio of power consumed in the branches  $(P + Q)$  and  $(R + S)$  is

A.  $1 : 1$

B.  $R : P$

C.  $P^2 : Q^2$

D.  $P^2 : R^2$



**Answer: B**



**View Text Solution**

**188.** An electric bulb rated for  $500W$  at  $100V$  is used in a circuit having a  $200V$  supply. The resistance  $R$  that must be put in series with bulb, so that the bulb delivers  $500W$  is ..... $\Omega$ .

A.  $10\Omega$

B.  $15\Omega$

C.  $20\Omega$

D.  $25\Omega$

**Answer: C**



**Watch Video Solution**

**189.** A rise of temperature of  $4^\circ C$  is observed in a conductor by passing a current. If the current is tripled, the rise of temperature will be

A.  $8^\circ C$

B.  $12^{\circ} C$

C.  $16^{\circ} C$

D.  $36^{\circ} C$

**Answer: D**



**Watch Video Solution**

**190.** Two electric bulbs marked 40 W, 220 V and 60 W, 220 V when connected in series, across same voltage supply of 220 V, the effective

power is  $P_1$  and when connected in parallel, the effective power is  $P_2$ . Then  $\frac{P_1}{P_2}$  is

A. 0.5

B. 0.48

C. 0.24

D. 0.16

**Answer: C**



**View Text Solution**

**191.** Two lamps, one rated 40 W at 220 V and the other 100 W at 220 V, are connected in parallel to the electric supply at 220V.

(a) Draw a circuit diagram to show the connections.

(b) Calculate the current drawn from the electric supply.

(c) Calculate the total energy consumed by the two lamps together when they operate for one hour.

A. 25 W

B. 14 W

C. 60 W

D. 100 W

**Answer: B**



**Watch Video Solution**

**192.** Two identical cells each of emf  $\varepsilon$ , having negligible internal resistance  $r$ , are connected in parallel with each other across an external

resistance  $R$ . What is the current through this resistance.

A.  $R = r / 2$

B.  $R = r$

C.  $R = r / 3$

D.  $R = 2r$

**Answer: A**



**Watch Video Solution**

**193.** A battery of internal resistance  $4\Omega$  is connected to the network of resistance as shown in the figure.



In order to give the maximum power to the network, the value of R should be

A.  $\frac{4}{9}\Omega$

B.  $\frac{8}{9}\Omega$

C.  $\frac{39}{7}\Omega$

D.  $\frac{11}{7}\Omega$



**Answer: C**



**View Text Solution**

**194.** Masses of three are in the ratio  $1:3:5$  their lengths are in the ratio  $5:3:1$  when they are connected in series to an external source, the amounts of heats produced in them are in the ratio

A.  $5:9:5$

B.  $25:9:1$

C. 125: 15: 1

D. 25: 15: 9

**Answer: C**



**Watch Video Solution**

**195.** An electric bulb marked as 50 W-200 V is connected across a 100 V supply. The present power of the bulb is

A. 37.5 W

B. 25 W

C. 12.5 W

D. 10 W

**Answer: C**



**Watch Video Solution**

**196.** Heat is produced at a rate given by  $H$  in a resistor when it is connected across a supply of voltage  $V$ . If now the resistance of the resistor is doubled and the supply voltage is

made  $V/3$  then the production of heat in the resistor will be

A.  $\frac{H}{18}$

B.  $\frac{H}{9}$

C.  $6H$

D.  $18H$

**Answer: A**



**View Text Solution**

**197.** Two electric bulbs marked 25W-220V and 100W-220V are connected in series to a 440 V supply. Which of the bulbs will fuse ?

- A. 100 W
- B. 25 W
- C. neither
- D. both

**Answer: B**



**Watch Video Solution**

**198.** A line having a total resistance of  $0.2\Omega$  delivers  $10\text{kW}$  at  $220\text{V}$  to a small factory. Calculate the efficiency of the transmission.

A. 0.65

B. 0.75

C. 0.85

D. 0.95

**Answer: D**



**Watch Video Solution**

**199.** Three electric bulbs of 200 W, 200 W and 400 W are shown in figure. The resultant power of the combination is



A. 800 W

B. 400 W

C. 200 W

D. 600 W

**Answer: C**



**View Text Solution**

## Check Your Neet Vitals

1. In an atom electrons revolves around the nucleus along a path of radius  $0.72\text{\AA}$ ... making  $9.4 \times 10^{18}$  revolution per second. The equivalent current is ( $e = 1.6 \times 10^{-19}C$ )

A. 1.2 A

B. 1.5 A

C. 1.4 A



D. 1.8 A

**Answer: B**



**Watch Video Solution**

2. A battery of emf 15 V and internal resistance of  $4\Omega$  is connected to a resistor. If the current in the circuit is 2A and the circuit is closed. Resistance of the resistor and terminal voltage of the battery will be

A.  $2.5\Omega$ , 6V

B.  $3.5\Omega$ ,  $6V$

C.  $2.5\Omega$ ,  $7V$

D.  $3.5\Omega$ ,  $7V$

**Answer: D**



**Watch Video Solution**

**3.** The resistance of the wire in the platinum resistance thermometer at ice point is  $5\Omega$  and at steam point is  $5.25\Omega$ . When the thermometer is inserted in an unknown hot

bath its resistance is found to be  $5.5\Omega$ . The temperature of the hot bath is

A.  $200^{\circ}C$

B.  $80^{\circ}C$

C.  $30^{\circ}C$

D.  $85^{\circ}C$

**Answer: B**



**Watch Video Solution**

4. An electric heater is connected to the voltage supply. After few seconds Current gets its steady value then its initial current will be

- A. equal to its steady current
- B. slightly higher than its steady current
- C. slightly less than its steady current
- D. zero

**Answer: A**



**Watch Video Solution**

5. A cylindrical rod is reformed to half of its original length keeping volume constant. If its resistance before this change were  $R$ , then the resistance after reformation of rod will be

A.  $R$

B.  $\frac{R}{4}$

C.  $\frac{3R}{4}$

D.  $\frac{R}{2}$

**Answer: B**



**Watch Video Solution**

6. A copper wire is stretched to make it 0.1 % longer. What is the percentage change in its resistance?

- A. increase by 0.05%
- B. increase by 0.2%
- C. decrease by 0.2%
- D. decrease by 0.05%

**Answer: B**



7. When a current of 2 A flows in a battery from negative to positive terminal, the potential difference across it is 20 V. If a current of 3 A flowing in the opposite direction produces a potential difference of 25 V, the emf of the battery is

A. 20 V

B. 22 V

C. 15.5 V

D. 14 V

**Answer: B**



**Watch Video Solution**

**8.** Three resistances  $2\Omega$ ,  $4\Omega$ ,  $5\Omega$  are combined in series and this combination is connected to a battery of 12 V emf and negligible internal resistance. The potential drop across these resistances are

A. (5.45, 4.36, 2.18)V



B. (2.18, 5.45, 4.36)V

C. (4.36, 2.18, 5.45)V

D. (2.18, 4.36, 5.45)V

**Answer: D**



**Watch Video Solution**

9. A copper cylindrical tube has inner radius  $a$  and outer radius  $b$ . The resistivity is  $\rho$ . The resistance of the cylinder between the two ends is

A.  $\frac{\rho l}{b^2 - a^2}$

B.  $\frac{\rho l}{2\pi(b - a)}$

C.  $\frac{\rho l}{\pi(b^2 - a^2)}$

D.  $\frac{\pi(b^2 - a^2)}{\rho l}$

**Answer: C**



**Watch Video Solution**

**10.** If voltage across a bulb rated 220 V, 160 W drops by 3% of its rated value, the percentage

of the rated value by which the power would decrease is

A. 0.2

B. 0.025

C. 0.06

D. 0.1

**Answer: C**



**Watch Video Solution**

11.  $n$  resistors each of resistance  $R$  first combine to give maximum effective resistance and then combine to give minimum. The ratio of the maximum resistance is

A.  $n$

B.  $n^2$

C.  $n^2 - 1$

D.  $n^3$

**Answer: B**



Watch Video Solution

12. The resistivity of alloy manganin is

A. Nearly independent of temperature

B. Increase rapidly with increase in temperature

C. Decrease with increase in temperature

D. Increase rapidly with decrease in temperature

**Answer: A**



**Watch Video Solution**

**13.** A potentiometer wire of length 100 cm has a resistance of  $100\Omega$  it is connected in series with a resistance and a battery of emf 2 V and of negligible internal resistance. A source of emf 10 mV is balanced against a length of 40 cm of the potentiometer wire. what is the value of the external resistance?

A.  $790\Omega$

B.  $890\Omega$

C.  $990\Omega$

D.  $1090\Omega$

**Answer: A**



**Watch Video Solution**

**14.** A boy has two spare light bulbs in his drawer. One is market 220V and 100W and the other is market 240V and 60W. He tries to

decide which of the following assertions are correct?

A. The 60 W light bulb has more resistance  
and therefore burns less brightly

B. The 60 W light bulb has less resistance  
and therefore burns less brightly

C. The 100 W bulb has more resistance and  
therefore burns more brightly

D. The 100 W bulb has less resistance and  
therefore burns less brightly



**Answer: A**



**Watch Video Solution**

**15.** In a potentiometer a cell of emf 1.5 V gives a balanced point at 32 cm length of the wire. If the cell is replaced by another cell then the balance point shifts to 65 cm. Then the emf of second cell is

A. 3.05 V

B. 2.05 V

C. 4.05 V

D. 6.05 V

**Answer: A**



**Watch Video Solution**

**16.** In a potentiometer the balancing with a cell is at length of 220cm. On shunting the cell with a resistance of  $3\Omega$  balance length becomes 130cm. What is the internal resistance of this cell.

A.  $4.5\Omega$

B.  $7.8\Omega$

C.  $6.3\Omega$

D.  $2.08\Omega$

**Answer: D**



**Watch Video Solution**

**Mcqs Aipmt Neet**

1. A potentiometer circuit is set up as shown. The potential gradient, across the potentiometer wire, is  $k$  volt/cm and the ammeter, present in the circuit, reads  $1.0$  A when two way key is switched off. The balance points, when the key between the terminals (i) 1 and 2 (ii) 1 and 3, is plugged in, are found to be at lengths  $l_1$  cm and  $l_2$  cm respectively. The magnitudes, of the resistors  $R$  and  $X$ , in ohms, are equal, respectively, to



A.  $k(l_2 - l_1)$  and  $kl_2$

B.  $kl_1$  and  $k(l_2 - l_1)$

C.  $k(l_2 - l_1)$  and  $kl_1$

D.  $kl_1$  and  $kl_2$

**Answer: B**



**View Text Solution**

**2.** Consider the following two statement.

(A) Kirchhoff's junction law follows from the conservation of charge.

(B) Krichhoff's loop law follows from the conservation of energy.

Which of the following is correct ?

- A. Both (A) and (B) is wrong
- B. (A) is correct and (B) is wrong
- C. (A) is wrong and (B) is correct
- D. Both (A) and (B) are correct

**Answer: D**



**Watch Video Solution**

3. A current of  $2A$  flows through a  $2\Omega$  resistor when connected across a battery. The same battery supplies a current of  $0.5A$  when connected across a  $9\Omega$  resistor. The internal resistance of the battery is

A.  $0.5\Omega$

B.  $1/3\Omega$

C.  $1/4\Omega$

D.  $1\Omega$

**Answer: B**



Watch Video Solution

4. If power dissipated in the  $9\Omega$  resistor in the circuit shown is 36 watt, the potential difference across the  $2\Omega$  resistor is



- A. 4 volt
- B. 8 volt
- C. 10 volt
- D. 2 volt



**Answer: C**



**View Text Solution**

5. In the circuit shown in the figure, if the potential at point A is taken to be zero, the potential at point B is



A.  $+1V$

B.  $-1V$

C.  $+2V$

D.  $-2V$

**Answer: A**



**View Text Solution**

6. In the circuit shown, the cells A and B have negligible resistance. For  $V_A = 12V$ ,  $R_1 = 500\Omega$  and  $R = 100\Omega$ , the galvanometer (G) shows no deflection. The value of  $V_B$  is



A.  $4V$

B.  $2V$

C.  $12V$

D.  $6V$

**Answer: B**



[View Text Solution](#)

7. If voltage across a bulb rated 22 volt 100 watt drops by 2.5% of its rated value, the

percentage of the rated value by which the power would decrease is

A. 20 %

B. 2.5 %

C. 5 %

D. 10 %

**Answer: C**



**Watch Video Solution**

8. The power dissipated in the circuit shown in the figure is 30 watts. The value of R is



A.  $20\Omega$

B.  $15\Omega$

C.  $10\Omega$

D.  $30\Omega$

**Answer: C**



**View Text Solution**

9. A cell having an emf  $\varepsilon$  and internal resistance  $r$  is connected across a variable external resistance  $R$ . As the resistance  $R$  is increased, the plot of potential difference  $V$  across  $R$  is given by

A. 

B. 

C. 

D. 

**Answer: C**



Watch Video Solution

10. The resistance of the four arms  $P, Q, R$  and  $S$  in a Wheatstone's bridge are  $10\text{ohm}$ ,  $30\text{ohm}$  and  $90\text{ohm}$  respectively. The e.m.f. and internal resistance of the cell are  $7\text{vo}$  and  $5\text{ohm}$  respectively. If the galvanometer resistance is  $50\text{ohm}$ , the current drawn for the cell will be

A.  $0.1A$

B.  $2.0A$

C.  $1.0A$

D.  $0.2A$

**Answer: D**



**Watch Video Solution**

**11.** The internal resistance of a  $2.1V$  cell which gives a current  $0.2A$  through a resistance of  $10\Omega$

A.  $0.8\Omega$



B.  $1.0\Omega$

C.  $0.2\Omega$

D.  $0.5\Omega$

**Answer: D**



**Watch Video Solution**

**12.** A wire of resistance  $4\Omega$  is stretched to twice its original length. The resistance of stretched wire would be

A.  $8\Omega$

B.  $16\Omega$

C.  $2\Omega$

D.  $4\Omega$

**Answer: B**



**Watch Video Solution**

**13.** Two cities are 150 km apart. Electric power is sent from one city to another city through copper wires. The fall of potential per km is 8

volt and the average resistance per km is  $0.5\Omega$ .

The power loss in the wire is

A. 19.2 W

B. 19.2 W

C. 12.2 W

D. 12.2 W

**Answer: B**



**Watch Video Solution**

14. The resistance in the two arms of the meter bridge are  $5\Omega$  and  $R\omega$  respectively. When the resistance R is shunted with an equal resistance, the new balance point is at  $1.6l_1$ . The resistance R is



A.  $10\Omega$

B.  $15\Omega$

C.  $20\Omega$

D.  $25\Omega$

**Answer: B**



**View Text Solution**

**15.** A potentiometer circuit has been setup for finding. The internal resistance of a given cell. The main battery used a negligible internal resistance. The potentiometer wire itself is  $4m$  long. When the resistance,  $R$ , connected across the given cell, has value of

(i) Infinity  $9.5\Omega$ ,

(ii) the 'balancing length' , on the

potentiometer wire are found to be  $3m$  and  $2.85m$ , respectively.

The value of internal resistance of the cell is

A.  $0.25\Omega$

B.  $0.95\Omega$

C.  $0.5\Omega$

D.  $0.75\Omega$

**Answer: C**



**Watch Video Solution**

16. A, B and C are voltmeters of resistance  $R$ ,  $1.5R$  and  $3R$  respectively as shown in the figure. When some potential difference is applied between X and Y, the voltmeter readings are  $V_A$ ,  $V_B$  and  $V_C$  respectively. Then



A.  $V_A = V_B \neq V_C$

B.  $V_A \neq V_B \neq V_C$

C.  $V_A = V_B = V_C$

D.  $V_A \neq V_B = V_C$

**Answer: C**



**View Text Solution**

**17.** Across a metallic conductor of non-uniform cross section a constant potential difference is applied. The quantity which remains constant along the conductor is

A. drift velocity

B. electric field

C. current density



D. current

**Answer: D**



**Watch Video Solution**

**18.** A potentiometer wire has length  $4m$  and resistance  $8\Omega$ . The resistance that must be connected in series with the wire and an accumulator of e.m.f.  $2V$ , so as to get a potential gradient  $1mV$  per cm on the wire is

A.  $44\Omega$

B.  $48\Omega$

C.  $32\Omega$

D.  $40\Omega$

**Answer: C**



**Watch Video Solution**

**19.** Two metal wires of identical dimensions are connected in series. If  $\sigma_1$  and  $\sigma_2$  are the conductivities of the metal wires respectively, the effective conductivity of the combination is

A.  $\frac{\sigma_1 + \sigma_2}{\sigma_1\sigma_2}$

B.  $\frac{\sigma_1\sigma_2}{\sigma_1 + \sigma_2}$

C.  $\frac{2\sigma_1\sigma_2}{\sigma_1 + \sigma_2}$

D.  $\frac{\sigma_1 + \sigma_2}{2\sigma_1\sigma_2}$

**Answer: C**



**Watch Video Solution**

**20.** A circuit contains an ammeter, a battery of  $30V$  and a resistance  $40.8\text{ohm}$  all connected in series. If the ammeter has a coil of

resistance  $480\text{ohm}$  and a shunt of  $20\text{ohm}$ , the reading in the ammeter will be

A.  $2A$

B.  $1A$

C.  $0.5A$

D.  $0.25A$

**Answer: C**



**Watch Video Solution**

21. A potentiometer wire of Length  $L$  and a resistance  $r$  are connected in series with a battery of e.m.f.  $E_0$  and a resistance  $r_1$ . An unknown e.m.f.  $E$  is balanced at a length  $l$  of the potentiometer wire. The e.m.f.  $E$  will be given by :

A.  $\frac{E_0 l}{L}$

B.  $\frac{LE_0 r}{(r + r_1)l}$

C.  $\frac{LE_0 r}{lr_1}$

D.  $\frac{E_0 r}{(r + r_1)} \cdot \frac{l}{L}$

**Answer: D**



**Watch Video Solution**

**22.** A potentiometer wire is  $100\text{cm}$  long and a constant potential difference is maintained across it. Two cells are connected in series first to support one another and then in opposite direction. The balance points are obtained at  $50\text{cm}$  and  $10\text{cm}$  from the positive end of the wire in the two cases. The ratio of emfs is:

A. 3:4

B. 3:2

C. 5:1

D. 5:4

**Answer: B**



**Watch Video Solution**

**23.** In Fig. 6,  $l$  and  $m$  are two parallel tangents to a circle with centre  $O$ , touching the circle at  $A$  and  $B$  respectively. Another tangent at  $C$

intersects the line at D and in at E. Prove that

$\angle ZDOE = 90^\circ$ .

A.  $\frac{a^3 R}{2b}$

B.  $\frac{a^3 R}{b}$

C.  $\frac{a^3 R}{6b}$

D.  $\frac{a^3 R}{3b}$

**Answer: C**



**Watch Video Solution**



24. The potential difference ( $V_A - V_B$ ) between the points A and B in the given figure is



A.  $-3V$

B.  $+3V$

C.  $+6V$

D.  $+9V$

**Answer: D**



**View Text Solution**

25. A filament bulb ( $500W, 100V$ ) is to be used in a  $230V$  main supply. When a resistance  $R$  is connected in series, it works perfectly and the bulb consumes  $500W$ . The value of  $R$  is

A.  $230\Omega$

B.  $46\Omega$

C.  $26\Omega$

D.  $13\Omega$

**Answer: C**



**Watch Video Solution**

**26.** The resistance of a wire is  $r$  ohm. If it is melted and stretched to  $n$  times its original length , its new resistance will be

A.  $R/n$

B.  $n^2 R$

C.  $R/n^2$

D.  $nR$

**Answer: B**



**Watch Video Solution**

27. A potentiometer is an accurate and versatile device to make electrical measurements of  $E.M.F.$  because the method involves

A. potential gradients

B. a condition of no current flow through the galvanometer

C. a combination of cells, galvanometer  
and resistances

D. cells

**Answer: B**



**Watch Video Solution**

**28.** A set of ' $n$ ' equal resistor, of value of ' $R$ ' each are connected in series to a battery of emf ' $E$ ' and internal resistance ' $R$ '. The current drawn is  $I$ . Now, the ' $n$ ' resistors are

connected in parallel to the same battery.

Then the current drawn from battery becomes

10.1. The value of ' $n$ ' is

A. 10

B. 11

C. 20

D. 9

**Answer: A**



**Watch Video Solution**

29. A battery consists of a variable number  $n$  of identical cells having internal resistance connected in series. The terminals of the battery are short circuited and the current  $I$  measured. Which one of the graph below shows the correct relationship between  $I$  and  $n$ ?

A. 

B. 

C. 

D. 

**Answer: A**



**Watch Video Solution**

**30.** A carbon resistor of  $(47 \pm 4.7)k\Omega$  is to be marked with rings of different colours for its identification. The colour code sequence will be

A. Violet - Yellow - Orange - Silver

B. Yellow - Violet - Orange - Silver

C. Yellow - Green - Violet - Gold



D. Green - Orange - Violet - Gold

**Answer: B**



**Watch Video Solution**

**31.** which of the following acts as a circuit protection device?

A. fuse

B. conductor

C. inductor

D. switch

**Answer: A**



**Watch Video Solution**

**32.** Six similar bulbs are connected as shown in the figure with a DC source of emf  $E$ , and zero internal resistance. The ratio of power consumption by the bulbs when (i) all are glowing and (ii) in the situation when two from section A and one from section B are

glowing, will be



A. 2:1

B. 4:9

C. 9:4

D. 1:2

**Answer: B**



**View Text Solution**