



PHYSICS

BOOKS - PUNJAB BOARD PREVIOUS YEAR PAPERS

ALTERNATING CURRENTS

Exercise

1. The instantaneous current from A.C.source is $I = 55 \sin 314t$. What is the peak value of current

?



Watch Video Solution

2. What is the peak value of 220V ac ?



Watch Video Solution

3. A 230 V variable frequency source is connected across a series combination of $L = 5H$, $C = 80\mu F$, $R = 40\Omega$

calculate Frequency of the source which
derives the circuit in resonance



[Watch Video Solution](#)

4. A 230 V variable frequency source is
connected across a series combination of
 $L = 5H$, $C = 80\mu F$, $R = 40\Omega$ calculate
Impedence of the circuit at resonance



[Watch Video Solution](#)

5. A 230 V variable frequency source is connected across a series combination of $L = 5H$, $C = 80\mu F$, $R = 40\Omega$ calculate Amplitude of the current at resonance



Watch Video Solution

6. A circuit consists of non inductive resistance of 50Ω , an inductance of 0.3 Henry and a capacitance of 40 microfarad in series and

supplied with a current of 200 V- 50Hz. Find impedance and current in the circuit.



Watch Video Solution

7. A 40Ω resistor, 3m H inductor and $2\mu F$ capacitor are connected in series to 110V, 5000 Hz AC source. Calculate Impedance of the circuit and value of current in the circuit.



Watch Video Solution

8. When an inductor L and resistor R in series are connected across a 12 volts 50 Hertz supply a current of 0.5 ampere flows in the circuit the circuit current differs in phase from applied voltage by $\frac{\pi}{3}$ Calculate the value R .



Watch Video Solution

9. A circuit consist of resistance 10 ohm and capacitance 0.1 microfarad. If an alternating

e.m.f. (electromotive force) of 100 volt and frequency 50 Hertz is applied, calculate the current in the circuit.



Watch Video Solution

10. In a series C- R circuit $R = 30$ ohms $C = 0.25$ microfarad, (μf) e.m.f. (electromotive force) = 100 volts and $\omega = 10,000$ radian/second. Find the current in the circuit and calculate voltage across resistor and the capacitor.



Watch Video Solution

11. A capacitor of capacitance 100μ and a coil of resistance 50Ω and inductance 0.5 henry are connected in series with a source of voltage 110V and frequency 50 hertz. Calculate the current in the circuit.



Watch Video Solution

12. An a.c. source of 200 V , 50 Hz is connected across a 400Ω resistor and capacitor of $25\mu\text{F}$ in series. Calculate reactance



Watch Video Solution

13. An a.c. source of 200 V, 50Hz is connected across a 300Ω resistor and capacitor of $\frac{25}{\pi} \mu F$ in series. Calculate (a) reactance: impedance



Watch Video Solution

14. An a.c. source of 200 V, 50Hz is connected across a 300Ω resistor and capacitor of $\frac{25}{\pi} \mu F$ in series. Calculate (a) reactance: impedance

μF in series. Calculate (a) reactance: current in the circuit.



[Watch Video Solution](#)

15. An a.c. source of 200 V, 50 Hz connected across a 400Ω resistor and an inductor of $\frac{3}{\pi}H$ in series. Calculate impedance



[Watch Video Solution](#)

16. An a.c. source of 200 V, 50 Hz connected across a 400Ω resistor and an inductor of $\frac{3}{\pi}H$ in series. Calculate impedance



Watch Video Solution

17. An a.c. source of 200 V, 50 Hz connected across a 400Ω resistor and an inductor of $\frac{3}{\pi}H$ in series. Calculate current in the circuit.



Watch Video Solution

18. A capacitor of capacitance 100μ and a coil of resistance 50 ohm and inductance 0.5 Henry are connected in series with 110 volt and 50 Hz source. Calculate the impedance of the circuit.



Watch Video Solution

19. A 230 V variable frequency source is connected across a series combination of $L = 5H$, $C = 80\mu F$, $R = 40\Omega$ calculate Frequency of the source which derives the circuit in resonance



[Watch Video Solution](#)

20. A 230 V variable frequency source is connected across a series combination of $L = 5H$, $C = 80\mu F$, $R = 40\Omega$ calculate Impedence of the circuit at resonance



[Watch Video Solution](#)

21. A 230 V variable frequency source is connected across a series combination of

$$L = 5H, C = 80\mu F, R = 40\Omega$$

calculate Amplitude of the current at resonance



Watch Video Solution

22. A series circuit with $L = 0.12H$, $C = 0.48 \text{ mF}$ and $R = 25 \text{ ohm}$, is connected to a $220V$ variable frequency power supply. At what frequency is the circuit current maximum ?



Watch Video Solution

23. A capacitor of unknown value and an inductor of 0.1H and a resistor of 10Ω are connected in series to a 220V , 50Hz ac source. It is found that the power factor of circuit is unity. Calculate the capacitance of capacitor and maximum amplitude of current



Watch Video Solution

24. A $60\mu\text{F}$ capacitor, a 0.3H inductor and a 50Ω resistor are connected in series with a

120V-60Hz a.c. source. Calculate the impedance of the circuit and current flowing in the circuit.



Watch Video Solution

25. A series LCR circuit with $R = 20\Omega$ (Ohm), $L = 1,5\text{H}$ (Henry) and $C = 35\mu\text{F}$ (Micro farad) is connected to a variable frequency 200 V (Volt) a.c. supply. When the frequency of the supply equals the natural frequency of the circuit, what is the average power transferred to the circuit in one complete cycle ?



Watch Video Solution

26. What is the relation between peak value and root mean square value of alternating e.m.f. ?



Watch Video Solution

27. What is the phase relationship between current and voltage in an inductor?



Watch Video Solution

28. What do you mean by power factor of an a.c. circuit ?



Watch Video Solution

29. Define inductive reactance of an inductor.



Watch Video Solution

30. What is Wattless current ?



Watch Video Solution

31. Define capacitive reactance of a capacitor.



Watch Video Solution

32. What is an idle current ?



Watch Video Solution

33. Define impedance of an a.c. circuit.



Watch Video Solution

34. What is the impedance of a circuit ?



Watch Video Solution

35. What is impedance of circuit at resonance ?



Watch Video Solution

36. For a circuit at resonance, voltage applied is $E = E_0 \sin \omega t$ and current is $I = I_0 \sin \omega t$, then power consumption in the circuit is :

A. $\frac{E_0 I_0}{2}$

B. $\frac{E_0 I_0}{\sqrt{2}}$

C. $\sqrt{2} E_0 I_0$

D. 0

Answer:



Watch Video Solution

37. For a circuit at resonance, voltage applied is $E = E_0 \sin \omega t$ and current is $I = I_0 \sin \omega t$, then power consumption in the circuit is :

A. $\frac{E_0 I_0}{2}$

B. $\frac{E_0 I_0}{\sqrt{2}}$

C. $\sqrt{2} E_0 I_0$

D. 0

Answer:



Watch Video Solution

38. Define resonant frequency of LCR series circuit.



Watch Video Solution

39. Which is more dangerous in use :a.c or d.c.
? Explain, why



Watch Video Solution

40. Define root mean square value of an alternating current.



Watch Video Solution

41. The frequency of an ac supply is doubled, what happens to inductive reactance X_L and capacitive reactance X_c ?



Watch Video Solution

42. How does capacitive reactance X_c of a capacitor vary in an a.c. and d.c. circuit ?



Watch Video Solution

43. How does inductive reactance X_L of an inductor vary in d.c. and high frequency a.c. circuit ?



Watch Video Solution

44. Define root mean square value of an alternating current.



Watch Video Solution

45. Derive an our expression for the Power of an L.C.R. alternating current circuit. (Without different cases).



Watch Video Solution

46. Derive the relation for mean or average value of alternating current.



Watch Video Solution

47. An alternating e.m.f is supplied through a pure inductance. Investigate the relationship between current flowing through it and the applied e.m.f.



Watch Video Solution

48. Derive an expression for average power in an LCR a.c. circuit.



Watch Video Solution

49. Prove mathematically that the average value of alternating current over one complete cycle is zero.



Watch Video Solution

50. Derive the expression for the impedance of an a.c. circuit with an inductor 'L', capacitor 'C' and a resistor 'R' in series. What is condition of resonance ?



Watch Video Solution

51. Define root mean square value of an alternating current.



Watch Video Solution

52. What do you mean by the average value of a.c. ? Derive the expression for it.



Watch Video Solution

53. Define root mean square value of an alternating current.



Watch Video Solution

54. With the help of phasor diagram derive an expression for impedance in LCR circuit.



Watch Video Solution

55. Using phasor diagram, derive an expression for impedance of an a.c. circuit containing LCR in series.



Watch Video Solution

56. Define root mean square value of an alternating current.



Watch Video Solution

57. Derive a relation for the average power of an alternating current circuit containing LCR in series. How true power differ from virtual power in a.c. circuit.



Watch Video Solution

58. Derive an expression for average power of an AC (alternating current) circuit.



Watch Video Solution

59. Derive average power associated with pure inductor.



Watch Video Solution

60. Define impedance of an electric circuit. How it differs from ohmic resistance ? Find an expression for the impedance of an a.c. circuit containing L-C-R in series.



Watch Video Solution

61. Define impedance of an electric circuit. How it differs from ohmic resistance ? Find an expression for the impedance of an a.c. circuit containing L-C-R in series.





[Watch Video Solution](#)

62. Derive an expression for average power of an AC (alternating current) circuit.



[Watch Video Solution](#)

63. Find a phase relation between current and voltage in an a.c. circuit containing a pure inductor. Why high frequency current can not passthrough a pure inductor easily ?



[Watch Video Solution](#)

64. Find a phase relation between current and voltage in an a.c. circuit containing a pure capacitance. A pure capacitor blocks direct current, why ?



Watch Video Solution

65. Derive an expression for average power of an AC (alternating current) circuit.



Watch Video Solution

66. What is meant by mean or average value of alternating current ? Show that mean value of ac over a complete cycle is zero.



Watch Video Solution