



## PHYSICS

# BOOKS - CHHAYA PHYSICS (BENGALI ENGLISH)

## ALTERNATING CURRENT

### Examples

1. Equation of an ac is  $I=10 \sin \left( 200\pi t - \frac{\pi}{15} \right)$  ampere. Determine the frequency and peak

value of the current.



[Watch Video Solution](#)

2. If an arc is represented by  $I = 100 \sin 200\pi t$  ampere, determine the peak value of current and time period.



[Watch Video Solution](#)

3. An alternating current having peak value 141 A is used to heat a metal wire. To produce the

same rate of heating effect, another constant current  $I_A$  is used. What is the value of  $I$ ?



[Watch Video Solution](#)

4. The peak value of an alternating magnetic field  $B$  is 0.01 T and Frequency is 100 Hz. IF a conducting ring of radius 1 m is held normal to the field , what emf will be induced in the ring?



[Watch Video Solution](#)

5. In an LCR series ac circuit  $R = 10\Omega$  ,  $L=50$  mH and  $C = 5\mu F$ . Find out the resonant frequency and Q-factor. Find also the bandwidth and half-power frequencies.



[Watch Video Solution](#)

6. In an LCR series combination,  $R=400\Omega$   $L=100$ mH and  $C = 1\mu F$ . This combination is connected to a  $25 \sin 2000t$  volt source. Find the impedance,



[Watch Video Solution](#)



7. In an LCR series combination,  $R=400\Omega$   
 $L=100\text{mH}$  and  $C = 1\mu\text{F}$ . This combination is  
connected to a  $25 \sin 2000t$  volt source. Find  
peak value of current,



[Watch Video Solution](#)

8. In an LCR series combination,  $R=400\Omega$   
 $L=100\text{mH}$  and  $C = 1\mu\text{F}$ . This combination is

connected to a  $25 \sin 2000t$  volt source. Find phase difference of voltage and current



[Watch Video Solution](#)

9. In an LCR series combination,  $R=400\Omega$   
 $L=100\text{mH}$  and  $C = 1\mu\text{F}$ . This combination is connected to a  $25 \sin 2000t$  volt source. Find power factor



[Watch Video Solution](#)

10. In an LCR series combination,  $R=400\Omega$ ,  $L=100\text{mH}$  and  $C = 1\mu\text{F}$ . This combination is connected to a  $25 \sin 2000t$  volt source. Find dissipated power in the circuit.



[Watch Video Solution](#)

11. Power factor of an LR circuit is  $\frac{1}{\sqrt{2}}$ . If the frequency of ac is doubled, what will be the power factor?



[Watch Video Solution](#)

**12.** IF the value of inductor  $L$  is  $1\text{mH}$  and the applied ac source frequency is  $50\text{ Hz}$ , find the inductive reactance in the above case.



[Watch Video Solution](#)

**13.** A series LC circuit has  $L=0.405\text{ H}$  and  $C = 25\mu\text{F}$ . The resistance  $R$  is zero, Find the frequency of resonance.



[Watch Video Solution](#)

**14.** In an LCR series circuit, the rms voltages across R, L and C are found to be 10 V, 10 V and 20 V respectively. The rms voltage across the entire combination is



**Watch Video Solution**

**15.** A capacitor, a resistor of  $5\Omega$  and an inductor of 50mH are in series with an ac source marked 100V,50Hz. It is found that the voltage is in phase with the current. Calculate

the capacitance of the capacitor and the impedance of the circuit.



[Watch Video Solution](#)

**16.** A capacitor and the resistor are connected in series with an ac source. IF the potential differences across C,R are 120 V, 90 V respectively and if the rms current of the circuit is 3A , calculate the impedance.



[Watch Video Solution](#)

17. A capacitor and the resistor are connected in series with an ac source. IF the potential differences across C,R are 120 V, 90 V respectively and if the rms current of the circuit is 3A , calculate the power factor of the circuit.



[Watch Video Solution](#)

18. A  $200\mu F$  capacitor is in series with a  $50\Omega$  resistor and is connected to a 220 V, 50 Hz ac source

- (i) What is the maximum current in the circuit
- (ii) What is the difference in time when the current and the voltage attain maximum values?



[Watch Video Solution](#)

**19.** A resistor,  $R = 300\Omega$  and a capacitor ,  $C = 25\mu F$  are connected in series with an ac source. The peak value of voltage ( $V_0$ ) and the frequency (f) of the source are 150 V and  $\frac{50}{\pi}$  Hz respectively. Find the peak value of



current and the power dissipated in the circuit.



[Watch Video Solution](#)

**20.** A series LCR circuit containing a resistance of  $120\Omega$  has angular resonance frequency  $4 \times 10^5 \text{ rad/s}$ . At resonance, the voltages across resistance and inductance are 60V and 40V, respectively. Find the values of L and C. At what frequency, does not current in the circuit lag behind the voltage by  $45^\circ$ ?



[Watch Video Solution](#)

21. The instantaneous value of emf and current in an A.C. circuit are;  $E=1.414\sin(100\pi t- 4\pi)$  ,  $I=0.707\sin(100\pi t)$  . The impedance of the circuit will be



[Watch Video Solution](#)

22. A 220V, 50Hz ac source is connected to an inductance of 0.2H and a resistance of  $20\Omega$  in series . What is the current in the circuit?



[Watch Video Solution](#)

**23.** An ac source of frequency 50 Hz is connected with a resistance ( $R = 36\Omega$ ) and L of 0.12 H in series. What is the phase different between current and voltage?



[Watch Video Solution](#)

**24.** A current of 1 A flows in a coil when connected to a 100 V dc source. IF the same

coll is connected to a 100 V, 50 Hz ac source, a current of 0.5 A flows in the coll. Calculate the inductance of the coll.



[Watch Video Solution](#)

**25.** A lamp in which 10 A current can flow at 15 V is connected with an alternating source of potential 220 V and frequency 50 Hz. What should be the inductance of choke coll required to light the bulb?



[Watch Video Solution](#)

26. What will be the peak value of the alternating current when a condenser of  $1\mu F$  is connected to an alternating voltage of 200V, 60 Hz?



[Watch Video Solution](#)

27. The number of turns in the primary and secondary coils of an ideal transformer are 140 and 280, respectively. If the current through

the primary coils is 4 A, what will be the current in the secondary coil?



[Watch Video Solution](#)

**28.** Initial voltage and input power of a transformer of efficiency 80 % are 100 V and 4 kW, respectively. IF the voltage of the secondary coil is 200 V, determine the currents flowing through the primary and the secondary coils?



[Watch Video Solution](#)

## High Order Thinking Skill Hots Questions

1. In an oscillating LC circuit the maximum charge on the capacitor is  $Q$ . When the charge is stored equally between the electric and magnetic fields, what is the charge on the capacitor?



[Watch Video Solution](#)

2. In the LCR circuit, capacitance is changed from  $C$  to  $2C$ . For the resonant frequency to remain unchanged what should be the change in the value of inductance  $L$ ?



[Watch Video Solution](#)

3. If the emf of an ac circuit be  $E = E_0 \sin \omega t$  and current  $I = I_0 \cos \omega t$ , what is the power dissipated in the circuit?



[Watch Video Solution](#)



4. What should be the nature of the graph of the impedance  $Z$  with respect to frequency in an alternating LCR circuit?



[Watch Video Solution](#)

5. How does the wattless current conforms to the particle of energy conservation?



[Watch Video Solution](#)

6. The current through a circuit is given by  $I = I_0 \sin(\omega t + \pi/6)$  when the supplied emf is  $V = V_0 \sin \omega t$ . Find the power dissipated in the circuit in one complete cycle. Draw the phasor diagram for the given current and voltage. What are the possible two elements in the circuit?



[Watch Video Solution](#)

7. How the resistance  $R$  changes with the change in frequency of ac? Show graphically.



[Watch Video Solution](#)

8. Sketch a graph to show how the reactance of an inductor varies as a function of frequency.



[Watch Video Solution](#)

9. Sketch a graph to show how the reactance of a capacitor varies as a function of frequency.



[Watch Video Solution](#)

**10.** How does an inductor behave in a dc circuit?



**Watch Video Solution**

**11.** Comparing the L-C oscillations with the oscillations of a spring-block system



**Watch Video Solution**

12. In the given circuit, the switch  $K_2$  is opened and the switch  $K_1$  is closed at time  $t=0$ . At time  $t = t_0$ , the switch  $K_1$  is opened and the switch  $K_2$  is simultaneously closed. Sketch the variation of the inductor current  $I$  with time.



**Watch Video Solution**

**13.** Show that in the free oscillations of an LC circuit, the sum of energies stored in the capacitor and the inductor is constant in time.



**Watch Video Solution**

## **Ncert Textbook Questions With Answer Hint**

**1.**  $60\mu F$  capacitor to a 110 V, 60 Hz ac supply.

Determine the rms value of the current in the

circuit. What is the net power absorbed by the circuit over a complete cycle?



[Watch Video Solution](#)

2. Determine the resonant frequency  $\omega_r$  of a series LCR circuit with  $L=2.0\text{ H}$ ,  $C=32\mu\text{F}$  and  $R=10\Omega$ . What is the Q-value of this circuit?



[Watch Video Solution](#)

3. A charged  $30\mu F$  capacitor is connected to a 27mH inductor.

What is the angular frequency of free oscillations of the circuit?



[Watch Video Solution](#)

4. A charged  $30\mu F$  capacitor is connected to a 27mH inductor.

If the initial charge on the capacitor is 6mC then What is the total energy stored in the



circuit initially. What is the total energy at a later time?



[Watch Video Solution](#)

5. A series LCR circuit with  $R=20\Omega$  ,  $L=1.5\text{ H}$  and  $C=35\mu\text{F}$  is connected to a variable frequency 200 V ac supply. When the frequency of the supply equals the natural frequency of the circuit, what is the average power transferred to the circuit in one complete cycle?



[Watch Video Solution](#)

6. A radio can tune over the frequency range of a portion of MW broadcast band: 800kHz to 1200kHz. IF its LC circuit has an effective inductance of  $200\mu H$ , what must be the range of the variable capacitor?

[Hint: for tuning, the natural frequency of the LC circuit should be equal to the frequency of the radio wave.]



**Watch Video Solution**

7. A series LCR circuit is connected to a variable frequency 230 V source ,  $L=5.0$  H,  
 $C = 80\mu F$ ,  $R = 40\Omega$

Determine the source frequency for which resonance occurs in the circuit.



[Watch Video Solution](#)

8. A series LCR circuit is connected to a variable frequency 230 V source ,  $L=5.0$  H,  
 $C = 80\mu F$ ,  $R = 40\Omega$

Obtain impedance of the circuit and amplitude of current at resonance.



[Watch Video Solution](#)

9. A series LCR circuit is connected to a variable frequency 230 V source ,  $L=5.0$  H,

$$C = 80\mu F, R = 40\Omega$$

Determine the rms potential drop across L and

C. Show that at resonance the potential drop

across LC combination is zero.



[Watch Video Solution](#)

**10.** An LC circuit has  $L = 20 \text{ mH}$ ,  $C = 50 \mu\text{F}$  and initial charge  $10 \text{ mC}$  the resistance being negligible.

what is the total energy stored initially? IT is conserved during LC oscillator?



**Watch Video Solution**

**11.** An LC circuit has  $L = 20 \text{ mH}$ ,  $C = 50 \mu\text{F}$  and initial charge  $10 \text{ mC}$  the resistance being

negligible.

What is the natural frequency of the circuit?



[Watch Video Solution](#)

**12.** An LC circuit has  $L = 20 \text{ mH}$ ,  $C = 50 \mu\text{F}$  and initial charge  $10 \text{ mC}$  the resistance being negligible.

After what time interval from the moment the circuit is switched on the energy stored is (i) completely electrical i.e., stored only in the

capacitor and (ii) completely magnetic ,i.e., stored only in the inductor?



[Watch Video Solution](#)

**13.** An LC circuit has  $L = 20 \text{ mH}$  ,  $C = 50 \mu\text{F}$  and initial charge  $10 \text{ mC}$  the resistance being negligible.

At what time is the total energy shared equally between the inductor and the capacitor?



[Watch Video Solution](#)

**14.** An LC circuit has  $L = 20 \text{ mH}$ ,  $C = 50 \mu\text{F}$  and initial charge  $10 \text{ mC}$  the resistance being negligible.

If a resistor is inserted in the circuit, how much energy is dissipated as heat?



[Watch Video Solution](#)

**15.** A coil of inductance  $0.50 \text{ H}$  and resistance  $100 \Omega$  is connected to a  $240 \text{ V}$ ,  $50 \text{ Hz}$  ac supply.  
what is the maximum current in the coil?



[Watch Video Solution](#)



**16.** A coil of inductance  $0.50\text{ H}$  and resistance  $100\Omega$  is connected to a  $240\text{ V}$ ,  $50\text{ Hz}$  ac supply.  
what is the time lag between the voltage maximum and current maximum?



**Watch Video Solution**

**17.** A coil of inductance  $0.50\text{ H}$  and resistance  $100\Omega$  is connected to a  $240\text{ V}$ ,  $50\text{ Hz}$  ac supply.  
What is the maximum current in the coil?



[Watch Video Solution](#)

**18.** A coil of inductance  $0.50\text{ H}$  and resistance  $100\Omega$  is connected to a  $240\text{ V}$ ,  $50\text{ Hz}$  ac supply.

How does an inductor behave in a dc circuit after the steady state?



[Watch Video Solution](#)

**19.** A circuit containing a  $80\text{ mH}$  inductor and a  $60\mu\text{F}$  capacitor in series is connected to a  $230\text{ V}$ ,  $50\text{ Hz}$  supply. The resistance of the circuit is

negligible.

Obtain the current amplitude and rms values.



[Watch Video Solution](#)

**20.** A circuit containing a 80 mH inductor and a  $60\mu F$  capacitor in series is connected to a 230 V , 50 Hz supply. The resistance of the circuit is negligible.

Obtain rms values of potential drop across the inductor and capacitor.



[Watch Video Solution](#)

**21.** A circuit containing a 80 mH inductor and a  $60\mu F$  capacitor in series is connected to a 230 V , 50 Hz supply. The resistance of the circuit is negligible.

What is the average power transferred to the inductor?



**Watch Video Solution**

**22.** A circuit containing a 80 mH inductor and a  $60\mu F$  capacitor in series is connected to a 230

V , 50 Hz supply. The resistance of the circuit is negligible.

What is the average power transferred to the capacitor?



[Watch Video Solution](#)

**23.** A circuit containing a 80 mH inductor and a  $60\mu F$  capacitor in series is connected to a 230 V , 50 Hz supply. The resistance of the circuit is negligible.

What is the total average power absorbed by the circuit?



[Watch Video Solution](#)

**24.** A series LCR circuit with  $L=0.12\text{H}$ ,  $C=480\text{nF}$ ,  $R=23\Omega$  is connected to a  $230\text{V}$  variable frequency supply.

What is the source frequency for which current amplitude is maximum. Obtain this maximum value.



[Watch Video Solution](#)

**25.** A series LCR circuit with  $L=0.12\text{H}$ ,  $C=480\text{nF}$ ,  $R=23\Omega$  is connected to a 230V variable frequency supply.

What is the source frequency for which average power absorbed by the circuit is maximum. Obtain the value of this maximum power.



**Watch Video Solution**

**26.** A series LCR circuit with  $L=0.12\text{H}$ ,  $C=480\text{nF}$ ,  $R=23\Omega$  is connected to a 230V variable frequency supply.

What is the Q-factor of the circuit?



**Watch Video Solution**

**27.** In any ac circuit, is the applied instantaneous voltage equal to the algebraic sum of the instantaneous voltages across the



series elements of the circuit? Is the same true for rms value?



[Watch Video Solution](#)

**28.** The instantaneous value of emf and current in an A.C. circuit are;  $E = 1.414 \sin(100\pi t - 4\pi)$ ,  $I = 0.707 \sin(100\pi t)$ . The impedance of the circuit will be



[Watch Video Solution](#)

**29.** Why a capacitor is used in the primary circuit of an induction coil?



**Watch Video Solution**

**30.** When a choke is connected in series with a lamp in dc line, the lamp shines brightly. Insertion of an iron core in the choke does not affect the brightness. What happens in case of ac line?



**Watch Video Solution**

**31.** Why a choke is needed with a fluorescent lamp with ac mains? Why a normal resistor can not be used in place of the choke?



**Watch Video Solution**

**32.** A small town with a demand of 800 kW of power at 220 V is situated 15 km away from an electric plant generating power at 440 V. The resistance of the two wire line carrying power is  $0.5\Omega.km^{-1}$ . The line gets power from the

line through a 4000-220 V step-down transformer at a substation in the town.

Estimate the line power loss in the form of heat?



[Watch Video Solution](#)

**33.** A small town with a demand of 800 kW of power at 220 V is situated 15 km away from an electric plant generating power at 440 V. The resistance of the two wire line carrying power is  $0.5\Omega.km^{-1}$ . The line gets power from the

line through a 4000-220 V step-down transformer at a substation in the town.

How much power must the plant supply, assuming there is negligible power loss due to leakage.



[Watch Video Solution](#)

**Ncert Textbook Questions With Answer Hint Mcq**

**1**

1. A small town with a demand of 800 kW of power at 220 V is situated 15 km away from an electric plant generating power at 440 V. The resistance of the two wire line carrying power is  $0.5\Omega.km^{-1}$ . The line gets power from the line through a 4000-220 V step-down transformer at a substation in the town.

Characterise the step-up transformer at the plant.



[Watch Video Solution](#)

2. The internal resistance and internal reactance of an alternating current generator are  $R_g$  and  $X_g$  respectively. Power from this source is supplied to a load consisting of resistance  $R_L$  and reactance  $X_L$ . For maximum power to be delivered from the generator to the load. The value of  $X_L$  is equal to

A. zero

B.  $X_g$

C.  $-X_g$

D.  $R_g$

**Answer: C**



**Watch Video Solution**

**3.** To reduce the resonant frequency in an LCR series circuit with a generator,

A. the frequency of the generator should  
be reduced



B. another capacitor should be connected  
is parallel with the first capacitor

C. the iron core of the inductor should be  
removed

D. the dielectric in the capacitor should be  
removed

**Answer: B**



**Watch Video Solution**

4. Which of the following combinations should be selected for fine tuning of an LCR circuit used for communication?

A.  $R = 20\Omega, L = 1.5H, C = 35\mu F$

B.  $R = 25\Omega, L = 2.5H, C = 45\mu F$

C.  $R = 15\Omega, L = 3.5H, C = 30\mu F$

D.  $R = 25\Omega, L = 1.5H, C = 45\mu F$

**Answer: C**



**Watch Video Solution**

1. The current through an ac circuit first increases and then decreases as its frequency is increased. Which among the followings are most likely combination of the circuit?

- A. inductor and capacitor
- B. resistor and inductor
- C. resistor and capacitor
- D. resistor, inductor and capacitor

**Answer: A::D**



**Watch Video Solution**

2. The current through an ac (series) circuit increases as the source frequency is increased. Which of the followings are the most suitable combinations of the circuit?

- A. only resistor
- B. resistor and an inductor
- C. resistor and a capacitor

D. only capacitor

**Answer: C::D**



**Watch Video Solution**

**3.** When an ac voltage of 220 V is applied to a capacitor C

A. the maximum voltage between plates is

220V

B. the current is in phase with the applied voltage

C. the charge on the plates is in phase with the applied voltage

D. power delivered to the capacitor is zero

**Answer: C::D**



**Watch Video Solution**

4. The line that draws power supply to your house has

A. zero average current

B. 220 V average voltage

C. voltage and current out of phase by  $90^\circ$

D. voltage and current possibly differing in

phase  $\phi$  such that  $|\phi| < \frac{\pi}{2}$

**Answer: A::D**



**Watch Video Solution**

## Exercise Multiple Choice Question

1. An alternating current is given by the equation  $I = i_1 \sin \omega t \cos \omega t$ . The rms current is given by

A.  $(i_2 + i_1) / \sqrt{2}$

B.  $(i_2 - i_1) / \sqrt{2}$

C.  $\sqrt{\{(i_1^2 + i_2^2) / 2\}}$

D.  $\sqrt{\{(i_1^2 + i_2^2) / (\sqrt{2})\}}$



**Answer: C**



**Watch Video Solution**

2. An ac having a peak value  $1.41\text{ A}$  is used to heat a wire. A dc producing the same heating rate will be

A.  $1.41\text{A}$

B.  $2.0\text{A}$

C.  $0.705\text{A}$

D.  $1.0\text{A}$

**Answer: D**



**Watch Video Solution**

3. The general equation for the instantaneous voltage of a 50 Hz generator with peak voltage 220 V is

- A.  $220 \sin 50\pi t$
- B.  $220 \sin 100\pi t$
- C.  $\pm 220 \sin 100\pi t$
- D.  $220 \sin 25\pi t$

**Answer: B**



**Watch Video Solution**

4. The relation between angular velocity ( $\omega$ ) and driving frequency( $f$ ) of an alternating current is

A.  $\omega = 2\pi f$

B.  $\omega = \frac{2\pi}{f}$

C.  $f = \frac{2\pi}{\omega}$

D.  $f = 2\pi\omega$

**Answer: A**



**Watch Video Solution**

5. Form factor of an alternating voltage is the ratio of

- A. peak value and rms value
- B. peak value and average value
- C. rms value and average value
- D. rms value and peak value

**Answer: C**



**Watch Video Solution**

6. The value of an ac voltage at time  $0 \leq t \leq \frac{\pi}{\omega}$  is given by  $V = V_0 \sin \omega t$  and at time  $\frac{\pi}{\omega} \leq t \leq \frac{2\pi}{\omega}$  is given by  $V = -V_0 \sin \omega t$ . The average value of V for a complete cycle is

A.  $\frac{V_0}{\sqrt{2}}$

B.  $\left(\frac{2}{\pi}\right) V_0$

C.  $\frac{V_0}{2}$

D. zero

**Answer: B**



**Watch Video Solution**

7. The rms value of potential difference  $V$  shown in the Fig.2.42 is



A.  $\frac{V_0}{\sqrt{3}}$

B.  $V_0$

C.  $\frac{V_0}{\sqrt{2}}$

D.  $\frac{V_0}{2}$

**Answer: C**



**Watch Video Solution**

**8.** The rms value and frequency of an ac current are 5A and 50 Hz respectively. The value of the current after  $\frac{1}{300}$  s from the time when its value becomes zero is

A.  $5\sqrt{2}A$

B.  $5\sqrt{\frac{3}{2}}A$

C.  $\frac{5}{6}A$

D.  $\frac{5}{\sqrt{2}}A$

**Answer: B**



**Watch Video Solution**

**9.** In an ac circuit containing capacitance , only the current



A. leads the voltage by  $180^\circ$

B. is in phase with the voltage

C. leads the voltage by  $90^\circ$

D. lags behind the voltage by  $90^\circ$

**Answer: C**



**Watch Video Solution**

**10.** In an LR circuit , the phase angle between alternating voltage and alternating current is  $45^\circ$  . The value of inductive reactance will be

A.  $\frac{R}{4}$

B.  $\frac{R}{2}$

C. R

D. data insufficient

**Answer: C**



**Watch Video Solution**

**11.** In an LCR series circuit, the capacitance is reduced to one-fourth, when in resonance. What change should be made in the

inductance, so that the circuit remains in resonance?

A. 4 times

B.  $\frac{1}{4}$  times

C. 8 times

D. 2 times

**Answer: A**



**Watch Video Solution**

12. The phase difference between V and I of an LCR circuit in series resonance is

A.  $\pi$

B.  $\frac{\pi}{2}$

C.  $\frac{\pi}{4}$

D. 0

**Answer: D**



**Watch Video Solution**

13. The reactance of an inductor of inductance  $\frac{1}{\pi}$  H at frequency 50 Hz is

A.  $\frac{50}{\pi} \Omega$

B.  $\frac{\pi}{50} \Omega$

C.  $100\Omega$

D.  $50\Omega$

**Answer: C**



**Watch Video Solution**

14. Which quantity in an ac circuit is not dependent on frequency?

A. resistance

B. impedance

C. inductive reactance

D. capacitive reactance

**Answer: A**



**Watch Video Solution**

15. The condition of getting maximum current in an LCR series circuit is

A.  $X_L = 0$

B.  $X_C = 0$

C.  $X_L = X_C$

D.  $R = X_L - X_C$

**Answer: C**



**Watch Video Solution**

16. The series resonant frequency of an LCR circuit is  $f$ . If the capacitance is made 4 times the initial value, then the resonant frequency will come

A.  $f/2$

B.  $2f$

C.  $f$

D.  $f/4$

**Answer: A**



Watch Video Solution



17. A coil has resistance  $30\Omega$  and inductive reactance  $20\Omega$  at 50 Hz frequency. If an ac source of 200V, 100 Hz is connected across the coil, the current in the coil will be

A. 2.0A

B. 4.0A

C. 8.0A

D.  $\frac{20}{\sqrt{13}}A$

**Answer: B**



**Watch Video Solution**

**18.** A fully charged capacitor  $C$  with initial charge  $q_0$  is connected to a coil of self-inductance  $L$  at  $t=0$ . The time at which the energy is stored equally between the electric and the magnetic field is

A.  $\frac{\pi}{4} \sqrt{LC}$

B.  $2\pi \sqrt{LC}$

C.  $\sqrt{LC}$

D.  $\pi\sqrt{LC}$

**Answer: A**



**Watch Video Solution**

**19.** A voltage  $V_0 \sin \omega t$  is applied across a series combination of resistance  $R$  and inductor  $L$ . The peak value of the current in the circuit is

A.  $\frac{V_0}{\sqrt{R^2 + \omega^2 L^2}}$

B.  $\frac{V_0}{\sqrt{R^2 - \omega^2 L^2}}$

C.  $\frac{V_0}{\sqrt{R^2 + \omega^2 L^2}} \sin \omega t$

D.  $\frac{V_0}{R}$

**Answer: A**



**Watch Video Solution**

**20.** When an ideal choke is connected to an ac source of 100V and 50Hz, a current of 8 A flows through the circuit, A current of 10 A flows

through the circuit when a pure resistor is connected instead of the choke coil. IF the two are connected in series with an ac supply of 100 V and 40 Hz, then the current in the circuit is

A.  $10A$

B.  $8A$

C.  $5\sqrt{2}A$

D.  $10\sqrt{2}A$

**Answer: C**



21. In an LCR circuit voltages across R,L and C are 10V,10V and 20V respectively. Voltage between the two end points of the whole combination is

A. 30V

B.  $10\sqrt{3}V$

C. 20V

D.  $10\sqrt{2}V$

**Answer: D**



**Watch Video Solution**

22. In an ac circuit alternating voltage  $E = 200\sqrt{2} \sin 100t$  volt is connected to a capacitor of capacity  $1\mu F$ . The rms value of the current in the circuit is

A. 10 mA

B. 100 mA

C. 200 mA

D. 20 mA

**Answer: D**



**Watch Video Solution**

**23.** The power factor of an LR circuit carrying an ac of angular frequency  $\omega$  is

A.  $\frac{R}{\omega L}$

B.  $\frac{\omega L}{R}$

C.  $\frac{R}{\sqrt{R^2 + \omega^2 L^2}}$



D.  $\frac{R}{\sqrt{R^2 - \omega^2 L^2}}$

**Answer: C**



**Watch Video Solution**

**24.** One of the condions to get a wattless current in an ac circuit is

A.  $L=0$

B.  $C=0$

C.  $R=0$

D.  $L=C$

**Answer: C**



**Watch Video Solution**

25. If an emf  $E = E_0 \cos \omega t$  is applied to a circuit, the current becomes  $I = I_0 \cos \omega t$ . What is the power factor of the circuit?

A. zero

B.  $\frac{1}{\sqrt{2}}$

C. 1

D.  $\infty$

**Answer: C**



**Watch Video Solution**

**26.** In an ac circuit ,  $V$  and  $I$  are given by  $V=100\sin(100t)V$ , and  $I=100\sin\left(100t + \frac{\pi}{3}\right)$  a respectively. The power dissipated in the circuit is

A.  $10^4$ W

B. 10 W

C. 2500 W

D. 5 W

**Answer: C**



**Watch Video Solution**

**27.** The inductance and capacitance in a closed circuit are 20 mH and  $2\mu F$  respectively. The natural frequency will be

A. 796 Hz

B. 5000 Hz

C. 40 Hz

D. 31400 Hz

**Answer: A**



**Watch Video Solution**

**28.** For an LC oscillator which one of the followings is not true?

A. IT converts dc current to ac current

B. IT can be used as filter

C. IT can sustain stable oscillations only for frequencies less than resonance frequency

D. The resonance frequency is  $\frac{1}{\sqrt{LC}}$  radians per second

**Answer: C**



**Watch Video Solution**

**29.** An ideal transformer is used to decrease an alternating voltage from 880 V and 220 V. If the number of turns of its primary coil is 4000, then what is that in the secondary coil?

A. 16000

B. 4000

C. 2000

D. 1000

**Answer: D**



**Watch Video Solution**

30. The core of any transformer is laminated so as to

A. increase the secondary voltage

B. reduce the energy loss due to eddy currents

C. reduce the energy loss due to hysteresis

D. make it robust and strong

**Answer: B**





**31.** In a non-ideal transformer the primary and secondary voltages and currents are  $V_1, I_1$  and  $V_2, I_2$  respectively. The efficiency of the transformer is

A.  $\frac{V_2}{V_1}$

B.  $\frac{I_2}{I_1}$

C.  $\frac{V_2 I_2}{V_1 I_1}$

D.  $\frac{V_1 I_1}{V_2 I_2}$

**Answer: C**



**Watch Video Solution**

**32.** The turns ratio of an ideal transformer is 1:n. the input to output power transfer ratio is

A. 1 : 1

B. 1 :  $n$

C.  $n$  : 1

D. 1 :  $n^2$

**Answer: A**



**Watch Video Solution**

## Exercise Very Short Answer Type

1. If the frequency of an alternating emf be 50 Hz, how many times the direction of emf will be reversed per second?



**Watch Video Solution**

2. What percentage of its peak value is the rms value of an ac?



[Watch Video Solution](#)

3. What is the peak value of the voltage of a 220V ac line?



[Watch Video Solution](#)

4. If an alternating current is represented by  $I = \sin 100\pi t$  mA. What is the peak value?



Watch Video Solution

5. If an alternating current is represented by .  
 $I = \sin 100\pi t \text{ mA}$ , then what is the frequency  
of that current?



Watch Video Solution

6. After what time will the direction of current  
is an electric supply line of frequency 50 Hz be  
reversed?



[Watch Video Solution](#)

7. An alternating source of emf  $E = E_0 \sin \omega t$  and of negligible resistance is connected directly to an ac voltmeter. What reading will it show?



[Watch Video Solution](#)

8. What changes are observed in the rms value of an ac with changes in the frequency?



[Watch Video Solution](#)

9. What is the rms value of an alternating current ,  $I = I_0 \sin \omega t$ ?



[Watch Video Solution](#)

10. What is the ratio between the peak value and the average value of a sinusoidal emf?



[Watch Video Solution](#)

**11.** The instantaneous current in an ac circuit is  $I = 6 \sin 314t A$ . What is the rms value of current ?



**Watch Video Solution**

**12.** An alternating current is  $I = \cos 100\pi t A$ . Find out its frequency, peak value and rms value.



**Watch Video Solution**



**13.** Why a dc voltmeter and dc ammeter cannot read ac?



**Watch Video Solution**

**14.** What will be the phase difference between current and emf when 220 V, 50 Hz ac source is connected to a circuit containing pure resistor?



**Watch Video Solution**

15. What is the unit of impedance?



[Watch Video Solution](#)

16. What is the reactance of pure resistances in an ac circuit?



[Watch Video Solution](#)

17. If an LCR circuit is connected to a dc source, what will be the current through the circuit?



[Watch Video Solution](#)

**18.** What will be the reactance if a current of frequency  $f$  flows through an inductor of self-inductance  $L$ ?



**Watch Video Solution**

**19.** What will be the reactance if a current of frequency  $f$  flows through a capacitor of capacitance  $C$ ?



**Watch Video Solution**

**20.** If the frequency of an circuit is increased, how would the reactance of an inductor change?



**Watch Video Solution**

**21.** If the frequency of an circuit is increased, how would the reactance of a capacitor change?



**Watch Video Solution**

22. In an LR circuit, the alternating current \_\_\_\_\_ the alternating emf by a certain phase angle.[Fill in the blanks]



[Watch Video Solution](#)

23. In a CR circuit, the alternating current \_\_\_\_\_ the alternating emf by a certain phase angle.[Fill in the blanks]



[Watch Video Solution](#)

24. In an alternating series LCR circuit ,what is the phase difference between the voltage drop across L and C?



[Watch Video Solution](#)

25. When does LCR series circuit have minimum impedance?



[Watch Video Solution](#)

**26.** What is the reactance of a capacitor of capacitance  $C$  at  $f$ Hz?



**Watch Video Solution**

**27.** What is the power factor of a circuit having a pure resistance only?



**Watch Video Solution**

28. What is the power dissipated in an ac circuit in which voltage and current are given by  $V = 230 \sin\left(\omega t + \frac{\pi}{2}\right)$  and  $I = 10 \sin \omega t$ ?



[Watch Video Solution](#)

29. What is the natural frequency of an LC oscillator?



[Watch Video Solution](#)



**30.** Indicate the change in emf produced by an ac dynamo in the following cases: the magnetic field is doubled



**Watch Video Solution**

**31.** Indicate the change in emf produced by an ac dynamo in the following cases: the angular velocity of the coil is decreased.



**Watch Video Solution**

**32.** If the area of the coil of an ac dynamo is halved, how would the emf generated change?



**Watch Video Solution**

**33.** If the angular velocity of coil of an ac dynamo is doubled ,how would the emf produced change?



**Watch Video Solution**

**34.** By what factor would the output voltage of an ac generator change, if the number of turns in its coil is doubled?



**Watch Video Solution**

**35.** The turns ratio of an ideal transformer is 4:1 what will be the current in the secondary if that in the primary is 1.2A?



**Watch Video Solution**

## Exercise Short Answer Type I

1. The number of turns in the coil of an AC generator are 100 and its cross-sectional area is  $2.5 \text{ m}^2$ . The coil is revolving in a uniform magnetic field of strength  $0.3\text{T}$  with the uniform angular velocity of  $60\text{rad/s}$ . The value of maximum voltage produced is \_\_\_\_\_ kV



[Watch Video Solution](#)

2. What is the form factor of a sinusoidal alternating current. How can it be obtained?



[Watch Video Solution](#)

3. The inductance of a resistanceless coil is 0.5 henry. In the coil, the value of alternating current is 0.2 A, whose frequency is 50 Hz. The reactance of circuit is



[Watch Video Solution](#)

4. What type of voltmeters or ammeters are used for measuring alternating voltage or current?



**Watch Video Solution**

5. Why a moving coil galvanometer cannot be used with an alternating current.



**Watch Video Solution**

6. Write down the conditions for which there will be no phase difference between alternating voltage and alternating current in a series LCR circuit?



[Watch Video Solution](#)

7. Why does a series LCR circuit connected to a DC source register zero current?



[Watch Video Solution](#)

8. In a circuit, the frequency is  $f = 1000/2\pi$  Hz and the inductance is 2 henry, then the reactance will be



[Watch Video Solution](#)

9. Show with a vector diagram the phase relations among the quantities related to an alternating CR circuit.



[Watch Video Solution](#)



**10.** What remedial steps are to be taken to minimise damping in LC oscillations.



**Watch Video Solution**

**11.** Show that a purely capacitive ac circuit dissipates no power.



**Watch Video Solution**

**12.** Show that a purely inductive ac circuit dissipates no power.



[Watch Video Solution](#)

**13.** Why is the use of a capacitor of variable capacitance less costly than the use of a variable resistance for regulating the speed of an electric fan?



[Watch Video Solution](#)

**14.** How would you explain wattless current in view of the law of conservation of energy?





[Watch Video Solution](#)

15. How does an LC oscillations behave in a closed LC circuit which includes a resistance?



[Watch Video Solution](#)

16. Explain whether the rms voltages are always the same for two alternating voltages of the same peak value and of the same frequency.



[Watch Video Solution](#)

17. Prove that high frequency ac can pass through a pure capacitor easily but not through a pure inductor.



[Watch Video Solution](#)

18. An alternating voltage  $E = E_0 \sin \omega t$  is applied across an inductor  $L$ . Show by calculation that the current lags the voltage

by a phase angle  $\pi / 2$  (Assume inductor L has no resistance).



[Watch Video Solution](#)

## Exercise Short Answer Type II

1. The natural frequency of an LC oscillations is  $f_0$ . Show that, during periodic oscillations the maximum current  $I_0$  flowing through the oscillator is related to the maximum charge  $Q_0$ , on the capacitor as  $I_0 = 2\pi f_0 Q_0$ .



[Watch Video Solution](#)

2. Sketch graphs to show the variation of (i) current and (ii) impedance of a series LCR circuit with the frequency of the ac source.



[Watch Video Solution](#)

3. Can the voltage drop across the inductor or the capacitor in a series LCR circuit be greater than the applied voltage of the ac source? Justify your answer.



[Watch Video Solution](#)

## Problem Set I

1. The frequency of an alternating current is 50 Hz .In what time will the value of current rise to rms value from zero?



[Watch Video Solution](#)

2. An alternating current is given by the equation  $I = I_1 \sin \omega t + I_2 \cos \omega t$ . What will be its rms value?



[Watch Video Solution](#)

3. The line voltage of a house, measured by an ac voltmeter is 324 V. If the frequency is 50Hz, establish the equation of the line voltage.



[Watch Video Solution](#)



4. The voltage of an source varies with time according to the equation ,  
 $V = 100 \sin 100\pi t \cos 100\pi t$ , where  $t$  is in second and  $V$  is in volt. What are the values of peak voltage and frequency of the source?



[Watch Video Solution](#)

5. What is the rms value of the alternating emf  
 $E = 10 \sin 100\pi t \cos 100\pi t$ ?



[Watch Video Solution](#)

6. Resistance , inductive reactance and capacitive reactance of an LCR series ac circuit are  $30\Omega$ ,  $60\Omega$  and  $20\Omega$  respectively. What is the phase difference between the ac-voltage and current in the circuit?



[Watch Video Solution](#)

7. The rms values of the terminal potential differences of R ,L and C of a series circuit are

80V ,70V and 10V respectively.What is the rms value of the applied emf in the circuit?



[Watch Video Solution](#)

8. A  $15.0\mu F$  capacitor is connected to 220V,50Hz source. Find the capacitive reactance and the rms current.



[Watch Video Solution](#)

**9.** An ac voltage of 100V,50Hz is connected across a  $20\Omega$  resistor and 2mH inductor in series. Calculate (i) impedance of the circuit (ii) rms current in the circuit.



**Watch Video Solution**

**10.** A bulb of resistance  $10\Omega$  connected to an inductor pf inductance L is in series with an ac source marked 100V, 50Hz. IF the phase angle

between voltage and current is  $\frac{\pi}{4}$

radian, calculate the value of L.



[Watch Video Solution](#)

**11.** A capacitor, a resistor and a 40 mH inductor are connected in series to an ac source of frequency 60Hz. Calculate the capacitance of the capacitor, if current is in phase with the voltage.



[Watch Video Solution](#)

12. The frequency of applied of ac voltage to an inductive coil is 1000Hz.  $L=25$  mH and the power factor of the circuit is 0.1. Find the resistance of the coil.



[Watch Video Solution](#)

13. What should be the percentage rise of impedance, the pure resistance remaining the same, so that the power factor of a circuit will be half?



[Watch Video Solution](#)

14. What is the  $Q$  factor of a series LCR circuit with  $L = 2 \text{ H}$ ,  $C = 32 \mu\text{F}$  and  $R = 10 \Omega$  ?



[Watch Video Solution](#)

15. The inductance in a closed circuit is  $40 \text{ mH}$  and the capacitance is  $1 \mu\text{F}$ . What is the frequency of LC oscillation?



[Watch Video Solution](#)

**16.** The length and breadth of a rectangular coil are 10cm and 8cm, respectively and the coil contains 500 turns . IF it is rotated with an angular velocity of  $1200\text{rad} / \text{min}$  in a magnetic field of intensity  $10\text{Wb } m^{-2}$ , find out the peak value of the induced emf.



**Watch Video Solution**

**17.** A rectangular coil of area  $20\text{cm} \times 15\text{cm}$  and of 485 turns is rotating with a speed of 1800 rpm in a magnetic field of intensity



$20 \text{ Wb} \cdot \text{m}^{-2}$ . When the coil is inclined at  $60^\circ$  with the magnetic field, what will be the induced emf in the coil?



[Watch Video Solution](#)

**18.** A transformer carries 8 A current in the primary of 100 turns. If the input power is 1kW, what should be the number of turns in the secondary to have a 500 V output?



[Watch Video Solution](#)

## Problem Set ii

1. Expression of an alternating current is  $I = 0.5 \sin 100\pi t A$ . Determine the frequency, peak value and rms value of the current.



[Watch Video Solution](#)

2. An alternating voltage is represented by

$$E = 311 \sin\left(100\pi t - \frac{\pi}{6}\right) V$$

Determine its frequency, time period, peak value and rms value.



[Watch Video Solution](#)

3. In an LCR circuit ,  $R=125\Omega$ ,  $L=100\text{ mH}$  and  $C=10^{-7}\text{ F}$ . Find out the resonance frequency and the Q-value of the circuit.



[Watch Video Solution](#)

4. A  $25\mu\text{F}$  capacitor, a  $0.10\text{ henry}$  inductor and a  $25.0\Omega$  resistor are connected in series with an ac source whose emf is given by

$E=310\sin 314t$ . what is the frequency of the emf?



[Watch Video Solution](#)

5. A  $25\mu F$  capacitor, a 0.10 henry inductor and a  $25.0\Omega$  resistor are connected in series with an ac source whose emf is given by  $E=310\sin 314t$ . Calculate (a) the reactance of the circuit, (b) the impedance of the circuit and (c) current in the circuit.



[Watch Video Solution](#)

6. An alternating current of 1.5mA and angular frequency  $300 \text{ radian } s^{-1}$  flows through a  $10 \text{ k}\Omega$  resistor and a  $0.50 \mu F$  capacitor in series. Find the rms voltage across the capacitor and impedance of the circuit.



[Watch Video Solution](#)

7. An ac source of 200 V, 50 Hz is connected in series to a capacitor with a 20 V-5W. Lamp. Determine the capacitance of the capacitor

needed to light the lamp with maximum brightness.



[Watch Video Solution](#)

**8.** For the series connection of an inductor (L), a capacitor (C) and a resistor (R), show that the current flowing through the circuit is maximum for a particular value of the capacitor. IF  $L=10\text{ mH}$ ,  $R=100\Omega$  and frequency is  $1000\text{ s}^{-1}$ , then what is the value of C for which current flowing in the circuit is maximum?



[Watch Video Solution](#)

9. When 100 volt dc is applied across a conducting coil, a current of 1A flows through it. When 100 volt ac of 50 cycles per second is applied to the same coil, only 0.5 A current flows through it. Calculate resistance of coil



[Watch Video Solution](#)

10. When 100 volt dc is applied across a conducting coil, a current of 1A flows through

it. When 100 volt ac of 50 cycles per second is applied to the same coil, only 0.5 A current flows through it. Calculate impedance of coil



[Watch Video Solution](#)

**11.** When 100 volt dc is applied across a conducting coil, a current of 1A flows through it. When 100 volt ac of 50 cycles per second is applied to the same coil, only 0.5 A current flows through it. Calculate inductive reactance of coil





[Watch Video Solution](#)

**12.** When 100 volt dc is applied across a conducting coil, a current of 1A flows through it. When 100 volt ac of 50 cycles per second is applied to the same coil, only 0.5 A current flows through it. Calculate inductance of coil.



[Watch Video Solution](#)

**13.** An LR circuit contains a resistance of  $40\Omega$  and an inductance of 25 mH .What would be

the power dissipated in the circuit for an applied alternating voltage of frequency 1000 Hz and peak value of 10 V?



[Watch Video Solution](#)

**14.** An alternating emf of  $E=20\sin 1000t$  V is applied on a circuit containing a pure resistance of  $25\Omega$  in series with a coil of self-inductance 40 mH and resistance  $15\Omega$ . Find out the phase difference between E and the current I.



[Watch Video Solution](#)

15. An alternating emf of  $E=20\sin 1000tV$  is applied on a circuit containing a pure resistance of  $25\Omega$  in series with a coil of self-inductance  $40\text{ mH}$  and resistance  $15\Omega$ . Find out the power factor of the circuit , Also , find out this capacitance of a capacitor that should be connected in series to raise the power factory to unity.



[Watch Video Solution](#)

**16.** A sinusoidal voltage  $v=200 \sin 314 t$  is applied to a resistor of  $10\Omega$  resistance.

Calculate the frequency of the supply



**Watch Video Solution**

**17.** A sinusoidal voltage  $v=200 \sin 314 t$  is applied to a resistor of  $10\Omega$  resistance.

Calculate the rms value of the voltage



**Watch Video Solution**

**18.** A sinusoidal voltage  $v=200 \sin 314 t$  is applied to a resistor of  $10\Omega$  resistance. Calculate the rms value of the current



**Watch Video Solution**

**19.** A sinusoidal voltage  $v=200 \sin 314 t$  is applied to a resistor of  $10\Omega$  resistance. Calculate the power dissipated as heat in watt.



**Watch Video Solution**

**20.** A circuit is set up connecting  $L=100\text{ mH}$ ,  $C=5\mu F$  and  $R=100\Omega$  is series, An alternating emf of  $(150\sqrt{2})\text{ volt}$ ,  $\frac{500}{\pi}\text{ Hz}$  is applied across this series combination. Calculate the impedance of the circuit. What is the average power dissipated in the resistor



**Watch Video Solution**

**21.** A circuit is set up connecting  $L=100\text{ mH}$ ,  $C=5\mu F$  and  $R=100\Omega$  is series, An alternating emf of  $(150\sqrt{2})\text{ volt}$ ,  $\frac{500}{\pi}\text{ Hz}$  is applied across this

series combination. What is the average power dissipated in the capacitor



[Watch Video Solution](#)

22. A circuit is set up connecting  $L=100\text{ mH}$ ,  $C=5\mu\text{F}$  and  $R=100\Omega$  in series, An alternating emf of  $(150\sqrt{2})\text{ volt}$ ,  $\frac{500}{\pi}\text{ Hz}$  is applied across this series combination. Calculate the impedance of the circuit. What is the average power dissipated in the inductor?



[Watch Video Solution](#)

**23.** A circuit draws a power of 550 W from a 220V-50 Hz source. The power factor of the circuit is 0.8. A current in the circuit lags behind the voltage. Show that a capacitor of about  $\frac{1}{42\pi} \times 10^{-2} F$  will have to be connected in the circuit to bring its power factor to unity.



**Watch Video Solution**



**24.** Find out the inductance of an inductor which should be connected in series with a capacitor of  $5\mu F$ , a resistance of  $10\Omega$  and an ac source of 50 Hz so that the power factor of the circuit is 1.



**Watch Video Solution**

**25.** An ac source is connected in series with an inductor of 5H and a resistor of  $1000\Omega$ . The rms value of voltage of the source is 100 V and

the frequency of the source is 50cps. What is the rms value of the current in the circuit? What is the phase difference of the voltage and the current in the circuit? What is the power dissipated in the circuit?



[Watch Video Solution](#)

**26.** The primary coil of an ideal step-up transformer has 100 turns, and the transformation ratio is also 100. The input voltage and power are 220 V and 1100 W ,

respectively, Calculate number of turns in the secondary



[Watch Video Solution](#)

27. The primary coil of an ideal step-up transformer has 100 turns, and the transformation ratio is also 100. The input voltage and power are 220 V and 1100 W , respectively, Calculate the current in the primary



[Watch Video Solution](#)

**28.** The primary coil of an ideal step-up transformer has 100 turns, and the transformation ratio is also 100. The input voltage and power are 220 V and 1100 W , respectively, Calculate the voltage across the secondary



**Watch Video Solution**

**29.** The primary coil of an ideal step-up transformer has 100 turns, and the

transformation ratio is also 100. The input voltage and power are 220 V and 1100 W , respectively, Calculate the current in the secondary



[Watch Video Solution](#)

**30.** The primary coil of an ideal step-up transformer has 100 turns, and the transformation ratio is also 100. The input voltage and power are 220 V and 1100 W ,

respectively, Calculate the power in the secondary.



[Watch Video Solution](#)

## Hots Numerical Problems

1. When an ac signal of frequency 1200 Hz is applied to a coil of reactance  $120\Omega$ , the applied voltage leads the current by  $45^\circ$ . Calculate the self inductance of the coil.



[Watch Video Solution](#)

2. A circuit draws 280 W from a 110V, 60Hz ac line. The current lags the voltage and the power factor is 0.5. Find the value of a capacitance which can be connected in series to make the power factor of the circuit unity.



[Watch Video Solution](#)

**Entrance Corner Assertion Reason Type**

1. Statement I: In series L-C-R AC circuit, current and voltage are in same phase at resonance. Statement II: In series L-C-R AC circuit, resonant frequency does not depend on the value of resistance. Hence current, at resonance, does not depend on resistance.

A. Statement I is true, statement II is true, statement II is a correct explanation for statement I.



- B. Statement I is true, statement II is true,  
statement II is not a correct explanation  
for statement I
- C. Statement I is true, statement II is false
- D. Statement I is false, statement II is true

**Answer: D**



**Watch Video Solution**

2. Statement I: Q-factor of a series LCR circuit

is  $\frac{1}{R} \sqrt{\frac{L}{C}}$

Statement II: Resonant frequency of an LCR circuit does not depend on the resistance of the circuit.

A. Statement I is true, statement II is true, statement II is a correct explanation for statement I.

B. Statement I is true, statement II is true, statement II is not a correct explanation

for statement I

C. Statement I is true, statement II is false

D. Statement I is false, statement II is true

**Answer: B**



**Watch Video Solution**

3. When the values of inductance and capacitance in an L-C circuit are 0.5 H and  $8 \mu\text{F}$  respectively then current in the circuit is

maximum. The angular frequency of alternating e.m.f. applied in the circuit will be



[Watch Video Solution](#)

4. Statement I: Form factor becomes different for different waveforms of alternating voltage and current.

Statement II: The mean value of alternating voltage or current

$$= \frac{2}{\pi} \quad \text{rms value} = \frac{1}{\sqrt{2}} \times \text{peak value}$$

for any wave form.

- A. Statement I is true, statement II is true, statement II is a correct explanation for statement I.
- B. Statement I is true, statement II is true, statement II is not a correct explanation for statement I
- C. Statement I is true, statement II is false
- D. Statement I is false, statement II is true

**Answer: C**



**View Text Solution**

5. Statement I: A series LCR circuit when connected to an ac source gives the terminal potential difference 50 V across each of resistor R, inductor L and capacitor C. Then the terminal potential difference across LC is zero.

Statement II: The terminal alternating voltages across the inductor and capacitor in a series LCR circuit are in opposite phase.

A. Statement I is true, statement II is true, statement II is a correct explanation for

statement I.

- B. Statement I is true, statement II is true,  
statement II is not a correct explanation  
for statement I
- C. Statement I is true, statement II is false
- D. Statement I is false, statement II is true

**Answer: A**



**Watch Video Solution**

6. Statement I: If the value of the output voltage of an ideal transformer is half the value of the input voltage, then the output current will become twice.

Statement II: No energy is dissipated in an ideal transformer.

A. Statement I is true, statement II is true, statement II is a correct explanation for statement I.



- B. Statement I is true, statement II is true,  
statement II is not a correct explanation  
for statement I
- C. Statement I is true, statement II is false
- D. Statement I is false, statement II is true

**Answer: A**



**Watch Video Solution**

7. Statement I: the alternating current lags behind the voltage by a phase angle  $\frac{\pi}{2}$  when ac flows through an inductor,

Statement II: The inductive reactance increases as the frequency of ac source decreases.

A. Statement I is true, statement II is true, statement II is a correct explanation for statement I.

- B. Statement I is true, statement II is true,  
statement II is not a correct explanation  
for statement I
- C. Statement I is true, statement II is false
- D. Statement I is false, statement II is true

**Answer: C**



**Watch Video Solution**

8. Statement I: An inductor acts as perfect conductor for dc.

Statement II: dc remains constant in magnitude and direction.

A. Statement I is true, statement II is true, statement II is a correct explanation for statement I.

B. Statement I is true, statement II is true, statement II is not a correct explanation for statement I

C. Statement I is true, statement II is false

D. Statement I is false, statement II is true


**Answer: B**



**Watch Video Solution**

**Entrance Corner Multiple Correct Answer**

1. For the circuit in Fig.2.47,

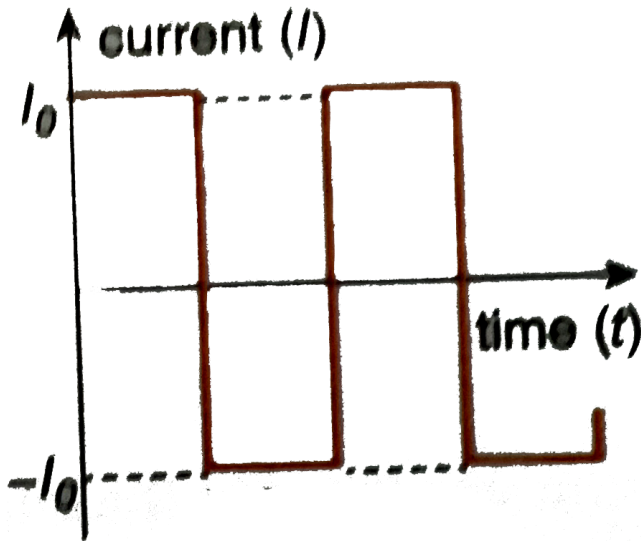

A. mean value =  $I_0$

B. rms value =  $\frac{I_0}{\sqrt{2}}$

C. form factor = 1

D. form factor =  $\frac{1}{\sqrt{2}}$

**Answer: A::C**



**Watch Video Solution**

2. An emf of  $V = V_0 \sin \omega t$  is applied on a series LCR circuit. IF there is no phase difference between the voltage and current then,

A.  $I = \frac{V_0}{R} \sin \omega t$

B.  $\omega L = \frac{1}{\omega L}$

C. effective power =  $\frac{V_0^2}{R}$

D. ratio of terminal potential difference

$$\text{across L and R} = \frac{1}{\omega CR}$$

**Answer: A::B::D**



**Watch Video Solution**

**3.** A coil of resistance  $8\Omega$  and self-inductance  $19.1\text{ mH}$  is connected with an ac source of peak voltage  $200\text{ V}$  and frequency  $50\text{ Hz}$

A. reactance due to induction  $=0.955\Omega$



B. impedance of the circuit  $=10\Omega$

C. rms value of current  $=10\sqrt{2}$  A

D. power dissipated  $=2000$  W

**Answer: B::C::D**



**Watch Video Solution**

4. IF only a capacitor is connected to an ac circuit

A. wattless current is obtained

B. the current is  $90^\circ$  ahead of voltage

C. the current lags the voltage by  $90^\circ$

D. effective power is inversely proportional  
to  $\omega C$

**Answer: A::B**



**Watch Video Solution**

5. The alternating current in an alternating circuit is given by  $I = I_0 \sin \omega t$  In this case

A. the time taken by the current to reach

maximum value of  $I_0$  from zero is  $\frac{\pi}{2\omega}$

B. the time taken by the current to reach

maximum value  $I_0$  from zero is  $\frac{\pi}{4\omega}$

C. the time taken by the current to reach

rms value from zero is  $\frac{\pi}{4\omega}$

D. the time taken by the current to reach

$-I_0$  from zero is  $\frac{\pi}{\omega}$

**Answer: A:C**



**Watch Video Solution**

6. In a series LCR circuit the resonant frequency  $f_0$ , alternating voltage  $V = V_0 \sin \omega t$  and current  $I = I_0 \sin(\omega t + \theta)$ . So if frequency

A.  $f < f_0$  then  $\theta > 0$

B.  $f < f_0$  then  $\theta < 0$

C.  $f > f_0$  then  $\theta > 0$

D.  $f > f_0$  then  $\theta < 0$

**Answer: A::D**



Watch Video Solution

7. In an ideal transformer, number of turns in the primary and secondary are  $N_1$  and  $N_2$ , current and power in the input and output are  $I_1, I_2$  and  $P_1, P_2$  respectively. Then

A.  $I_2 = I_1 \frac{N_1}{N_2}$

B.  $I_2 = I_1 \cdot \frac{N_2}{N_1}$

C.  $P_2 = P_1$

D.  $P_2 = P_1 \frac{N_1}{N_2}$

**Answer: A::C**



**Watch Video Solution**

8. L,C,R represents the inductance, capacitance and reactance respectively. Which of the following combinations have the same dimensions as that of frequency?

A.  $\frac{1}{RC}$

B.  $\frac{R}{L}$

C.  $\frac{1}{\sqrt{LC}}$

D.  $\frac{C}{L}$

**Answer: A::B::C**



**Watch Video Solution**

**9.** In a resonant LCR circuit,

A. power factor is zero

B. power factor is one

C. power dissipated in the resistor is zero



D. power dissipated in the capacitor is zero

Answer: B::D



Watch Video Solution

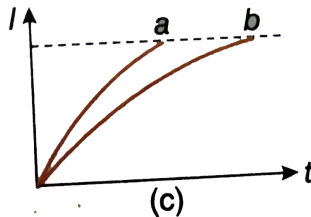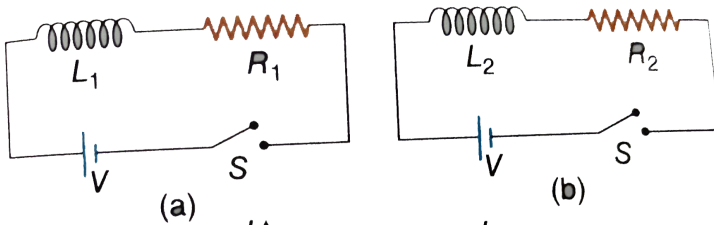10. Two LR circuit show in the fig.2.48(A) and (b). The change in current in this circuit shown in the fig.2.48( c ). Chosse the correct options.





A.  $R_1 > R_2$

B.  $R_1 = R_2$

C.  $L_1 > L_2$

D.  $L_1 < L_2$

**Answer: B::D**



**Watch Video Solution**

**Entrance Corner Matrix Match Type**

1. Match the columns for a series LCR circuit.

Column I	Column II
(i) Impedance	(A) $\omega L - \frac{1}{\omega C}$
(ii) Reactance	(B) $\frac{1}{\omega CR}$
(iii) Power factor	(C) $\frac{R}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$
(iv) Q-factor	(D) $\frac{R}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$



Watch Video Solution

2. An LCR circuit

( $R = 40\Omega$ ,  $L = 100mH$ ,  $C = 0.242\mu F$ ) is

connected with an ac voltage source of peak

voltage 200 V and frequency 1000 Hz.

<i>Column I</i>	<i>Column II</i>
(i) Impedance of the circuit (in $\Omega$ )	<b>A</b> 2512
(ii) Potential difference across $R$ (in V)	<b>B</b> 2632
(iii) Potential difference across $L$ (in V)	<b>C</b> 160
(iv) Potential difference across $C$ (in V)	<b>D</b> 50



**Watch Video Solution**

3. Colum I describes some action and column II the required device.

<i>Column I</i>	<i>Column II</i>
(i) Increase or decrease of ac line voltage	<b>A</b> Dynamo
(ii) Selection of signal of a particular frequency	<b>B</b> Motor
(iii) Transfer of mechanical energy to electrical energy	<b>C</b> LC oscillator
(iv) Transfer of electrical energy to mechanical energy	<b>D</b> Transformer



Watch Video Solution

4. In an LR circuit instantaneous voltage and instantaneous current are  $V=100 \sin 100 t$ , and


$i = 10 \sin\left(100t - \frac{\pi}{4}\right)$  respectively.

Column I	Column II
(i) Resistance	<input type="radio"/> A $\frac{1}{10\sqrt{2}}$ unit
(ii) Inductive reactance	<input type="radio"/> B $5\sqrt{2}$ unit
(iii) Inductance	<input type="radio"/> C $10\sqrt{2}$ unit
(iv) Average power in a cycle	<input type="radio"/> D $250\sqrt{2}$ unit



Watch Video Solution

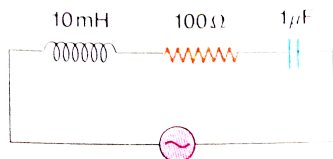5. Referring to the given circuit, match the following .



$$V = 10 \sin \omega t$$

Fig 2.49

Column I	Column II
(i) When $\omega = 8000$ rad/s	(A) peak current in the circuit is less than 0.1 A
(ii) When $\omega = 10000$ rad/s	(B) voltage and current across the circuit are in the same phase
(iii) When $\omega = 1000$ rad/s	(C) voltage leads the current across the circuit
(iv) When $\omega = 10500$ rad/s, if $R = 50 \Omega$ instead of $100 \Omega$	(D) current leads the voltage across the circuit



Watch Video Solution

Entrance Corner Comprehension Type

1. A series combination of an inductor of self-inductance  $L$ , capacitor of capacitance  $C$  and resistor  $R$  is connected to an alternating voltage source of  $V = V_0 \sin \omega t$ . The current through the circuit is  $I = I_0 \sin(\omega t - \theta)$

,where 
$$I_0 = \frac{V_0}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$
 and

$$\theta = \tan^{-1} \frac{1}{R} \left( \omega L - \frac{1}{\omega C} \right).$$

Now that, the frequency of both voltage and current is  $f = \frac{\omega}{2\pi}$ . The rms value of these parameters during one complete cycles are

$$V_{rms} = \frac{V_0}{\sqrt{2}} \text{ and } I_{rms} = \frac{I_0}{\sqrt{2}} \quad \text{respectively.}$$

These values are shown in alternating voltmeter and ammeter.

The power consumed by the circuit  $P=VI$ . The mean value i.e., the effective power of the circuit in a complete cycle is

$\bar{P} = V_{rms} I_{rms} \cos \theta$ . This  $\cos \theta$  is termed the power factor.

$V = V_0 \sin \omega t$  electromotive force is applied to an alternating circuit consisting of resistance  $R'$  and an inductor of self-inductance  $L$ . The phase difference between the voltage and current is

A.  $90^\circ$

B.  $\tan^{-1} \frac{\omega L}{R'}$

C.  $\tan^{-1} \frac{R'}{\sqrt{R'^2 + \omega^2 L^2}}$

D.  $\frac{\sqrt{R'^2 + \omega^2 L^2}}{R'}$

**Answer: B**



**Watch Video Solution**

2. A series combination of an inductor of self-inductance  $L$ , capacitor of capacitance  $C$  and resistor  $R$  is connected to an alternating



voltage source of  $V = V_0 \sin \omega t$ . The current through the circuit is  $I = I_0 \sin(\omega t - \theta)$

,where 
$$I_0 = \frac{V_0}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$
 and

$$\theta = \tan^{-1} \frac{1}{R} \left( \omega L - \frac{1}{\omega C} \right).$$

Now that, the frequency of both voltage and current is  $f = \frac{\omega}{2\pi}$ . The rms value of these

parameters during one complete cycles are

$$V_{rms} = \frac{V_0}{\sqrt{2}} \text{ and } I_{rms} = \frac{I_0}{\sqrt{2}} \quad \text{respectively.}$$

These values are shown in alternating voltmeter and ammeter.

The power consumed by the circuit  $P=VI$ . The mean value i.e., the effective power of the

circuit in a complete cycle is

$\bar{P} = V_{rms} I_{rms} \cos \theta$ . This  $\cos \theta$  is termed the power factor.

the power factor of the circuit is question (i) is

A. zero

B.  $\frac{\omega L}{R'}$

C.  $\frac{R'}{\sqrt{R'^2 + \omega^2 L^2}}$

D.  $\frac{\sqrt{R'^2 + \omega^2 L^2}}{R'}$

**Answer: C**



**Watch Video Solution**

**3.** A series combination of an inductor of self-inductance  $L$ , capacitor of capacitance  $C$  and resistor  $R$  is connected to an alternating voltage source of  $V = V_0 \sin \omega t$ . The current through the circuit is  $I = I_0 \sin(\omega t - \theta)$

,where 
$$I_0 = \frac{V_0}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$
 and

$$\theta = \tan^{-1} \frac{1}{R} \left( \omega L - \frac{1}{\omega C} \right).$$

Now that, the frequency of both voltage and current is  $f = \frac{\omega}{2\pi}$ . The rms value of these parameters during one complete cycles are

$V_{rms} = \frac{V_0}{\sqrt{2}}$  and  $I_{rms} = \frac{I_0}{\sqrt{2}}$  respectively.

These values are shown in alternating voltmeter and ammeter.

The power consumed by the circuit  $P=VI$ . The mean value i.e., the effective power of the circuit in a complete cycle is

$\bar{P} = V_{rms} I_{rms} \cos \theta$ . This  $\cos \theta$  is termed the power factor.

In the circuit in question (i) the inductor is replaced by a pure capacitor, the phase difference between the current and terminal voltage of the capacitor is

A.  $-90^\circ$

B. between  $-90^\circ$  and zero

C. zero

D.  $+90^\circ$

**Answer: A**



**Watch Video Solution**

4. A series combination of an inductor of self-inductance  $L$ , capacitor of capacitance  $C$  and resistor  $R$  is connected to an alternating

voltage source of  $V = V_0 \sin \omega t$ . The current through the circuit is  $I = I_0 \sin(\omega t - \theta)$

,where 
$$I_0 = \frac{V_0}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$
 and

$$\theta = \tan^{-1} \frac{1}{R} \left( \omega L - \frac{1}{\omega C} \right).$$

Now that, the frequency of both voltage and current is  $f = \frac{\omega}{2\pi}$ . The rms value of these

parameters during one complete cycles are

$$V_{rms} = \frac{V_0}{\sqrt{2}} \text{ and } I_{rms} = \frac{I_0}{\sqrt{2}} \quad \text{respectively.}$$

These values are shown in alternating voltmeter and ammeter.

The power consumed by the circuit  $P=VI$ . The mean value i.e., the effective power of the

circuit in a complete cycle is

$\bar{P} = V_{rms} I_{rms} \cos \theta$ . This  $\cos \theta$  is termed the power factor.

The power factor of the circuit in question (iii) is

- A. -1
- B. zero
- C. between zero and 1
- D. 1

**Answer: C**



5. A series combination of an inductor of self-inductance  $L$ , capacitor of capacitance  $C$  and resistor  $R$  is connected to an alternating voltage source of  $V = V_0 \sin \omega t$ . The current through the circuit is  $I = I_0 \sin(\omega t - \theta)$

,where 
$$I_0 = \frac{V_0}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$
 and

$$\theta = \tan^{-1} \frac{1}{R} \left( \omega L - \frac{1}{\omega C} \right).$$

Now that, the frequency of both voltage and current is  $f = \frac{\omega}{2\pi}$ . The rms value of these parameters during one complete cycles are



$$V_{rms} = \frac{V_0}{\sqrt{2}} \text{ and } I_{rms} = \frac{I_0}{\sqrt{2}} \quad \text{respectively.}$$

These values are shown in alternating voltmeter and ammeter.

The power consumed by the circuit  $P=VI$ . The mean value i.e., the effective power of the circuit in a complete cycle is  $\bar{P} = V_{rms} I_{rms} \cos \theta$ . This  $\cos \theta$  is termed the power factor.

The voltage applied in an LCR circuit having

$$R = 10\Omega, L = 10mH \text{ and } C = 1\mu F \text{ is}$$

$V = 20 \sin \omega t$  volt. For what frequency of the applied voltage will the current reach its peak value?

A. 159 Hz

B. 1592 Hz

C.  $1.59 \times 10^4 \text{ Hz}$

D.  $1.59 \times 10^5 \text{ Hz}$

**Answer: B**



**Watch Video Solution**

**6.** A series combination of an inductor of self-inductance  $L$ , capacitor of capacitance  $C$  and resistor  $R$  is connected to an alternating

voltage source of  $V = V_0 \sin \omega t$ . The current through the circuit is  $I = I_0 \sin(\omega t - \theta)$

,where 
$$I_0 = \frac{V_0}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$
 and

$$\theta = \tan^{-1} \frac{1}{R} \left( \omega L - \frac{1}{\omega C} \right).$$

Now that, the frequency of both voltage and current is  $f = \frac{\omega}{2\pi}$ . The rms value of these

parameters during one complete cycles are

$$V_{rms} = \frac{V_0}{\sqrt{2}} \text{ and } I_{rms} = \frac{I_0}{\sqrt{2}} \quad \text{respectively.}$$

These values are shown in alternating voltmeter and ammeter.

The power consumed by the circuit  $P=VI$ . The mean value i.e., the effective power of the

circuit in a complete cycle is

$\bar{P} = V_{rms} I_{rms} \cos \theta$ . This  $\cos \theta$  is termed the power factor.

The phase difference between the voltage and peak current in question (v) is

A. zero

B.  $-90^\circ$

C.  $+90^\circ$

D.  $180^\circ$

**Answer: A**



7. A series combination of an inductor of self-inductance  $L$ , capacitor of capacitance  $C$  and resistor  $R$  is connected to an alternating voltage source of  $V = V_0 \sin \omega t$ . The current through the circuit is  $I = I_0 \sin(\omega t - \theta)$

,where 
$$I_0 = \frac{V_0}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$
 and

$$\theta = \tan^{-1} \frac{1}{R} \left( \omega L - \frac{1}{\omega C} \right).$$

Now that, the frequency of both voltage and current is  $f = \frac{\omega}{2\pi}$ . The rms value of these parameters during one complete cycles are

$$V_{rms} = \frac{V_0}{\sqrt{2}} \text{ and } I_{rms} = \frac{I_0}{\sqrt{2}} \quad \text{respectively.}$$

These values are shown in alternating voltmeter and ammeter.

The power consumed by the circuit  $P=VI$ . The mean value i.e., the effective power of the circuit in a complete cycle is

$\bar{P} = V_{rms} I_{rms} \cos \theta$ . This  $\cos \theta$  is termed the power factor.

Which element is responsible for the power consumption in an alternating current circuit?

A. only resistor

B. only inductor

C. only capacitor

D. resistor, inductor and capacitor

**Answer: A**



**Watch Video Solution**

**8.** A series combination of an inductor of self-inductance  $L$ , capacitor of capacitance  $C$  and resistor  $R$  is connected to an alternating voltage source of  $V = V_0 \sin \omega t$ . The current through the circuit is  $I = I_0 \sin(\omega t - \theta)$

,where 
$$I_0 = \frac{V_0}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}} \text{ and}$$

$$\theta = \tan^{-1} \frac{1}{R} \left( \omega L - \frac{1}{\omega C} \right).$$

Now that, the frequency of both voltage and current is  $f = \frac{\omega}{2\pi}$ . The rms value of these parameters during one complete cycles are

$$V_{rms} = \frac{V_0}{\sqrt{2}} \text{ and } I_{rms} = \frac{I_0}{\sqrt{2}} \quad \text{respectively.}$$

These values are shown in alternating voltmeter and ammeter.

The power consumed by the circuit  $P=VI$ . The mean value i.e., the effective power of the circuit in a complete cycle is

$$\bar{P} = V_{rms} I_{rms} \cos \theta. \text{ This } \cos \theta \text{ is termed the}$$



power factor.

The frequency of the applied alternating voltage in an ac circuit is 50 Hz. Resistance and self inductance are  $37.6\Omega$  and 120 mH . The phase difference between the voltage and current is

A. zero

B.  $45^\circ$

C.  $60^\circ$

D.  $90^\circ$

**Answer: B**



[Watch Video Solution](#)

**9.** Transformer is a device used to increase or decrease the voltage in the transmission line according to requirement, Generally the input line voltage is fed in a primary coil and the output line voltage is obtained from the terminals of another coil. In an ideal transformer, the primary and secondary coils are linked in such a way that there is no loss of magnetic flux and electrical energy.

In an ideal transformer, if the number of turns

and input voltage across the terminals of the primary coils be  $N_1$  and  $V_1$ , then the output voltage at the two terminals of the secondary coil  $V_2 = V_1 \cdot \frac{N_2}{N_1}$ , where  $N_2$  is the number of turns in the secondary coil .

The ratio of number of turns of the primary and secondary coils of an ideal transformer is 2:1 IF the input voltage is 440 V, then output voltage is if the input power of the transformer be 44 W, then output power is In the above mentioned transformer the input and output currents are respectively.

A. 220 V

B. 440 V

C. 880V

D. None of these

**Answer: A**



**Watch Video Solution**

**10.** Transformer is a device used to increase or decrease the voltage in the transmission line according to requirement, Generally the input

line voltage is fed in a primary coil and the output line voltage is obtained from the terminals of another coil. In an ideal transformer, the primary and secondary coils are linked in such a way that there is no loss of magnetic flux and electrical energy.

In an ideal transformer, if the number of turns and input voltage across the terminals of the primary coils be  $N_1$  and  $V_1$ , then the output voltage at the two terminals of the secondary coil  $V_2 = V_1 \cdot \frac{N_2}{N_1}$ , where  $N_2$  is the number of turns in the secondary coil .

In question (i) if the input power of the transformer be 44 W, then output power is

A. 22 W

B. 44 W

C. 88 W

D. None of these

**Answer: B**



**Watch Video Solution**

**11.** Transformer is a device used to increase or decrease the voltage in the transmission line according to requirement, Generally the input line voltage is fed in a primary coil and the output line voltage is obtained from the terminals of another coil In an ideal transformer, the primary and secondary coils are linked in such a way that there is no loss of magnetic flux and electrical energy.

In an ideal transformer, if the number of turns and input voltage across the terminals of the primary coils be  $N_1$  and  $V_1$ , then the output

voltage at the two terminals of the secondary coil  $V_2 = V_1 \cdot \frac{N_2}{N_1}$ , where  $N_2$  is the number of turns in the secondary coil .

In the above mentioned transformer the input and output currents are respectively.

- A. 100 mA,100mA
- B. 200 mA,200mA
- C. 100mA,200mA
- D. 200mA,100mA

**Answer: C**







[Watch Video Solution](#)

## Entrance Corner Integer Answer Type

1. A resistance and a capacitor is connected in series with an alternating voltage of rms value 13 V. The terminal voltage of the resistor is 12V and that across the capacitor is  $(n+0.38)V$ . What is the value of  $n$ ?



[Watch Video Solution](#)

2. The current and voltage in an ac circuit are

$$I = \sin\left(100t + \frac{\pi}{3}\right) \text{ A} \quad \text{and} \quad V = 20\sin 100t \text{ V.}$$

Calculate the power of the circuit in W.



[Watch Video Solution](#)

3. In a series LCR circuit the capacitance  $C$  is replaced by  $2C$ . To keep the resonance frequency unchanged, the inductance has to be replaced by an inductance of  $L'$ . Find the ratio of  $L$  and  $L'$ .





[Watch Video Solution](#)

4. An alternating voltage 5V of frequency 50 Hz is connected to a series LCR circuit. The potential difference across the inductor and resistor are 6V and 4V respectively. What is the voltage across the capacitor (in V)?



[Watch Video Solution](#)

5. In a series LCR circuit  $R = 1k\Omega$ ,  $C = 2\mu F$  and potential difference across R is 2V. At

resonance  $\omega = 200 \text{ rad. s}^{-1}$ . What is the potential difference (in V) across L at resonance?



[Watch Video Solution](#)

6. In a series LCR circuit  $R=25\Omega, L=10 \text{ mH}$  and  $C = 1\mu F$ . The circuit is connected with an ac source of variable frequency . What is the Q-factor of the circuit?



[Watch Video Solution](#)


7. A current of 50mA flows through a  $4\mu F$  capacitor connected to a 500 Hz ac source. The terminal potential difference (in V) across the capacitor is  $(\eta + 0.98)$  .what is the value of  $\eta$ ? ( $\pi=3.14$ )



[Watch Video Solution](#)

8. In the figure an LCR series circuit is shown. What would be the ammeter reading in

ampere?

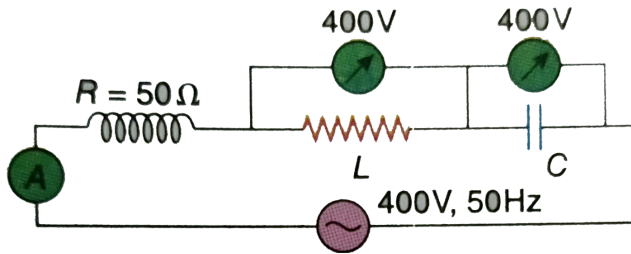

[Watch Video Solution](#)

## Examination Archive With Solutions Wbchse

1. An ac having a peak value 1.41 A is used to heat a wire. A dc producing the same heating rate will be approximately

A. 1.41 A

B. 2.0 A

C. 0.705 A

D. 1.0 A

**Answer: D**



**Watch Video Solution**

2. An ac voltage  $e = E_0 \sin \omega t$  is applied across an ideal inductor of self-inductance [L].

Write down the peak current.



[Watch Video Solution](#)

3. The instantaneous voltage from an ac source is given by  $e=200\sin 314t$  volt. Find the rms voltage .What is the frequency of the source?



[Watch Video Solution](#)

4. State the condition under which the phenomenon of resonance occurs in series



LCR circuit when ac voltage is applied. In a series LCR circuit, the current is in same phase with voltage. Calculate the value of self-inductance if the capacitor used is  $20\mu F$  and resistance used is 10 ohm with the ac source of frequency 50 Hz.



**Watch Video Solution**

5. A series LCR circuit acts as a purely resistive circuit, when

$$A. \omega L > \frac{1}{\omega C}$$

B.  $\omega L < \frac{1}{\omega C}$

C.  $\omega L = \frac{1}{\omega C}$

D. None of these

**Answer: C**



**Watch Video Solution**

**6. What is Q-factor?**



**Watch Video Solution**

7. Define the term 'root mean square' (rms) value of alternating current.



[Watch Video Solution](#)

8. An ac source  $e = E_0 \sin \omega t$  is applied across an ideal inductor of inductance  $L$ . Show mathematically that the current lags the voltage by a phase angle of  $\frac{\pi}{2}$ .



[Watch Video Solution](#)

9. IF  $L$  is 100mH and the applied ac source frequency be 50 Hz, find the inductive reactance in the above case.



[Watch Video Solution](#)

10. Define wattless current.



[Watch Video Solution](#)

**11.** Show that in ac circuit the average power dissipated per cycle in a pure inductor is zero.



**Watch Video Solution**

**12.** Compare between inductive reactance and capacitive reactance.



**Watch Video Solution**

**13.** State the factors on which the peak value of alternating emf depends.



**Watch Video Solution**

**14.** In an LCR series combination,  $R=400\Omega$ ,  $L=100\text{ mH}$  and  $C=1\mu F$ . This combination is connected to a  $25\sin 2000t$  volt voltage source. Find the impedance of the circuit and the peak value of the circuit current.



**Watch Video Solution**

**15.** State the working principle of ac generator.



**Watch Video Solution**

**16.** Why is the use of ac voltage preferred over dc voltage?



**Watch Video Solution**

17. The power factor of LR circuit is  $\frac{1}{\sqrt{3}}$ . IF the frequency of ac be doubled, what will be the power factor?



[Watch Video Solution](#)

18. IF the rotating speed of a dynamo is doubled, the induced electromotive force will be

A. doubled



B. halved

C. four times as much

D. unchanged

**Answer: A**



**Watch Video Solution**

**19.** The number of turns of the primary and secondary of a transformer are 500 and 5000 respectively. The primary is connected to a 20

V, 50Hz ac supply. The output of the secondary will be

- A. 2V,50Hz
- B. 200 V,50 Hz
- C. 200V,5 Hz
- D. 200V,500Hz

**Answer: B**



**Watch Video Solution**

20. What is the rms value of the current

$$i = 5\sqrt{2} \sin 100\pi t \text{ A?}$$




[Watch Video Solution](#)

**Examination Archive With Solutions Wbjee**

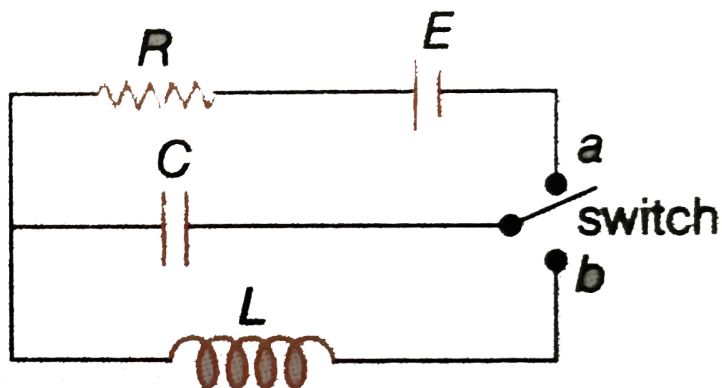1. In the circuit shown below , the switch is kept in position a for a long time and is then thrown to position b. The amplitude of the

resulting oscillating current is given by



A.  $E\sqrt{L/C}$

B.  $E/R$

C. infinity

D.  $E\sqrt{C/L}$

**Answer: D**



**Watch Video Solution**

2. When the frequency of the ac voltage applied to a series LCR circuit is gradually increased from a low value, the impedance of the circuit.

- A. monotonically increases
- B. first increases and then decreases
- C. first decreases and then increases
- D. monotonically decreases

**Answer: C**



**Watch Video Solution**

3. An alternating current is flowing through a series LCR circuit. IT is found that the current reaches a value of 1mA at both 200 Hz and 800Hz frequency. What is the resonance frequency of the circuit?

A. 600 Hz

B. 300 Hz

C. 500 Hz

D. 400 Hz

**Answer: D**



**Watch Video Solution**

**Examination Archive With Solutions Jee Main**

1. An inductor ( $L=0.03\text{H}$ ) and a resistor ( $R=0.15\text{k}\Omega$ ) are connected in series to a battery of 15 V emf in a circuit shown below. The key  $K_1$  has

been kept closed for a long time. Then at  $t=0$ ,  $K_1$  is opened and key  $K_2$  is closed simulatenously. At  $t=1$  ms, the current in the circuit will be ( $e^5 \cong 150$ )

A. 100 mA

B. 67 mA

C. 6.7mA

D. 0.67 mA


**Answer: D**



**View Text Solution**







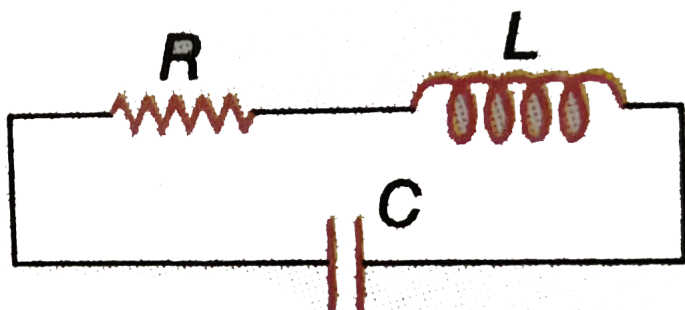2. An LCR circuit is equivalent to a damped pendulum. In an LCR circuit the capacitor is charged to  $Q_0$  and then connected to the L and R as shown below:



If the student plots graphs of the square of maximum charge ( $Q_{\max}^2$ ) on the capacitor with time ( $t$ ) for two different values  $L_1$  and  $L_2$  ( $L_1 > L_2$ ) of  $L$  then which of the following

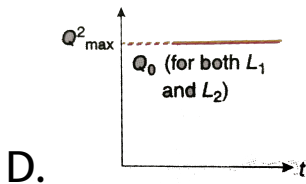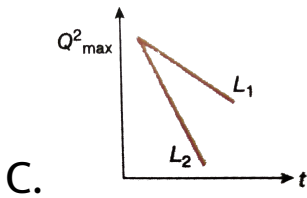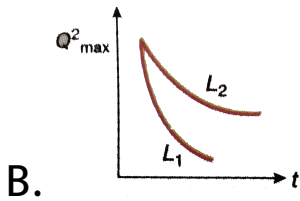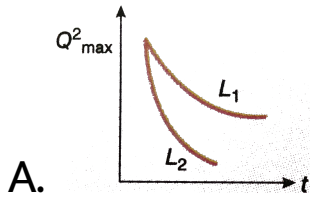represents this graph correctly?(plots are schematic are not drawn to scale)



**Answer: A**



Watch Video Solution

3. An arc lamp requires a direct current of 10A at 80V to function . It is connected to a 220V(rms), 50 Hz ac supply, the series inductor needed for it to work is close to

A. 80 H

B. 0.08 H

C. 0.044 H

D. 0.065 H

**Answer: D**



**Watch Video Solution**

4. For an RLC circuit driven with voltage of amplitude  $v_m$  and frequency  $\omega_0 = \frac{1}{\sqrt{LC}}$  the current exhibits resonance. The quality factor,  $Q$  is given by

A.  $\frac{R}{(\omega_0 C)}$

B.  $\frac{CR}{\omega_0}$

C.  $\frac{\omega_0 L}{R}$

D.  $\frac{\omega_0 R}{L}$

**Answer: C**



**Watch Video Solution**

5. In an ac circuit, the instantaneous emf and current are given by

$$e = 100 \sin 30t, i = 20 \sin\left(30t - \frac{\pi}{4}\right).$$

In one cycle of ac, the average power consumed by the circuit and the wattless current are, respectively

A.  $\frac{50}{\sqrt{2}}, 0$

B. 50, 0

C. 50, 10

D.  $\frac{1000}{\sqrt{2}}, 10$

**Answer: D**



**Watch Video Solution**

**Examination Archive With Solutions Aipmt**

1. A transformer having efficiency of 90% is working on 200 V and 3kW power supply. If the current in the secondary coil is 6A, the voltage across the secondary coil and the current in the primary coil respectively are

A. 300V,15A

B. 450V,15A

C. 450V,13.5A

D. 600V,15A

**Answer: B**



Watch Video Solution

2. A resistance  $R$  draws power  $P$  when connected to an ac source. IF an inductance is now placed in series with the resistance, such that the impedance of the circuit becomes  $Z$ , the power drawn will be:

A.  $P \left( \frac{R}{Z} \right)^2$

B.  $P \sqrt{\frac{R}{Z}}$

C.  $P \left( \frac{R}{Z} \right)$



D. P

**Answer: A**



**Watch Video Solution**

**Examination Archive With Solutions Neet**

1. A small signal voltage  $V(t) = V_0 \sin \omega t$  is applied across an ideal capacitor C.

- A. over a full cycle, the capacitor  $C$  does not consume any energy from the voltage source
- B. current  $I(t)$  is in phase with voltage  $V(t)$
- C. current  $I(t)$  leads voltage  $V(t)$  by  $180^\circ$
- D. current  $I(t)$  lags voltage  $V(t)$  by  $90^\circ$

**Answer: A**



**Watch Video Solution**

2. An inductor  $20\text{mH}$ , a capacitor  $50\mu\text{F}$  and a resistor  $40\Omega$  are connected in series across a source of emf  $V=10\sin 340t$ . The power loss in ac circuit is

A.  $0.67\text{W}$

B.  $0.76\text{W}$

C.  $0.89\text{W}$

D.  $0.51\text{W}$

**Answer: D**



Watch Video Solution

3. An inductor  $20\text{mH}$ , a capacitor  $100\mu\text{F}$  and a resistor  $50\Omega$  are connected in series across a source of emf  $V=10\sin 314t$ . The power loss in the circuit is

A.  $2.74\text{ W}$

B.  $0.43\text{ W}$

C.  $0.79\text{ W}$

D.  $1.13\text{ W}$

**Answer: C**



**Watch Video Solution**

**Cbse Scanner**

**1. Mention the two characteristic properties of the material suitable for making core of a transformer.**



**Watch Video Solution**

2. State the underlying principle of a transformer. How is the large scale transmission of electrical energy over long distances done with the use of transformer?



[Watch Video Solution](#)

3. An alternating voltage given by  $V=140\sin 314t$  is connected across a pure resistor of  $50\Omega$ . Find the frequency of the source



[Watch Video Solution](#)

4. An alternating voltage given by  $V=140\sin 314t$  is connected across a pure resistor of  $50\Omega$ . Find the rms current through the resistor.



[Watch Video Solution](#)

5. In an A.C. circuit, the potential difference across an inductance and a resistance joined in series are respectively 16V and 20V. The total potential difference across the circuit is



[Watch Video Solution](#)

6. For a given ac  $i = i_m \sin \omega t$ , show that the average power dissipated in a resistor  $R$  over complete cycle is  $\frac{1}{2}i_m^2 R$ .



[Watch Video Solution](#)

7. A light bulb is rated at 100 W for a 220V ac supply. Calculate the resistance of the bulb.



[Watch Video Solution](#)



8. Why is the use of ac voltage preferred over dc voltage? Given two reasons.



[Watch Video Solution](#)

9. A voltage  $V_0 \sin \omega t$  is applied to a series LCR circuit, Derive the expression for the average power dissipated over a cycle.

Under what condition is (i) no power dissipated even though the current flows

through the circuit,(ii) maximum power dissipated in the circuit?



[Watch Video Solution](#)

**10.** Define the term 'quality factor' of resonance in series LCR circuit. What is its SI unit?



[Watch Video Solution](#)

**11.** Show that the average power consumed in an inductor  $L$  connected to an source is zero.



**Watch Video Solution**

**12.** In a series LR circuit,  $X_L = R$  and the power factor of the circuit is  $P_1$ . When a capacitor with capacitance  $C$  such that  $X_C = X_L$  is put in series, the power factor becomes  $P_2$ . Find out  $P_1 / P_2$ .



**Watch Video Solution**

**13.** State the principle of an ac generator.



**Watch Video Solution**

**14.** Explain briefly, with the help of labelled diagram, and obtain the expression for the emf generated in the rotating coil in the magnetic field.



**Watch Video Solution**

**15.** Draw a schematic diagram showing the nature of the alternating emf generated by the rotating coil in the magnetic field during one cycle.




**Watch Video Solution**

**16.** When an ac source is connected to an ideal capacitor, show that the average power supplied by the source over a complete cycle is zero.



**Watch Video Solution**

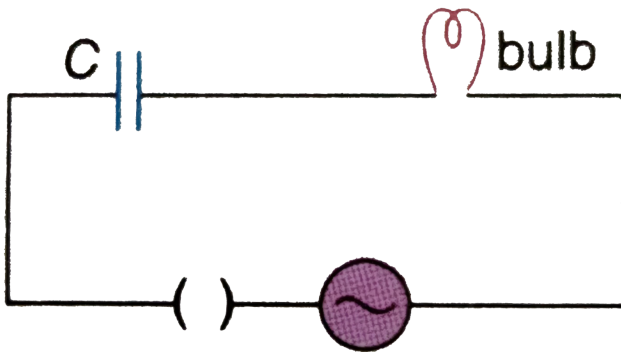17. A bulb is connected in series with a variable capacitor and an ac source as shown . What happens to the brightness of the bulb when the key is plugged in an capacitance of the capacitor is gradually reduced?



[Watch Video Solution](#)


**18.** In a series LCR circuit connected to an ac source of voltage  $v = v_m \sin \omega t$ , use phasor diagram to derive an expression for the current in the circuit. Hence obtain the expression for the power dissipated in the circuit. Show that power dissipated at resonance is maximum.



**Watch Video Solution**

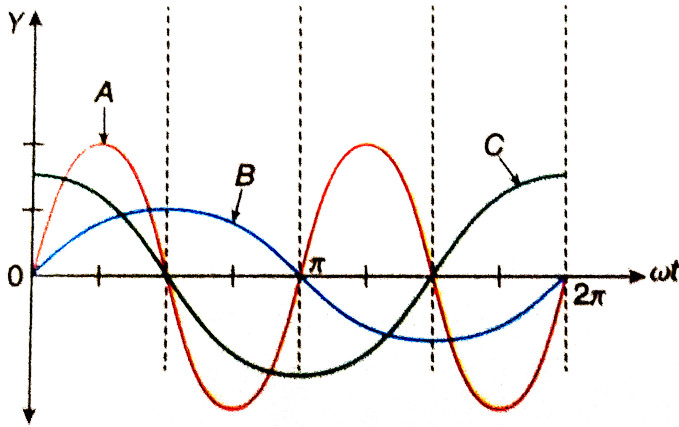**19.** A diode 'X' is connected to an ac source  $V = V_0 \sin \omega t$ . The variation of voltage, current

and power in one cycle is shown in the following graph:



Identify the device 'X'.




[View Text Solution](#)

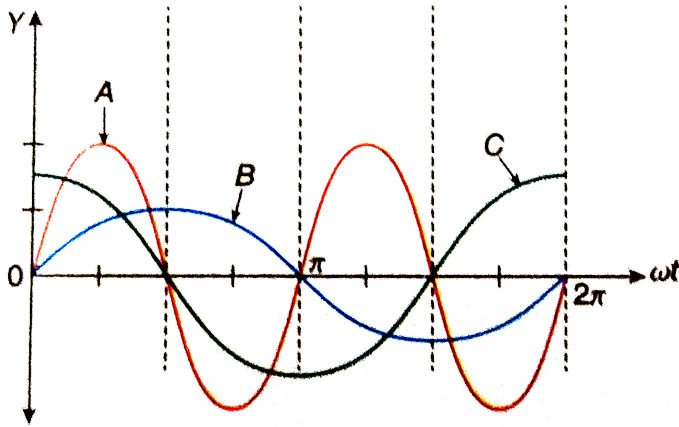20. A device 'X' is connected to an ac source

$V = V_0 \sin \omega t$ . The variation of voltage, current



and power in one cycle is shown in the following graph:



Which of the curves A, B and C represent the voltage , current and the power consumed in the circuit ? Justify your answer .




[Watch Video Solution](#)

21. How does its impedance vary with frequency of the ac source ? Show graphically.



**Watch Video Solution**

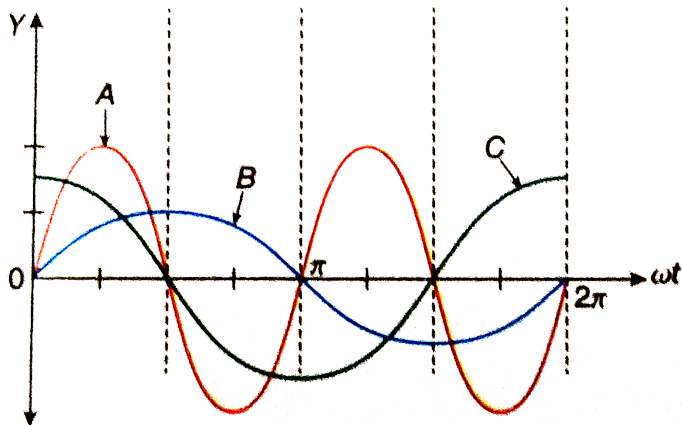22. A device 'X' is connected to an ac source  $V = V_0 \sin \omega t$ . The variation of voltage, current and power in one cycle is shown in the following graph:




Which of the curves A,B and C represent the voltage , current and the power consumed in the circuit ? Justify your answer .



**Watch Video Solution**

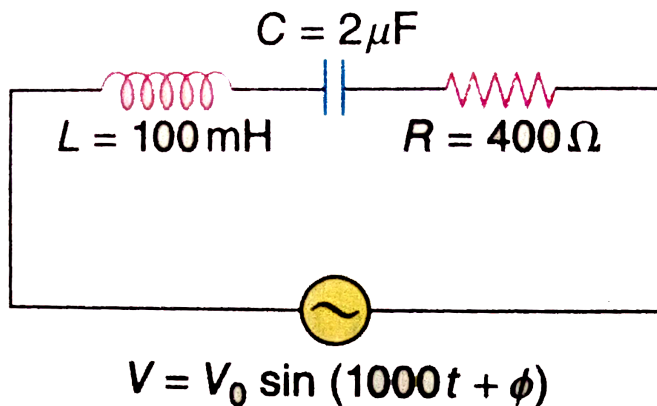**23.** Find the value of the phase difference between the current and the voltage in the


series LCR circuit shown below. Which one leads in phase: current or voltage?



[Watch Video Solution](#)

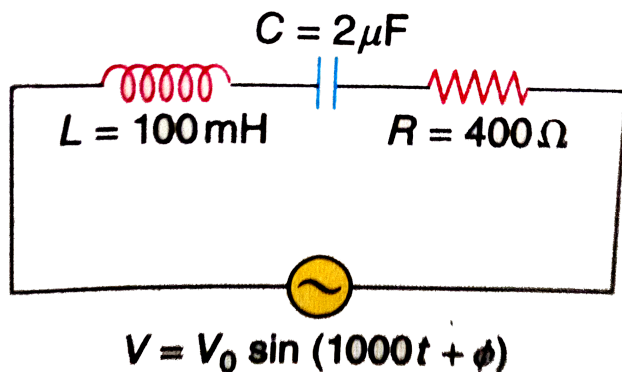24. Without making any other change, find the value of the additional capacitor  $C_1$ , to be connected in parallel with the capacitor  $C$ , in

order to make the power factor of the circuit unity.



[Watch Video Solution](#)

25. Draw a labelled diagram of a step-up transformer. Obtain the ratio of secondary to

primary voltage in terms of number of turns and current in the two coils.



[Watch Video Solution](#)

**26.** A power transmission line feeds input power at 2200 V to a step-down transformer with its primary windings having 3000 turns. Find the number of turns in the secondary to get the power output at 220 V.



[Watch Video Solution](#)

**27.** A device X is connected across an ac source of voltage  $V = V_0 \sin \omega t$ . The current through X is given as  $I = I_0 \sin\left(\omega t + \frac{\pi}{2}\right)$ .

Identify the device X and write the expression for its reactance.



**Watch Video Solution**

**28.** A device X is connected across an ac source of voltage  $V = V_0 \sin \omega t$ . The current through X is given as  $I = I_0 \sin\left(\omega t + \frac{\pi}{2}\right)$ .

Draw graphs showing variations of voltage

and current with time over one cycle of ac, for X.



[Watch Video Solution](#)

**29.** A device X is connected across an ac source of voltage  $V = V_0 \sin \omega t$ . The current through X is given as  $I = I_0 \sin\left(\omega t + \frac{\pi}{2}\right)$ .

Draw the phasor diagram for the device X.



[Watch Video Solution](#)



**30.** A device X is connected across an ac source of voltage  $V = V_0 \sin \omega t$ . The current through X is given as  $I = I_0 \sin\left(\omega t + \frac{\pi}{2}\right)$ .

Device X is a capacitor.



**Watch Video Solution**

**31.** The teachers of Geeta's school took the students on a study trip to a power generating station, located nearly 200km away from the city. The teacher explained that

electrical energy is transmitted over such a long distance to their city. In the form of alternating current (ac) raised to a high voltage. At the receiving end in the city, the voltage is reduced to operate the devices. As a result, the power loss is reduced. Geeta listened to the teacher and asked questions about how the ac is converted to a higher or lower voltage.

Name the device used to change the alternating voltage to a higher or lower value.



**Watch Video Solution**

**32.** The teachers of Geeta's school took the students on a study trip to a power generating station, located nearly 200km away from the city. The teacher explained that electrical energy is transmitted over such a long distance to their city. In the form of alternating current (ac) raised to a high voltage. At the receiving end in the city, the voltage is reduced to operate the devices. As a result, the power loss is reduced. Geeta listened to the teacher and asked questions about how the ac is converted to a higher or

lower voltage.

Explain with an example , how power loss is reduced if the energy is transmitted over long distances as an alternating current rather than a direct current .



[Watch Video Solution](#)

**33.** The teachers of Geeta's school took the students on a study trip to a power generating station, located nearly 200km away from the city. The teacher explained that

electrical energy is transmitted over such a long distance to their city. In the form of alternating current (ac) raised to a high voltage. At the receiving end in the city, the voltage is reduced to operate the devices. As a result, the power loss is reduced. Geeta listened to the teacher and asked questions about how the ac is converted to a higher or lower voltage.

Write two values each shown by the teachers and geeta,



**Watch Video Solution**

