



PHYSICS

BOOKS - CHHAYA PHYSICS (BENGALI ENGLISH)

SEMICONDUCTORS AND ELECTRONICS

Numerical Examples

1. An intrinsic semiconductor has 5×10^{28} atoms and the carrier concentration 1.5×10^{16} . If it is doped by a pentavalent impurity in the ratio $1:10^6$, then calculate number density of holes as charge carriers.



[Watch Video Solution](#)

2. A semiconductor has equal electron and hole concentrations of $6 \times 10^8 \text{ m}^{-3}$. On doping with a certain impurity, the electron concentration of the semiconductor increases to $8 \times 10^{12} \text{ m}^{-3}$. (i) What type of semiconductor is obtained on doping? (ii) Calculate the new hole concentration of the semiconductor.



[Watch Video Solution](#)

3. A semiconductor has the electron concentration $0.45 \times 10^{12} \text{m}^{-3}$ and the hole concentration $5 \times 10^{20} \text{m}^{-3}$. Calculate the conductivity of the material of this semiconductor.

Given, Electron mobility = $0.135 \text{m}^2 \cdot \text{V}^{-1} \cdot \text{s}^{-1}$ and hole mobility = $0.048 \text{m}^2 \cdot \text{V}^{-1} \cdot \text{s}^{-1}$.



[Watch Video Solution](#)

4. The potential barrier of a p-n junction diode is 0.4 V. If the thickness of the depletion region be , what will be 4.0×10^{-7} the electric field intensity in this region? An electron from the n-region moves towards

the p-n junction with velocity $6 \times 10^5 \text{ m. s}^{-1}$. What will be the velocity of the electron with which it enters the p-region?

 [Watch Video Solution](#)

5. In a common-emitter circuit, collector-emitter voltage is fixed at 5V. For base currents $30 \mu\text{A}$ and $40 \mu\text{A}$, the collector currents are 8.2 mA and 9.4 mA respectively. Calculate current gain of the circuit.

 [Watch Video Solution](#)

6. The collector current in an n-p-n transistor is 10 mA. If 99.5% of the emitted electrons reach the collector, determine the emitter current, base current and amplification factor of the transistor.



[Watch Video Solution](#)

7. An n-p-n transistor is kept in common-emitter configuration. Amplification factor of the transistor is 100. If the collector current is changed by 1 mA, what will be the corresponding change in the emitter current?



[Watch Video Solution](#)

8. The input resistance of a silicon transistor is 100Ω . Base current is changed by $40\mu\text{ A}$ which results in a change in collector current by 2 mA . This transistor is used as a common emitter amplifier with a load resistance of $4\text{ k}\Omega$. What is the voltage of the amplifier?

 [Watch Video Solution](#)

Section Related Questions

1. What do you mean by a semiconductor ?

 [Watch Video Solution](#)

2. Given two examples of each of conductor insulator and semiconductor.

 [Watch Video Solution](#)

3. How does the resistance of a semiconductor vary with temperature ?

 [Watch Video Solution](#)

4. Explain the electrical conductivity of a semiconductor with the help of band theory.

 [Watch Video Solution](#)

5. Distinguish between a metal and an insulator with the help of energy band diagram.

 [Watch Video Solution](#)

6. What do you mean by a hole ? How is it produced ?

 [Watch Video Solution](#)

7. Write down the difference between conductor semiconductor and insulator.

 [Watch Video Solution](#)

8. What are the charge carriers in (i) conductors (ii) insulators and (iii) semiconductors ?

 [Watch Video Solution](#)

9. Draw the energy band diagram of an intrinsic semiconductor.

 [Watch Video Solution](#)

10. What is meant by doping in semiconductors?

 [Watch Video Solution](#)

11. What do you mean by n-type [HS'01] and p-type semiconductors?

Or , What are p-type semiconductors?



Watch Video Solution

12. Explain how an intrinsic semiconductor can be converted into an n-type semiconductor and a p-type semiconductors. Draw the energy band diagrams of n-type and p-type semicon ductors.



Watch Video Solution

13. State the difference between n-type and p-type semiconductors.

 [Watch Video Solution](#)

14. What do you mean by donor atom and acceptor atom?

 [Watch Video Solution](#)

15. State the expression of the electrical conductivity of the material of a semiconductor in terms of the mobilities of electrons and holes.



[Watch Video Solution](#)



[Watch Video Solution](#)

16. Write the working principles of n-type and p-type semiconductors.



[Watch Video Solution](#)

17. What is a p-n junction diode?

Or, What is a junction diode?



[Watch Video Solution](#)

18. Explain the working principle of a p-n junction.



 [Watch Video Solution](#)

19. What do you mean by depletion layer?

 [Watch Video Solution](#)

20. Draw the characteristic curve of a semiconductor diode.

 [Watch Video Solution](#)

21. Draw the circuit diagram of a junction diode acting as a full-wave rectifier.



 [Watch Video Solution](#)

22. Why is a silicon diode better than a germanium diode in a rectifier circuit?

 [Watch Video Solution](#)

23. Draw the circuit diagram of a forward biased and reverse biased p-n junction diode.

 [Watch Video Solution](#)

24. What is rectification ? Explain with diagram how a p-n junction diode acts as a half-wave rectifier.



Watch Video Solution

25. Draw the circuit diagram of a half -wave rectifier using p-n junction diodes. Draw the input and output voltage form by a schematic graph.



Watch Video Solution

26. Explain what happens to the depletion layer ,if the junction is forward biased and reverse biased.



[Watch Video Solution](#)

27. What is a Zener diode?



[Watch Video Solution](#)

28. What is the breakdown of a diode?



[Watch Video Solution](#)

29. Draw the characteristic curve of a Zener diode.

From this curve, explain the speciality of a Zener diode in respect to a general semiconductor diode.



[Watch Video Solution](#)

30. For what purpose is the Zener diode generally used?



[Watch Video Solution](#)

31. Draw a circuit diagram to illustrate the action of a Zener diode as a voltage regulator.

Draw the current versus voltage characteristics curve of a Zener diode. Indicate the position of Zener voltage in the curve.



[Watch Video Solution](#)

32. What do you mean by the load regulation in a voltage regulator?

 [Watch Video Solution](#)

33. What is a light emitting diode (LED)?

 [Watch Video Solution](#)

34. Draw the characteristic curve of a LED. Can you recognise any difference from the characteristic curve of an ordinary semiconductor diode?

 [Watch Video Solution](#)

35. What is meant by a photodiode ? What are its main practical uses?

 [Watch Video Solution](#)

36. Draw the ampere-volt characteristic curve of a photodiode and mention the significance of its salient features.

 [Watch Video Solution](#)

37. What is a solar cell? How does a solar diode behave as a battery?

 [Watch Video Solution](#)

38. How many kinds of transistor are there? What is the main function of a transistor?

 [Watch Video Solution](#)

39. Draw the circuit diagrams of p-n-p and n-p-n transistors.

 [Watch Video Solution](#)

40. Show the structures of a p-n-p transistor and an n-p-n transistor with the help of diagrams.

 [Watch Video Solution](#)

41. What do you mean by current amplification factor?

 [Watch Video Solution](#)

42. What do you understand by active region, saturation region and cut-off region of a transistor?

 [Watch Video Solution](#)

43. What are the input and output resistance of a transistor in its CE mode?



Watch Video Solution

44. Draw few output characteristics of a given p-n-p transistor in CE configuration from which β can be obtained and explain how to determine it. (Take different I_B).



Watch Video Solution

45. What do you understand by the term current gain

$-\beta$ of a transistor ?



[Watch Video Solution](#)

46. Define α and β parameters of a transistor. What is

the relation between them?



[Watch Video Solution](#)

47. What do you mean by transistor switch?



[Watch Video Solution](#)

48. Draw the circuit diagram for plotting the characteristics of a transistor in common emitter configuration. What is current magnification?



Watch Video Solution

49. Draw a circuit diagram of a CE amplifier by using n-p-n transistor and show input and output voltages graphically.



Watch Video Solution

50. What do you mean by an oscillator ?



[Watch Video Solution](#)

51. Write down Barkhausen Criterion of oscillation. What is the importance of this criterion?



[Watch Video Solution](#)

52. What is feedback in an amplifier circuit?



[Watch Video Solution](#)

53. Derive the relationship between open loop gain and closed loop gain of an amplifier circuit with

reference to feedback ratio.



[Watch Video Solution](#)

54. Given a brief description of LC feedback oscillator.

What is the source of its input signal ? What is the

frequency of its output signal ?



[Watch Video Solution](#)

55. What is the practical utility of positive feedback

and negative feedback?



[Watch Video Solution](#)

Higher Order Thinking Skill Hots Questions

1. When a semiconductor is irradiated by light of definite wavelength its resistance decreases. Explain why.



[Watch Video Solution](#)

2. What happens if the amount of reverse bias in a p-n junction diode is gradually increased ?



[Watch Video Solution](#)

3. At absolute zero temperature the conductivities of both the insulators and the semiconductors are zero.

At any higher temperature the semiconductor may have some conductivity but for insulator it is zero.

Explain why.



[Watch Video Solution](#)

4. You are given two bars of same resistance, one of them is a conductor and the other is a semiconductor.

How will you distinguish them experimentally?



[Watch Video Solution](#)

5. Draw the voltage-current characteristics of a p-n junction and compare it with the characteristics of a resistor.

 [Watch Video Solution](#)

6. What is the effect of doping on the depletion layer of a p-n junction?

 [Watch Video Solution](#)

7. Why does the conductivity of a pure semiconductor increases with rise in temperature ?



 [Watch Video Solution](#)

8. In which kind of biasing of a p-n junction the net holes flows the n-region to the p-region ?

 [Watch Video Solution](#)

9. Explain why the resistance of a semiconductor decreases with increase in temperature.

 [Watch Video Solution](#)

10. In a transistor the base is made very thin. Explain the reason.

 [Watch Video Solution](#)

11. Why is a transistor called temperature- sensitive device?

 [Watch Video Solution](#)

12. In a transistor the forward bias is always small as compared to the reverse bias. Why?

 [Watch Video Solution](#)

13. Explain why the input resistance of a transistor is low while the output resistance is high.



Watch Video Solution

14. The gain of a common-emitter amplifier is given by $A_v = -g_m R_L$. Does it mean that if we keep on increasing R_L indefinitely, the gain of the amplifier will also increase indefinitely? Explain your answer.



Watch Video Solution

15. If the emitter and base of a transistor have same doping concentration, how will the base current and the collector current be affected?

 [Watch Video Solution](#)

16. How will you test whether a transistor is damaged or not?

 [Watch Video Solution](#)

17. Under normal use of transistors, the emitter is forward biased while the collector is reverse biased.

Can either of these biasing be changed? Explain.



[Watch Video Solution](#)

18. Can two separate p-n junction diodes placed back to back be used to form a p-n-p transistor ?



[Watch Video Solution](#)

Ncert Textbook Questions With Answer Hint

1. In an n-type silicon, which of the following statements is true?

A. electrons are majority carriers and trivalent atoms are the dopants

B. electrons are minority carriers and pentavalent atoms are dopants

C. holes are minority carriers and pentavalent atoms are dopants

D. holes are majority carriers and trivalent atoms are dopants

Answer: C



Watch Video Solution

2. In an unbiased p-n junction holes diffuse from the p-region to the n-region because

A. free electrons in the n-region attract them

B. they move across the junction by the potential difference

C. hole concentration in p-region is more as compared to n-region

D. all the above

Answer: C



Watch Video Solution

3. Carbon silicon and germanium have four valence electrons each. These are characterised by valence and conduction bands separated by energy band gap respectively equal to $(E_g)_C$, $(E_g)_{Si}$ and $(E_g)_{Ge}$ which of the following statements is true?

A. $(E_g)_{Si} < (E_g)_{Ge} < (E_g)_C$

B. $(E_g)_C < (E_g)_{Ge} < (E_g)_{Si}$

C. $(E_g)_C > (E_g)_{Si} > (E_g)_{Ge}$

D. $(E_g)_C = (E_g)_{Si} = (E_g)_{Ge}$

Answer: C



Watch Video Solution

4. In half-wave rectification what is the output frequency if the input frequency is 50 Hz. What is the output frequency of a full-wave rectifier for the same input frequency?



[Watch Video Solution](#)

5. For a CE -transistor amplifier the audio signal voltage across the collector resistance of $2\text{ k}\Omega$ is 2V. Suppose the current amplification factor of the transistor is 100 find the input signal voltage and base current if the base resistance is $1\text{ k}\Omega$.



[Watch Video Solution](#)

6. The amplifiers are connected one after the other in series (cascaded). The first amplifier has a voltage gain of 10 and the second has a voltage gain of 20. If the input signal is 0.01 V, calculate the output ac signal.



[Watch Video Solution](#)

7. A p-n photodiode is fabricated from a semiconductor with band gap of 2.8 eV. Can it detect a wavelength of 6000 nm?



[Watch Video Solution](#)

8. In an intrinsic semiconductor the energy gap E_g is 1.2 eV. Its hole mobility is much smaller than electron mobility and independent of temperature. What is the ratio between conductivity at 600 K and that at 300 K? Assume that the temperature dependence of intrinsic carrier concentration n_i is given by

$$n_i = n_0 \exp\left(-\frac{E_g}{2k_B T}\right) \text{ where } n_0 \text{ is a constant.}$$



[Watch Video Solution](#)


9. The number of silicon atoms per m^3 is 5×10^{28} . This is doped simultaneously with 5×10^{22} atoms per m^3 of arsenic and 5×10^{20} atoms per m^3 of indium. Calculate the number of electrons and holes. Given

that $n_i = 1.5 \times 10^{16} \text{ m}^{-3}$. Is the material n-type or p-type?

 [Watch Video Solution](#)

Ncert Exemplar Questions With Answer Hint Single Option Correct

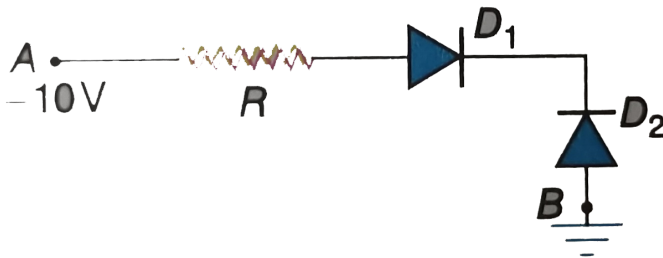1. In Fig 1.50 assuming the diodes to be ideal



A. D_1 is forward biased and D_2 is reverse biased

hence current flows from A to B

B. D_2 is forward biased and D_1 is reverse biased

hence no current flows from B to A and vice versa

C. D_1 and D_2 are both forward biased and hence

current flows A to B

D. D_1 and D_2 are both reverse biased and hence


no current flows from A to B and vice versa

Answer: B



Watch Video Solution

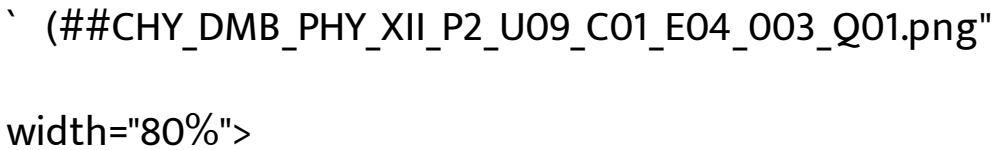2. A 220 V ac supply is connected between points A and B [Fig.1.51]. What will be the potential difference V across the capacitor?



A. 220 V

B. 110 V

C. 0 V


D. $222\sqrt{2}$ V

Answer: D



[View Text Solution](#)

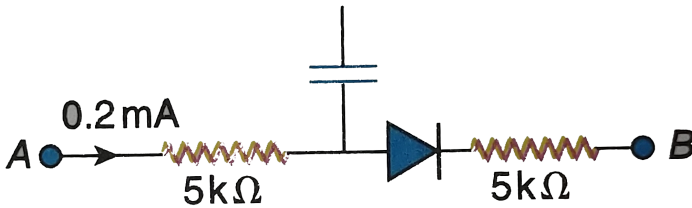3. In the circuit shown in Fig 1.52, if the diode forward voltage drop is 0.3 V the voltage difference between A and B is



A. 1.3 V

B. 2.3 V

C. 0


D. 0.5 V

Answer: B



Watch Video Solution

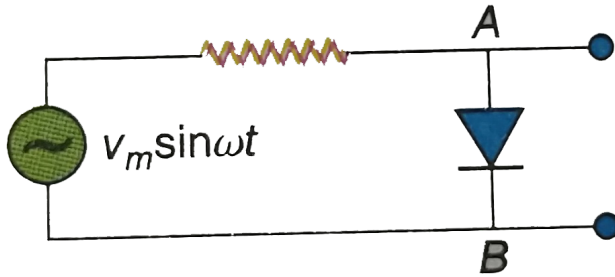4. The output of the given circuit in Fig 1.53.



A. would be zero

B. would be like a half-wave rectifier with positive cycles in output

C. would be like a half-wave rectifier with negative cycles in output

D. would be like that of a full-wave rectifier

Answer: C



Watch Video Solution

5. The breakdown in a reverse biased p-n junction is more likely to occur due to the

A. large velocity of the minority charge carriers if the doping concentration is small

B. large velocity of the minority carriers if the doping concentration is large

C. strong electric field in a depletion region if the doping concentration is small

D. strong electric field in the depletion region if the doping concentration is large

Answer: A::D



Watch Video Solution

6. In an n-p-n transistor circuit, the collector current is 10 mA. If 95% of the electrons emitted reach the collector, which of the following statements are true?

- A. the emitter current will be 8 mA
- B. the emitter current will be 10.53 mA
- C. the base current will be 0.53 mA

D. the base current will be 2mA

Answer: B::C



Watch Video Solution

Ncert Exemplar Questions With Answer Hint Multiple Options Correct

1. Consider an n-p-n transistor with its base -emitter junction forward biased and collector -base junction reverse biased. Which of the following statements are true ?

A. electrons cross over over from emitter to collector

B. holes move from base to collector

C. electrons move from emitter to base

D. electrons from emitter move out of base without going to the collector

Answer: A::C



Watch Video Solution

Exercise Multiple Choice Questions

1. If potential difference is applied the value of electric current

A. becomes infinite for an insulator kept at 0 K

B. becomes zero for a semiconductor kept 0 K

C. becomes finite for a metal kept at 0 K

D. becomes infinite in a forward biased p-n junction diode kept at 300 K

Answer: B



Watch Video Solution

2. Two pieces of copper and germanium are cooled from room temperature to 77 K. As a result

A. resistance of both the pieces will increase

B. resistance of both the pieces will decrease

C. resistance of copper will decrease but that of germanium will increase

D. resistance of copper will increase but that of germanium will decrease

Answer: C



Watch Video Solution

3. For in intrinsic semiconductor the energy gap of forbidden zone is approximately

A. 0.01 eV

B. 0.1 eV

C. 1 eV

D. 10 eV

Answer: C



Watch Video Solution

4. In a semiconducting material the mobilities of electrons and holes are μ_e and μ_h respectively. Which of the following is true ?

A. $\mu_e > \mu_h$

B. $\mu_e < \mu_h$

C. $\mu_e = \mu_h$

D. $\mu_e < 0, \mu_h > 0$

Answer: A



Watch Video Solution

5. In some substance charge can flow at ordinary temperature but not at very low temperatures. These are called

A. conductors

B. insulators

C. semiconductors

D. dielectrics

Answer: C



Watch Video Solution

6. If a small amount of antimony is added to germanium crystal

A. it becomes a p-type semiconductor

B. the antimony becomes an acceptor atom

C. there will be more free electrons than holes in the semiconductor

D. its resistance is increased

Answer: C



Watch Video Solution

7. Pure Si at 500 K has equal number of electron (n_e) and hole (n_h) concentrations of $1.5 \times 10^{16} \text{m}^{-3}$.

Doping by indium increases n_h to $4.5 \times 10^{22} \text{m}^{-3}$. The doped semiconductor is of

A. p-type having electron concentration

$$n_e = 5 \times 10^9 \text{m}^{-3}$$

B. n-type having electron concentration

$$n_e = 5 \times 10^{22} \text{m}^{-3}$$

C. p-type having electron concentration

$$n_e = 2.5 \times 10^{10} \text{m}^{-3}$$

D. n-type having electron concentration

$$n_e = 2.5 \times 10^{23} \text{m}^{-3}$$

Answer: A



Watch Video Solution

8. If a p-n junction diode is not connected in a circuit then

- A. potential is same everywhere
- B. potential of p-end is more than n-end
- C. an electric field acts from the n-end to p-end at the junction

D. an electric field acts from the p-end to n-end at the junction


Answer: C



Watch Video Solution

9. In the circuit shown in Fig 1.54 the forward bias resistances of both the diodes are 50Ω and reverse bias resistances are infinite. If the battery voltage be $6V$, the current through 100Ω resistance in the unit

A is

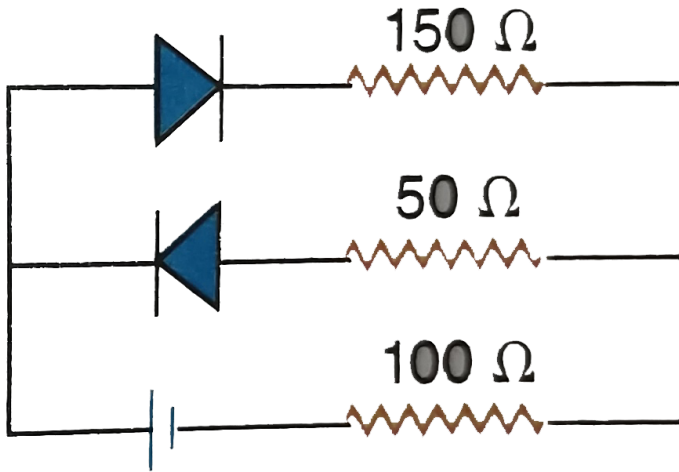

- A. zero
- B. 0.02
- C. 0.03
- D. 0.036

Answer: B

 [Watch Video Solution](#)

10. When a p-n diode is reverse biased then

A. no current flows

B. the depletion region is increased

C. the depletion region is reduced the height of the potential barrier is reduced.


D.

Answer: B



Watch Video Solution

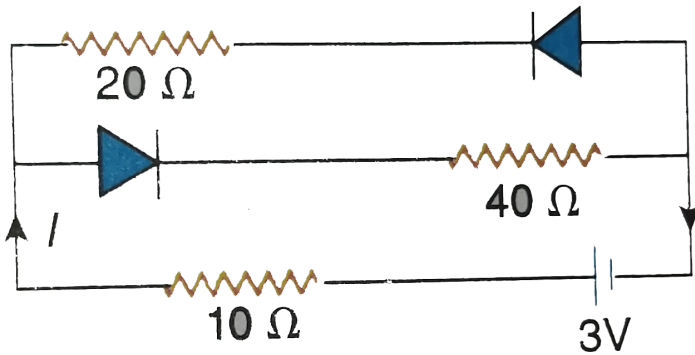11. The current through the given circuit of Fig .1.56.



A. $\frac{3}{40}$ A

B. $\frac{1}{10}$ A

C. $\frac{3}{50}$ A

D. $\frac{3}{10}$ A

Answer: C

 **Watch Video Solution**

12. The impurity atoms that should be added to germanium to make it n-type semiconductor is

A. iodine

B. indium

C. arsenic


D. aluminium

Answer: C



Watch Video Solution

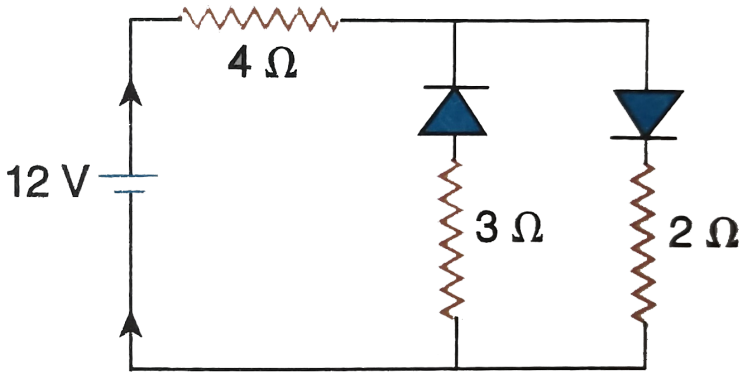13. The circuit has two oppositely connected ideal diodes in parallel. What is the current in the circuit ?



- A. 1.33 A
- B. 1.71 A
- C. 2.00 A
- D. 2.31 A

Answer: C



Watch Video Solution

14. When a p-n junction is reverse biased then


- A. no current flows
- B. the depletion layer is increased
- C. the depletion layer is decreased
- D. height of potential barriers is reduced

Answer: B



Watch Video Solution

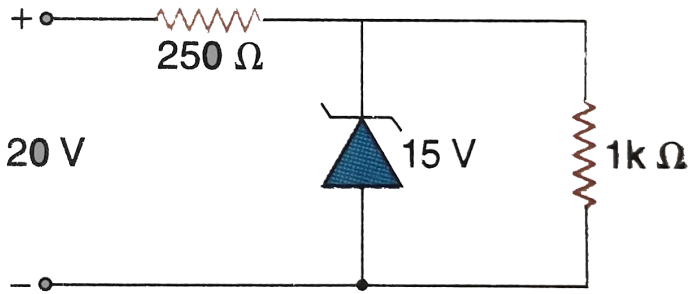15. A Zener diode having breakdown voltage equal to 15V, is used in a voltage regulator circuit shown in Fig 1.58. The current through the diode is



- A. 5 mA
- B. 10 mA
- C. 15 mA
- D. 20 mA

Answer: A

16. If the rate of doping in the emitter base and collector of a transistor be D_e , D_b and D_c respectively then

A. $D_e = D_b = D_c$

B. $D_e < D_b = D_c$

C. $D_e > D_b > D_c$

D. $D_e > D_c > D_b$

Answer: D

17. In the active region of a transistor the biasing at the emitter-base junction and collector - base junction are respectively

A. forward , forward

B. forward ,reverse

C. reverse, forward

D. reverse , reverse

Answer: B



Watch Video Solution

18. A transistor is used as

A. a rectifier

B. an amplifier

C. an oscillator

D. a source of electrons and holes

Answer: B



Watch Video Solution

19. In an n-p-n transistor circuit collector current is 10 mA. If 90% of electrons from the emitter enter into

the collector then,

A. emitter current =11.11 mA

B. emitter current =9mA

C. base current =2.1 mA

D. base current =0.9 mA

Answer: A



[Watch Video Solution](#)

20. For a transistor if $\frac{\Delta I_C}{\Delta I_E} = 0.96$ then the current gain β is

A. 6

B. 12

C. 24

D. 48

Answer: C



Watch Video Solution

21. A transistor is operated in common-emitter configuration at $V_C = 2V$ such that a change in the base current from $100 \mu A$ to $300 \mu A$ produces in the

collector current from 10 mA to 20 mA. The current gain is

- A. 50
- B. 75
- C. 100
- D. 25

Answer: A



Watch Video Solution

Exercise Semiconductor Diode

1. A rectifier converts

- A. mechanical energy into electrical energy
- B. light energy into electrical energy
- C. ac to dc
- D. dc to ac

Answer: C



Watch Video Solution

Exercise Osillator

1. If open loop gain and feedback ratio of a positive feedback oscillator are A and r respectively then closed loop gain A_f is

A. 1

B. $< A$

C. $< Ar$

D. infinity

Answer: D



Watch Video Solution

1. What type of impurity is required to prepare an n-type semiconductor ?



[Watch Video Solution](#)

2. What type of impurity is required to prepare a p-type semiconductor ?



[Watch Video Solution](#)

3. What kind of semiconductor will be produced if it is doped with a donor element?





[Watch Video Solution](#)

4. What is the effective electric charge of a hole?



[Watch Video Solution](#)

5. The total number of negative charge carriers in an intrinsic semiconductor is n . What is the total number of positive charge carriers in this semiconductor ?



[Watch Video Solution](#)

6. What change in the energy band gap of a pure semiconductor is occurs due to increase of temperature ?

 [Watch Video Solution](#)

7. What change in the energy band gap of a semiconductor occurs due to increase of doping ?

 [Watch Video Solution](#)

8. At which temperature is a semiconductor completely transformed into an insulator ?



[Watch Video Solution](#)

9. What kind of semiconductor will be produced if a silicon crystal is doped with arsenic?



[Watch Video Solution](#)

Very Short Answer Type Questions Semiconductor Diode

1. If full-wave rectifier draws an input from a 50 Hz mains what will be the ripple frequency of the output?



[Watch Video Solution](#)

2. What will be the change in the thickness of depletion region if a p-n junction is forward biased ?

 [Watch Video Solution](#)

3. In which condition does a semiconductor diode behave like an open switch?

 [Watch Video Solution](#)

4. What kind of biasing is required to use a Zener diode as a voltage regulator ?

 [Watch Video Solution](#)

5. What type of biasing gives a semiconductor diode very high resistance?



[Watch Video Solution](#)

6. Mention the practical importance of a Zener diode in the laboratory.



[Watch Video Solution](#)

7. Under what condition does a p-n junction diode work as an open switch ?



[Watch Video Solution](#)

Very Short Answer Type Questions Transistor

1. How many effective regions are found in the CE mode of a transistor ?



[Watch Video Solution](#)

2. In which region of the output characteristics is a transistor generally used ?



[Watch Video Solution](#)

3. What is the majority charge carrier in a p-n-p transistor ?

 [Watch Video Solution](#)

4. What is the majority charge carrier in a n-p-n transistor ?

 [Watch Video Solution](#)

5. What is the relation among emitter current (I_E) collector current (I_C) and base current (I_B) for a transistor ?

 [Watch Video Solution](#)

6. How will you recognise from a transistor circuit whether the transistor is n-p-n or p-n-p ?

 [Watch Video Solution](#)

7. Calculate the change in collector current due to the change of $10 \mu\text{A}$ in base current of a transistor having $\beta=150$.

 [Watch Video Solution](#)

Very Short Answer Type Questions Oscillator

1. What is the product of open loop gain and feedback ratio of the amplifier in a feedback oscillator.



[Watch Video Solution](#)

2. What is the natural frequency of an LC oscillator?



[Watch Video Solution](#)

1. How will you identify a conductor and a semiconductor from two given rods of same resistance ?

 [Watch Video Solution](#)

2. What change in energy band gap of a semiconductor due to doping of of pentavalent element?

 [Watch Video Solution](#)

3. What is the effect of doping on electric conductivity of a semiconductor ?

 [Watch Video Solution](#)

4. How is sample of an n-type semiconductor electrically neutral though it has an excess of negative charge carriers?

 [Watch Video Solution](#)


5. Explain the law of mass action ($np = n_i^2$).

 [Watch Video Solution](#)

6. Draw V-I characteristic curve of a p-n junction and compare it with the characteristic of a resistance.

 [Watch Video Solution](#)

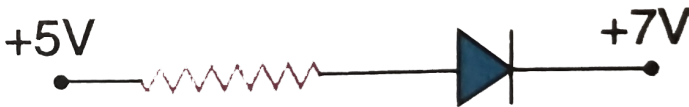7. What type of biasing has been given to the diode of Fig 1.60?



 [Watch Video Solution](#)

8. When breakdown voltage of a Zener diode is around 6 V, then the value of this voltage does not depend upon temperature -Explain.



[Watch Video Solution](#)

9. What is the relation between the energy band gap of an LED and maximum possible wavelength of emitted light from it ?



[Watch Video Solution](#)

10. In case of solar diode what is the significance of voltampere relation of characteristic curve in fourth quadrant ?

 [Watch Video Solution](#)

11. Why is the base of a transistor lightly doped ?

 [Watch Video Solution](#)

12. In which region will a transistor act if both emitter - base and collector-base junctions are reverse biased?

 [Watch Video Solution](#)

13. In which region will a transistor act if both emitter - base and collector-base junctions are forward biased?



Watch Video Solution

14. Without any any input signal a feedback oscillator gives output signal. Explain how the conservation of energy is not violated.



Watch Video Solution

15. What is the significance of Barkhausen criterion?



Watch Video Solution

16. Open loop gain of an amplifier is A . If a feedback oscillator is made by this amplifier then what feedback ratio is to be taken?



Watch Video Solution

Short Answer Type Questions II

1. The current in the forward bias is known to be more ($-mA$) than the current in the reverse bias ($-\mu a$). What

is the reason then to operate in the photodiode in reverse bias ?

 [Watch Video Solution](#)

2. Explain why the p-n junction contact potential cannot be measured by a voltmeter across the diode terminals.

 [Watch Video Solution](#)

3. Why two diodes connected back to back cannot behave as a transistor?

 [Watch Video Solution](#)

4. Why is the base region of transistor usually made thin?

 [Watch Video Solution](#)

5. Explain why Si and Ge are not used in LED.

 [Watch Video Solution](#)

Problem Set I Semiconductor

1. A semiconductor has the electron concentration of $8 \times 10^{13} \text{cm}^{-3}$ and hole concentration $4 \times 10^{12} \text{cm}^{-3}$.

Is this semiconductor n-type or p-type ? Also calculate resistivity of its material.

Given : Electron mobility = $24000 \text{cm}^2 \cdot \text{V}^{-1} \cdot \text{s}^{-1}$. and
hole mobility = $200 \text{cm}^2 \cdot \text{V}^{-1} \cdot \text{s}^{-1}$



[Watch Video Solution](#)

2. Pure silicon at 300 K has same electron and hole concentrations of $1.5 \times 10^{16} \text{m}^{-3}$. Doping by indium the concentration of holes increases to

$4.5 \times 10^{22} \text{m}^{-3}$. Calculate electron concentration in doped silicon.

 [Watch Video Solution](#)

3. A semiconductor has the electron concentration of $4 \times 10^{12} \text{cm}^{-3}$ and the hole concentration of $7 \times 10^{13} \text{cm}^{-3}$. Is this semiconductor n-type or p-type ?

Also calculate conductivity of its material.

Given : Electron mobility = $22000 \text{ cm}^2 \cdot \text{V}^{-1} \cdot \text{s}^{-1}$ and

hole mobility = $150 \text{ cm}^2 \cdot \text{V}^{-1} \cdot \text{s}^{-1}$

 [Watch Video Solution](#)

4. Calculate the conductivity of a semiconductor having electron concentration $5 \times 10^{12} \text{cm}^{-3}$ and hole concentration $8 \times 10^{13} \text{cm}^{-3}$

$$\left[\mu_e = 2.3 \text{V}^{-1} \cdot \text{s}^{-1} \cdot \text{m}^2 \quad \text{and} \quad \mu_h = 0.1 \text{V}^{-1} \cdot \text{s}^{-1} \cdot \text{m}^2 \right]$$

 [Watch Video Solution](#)

5. The energy of a photon of light ($\lambda = 590 \text{nm}$) equals the band gap of a semiconducting material. Find the minimum energy required to create a hole-electron pair.

 [Watch Video Solution](#)

Problem Set I

1. If an unregulated voltage of 10 V is regulated by a Zener diode of rating 4.7 V-1W calculate minimum resistance to be connected to the circuit for safe current.



[Watch Video Solution](#)

2. A transistor has $\beta=100$ and $I_B = 20\mu$ A. Find the emitter current.



[Watch Video Solution](#)

3. Current gain of a common-emitter transistor amplifier is 50. If the emitter current is 6.6 mA , calculate collector current and base current.

 [Watch Video Solution](#)

4. In CE circuit if base of the transistor is increased from $100 \mu\text{A}$ to $150 \mu\text{A}$, then collector current increases to 10 mA from 5 mA. Calculate current gain β of the transistor.

 [Watch Video Solution](#)

5. In LC circuit of a feedback oscillator , $L = 36 \text{ mH}$. If the oscillator is used as an alternating source of different frequencies in the range 100 Hz to 1000 Hz , then find the range in which the capacitance of C should be kept.



[Watch Video Solution](#)

Problem Set II Semiconductor

1. An LED is constructed from a p-n junction based on a certain Ga-As-P semiconducting material whose

energy is 1.9 eV. What is the wavelength of the emitted light?



[Watch Video Solution](#)

Hots Numerical Problems

1. The base current of a transistor is $105 \mu\text{A}$ and collector current is 2.05 mA .

Determine the values of β , I_E and α .



[Watch Video Solution](#)

2. The base current of a transistor is $105 \mu\text{A}$ and collector current is 2.05 mA .

A change of $27 \mu\text{A}$ in the base current produces a change of 0.65 mA in the collector current. Find β_{ac} .



[Watch Video Solution](#)

3. Following current readings are obtained in a transistor circuit : $I_E=2\text{ mA}$ and $I_B =20 \mu\text{ A}$. Compute the values of I_C and α .



[Watch Video Solution](#)

Entrance Corner Assertion Reason Type

1. Direction : These question have statement I and statement II. Of the four choices given below choose the one that best describes the two statements.

Statement I: The depletion of thermal layer is also generated at the junction of a p-n junction diode without any applied biasing.

Statement II. The diffusion of thermal electrons and holes takes place from one region to another.

A. Statement I is true statement II is true, statement II is a correct explanation for statement I.

B. Statement I is true statement II is true, statement II is not a correct explanation for statement I.

C. Statement I is true statement II is false.

D. Statement I is false statement II is true.

Answer: B

 [Watch Video Solution](#)

2. Statement I: The holes are created in the valence band only if the electrons from the valence band transit to the conduction band.

Statement II: Due to applied electric field the hole in a semiconductor gains velocity which is less than that of a free electron.

A. Statement I is true statement II is true, statement II is a correct explanation for statement I.

B. Statement I is true statement II is true, statement II is not a correct explanation for statement I.

C. Statement I is true statement II is false.

D. Statement I is false statement II is true.

Answer: B



Watch Video Solution

3. Statement I: In p-type semiconductor the drift velocity of charge carrier holes is higher than of electrons.

Statement -II : In p-type semiconductor majority charge carriers are holes.

A. Statement I is true statement II is true,
statement II is a correct explanation for
statement I.

B. Statement I is true statement II is true, statement II is not a correct explanation for statement I.

C. Statement I is true statement II is false.

D. Statement I is false statement II is true.

Answer: D

 [Watch Video Solution](#)

4. Statement I : In CE mode of a transistor if the input signal is applied at base then the output signal is obtained at collector.

Statement II : In a transistor most of the emitter current is transformed into the collector current.

A. Statement I is true statement II is true, statement II is a correct explanation for statement I.

B. Statement I is true statement II is true, statement II is not a correct explanation for statement I.

C. Statement I is true statement II is false.

D. Statement I is false statement II is true.

Answer: B





5. Statement I : The frequency of the output signal from a feedback oscillator depends on its feedback ratio.

Statement II : A feedback oscillator circuit is made in such a way that the closed loop gain of the amplifier reaches to an infinite value.

A. Statement I is true statement II is true, statement II is a correct explanation for statement I.

B. Statement I is true statement II is true, statement II is not a correct explanation for

statement I.

C. Statement I is true statement II is false.

D. Statement I is false statement II is true.

Answer: D



Watch Video Solution

6. Statement I: In spite of increasing in doping level the conductivity of the semiconductor does not change.

Statement II : By increasing in doping level the conductivity the concentration of one type of charge carriers (electrons or holes) is increased and at the

same time concentration of other charge carrier decreases.

A. Statement I is true statement II is true, statement II is a correct explanation for statement I.

B. Statement I is true statement II is true, statement II is not a correct explanation for statement I.

C. Statement I is true statement II is false.

D. Statement I is false statement II is true.

Answer: D





7. Statement I : If the frequency of light below a certain minimum value is made incident on a photodiode , then no current will flow through it.

Statement II : If the energy of incident photon is less than a minimum value then in a photodiode there is no possibility of recombination of electron-hole pairs.

A. Statement I is true statement II is true, statement II is a correct explanation for statement I.

B. Statement I is true statement II is true, statement II is not a correct explanation for

statement I.

C. Statement I is true statement II is false.

D. Statement I is false statement II is true.

Answer: C



Watch Video Solution

Entrance Corner Multiple Correct Answers Type

1. Depletion region of p-n junction completely vanishes

if

A. a suitable forward bias is applied

B. a suitable reverse bias is applied

C. a light of suitable frequency is made incident
from outside

D. Zener effect takes place

Answer: A::C::D



Watch Video Solution

2. If a pentavalent element is doped in an intrinsic semiconductor then

A. a p-type semiconductor is formed

- B. effective energy gap of the forbidden zone decreases
- C. the energy states of free electrons in the pentavalent element come nearer to the conduction band
- D. the energy states of free in the pentavalent element come down near the valence band

Answer: B::C



Watch Video Solution

3. If a p-n junction is reverse biased then

- A. a potential barrier is created at the junction
- B. the effective resistance reaches an infinite value
- C. a small current is obtained due to diffusion of majority carrier electrons and holes
- D. In spite of increasing the reverse bias the reverse current remains almost unchanged

Answer: A::B::D



Watch Video Solution

4. In case of a transistor

A. the emitter region is heavily doped

B. in CE configuration if the base-emitter and the collector-emitter both junction are forward biased then the transistor acts in saturation region

C. to use as an amplifier it is operated in active region

D. to use as a switch it is operated in between saturation region and cut off region

Answer: A::B::C::D



Watch Video Solution

5. In case of a Zener diode,

A. to use as a voltage regulator it is kept in reverse bias.

B. power consumption in reverse bias is higher than that of an ordinary semiconductor diode

C. in forward bias it behaves as an ordinary semiconductor diode is

D. If Zener voltage is applied in reverse bias then a high potential barrier is created at its junction

Answer: A::B::C



Watch Video Solution

6. In a feedback oscillator,

A. effective amplification of the amplifier used in this oscillator is infinity

B. the output ac signal frequency is only determined by the feedback ration

C. the output ac signal frequency is controlled by a tank circuit in the feedback device

D. the output ac signal is obtained without any externally applied input

Answer: A::C::D



Watch Video Solution

7. In an n-type semiconductor if n and p are the concentration of electrons and holes respectively and n_i is the concentration of electron-hole pairs in a pure semiconductor then

A. $n=p$

B. $n > p$

C. $n < p$

D. $np=n_i^2$

Answer: B::D



Watch Video Solution

Entrance Corner Integer Answer Type

1. For an n-type doping in a pure semiconductor the concentration of charge carrier electrons increases 5 times. Find hole concentration as percentage of the electron concentration.



Watch Video Solution

2. An extrinsic semiconductor has the concentration of holes as charge carriers $5 \times 10^{20} \text{ m}^{-3}$. The electron concentration is negligible as compared to hole concentration. If mobility of holes is $0.05 \text{ m}^2 \cdot \text{V}^{-1} \cdot \text{s}^{-1}$ then find the conductivity (in $\text{mho} \cdot \text{m}^{-1}$) of the semiconductor ?

 [Watch Video Solution](#)

3. The maximum output voltage of an unregulated voltage source is 10V. A Zener diode of rating 1 W is connected in reverse bias with this voltage source through a resistance R. The Zener diode will be burnt

if R is less than 24Ω . Find the maximum value of Zener voltage (in volt) of the diode.



Watch Video Solution

4. In a transistor the value of $\beta = 200$. In CE configuration it is kept in a stable dc bias. Now if an input signal is applied then output signal will vary in the range of 5.6 mA to 6.4 mA. Find the amplitude of the input signal (in μA).



Watch Video Solution

5. The emitter of an n-p-n transistor emits 1.25×10^{10} electrons per micro-second (μs). Find the emitter current in mA. (Given : electronic charge, $e = 1.6 \times 10^{-19}$ coulomb).



[Watch Video Solution](#)

Examination Archive With Solutions Wbchse

1. What are the majority carriers in a p-type semiconductor?



[Watch Video Solution](#)

2. What type of semiconductor is produced if germanium crystal is doped with arsenic?



[Watch Video Solution](#)

3. Draw the circuit diagram of a full-wave rectifier using p-n junction diode and explain its operation. To which factor is the pulsating nature of the output due?



[Watch Video Solution](#)

4. The impurity atom when added to germanium makes it an n-type semiconductor is

A. boron

B. indium

C. arsenic

D. aluminium

Answer:



Watch Video Solution

5. Draw the I-V characteristics of a light emitting diode (LED) and explain its working principle.

 [Watch Video Solution](#)

6. Draw the output characteristics of an n-p-n transistor in common emitter configuration for five base currents. What is an oscillator?

 [Watch Video Solution](#)

7. What is Zener diode? Draw its voltage vs current characteristics in the reverse bias and indicate the

breakdown voltage on the characteristics. Mention one important use of this diode.



[Watch Video Solution](#)

8. What will happen if the amount of reverse biasing in a p-n junction diode is gradually increased?

A. thickness of depletion region will increase

B. flow of current due to majority carriers will increase

C. thickness of depletion region will decrease

D. flow of current due to majority carriers will decrease

Answer: C



Watch Video Solution

9. What is a p-n junction diode ? Draw the circuit diagram of a full-wave rectifier using p-n junction diodes. Show the input and output voltage waveforms by a schematic graph.



Watch Video Solution

10. What is a photodiode ? Draw the I-V characteristic curve of a photodiode. Mention one use of photodiode.

 [Watch Video Solution](#)

11. Draw the V-I characteristic curve for forward and reverse bias of a p-n junction diode. (Graph sheet is not required)

 [Watch Video Solution](#)

12. State one difference between n-type and p-type semiconductors.

 [Watch Video Solution](#)

13. In a transistor emitter-base junction is always forward biased while the collector-base junction is reverse biased. Why ?

 [Watch Video Solution](#)

14. For a transistor if $\beta = 100$, then α will be

A. 0.99

B. 1.01

C. 100

D. 0.01

Answer: A



Watch Video Solution

15. The lengths radii and specific resistance of two conducting wires are each in the ratio of 1:3. If the resistance of the thinner wire is 10Ω then the resistance of the other wire will be

A. 49Ω

B. 20Ω

C. 10Ω

D. 5Ω

Answer: C



Watch Video Solution

16. Explain with diagram the action of p-n diode as a full wave rectifier.



Watch Video Solution

17. Draw the output characteristic curves of a n-p-n transistor in a CE configuration and find the output resistance from it.

 [Watch Video Solution](#)

18. Explain with circuit diagram the action of a transistor as a switch.

 [Watch Video Solution](#)

19. In normal transistor operation

A. emitter -base junction and collector-base junction are both in reverse bias

B. emitter -base junction is in forward bias and collector -base junction is in reverse bias

C. emitter-base junction and collector-base junction both are in forward bias

D. emitter-base junction is in reverse bias and collector -base junction is in forward bias

Answer: B



Watch Video Solution

20. (i) What is Zener diode?

(ii) Explain with circuit diagram how a Zener diode regulates voltage across a load resistance.

 [Watch Video Solution](#)

21. Why does a photodiode function in reverse bias?

 [Watch Video Solution](#)

Examination Archive With Solutions Wbjee

1. In a transistor output characteristic commonly used in common-emitter configuration the base current I_B

the collector current I_C and the collector -emitter voltage V_{CE} have values of the following orders of the magnitude in the active region

- A. I_B and I_C are both in μA and V_{CE} in V
- B. I_B is in μA I_C in mA and V_{CE} in mV
- C. I_B is in mA, I_C in μA and V_{CE} in mV
- D. I_B is in mA I_C is in mA and V_{CE} in mV

Answer: B



Watch Video Solution

2. In the circuit shown assume the diode to be ideal.
When V_i increases from 2 V to 6 V the changes in the current is (in mA)



- A. zero
- B. 20
- C. $\frac{80}{3}$
- D. 40

Answer:



View Text Solution

3. If the band gap between valence band and conduction band in a material is 5.0 eV, then the material is

- A. semiconductor
- B. good conductor
- C. superconductor
- D. insulator

Answer: D



Watch Video Solution

4. Assume that each diode shown in Fig 1.70 has a forward bias resistance of $50\ \Omega$ and an infinite reverse bias resistance. The current through the resistance $150\ \Omega$ is



A. 0.66 A

B. 0.05 A

C. zero

D. 0.04

Answer: D



View Text Solution

5. In case of a bipolar transistor $\beta = 45$. The potential drop across the collector resistance of $1 \text{ k}\Omega$ is 5 V . The base current is approximately

A. $222 \mu \text{ A}$

B. $55 \mu \text{ A}$

C. $111 \mu \text{ A}$

D. $45 \mu \text{ A}$

Answer: C



Watch Video Solution

6. A zener diode having breakdown voltage 5.6 V is connected in reverse bias with a battery of emf 10 V and a resistance of 100Ω in series . The current flowing through the zener is.

A. 88 mA

B. 0.88 mA

C. 4.4 mA

D. 44 mA

Answer: D



Watch Video Solution

7. When a semiconductor device is connected in series with a battery and a resistance a current is found to flow in the circuit. If however the polarity of the battery is reversed practically no current flows in the circuit. The device may be

- A. a p-type semiconductor
- B. a n-type semiconductor
- C. an intrinsic semiconductor
- D. a p-n junction

Answer: D



Watch Video Solution

8. What will be the current flowing through the $6\text{ k}\Omega$ resistor in the circuit shown where the breakdown voltage of the Zener is 6 V ?



A. $\frac{2}{3}\text{ mA}$

B. 1 mA

C. 10 mA

D. $\frac{3}{2}\text{ mA}$

Answer: A



View Text Solution

1. The forward biased diode connection is

A. 

B. 

C. 

D. 

Answer: A



[View Text Solution](#)

2. For a common emitter configuration if α and β have their usual meanings the incorrect relationship between α and β is

A. $\frac{1}{\alpha} = \frac{1}{\beta} + 1$

B. $\alpha = \frac{\beta}{1 - \beta}$

C. $\alpha = \frac{\beta}{1 + \beta}$

D. $\alpha = \frac{\beta^2}{1 + \beta^2}$

Answer: C



Watch Video Solution

3. In a common-emitter amplifier circuit using an n-p-n transistor the phase difference between the input and the output voltages will be

A. 45°

B. 90°

C. 135°

D. 180°

Answer: D



Watch Video Solution

4. The reading of the ammeter for a silicon diode in the given circuit is



A. 11.5 mA

B. 13.5 mA

C. 0

D. 15 mA

Answer: A



[View Text Solution](#)

1. The barrier potential of a p-n junction depends on (i) type of semiconductor material (ii) amount of doping and (iii) temperature. Which one of the following is correct?

- A. (i) and (ii) only
- B. (ii) only
- C. (ii) and (iii) only
- D. (i),(ii) and (iii)

Answer: D



Watch Video Solution

2. If in a p-n junction a square input signal of 10 V is applied as shown then the output across R_L will be



A. 

B. 

C. 

D. 

Answer: D



[View Text Solution](#)

1. Consider the junction diode as ideal. The value of current flowing through AB is



A. 10^{-2} A

B. 10^{-1} A

C. 10^{-3} A

D. 0

Answer: A



View Text Solution

2. A n-p-n transistor is connected to common emitter configuration in a given amplifier. A load resistance of 800Ω is connected in the collector circuit and the voltage drop across it is 0.8 V . If the current amplification factor is 0.96 and the input resistance of the circuit is 192Ω the voltage gain and the power gain of the amplifier will respectively be

A. $3.69, 3.84$

B. $4, 4$

C. $4, 3.69$


D. $4, 3.84$

Answer: D



Watch Video Solution

3. Two sides of a semiconductor germanium crystal A and B are doped with arsenic and indium respectively. They are connected to a battery as shown in figure.

 The correct graph between current and voltage for the arrangement is

A. 

B. 

C. 

D. 

Answer: A



View Text Solution

4. A common-emitter amplifier circuit is shown in the figure below. For the transistor used in the circuit the current amplification factor , $\beta_{dc} = 100$. Other parameters are mentioned in the figure.



We that

$$\text{A. } V_{BE} = +18.2V, V_{BC} = -3.45 \text{ V and}$$

amplifier is working

B. $V_{BE} = +18.5V$, $V_{BC} = +2.85$ V and

amplifier is not working

C. $V_{BE} = +20.7V$, $V_{BC} = +3.75V$ and amplifier

is not working

D. $V_{BE} = +21.5V$, $V_{BC} = -2.75$ V and

amplifier is working

Answer: C



View Text Solution

5. In the circuit shown in the figure the input voltage

V_i is 20 V, $V_{BE} = 0$ and $V_{CE} = 0$. The values of I_B , I_C and

β are given by



A. $I_B = 20\mu A, I_C = 5\text{mA}, \beta=250$

B. $I_B = 25\mu A, I_C = 5\text{mA}, \beta=200$

C. $I_B = 40\mu A, I_C = 5\text{mA}, \beta=250$

D. $I_B = 40\mu A, I_C = 5\text{mA}, \beta=125$

Answer: D



View Text Solution

6. In a p-n junction diode change in temperature due to heating

A. does not affect resistance of p-n junction

B. affects only forward resistance

C. affects only reverse resistance

D. affects the overall V-I characteristic of p-n junction

Answer: D



Watch Video Solution

Cbse Scanner

1. (a) Describe briefly with the help of a diagram the role of the two important processes involved in the formation of a p-n junction.

 [Watch Video Solution](#)

2. Name the device which is used as a voltage regulator. Draw the necessary circuit diagram and explain its working.

 [Watch Video Solution](#)

3. Explain briefly the principle on which a transistor-amplifier works as an oscillator. Draw the necessary circuit diagram and explain its working.



[Watch Video Solution](#)

4. Draw V-I characteristics of p-n junction diode.

Answer the following questions giving reasons:

Why is the current under reverse bias almost independent of the applied potential up to a critical voltage?



[Watch Video Solution](#)

5. Draw V-I characteristics of p-n junction diode.

Answer the following questions giving reasons:

Why does the reverse current show a sudden increase at the critical voltage?

Name any semiconductor device which operates under the reverse bias in the breakdown region.



[Watch Video Solution](#)

6. Draw typical output characteristics of an n-p-n transistor in CE configuration. Show how these characteristics can be used to determine output resistance.



[Watch Video Solution](#)

[Watch Video Solution](#)

7. Draw a circuit diagram of n-p-n transistor amplifier in CE configuration. Under what condition does the transistor act as an amplifier.

 [Watch Video Solution](#)

8. Explain with the help of a circuit diagram the working of a p-n junction diode as a half -wave rectifier.

 [Watch Video Solution](#)

9. Write any two distinguishing features between conductors semiconductors and insulators on the basis of energy band diagrams.

 [Watch Video Solution](#)

10. Explain with the help of suitable diagram the two important processes that occur during the formation of p-n junction. Hence define the terms : depletion region and barrier potential.

 [Watch Video Solution](#)

11. How is a light emitting diode fabricated ? Briefly state its working. Write any two important advantages of LEDs over the conventional incandescent low power lamps.



Watch Video Solution

12. Distinguish between a conductor and a semiconductor on the basis of energy band diagram.



Watch Video Solution

13. Name the important processes that occur during the formation of a p-n junction.



Watch Video Solution

14. Draw the circuit diagram of a full wave rectifier along with the input and output waveforms. Briefly explain how the output voltage/ current is unidirectional.



Watch Video Solution

15. Write the two processes that take place in the formation of a p-n junction. Explain with the help of a diagram, the formation of depletion region and barrier potential in a p-n junction.



Watch Video Solution

16. In the following diagram, is the junction diode forward biased or reverse biased?



View Text Solution

17. Draw the circuit diagram of a full wave rectifier and state how it works.



Watch Video Solution

18. A Zener diode is fabricated by heavily doping both p and n-sides of the junction. Explain why? Briefly explain the use of Zener diode as a dc voltage regulator with the help of a circuit diagram.



Watch Video Solution

19. In the following diagram which bulb out of B_1 and B_2 will glow and why ?



 [View Text Solution](#)

20. Draw a diagram of an illuminated p-n junction solar cell.

 [Watch Video Solution](#)

21. Explain briefly the three processes due to which generation of emf takes place in solar cell.

 [Watch Video Solution](#)

22. In the following diagram 'S' is a semiconductor. Would you increase or decrease the value of R to keep the reading of the ammeter A constant when S is heated ? Give reason for your answer.



 [View Text Solution](#)

23. Draw the circuit diagram of a photodiode and explain its working. Draw its I-V characteristics.

 [Watch Video Solution](#)

24. Name the junction diode whose I-V characteristics are drawn below



View Text Solution

25. For a CE -transistor amplifier the audio signal voltage across the collector resistance of $2\text{ k}\Omega$ is 2 V . Given the current amplification factor of the transistor is 100 find the input signal voltage and base current if the base resistance is $1\text{ k}\Omega$.



Watch Video Solution

26. Write the functions of the three segments of a transistor.

 **Watch Video Solution**

27. Draw the circuit diagram for studying the characteristics of a transistor in common emitter configuration. Explain briefly and show how input and output characteristics are drawn.

 **Watch Video Solution**

28. Draw the circuit diagram of an n-p-n transistor amplifier in common emitter configuration.

 [Watch Video Solution](#)

29. Derive an expression for voltage gain of the amplifier and hence show that the output voltage is in opposite phase with the input voltage.

 [Watch Video Solution](#)

30. A student wants to use two p-n junction diodes to convert alternating current into direct current. Draw

the labelled circuit diagram she would use and explain how it works.

 [Watch Video Solution](#)

31. Draw the typical input and output characteristics of an n-p-n transistor in CE configuration. Show how these characteristics can be used to determine (a) the input resistance (r_i) and (b) current amplification factor (β).

 [Watch Video Solution](#)