




# PHYSICS

## BOOKS - MARVEL PHYSICS (HINGLISH)

### CURRENT ELECTRICITY

Mcq

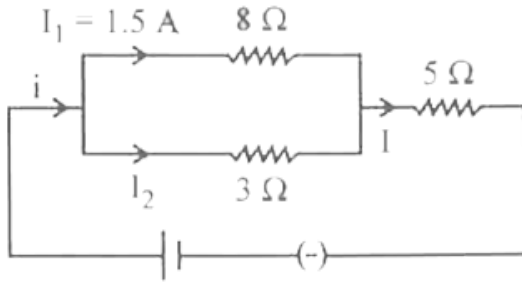

1.

In the given circuit, the current in the  $8\ \Omega$  resistance is  $1.5\ \text{A}$ . What is the total current ( $I$ ) flowing in the circuit ?

A.  $3\ \text{A}$

B.  $4\ \text{A}$

C.  $5\ \text{A}$


D.  $5.5\ \text{A}$

**Answer: D**



**Watch Video Solution**

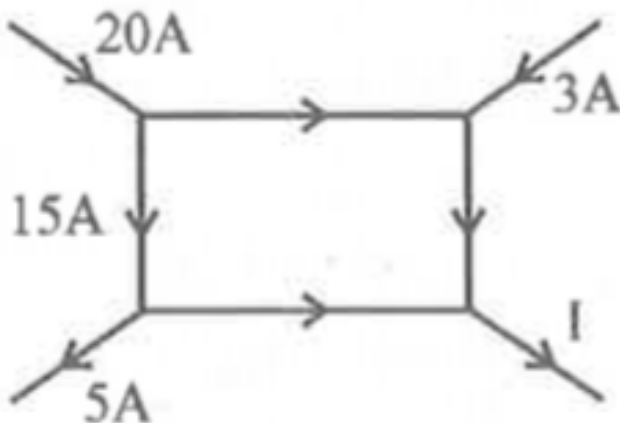2. The value of the current  $I$  in the given circuit is



A. 10A

B. 12A

C. 18A


D. 15A

**Answer: C**



**Watch Video Solution**

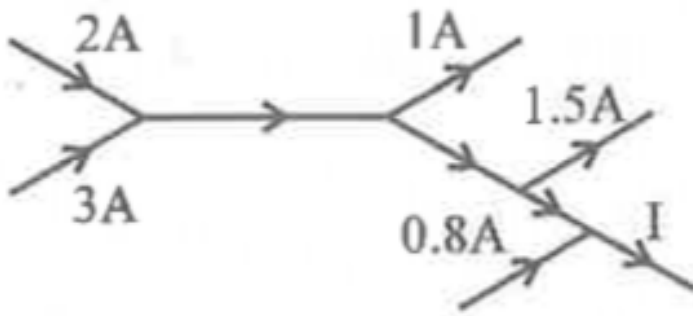**3.** What is the value of the current  $I$  in the following part of an electrical network ?



A.  $1.3A$

B.  $2.7A$

C.  $3.3A$

D.  $4.7A$

**Answer: C**



**Watch Video Solution**

4. In an open circuit and in a short circuit we have

A. zero resistance and infinite resistance  
respectively

B. infinite resistance and zero resistance  
respectively

C. maximum current and zero resistance  
respectively

D. zero current and maximum resistance  
respectively

**Answer: B**



**Watch Video Solution**

5. The Kirchhoff's first law  $\left(\sum i = 0\right)$  and second law  $\left(\sum IR = \sum E\right)$  are respectively based upon the conservations of

A. Charge, Momentum

B. Energy, Charge

C. Momentum, Charge

D. Charge, Energy

**Answer: D**




**Watch Video Solution**

6. Two batteries, one of emf 18 volts and internal resistance  $2\Omega$  and the other fo emf 12 volts and internal resistance  $1\Omega$ , are connected as shown. The voltmeter  $V$  will



record a reading of

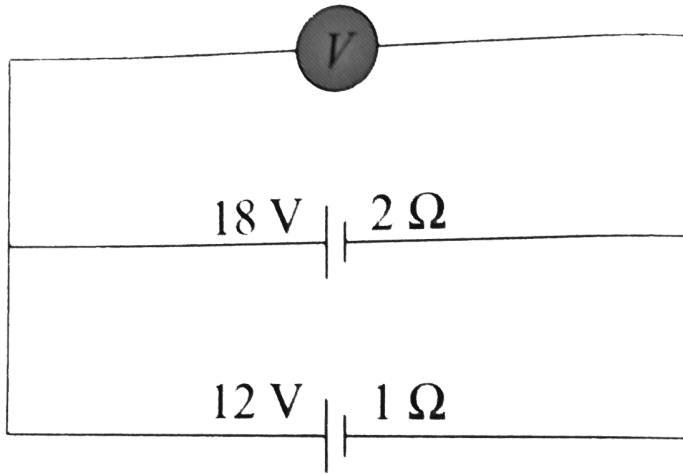


- A. 18V
- B. 16V
- C. 14 V
- D. 12 V

**Answer: C**



Watch Video Solution

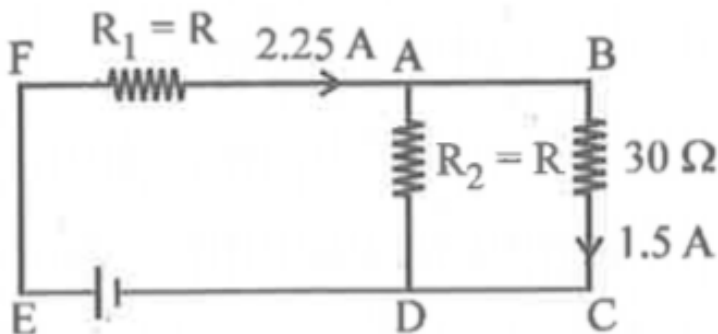7. What is the value of the resistance  $R_1$  in the following circuit ?



A.  $30\ \Omega$

B.  $45\ \Omega$

C.  $60\ \Omega$


D.  $80\Omega$

**Answer: C**



**Watch Video Solution**

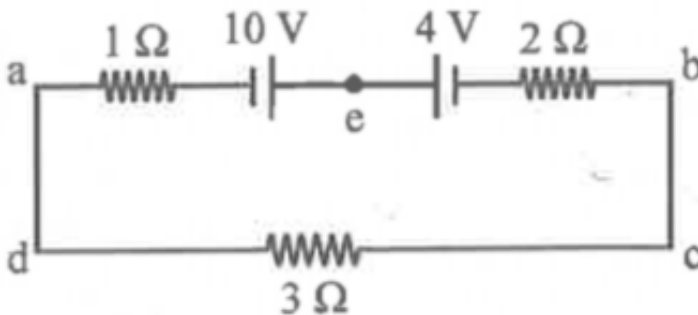**8.** What is the magnitude and direction of the current in the following circuit ?



A. 1 A from b to a through c

B. 1 A from a to b through e

C.  $\frac{2}{3}$  A from a to b through e

D.  $\frac{5}{7}$  A from b to a through e


**Answer: B**



**Watch Video Solution**

**9.** Five current carrying conductor meet at a point P. What is the magnitude and direction

of the current in the fifth conductor ?

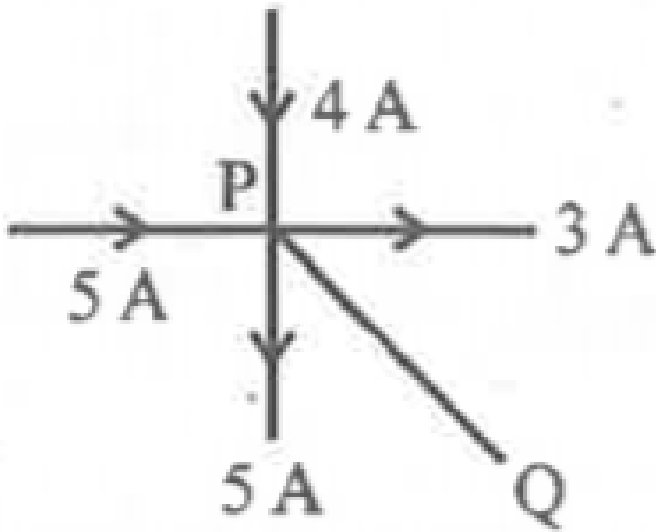

- A. 1A from Q to P
- B. 1 A from P to Q
- C. 3 A from P to Q
- D. 2 A from Q to P


**Answer: B**



**Watch Video Solution**

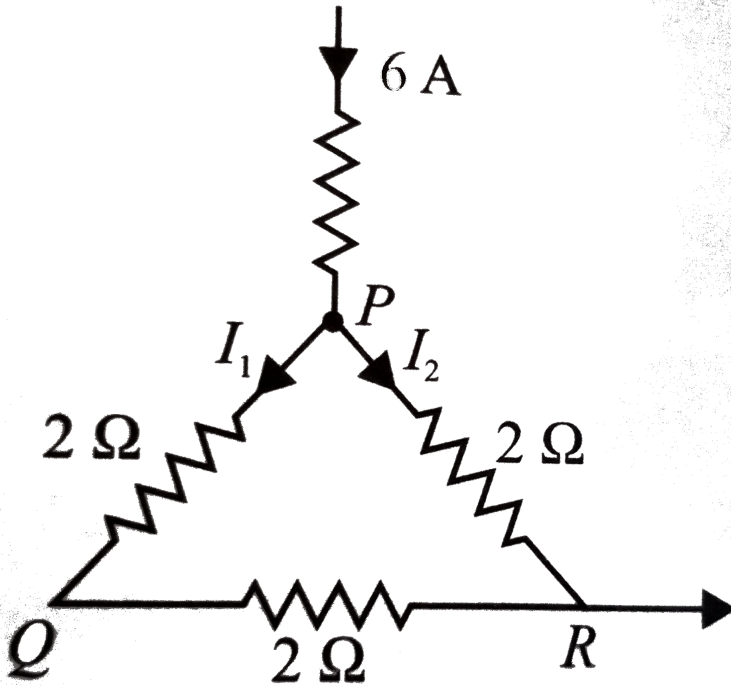**10.** A current of 6 A enters one corner P of an equilateral triangle PQR having 3 wires of resistances  $2Q$  each and leaves by the corner

R. Then the currents  $I_1$  and  $I_2$  are



A. 2A, 4A

B. 4A, 2A

C. 1A, 2A


D. 2A, 3A

**Answer: A**



**Watch Video Solution**

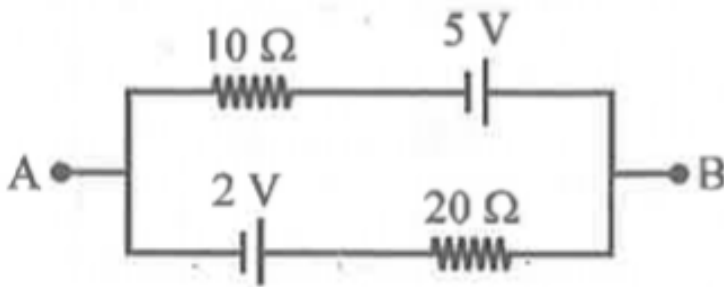**11.** What is the current in the given circuit ?



A.  $0.1\ \text{A}$

B.  $0.2\ \text{A}$

C.  $0.3\ \text{A}$



D. 0.4 A

**Answer: A**




**Watch Video Solution**

**12.** In the circuit shown the cells  $A$  and  $B$  have negligible resistance. For

$V_A = 12V$ ,  $R_1 = 500\Omega$  and  $R = 100\Omega$ , the galvanometer ( $G$ ) shows no deflection. The

value of  $V_B$  is

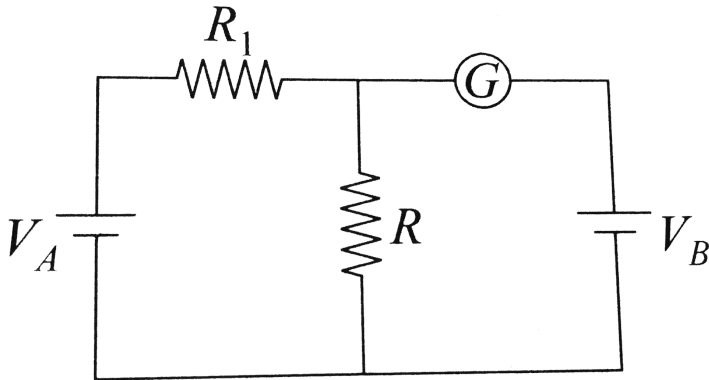

- A. 4 V
- B. 2V
- C. 12 V
- D. 6V


**Answer: B**



**Watch Video Solution**

**13.** A bridge circuit is shown in the diagram. A student wrote the following expressions for currents at the points A, B, C and D by using Kirchhoff's first law. Point out the wrong

equation.

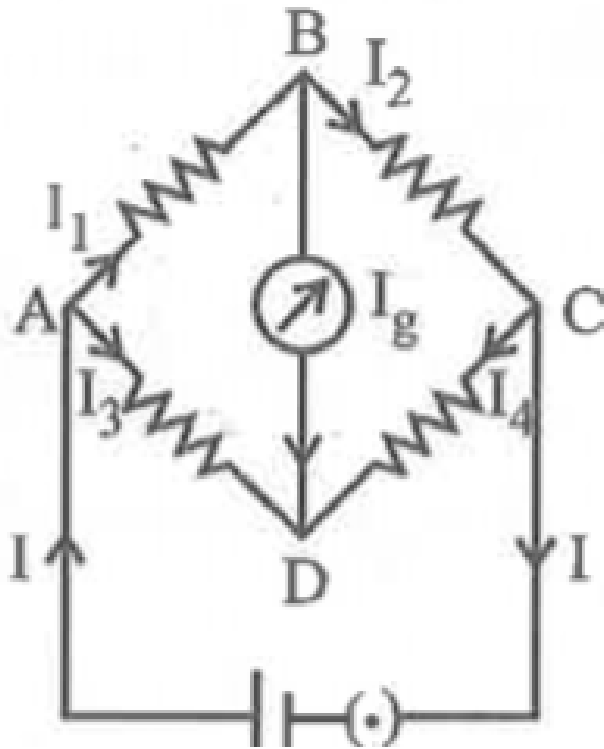

A. at  $A$ ,  $I = I_1 + I_3$

B. at  $B$ ,  $I_1 = I_2 + I_g$

C. at  $C$ ,  $I_2 = I_4 + I$

D. at  $D$ ,  $I_3 + I_g = I_4$


**Answer: D**



**Watch Video Solution**

**14.** Twelve identical wires each of resistance  $R$  are joined to form a cube as shown in the figure. A current of 6 ampere enters the cube at  $A$  and leaves at  $G$ . The current  $I$  in the

branch FG is

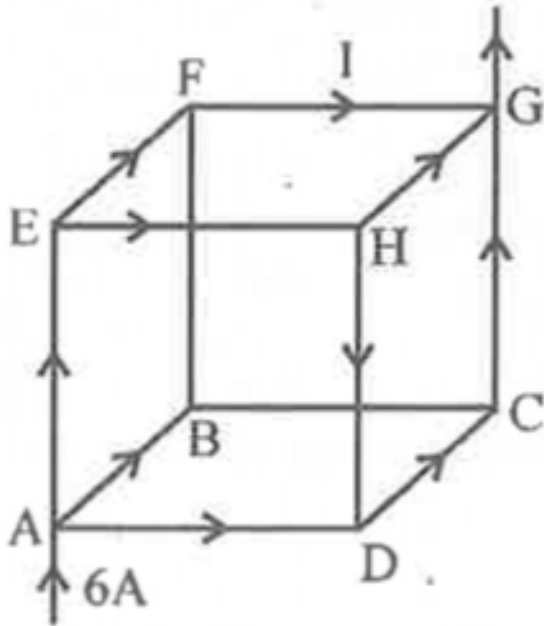

A.  $1A$

B.  $2A$

C.  $3A$

D.  $4A$


**Answer: B**



**View Text Solution**

**15.** 12 identical wires, each of resistance  $R$  are joined to form a cube as shown in the figure. A current of 6 Amperes enters the cube at A. If the wire HG is removed, then the current  $I$

leaving the network at G is

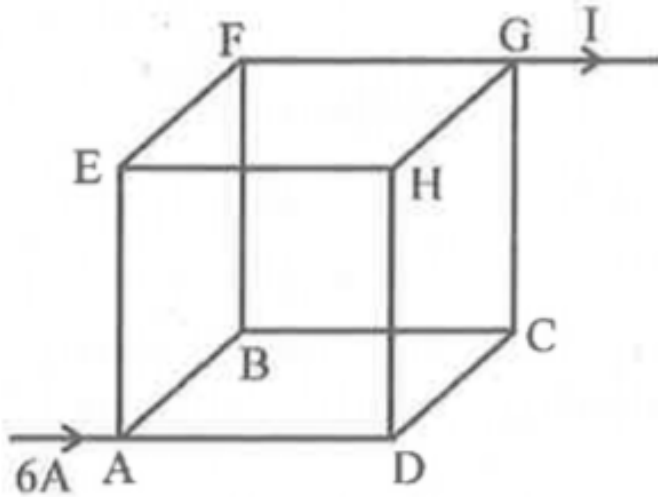

A.  $3A$

B.  $4A$

C.  $6A$

D.  $0.6A$

**Answer: C**





[View Text Solution](#)

16. A 220 volt, 1000 watt bulb is connected across a 110 volt mains supply. What is the power consumed in the circuit ?

A. 1000 watt

B. 250 watt

C. 750 watt

D. 500 watt

**Answer: B**



Watch Video Solution

17. What is the potential difference across the  $3\Omega$  resistor ?



A. Zero

B. 1V

C. 3.5V


D. 7V

**Answer: A**



View Text Solution

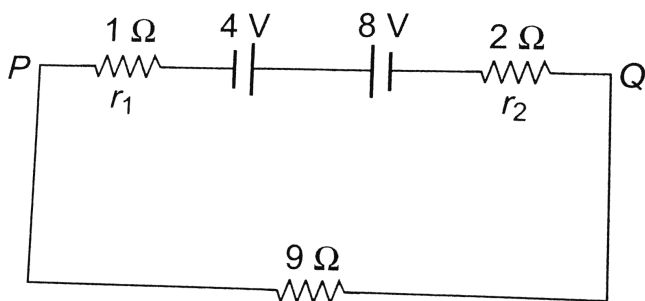18. Two batteries of e.m.f.  $4V$  and  $8V$  with internal resistances  $1\Omega$  and  $2\Omega$  are connected in a circuit with a resistance of  $9\Omega$  as shown in figure. The current and potential difference between the points  $P$  and  $Q$



A.  $\frac{1}{3}A$  and  $4V$

B.  $\frac{1}{3}A$  and  $3V$

C.  $\frac{1}{2}A$  and  $5V$

D.  $\frac{1}{6}A$  and  $3V$


**Answer: B**



**Watch Video Solution**

**19.** What are the values of  $E$  in the following circuit, if a current of  $2\text{ A}$  flows in the clockwise

as well as in anticlockwise direction ?

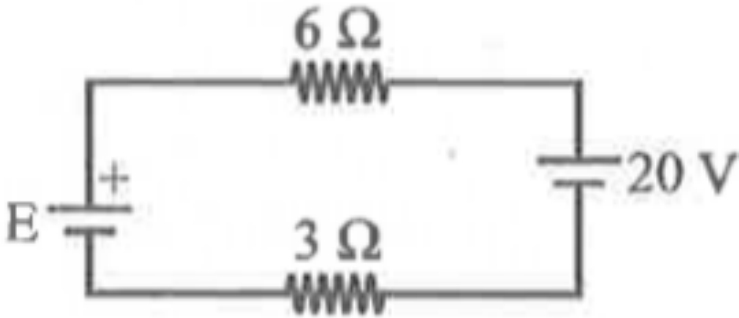

A. 3 V, 28 V

B. 38 V, 2V

C. 3V, 30V


D. 3V, 2.8 V

**Answer: B**



**Watch Video Solution**

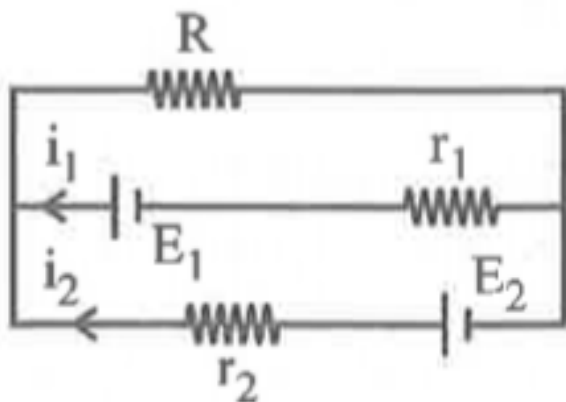20. Which one of the following equations is the correct equation for the electrical circuit shown in the figure ?



A.  $E_1 - (i_1 + i_2)R + i_1 r_1 = 0$

B.  $E_1 - (i_1 + i_2)R - i_1 r_1 = 0$

C.  $E_2 - i_2 r_2 - E_1 - i_1 r_1 = 0$

$$D. E_2 - (i_1 + i_2)R + i_2R_2 = 0$$


**Answer: B**



**Watch Video Solution**

**21.** If the galvanometer in the circuit of figure reads zero, calculate the value of the resistor  $R$  (in  $K\omega$ ) assuming that the 12 V source has

negligible internal resistance.

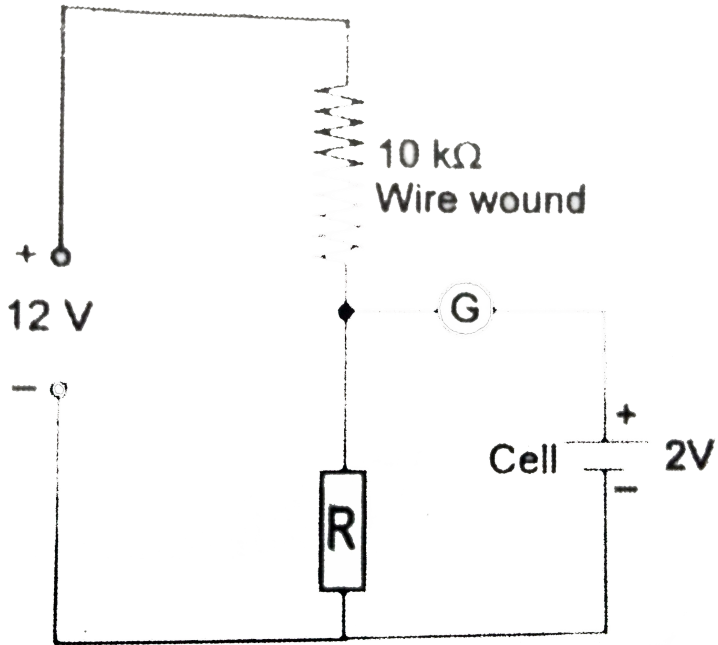

A.  $1000\Omega$

B.  $2000\Omega$

C.  $1500\Omega$

D.  $3500\Omega$




Answer: B



Watch Video Solution

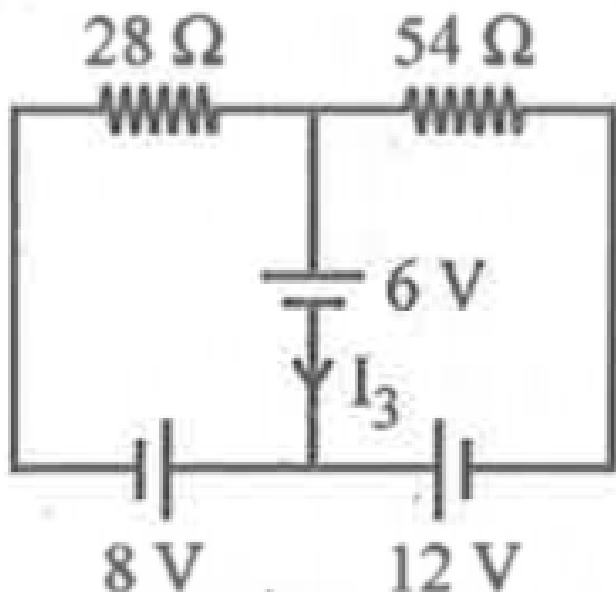22. Consider the circuit shown in the figure.

What is the value of the current  $I_3$  ?



A. 5 amp

B. 3 amp

C.  $-3$  amp


D.  $-\frac{5}{6}$  amp

**Answer: D**



**Watch Video Solution**

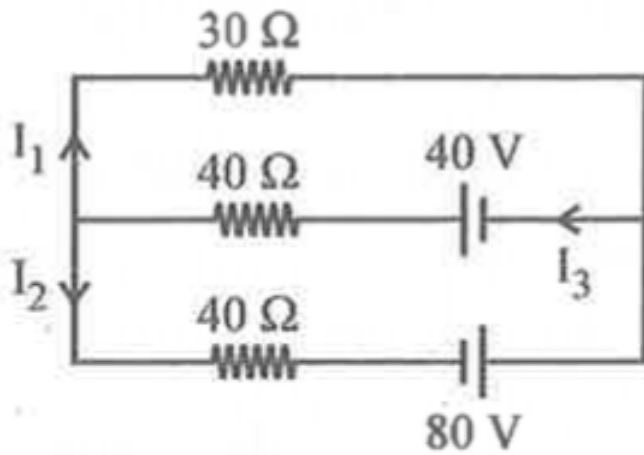**23.** What is the value of the current  $I_1$  in the given circuit ?



A.  $0.4\text{ A}$

B.  $-0.4\text{ A}$

C.  $0.8\text{ A}$


D.  $-0.8\text{ A}$

**Answer: B**



**Watch Video Solution**

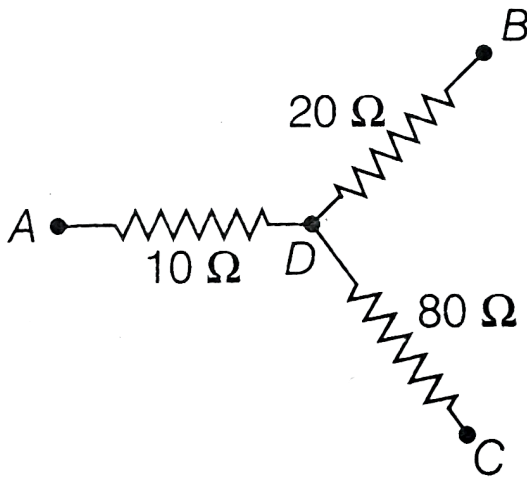24. In the circuit given here, the points A,B and C are 70 V, zero, 10 V respectively . Then,



- A. The point D will be at a potential of 60 V
- B. The point D will be at a potential of 20 V

C. Currents in the path AD, DB and DC are  
in the ratio of 1 : 2 : 3

D. Currents in the paths AD, DB and DC are  
in the ratio of 3 : 2 : 1


**Answer: D**



**Watch Video Solution**

**25.** In the circuit shown in the figure, if potential at point  $A$  is taken to be zero, the

potential at point  $B$  is

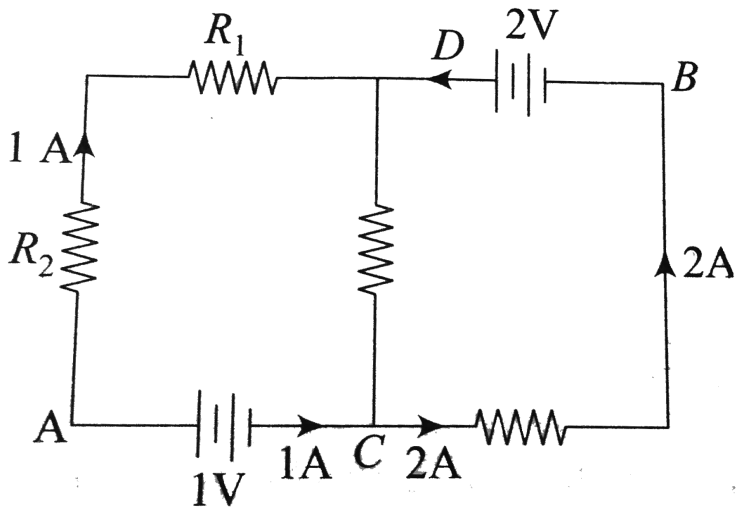

A.  $-2V$

B.  $+1V$

C.  $-1V$


D.  $+2V$

**Answer: B**



Watch Video Solution

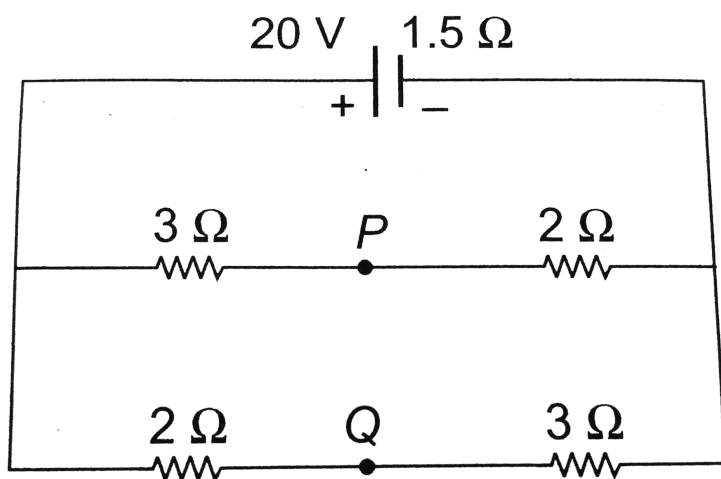26. If in the circuit shown below, the internal resistance of the battery is  $1.5\Omega$  and  $V_P$  and  $V_Q$  are the potential at  $P$  and  $Q$  respectively, what is the potential difference between the point  $P$  and  $Q$ ?



A. Zero

B.  $4V (V_P > V_Q)$

C.  $4V (V_Q > V_P)$

D.  $2.5V (V_Q > V_P)$

**Answer: D**




**Watch Video Solution**

**27.** A  $5V$  battery with internal resistance  $2\Omega$  and a  $2V$  battery with internal resistance  $1\Omega$  are connected to a  $10\Omega$  resistor as shown in



the figure.

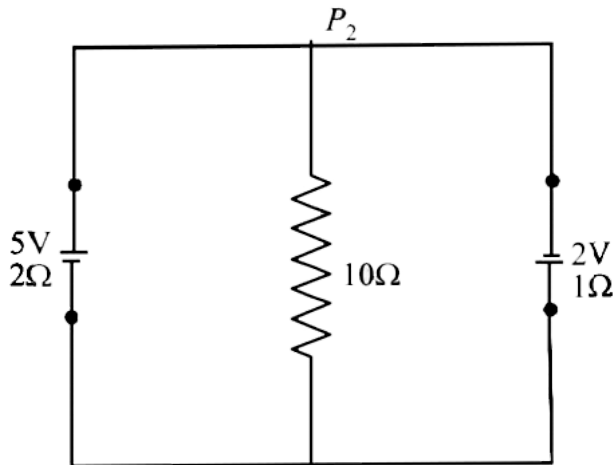

The current in the  $10\Omega$  resistor is


- A. 0.03 A from  $P_1$  to  $P_2$
- B. 0.03 A from  $P_2$  to  $P_1$
- C. 0.28 A from  $P_1$  to  $P_2$
- D. 0.28 A from  $P_2$  to  $P_1$

**Answer: D**



**Watch Video Solution**

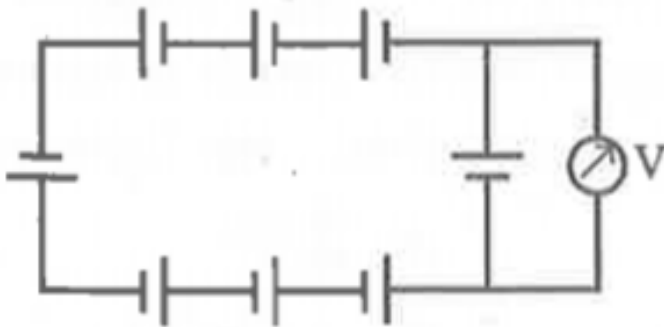**28.** In the following circuit, each cell has an e.m.f. of 5 V and an internal resistance of  $0.2\Omega$ .  
What is the reading of the ideal voltmeter V in volts ?



A. 5V

B. 40V

C. 0 V

D. 35 V


**Answer: C**



**View Text Solution**

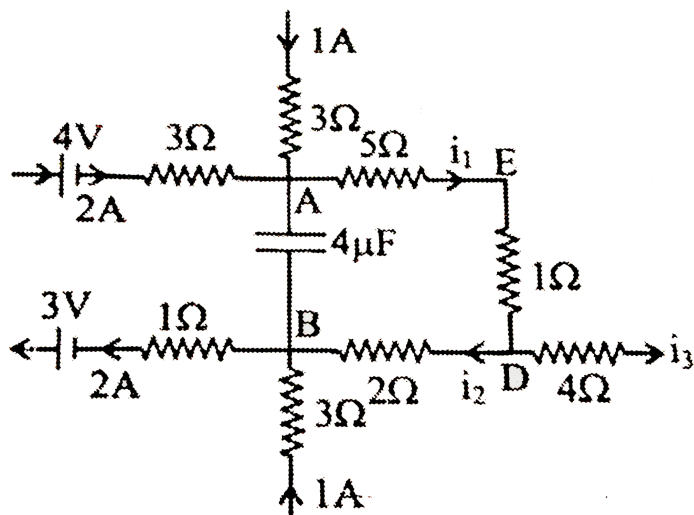**29.** The figure shows a part of the circuit in the steady state. The currents, the values of resistances and emfs of the cells are shown in

the figure. The circuit also contains a capacitor of capacitance  $C = \mu F$ . The value of  $i_1$  is-



- A. 1A, 2A, 3A
- B. 3A, 2A, 1A
- C. 2A, 1A, 3A
- D. 3A, 1A, 2A

**Answer: D**






**Watch Video Solution**

**30.** The three resistance of equal value are arranged in the different combination shown below. Arrange them in increasing order of power dissipation.



(I)

(II)

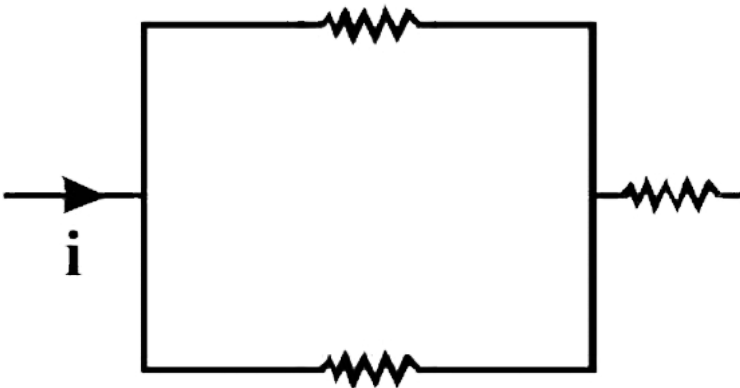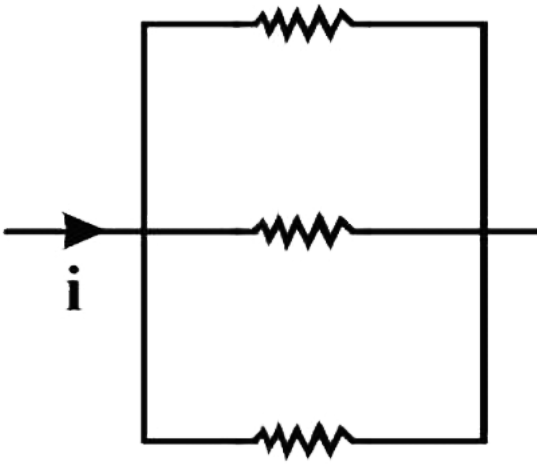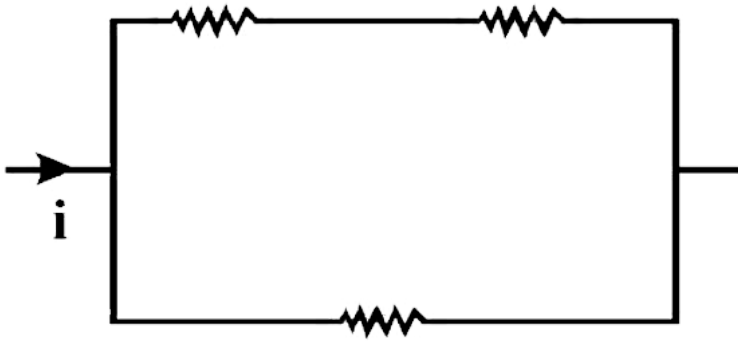

(IV)

A.  $I < III < II < IV$

B.  $II < III < IV < I$

C.  $III < II < IV < I$


D.  $I < IV < III < II$

**Answer: D**



**Watch Video Solution**

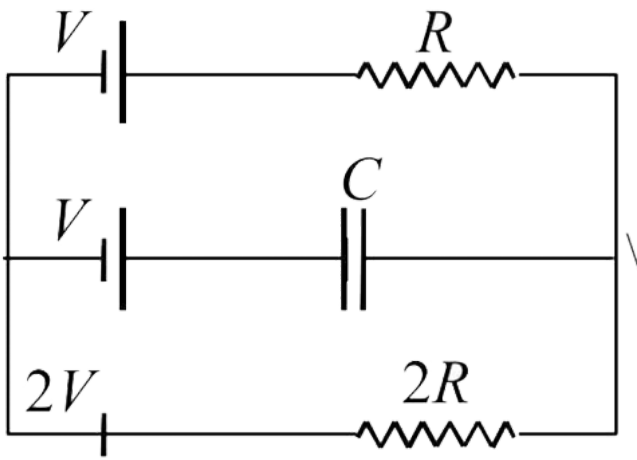**31.** In the given circuit, with steady current, the potential drop across the capacitor must be



A.  $V$

B.  $V/2$

C.  $V/3$

D.  $2V/3$

**Answer: C**



**Watch Video Solution**



**32.** Incandescent bulbs are designed by keeping in mind that the resistance of their filament increases with the increase in temperature. If at room temperature,  $100W$ ,  $60W$  and  $40W$  bulbs have filament resistances  $R_{100}$ ,  $R_{60}$  and  $R_{40}$ , respectively, the relation between these resistances is

A. 
$$\frac{1}{R_{100}} = \frac{1}{R_{40}} + \frac{1}{R_{60}}$$

B. 
$$R_{100} = R_{40} + R_{60}$$

C. 
$$R_{100} > R_{60} > R_{40}$$

$$\text{D. } \frac{1}{R_{100}} > \frac{1}{R_{60}} > \frac{1}{R_{40}}$$


**Answer: D**



**Watch Video Solution**

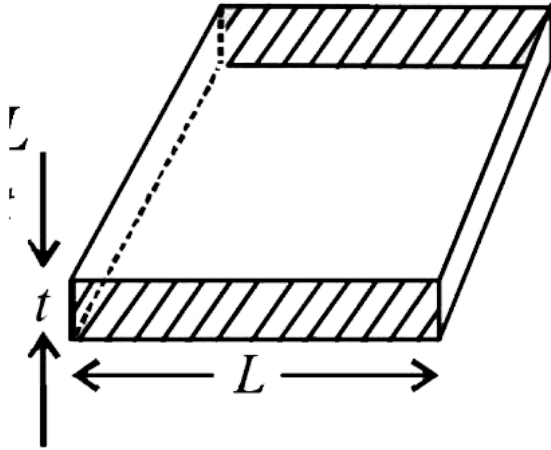**33.** Consider a thin square sheet of side  $L$  and thickness  $t$ , made of a material of resistivity  $\rho$ . The resistance between two opposite faces,

shown by the shaded areas in the figure is




- A. directly proportional to  $L$
- B. directly proportional to  $t$
- C. independent of  $L$
- D. independent of  $t$

**Answer: C**



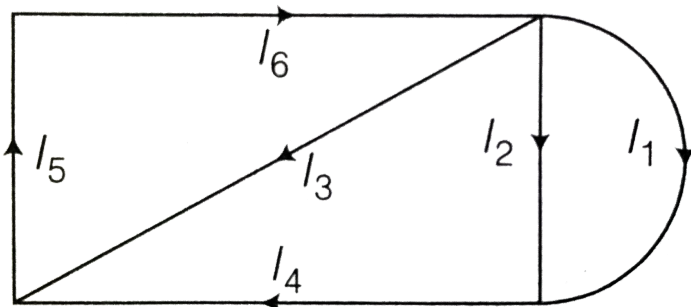34. In the following network of 5 branches, the respective current are  $l_1, l_2, l_3$  etc. given that  $l_1 = -0.5A, l_4 = 1A$  and  $l_5 = 0.5A$ , the remaining currents are



A.  $I_2 = -1.5A, I_3 = 0.5A, I_6 = 0.5A$

B.  $I_2 = 1.5A, I_3 = -0.5A, I_6 = 0.5A$

C.  $I_2 = 1.5A, I_3 = 0.5A, I_6 = -0.5A$

D.  $I_2 = 1.5A, I_3 = 0.5A, I_6 = 0.5A$

**Answer: B**



**Watch Video Solution**

**35.** Time taken by a 836 W heater to heat one litre of water from  $10^\circ C \rightarrow 40^\circ C$  is

A. 100 s

B. 150 s

C. 200 s

D. 50 s


**Answer: B**



**Watch Video Solution**

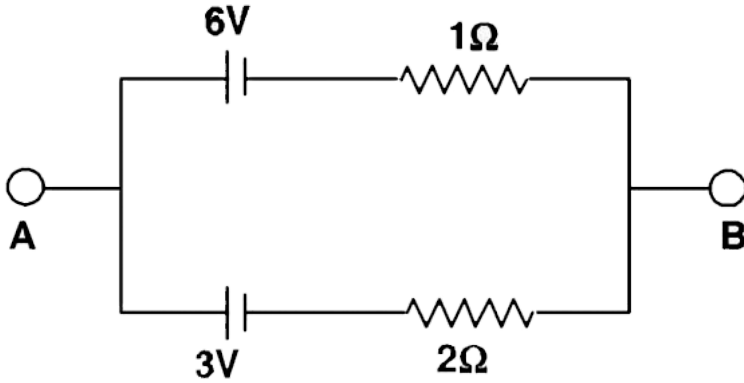**36.** Two batteries of different emfs and different internal resistances are connected as

shown. The voltage across AB in volts is.



A. 3V

B. 4V

C. 5V

D. 6V

**Answer: C**



Watch Video Solution

**37.** For resistances  $10\Omega$ ,  $10\Omega$ ,  $10\Omega$  and  $15\Omega$  form a Wheatstone's network. What shunt is required across  $15\Omega$  resistor to balance the bridge ?

A.  $10\Omega$

B.  $15\Omega$

C.  $20\Omega$

D.  $30\Omega$




**Answer: D**



**Watch Video Solution**

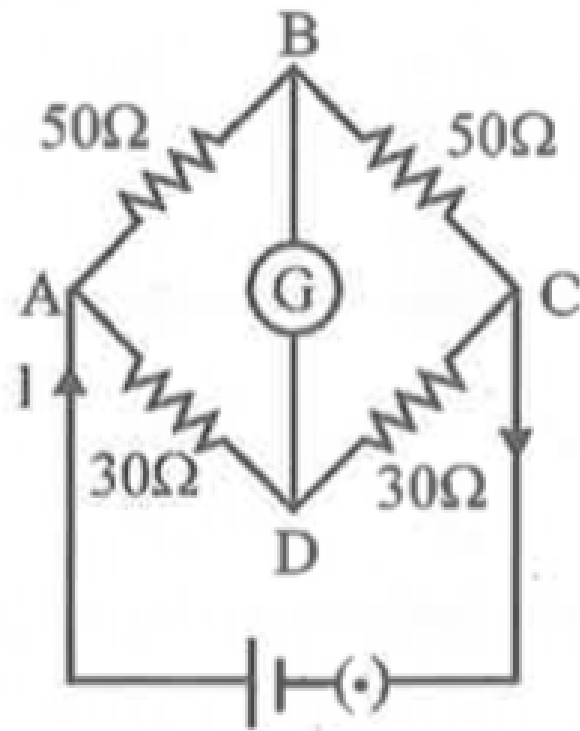**38.** In the given circuit, the current in the arm  
BD is



A.  $I/2$

B. zero

C.  $2I$


D.  $I/3$

**Answer: B**



**Watch Video Solution**

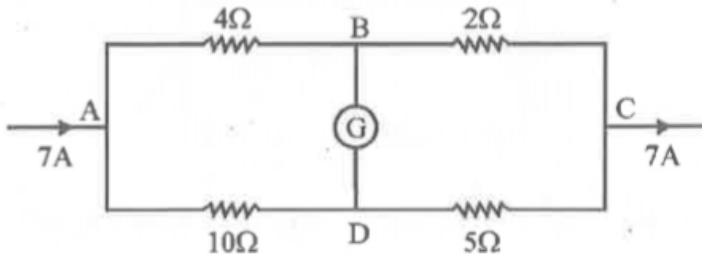**39.** In the given circuit, the potential difference between the points A and B is



A. 10 V

B. 15 V

C. 20 V

D. 5V


**Answer: C**



**Watch Video Solution**

**40.** The Wheatstone's network is shown in the figure. If the key K is closed, then the

galvanometer will

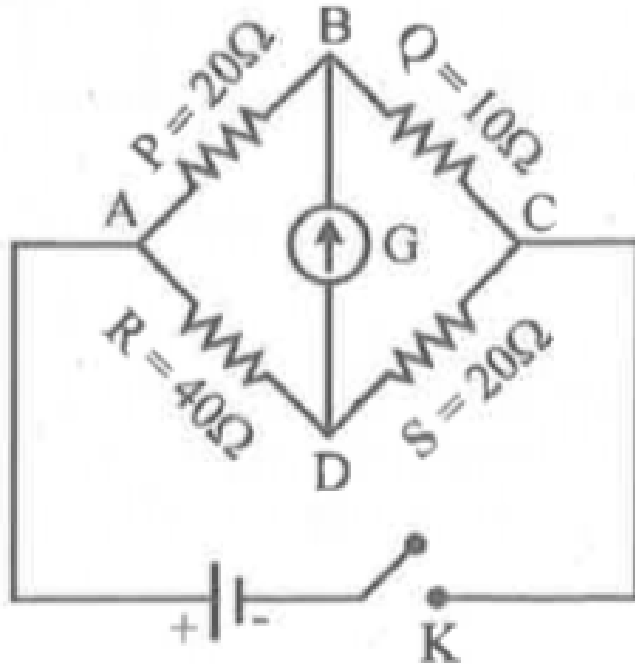


- A. deflect on the left side
- B. deflect on the right side
- C. deflect on either side
- D. not show any deflection

**Answer: D**



**Watch Video Solution**

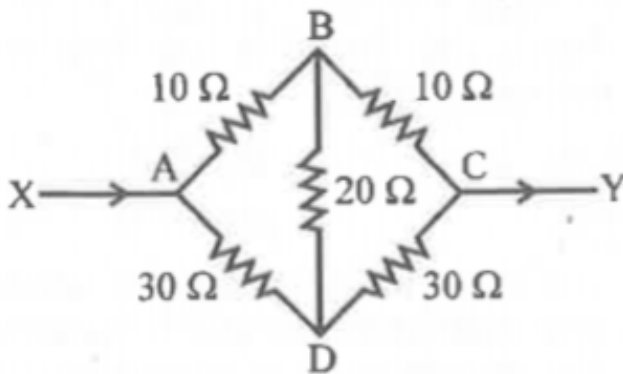**41.** Five resistances are joined as shown in the figure.



The equivalent resistance between the points X and Y is

A.  $10\Omega$

B.  $15\Omega$

C.  $20\Omega$


D.  $30\Omega$

**Answer: B**



**Watch Video Solution**

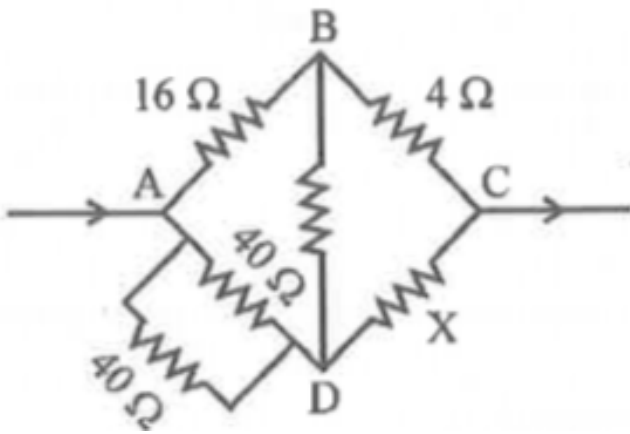**42.** In the given circuit, the potential difference between the points B and D is zero



The unknown resistance (X) is

- A.  $4\ \Omega$
- B.  $20\ \Omega$
- C.  $10\ \Omega$
- D.  $5\ \Omega$

**Answer: D**







**43.** The resistances in the left and right gaps of a metre bridge are  $10\Omega$  and  $30\Omega$  respectively. If the bridge is balanced, then the distance of the null point from the centre of the wire is

- A. 20 cm
- B. 30 cm
- C. 40 cm
- D. 25 cm

**Answer: D**



**Watch Video Solution**

**44.** A circular coil has a resistance of  $40\Omega$ . Two points P and Q of the coil, which are one quarter of the circumference apart are connected to a 16 V battery, having an internal resistance of  $0.5\Omega$  ? What is the main current flowing in the circuit ?

A. 0.5 A

B. 1A

C. 2A

D. 3A

**Answer: C**



**Watch Video Solution**

**45.** In a metre bridge experiment, the balancing length from the left end is found to be 20 cm. If a standard resistance of 20 ohm is

kept in the right gap, then the value of the unknown resistance in the left gap is

A.  $5\Omega$

B.  $10\Omega$

C.  $15\Omega$

D.  $7.5\Omega$

**Answer: A**



**Watch Video Solution**

**46.** To find the resistance of a gold bangle, two diametrically opposite points of the bangle are connected to the two terminals of the left gap of a metre bridge. A resistance of  $4\Omega$  is introduced in the right gap. What is the resistance of the bangle if the null point is at 20 cm from the left end ?

A.  $2\Omega$

B.  $4\Omega$


C.  $8\Omega$

D.  $16\Omega$

**Answer: B**

 [Watch Video Solution](#)

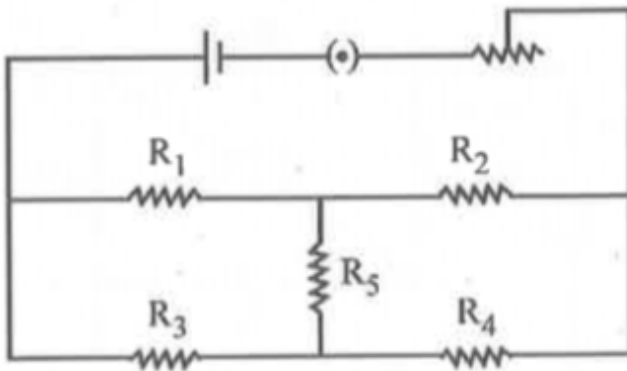47. 5 resistances  $R_1, R_2, R_3, R_4, R_5$  are joined as shown in the figure.



The values of  $R_1, R_2, R_3$  and  $R_4$  are so

adjusted that the current in the circuit does not change for any value of the resistance  $R_5$ .

This is possible for the following relation

A.  $R_1 + R_2 = R_3 + R_4$

B.  $\frac{R_1}{R_4} = \frac{R_2}{R_3}$

C.  $R_1 R_4 = R_3 R_2$


D.  $\frac{1}{R_1} + \frac{1}{R_3} = \frac{1}{R_2} + \frac{1}{R_4}$

**Answer: C**



**Watch Video Solution**

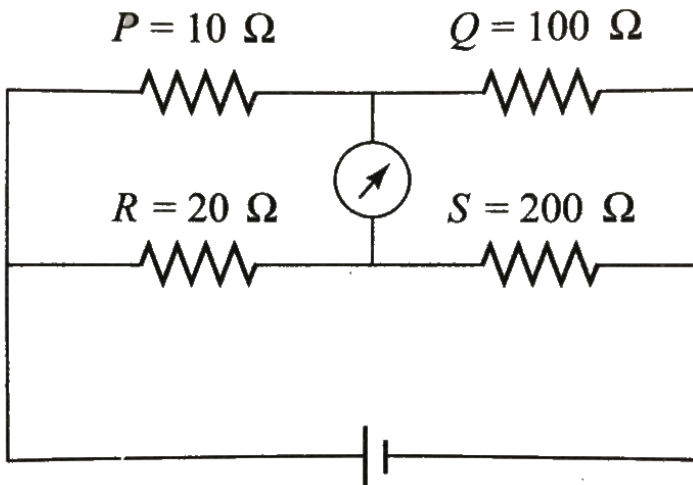48. Figure 6.52 shows a balanced wheatstone network. Now, it is disturbed by changing  $P$  to  $11\Omega$ . Which of the following steps will not bring the bridge to balance again?



- A. increasing  $R$  by  $2\Omega$
- B. increasing  $Q$  by  $10\Omega$
- C. increasing  $S$  by  $20\Omega$



D. making the product  $QR = 2200\Omega$

**Answer: C**



**Watch Video Solution**

**49.** If  $P = Q = R = 10\Omega$  and  $S = 20\Omega$ , then what resistance should be joined with S to balance the wheatstone's network ?

- A. Join a resistance of  $10\Omega$  in series with S
- B. Join a resistance of  $10\Omega$  in parallel with S

C. Join a resistance of  $20\Omega$  in parallel with S

D. Join a resistance of  $20\Omega$  in series with S

**Answer: C**



**Watch Video Solution**

**50.** The wheatstone's network is most sensitive when the ratio of its arms is

A. 1 : 1

B. zero

C. 10:1

D. 1:100


**Answer: A**



**Watch Video Solution**

**51.** In the given circuit, the galvanometer G gives zero deflection. What is the value of

resistance X ?

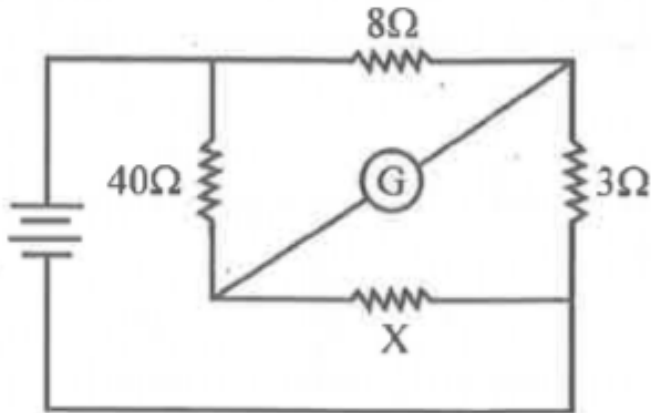

A.  $10\Omega$

B.  $12\Omega$

C.  $15\Omega$

D.  $20\Omega$

**Answer: C**



52. Two resistances are connected in the two gaps of a meter bridge. The balance point is  $20\text{cm}$  from the zero end. When a resistance  $15\Omega$  is connected in series with the smaller of two resistance, the null point shifts to  $40\text{cm}$ . The smaller of the two resistance has the value.

A.  $5\Omega$

B.  $7\Omega$

C.  $9\Omega$

D.  $12\Omega$

**Answer: C**



**Watch Video Solution**

**53.** For resistances arranged to form a wheatstone's network are  $10\Omega$ ,  $15\Omega$ ,  $6\Omega$  and  $36\Omega$ . What resistance should be connected across the  $36\Omega$  resistance to balance the bridge ?

A.  $9\Omega$

B.  $12\Omega$

C.  $15\Omega$

D.  $18\Omega$


**Answer: B**



**Watch Video Solution**

**54.** In the given network, if the points B and D are connected by a copper wire, then the

current in the wire will

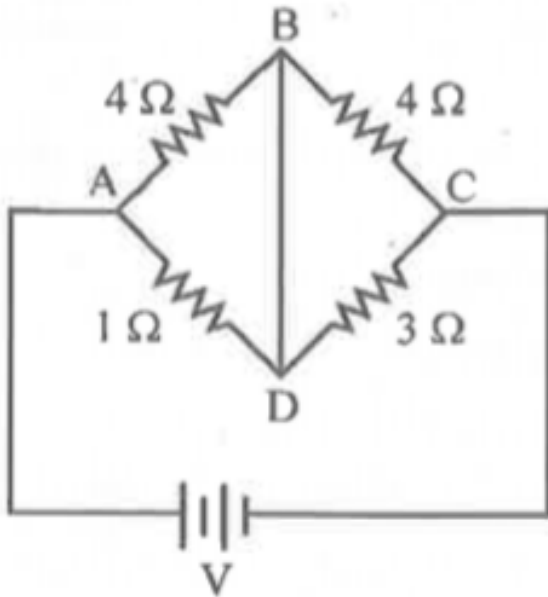

A. be zero

B. will flow from B to D

C. will flow from D to B



D. flow in that direction which will be decided by the total resistance and voltage  $V$

**Answer: C**



**Watch Video Solution**

**55.** An unknown resistance  $R_1$  is connected in series with a resistance of  $10\Omega$ . This combination is connected to one gap of a meter bridge, while other gap is connected to

another resistance  $R_2$ . The balance point is at  $50\text{cm}$ . Now, when the  $10\Omega$  resistance is removed, the balanced point shifts to  $40\text{cm}$ . Then the value of  $R_1$  is.

A.  $40\Omega$

B.  $30\Omega$

C.  $20\Omega$

D.  $10\Omega$

**Answer: C**



**Watch Video Solution**

**56.** The resistance of each arm of the wheat stone bridge is  $10\Omega$ . A resistance of  $10\Omega$  is connected in series with galvanometer then the equivalent resistance across the battery will be:-

A.  $40\Omega$

B.  $30\Omega$

C.  $20\Omega$

D.  $10\Omega$


**Answer: D**



**Watch Video Solution**

57.  $R_1, R_2, R_3$  are different values  $R$ .  $A, B$  and  $C$  are the null points obtained corresponding to  $R_1, R_2$  and  $R_3$  respectively. For which resistor, the value of  $R$  will be the

most accurate and why?

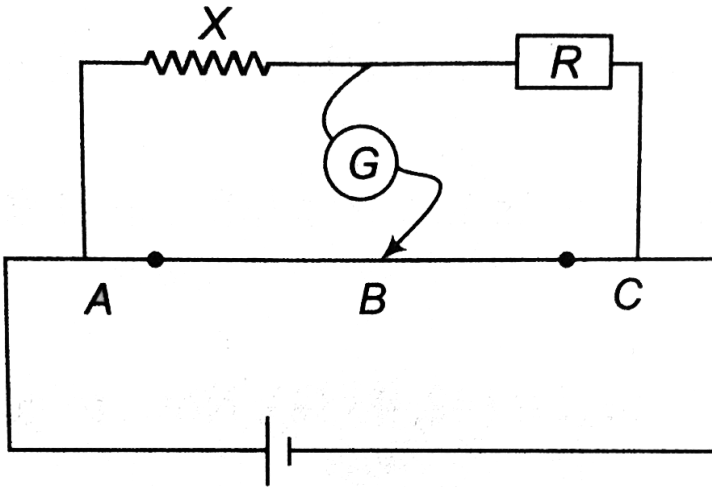

A. Resistance  $R_1$

B. Resistance  $R_2$

C. Resistance  $R_3$

D. All the three ( $R_1, R_2, R_3$ ) will give the

same accuracy

**Answer: B**



**Watch Video Solution**

**58.** Two resistances of values  $20\Omega$  and  $20\Omega$  are introduced in the left and right gaps of a metre bridge. What is the shift in the null point if a resistance of  $40\Omega$  is connected in series with the resistance in the left gap ?

A. 25 cm towards left of the centre

B. 25 cm towards right of the centre

C. 15 cm towards right of the centre


D. 15 cm towards left of the centre

**Answer: B**



**Watch Video Solution**

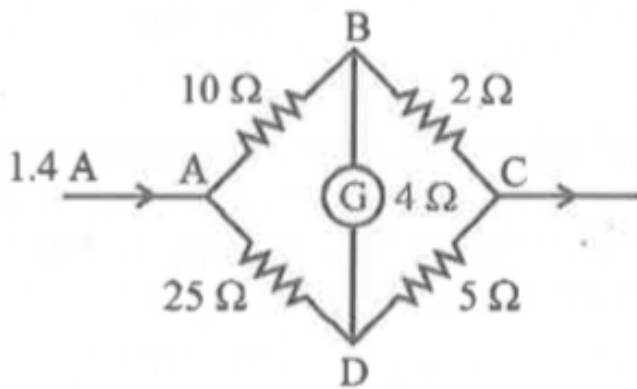**59.** What is the current in  $10\Omega$  resistance in the following network ?



- A. 1A
- B. 1.2A
- C. 0.8A
- D. 2A


**Answer: A**



**Watch Video Solution**



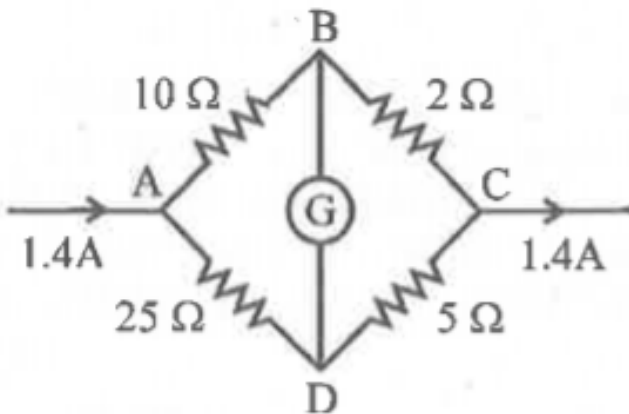60. In the given circuit, when the galvanometer G shows no deflection, the current in the  $5\Omega$  resistance is ,



- A.  $0.4\text{A}$
- B.  $0.6\text{A}$
- C.  $0.8\text{A}$

D. 1.0A

**Answer: A**



**Watch Video Solution**

**61.** In a typical Wheatstone's network, the resistances in the cyclic order are  $P = 10\Omega$ ,  $Q = 5\Omega$ ,  $S = 4\Omega$  and  $R = 4\Omega$ .

For balancing the bridge, a resistance of


- A.  $10\Omega$  should be connected in series with  
P
- B.  $10\Omega$  should be connected in parallel with  
P
- C.  $10\Omega$  should be connected in series with  
Q
- D.  $10\Omega$  should be connected in parallel with  
Q

**Answer: B**



**Watch Video Solution**

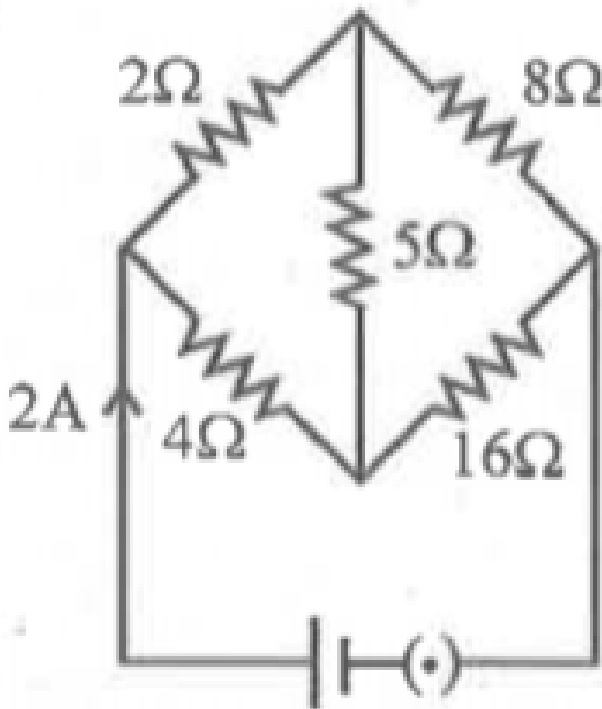62. In the following circuit, the current drawn from the battery is 2A. If the  $5\Omega$  resistance is replaced by a  $20\Omega$  resistor, then the current drawn from the battery will be



A. 0.5A

B. 1A

C. 8A

D. 2A


**Answer: D**



**Watch Video Solution**

**63.** In the given circuit, the galvanometer will not show any deflection if the value of the

resistance X is

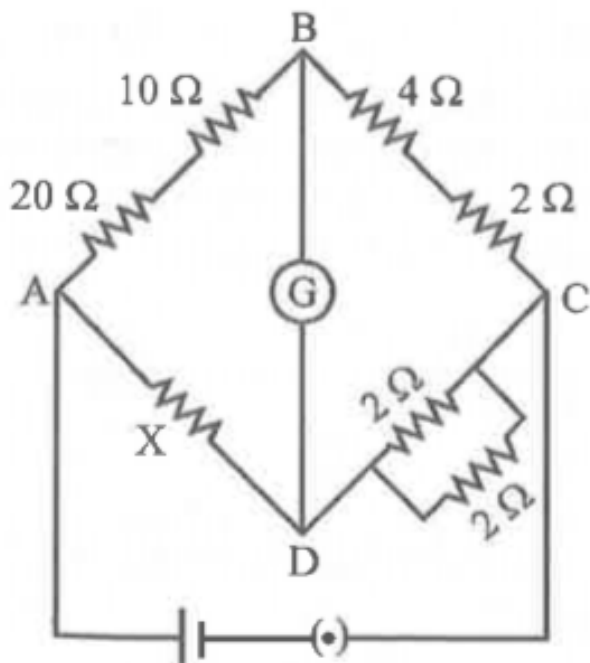

A.  $3\ \Omega$

B.  $4\ \Omega$

C.  $5\ \Omega$


D.  $6\ \Omega$

**Answer: C**



**Watch Video Solution**

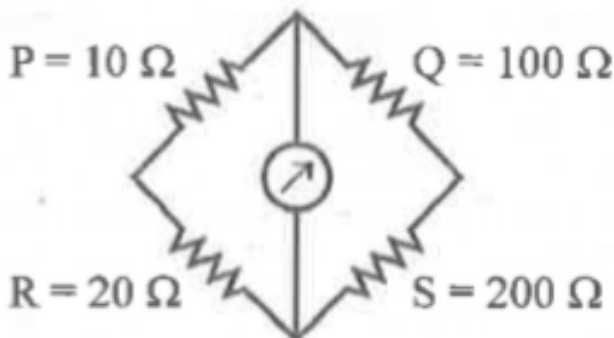**64.** A balanced Wheatstone's network is shown in the figure. If the balance is disturbed by changing  $P$  to  $15\Omega$ , then which one of the following steps will not bring the bridge to balance again ?



A. increase R by  $10\Omega$

B. increase S by  $20\Omega$

C. increase Q by  $50\Omega$

D. make  $RQ = 3000\Omega$

**Answer: B**



**Watch Video Solution**

**65.** Resistance in the two gaps of a meter bridge are  $10\text{ohm}$  and  $30\text{ohm}$  respectively. If



the resistances are interchanged the balance point shifts by

A. 33.3 cm

B. 66.67 cm

C. 25 cm

D. 50 cm

**Answer: D**



**Watch Video Solution**

**66.** A wire of length 3 m connected in the left gap of a metre bridge balances a  $8\Omega$  resistance in the right gap at a point, which divides the bridge wire in the ratio of 3:2 .  
What is the length of the wire corresponding to a resistance of the length of the wire corresponding to a resistance of  $1\Omega$  ?

A. 1m

B. 0.75 m

C. 0.5 m

D. 0.25 m

**Answer: D**



**Watch Video Solution**

**67.** 6 resistances, each of  $4\Omega$  are joined as shown in the figure. What is the equivalent resistance between A and B ?



A.  $4\Omega$

B.  $8\Omega$

C.  $6\Omega$

D.  $2\Omega$

**Answer: D**



**View Text Solution**

**68.** In the given figure, when the galvanometer shows no deflection, the current (in amperes) flowing through the  $5\Omega$  resistance will be



A. 0.2 A

B. 0.6A

C. 0.9A


D. 1.5A

**Answer: B**



**View Text Solution**

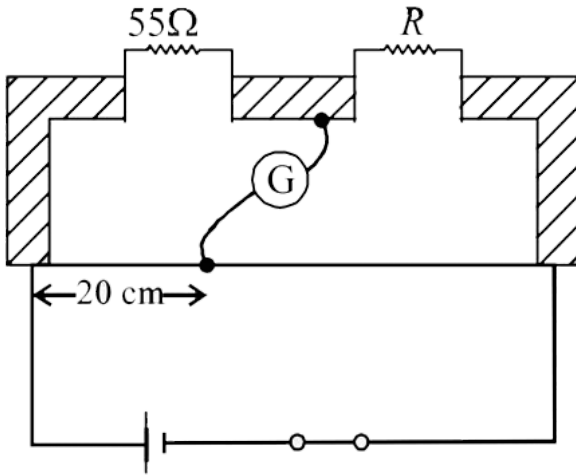**69.** Shown in the figure below is a meter-bridge set up will null deflection in the galvanometer.



The value of the unknown resistor  $R$  is

- A.  $55\Omega$
- B.  $110\Omega$
- C.  $220\Omega$
- D.  $13.75\Omega$

**Answer: C**



Watch Video Solution

70. If in the experiment of Wheatstone's bridge, the positions of cells and galvanometer are interchanged, then balance point will

A. remains unaltered

B. alters

C. may or may not altered depending on the resistance of the galvanometer and

the battery

D. none of these

**Answer: A**



**Watch Video Solution**

**71.** In a Wheatstone's bridge, three resistances P, Q and R connected in the three arms and the fourth arm is formed by two resistances  $S_1$  and  $S_2$  connected in parallel. The condition for the bridge to be balanced will be



$$\text{A. } \frac{P}{Q} = \frac{R(S_1 + S_2)}{S_1 + S_2}$$

$$\text{B. } \frac{P}{Q} = \frac{R}{S_1 + S_2}$$

$$\text{C. } \frac{P}{Q} = \frac{R(S_1 + S_2)}{S_1 S_2}$$

$$\text{D. } \frac{P}{Q} = \frac{R(S_1 + S_2)}{2S_1 S_2}$$

**Answer: C**



**Watch Video Solution**

**72.** In the given arrangement of the metre bridge, the null point is obtained at a distance  $x$  from the end A. What will be the distance of

the null point from A, if the radius of the wire

AB is doubled ?



A.  $2x$

B.  $\frac{x}{2}$

C.  $x$

D.  $3x$

**Answer: C**



**View Text Solution**

**73.** In a meter bridge experiment, the null point is obtained at  $20\text{cm}$  from one end of the wire when resistance  $X$  is balanced against another resistance  $Y$ . If  $X < Y$ , then where will be the new position of the null point from the same end, if one decides to balanced a resistance of  $4X$  against  $Y$ ?

A. 30 cm

B. 40 cm

C. 50 cm


D. 60 cm

**Answer: C**



**Watch Video Solution**

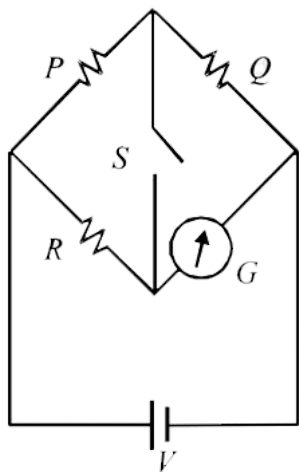**74.** In the circuit  $P \neq R$ , the reading of the galvanometer is same with switch  $S$  open or closed. Then



A.  $I_R = I_G$

B.  $I_P = I_G$

C.  $I_Q = I_G$

D.  $I_Q = I_R$

**Answer: A**



**Watch Video Solution**

**75.** A post office box is shown in figure. In order to calculate the value of an external

resistance, it should be connected between



A. B and C

B. C and D

C. A and D

D.  $B_1$  and  $C_1$

**Answer: C**



**View Text Solution**

76. In the circuit shown, a metre bridge is in its balanced state. The metre bridge wire has a resistance  $0.1 \text{ ohm/cm}$ . What are the values of the unknown resistance  $X$  and the current drawn from the battery of negligible resistance ?



A.  $6\Omega$ ,  $5\text{amp}$

B.  $10\Omega$ ,  $0.1\text{amp}$

C.  $4\Omega$   $1.0 \text{ amp}$

D.  $12\Omega$ , 0.5 amp

**Answer: C**



**View Text Solution**

77. Each of the resistance in the network shown in the figure is equal to  $R$ . The resistance between the terminals A and B is



A.  $3R$



B. R

C. 5R

D. 6R


**Answer: B**



**View Text Solution**

**78.** In the following circuit, a conducting wire is connected between the terminals B and D, the

current in the wire will

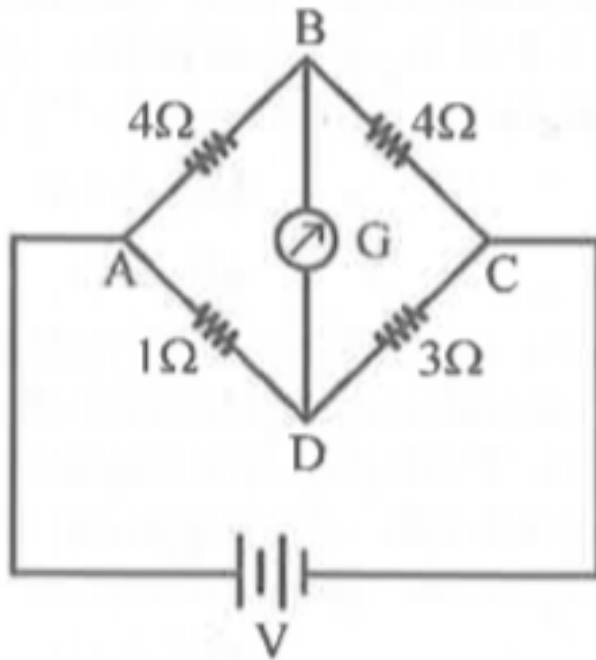

- A. flow from B to D
- B. flow from D to B
- C. the zero

D. flow in the direction which will be decided by the voltage  $V$

**Answer: B**



**Watch Video Solution**

**79.** In the Wheatstone bridge shown below, in order to balance the bridge, we must have



A.  $R_1 = 3\Omega, R_2 = 3\Omega$

B.  $R_1 = 6\Omega, R_2 = 15\Omega$

C.  $R_1 = 1.5\Omega, R_2 = \text{any finite value}$

D.  $R_1 = 3\Omega, R_2 = \text{any finite value}$

**Answer: D**



**View Text Solution**

**80.** A metre bridge is set-up as shown in the figure to determine an unknown resistance 'X' using a standard 10 ohm resistor. The galvanometer shows null point when the

tapping-key is at 52 cm mark. The end-correction are 1 cm and 2 cm respectively for the ends A and B. What is the value of 'X' ?



A.  $10.2\Omega$

B.  $10.6\Omega$

C.  $10.8\Omega$


D.  $11.1\Omega$

**Answer: B**



**View Text Solution**

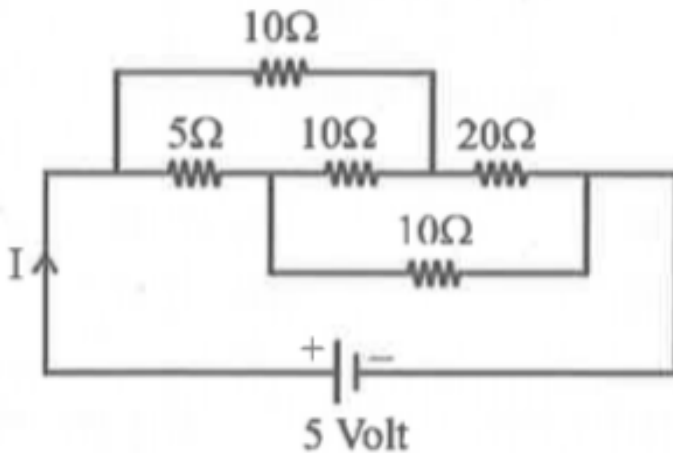81. In the adjoining circuit, the current  $I$  drawn from the 5 volt source will be



A. 0.67 A

B. 0.17A

C. 0.33A

D. 0.5A


**Answer: D**



**Watch Video Solution**

**82.** A battery of internal resistance  $4\Omega$  is connected to the network of resistance as shown . In order that the maximum power can be delivered to the network, the value of R in

$\Omega$  should be

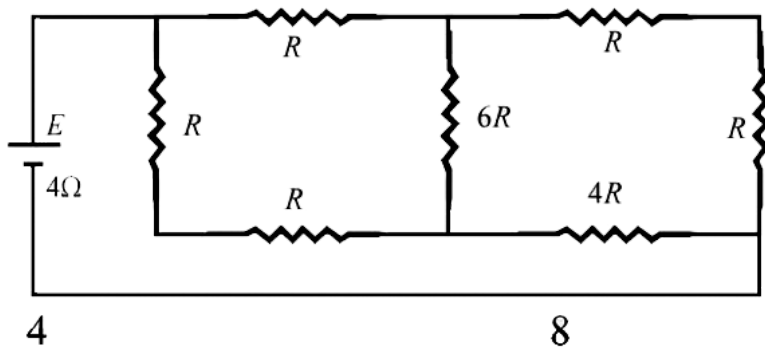

- A.  $2\Omega$
- B.  $\frac{8}{3}\Omega$
- C.  $18\Omega$
- D.  $\frac{4}{9}\Omega$


**Answer: A**





Watch Video Solution

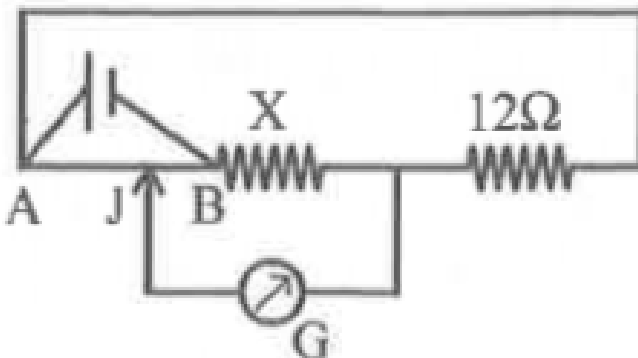83. A uniform wire AB of length 1 m, an unknown resistance X and a resistance of  $12\Omega$  are connected to a battery and a galvanometer G as shown in the figure. The galvanometer shows no deflection when  $AJ=60$  cm. What is the value of X (in ohm) ?



A.  $6\Omega$

B.  $8\Omega$

C.  $10\Omega$

D.  $4\Omega$

**Answer: B**



**Watch Video Solution**

**84.** The resistances in left and right gap of a meter bridge are  $20\ \omega$  and  $30\ \omega$  respectively

when the resistance in the left gap is reduced to half its value then balance point shifts by

- A. 15 cm to the right
- B. 15 cm to the left
- C. 20 cm to the right
- D. 20 cm to the left

**Answer: B**



**Watch Video Solution**

**85.** The resistance in the two arms of the metre bridge are  $5\Omega$  and  $R\Omega$ , respectively. When the resistance  $R$  is shunted with an equal resistance, the new balance point is at  $1.6l_1$ . The resistance  $R$  is



A.  $20\Omega$

B.  $25\Omega$

C.  $10\Omega$

D.  $15\Omega$

**Answer: D**



**View Text Solution**

**86.** In a typical wheatstone network, the resistances in cyclic order are  $A = 10\Omega$ ,  $B = 5\Omega$ ,  $D = 4\Omega$  and  $C = 4\Omega$ .

For the bridge to be balanced



A.  $10\Omega$  should be connected in series with

A

B.  $5\Omega$  should be connected in series with B

C.  $5\Omega$  should be connected in parallel with

B

D.  $10\Omega$  should be connected in parallel with

A

**Answer: D**



**View Text Solution**

87. What is the equivalent resistance between the points P and Q in the network shown in the figure ?



- A.  $7.5\Omega$
- B.  $12.5\Omega$
- C.  $2.5\Omega$
- D.  $10\Omega$

**Answer: A**



**View Text Solution**

**88.** A cell of e.m.f. of 1.08 V is balanced by a 216 cm length of a potentiometer. What is the length of the wire that would balance a cell of e.m.f. 1.5 V ?

- A. 250 cm
- B. 290 cm
- C. 300 cm
- D. 310 cm



**Answer: C**



**Watch Video Solution**

**89.** In a potentiometer experiment, the null point is obtained at 140 cm for a cell of e.m.f. 1.2 V. With another cell of unknown e.m.f., the null point is obtained at 210 cm. The unknown e.m.f. is

A. 1.5 V

B. 1.6 V

C. 1.8 V

D. 2 V

**Answer: C**



**Watch Video Solution**

**90.** In a potentiometer experiment, the balancing length is found to be 1.8 m for a cell of e.m.f. 1.5 V. What is the balancing length for a cell of e.m.f. 1 V ?

A. 1 m

B. 1.5 m

C. 1.2 m

D. 2 m

**Answer: C**



**Watch Video Solution**

**91.** Two cells of e.m.f.'s  $E_1$  and  $E_2$  where  $E_1 > E_2$ , are connected in series so as to assist each other, the balancing length is 2.7m

. When the cells are connected in series so as to oppose each other, the balancing length is found to be  $0.3m$  . What is the ratio of their e.m.f.'s ?

A. 1.1

B. 1.25

C. 1.5

D. 1.6

**Answer: B**



**Watch Video Solution**

92. A cell of e.m.f. 1.2 V is balanced by 150 cm of potentiometer wire. When the cell is shunted by a resistance of  $4\Omega$ , the balancing length is reduced by 30 cm. What is the internal resistance of the cell ?

A.  $1\Omega$

B.  $2\Omega$

C.  $0.5\Omega$

D.  $0.75\Omega$

**Answer: A**



**Watch Video Solution**

**93.** A potentiometer wire of length 400 cm has a resistance of  $8\Omega$ . If a potential gradient of 0.5 V/m is maintained throughout the length of the wire, then the current flowing through the wire is

A. 0.5 A

B. 0.25 A

C.  $1A$

D.  $0.75 A$

**Answer: B**



**Watch Video Solution**

**94.** A potentiometer wire is  $10\text{ m}$  long and a P.D. of  $6\text{ V}$  is maintained between its ends. The e.m.f. of the cell which balances against a length of  $200\text{ cm}$  of the potentiometer wire is

A. 1 V

B. 1.2 V

C. 2.4 V

D. 1.5V

**Answer: B**



**Watch Video Solution**

**95.** A potentiometer wire has a length 2 m and resistance of  $10\Omega$ . It is connected in series



with a resistance of  $990\Omega$  and a cell of e.m.f. 2

V. The potential gradient along the wire is

A.  $0.01V / m$

B.  $0.02V / m$

C.  $0.03V / m$

D.  $0.025V / m$

**Answer: A**



**Watch Video Solution**

**96.** A cell of e.m.f. 2 V and negligible internal resistance is connected to a potentiometer wire of resistance  $10\Omega$  and length 4 m. The potential difference per unit length (potential gradient ) of the wire is

A. 5 volt / metre

B. 10 volt / metre

C. 0.5 volt / metre

D. 1.5 volt / metre

**Answer: C**



Watch Video Solution

97. As is the cross sectional area and  $\rho$  is the specific resistance of a potentiometer wire. If  $I$  is the current passing through the potentiometer wire, then the potential gradient along the length of the wire is given by

A.  $\frac{IA}{\rho}$

B.  $IA\rho$

C.  $\frac{I\rho}{A}$

D.  $\frac{I}{\rho A}$

**Answer: C**



**Watch Video Solution**

**98.** A potentiometer experiment is set up to compare the e.m.f.'s  $E_1$  and  $E_2$  of two cells.

When the null point is obtained, the current is drawn from

A. only the driver cell

B. only the cell of e.m.f.  $E_1$

C. only the cell of e.m.f.  $E_2$

D. both the driver cell and the cells of  
e.m.f.s  $E_1$  and  $E_2$

**Answer: A**



**Watch Video Solution**

**99.** A cell of e.m.f. 4 V and of negligible internal resistance is connected in series with a potentiometer wire of length 400 cm. The

e.m.f. of a Leclanche cell is found to be balanced at 150 cm from the positive end of the potentiometer wire. What is the e.m.f. of the Leclanche cell ?

A. 1 V

B. 1.5 V

C. 2 V

D. 2.5 V

**Answer: B**



**Watch Video Solution**

**100.** A 10 m long wire of resistance  $20\Omega$  is connected in series with battery of EMF  $3V$  and negligible internal resistance and a resistance of  $10\Omega$ . The potential gradient along the wire is :

A.  $1V / m$

B.  $0.5V / m$

C.  $0.2V / m$

D.  $0.1V / m$

**Answer: C**



**Watch Video Solution**

**101.** In a potentiometer experiment of measuring the e.m.f. of a cell, the null point is at 300 cm, when we have a resistance of  $200\Omega$  in series with the cell and the galvanometer. If the resistance is increased to  $300\Omega$ , the null point will be shifted through

A. 100 cm



B. 50 cm

C. 25 cm

D. zero cm

**Answer: D**



**Watch Video Solution**

**102.** In a potentiometer experiment, to measure the e.m.f. of a cell, the potentiometer consists of six wires each of length 100 cm. The null point is obtained on the third wire. If

we want to shift the null point to the 5th wire,  
then we should

A. increase the resistance in the main  
circuit

B. decrease the resistance in the main  
circuit

C. increase the resistance in series with the  
cell, whose e.m.f. is to be measured

D. decrease the resistance in series with  
the cell, whose e.m.f. is to be measured

**Answer: A**



**Watch Video Solution**

**103.** The specific resistance of a potentiometer wire is  $10^{-7} \Omega\text{m}$  and the cross sectional area of the wire is  $10^{-6} \text{m}^2$ . If a current of 0.1 A flows through the wire, then the potential gradient will be

A.  $10^{-4} \text{V} / \text{m}$

B.  $10^{-3} \text{V} / \text{m}$

C.  $10^{-2}V/m$

D.  $10^{-5}V/m$

**Answer: C**



**Watch Video Solution**

**104.** In an experiment to find the internal resistance of a cell by a potentiometer, a balance was obtained for 50 cm length of the potentiometer wire, with a cell of e.m.f. 2V. When the cell was shunted by a resistance of

$2\Omega$ , the balancing length of the potentiometer wire was 40 cm. What was the internal resistance of the cell ?

A.  $0.25\Omega$

B.  $0.75\Omega$

C.  $0.5\Omega$

D.  $1\Omega$

**Answer: C**



**Watch Video Solution**

**105.** In a potentiometer experiment two cells of e.m.f.  $E_1$  and  $E_2$  are used in series and in conjunction and the balancing length is found to be 58 cm of the wire. If the polarity of  $E_2$  is reversed, then the balancing length becomes 29 cm. The ratio  $\frac{E_1}{E_2}$  of the e.m.f. of the two cells is

A. 1 : 2

B. 3 : 1

C. 2 : 1

D. 4 : 1


**Answer: B**



**Watch Video Solution**

**106.** What is the potential difference between the ends A and B of the given potentiometer wire, in the following circuit ? The

galvanometer G shows no deflection.

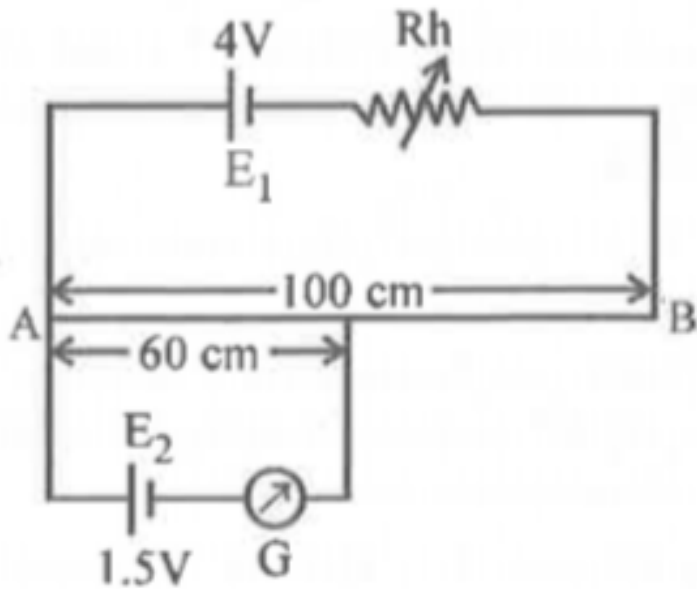

A. 1.5 V

B. 2 V

C. 2.5 V

D. 3 V



**Answer: C**



**Watch Video Solution**

**107.** A cell can be balanced against  $110\text{cm}$  and  $100\text{cm}$  of potentiometer wire, respectively with and without being short circuited through a resistance of  $10\Omega$ . Its internal resistance is

A. zero

B.  $6.5\Omega$

C.  $0.7\Omega$

D.  $1\Omega$

**Answer: D**



**Watch Video Solution**

**108.** The potential gradient along the length of a uniform wire is 10 volt / metre. B and C are the two points at 30 cm and 70 cm point on a metre scale fitted along the wire. What is the potential difference between B and C ?

A. 3 V

B. 4 V

C. 5 V

D. 6 V

**Answer: B**



**Watch Video Solution**

**109.** In an experiment to measure the internal resistance of a cell by a potentiometer, it is found that the balance point is at a length of

$2m$  when the cell is shunted by a  $5\Omega$  resistance and is at a length of  $3m$  when the cell is shunted by a  $10\Omega$  resistance, the internal resistance of the cell is then

A.  $5\Omega$

B.  $10\Omega$

C.  $15\Omega$

D.  $7.5\Omega$

**Answer: B**



**Watch Video Solution**

**110.** The resistivity of a potentiometer wire is  $40 \times 10^{-8}$  ohm-m and its area of cross-section is  $8 \times 10^{-6} m^2$ . If a current of 0.4 A is flowing through the wire, then the potential gradient will be

A.  $10^{-2} V / m$

B.  $10^{-1} V / m$

C.  $2 \times 10^{-2} V / m$

D.  $1 V / m$

**Answer: C**



**Watch Video Solution**

**111.** A potentiometer having the potential gradient of  $2mV/cm$  is used to measure the difference of potential across a resistance of  $10\Omega$ . If a length of  $50cm$  of the potentiometer wire is required to get null point, the current passing through the  $10\Omega$  resistor is (in  $mA$ )

A. 1 mA

B. 2 mA

C. 5 mA

D. 10 mA

**Answer: D**



**Watch Video Solution**

**112.** If the length of a potentiometer wire is increased by keeping constant potential difference across the wire, then

- A. the null point is obtained at larger distance
- B. there is no change in the null point
- C. the potential gradient is increased
- D. the null point is obtained at shorter distance

**Answer: A**



**Watch Video Solution**



**113.** Two cells of emfs approximately 5V and 10V are to be accurately compared using a potentiometer of length 400 cm.

A. The battery that runs the potentiometer should have voltage of 8 V

B. The battery of potentiometer can have a voltage of 15 V and R adjusted so that the potential drop across the wire slightly exceeds 10 V

C. The first portion of 50 cm of wire itself should have a potential drop of 10 V

D. Potentiometer is usually used for comparing resistances and not voltages

**Answer: B**



**Watch Video Solution**

**114.** A potentiometer circuit has been setup for finding. The internal resistance of a given cell. The main battery used a negligible internal

resistance. The potentiometer wire itself is  $4m$  long. When the resistance,  $R$ , connected across the given cell, has value of

(i) Infinity  $9.5\Omega$ ,

(ii) the 'balancing length' , on the potentiometer wire are found to be  $3m$  and  $2.85m$ , respectively.

The value of internal resistance of the cell is

A.  $0.5\Omega$

B.  $0.75\Omega$

C.  $0.25\Omega$

D.  $0.95\Omega$

**Answer: A**



**Watch Video Solution**

**115.** Sensitivity of potentiometer can be increased by

A. increasing the length

B. increasing the P.D.

C. decreasing the series resistance

D. increasing the current in the potentiometer wire

**Answer: A**



**Watch Video Solution**

**116.** What is the potential gradient along a wire having an area of cross-section  $4 \times 10^{-4} m^2$ , if the current flowing through the wire is 0.2 A and its specific resistance is  $80 \times 10^{-6} ohm / m$  ?

A.  $0.1V / m$

B.  $0.5V / m$

C.  $0.04V / m$

D.  $0.2V / m$

**Answer: C**



**Watch Video Solution**

**117.** A potentiometer wire has a length of 4 and a resistance of 8 ohm. It is connected in series with a cell of e.m.f. 2 V and internal

resistance 2 ohm. The potential drop per unit length of the wire is

A.  $0.5V / m$

B.  $0.4V / m$

C.  $0.1V / m$

D.  $0.2V / m$

**Answer: B**



**Watch Video Solution**

**118.** A cell in the secondary circuit gives null deflection for 2.5 m length of a potentiometer having 10m length of wire. If the length of the potentiometer wire is increased by 1m without changing the cell in the primary, the position of the null point will be

A. 3.5 m

B. 3 m

C. 2.75 m

D. 2.0 m



**Answer: C**



**Watch Video Solution**

**119.** A potentiometer wire 10 long has a resistance of  $40\Omega$ . It is connected in series with a resistances box and a 2 v storage cell. If the potential gradient along the wire is  $0.01\frac{V}{m}$  the resistance unplugged in the box is

A.  $560\Omega$

B.  $760\Omega$

C.  $960\Omega$

D.  $660\Omega$

**Answer: B**



**Watch Video Solution**

**120.** An electron (charge  $q = 1.6 \times 10^{-19} C$ ) in the potentiometer wire experiences a force of  $2.4 \times 10^{-19} N$ . The length of the potentiometer wire is 6 m. The e.m.f. of the battery connected across the wire is

A. 12 V

B. 9 V

C. 6 V

D. 3 V

**Answer: B**



**Watch Video Solution**

**121.** AB is a potentiometer wire (see the figure).

If the value of R is increased, in which direction

will be the balance point J shift ?




- A. the balance point will shift towards A
- B. the balance point will shift towards B
- C. the balance point will remain at J
- D. the balance may shift towards A or B

**Answer: B**



**View Text Solution**

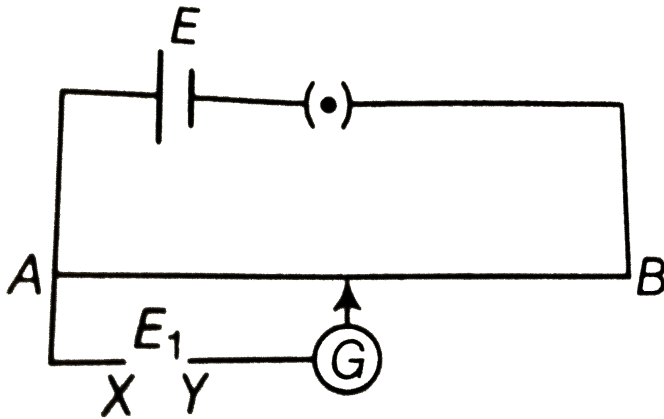

122.

While doing an experiment with potentiometer (figure) it was found that the deflection is one sided and (i) the deflection decreased while moving from one end A of the wire, to the end R, (ii) the deflection increased, while the jockey was moved towards the end D.

(i). Which terminal positive or negative of the cell  $E_1$  is connected at X in case (i) and how is

$E_1$ , related to  $E$ ?

(ii). Which terminal of the cell  $E_1$  is connected at X in case (1 in 1)?

A.  $E > E_1$  and  $+ve$  terminal of  $E_1$  is connected to X

B.  $E < E_1$  and  $-ve$  terminal of  $E_1$  is connected to X

C.  $E > E_1$  and  $-ve$  terminal of  $E_1$  is connected to X

D.  $E < E_1$  and  $+ve$  terminal of  $E_1$  is connected to X

**Answer: B**



**Watch Video Solution**

**123.** A cell balances against a length of 150 cm on a potentiometer wire when it is shunted by a resistance of  $5\Omega$ . But when it is shunted by a resistance of  $10\Omega$ , the balancing length

increases by 25 cm. What is the balancing length when the cell is in an open circuit ?

- A. 200 cm
- B. 210 cm
- C. 225 cm
- D. 250 cm

**Answer: B**



**Watch Video Solution**



**124.** A potentiometer wire has length  $4m$  and resistance  $8\Omega$ . The resistance that must be connected in series with the wire and an accumulator of e.m.f.  $2V$ , so as to get a potential gradient  $1mV$  per cm on the wire is

A.  $40\Omega$

B.  $44\Omega$

C.  $48\Omega$

D.  $32\Omega$

**Answer: D**



Watch Video Solution

**125.** The voltage current variation of two metallic wires X and Y at constant temperature are as shown in figure. Assume that the wires have the same length and same diameter. If  $R_X$  and  $R_Y$  are the resistances of wires X and Y, then



A.  $R_X = R_Y$

B.  $R_X > R_Y$

C.  $R_X < R_Y$

D.  $R_X \geq R_Y$

**Answer: C**



[View Text Solution](#)

**126.** The voltage  $V$  and current  $I$  graph for a conductor at two different temperature  $T_1$  and  $T_2$  is shown in the figure. The relation between  $T_1$  and  $T_2$  is



A.  $T_1 = T_2$

B.  $T_1 \approx T_2$

C.  $T_1 < T_2$

D.  $T_1 > T_2$

**Answer: D**



**View Text Solution**

**127.** Kirchhoffs voltage law and current law are respectively in accordance with the conservation of

A. Charge and momentum

B. Charge and energy

C. Energy and charge

D. Energy and momentum

**Answer: C**



**Watch Video Solution**

**128.** The accuracy of a potentiometer can be easily increased by

- A. increasing the resistance of the wire
- B. decreasing the resistance of the wire
- C. increasing the length of the wire
- D. decreasing the length of the wire

**Answer: C**



**Watch Video Solution**

**129.** Instrument which can measure terminal potential difference as well as electromotive force (e.m.f.) is

A. Wheatstone's metre bridge

B. Voltmeter

C. Potentiometer

D. Galvanometer

**Answer: C**



**Watch Video Solution**

**130.** Kirchhoffs junction law is equivalent to

A. Conservation of energy

B. Conservation of charge

C. Conservation of electric potential

D. Conservation of electric flux

**Answer: B**



**Watch Video Solution**

**131.** Two resistances  $X$  and  $Y$  in the left and right gaps of a metre bridge give a null point dividing the wire in the ratio of  $2:3$ . When each resistance is increased by  $30\Omega$ , the new null



point divides the wire in the ratio of 5 : 6.

What are the values of  $X$  and  $Y$  ?

A.  $X = 20\Omega, Y = 30\Omega$

B.  $X = 30\Omega, Y = 20\Omega$

C.  $X = 10\Omega, Y = 30\Omega$

D.  $X = 30\Omega, Y = 10\Omega$

**Answer: A**



**Watch Video Solution**

**132.** In potentiometer experiment, if  $l_1$  is the balancing length for e.m.f. of the cell of internal resistance  $r$  and  $l_2$  is the balancing length for its terminal potential difference when shunted with resistance  $R$  then :

A.  $l_1 = l_2 \left( \frac{R + r}{R} \right)$

B.  $l_1 = l_2 \left( \frac{R}{R + r} \right)$

C.  $l_1 = l_2 \left( \frac{R}{R - r} \right)$

D.  $l_1 = l_2 \left( \frac{R - r}{R} \right)$

**Answer: A**



Watch Video Solution

**133.** In potentiometer experiment, null point is obtained at a particular point for a cell on potentiometer wire  $x$  cm long. If the length of the potentiometer wire is increased without changing the cell, the balancing length will  
(Driving source is not changed)

- A. increase
- B. decrease
- C. not change

D. becomes zero

**Answer: A**



**Watch Video Solution**

**134.** In balanced meter bridge, the resistance of bridge wire is  $0.1\Omega/cm$  . Unknown resistance X is connected in left gap and  $6\Omega$  in right gap, null point divides the wire in the ratio 2:3 . Find the current drawn the battery of 5V having negligible resistance

A.  $1A$

B.  $1.5A$

C.  $2A$

D.  $5A$

**Answer: A**



**Watch Video Solution**

**135.** Two unknown resistances are connected in two gaps of a meter-bridge. The null point is obtained at 40 cm from left end. A  $30\Omega$

resistance is connected in series with the smaller of the two resistances, the null point shifts by 20 cm to the right end. The value of smaller resistance in  $\Omega$  is

A. 12

B. 24

C. 36

D. 48

**Answer: B**



**Watch Video Solution**

**136.** The resistivity of potentiometer wire is  $40 \times 10^{-8}$  ohm-metre and its area of cross-section is  $8 \times 10^{-6} m^2$ . If 0.2 ampere current is flowing through the wire, the potential gradient of the wire is

A.  $10^{-1} V / m$

B.  $10^{-2} V / m$

C.  $10^{-3} V / m$


D.  $10^{-4} V / m$

**Answer: B**



**Watch Video Solution**

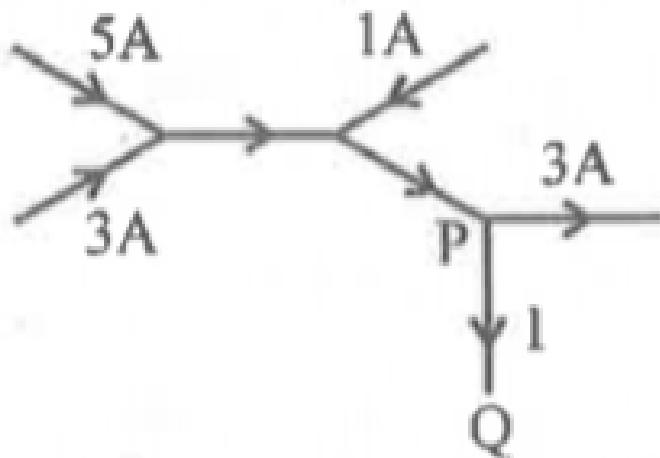**137.** The currents in various parts of an electrical network are as shown in the figure.



The current  $I$  in the branch PQ is



A.  $3A$

B.  $4A$

C.  $5A$

D.  $6A$

**Answer: D**



**Watch Video Solution**

**138.** The current in the arm CD of the circuit will be



A.  $I_1 + I_2$

B.  $I_1 + I_3$

C.  $I_2 + I_3$

D.  $I_1 - I_2 - I_3$

**Answer: C**



**View Text Solution**

**139.** In the section XY of the circuit, a power of 100 Watt is absorbed. What is the resistance

of the device D ?



A.  $10\Omega$

B.  $15\Omega$

C.  $20\Omega$

D.  $25\Omega$

**Answer: C**



**View Text Solution**

**140.** When the switch S is closed in the following circuit, the current passing through the branch BD is



A. 4.5 A

B. 6.0 A

C. 3.0 A


D. Zero

**Answer: A**



**View Text Solution**

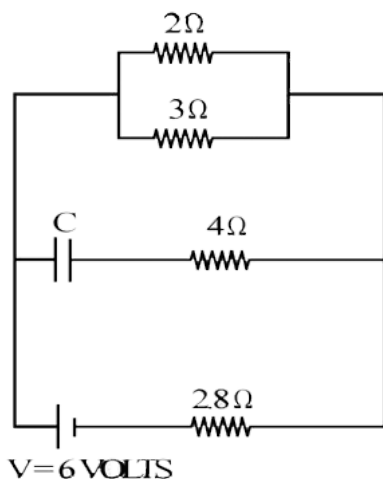**141.** Calculate the steady state current in the 2-ohm resistor shown in the circuit in the figure. The internal resistance of the battery is negligible and the capacitance of the condenser C is 0.2 microfarad.



A. 0.6A

B. 0.7A

C. 0.8A

D. 0.9A

**Answer: D**



**Watch Video Solution**

**142.** With resistances  $P$  and  $Q$  in the left and right gaps of a metre bridge respectively, the null point divides the wire in the ratio  $1 : 2$ . If  $P$

and  $Q$  are increased by  $20\Omega$  each, the null point divides the wire in the ratio  $3 : 4$ , then the resistances  $P$  and  $Q$  are given as :

A.  $P = 10\Omega, Q = 10\Omega$

B.  $P = 10\Omega, Q = 20\Omega$

C.  $P = 40\Omega, Q = 10\Omega$

D.  $P = 20\Omega, Q = 40\Omega$

**Answer: B**



**Watch Video Solution**

143. In the given circuit, no current flows in the  $2\Omega$  resistance.



The equivalent resistance of the given circuit is

A.  $\frac{30}{15}\Omega$

B.  $10\Omega$


C.  $\frac{20}{5}\Omega$

D.  $1\Omega$

**Answer: B**



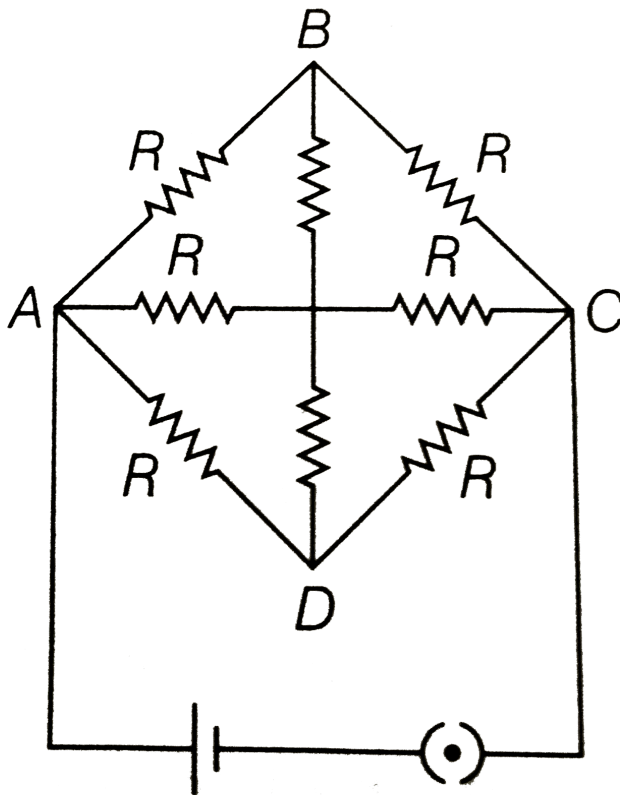144. What is the effective resistance between the points A and C in the following network?



A.  $\frac{R}{3}$

B.  $\frac{2R}{3}$

C.  $\frac{3R}{2}$

D.  $\frac{R}{2}$

**Answer: B**



**Watch Video Solution**

**145.** In the given circuit it is observed that the current  $I$  is independent of the value of the resistance  $R_6$ . Then the resistance values must

satisfy



A.  $R_1 R_4 = R_2 R_3$

B.  $R_1 R_3 = R_2 R_4 = R_5 R_6$

C.  $R_1 R_2 R_5 = R_3 R_4 R_6$

D.  $\frac{1}{R_5} + \frac{1}{R_6} = \frac{1}{R_1 + R_2} + \frac{1}{R_3 + R_4}$

**Answer: A**



**View Text Solution**

**146.** A resistance  $R$  is to be measured using a meter bridge. Student chooses the standard resistance  $S$  to be  $100\Omega$ . He finds the null point at  $l_1 = 2.9\text{cm}$ . He is told to attempt to improve the accuracy. Which of the following is a useful way?

A. He should measure  $L_1$  more accurately

B. He should change  $S$  to  $1000\Omega$  and repeat the experiment

C. He should change  $S$  to  $3\Omega$  and repeat the experiment

D. He should give up hope of a more accurate measurement with a metre bridge

**Answer: C**



**Watch Video Solution**

147. For a cell of e.m.f.  $2\text{ V}$  , a balance is obtained for  $50\text{ cm}$  of the potentiometer wire. If the cell is shunted by a  $2\Omega$  resistor and the balance is obtained across  $40\text{ cm}$  of the wire, then the internal resistance of the cell is

A.  $0.25\Omega$

B.  $0.5\Omega$

C.  $0.75\Omega$

D.  $1.00\Omega$

**Answer: B**



Watch Video Solution

**148.** A current of 0.01 A flows through a potentiometer wire of cross section area  $10^{-6}m^2$ . If the specific resistance of the potentiometer wire is  $10^{-7}$  ohm-m, then the potential gradient will be

A.  $10^{-1}V/m$

B.  $10^{-3}V/m$

C.  $10^{-2}V/m$

$$D. 0.5 \times 10^{-2} V / m$$

**Answer: B**



**Watch Video Solution**

**149.** With a certain cell, the balance point is obtained at 65 cm from the zero end of a potentiometer wire. With another cell, whose e.m.f. is less than that of the first by 0.1 V, the balance point is obtained at 60 cm. What is the e.m.f. of the first cell ?



A.  $1.0V$

B.  $1.2 V$

C.  $1.3 V$

D.  $1.5 V$

**Answer: C**



**Watch Video Solution**

**150.** A P.D. of 2 volts exists across a potentiometer wire of length 4 m. When the P.D. across a  $2\Omega$  resistance of a second circuit

is measured by this potentiometer, the balancing length is found to be 4 cm, the current in the second circuit is

A. 1 mA

B. 10 mA

C. 100 mA

D. 50 mA

**Answer: B**



**Watch Video Solution**

**151.** The length of a potentiometer wire is 200 cm and the e.m.f. of the battery connected to it is  $E$ . It is used to measure the e.m.f. of a cell whose internal resistance is  $0.5\Omega$ . If the balance point is obtained at  $l=40$  cm from the positive end, then the e.m.f. of the cell is

A.  $\frac{40E}{200}$

B.  $\frac{40E}{200 + 0.5}$

C.  $\frac{40(E - 0.5)}{200}$

D.  $\frac{40E}{200 - 0.5}$

**Answer: A**



**Watch Video Solution**