



# PHYSICS

## BOOKS - TARGET PHYSICS (HINGLISH)

### CURRENT ELECTRICITY

#### Classical Thinking

1. According to the Kirchoff's laws in an electric circuit, the algebraic sum of current at any junction is

A. negligible

B. zero

C. infinite

D. finite

**Answer:**



**Watch Video Solution**

2. According to Kirchhoff's law, the algebraic sum of products of current and resistance as well as e.m.f.s in a closed loop is

A. greater than zero

B. zero

C. less than zero

D. determined by the e.m.f.

**Answer:**



**Watch Video Solution**

**3.** In a closed circuit, the vector sum of total e.m.f.s is equal to the sum of the

A. currents.

B. resistances.

C. products of current and the resistances.

D. internal resistance of cell.

**Answer:**



**Watch Video Solution**

**4. What determines the conventional direction of the product of current and resistance while applying the Kirchhoff's law ?**

A. Magnitude of current

B. Value of resistance

C. Direction of current

D. Value of P.D.

**Answer:**



**Watch Video Solution**

**5.** On sending the current in the Wheatstone's network, the network is said to be balanced, if

A. there is no deflection in the galvanometer.

B. there is a full deflection in the galvanometer.

C. there is partial deflection in the galvanometer.

D. there is zero P.D. between two ends.

**Answer:**



**Watch Video Solution**

6. Wheatstone bridge is most sensitive when the resistance of all four arms are

A. different order.

B. same order.

C. partially different order.

D. no connection with the order.

**Answer:**



**Watch Video Solution**

7. Which of the following instruments is generally used with a galvanometer to show null reading ?

A. Ammeter

B. Potentiometer

C. Voltmeter

D. Metrebridge

**Answer:**



**Watch Video Solution**



8. Accuracy of a metrebridge is maximum when the null point is obtained at the midpoint of the bridge wire. This is because

A. the error due to non uniformity of diameter of the wire is minimum in that case.

B. the error due to the end resistances is minimum.

C. the error due to heating up of wire is minimum.

D. the error due to faulty galvanometer is minimum.

**Answer:**



**Watch Video Solution**

9. In Kelvin's method of finding the resistance of a galvanometer, we

A. use the balance point method.

B. use the null point method.

C. use the half deflection method.

D. interchange the positions of the battery  
and the galvanometer.

**Answer:**



**Watch Video Solution**

**10.** A metrebridge cannot be used to  
determine

A. resistance of a wire.

B. Specific resistance.

C. conductivity.

D. e.m.f of a cell.

**Answer:**



**Watch Video Solution**

**11. Select the WRONG statement.**

A. A potentiometer is a constant voltage device.

B. A potentiometer is a constant current device.

C. A potentiometer is used to measure e.m.f. of a cell.

D. A potentiometer is used to measure potential drop between two points in an electric circuit.

**Answer:**



**Watch Video Solution**

12. Slide wire bridge does not operate on the same principle as the

- A. Wheatstone bridge
- B. Potentiometer
- C. post office box arrangement
- D. metrebridge

**Answer:**



**Watch Video Solution**

13. Which of the following can cause the null point of a potentiometer to shift beyond the wire ?

A. Low e.m.f. of auxiliary battery.

B. High e.m.f. of auxiliary battery.

C. Shorter length of wire.

D. Longer length of wire.

**Answer:**



**Watch Video Solution**

14. In potentiometer experiment, when the galvanometer shows no deflection, then no current flows in

- A. potentiometer wire
- B. galvanometer circuit
- C. main circuit
- D. battery

**Answer:**



**Watch Video Solution**



15. Potentiometer is better for measuring the potential difference than the voltmeter because

A. it uses a long wire.

B. it uses an auxiliary battery of large e.m.f.

C. it does not disturb the potential difference to be measured.

D. it is based on the principle of Wheatstone bridge.

**Answer:**



**Watch Video Solution**

**16.** In potentiometer experiment to determine internal resistance of the cell, balance point has been obtained in fourth wire. It can be shifted to 5<sup>th</sup> wire by

A. decreasing the current through potentiometer wire.

B. increasing the current through potentiometer wire.

C. connecting suitable shunt resistance across the cell.

D. connecting a resistance in series with the cell.

**Answer:**



**Watch Video Solution**

17. The potential gradient along the length of uniform wire is  $10 \text{ Vm}^{-1}$ . The length of the wire is 1 m. What is the potential difference across two points on the wire separated by 25 cm?

A.  $2.5 \text{ V}$

B.  $5.0 \text{ V}$

C.  $7.5 \text{ V}$

D.  $10 \text{ V}$

**Answer:**



Watch Video Solution

18. In a potentiometer experiment the balancing with a cell is at length 240 cm. On shunting the cell with a resistance of  $2\Omega$ , the balancing length becomes 120 cm. The internal resistance of the cell is

A.  $4\Omega$

B.  $2\Omega$

C.  $1\Omega$

D.  $0.5\Omega$

**Answer:**



**Watch Video Solution**

**19.** In a metrebridge, copper strips are used to

- A. decrease contact resistance.
- B. to reduce thermoelectric effect.
- C. to increase grip of wire.
- D. none of these.

**Answer:**



**Watch Video Solution**

20. In potentiometer experiment, a cell is balanced by length 120 cm. When a cell is shunted by resistance of  $5\Omega$ , the balancing length is 80 cm. The internal resistance of cell is

A.  $2.5\Omega$

B.  $3\Omega$

C.  $4\Omega$

D.  $5\Omega$

**Answer:**



**Watch Video Solution**

**21.** A  $2.0\text{ V}$  potentiometer is used to determine the internal resistance of  $1.5\text{ V}$  cell. The balance point of the cell in the circuit is  $75\text{ cm}$ . When a resistor of  $10\Omega$  is connected across



cel, the balance point sifts to  $60\text{cm}$ . The internal resistance of the cell is

A.  $1.5\Omega$

B.  $2.5\Omega$

C.  $3.5\Omega$

D.  $4.5\Omega$

**Answer:**



**Watch Video Solution**

**22. Assertion:** We prefer a potentiometer with a longer bridge wire.

**Reason :** By doing this, the sensitivity of the bridge is increased because for longer wire potential drop per unit length will be small.

A. Assertion is True, Reason is True, Reason is a correct explanation for Assertion

B. Assertion is True, Reason is True, Reason is not a correct explanation for Assertion

C. Assertion is True, Reason is False

D. Assertion is False but Reason is True.

**Answer:**



**Watch Video Solution**

**23.** Assertion : The e.m.f. of the driver cell in the potentiometer experiment should be greater than the e.m.f. of the cell to be determined.

A. Assertion is True, Reason is True,

Reason is a correct explanation for

## Assertion

- B. Assertion is True, Reason is True, Reason is not a correct explanation for Assertion
- C. Assertion is True, Reason is False
- D. Assertion is False but Reason is True.

**Answer:**



**Watch Video Solution**

**Critical Thinking**

1. A  $50V$  battery is connected across a  $10\ \text{ohm}$  resistor. The current is  $4.5$  amperes. The internal resistance of the battery is

A.  $10\Omega$

B.  $0.5\Omega$

C.  $1.1\Omega$

D.  $5\Omega$

**Answer:**



**Watch Video Solution**

2. Four resistors P, Q, R and S having resistances  $3\Omega$ ,  $3\Omega$ ,  $4\Omega$  and  $6\Omega$  respectively, are arranged to form a Wheatstone's bridge. The value of the resistance with which S must be shunted in order to balance the bridge is

A.  $12\Omega$

B.  $3\Omega$

C.  $4\Omega$

D.  $16\Omega$

**Answer:**



Watch Video Solution

3. At which point will the null point be obtained on a metrebridge if the ratio of the resistances in the two gaps is 2 : 3 ?

A. 25 cm

B. 30 cm

C. 40 cm

D. 60 cm

**Answer:**



Watch Video Solution

4. In a meter-bridge experiment with a resistance  $R_1$  in left gap and a resistance  $X$  in a right gap. null point is obtained at  $40\text{cm}$  from the left emf. With a resistance  $R_2$  in the left gap, the null point is obtained at  $50\text{cm}$  from left hand. Find the position of the left gap is containing  $R_1$  and  $R_2$  (i) in series and (ii) in parallel.

A. 25.6 cm from left



B. 68.4 cm from left

C. 31.6 cm from left

D. 74.4 cm from left

**Answer:**



**Watch Video Solution**

5. Two resistances are connected in the two gaps of a meter bridge. The balance point is  $20\text{cm}$  from the zero end. When a resistance  $15\Omega$  is connected in series with the smaller of

two resistance, the null point+ shifts to  $40\text{cm}$ .

The smaller of the two resistance has the value.

A.  $8\Omega$

B.  $9\Omega$

C.  $10\Omega$

D.  $12\Omega$

**Answer:**



**Watch Video Solution**

6. The material of wire of potentiometer is

A. copper

B. steel

C. manganin

D. aluminium

**Answer:**



**Watch Video Solution**

7. A potentiometer wire is 10 m long and has a resistance of  $2\Omega/\text{m}$ . It is connected in series with a battery of e.m.f. 3 V and a resistance of  $10\Omega$ . The potential gradient along the wire in V/m is

A. 0.01

B. 0.02

C. 0.1

D. 0.2

**Answer:**



Watch Video Solution

8. A potentiometer wire has a resistivity of  $10^9 \Omega \text{ cm}$  and area of cross-section is  $10^{-2} \text{ cm}^2$ . If current of  $0.01 \text{ mA}$  passes through the wire, potential gradient is

A.  $10^9 \text{ V / m}$

B.  $10^{10} \text{ V / m}$

C.  $10^{11} \text{ V / m}$

D.  $10^8 \text{ V / m}$

**Answer:**



**Watch Video Solution**

9. A battery of e.m.f. 2 V and internal resistance  $2\Omega$  is connected to an external resistance  $8\Omega$ . If the length of the conductor is 4 m, then potential gradient between the two ends of the wire is

A.  $0.4 \text{ V/m}$

B.  $8 \text{ V/m}$

C. 4 V/m

D. 2 V/m

**Answer:**



**Watch Video Solution**

**10.** A resistance of  $990\Omega$  and a cell of emf 2 V is connected in series with a potentiometer wire having a length 2 m and resistance  $10\Omega$ . The potential gradient along the wire will be

A.  $0.01 \text{ V/m}$

B.  $0.02 \text{ V/m}$

C.  $0.03 \text{ V/m}$

D.  $0.04 \text{ V/m}$

**Answer:**



**Watch Video Solution**

**11.** An accumulator of 5 volt is connected through a resistance of  $40\Omega$  to a potentiometer wire 10 m long and of



resistance  $10\Omega$ . For a cell, the null point is found at a length of 8 m from the common terminal. The current through the wire is

A. 0.05 A

B. 0.1 A

C. 0.15 A

D. 0.2

**Answer:**



**Watch Video Solution**

12. The resistance per unit length of a wire is  $1\Omega/\text{m}$ . A Leclanche cell of e.m.f. 1.45 V is balanced against 2.9 m length of potentiometer wire. The current through the wire is

A. 1 A

B. 2 A

C. 0.5 A

D. 0.1 A

**Answer:**



**13.** The e.m.f.  $E$  of the battery is balanced by p.d. across 75 cm of a potentiometer wire. For a standard cell of e.m.f. 1.02 V, the balancing length is 50 cm. The value of  $E$  is

A. 0.68 V

B. 1.24 V

C. 1.53 V

D. 1.08 V

**Answer:**



**Watch Video Solution**

14. A potentiometer having a wire of length 10 m and resistance  $20\Omega$  is connected to an accumulator of e.m.f.  $E$  through a resistance box. When the resistance in the box is  $20\Omega$ , a null point is observed at 5 m for a cell of e.m.f.  $E_1$ . The ratio of  $E$  to  $E_1$  is

A.  $1/4$

B. 2/1

C. 3/1

D. 4/1

**Answer:**



**Watch Video Solution**

**15.** When two cells of e.m.f. 1.5 V and 1.1 V connected in series are balanced on a potentiometer, the balancing length is 260 cm.

The balancing length, when they are connected in opposition is (in cm)

A. 100

B. 110

C. 40

D. 65

**Answer:**



**Watch Video Solution**

**16.** When a balance point is obtained in a potentiometer for finding the internal resistance of a cell, the current through the potentiometer wire is due to

- A. the cell whose internal resistance is to be found.
- B. the auxiliary battery.
- C. both cell and auxiliary battery.
- D. neither cell nor the battery.

**Answer:**



**Watch Video Solution**

17. With resistances  $P$  and  $Q$  in the left and right gaps of a metre bridge, the balance point divides the wire in the ratio  $1/3$ . When  $P$  and  $Q$  are increased by  $40\Omega$ , the balance point divides the wire in the ratio  $3/5$ . The values of  $P$  and  $Q$  will be respectively

A.  $30\Omega$ ,  $10\Omega$



B.  $10\Omega$ ,  $30\Omega$

C.  $20\Omega$ ,  $60\Omega$

D.  $60\Omega$ ,  $40\Omega$

**Answer: C**



**Watch Video Solution**

**18.** A cell of e.m.f. 2 V and negligible internal resistance is connected in series with a potentiometer wire of length 100 cm. The e.m.f of the Leclanche cell is found to balance on 75

cm of the potentiometer wire. The e.m.f. of the cell is

A. 3.5 V

B. 2.5 V

C. 1.5 V

D. 0.5 V

**Answer:**



**Watch Video Solution**

19. An accumulator of 4 V is connected through a resistance of  $30\Omega$  to a potentiometer wire 10 m long and resistance  $30\Omega$ . When a cell is connected through a galvanometer to the potentiometer the null point is found at 5.5 m from the common terminal. The potential gradient in the wire is

A.  $\frac{1}{15} \text{ V/m}$

B.  $\frac{1}{10} \text{ V/m}$

C.  $\frac{1}{5} \text{ V/m}$

D.  $\frac{1}{3} \text{V/m}$

**Answer:**



**Watch Video Solution**

**20.** A potentiometer has uniform potential gradient. The specific resistance of the material of the potentiometer wire is  $10^{-7}$  ohm-metre and the current passing through it is 0.1 ampere, cross-section of the wire is

$10^{-6} \text{ m}^2$ . The potential gradient along the potentiometer wire is

A.  $10^{-4} \text{ V/m}$

B.  $10^{-6} \text{ V/m}$

C.  $10^{-2} \text{ V/m}$

D.  $10^{-8} \text{ V/m}$

**Answer:**



**Watch Video Solution**

21. In a potentiometer experiment, when three cells A, B and C are connected in series, the balancing length is found to be 740 cm. If A and B are connected in series, balancing length is 440 cm and for B and C connected in series, it is 540 cm. The emf of  $E_A$ ,  $E_B$  and  $E_C$  are respectively (in volts)

A. 1, 1.2 and 1.5

B. 1, 2, and 3

C. 1.5, 2 and 3

D. 1.5, 2.5 and 3.5

**Answer:**



**Watch Video Solution**

22. Potentiometer wire of length  $1m$  is connected in series with  $490\Omega$  resistance and  $2V$  battery. If  $0.2m\frac{V}{c}m$  is the potential gradient, then resistance of the potentiometer wire is approximately

A.  $4.9\Omega$

B.  $7.9\Omega$

C.  $5.9\Omega$

D.  $6.9\Omega$

**Answer:**



**Watch Video Solution**

**23.** Assertion: In a metrebridge, length of the wire is 1 metre.

Reason: Greater the length of wire, better is the accuracy.



- A. Assertion is True, Reason is True, Reason is a correct explanation for Assertion
- B. Assertion is True, Reason is True, Reason is not a correct explanation for Assertion
- C. Assertion is True, Reason is False
- D. Assertion is False but Reason is True.

**Answer:**



**Watch Video Solution**

**24.** Assertion: A slide wire bridge is also called a metrebridge.

Reason: It is because, the length of wire in a slide wire bridge is one metre.

A. Assertion is True, Reason is True, Reason

is a correct explanation for Assertion

B. Assertion is True, Reason is True, Reason

is not a correct explanation for Assertion

C. Assertion is True, Reason is False

D. Assertion is False Reason is True.

**Answer:**



**Watch Video Solution**

## Competitive Thinking

1. Kirchhoff's current law is the law of conservation of

A. energy

B. momentum

C. charge


## D. angular momentum

**Answer:**



**Watch Video Solution**

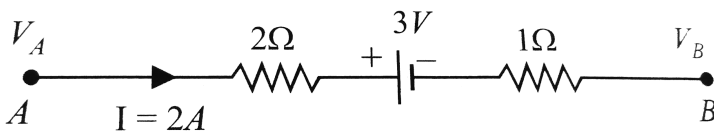2. The potential difference ( $V_A - V_B$ ) between the point  $A$  and  $B$  in the given figure is



A.  $+9V$

B.  $-3V$

C.  $+3V$

D.  $+6V$

**Answer:**



**Watch Video Solution**

**3.** In meter bridge of Wheatstone bridge for measurement of resistance, the known and the unknown resistance are interchanged. The error so removed is

A. minor error

B. observational error

C. error due to thermoelectric effect

D. connection error

**Answer:**



**Watch Video Solution**

4. In a Wheatstone's bridge, three resistances P, Q and R connected in the three arms and the fourth arm is formed by two resistances

$S_1$  and  $S_2$  connected in parallel. The condition for the bridge to be balanced will be

A.  $\frac{R(S_1 + S_2)}{S_1 S_2}$

B.  $\frac{S_1 S_2}{R(S_1 + S_2)}$

C.  $\frac{RS_1 S_2}{(S_1 + S_2)}$

D.  $\frac{(S_1 + S_2)}{RS_1 S_2}$

**Answer:**



**Watch Video Solution**

5. Four resistances arranged to form a Wheatstone network are  $8\Omega$ ,  $12\Omega$ ,  $6\Omega$  and  $27\Omega$  resistance, so that the bridge is balanced, is

A.  $13.5\Omega$

B.  $14.5\Omega$

C.  $13\Omega$


D.  $14\Omega$

**Answer:**



**Watch Video Solution**



6. In a Wheatstone's network,  $P = 2\Omega$ ,  $Q = 2\Omega$ ,  $R = 2\Omega$  and  $S = 3\Omega$ . The resistance with which  $S$  is to be shunted in order that the bridge may be balanced is 

A.  $4\Omega$

B.  $1\Omega$

C.  $6\Omega$

D.  $2\Omega$

**Answer:**



**Watch Video Solution**

7. In Wheatstone bridge, the resistances in four arms are  $10\Omega$ ,  $10\Omega$ ,  $10\Omega$  and  $20\Omega$ . To make the bridge balance, resistance connected across  $20\Omega$  is

A.  $10\Omega$

B.  $5\Omega$

C.  $20\Omega$

D.  $40\Omega$

**Answer:**



**Watch Video Solution**

8. A uniform wire of  $16\Omega$  is made into the form of a square. Two opposite corners of the square are connected by a wire of resistance  $16\Omega$ . The effective resistance between the other two opposite corners is

A.  $32\Omega$

B.  $20\Omega$

C.  $8\Omega$

D.  $4\Omega$

**Answer:**



**Watch Video Solution**

9. In an experiment of meter bridge, a null point is obtaining at the center of the bridge wire. When a resistance of  $10\text{ohm}$  is connected in one gap, the value of resistance other gap is

A.  $10\Omega$

B.  $5\Omega$

C.  $1/5\Omega$

D.  $500\Omega$

**Answer:**



**Watch Video Solution**

**10. v20.1**

A.  $10\Omega$

B.  $20\Omega$

C.  $40\Omega$

D. None of the above three values

**Answer:**



**Watch Video Solution**

**11.** Four resistors,  $100\Omega$ ,  $200\Omega$ ,  $300\Omega$ , and  $400\Omega$  are connected to form four sides of a square. The resistors can be connected in any order.

What is the maximum possible equivalent resistance across the diagonal of the square?

A.  $210\Omega$

B.  $240\Omega$

C.  $300\Omega$

D.  $250\Omega$

**Answer:**



**Watch Video Solution**

12. In meter bridge , the balancing length from left is found to be 20 cm when standard connected of  $1\Omega$  is in right gap . The value of unknown resistance is

A.  $0.8\Omega$

B.  $0.5\Omega$

C.  $0.4\Omega$

D.  $0.25\Omega$

**Answer:**



Watch Video Solution



13. In metre bridge experiment, with a standard resistance in the right gap and a resistance coil dipped in water (in a beaker) in the left gap, the balancing length obtained is '1'. If the temperature of water is increased, the new balancing

A.  $< 1$

B.  $> 1$

C.  $= 0$

$$D. = 1$$

**Answer:**



**Watch Video Solution**

**14.** Resistance in the two gaps of a meter bridge are  $10\text{ohm}$  and  $30\text{ohm}$  respectively. If the resistances are interchanged the balance point shifts by

**A. 33.3**

B. 66.67

C. 25

D. 50

**Answer:**



**Watch Video Solution**

**15.** The resistances in left and right gap of a meter bridge are  $20 \omega$  and  $30 \omega$  respectively when the resistance in the left gap is reduced to half its value then balance point shifts by

A. 15 cm to the right.

B. 15 cm to the left.

C. 20 cm to the right.

D. 20 cm to the left.

**Answer:**



**Watch Video Solution**

**16.** An unknown resistance  $R_1$  is connected in series with a resistance of  $10\Omega$ . This combination is connected to one gap of a

meter bridge, while other gap is connected to another resistance  $R_2$ . The balance point is at  $50\text{cm}$  Now , when the  $10\Omega$  resistance is removed, the balanced point shifts to  $40\text{cm}$  Then the value of  $R_1$  is.

A. 60

B. 40

C. 20

D. 10

**Answer:**



17. Two unknown resistances are connected in two gaps of a meter-bridge. The null point is obtained at 40 cm from left end. A  $30\Omega$  resistance is connected in series with the smaller of the two resistances, the null point shifts by 20 cm to the right end. The value of smaller resistance in  $\Omega$  is

A. 12

B. 24

C. 36

D. 48

**Answer:**



**Watch Video Solution**

**18.** In a meter bridge experiment null point is obtained at 20 cm. from one end of the wire when resistance  $X$  is balanced against another resistance  $Y$ . If  $X < Y$ , then where will be the new position of the null point from the same

end, if one decides to balance a resistance of 4  
X against Y

A. 50 cm

B. 80 cm

C. 40 cm

D. 70 cm

**Answer:**



**Watch Video Solution**



**19.** In a metre bridge experiment, when a nichrome wire is in the right gap, the balancing length is 60 cm. When the nichrome wire is uniformly stretched to increase its length by 20% and again connected in the right gap balancing length is nearly

A. 61 cm

B. 31 cm

C. 51 cm

D. 41 cm

**Answer:**



**Watch Video Solution**

20. On interchanging the resistances, the balance point of a meter bridge shifts to the left by 10 cm. The resistance of their series combination is  $1k\Omega$ . How much was the resistance on the left slot before interchanging the resistances ?

A.  $550\Omega$

B.  $910\Omega$

C.  $990\Omega$

D.  $505\Omega$

**Answer:**



**Watch Video Solution**

21. In balanced meter bridge, the resistance of bridge wire is  $0.1\Omega/cm$ . Unknown resistance  $X$  is connected in left gap and  $6\Omega$  in right gap, null point divides the wire in the ratio 2:3.

Find the current drawn the battery of 5V  
having negligible resistance

A. 1 A

B. 1.5 A

C. 2 A

D. 5 A

**Answer:**



**Watch Video Solution**

22. A potentiometer is an accurate and versatile device to make electrical measurements of  $E.M.F.$  because the method involves

A. cells.

B. potential gradients.

C. a condition of no current flow through the galvanometer.

D. a combination of cells, galvanometer and resistances.

**Answer:**



**Watch Video Solution**

**23.** In potentiometer experiment, null point is obtained at a particular point for a cell on potentiometer wire  $x$  cm long. If the length of the potentiometer wire is increased without changing the cell, the balancing length will (Driving source is not changed)

A. increase

B. decrease

C. not change

D. becomes zero

**Answer:**



**Watch Video Solution**

**24.** A potentiometer consists of a wire of length 4 m and resistance  $10\Omega$ . If is connected of cell of emf  $2V$ . The potential difference per unit length of the wire will be

A.  $0.5 \text{ V/m}$

B.  $10 \text{ V/m}$

C.  $2 \text{ V/m}$

D.  $5 \text{ V/m}$

**Answer:**



**Watch Video Solution**

**25.** A potentiometer wire of length 10 m is connected in series with a battery the emf of a cell balances against 250 cm length of wire if



length of potentiometer wire is increased by 1 m then new balancing length of wire will be

A. 2.00 m

B. 2.25 m

C. 2.50 m

D. 2.75 m

**Answer:**



**Watch Video Solution**

26. A 2 volt battery, a  $15\Omega$  resistor and a potentiometer of  $100\text{cm}$  length, all are connected in series. If the resistance of potentiometer wire is  $5\Omega$ , then the potential gradient of the potentiometer wire is

A.  $0.005 \text{ V/cm}$

B.  $0.05\text{V/cm}$

C.  $0.02 \text{ V/cm}$

D.  $0.2 \text{ V/cm}$

**Answer:**



**Watch Video Solution**

27. The resistivity of a potentiometer wire is  $40 \times 10^{-8} \Omega - m$  and its area of cross section is  $8 \times 10^{-6} m^2$ . If 0.2 A current is flowing through the wire the potential gradient will be

A.  $10^{-1} \text{ V/m}$

B.  $10^{-2} \text{ V/m}$

C.  $10^{-3} \text{ V/m}$

D.  $10^{-4} \text{ V/m}$

**Answer:**



**Watch Video Solution**

**28.** A potentiometer wire has length  $4m$  and resistance  $8\Omega$ . The resistance that must be connected in series with the wire and an accumulator of e.m.f.  $2V$ , so as to get a potential gradient  $1mV$  per cm on the wire is

A.  $32\Omega$

B.  $40\Omega$

C.  $57\Omega$

D.  $35\Omega$

**Answer:**



**Watch Video Solution**

**29.** A wire of length 100 cm is connected to a cell of emf 2 V and negligible internal resistance. The resistance of the wire is  $3\Omega$ .

The additional resistance required to produce a potential drop of 1 milli volt per cm is

A.  $60\Omega$

B.  $47\Omega$

C.  $57\Omega$

D.  $35\Omega$

**Answer:**



**Watch Video Solution**

30. A potentiometer wire of length 1m and resistance  $10\Omega$  is connected in series with a cell of emf 2V with internal resistance  $1\Omega$  and a resistance box including a resistance R. If potential difference between the ends of the wire is 1 mV, the value of R is

A.  $20000\Omega$

B.  $19989\Omega$

C.  $10000\Omega$

D.  $9989\Omega$

**Answer:**



**Watch Video Solution**

**31.** Two cells with the same emf  $E$  and different internal resistances  $r_1$  and  $r_2$  are connected in series to an external resistance  $R$ . The value of  $R$  so that the potential difference across the first cell be zero is

A.  $R = 2(r_1 + r_2)$

B.  $R = r_2 - r_1$



$$C. R = r_1 - r_2$$

$$D. R = 2(r_1 - r_2)$$

**Answer:**



**Watch Video Solution**

**32.** A set of ' $n$ ' equal resistor, of value of ' $R$ ' each are connected in series to a battery of emf ' $E$ ' and internal resistance ' $R$ '. The current drawn is  $I$ . Now, the ' $n$ ' resistors are connected in parallel to the same battery.

Then the current drawn from battery becomes

10.1. The value of ' $n$ ' is

A. 10

B. 11

C. 20

D. 9

**Answer:**



**Watch Video Solution**

**33.** A potentiometer circuit has been setup for finding the internal resistance of a given cell. The main battery used has a negligible internal resistance. The potentiometer wire itself is  $4m$  long. When the resistance,  $R$ , connected across the given cell, has a value of

(i)  $9.5\Omega$ ,

(ii) the 'balancing length' on the potentiometer wire are found to be  $3m$  and  $2.85m$ , respectively.

The value of internal resistance of the cell is

A.  $0.25\Omega$

B.  $0.95\Omega$

C.  $0.5\Omega$

D.  $0.75\Omega$

**Answer:**



**Watch Video Solution**

**34.** A Daniel cell is balanced on  $125\text{cm}$  length of a potentiometer wire. Now the cells is short-circuited by a resistance  $2\text{ohm}$  and the

balance is obtained at  $100\text{cm}$ . The internal resistance of the Dainel cell is

A.  $0.5\ \text{ohm}$

B.  $1.5\ \text{ohm}$

C.  $1.25\ \text{ohm}$

D.  $4/5\ \text{ohm}$

**Answer:**



**Watch Video Solution**

**35.** In a potentiometer experiment it is found that no current passes through the galvanometer when the terminals of the cell are connected across  $0.52m$  of the potentiometer wire. If the cell is shunted by a resistance of  $5\Omega$  balance is obtained when the cell connected across  $0.4m$  of the wire. Find the internal resistance of the cell.

A.  $2\Omega$

B.  $2.5\Omega$

C.  $1\Omega$

D.  $1.5\Omega$

**Answer:**



**Watch Video Solution**

**36.** In potentiometer experiment, a cell of emf  $1.25V$  gives balancing length of 30 cm. If the cell is replaced by another cell, then balancing length is found to be 40 cm. What is the emf of second cell ?

A. = 1.57 V

$$B. = 1.67 \text{ V}$$

$$C. = 1.47 \text{ V}$$

$$D. = 1.37 \text{ V}$$

**Answer:**



**Watch Video Solution**

**37.** In a potentiometer experiment two cells of e.m.f.  $E$  and  $E$  are used in series and in conjunction and the balancing length is found to be 58 cm of the wire. If the polarity of  $E$  is



reversed, then the balancing length becomes 29 cm . The ratio  $\frac{E_1}{E_2}$  of the e.m.f. of the two cells is

A. 1 : 1

B. 2 : 1

C. 3 : 1

D. 4 : 1

**Answer:**



**Watch Video Solution**

**38.** A potentiometer has uniform potential gradient across it. Two cells connected in series (i) to support each other and (ii) to oppose each other are balanced over 6 m and 2 m respectively on the potentiometer wire. The e.m.f.'s of the cells are in the ratio of

A. 1 : 2

B. 1 : 1

C. 3 : 1

D. 2 : 1

**Answer:**



**Watch Video Solution**

**39.** A potentiometer wire is  $100\text{cm}$  long and a constant potential difference is maintained across it. Two cells are connected in series first to support one another and then in opposite direction. The balance points are obtained at  $50\text{cm}$  and  $10\text{cm}$  from the positive end of the wire in the two cases. The ratio of emfs is:

A. 3:4

B. 3:2

C. 5:1

D. 5:4

**Answer:**



**Watch Video Solution**

**40.** A potentiometer wire of Length  $L$  and a resistance  $r$  are connected in series with a battery of e.m.f.  $E_0$  and a resistance  $r_1$ . An

unknown e.m.f.  $E$  is balanced at a length  $l$  of the potentiometer wire. The e.m.f.  $E$  will be given by :

A.  $\frac{LE_0r}{(r + r_1)l}$

B.  $\frac{LE_0r}{lr_1}q$

C.  $\frac{E_0r}{(r + r_1)} \frac{l}{L}$

D.  $\frac{E_0l}{L}$

**Answer:**



**Watch Video Solution**

41. A conducting wire has length  $L_1$  and diameter  $d_1$ . After stretching the same wire length becomes  $L_2$  and diameter  $d_2$ , The ratio of resistances before and after stretching is

A.  $d_2^4 : d_1^4$

B.  $d_1^4 : d_2^4$

C.  $d_2^2 : d_1^2$

D.  $d_1^2 : d_2^2$

**Answer:**



**Watch Video Solution**

**42.** Which of the following statements is false ?

A. A rheostat can be used as a potential divider.

B. Kirchhoff's second law represents energy conservation.

C. Wheatstone bridge is the most sensitive when all the four resistances are of the same order of magnitude.

D. In a balanced Wheatstone bridge if the cell and the galvanometer are exchanged, the null point is disturbed.

**Answer: D**



**Watch Video Solution**

**43.** You are given 10 resistors each of resistance  $2\Omega$ . First they are connected to obtain possible minimum resistance. Then they are connected to obtain possible



maximum resistance. The ratio of maximum and minimum resistance is \_\_\_\_\_ .

A. 100

B. 10

C. 2.5

D. 25

**Answer:**



**Watch Video Solution**

**44.** A filament bulb ( $500W, 100V$ ) is to be used in a  $230V$  main supply. When a resistance  $R$  is connected in series, it works perfectly and the bulb consumes  $500W$ . The value of  $R$  is

A.  $13\Omega$

B.  $230\Omega$

C.  $46\Omega$

D.  $26\Omega$

**Answer:**



Watch Video Solution

**45.** An electron in potentiometer experiences a force  $2.4 \times 10^{-19} N$ . The length of potentiometer wire is 6m. The emf of the battery connected across the wire is (electronic charge  $= 1.6 \times 10^{-19} C$ )

A. 6 V

B. 9 V

C. 12 V

D. 15 V


**Answer:**



**Watch Video Solution**

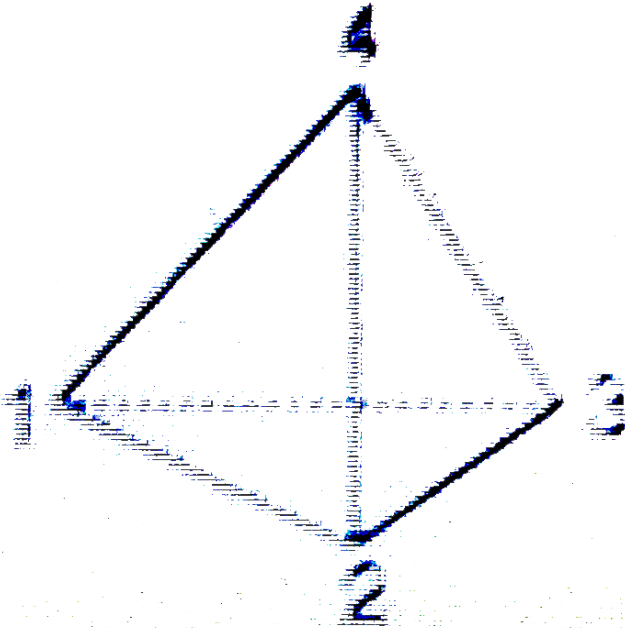**46.** Six wires each of resistance  $r$  form a tetrahedron. The equivalent resistance

between corners 1-2 and 1-3 are respectively



- A.  $r$
- B.  $2r$
- C.  $\frac{r}{3}$
- D.  $\frac{r}{2}$

**Answer:**



**Watch Video Solution**

**47.** Two batteries with e.m.f 12 V and 13 V are connected in parallel across a load resistor of  $10\Omega$ . The internal resistances of the two batteries are  $1\Omega$  and  $2\Omega$  respectively. The voltage across the load lies between :

A. 11.4 V and 11.5 V

B. 11.7 V and 11.8 V

C. 11.6 V and 11.7 V

D. 11.5 V and 11.6 V

**Answer:**



**Watch Video Solution**

**48.** Statement-1 : In a Meter Bridge experiment, null point for an unknown resistance is measured. Now, the unknown resistance is put inside an enclosure maintained at a higher temperature. The null point can be obtained

at the same point as before by decreasing the value of the standard resistance.

Statement-2 : Resistance of metal increases with increase in temperature.

- A. Assertion is True, Reason is True, Reason is a correct explanation for Assertion
- B. Assertion is True, Reason is True, Reason is not a correct explanation for Assertion
- C. Assertion is True, Reason is False
- D. Assertion is False, Reason is True.



**Answer:**



**Watch Video Solution**

## Evaluation Test

1. A circuit consists of two cells, each of e.m.f.  $E$  and internal resistances  $r_1$  and  $r_2$  are connected in series through an external resistance  $X$ . If the potential difference between the ends of the first cell is zero, the value of  $X$  in terms of  $r_1$  and  $r_2$  will be

A.  $r_1 + r_2$

B.  $r_1 - r_2$

C.  $r_1 r_2$

D. zero

**Answer:**



**Watch Video Solution**

2. An ammeter and a voltmeter are joined in series to a cell. Their readings are A and V

respectively. If a resistance is now joined in parallel with the voltmeter

- A. both X and Y will increase
- B. both X and Y will decrease
- C. X will decrease, Y will increase
- D. X will increase, Y will decrease

**Answer:**



**Watch Video Solution**

3. A person decides to use his bath tub water to generate electric power to run a 40W bulb. The bath tub is located at a height of 10m from the ground and it holds 200 litres of water. He installs a water driven wheel generator on the ground. At what rate should the water drain from the bath tub to light the bulb? How long can he keep the bulb on, if bath tub was full initially? Efficiency of generator is 90%. Take  $g = 9.8m/s^2$

A. 0.21, 15.9 s

B. 0.63, 159 s

C. 0.84, 0.159 s

D. 1.05, 1.59 s

**Answer:**



**Watch Video Solution**

4. A cell has an emf of 3 volt and internal resistance  $2\Omega$ . It is connected to an ammeter having resistance  $2\Omega$  and to an external resistance of  $100\Omega$ . When a voltmeter is

connected across the  $100\Omega$ . Resistance, the ammeter reading is 40 mA. The resistance of the voltmeter is

A.  $49\Omega$

B.  $98\Omega$

C.  $147\Omega$

D.  $245\Omega$

**Answer:**



**Watch Video Solution**

5. A certain wire is made up into two squares with a common side of length 5 cm. A current enters the rectangular network at one of the corners and leaves at the diagonally opposite corner. The current in the common side in terms of the entering current is

A.  $I/2$

B.  $I/3$

C.  $I/4$

D.  $I/5$

**Answer:**



**Watch Video Solution**

**6. Assertion :** A wire of uniform cross-section and uniform resistivity is connected across an ideal cell. Now the length of wire is doubled keeping volume of wire constant. The drift velocity of electrons after stretching the wire becomes one fourth of what it was before stretching the wire.

**Reason:** If a wire (of uniform resistivity and



uniform cross-section) of length  $l_0$  is stretched by a factor  $n$ , then its resistance becomes  $n^2$  times the one before stretching the wire (the volume of wire is kept constant in stretching process.) Further at constant potential difference, current is inversely proportional to resistance. Drift velocity of free electron is directly proportional to current and inversely proportional to cross-sectional area of current carrying wire.

A. Assertion is True, Reason is True, Reason is a correct explanation for Assertion

B. Assertion is True, Reason is True, Reason

is not a correct explanation for Assertion

C. Assertion is True, Reason is False

D. Assertion is False but Reason is True.

**Answer:**



**Watch Video Solution**