



PHYSICS

BOOKS - PUNJAB BOARD PREVIOUS YEAR PAPERS

Electric Current, Resistance and E.M.F.

Exercise

1. A current 5.0A flows through an electric press of resistance 11Ω Calculate the energy

consumed by the press in 5 minutes.



Watch Video Solution

2. A lamp of 100 W works at 220 volt. What is its resistance and current capacity?



Watch Video Solution

3. A 60W-220V bulb and 100W-220V bulb are connected in parallel to main supply. Which bulb will draw more current?



[Watch Video Solution](#)

4. What is resistance of carbon resistance on which colour of ring in sequence is black, brown, black and gold?



[Watch Video Solution](#)

5. A carbon resistor of $47k\Omega$ is to be marked with rings of different colours for its identification. Write its sequence of colours.



[Watch Video Solution](#)


6. What is the colour coding of strips on the carbon resistor of resistor $200\Omega \pm 10\%$?



[Watch Video Solution](#)

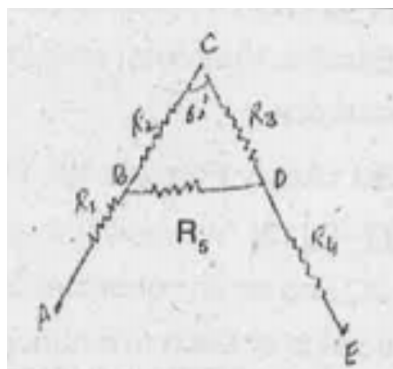7. A letter .A. consists of a uniform wire of resistance .A. one ohm per cm. The sides of the letter are each 20 cm long and crosspiece in the middle is 10cm long, while the apex angle is 60° . Find the resistance of the letter

between two ends of the legs A. and E as shown in figure given below.



[Watch Video Solution](#)

8. To produce 10^3 Joules of heat in 10 seconds, how much voltage should be applied to 100 ohm resistance?



[Watch Video Solution](#)

9. A current of 5 ampere flows in a 10 ohm resistor. Calculate rate of heat energy produced in the resistor.



Watch Video Solution

10. A heater is rated as 220 volts, 880 watts. What is the current drawn by the heater when connected to a 220V a.c. mains? Calculate the resistance of heater.



[Watch Video Solution](#)

11. A carbon resistor has three colours yellow, blue and red respectively. What will be the resistance ?



[Watch Video Solution](#)

12. A carbon resistor has three colours red, yellow and blue respectively. What will be the resistance ?



[Watch Video Solution](#)

13. Two resistances when connected in series give a total resistance of 18Ω and when connected in parallel gives a total resistance of 4Ω . Find the value of each resistance.



Watch Video Solution

14. Two resistances are in the ratio of 1:4. If these are connected in parallel, their total

resistance becomes 16Ω . Find the value of each resistance.



[Watch Video Solution](#)

15. Two resistances when connected in series give a resistance of 9Ω and when connected in parallel gives a resistance of 2Ω . Calculate the value of each resistance.



[Watch Video Solution](#)

16. How will you represent aresistance of 3700 $\Omega \pm 10\%$ by colour coding?



Watch Video Solution

17. Calculate the resistivity of the material of wire 1.0 m (meter) long 0.4 mm (millimeter) in diameter and having resistance of 2.0 ohm.



Watch Video Solution

18. A wire of length 15 m (meter) and uniform area of cross section $6.0 \times 10^{-7} \text{ m}^2$ has resistance of 5.0Ω (ohm). What is the resistivity of the material of the wire ?



Watch Video Solution

19. A wire of length 2.0 m, diameter 1.0 mm has $50 \times 10^{-3} \Omega$ (ohm) resistance. Calculate the resistivity of the material of a wire.



Watch Video Solution

20. A parallel combination of three resistors takes a current of 5A from a 20V supply. If the two resistors are of 10 ohm and 8 ohm, find the value of third resistor.



Watch Video Solution

21. The parallel combination of three resistors takes a current of 7.5A from a 30V supply. If the two resistors are of 10 ohm and 12 ohm, find the third one.



[Watch Video Solution](#)

22. A series combination of three resistors takes a current of 2A from a 24V supply. If the resistors are in the ratio 1 : 2 :3, find the value of unknown resistors.



[Watch Video Solution](#)

23. A wire has a resistance of 10.5Ω at $21^\circ C$ and 16.4Ω at $147^\circ C$. Find the value of

temperature coefficient of resistance.



[Watch Video Solution](#)

24. A resistance of a tungsten filament at $150^{\circ}C$ is 133Ω . What will be its resistance at $500^{\circ}C$? The temperature coefficient of resistance of tungsten at $0^{\circ}C$ is $0.0045^{\circ}C^{-1}$.



[Watch Video Solution](#)

25. A silver wire has a resistance of 2.1Ω at $27.5^\circ C$ and a resistance of 2.7Ω at $100^\circ C$.

Determine the temperature coefficient of wire



Watch Video Solution

26. Three identical cells of emf $4V$ each and unknown internal resistances are connected in parallel. The combination is connected to 10 ohm resistor. If terminal voltage across the cells is $2V$, find internal resistance of each cell.





[Watch Video Solution](#)

27. If maximum resistance from the combination of two resistances is 18 ohm and minimum resistance is 4 ohm, find two resistances



[Watch Video Solution](#)

28. A wire with an area of cross-section as 10mm^2 has a resistance of 5Ω , when a potential difference across its ends is 25V.

Calculate the drift velocity of electrons. Given the number density of electrons as 5×10^{20} electrons per cubic meter (e/m^{-3})



[Watch Video Solution](#)

29. A wire with an area of cross-section as 1 mm^2 has a resistance of 10Ω , when a potential difference across its ends is 8V . Calculate the drift velocity of electrons. Given, number density of electrons in wire as 8×10^{20} electrons per cubic meter.



Watch Video Solution

30. Given three resistors of resistances 1Ω (Ohm), 2Ω (Ohm) and 3Ω (Ohm). How will you combine them to get an equivalent resistance of $\frac{11}{5}\Omega$ (Ohm) ?



Watch Video Solution

31. How many electrons pass through a lamp in one minute if current flowing in lamp is 200mA ?



[Watch Video Solution](#)

32. How does the conductivity of metals varies with the rise in their temperature?



[Watch Video Solution](#)

33. Why Eureka metal is used to make standard resistance coil?



[Watch Video Solution](#)

34. Why copper is used to make connecting wires ?



Watch Video Solution

35. How does the conductivity of semi-conductors varies with the rise in their temperature ?



Watch Video Solution

36. Why Manganin is used to make standard resistance coil ? How does the electric resistance of metal varies with the rise in its temperature ?



Watch Video Solution

37. Define one Ampere of current.



Watch Video Solution

38. What is the resistance of an ideal voltmeter and an ammeter?



Watch Video Solution

39. The specific resistance of a conductor increases with Increase in temperature:



Watch Video Solution

40. The specific resistance of a conductor increases with Increase in cross-sectional area..



Watch Video Solution

41. The specific resistance of a conductor increases with Decrease in length



Watch Video Solution

42. The specific resistance of a conductor increases with Increase in cross-sectional area..



Watch Video Solution

43. Why the fuse wire should have high resistance and low melting point?



Watch Video Solution

44. Why the fuse wire should have high resistance and low melting point?



Watch Video Solution

45. A fuse wire is a wire of Low resistance and high melting point.



Watch Video Solution

46. Why the fuse wire should have high resistance and low melting point?



[Watch Video Solution](#)

47. One kilowatt hour is equal to

A. $36 \times 10^5 J$

B. $36 \times 10^3 J$

C. $36 \times 10^{-5} J$

D. $3.6 \times 10^{-6} J$

Answer:



Watch Video Solution

48. Which out of the following is used to make standard resistance

A. Carbon

B. Copper

C. Silicon

D. Constantan

Answer:



Watch Video Solution

49. The rings on carbon resistance have colours in the sequence Red, Yellow, Violet and Silver. Then resistance is :

A. $24 \times 10^7 \pm 10\%$

B. $42 \times 10^5 \pm 10\%$

C. $68 \times 10^4 \pm 10\%$

D. $37 \times 10^2 \pm 5\%$

Answer:



Watch Video Solution

50. With increase in temperature, resistance of metals :

A. decreases

B. increases

C. first decreases then increases

D. remains constant

Answer:



Watch Video Solution

51. For alloys the value of temperature coefficient of resistance is very high.

(True/False)



Watch Video Solution

52. For metallic conductors the value of temperature coefficient of resistance is

negative. (True/False)



[Watch Video Solution](#)

53. S.I. unit of electromotive force is volt.

(True/False)



[Watch Video Solution](#)

54. On what factor does the internal resistance of a cell depends?



[Watch Video Solution](#)

55. With the help of a diagram derive the formula for the equivalent resistance of three resistances connected in parallel?



Watch Video Solution

56. What is the internal resistance of a cell ?
How it can be measured ?



Watch Video Solution

57. What is Non-ohmic device ? Give one example.



Watch Video Solution

58. What is a drift velocity ? Establish the relations between the drift velocity and electric current.



Watch Video Solution

59. If drift velocity of electron as well as charge on electron is very small, how can we still obtain large amount of current in a conductor?



Watch Video Solution

60. Define internal resistance of a cell and find an expression for it.



Watch Video Solution

61. Establish the relation between drift velocity of electrons and electric field applied to the conductor.



Watch Video Solution

62. The number density of free electrons in a metal piece is a very large of the order of $10^{+29} m^{-3}$. Why is there no current in the metal piece in the absence of electric field across it ?





[Watch Video Solution](#)

63. Standard resistance coils are made up of which material why ?



[Watch Video Solution](#)

64. What is the effect of the temperature on resistivity of metals



[Watch Video Solution](#)

65. What is the effect of the temperature on resistivity of semiconductors ?



Watch Video Solution

66. Why connecting wires are made up of copper ?



Watch Video Solution

67. What is resistance of a wire ? What are the factors on which resistance of a conductor

depends?



[Watch Video Solution](#)

68. What is the difference between emf of a cell and potential difference of a cell?



[Watch Video Solution](#)

69. What is resistivity of a wire ? What are the physical conditions on which resistivity of a metal depends ?



[Watch Video Solution](#)

70. What are the factors on which the resistance of the conductor depends hence define resistivity of the conductor ?



[Watch Video Solution](#)

71. Distinguish between emf and potential difference.



[Watch Video Solution](#)

72. Explain colour code for carbon resistor .



Watch Video Solution

73. Establish the relation between drift velocity of electrons and electric field applied to the conductor.



Watch Video Solution

74. A large number of free electrons are present in metals. Why is there no current in the absence of electric field across it ?



Watch Video Solution

75. What is a drift velocity ? Establish the relations between the drift velocity and electric current.



Watch Video Solution

76. Why connecting wires are made up of copper ?



Watch Video Solution

77. What are ohmic and non-ohmic devices ?
Give one example of each.



Watch Video Solution

78. What is the resistance of a conductor?

State the factors on which resistance of a conductor depends?



Watch Video Solution

79. Which out of the following is used to make standard resistance



Watch Video Solution

80. Why connecting wires are made up of copper ?



Watch Video Solution

81. Standard resistance coils are made up of which material why ?



Watch Video Solution

82. What is the internal resistance of a cell ?

Derive an expression for it.



Watch Video Solution

83. Why connecting wires are made up of copper ?



Watch Video Solution

84. What is the internal resistance of a cell ?

Derive an expression for it.



Watch Video Solution

85. What is e.m.f. of a cell ? On what factors does its value depend ?



Watch Video Solution

86. Establish the relation between drift velocity of electrons and electric field applied to the conductor.



Watch Video Solution

87. What do you mean by conductivity of a material? Give its SI unit.



Watch Video Solution

88. What is effect of rise in temperature on the resistivity of metallic conductors and semiconductors ?



Watch Video Solution

89. What is meant by resistivity ? Write its S.I. unit.



Watch Video Solution

90. What is the effect of rise in temperature on the conductivity of copper and silicon ?



Watch Video Solution

91. What is meant by resistance of conductor and define its units.



Watch Video Solution

92. What is effect of rise in temperature on the conductivity of metallic conductors and semiconductors ?



Watch Video Solution

93. Distinguish between emf and potential difference.



Watch Video Solution

94. What is the internal resistance of a cell ?

Derive an expression for it.



Watch Video Solution

95. What is a drift velocity ? Establish the relations between the drift velocity and electric current.



Watch Video Solution

96. State Ohm's law. Derive the laws of resistance, when they are connected in series



Watch Video Solution

97. State Ohm's law. Derive the laws of resistance, when they are connected in parallel.



Watch Video Solution

98. Find the equivalent of resistances of the individual resistance connected in series?



Watch Video Solution

99. With the help of a diagram derive the formula for the equivalent resistance of three resistances connected in parallel?



Watch Video Solution

100. State Ohm's law and derive it from the basic idea of drift velocity of electrons.



Watch Video Solution