



# PHYSICS

## NCERT - NCERT PHYSICS(HINGLISH)

### ELECTRICITY

#### Solved Examples

1. A current of  $0.5A$  is drawn by a filament of an electric bulb for 10 minutes. Find the

amount of electric charge that flows through the electric circuit.



**Watch Video Solution**

2. How much work is done in moving a charge of  $2C$  across two points having a potential difference of  $12V$  ?



**Watch Video Solution**

3. (a) How much current will an electric bulb draw from a  $220V$  source, if the resistance of the bulb filament is  $1200\Omega$  ?

(b) How much current will an electric heater draw from a  $220V$  source, if the resistance of the heater coil is  $100\Omega$  ?



**Watch Video Solution**

4. The potential difference between the terminals of an electric heater is  $60V$  when it

draws a current of  $4A$  from the source. What current will the heater draw if the potential difference is increased to  $120V$  ?



[Watch Video Solution](#)

5. Resistance of a metal wire of length  $1\text{ m}$  is  $26\Omega$  at  $20^\circ C$ . If the diameter of the wire is  $0.3\text{mm}$ , what will be the resistivity of the metal at that temperature ? Using Table 1.1, predict the material of the wire.



[Watch Video Solution](#)

6. A wire of given material having length  $l$  and area of cross-section  $A$  has a resistance of  $4\Omega$ . What would be the resistance of another wire of the same material having length  $l/2$  and area of cross-section  $2A$  ?



[Watch Video Solution](#)


7. An electric lamp, whose resistance is  $20\Omega$  and a conductor of  $4\Omega$  resistance are connected to a  $6V$  battery as shown in (Fig.

3.18) Calculate.

(a) the total resistance of the circuit,


(b) the current through the circuit, and

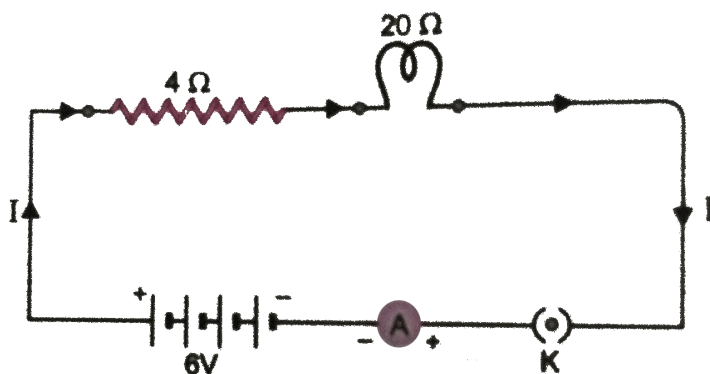(c) the potential difference across the electric lamp and the conductor.



[Watch Video Solution](#)

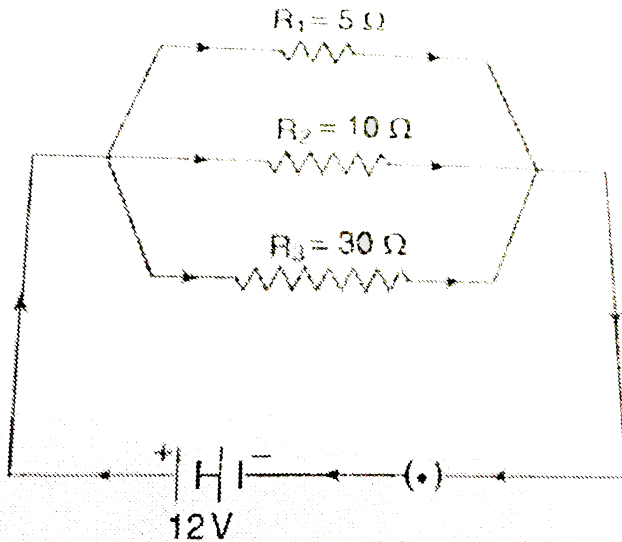8. In the circuit diagram given below, three resistors  $R_1$ ,  $R_2$ , and  $R_3$  of  $5\Omega$ ,  $10\Omega$  and  $30\Omega$ , respectively are connected as shown.



Calculate:

- current through each resistor.
- total current in the circuit.
- total resistance in the circuit.



[Watch Video Solution](#)

9. If in Fig. 12.12,  $R_1 = 10\Omega$ ,  $R_2 = 40\Omega$ ,  $R_3 = 30\Omega$ ,  $R_5 = 60\Omega$ , and a 12 V battery is connected to the arrangement. Calculate (a) the total resistance in the circuit, and (b) the total current flowing in the circuit.



[Watch Video Solution](#)



10. A electric iron consumes energy at the rate of

(a)  $840W$  when heating is at the maximum rate and

(b)  $360W$  when the heating is at the minimum.

The voltage is  $220V$ . What are the current and the resistance in each case ?



[Watch Video Solution](#)

11.  $100J$  of heat are produced each second in a  $4\Omega$  resistance. Find the potential difference across the resistor.



[Watch Video Solution](#)

12. An electric bulb is connected to a  $220V$  generator. The current is  $0.50A$ . What is the power of the bulb ?



[Watch Video Solution](#)

13. An electric refrigerator rated  $400W$  operates  $8\text{hour} / \text{day}$ . What is the cost of the energy to operate it for 30 days at Rs. 3.00 per  $kWh$  ?



[Watch Video Solution](#)

## Exercise

1. What does an electric circuit mean ?



[Watch Video Solution](#)

2. Define the unit of current.



[Watch Video Solution](#)

3. Calculate the number of electrons constituting one coulomb of charge.



[Watch Video Solution](#)

4. Name a device that helps to maintain a potential difference across a conductor.



[Watch Video Solution](#)

5. What is meant by saying that the potential difference between two points is  $1V$  ?



[Watch Video Solution](#)

6. How much energy is given to each coulomb of charge passing through a  $6V$  battery ?



[Watch Video Solution](#)

7. On what factors does the resistance of a conductor depend ?



**Watch Video Solution**

8. Will current flow more easily through a thick wire or a thin wire of the same material when connected to the same source ? Why ?



**Watch Video Solution**

**9.** Let the resistance of an electrical component remain constant while the potential difference across the two ends of the component decreases to half its former value. What change will occur in the current through it ?



**Watch Video Solution**

**10.** Why are coils of electric toasters and electric irons made of an alloy rather than a

pure metal ?



**Watch Video Solution**

**11.** Use the data in Table 3.1 to answer the following :

(a) Which among iron and mercury is a better conductor ?

(b) Which material is the best conductor ?



**Watch Video Solution**



**12.** Draw a schematic diagram of a circuit consisting of a battery of three cells of  $2V$  each, a  $5\ \text{ohm}$  resistor, an  $8\ \text{ohm}$  resistor, and a  $12\ \text{ohm}$  resistor, and a plug key, all connected in series.



**Watch Video Solution**

**13.** Redraw the circuit of  $Q.12$ , putting in an ammeter to measure the current through the resistors and a voltmeter to measure the

voltage across the  $120\text{ohm}$  resistor. What would be the readings in the ammeter and the voltmeter ?



[Watch Video Solution](#)

**14.** Judge the equivalent resistance when the following are connected in parallel.

(a)  $1\Omega$  and  $10^6\Omega$

(b)  $1\Omega$  and  $10^8\Omega$  and  $10^6\Omega$ .



[Watch Video Solution](#)

15. An electric lamp of  $100\Omega$ , a toaster of resistance  $50\Omega$  and a water filter of resistance  $500\Omega$  are connected in parallel to a  $220V$  source. What is the resistance of an electric iron connected to the same source that takes as much current as all three appliances and what is the current through it ?



[Watch Video Solution](#)

16. What are the advantages of connecting electrical devices in parallel with the battery

instead of connected them in series ?



[Watch Video Solution](#)

17. How can three resistors of resistances  $2\Omega$ ,  $3\Omega$ , and  $6\Omega$  be connected to give a total resistance of

(a)  $4\Omega$

(b)  $1\Omega$  ?



[Watch Video Solution](#)

**18.** What is : (a) the highest (b) the lowest total resistances that can be obtained by combinations of four coils of resistances  $4\Omega$ ,  $8\Omega$ ,  $12\Omega$ ,  $24\Omega$  ?



**Watch Video Solution**

**19.** Why does the cord of an electric heater not glow while the heating element does ?



**Watch Video Solution**

20. Compute the heat generated while transferring 96000 coulombs of charge in one hour through a potential difference of 50V.



[Watch Video Solution](#)

21. An electric iron of resistance  $20\Omega$  takes a current of 5A. Calculate the heat developed in 30s.



[Watch Video Solution](#)

**22.** What determines the rate at which energy is delivered by a current ?



**Watch Video Solution**

**23.** An electric motor takes  $5A$  from a  $220V$  line. Determine the power and energy consumed in  $2h$ .



**Watch Video Solution**

24. A piece of wire of resistance  $R$  is cut into five equal parts. These parts are then connected in parallel. If the equivalent resistance of this combination is  $R'$ , then the ratio  $R/R'$  is :

A.  $\frac{1}{25}$

B.  $\frac{1}{5}$

C. 5

D. 25

**Answer:**





Watch Video Solution

25. Which of the following terms does not represent electrical power in a circuit :

A.  $I^2 R$

B.  $IR^2$

C.  $VI$

D.  $\frac{V^2}{R}$

**Answer: B**



26. An electric bulb is rated  $220V$  and  $100W$ .  
When it is operated on  $110V$ , the power consumed will be :

A.  $100W$

B.  $75W$

C.  $50W$

D.  $25W$

**Answer:**



27. Two conducting wires of the same material and of equal length and equal diameters are first connected in series and then in parallel in an electric circuit. The ratio of the heat produced in series and parallel combinations would be :

A. 1 : 2

B. 2 : 1

C. 1 : 4

D. 4: 1

**Answer:**



**Watch Video Solution**

**28.** How is voltmeter connected in the circuit to measure potential difference between two points ?



**Watch Video Solution**

**29.** A copper wire has a diameter of  $0.5\text{mm}$  and a resistivity of  $1.6 \times 10^{-6}\Omega\text{cm}$ . How much of this wire would be required to make a  $10\Omega$  coil ? How much does the resistance change if the diameter is doubled ?



**Watch Video Solution**

**30.** The value of current,  $I$ , flowing in a given resistor for the corresponding values of potential difference,  $V$ , across the resistor are

given below :

$I$ (ampere)	0.5	1.0	2.0	3.0	4.0
$V$ (volt)	1.6	3.4	6.7	10.2	13.2

Plot a graph between  $V$  and  $I$  and calculate the resistance of the resistor.



[Watch Video Solution](#)

**31.** When a  $12V$  battery is connected across an unknown resistor, there is a current of  $2.5mA$  in the circuit. Find the value of the resistance of the resistor.



[Watch Video Solution](#)

**32.** A battery of  $9V$  is connected in series with resistors of  $0.2\Omega$ ,  $0.3\Omega$ ,  $0.4\Omega$ ,  $0.5\Omega$  and  $12\Omega$ . How much current would flow through the  $12\Omega$  resistor ?



**Watch Video Solution**

**33.** How many  $176\Omega$  resistors (in parallel) are required to carry  $5 A$  in  $220 V$  line ?



**Watch Video Solution**

**34.** Show how you would connect three resistors, each of resistance  $6\Omega$ , so that the combination has a resistance of

(i)  $9\Omega$

(ii)  $2\Omega$ .



**Watch Video Solution**

**35.** Several electric bulbs designed to be used on a  $220V$  electric supply line, are rated  $10W$ .

How many lamps can be connected in parallel



with each other across the two wires of  $220V$  line if the maximum allowable current is  $5A$  ?



[Watch Video Solution](#)

**36.** A hot plate of an electric oven connected to a  $220V$  lines has two resistance coils  $A$  and  $B$ , each of  $24\Omega$  resistance, which may be used separately, in series or in parallel. What are the currents in the three cases ?



[Watch Video Solution](#)

**37.** Compare the power used in the  $2\Omega$  resistor in each of the following circuits :

(i) a  $6V$  battery in series with  $1\Omega$  and  $2\Omega$  resistors, and

(ii) a  $4V$  battery in parallel with  $12\Omega$  and  $2\Omega$  resistors.



**Watch Video Solution**

**38.** Two lamps, one rated  $100W$  at  $220V$ , and the other  $60W$  at  $220V$ , are connected in parallel to the electric mains supply. What

current is drawn from the line if the supply voltage is  $220V$  ?



[Watch Video Solution](#)

**39.** Which uses more energy, a  $250W$  TV set in  $1h$  or a  $1200W$  toaster in 10 minutes ?



[Watch Video Solution](#)

**40.** An electric heater of resistance  $8\Omega$  draws  $15A$  from the service mains for 2 hours.

Calculate the rate at which heat is developed in the heater.



[Watch Video Solution](#)

**41.** Explain the following :

(a) Why is tungsten used almost exclusively for filament of incandescent lamp ?

(b) Why are the conductors of electric heating devices, such as toaster and electric irons, made of an alloy rather than a pure metal ?

( c ) Why is the series arrangement not used

for domestic circuits ?

(d) How does the resistance of a wire vary with its cross-sectional area ?

(e ) Why are copper and aluminium wires usually employed for electricity transmission.



**Watch Video Solution**