



PHYSICS

FOR IIT JEE ASPIRANTS OF CLASS 12

FOR PHYSICS

ALTERNATING CURRENT

Example

1. You have two copper cables of equal length for carrying current. One of them has a single

wire of area of across section A , the other has ten wires each of cross section area $A/10$. Judge their suitability for transporting ac and dc .



Watch Video Solution

2. If the voltage in an ac circuit is represented by the equation.

$V = 220\sqrt{2}\sin(314t - \phi)$ volt calculate (a) peak and rms value of the voltage, (b) average voltage, (c) frequency of ac .



 [Watch Video Solution](#)


3. A current is made of two components a *dc* component $i_1 = 3A$ and an *ac* component $i_2 = 4\sqrt{2}\sin\omega t$. Find the reading of hot wire ammeter?



[Watch Video Solution](#)

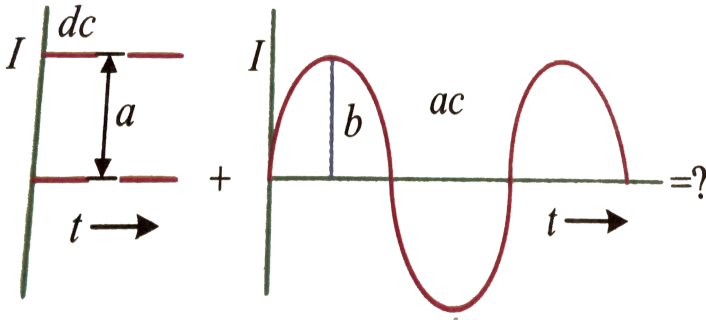
4. If a direct current of value a ampere is superimposed on an alternating current $i = b\sin\omega t$ flowing through a wire, what is the

effective value of the resulting current in the circuit?



[Watch Video Solution](#)

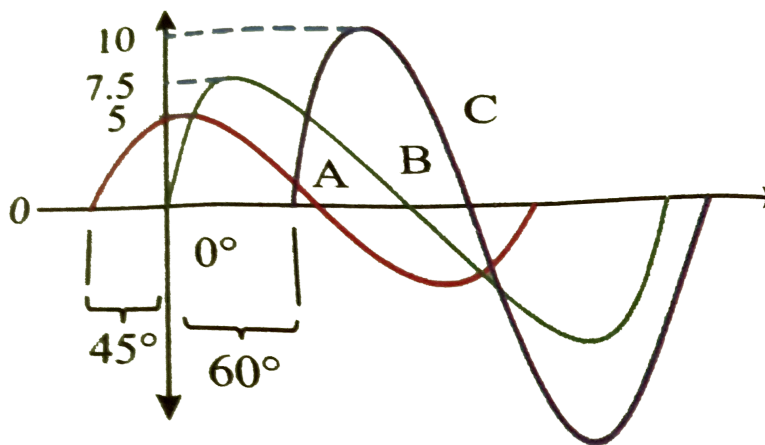5. Use a phasor diagram to represent the sine waves in the following Figure.



[▶ Watch Video Solution](#)

6. An alternating voltage $E = 200\sqrt{2}\sin(100t)V$ is connected to a $1\mu F$ capacitor through an ac ammeter (it reads rms value). What will be the reading of the ammeter?

[▶ Watch Video Solution](#)

7. Find the maximum value of current when inductance of two henry is connected to 150 volt, 50 cycle supply.



[Watch Video Solution](#)

8. An inductor of 1 henry is connected across a 220v, 50Hz supply. The peak value of the current is approximately.



[Watch Video Solution](#)

9. A capacitor of capacitance $2\mu F$ is connected in the tank circuit of an oscillator oscillating with a frequency of 1 kHz. If the current flowing in the circuit is $2mA$, the voltage across the capacitor will be



Watch Video Solution

10. A $0.21H$ inductor and a $12ohm$ resistance are connected in series to a $220V, 50Hz$ ac source. Calculate the current in the circuit and the

phase angle between the current and the source voltage.



[Watch Video Solution](#)

11. When 100 volt dc is applied across a coil, a current of 1amp flows through it, when 100V ac of 50Hz is applied to the same coil, only 0.5 amp flows. Calculate the resistance and inductance of the coil.



[Watch Video Solution](#)

12. A $10\mu\text{g}$ capacitor is in series with a 50Ω resistance and the combination is connected to a 220V , 50Hz line. Calculate (i) the capacitive reactance, (ii) the impedance of the circuit and (iii) the current in the circuit.



Watch Video Solution

13. A coil has an inductance of 0.7 H and is joined in series with a resistance of 220 ohm . Find the wattless component of current in the

circuit, when an alternating e.m.f. of 220 V at a frequency of 50 Hz is supplied to it.



[Watch Video Solution](#)

14. In a circuit L , C and R are connected in series with an alternating voltage source of frequency f . The current lead the voltages by 45° . The value of C is :



[Watch Video Solution](#)

15. In a series LCR circuit, the voltage across the resistance, capacitance and inductance is 10 V each. If the capacitance is short circuited, the voltage across the inductance will be



[Watch Video Solution](#)

16. An inductance of $\frac{200}{\pi} mH$ a capacitance of $\frac{10^{-3}}{\pi}$ and a resistance of 10Ω are connected in series with an AC source of 220V, 50Hz. The phase angle of the circuit is





[Watch Video Solution](#)

17. In a series LCR circuit $R = 200(\Omega)$ and the voltage and the frequency of the main supply is 220V and 50 Hz respectively. On taking out the capacitance from the circuit the current lags behind the voltage by 30° . On taking out the inductor from the circuit the current leads the voltage by 30° . The power dissipated in the LCR circuit is



[Watch Video Solution](#)

18. An LCR circuit has $L = 10mH$. $R = 3$ ohm and $C = 1\mu F$ connected in series to a source is $15\cos\omega t$ volt. What is average power dissipated per cycle at a frequency that is 10% lower than the resonant frequency?



Watch Video Solution

19. A $750Hz$, $20V$ source is connected to a resistance of 100Ω an inductance of $0.1803H$ and a capacitance of $10\mu F$ all in series. Calculate the time in which the resistance

(thermal capacity $2J/^\circ C$) will get heated by $10^\circ C$.



[Watch Video Solution](#)

20. An ideal choke coil takes a current of 8 ampere when connected to an AC supply of 100 volt and $50Hz$. A pure resistor under the same conditions takes a current of 10 ampere. If the two are connected to an AC supply of 150 volts and $40Hz$ then the current in a series combination of the above resistor and inductor is



[Watch Video Solution](#)

21. An electric bulb has a rated power of $50W$ at $100V$. If it is used on *AC* source of $200V, 50Hz$, a choke has to be used in series with it. This choke should have an inductance of



[Watch Video Solution](#)

22. A transformer having efficiency 90% is working on $100V$ and at $2.0kW$ power. If the current in the secondary coil is $5A$, calculate (i)

the current in the primary coil and (ii) voltage across the secondary coil.



[Watch Video Solution](#)

23. A step up transformer operates on a 230V line and a load current of 2 ampere. The ratio of the primary and secondary windings is 1 : 25. What is the current in the primary?



[Watch Video Solution](#)

1. In an ac circuit the current

A. is in phase with the voltage

B. leads the voltage

C. lags the voltage

D. any of the above depending on the
circumstances

Answer: D



Watch Video Solution

2. The average emf during the positive half cycle of an ac supply of peak value E_0 is .

A. E_0/π

B. $E_0/\sqrt{2}$

C. $E_0/2\pi$

D. $2E_0/\pi$

Answer: 4



Watch Video Solution

3. Alternating current is transmitted to distant places at

- A. high voltage and low current
- B. high voltage and high current
- C. low voltage and low current
- D. low voltage and high current

Answer: 1



Watch Video Solution

4. In case of *a. c* circuit, Ohm's law holds good for

a) Peak values of voltage and current

b) Effective values of voltage and current

c) Instantaneous values of voltage and current

A. only a is true

B. only a and b are true

C. only c is true

D. a,b and c are true

Answer: 2



Watch Video Solution

5. In case of AC circuits the relation $V = iZ$, where Z is impedance, can directly applied to

A. peak value of voltage and current only

B. rms values of voltage and current only

C. instantaneous value of voltage and current only

D. both 1 and 2 are true

Answer: 4



Watch Video Solution

6. Alternating current can not be measured by

D.C. Ammeter because

A. alternating current can not pass through

an ammeter

B. the average value of current for complete

cycle is zero

C. some amount of alternating current is

destroyed in the ammeter

D. peak value of current is zero

Answer: 2



Watch Video Solution

7. The r.m.s value of Potential due to superposition of given two alternating potentials $E_1 = E_0 \sin \omega t$ and $E_2 = E_0 \cos \omega t$ will be

A. E_0

B. $2E_0$

C. $E_0\sqrt{2}$

D. Zero

Answer: 1



Watch Video Solution

8. If the instantaneous current in a circuit is given by $i = 2\cos(\omega t - \phi)$ ampere, the r.m.s. value of the current is

A. 2

B. $\sqrt{2}$

C. $2\sqrt{2}$

D. zero

Answer: 2



Watch Video Solution

9. If a capacitor is connected to two different
A. C generators, then the value of capacitive
reactance is

A. directly proportional frequency

B. inversely proportional to frequency

C. independent of frequency

D. inversely proportional to the square of frequency

Answer: 2



Watch Video Solution

10. In general in an alternating current circuit

A. the average value of current is zero

B. the average value of square of the current is zero

C. average power dissipation is zero

D. the phase difference between voltage and current is zero

Answer: 1



Watch Video Solution

11. The magnitude induced e.m.f. in an LR circuit at break of circuit as compared to its value at make of circuit will be

A. less

B. more

C. some times less and some times more

D. nothing can be said

Answer: 2



Watch Video Solution

12. The emf and current in a circuit are such that $E = E_0 \sin \omega t$ and $I = I_0 \sin(\omega t - \theta)$. This AC circuit contains

A. R and L

B. R and C

C. only R





D. only C

Answer: 1



Watch Video Solution

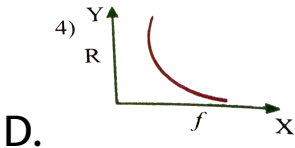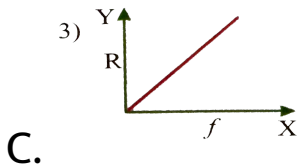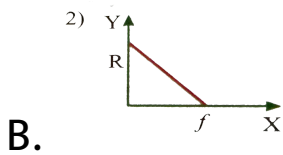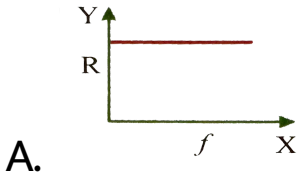13. The correct variation of resistance R with frequency f is given by



Answer: 1



Watch Video Solution

14. Same current is flowing in two alternating circuits. The first circuit contains only inductances and the other contains only a capacitor, if the frequency of the e.m.f of AC is increased, the effect on the value of the current will be

A. increases in first circuit and decrease in the other

B. increase in both circuits

C. decrease in both circuits

D. decrease in first circuit and increase in
the other

Answer: 4



Watch Video Solution

15. When an a.c source is connected across a resistor

A. The current leads the voltage in phase

B. The current lags behind the voltage in phase

C. The current and voltage are in same phase

D. The current and voltage are out of phase

Answer: 3



Watch Video Solution

16. The phase angle between current and voltage in a purely inductive circuit is

A. zero

B. π

C. $\pi/4$

D. $\pi/2$

Answer: 4



Watch Video Solution

17. Ratio of impedance to capacitive reactance has

A. no units

B. ohm

C. ampere

D. tesla

Answer: 1



Watch Video Solution

18. An inductor-coil having some resistance is connected to an AC source. Which of the

following quantities have zero average value over a cycle?

A. induced emf in the inductor only

B. current only

C. both 1 and 2

D. neither 1 nor 2

Answer: 3



Watch Video Solution

19. Why the current does not rise immediately in a circuit containing inductance

- A. because of induced emf
- B. because of high voltage drop
- C. both 1 and 2
- D. because of joule heating

Answer: 3



Watch Video Solution

20. In an AC circuit containing only capacitance the current

A. leads the voltage by 180°

B. lags the voltage by 90°

C. leads the voltage by 90°

D. remains in phase with the voltage

Answer: 3



Watch Video Solution

21. A bulb is connected first with DC and the then AC of same voltage then it will shine brightly with

A. AC

B. DC

C. Equally with both

D. Brightness will be in ratio $1/4$

Answer: 3



Watch Video Solution

22. A capacitor of capacity C is connected in A. C circuit. If the applied emf is $V = V_0 \sin \omega t$, then the current is

A. $I = \frac{V_0}{L\omega} \sin \omega t$

B. $I = \frac{V_0}{\omega C} \sin \left(\omega t + \frac{\pi}{2} \right)$

C. $I = V_0 C \omega \sin \omega t$

D. $I = V_0 C \omega \sin \left(\omega t + \frac{\pi}{2} \right)$

Answer: 4



Watch Video Solution

23. At low frequency a condenser offers

A. high impedance

B. low impedance

C. zero impedance

D. impedance of condenser is independent
of frequency

Answer: 1



Watch Video Solution

24. Statement (A) : The reactance offered by an inductance in *A.C.* Circuit decreases with increase of *AC* frequency

Statement (B) : The reactance offered by capacitor in *AC* circuit increases with increase of *AC* frequency.

A. *A* is true but *B* is false

B. Both *A* and *B* are true

C. *A* is false but *B* is true

D. Both *A* and *B* are false

Answer: 4



Watch Video Solution

25. Statement (A) : With increase in frequency of AC supply inductive reactance increases.

Statement (B) : With increase in frequency of AC supply capacitive reactance increase

A. *A* is true but *B* is false

B. Both *A* and *B* are true

C. *A* is false but *B* is true

D. Both A and B are false

Answer: 1



Watch Video Solution

26. In an $A.C$ circuit having resistance and capacitance

A. emf leads the current

B. current lags behind the emf

C. both the current and emf are in phase

D. current leads the emf.

Answer: 4



Watch Video Solution

27. Select the correct options among the following In an $R - C$ circuit

(a) instantaneous A.C is given by

$$I = I_0 \sin(\omega t + \phi)$$

(b) the alternating current in the circuit leads the emf by a phase angle ϕ .

(c) Its impedance is $\sqrt{R^2 + (\omega C)^2}$

(d) Its capacitive reactance is ωC

A. *a, b* are true

B. *b, c, d* are true

C. *c, d* are true

D. *a, c* are true

Answer: 1



Watch Video Solution

28. If the frequency of alternating e.m.f. is in $L - C - R$ circuit, then the value of impedance Z will change with \log (frequency) as

A. increase

B. increases and then becomes equal to resistance, then it will start decreasing

C. decreases and when it becomes minimum equal to the resistance then it will start increasing

D. go on decreasing

Answer: 3



Watch Video Solution

29. An inductor and a resistor are connected in series with an ac source. In this circuit.

A. the current and $P.d$ across the resistance

lead $P.d$ across the inductance by $\pi/2$

B. the current and $P.d$ across the resistance

lags behind the $P.d$ across the

inductance by angle $\pi/2$

C. The current across resistance leads and the $P. d$ across resistance lags behind the $P. d$ across the inductance by $\pi/2$

D. the current across resistance lags behind and the $P. d$ across the resistance leads the $P. d$ across the inductance by $\pi/2$

Answer: 2



Watch Video Solution

30. An LCR circuit is connected to a source of alternating current. At resonance, the applied voltage and the current flowing through the circuit will have a phase difference of

A. $\pi/4$

B. zero

C. π

D. $\pi/2$

Answer: 2



Watch Video Solution

31. The incorrect statement for $L - R - C$ series circuit is

A. The potential difference across the resistance and the applied current are always in same phase.

B. The phase difference across inductive coil is 90°

C. The phase difference between the potential difference across capacitor and

potential difference across inductance is

90°

D. The phase difference between potential

difference across capacitor and potential

difference across resistance is 90°

Answer: 3



Watch Video Solution

32. In series $L - C - R$ resonant circuit, to increase the resonant frequency

A. L will have to be increased

B. C will have to be increased

C. LC will have to be decreased

D. LC will have to be increased

Answer: 3



Watch Video Solution

33. In an LCR series ac circuit the voltage across L , C and R are V_1 , V_2 and V_3 respectively

The voltage of the source is .

A. $V_1 + V_2 + V_3$

B. $\sqrt{V_1^2 + (V_2 + V_3)^2}$

C. $V_1 - V_2 - V_3$

D. $\sqrt{V_1^2 - (V_2 - V_3)^2}$

Answer: 4



Watch Video Solution

34. In the non-resonant circuit, what will be the nature of the circuit for frequencies higher than the resonant frequency?

A. resistive

B. capacitive

C. inductive

D. both 1 and 2

Answer: 3



Watch Video Solution

35. The phase difference between voltage and current in an *LCR* series circuit is

A. zero always

B. $\pi/4$ always

C. π

D. between 0 and $\pi/2$

Answer: 4



Watch Video Solution

36. In an *LCR* a.c. circuit at resonance, the current

A. Is always in phase with the voltage

B. Always leads the voltage

C. Always lags behind the voltage

D. May lead or lag behind the voltage

Answer: 1



Watch Video Solution

37. An inductance L and capacitance C and resistance R are connected in series across an

AC source of angular frequency ω . If $\omega^2 > \frac{1}{LC}$

then

A. emf leads the current

B. both the emf and the current are in
phase

C. current lead the emf

D. emf lags behind the current

Answer: 1



Watch Video Solution

38. Consider the following two statements A and B and identify the correct answer.

A) At resonance of $L - C$ series circuit, the reactance of circuit is minimum.

B) The reactance of a capacitor is an $A.C$ circuit is similar to the reactance of a capacitor in a $D.C$ circuit

A. A is true but B is false

B. Both A and B are true

C. A is false but B is true

D. Both A and B are false

Answer: 1



Watch Video Solution

39. Choose the wrong statement of the following

A. The peak voltage across the inductor can be less than the peak voltage of the source in an *LCR* circuit

B. In a circuit containing a capacitor and an ac source the current is zero at the

instant source voltage is maximum

- C. When an AC source is connected to a capacitor, then the rms current in the circuit gets increased if a dielectric slab is inserted into the capacitor
- D. In a pure inductive circuitd emf will be in phase with the current.

Answer: 4



Watch Video Solution

40. The essential difference between a *d. c* dynamo and an *a. c* dynamo is that

A. a.c. has an electromagnet but d.c. has a permanent magnet

B. a.c. will generate a higher voltage

C. a.c. has slip rings but the d.c. has a commutator

D. a.c. dynamo has a coil wound on soft iron, but the d.c. dynamo has a coil wound on copper

Answer: 3



Watch Video Solution

41. The unit of impedance is

A. ohm

B. mho

C. ampere

D. volt

Answer: 1



42. The power factor of an AC circuit having resistance (R) and inductance (L) connected in series and an angular velocity ω is

A. $\frac{\sqrt{R^2 + \omega^2 L^2}}{R}$

B. $\frac{R}{\sqrt{R^2 + \omega^2 L^2}}$

C. $\frac{\omega L}{R}$

D. $\frac{R}{\omega L}$

Answer: 2



Watch Video Solution

43. The capacitor offers zero resistance to

A. *D. C* only

B. *A. C & D. C*

C. *A. C* only

D. neither *A. C* nor *D. C*

Answer: 4



Watch Video Solution

44. Power factor is defined as

- A. apparent power / true power
- B. true power / apparent power
- C. true power (apparent power)²
- D. true power x apparent power

Answer: 2



Watch Video Solution

45. The core of any transformer is laminated so as to

A. energy loss due to eddy currents may be reduced

B. rusting of the core may be prevented

C. change in flux may be increased

D. ratio of voltage in the primary to that in the secondary may be increased

Answer: 1





46. A step up transformer is used to

A. increase the current and increase the
voltage

B. decrease the current and increase the
voltage

C. increase the current and decrease the
voltage

D. decrease the current and decrease the voltage

Answer: 2



Watch Video Solution

47. A transformer changes the voltage

A. without changing the current and frequency

B. without changing the current but
changes the frequency

C. without changing the frequency but
changes the current

D. without changing the frequency as well
as the current

Answer: 3



Watch Video Solution

48. A step up transformer is connected on the primary side to a rechargeable battery which can deliver a large current. If a bulb is connected in the secondary, then

A. the bulb will glow very bright

B. the bulb will get fused

C. the bulb will glow, but with less
brightness

D. the bulb will not glow

Answer: 4



Watch Video Solution

49. The ratio of primary voltage to secondary voltage in a transformer is ' n '. The ratio of the primary current to secondary current in the transformer is

A. n

B. $1/n$

C. n^2

D. $1/n^2$

Answer: 2



Watch Video Solution

50. In a step down transformer, the number of turns in the primary is always

A. greater than the number of turns in the secondary

B. less than the number of turns in the secondary

C. equal to the number of turns in the secondary

D. either greater than or less than the number of turns in the secondary

Answer: 1



Watch Video Solution

51. The transformer ratio of a step up transformer is

A. greater than one

B. less than one

C. less than one and some times greater
than one

D. greater than one and some times less
than one

Answer: 1



Watch Video Solution

52. A setup transformer develops $440V$ in secondary coil for an input of $200VA$. Then the type of transformer is

A. Stepped down

B. stepped up

C. Same

D. Same but with reversed direction

Answer: 2



Watch Video Solution

53. Assertion (A) : If changing current is flowing through a machine with iron parts, results in loss of energy.

Reason (R) : Changing magnetic flux through an area of the iron parts causes eddy currents.

A. Both *A* and *R* are individually true and *R* is the correct explanation of *A*

B. Both *A* and *R* are individually true but *R* is not the correct explanation of *A*

C. *A* is true but *R* is false

D. Both A and R are false

Answer: 1



Watch Video Solution

54. Transformers are used

A. d.c circuit only

B. a.c. circuit only

C. Both a.c and d.c circuits

D. Integrated circuits

Answer: 2



Watch Video Solution

55. The magnitude of the e.m.f. across the secondary of a transformer does not depend on

- A. The number of the turns in the primary
- B. The number of the turns in the secondary
- C. The magnitude of the e.m.f applied across the primary

D. The resistance of the primary and the secondary

Answer: 4



Watch Video Solution

56. For an ideal transformer ratio of output ot the input power is always

A. greater than one

B. equal ot one

C. less than one

D. zero

Answer: 2



Watch Video Solution

57. Consider the following two statements *A* and *B* and identify the correct answer.

(A) In a transformer a large alternating current at low voltage can be transformed into a small alternating current at high voltage

(B) Energy in current carrying coil is stored in the form of magnetic field.

A. A is true but B is false

B. Both A and B is true

C. A is false but B is true

D. Both A and B are false

Answer: 2



Watch Video Solution

58. Statement (A) : Flux leakage in a transformer can be minimized by winding the primary and secondary coils one over the other.
Statement (B) : Core of the transformer is made of soft iron

- A. *A* is true but *B* is false
- B. Both *A* and *B* is true
- C. *A* is false but *Bd* is true
- D. Both *A* and *B* are false

Answer: 4



Watch Video Solution

59. Statement (A) : In high current low voltage windings of a transformer thick wire is used to minimize energy loss due to heat produced

Statement (B) : The core of any transformer is laminated so as to reduce the energy loss due to eddy currents.

A. A is true but B is false

B. Both A and B is true

C. A is false but B is true

D. Both A and B are false

Answer: 2



Watch Video Solution

60. Statement (A) : Step up transformer converts low voltage, high current to high voltage, low current

Statement (B) : Transformer works on both ac and dc.

A. A is true but B is false

B. Both A and B is true

C. A is false but B is true

D. Both A and B are false

Answer: 1



Watch Video Solution

61. To reduce the iron losses in a transformer, the core must be made of a material having

A. low permeability and high resistivity

B. high permeability and high resistivity

C. low permeability and low resistivity

D. high permeability and low resistivity

Answer: 2



Watch Video Solution

62. Maximum efficiency of a transformer depends on

A. the working conditions of technicians.

B. weather copper loss = $1/2x$ irons loss

C. weather copper loss = iron loss

D. weather copper loss = $2x$ iron loss

Answer: 3



Watch Video Solution

63. For an LCR series circuit with an aac source of angular frequency ω .

A. circuit will be capactive if $\omega > \frac{1}{\sqrt{LC}}$

B. circuit will be inductive if $\omega = \frac{1}{\sqrt{LC}}$

C. power factor of circuit will be unity of capacitive reactance equal inductive reactance

D. current will be leading voltage if

$$\omega > \frac{1}{\sqrt{LC}}$$

Answer: 3



Watch Video Solution

64. The value of current in two series LCR circuits at resonance is same, then

A. both circuits must be having same value of capacitance and inductance

B. in both circuits ratio of L and C will be same

C. for both the circuit X_L/X_C must be same at the frequency

D. both circuits must have same impedance at all frequencies


Answer: 3



Watch Video Solution

65. When an ac source of emf $e = E_0 \sin(100t)$ is connected across a circuit, the phase difference between emf e and current I in the circuit is observed to be $(\pi)/4$ as shown in fig. If the circuit consists possibly only of R-C or R-C of L-R series, find the relationship find the

relationship between the two elements.

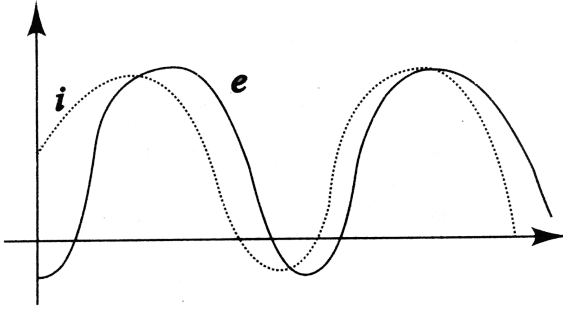

- A. $R = 1k\Omega, C = 10\mu F$
- B. $R = 1k\Omega, C = 1\mu F$
- C. $R = 1k\Omega, L = 10H$
- D. $R = k\Omega, L = 1H$

Answer: 1



66. An AC voltage source of variable angular frequency (ω) and fixed amplitude V_0 is connected in series with a capacitance C and an electric bulb of resistance R (inductance zero).

When (ω) is increased

A. the bulb glows dimmer

B. the bulb glows brighter

C. total impedance of the circuits is

unchanged

D. total impedance of the circuit increases

Answer: 2



Watch Video Solution

67. In an ac circuit the current



Watch Video Solution

68. The average emf during the positive half cycle of an ac supply of peak value E_0 is .



[Watch Video Solution](#)

69. Alternating current is transmitted to distant places at



[Watch Video Solution](#)

70. In case of *a. c* circuit, Ohm's law holds good for

- a) Peak values of voltage and current
- b) Effective values of voltage and current
- c) Instantaneous values of voltage and current



[Watch Video Solution](#)

71. In case of AC circuits the relation $V = iZ$, where Z is impedance, can directly applied to



[Watch Video Solution](#)

72. Alternating current can not be measured by D.C. Ammeter because



[Watch Video Solution](#)

73. The r.m.s value of Potential due to superposition of given two alternating potentials $E_1 = E_0 \sin \omega t$ and $E_2 = E_0 \cos \omega t$ will be



[Watch Video Solution](#)

74. If the instantaneous current in a circuit is given by $I = 2 \cos(\omega t + \phi)A$, the rms value of the current is



[Watch Video Solution](#)

75. If a capacitor is connected to two different A. C generators, then the value of capacitive reactance is



Watch Video Solution

76. In general in an alternating current circuit



Watch Video Solution

77. The magnitude induced e.m.f. in an LR circuit at break of circuit as compared to its value at make of circuit will be



[Watch Video Solution](#)

78. The emf and current in a circuit are such that $E = E_0 \sin \omega t$ and $I = I_0 \sin(\omega t - \theta)$. This AC circuit contains



[Watch Video Solution](#)

79. Same current is flowing in two alternating circuits. The first circuit contains only inductances and the other contains only a capacitor, if the frequency of the e.m.f of AC is increased, the effect on the value of the current will be



Watch Video Solution

80. When an a.c source is connected across a resistor



Watch Video Solution

81. The phase angle between current and voltage in a purely inductive circuit is



Watch Video Solution

82. Ratio of impedance to capacitive reactance has



Watch Video Solution

83. An inductor-coil having some resistance is connected to an AC source. Which of the following quantities have zero average value over a cycle?



Watch Video Solution

84. Why the current does not rise immediately in a circuit containing inductance



Watch Video Solution

85. In an AC circuit containing only capacitance the current



Watch Video Solution

86. A bulb is connected first with DC and the then AC of same voltage then it will shine brightly with



Watch Video Solution

87. A capacitor of capacity C is connected in A. C circuit. If the applied emf is $V = V_0 \sin \omega t$, then the current is



Watch Video Solution

88. At low frequency a condenser offers



Watch Video Solution

89. Statement (A) : The reactance offered by an inductance in *A.C.* Circuit decreases with increase of *AC* frequency

Statement (B) : The reactance offered by capacitor in *AC* circuit increases with increase of *AC* frequency.



Watch Video Solution

90. Statement (A) : With increase in frequency of *AC* supply inductive reactance increases.

Statement (B) : With increase in frequency of AC supply capacitive reactance increase



[Watch Video Solution](#)

91. In an A.C circuit having resistance and capacitance



[Watch Video Solution](#)

92. Select the correct options among the following In an $R - C$ circuit

(a) instantaneous A.C is given by

$$I = I_0 \sin(\omega t + \phi)$$

(b) the alternating current in the circuit leads the emf by a phase angle ϕ .

(c) Its impedance is $\sqrt{R^2 + (\omega C)^2}$

(d) Its capacitive reactance is ωC



[Watch Video Solution](#)

93. If the frequency of alternating e.m.f. is in $L - C - R$ circuit, then the value of impedance Z will change with \log (frequency) as



[Watch Video Solution](#)

 [Watch Video Solution](#)

94. An inductance and a resistance are connected in series with an AC potential . In this circuit



[Watch Video Solution](#)

95. An *LCR* circuit is connected to a source of alternating current. At resonance, the applied voltage and the current flowing through the circuit will have a phase difference of



[Watch Video Solution](#)

96. The incorrect statement for $L - R - C$ series circuit is



[Watch Video Solution](#)

97. In series $L - C - R$ resonant circuit, to increase the resonant frequency



[Watch Video Solution](#)

98. In an LCR series ac circuit the voltage across L , C and R are V_1 , V_2 and V_3 respectively

The voltage of the source is .



Watch Video Solution

99. In the non-resonant circuit, what will be the nature of the circuit for frequencies heigher than the resonant frequency?



Watch Video Solution

100. The phase difference between voltage and current in an *LCR* series circuit is



Watch Video Solution

101. In an *LCR* a.c. circuit at resonance, the current



Watch Video Solution

102. An inductance L and capacitance C and resistance R are connected in series across an AC source of angular frequency ω . If $\omega^2 > \frac{1}{LC}$ then



Watch Video Solution

103. Consider the following two statements A and B and identify the correct answer.

A) At resonance of $L - C$ series circuit, the reactance of circuit is minimum.

B) The reactance of a capacitor is an A.C

circuit is similar to the reactance of a capacitor
in a *D. C* circuit



[Watch Video Solution](#)

104. Choose the wrong statement of the
following



[Watch Video Solution](#)

105. The essential difference between a *d. c*
dynamo and an *a. c* dynamo is that



[Watch Video Solution](#)

106. The unit of impedance is



[Watch Video Solution](#)

107. The power factor of an AC circuit having resistance (R) and inductance (L) connected in series and an angular velocity ω is



[Watch Video Solution](#)

108. The capacitor offers zero resistance to



Watch Video Solution

109. Power factor is defined as



Watch Video Solution

110. The core of transformer is laminated so
that



Watch Video Solution

111. A step up transformer is used to



Watch Video Solution

112. A transformer changes the voltage



Watch Video Solution

113. A step up transformer is connected on the primary side to a rechargeable battery which

can deliver a large current. If a bulb is connected in the secondary, then



[Watch Video Solution](#)

114. The ratio of primary voltage to secondary voltage in a transformer is ' n '. The ratio of the primary current to secondary current in the transformer is



[Watch Video Solution](#)

115. In a step down transformer, the number of turns in the primary is always



Watch Video Solution

116. The transformer ratio of a step up transformer is



Watch Video Solution

117. A setup transformer develops $440V$ in secondary coil for an input of $200VA$. C Then the type of transformer is



[Watch Video Solution](#)

118. Assertion (A) : If changing current is flowing through a machine with iron parts, results in loss of energy.

Reason (R) : Changing magnetic flux through an area of the iron parts causes eddy currents.



[Watch Video Solution](#)

[Watch Video Solution](#)

119. Transformers are used



[Watch Video Solution](#)

120. The magnitude of the e.m.f. across the secondary of a transformer does not depend on



[Watch Video Solution](#)

121. For an ideal transformer ratio of output to the input power is always



Watch Video Solution

122. Consider the following two statements A and B and identify the correct answer.

(A) In a transformer a large alternating current at low voltage can be transformed into a small alternating current at high voltage

(B) Energy in current carrying coil is stored in the form of magnetic field.



[Watch Video Solution](#)

123. Statement (A) : Flux leakage in a transformer can be minimized by winding the primary and secondary coils one over the other.
Statement (B) : Core of the transformer is made of soft iron



[Watch Video Solution](#)

124. Statement (A) : In high current low voltage windings of a transformer thick wire is used to

minimize energy loss due to heat produced

Statement (B) : The core of any transformer is laminated so as to reduce the energy loss due to eddy currents.



[Watch Video Solution](#)

125. Statement (A) : Step up transformer converts low voltage, high current to high voltage, low current

Statement (B) : Transformer works on both ac and dc.



 [Watch Video Solution](#)

126. To reduce the iron losses in a transformer, the core must be made of a material having

 [Watch Video Solution](#)

127. Maximum efficiency of a transformer depends on

 [Watch Video Solution](#)

128. For an LCR series circuit with an aac source of angular frequency ω .




Watch Video Solution

129. The value of current in two series *LCR* circuits at resonance is same when connected across a sinusodial voltage source. Then:



Watch Video Solution

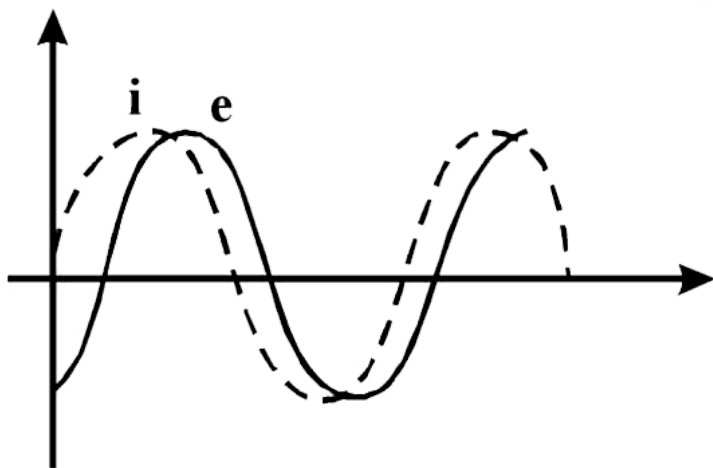130. When an AC source of $emf = E_0 \sin(100t)$ is connected across a circuit, the phase difference between the emf e and the current i in the circuit is observed to be $(\pi/4)$, as shown in the diagram. If the circuit consists possibly only of R-C or R-L or L-C in series, find the relationship between the two elements



 [Watch Video Solution](#)

131. An AC voltage source of variable angular frequency (ω) and fixed amplitude V_0 is connected in series with a capacitance C and an electric bulb of resistance R (inductance zero).
When (ω) is increased



[Watch Video Solution](#)

132. In an ac circuit the current



[Watch Video Solution](#)

133. The average emf during the positive half cycle of an ac supply of peak value E_0 is .



Watch Video Solution

134. Alternating current is transmitted to distant places at



Watch Video Solution

135. In case of *a. c* circuit, Ohm's law holds good for

- a) Peak values of voltage and current
- b) Effective values of voltage and current
- c) Instantaneous values of voltage and current



Watch Video Solution

136. In case of *AC* circuits the relation $V = iZ$, where Z is impedance, can directly applied to



Watch Video Solution

137. Alternating current can not be measured by D.C. Ammeter because



Watch Video Solution

138. The r.m.s value of Potential due to superposition of given two alternating potentials $E_1 = E_0 \sin \omega t$ and $E_2 = E_0 \cos \omega t$ will be



Watch Video Solution

139. If the instantaneous current in a circuit is given by $i = 2\cos(\omega t - \phi)$ ampere, the r.m.s. value of the current is



Watch Video Solution

140. If a capacitor is connected to two different A. C generators, then the value of capacitive reactance is



Watch Video Solution

141. In general in an alternating current circuit



Watch Video Solution

142. The magnitude inducted e.m.f. in an LR circuit at break of circuit as compared to its value at make of circuit will be



Watch Video Solution

143. The emf and current in a circuit are such that $E = E_0 \sin \omega t$ and $I = I_0 \sin(\omega t - \theta)$. This AC circuit contains



Watch Video Solution

144. The correct variation of resistance R with frequency f is given by



Watch Video Solution

145. Same current is flowing in two alternating circuits. The first circuit contains only inductances and the other contains only a capacitor, if the frequency of the e.m.f of AC is increased, the effect on the value of the current will be



Watch Video Solution

146. When an a.c source is connected across a resistor



Watch Video Solution

[Watch Video Solution](#)

147. The phase angle between current and voltage in a purely inductive circuit is



[Watch Video Solution](#)

148. Ratio of impedance to capacitive reactance has



[Watch Video Solution](#)

149. An inductor-coil having some resistance is connected to an AC source. Which of the following quantities have zero average value over a cycle?



Watch Video Solution

150. Why the current does not rise immediately in a circuit containing inductance



Watch Video Solution

151. In an AC circuit containing only capacitance the current



Watch Video Solution

152. A bulb is connected first with DC and then AC of same voltage then it will shine brightly with



Watch Video Solution

153. A capacitor of capacity C is connected in A. C circuit. If the applied emf is $V = V_0 \sin \omega t$, then the current is



Watch Video Solution

154. At low frequency a condenser offers



Watch Video Solution

155. Statement (A) : The reactance offered by an inductance in *A.C.* Circuit decreases with increase of *AC* frequency

Statement (B) : The reactance offered by capacitor in *AC* circuit increases with increase of *AC* frequency.



Watch Video Solution

156. Statement (A) : With increase in frequency of *AC* supply inductive reactance increases.

Statement (B) : With increase in frequency of AC supply capacitive reactance increase



[Watch Video Solution](#)

157. In an A.C circuit having resistance and capacitance



[Watch Video Solution](#)

158. Select the correct options among the following In an $R - C$ circuit

(a) instantaneous A.C is given by

$$I = I_0 \sin(\omega t + \phi)$$

(b) the alternating current in the circuit leads the emf by a phase angle ϕ .

(c) Its impedance is $\sqrt{R^2 + (\omega C)^2}$

(d) Its capacitive reactance is ωC



[Watch Video Solution](#)

159. If the frequency of alternating e.m.f. is in $L - C - R$ circuit, then the value of impedance Z will change with \log (frequency) as



[Watch Video Solution](#)

 [Watch Video Solution](#)

160. An inductance and a resistance are connected in series with an AC potential . In this circuit



[Watch Video Solution](#)

161. An LCR circuit is connected to a source of alternating current. At resonance, the applied voltage and the current flowing through the circuit will have a phase difference of



[Watch Video Solution](#)

162. The incorrect statement for $L - R - C$ series circuit is



[Watch Video Solution](#)

163. In series $L - C - R$ resonant circuit, to increase the resonant frequency



[Watch Video Solution](#)

164. If in a series L-C-R ac circuit, the voltages across R,L,C are V_1 , V_2 , V_3 respectively. Then the voltage of applied AC source is always equal to



Watch Video Solution

165. In the non-resonant circuit, what will be the nature of the circuit for frequencies heigher than the resonant frequency?



Watch Video Solution

166. The phase difference between voltage and current in an *LCR* series circuit is



Watch Video Solution

167. In an *LCR* a.c. circuit at resonance, the current



Watch Video Solution

168. An inductance L and capacitance C and resistance R are connected in series across an AC source of angular frequency ω . If $\omega^2 > \frac{1}{LC}$ then



Watch Video Solution

169. Consider the following two statements A and B and identify the correct answer.

A) At resonance of $L - C$ series circuit, the reactance of circuit is minimum.

B) The reactance of a capacitor is an A.C

circuit is similar to the reactance of a capacitor
in a *D. C* circuit



[Watch Video Solution](#)

170. Choose the wrong statement of the
following



[Watch Video Solution](#)

171. The essential difference between a *d. c*
dynamo and an *a. c* dynamo is that



[Watch Video Solution](#)

172. The unit of impedance is



[Watch Video Solution](#)

173. The power factor of an AC circuit having resistance (R) and inductance (L) connected in series and an angular velocity ω is



[Watch Video Solution](#)

174. The capacitor offers zero resistance to



Watch Video Solution

175. Power factor is defined as



Watch Video Solution

176. The core of transformer is laminated so
that



Watch Video Solution

177. A step up transformer is used to



Watch Video Solution

178. A transformer changes the voltage



Watch Video Solution

179. A step up transformer is connected on the primary side to a rechargeable battery which

can deliver a large current. If a bulb is connected in the secondary, then



[Watch Video Solution](#)

180. The ratio of primary voltage to secondary voltage in a transformer is ' n '. The ratio of the primary current to secondary current in the transformer is



[Watch Video Solution](#)

181. In a step down transformer, the number of turns in the primary is always



Watch Video Solution

182. The transformer ratio of a step up transformer is



Watch Video Solution

183. A setup transformer develops $440V$ in secondary coil for an input of $200VA$. C Then the type of transformer is



[Watch Video Solution](#)

184. Assertion (A) : If changing current is flowing through a machine with iron parts, results in loss of energy.

Reason (R) : Changing magnetic flux through an area of the iron parts causes eddy currents.



[Watch Video Solution](#)

[Watch Video Solution](#)

185. Transformers are used



[Watch Video Solution](#)

186. The magnitude of the e.m.f. across the secondary of a transformer does not depend on



[Watch Video Solution](#)

187. For an ideal transformer ratio of output to the input power is always



Watch Video Solution

188. Consider the following two statements A and B and identify the correct answer.

(A) In a transformer a large alternating current at low voltage can be transformed into a small alternating current at high voltage

(B) Energy in current carrying coil is stored in the form of magnetic field.



[Watch Video Solution](#)

189. Statement (A) : Flux leakage in a transformer can be minimized by winding the primary and secondary coils one over the other.
Statement (B) : Core of the transformer is made of soft iron



[Watch Video Solution](#)

190. Statement (A) : In high current low voltage windings of a transformer thick wire is used to

minimize energy loss due to heat produced

Statement (B) : The core of any transformer is laminated so as to reduce the energy loss due to eddy currents.



[Watch Video Solution](#)

191. Statement (A) : Step up transformer converts low voltage, high current to high voltage, low current

Statement (B) : Transformer works on both ac and dc.



[Watch Video Solution](#)



[Watch Video Solution](#)

192. To reduce the iron losses in a transformer, the core must be made of a material having



[Watch Video Solution](#)

193. Maximum efficiency of a transformer depends on



[Watch Video Solution](#)

194. For an LCR series circuit with an aac source of angular frequency ω .




Watch Video Solution

195. The value of current in two series *LCR* circuits at resonance is same when connected across a sinusodial voltage source. Then:



Watch Video Solution

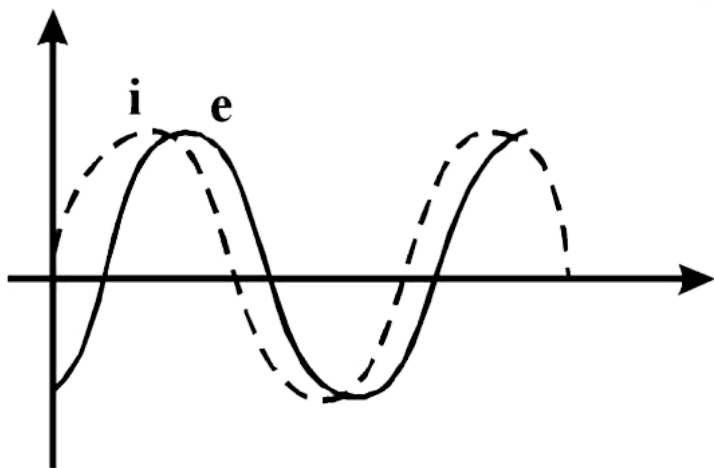196. When an AC source of $emf = E_0 \sin(100t)$ is connected across a circuit, the phase difference between the emf e and the current i in the circuit is observed to be $(\pi/4)$, as shown in the diagram. If the circuit consists possibly only of R-C or R-L or L-C in series, find the relationship between the two elements



 [Watch Video Solution](#)

197. An AC voltage source of variable angular frequency (ω) and fixed amplitude V_0 is connected in series with a capacitance C and an electric bulb of resistance R (inductance zero).
When (ω) is increased



[Watch Video Solution](#)

Assertion & Reason

1. Assertion (A) : The average value of $\langle \sin^2 \omega t \rangle$ is zero.

Reason (R) : The average value of function $F(t)$

over a period T is $\langle F(t) \rangle = \frac{1}{T} \int_0^T F(t) dt$

A. Both Assertion and Reason are true and

Reason is the correct explanation of

Assertion.

B. Both Assertion and Reason are true but

Reason is not the correct explanation of

Assertion.

C. Assertion is true but Reason is false

D. Assertion is false but Reason is true

Answer: 4



Watch Video Solution

2. Assertion (A) : If current varies sinusoidally the average power consumed in a cycle is zero.

Reason (R) : If current sinusoidally the average power consumed is zero

A. Both Assertion and Reason are true and Reason is the correct explanation of Assertion.

B. Both Assertion and Reason are true but Reason is not the correct explanation of Assertion.

C. Assertion is true but Reason is false

D. Assertion is false but Reason is true

Answer: 4



Watch Video Solution

3. Assertion (A) : The power consumed in an electric circuit is never negative

Reason (R) : The average power consumed in an

electric circuit is $P = \frac{V^2}{R} = I^2R$

A. Both Assertion and Reason are true and

Reason is the correct explanation of

Assertion.

B. Both Assertion and Reason are true but

Reason is not the correct explanation of

Assertion.

C. Assertion is true but Reason is false

D. Assertion is false but Reason is true

Answer: 1



Watch Video Solution

4. Assertion (A) : The inductive reactance limits the currents in a purely inductive circuit in the same way as the resistance in a resistive circuit.

Reason (R) : The inductive reactance is directly

proportional to the inductance and to the frequency of the varying current.

A. Both Assertion and Reason are true and

Reason is the correct explanation of Assertion.

B. Both Assertion and Reason are true but

Reason is not the correct explanation of Assertion.

C. Assertion is true but Reason is false

D. Assertion is false but Reason is true

Answer: 2



Watch Video Solution

5. Assertion (A) : An ac emf which oscillates symmetrically about zero, the current it sustains also oscillates symmetrically about zero.

Reason (R) : In any circuit element, current is always in the phase with voltage

A. Both Assertion and Reason are true and Reason is the correct explanation of Assertion.

B. Both Assertion and Reason are true but Reason is not the correct explanation of Assertion.

C. Assertion is true but Reason is false

D. Assertion is false but Reason is true

Answer: 4



Watch Video Solution

6. Assertion (A) : A lamp is connected in series with a capacitor and ac source connected across their terminal consequently current flow in the circuit and the lamp will shine.

Reason (R) : Capacitor block dc current and allow ac current

A. Both Assertion and Reason are true and Reason is the correct explanation of Assertion.

B. Both Assertion and Reason are true but Reason is not the correct explanation of Assertion.

C. Assertion is true but Reason is false

D. Assertion is false but Reason is true

Answer: 1



Watch Video Solution

7. Assertion (A) : An electric lamp is connected in series with a long solenoid of copper with air

core and then connected to *AC* source. If an iron rod is inserted in solenoid the lamp will become dim.

Reason (R) : If iron rod is inserted in solenoid, the induction of solenoid increases.

A. Both Assertion and Reason are true and

Reason is the correct explanation of Assertion.

B. Both Assertion and Reason are true but

Reason is not the correct explanation of Assertion.

C. Assertion is true but Reason is false

D. Assertion is false but Reason is true

Answer: 1



Watch Video Solution

8. An inductor, a capacitor, and a resistor are connected in series. The combination is connected across an ac source.

Statement 1: Peak current through each remains same.

Statement 2: Average power delivered by source is equal to average power developed across resistance.

- A. Both Assertion and Reason are true and Reason is the correct explanation of Assertion.
- B. Both Assertion and Reason are true but Reason is not the correct explanation of Assertion.
- C. Assertion is true but Reason is false
- D. Assertion is false but Reason is true

Answer: 2



Watch Video Solution

9. Assertion: When frequency is greater than resonance frequency in a series LCR circuit, it will be an inductive circuit.

Reason : Resultant voltage will lead the current.

A. Both Assertion and Reason are true and

Reason is the correct explanation of

Assertion.

B. Both Assertion and Reason are true but Reason is not the correct explanation of Assertion.

C. Assertion is true but Reason is false

D. Assertion is false but Reason is true

Answer: 1



Watch Video Solution

10. Assertion (A) : Maximum power is dissipated in a circuit (through R) in resonance

Reason (R) : At resonance in a series *LCR* circuit, the voltage across inductor and capacitor are out phase.

- A. Both Assertion and Reason are true and Reason is the correct explanation of Assertion.
- B. Both Assertion and Reason are true but Reason is not the correct explanation of Assertion.
- C. Assertion is true but Reason is false
- D. Assertion is false but Reason is true

Answer: 1



Watch Video Solution

11. Statement 1: Both dc and ac can be measured by a hot wire instrument.

Statement 2: the hot wire instrument is based on the principle of magnetic effect of current.

A. Both Assertion and Reason are true and Reason is the correct explanation of Assertion.

B. Both Assertion and Reason are true but Reason is not the correct explanation of Assertion.

C. Assertion is true but Reason is false

D. Assertion is false but Reason is true

Answer: 3



Watch Video Solution

12. Assertion (A) : The electrostatic energy stored in capacitor plus magnetic energy

stored in inductor will always be zero in series *LCR* circuit driven by ac voltage source under condition of resonance.

Reason (R) : The complete voltage of ac source appears across the resistor in a series *LCR* circuit driven by ac voltage source under condition of resonance.

A. Both Assertion and Reason are true and Reason is the correct explanation of Assertion.

B. Both Assertion and Reason are true but Reason is not the correct explanation of Assertion.

C. Assertion is true but Reason is false

D. Assertion is false but Reason is true

Answer: 4



Watch Video Solution

13. Assertion (A) : The r.m.s value of alternating current is defined as the square root of the

average of I^2 during a complete cycle.

Reason (R) : For sinusoidal a.c.

$$\left(I = I_0 \sin \omega t \right) I_{\text{rms}} = \frac{I_0}{\sqrt{2}}$$

A. Both Assertion and Reason are true and

Reason is the correct explanation of

Assertion.

B. Both Assertion and Reason are true but

Reason is not the correct explanation of

Assertion.

C. Assertion is true but Reason is false

D. Assertion is false but Reason is true

Answer: 2



Watch Video Solution

14. Assertion: In series LCR circuit resonance can take place.

Reason: Resonance takes place if inductance and capacitive reactance are equal and opposite.

A. Both Assertion and Reason are true and Reason is the correct explanation of Assertion.

B. Both Assertion and Reason are true but Reason is not the correct explanation of Assertion.

C. Assertion is true but Reason is false

D. Assertion is false but Reason is true

Answer: 1



Watch Video Solution

LEVEL - I (C.W)

1. The r.m.s value of an a.c of 59Hz is 10A . The time taken by the alternating current in reaching from zero to maximum value and the peak value of current will be

A. $2 \times 10^{-2}\text{sec}$ and 14.14A

B. $1 \times 10^{-2}\text{sec}$ and 7.07A

C. $5 \times 10^{-3}\text{sec}$ and 7.07A

D. $5 \times 10^{-3}\text{sec}$ and 14.14A

Answer: 4



Watch Video Solution

2. An inductor has a resistance R inductance L . It is connected to an *A.C* source of e.m.f. E_V and angular frequency ω then the current I_V in the circuit is

A. $\frac{E_V}{\omega L}$

B. $\frac{E_V}{R}$

$$\text{C. } \frac{E_V}{\sqrt{R^2 + \omega^2 L^2}}$$

$$\text{D. } \sqrt{\left(\frac{E_V}{R}\right)^2 + \left(\frac{E_V}{\omega L}\right)^2}$$

Answer: 3



Watch Video Solution

3. The peak value of AC mains (in volt) is

A. 155.6

B. 220.0

C. 311

D. 440.0

Answer: 3



Watch Video Solution

4. The peak value A.C is $2\sqrt{2}A$. It's apparent value will be

A. $1A$

B. $2A$

C. 4A

D. zero

Answer: 2



Watch Video Solution

5. Alternating current in circuit is given by

$I = I_0 \sin 2\pi nt$. Then the time by the current to

rise from zero to r.m.s value is equal to

A. $1/2n$

B. $1/n$

C. $1/4n$

D. $1/8n$

Answer: 4



Watch Video Solution

6. Using an ac voltmeter, the potential difference in the electrical line in a house is read to be 234 V. If the line frequency is known

to be 50 cycles per second, the equation for the line voltage is

A. $V = 165\sin(100\pi t)$

B. $V = 331\sin(100\pi t)$

C. $V = 220\sin(100\pi t)$

D. $V = 440\sin(100\pi t)$

Answer: 2



Watch Video Solution

7. A mixer of 100Ω resistance is connected to an A.C source of $200V$ and 50cycles/sec . The value of average potential difference across the mixer will be

A. $308V$

B. $264V$

C. $220V$

D. zero

Answer: 4



Watch Video Solution

8. The equation of an alternating voltage is $E = 220\sin(\omega t + \pi/6)$ and the equation of the current in the circuit is $I = 10\sin(\omega t - \pi/6)$. Then the impedance of the circuit is

A. 10 ohm

B. 22 ohm

C. 11 ohm

D. 17 ohm

Answer: 2



Watch Video Solution

9. A steady *P. D* of $10V$ produces heat at a rate ' x ' in resistor. The peak value of *A. C* voltage which will produce heat at rate of $x/2$ in same resistor is

A. $5V$

B. $5\sqrt{2}$

C. $10V$

D. $10\sqrt{2}V$

Answer: 3



Watch Video Solution

10. An alternating voltage $E = 200\sqrt{2}\sin(100t)V$ is connected to a $1\mu F$ capacitor through an ac ammeter (it reads rms value). What will be the reading of the ammeter?

A. $10mA$

B. $40mA$

C. $80mA$

D. 20mA

Answer: 4



Watch Video Solution

11. A 120 volt *AC* source is connected across a pure inductor of inductance 0.70 henry. If the frequency of the source is 60Hz , the current passing through the inductor is

A. 4.55A

B. 0.355A

C. 0.455A

D. 3.55A

Answer: 3



Watch Video Solution

12. A transformer steps an *A. C* voltage from 230V to 2300V. If the number of turns in the secondary coil is 1000, the number of turns in the primary coil will be

A. 100

B. 10, 000

C. 500

D. 1000

Answer: 1



Watch Video Solution

13. The transformer ratio of a transformer is 5.

If the primary voltage of the transformer is

400V, 50Hz the secondary voltage will be

A. 2000V, 250Hz

B. 80V, 50Hz

C. 80V, 10Hz

D. 2000V, 50Hz

Answer: 4



Watch Video Solution

14. A step-up transformer works on 220V and gives 2A to an external resistor. The turn ratio between the primary and secondary coils is 2 :

25. Assuming 100% efficiency, find the secondary voltage, primary current and power delivered respectively

A. 2750V, 25A, 5500W

B. 2750V, 20A, 5000W

C. 2570V, 25A, 550W

D. 2750V, 20A, 55W

Answer: 1



Watch Video Solution

15. A coil of self-inductance $\left(\frac{1}{\pi}\right)H$ is connected in series with a 300Ω resistance. A voltage of $200V$ at frequency $200Hz$ is applied to this combination. The phase difference between the voltage and the current will be

A. $\tan^{-1}\left(\frac{4}{3}\right)$

B. $\tan^{-1}\left(\frac{3}{4}\right)$

C. $\tan^{-1}\left(\frac{1}{4}\right)$

D. $\tan^{-1}\left(\frac{5}{4}\right)$

Answer: 1



Watch Video Solution

16. A condenser of $10\mu F$ and an inductor of $1H$ are connected in series with an *A. C* source of frequency $50Hz$. The impedance of the combination will be (take $\pi^2 = 10$)

A. zero

B. Inifnity

C. 44.7Ω

D. 5.67Ω

Answer: 1



Watch Video Solution

17. A 100km telegraph wire hasd capacity of $0.02\mu\text{F}/\text{km}$, if it carries an alternating current of frequency 5kHZ . The value of an inductrance required to be connected in series so that the impedance is minimum.

A. 50.7mH

B. $5.07mH$

C. $0.507mH$

D. $507mH$

Answer: 3



Watch Video Solution

18. In an LCR series circuit the rms voltages across R , L and C are found to be $10V$, $10V$ and $20V$ respectively. The rms voltage across the entire combination is

A. $30V$

B. $1V$

C. $20V$

D. $10\sqrt{2}V$


Answer: 4



Watch Video Solution

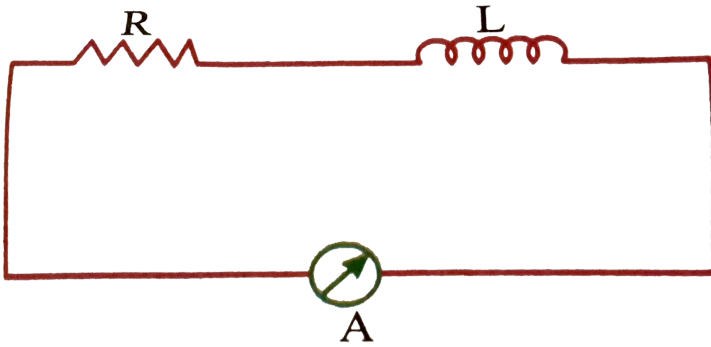19. In the circuit shown, a $30V$ d.c. source gives a current $2.0A$ as recorded in the ammeter A and $30V$ a.c. source of frequency $100Hz$ gives a

current is 1.2 A. The inductive reactance is



A. 10 ohm

B. 20 ohm

C. $5\sqrt{34}$ ohm

D. 40 ohm

Answer: 2



Watch Video Solution

20. A choke coil has negligible resistance. The alternating potential drop across it is 220 volt and the current is 5mA . The power consumed is

A. $220 \times \frac{5}{1000} \text{W}$

B. $\frac{220}{5} \text{W}$

C. zero

D. $2.20 \times 5 \text{W}$

Answer: 3



Watch Video Solution

21. In an AC circuit, the instantaneous values of e.m.f and current are $e = 200\sin 314t$ volt and $i = \sin\left(314t + \frac{\pi}{3}\right)$ ampere. The average power consumed in watt is

A. 200

B. 100

C. 0

D. 50


Answer: 4



Watch Video Solution

22. In a black box of unknown elements (L or R or any other combination), an ac voltage $E = E_0 \sin(\omega t + \phi)$ is applied and current in the circuit was found to be $I = (I_0) \sin[\omega t + \phi + (\pi/4)]$. Then the unknown

elements in the box may be

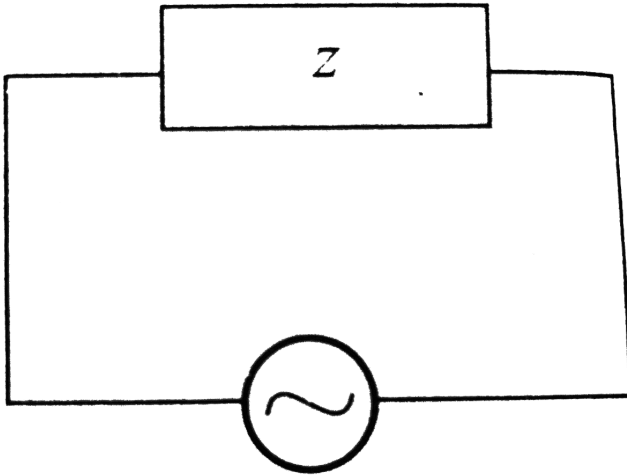

A. only capacitor

B. both inductor and resistor

C. either capacitor, resistor and inductor or


only capacitor and resistor

D. only resistor

Answer: 3

 **Watch Video Solution**

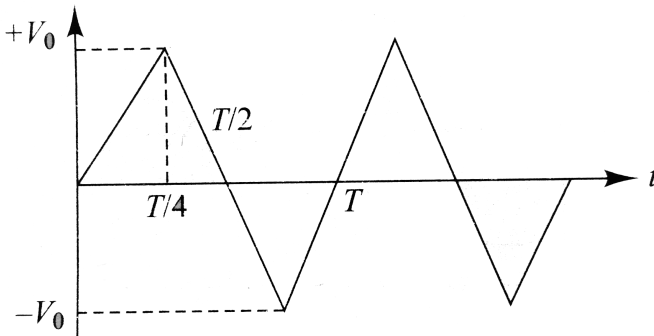23. The voltage time (V-t) graph for triangular wave having peak value (V_0) is as shown in fig.



A. $\frac{V_0}{\sqrt{3}}$

B. $\frac{V_0}{2}$

C. $\frac{V_0}{\sqrt{2}}$

D. $2V_0$

Answer: 1



Watch Video Solution

LEVEL - II (C.W)

1. The average current of a sinusoidally varying alternating current of peak value $5A$ with initial phase zero, between the instants $t = T/8$ to $t = T/4$ is (where ' T ' is time period)

A. $\frac{10}{\pi}\sqrt{2}A$

B. $\frac{5}{\pi}\sqrt{2}A$

C. $\frac{20\sqrt{2}}{\pi}$

D. $\frac{10}{\pi}A$

Answer: 1



Watch Video Solution

2. A 100Ω resistance is connected in series with a $4H$ inductor. The voltage across the resistor is $V_R = 2\sin(1000t)V$. The voltage across the inductors is

A. $80\sin\left(1000t + \frac{\pi}{2}\right)$

B. $40\sin\left(1000t + \frac{\pi}{2}\right)$

C. $80\sin\left(1000t - \frac{\pi}{2}\right)$


D. $40\sin\left(1000\pi - \frac{\pi}{2}\right)$

Answer: 1



Watch Video Solution

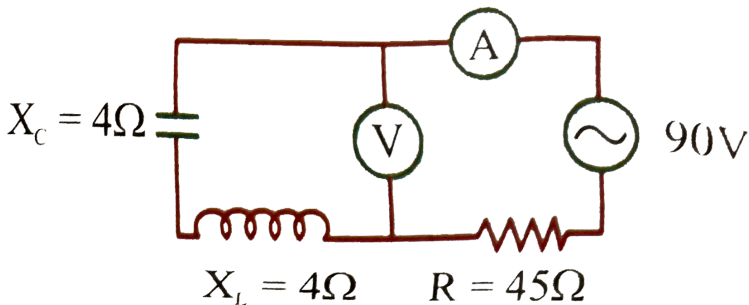3. The reading of voltmeter and ammeter in the following figure will respectively be



A. 0 and 2A

B. 2A and 0V

C. $2V$ and $2A$

D. $0V$ and $0A$


Answer: 1



Watch Video Solution

4. In the following circuit, the value of current flowing in the circuit at $f = 0$ and $f = \infty$ will


respectively be

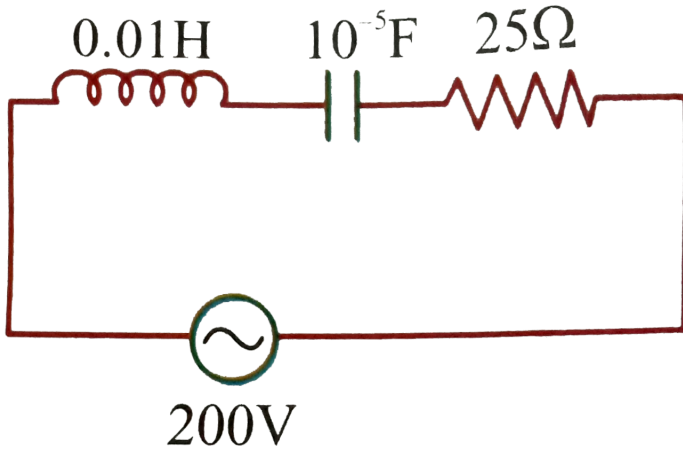

- A. 8A and 0A
- B. 0A and 0A
- C. 8A and 8A
- D. 0A and 8A

Answer: 2

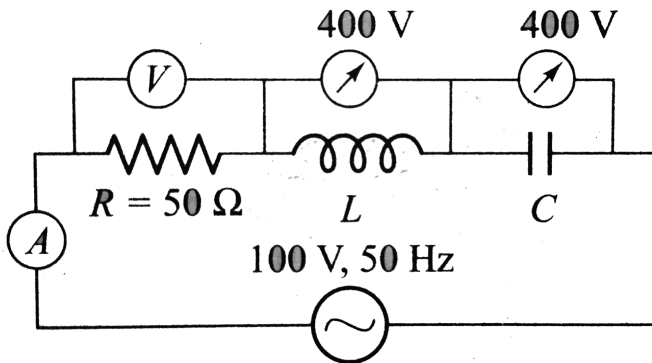5. In the series LCR circuit , the voltmeter and ammeter reading are:



- A. $V = 100$ volt, $I = 2A$
- B. $V = 100$ volt, $I = 5A$
- C. $V = 1000$ volt, $I = 2A$

D. $V = 300 \text{ volt}, I = 1\text{A}$

Answer: 1



Watch Video Solution

6. The potential difference between the ends of a resistance R is V_R , between the ends of capacitor is $V_C = 2V_R$ and between the ends of inductance is $V_L = 3V_R$. Then the alternating potential of the source in terms of V_R will be

A. $\sqrt{2}V_R$

B. V_R

C. $\frac{V_R}{\sqrt{2}}$

D. $5V_R$

Answer: 1



Watch Video Solution

7. A 220-V, 50 Hz, ac generator is connected to an inductor and a 50Ω resistance in series. The current in the circuit is 1.0A. What is the PD across inductor?

A. $102.2V$

B. $186.4V$

C. $213.6V$

D. $302V$


Answer: 3



Watch Video Solution

8. The figure shows variation of R , X_L and X_C with frequency f in a series L, C, R circuit. Then for what frequency point, the circuit is

inductive ?

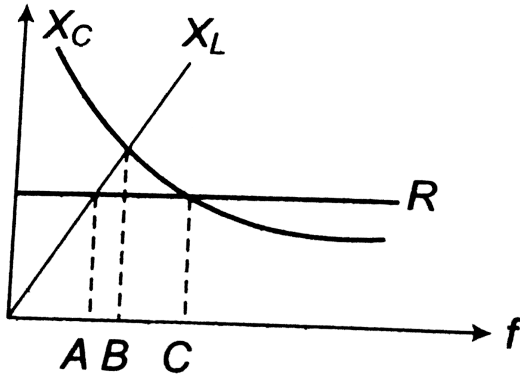

A. A

B. B

C. C


D. All points

Answer: 3




Watch Video Solution

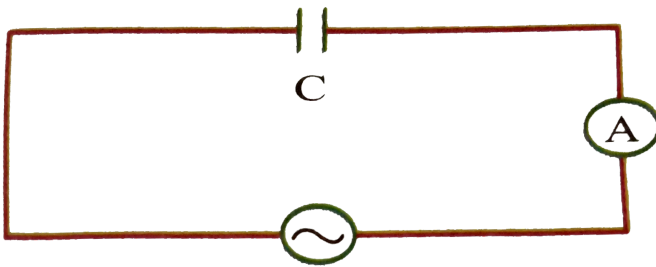
9. A constant voltage at different frequencies is applied across a capacitance C as shown in the figure. Which of the following graphs correctly depicts the variation of current with frequency




A.C. generator

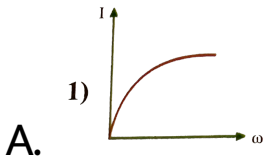


B.

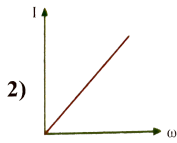

C.

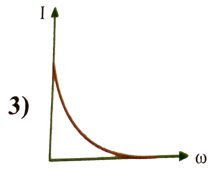

D.

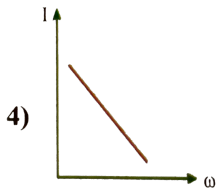

Answer: 2



Watch Video Solution

10. In a series LCR circuit $R = 200(\Omega)$ and the voltage and the frequency of the main supply is 220V and 50 Hz respectively. On taking out the capacitance from the circuit the current lags behind the voltage by 30° . On taking out the inductor from the circuit the current leads the voltage by 30° . The power dissipated in the LCR circuit is

A. 305W

B. 210W

C. zero

D. 242W

Answer: 4



Watch Video Solution

11. In a series resonant LCR circuit the voltage across R is 100 volts and $R = 1k(\Omega)$ with $C = 2(\mu)F$. The resonant frequency (ω) is $200rad/s$. At resonance the voltage across L is

A. $2.5 \times 10^{-2}V$

B. $40V$

C. 250V

D. $4 \times 10^{-3}V$

Answer: 2



Watch Video Solution

LEVEL - III (C.W)

1. An AC voltage source of variable angular frequency (ω) and fixed amplitude V_0 is connected in series with a capacitance C and an

electric bulb of resistance R (inductance zero).

When (ω) is increased

- A. The bulb glows dimmer
- B. The bulb glows brighter
- C. Total impedance of the circuits is unchanged
- D. Total impedance of the circuit increases

Answer: 2



Watch Video Solution

2. In an *A. C* circuit the instantaneous values of current and voltage are $I = 120\sin\omega t$ ampere and $E = 300\sin(\omega t + \pi/3)$ volt respectively.

What will be the inductive reactance of series *LCR* circuit if the resistance and capacitive reactance are 2 ohm and 1 ohm respectively?

- A. 4.5 ohms
- B. 2 ohms
- C. 2.5 ohms
- D. 3 ohms

Answer: 1



Watch Video Solution

3. A pure resistive circuit element ' x ' when connected to an *A.C* supply of peak voltage $100V$ gives a peak current of $4A$ which is in phase with the voltage. A second circuit element ' y ' when connected to the same *AC* supply also gives the same value of peak current but the current lags behind by 90° . If the series combination to of ' x ' and ' y ' is

connected to the same supply. *R. M. S* value of current is

A. $\frac{5}{\sqrt{2}}A$

B. $2A$

C. $1/2A$

D. $\frac{\sqrt{2}}{5}A$

Answer: 2



Watch Video Solution

4. An ideal inductor takes a current of $10A$ when connected to a $125V, 50HzAC$ supply, A pure resistor across the same source takes $12.5A$. If the two are connected in series across a $100\sqrt{2}V, 40Hz$ supply, the current through the circuit will be

A. $10A$

B. $12.5A$

C. $20A$

D. $25A$

Answer: 1



Watch Video Solution

5. A circuit containing resistance R_1 , Inductance L_1 and capacitance C_1 connected in series resonates at the same frequency n' as a second combination of R_2, L_2 and C_2 . If the two are connected in series. Then the circuit will resonate at

A. n

B. $2n$

C. $\sqrt{\frac{L_2 C_2}{L_1 C_1}}$

D. $\sqrt{\frac{L_1 C_1}{L_2 C_2}}$

Answer: 1



Watch Video Solution

6. An AC source of variable frequency is applied across a series $L - C - R$ circuit. At a frequency double the resonance frequency. The impedance

is $\sqrt{10}$ times the minimum impedance. . The inductive reactance is

A. R

B. $2R$

C. $3R$

D. $4R$

Answer: 4



Watch Video Solution

7. A 750Hz , 20V source is connected to a resistance of 100Ω , an inductance of 0.1803H and a capacitance of $10\mu\text{F}$ all in series. Calculate the time in which the resistance (thermal capacity $2\text{J}/^\circ\text{C}$) will get heated by 10°C .

A. 328 sec

B. 348 sec

C. 3.48 sec

D. 4.32 sec

Answer: 2



Watch Video Solution

8. An ac source of angular frequency ω is fed across a resistor R and a capacitor C in series. The current registered is I . If now the frequency of source is changed to $\omega/3$ (but maintaining the same voltage), the current in the circuit is found to be halved. Calculate the ratio of the reactance to resistance at the original frequency ω .

A. $\sqrt{\frac{3}{5}}$

B. $\sqrt{\frac{5}{3}}$

C. $\frac{3}{5}$

D. $\frac{5}{3}$

Answer: 1



Watch Video Solution

9. An LCR circuit has $L = 10mL$, $R = 3\Omega$, and $C = 1\mu F$ connected in series to a source of

$15\cos\omega t$ volt. The current amplitude at a frequency that is 10% lower than the resonant frequency is

A. 0.5A

B. 0.7A

C. 0.9A


D. 1.1A

Answer: 2



Watch Video Solution

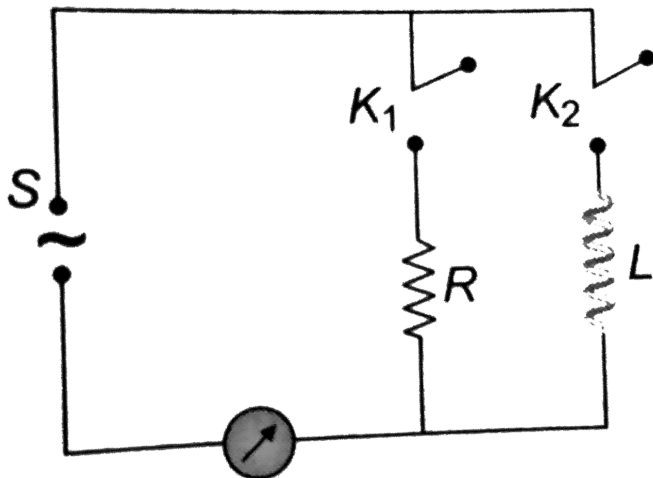10. In the circuit shown, R is a pure resistor, L is an inductor of negligible resistance (as compared to R) and S is a 100V , 50HzAC source of negligible resistance. With either key k_1 alone or k_2 alone closed, the current is I_0 . if the source is changed to 100V , 100Hz , the current with k_1 alone closed and with k_2 alone closed will be respectively



A. $I, I/2$

B. $I, 2I$

C. $2I, I$

D. $2I, I/2$

Answer: 1



Watch Video Solution

11. A capacitor has a resistance of $1200M\Omega$ and capacitance of $22\mu F$. When connected to an a.c. supply of frequency 80 hertz, then the

alternating voltage supply required to drive a current of 10 virtual ampere is

A. $904\sqrt{2}V$

B. $904V$

C. $904\sqrt{2}V$

D. $452V$

Answer: 2



Watch Video Solution

12. A 120V, 60Hz a.c. power is connected 800Ω non-inductive resistance and unknown capacitance in series. The voltage drop across the resistance is found to be 102V, then voltage drop across capacitor is

A. 8V

B. 102V

C. 63V

D. 55V

Answer: 3



Watch Video Solution

13. A $100V$ a.c. source of frequency $50Hz$ is connected to a LCR circuit with $L = 8.1$ millihenry, $C = 12.5\mu F$ and $R = 10$ ohm, all connected in series. What is the potential difference across the resistance?

A. $100V$

B. $200V$

C. $300V$

D. $450V$

Answer: 1



Watch Video Solution

14. A coil has an inductance of $0.7H$ and is joined in series with a resistance of 220Ω . When an alternating e.m.f of $220V$ at 50 c.p.s. is applied to it, then the wattless component of the current in the circuit is

A. 5 ampere

B. 0.5 ampere

C. 0.7 ampere

D. 7 ampere

Answer: 2



Watch Video Solution

15. Two alternating voltage generators produce emfs of the same amplitude (E_0) but with a phase difference of $(\pi)/3$. The resultant emf is

A. $E_0 \sin\left(\omega t + \frac{\pi}{3}\right)$

B. $E_0 \sin\left(\omega t + \frac{\pi}{6}\right)$

C. $\sqrt{3}E_0 \sin\left(\omega t + \frac{\pi}{6}\right)$

D. $\sqrt{3}E_0 \sin\left(\omega + \frac{\pi}{2}\right)$


Answer: 3



Watch Video Solution

16. The potential difference across a $2H$ inductor as a function of time is shown in figure. At time $t = 0$, current is zero

Current $t = 2$ second is

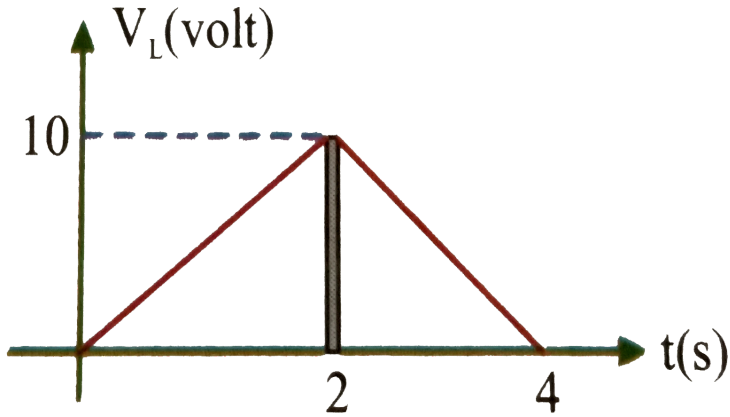

A. 1A

B. 3A

C. 4A

D. 5A


Answer: 4



Watch Video Solution

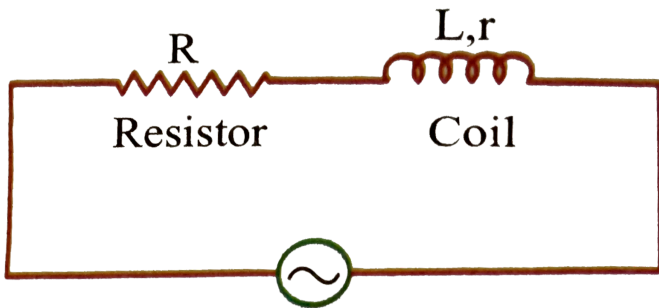17. For the circuit shown in the figure the rms value of voltage across R and coil are E_1 and E_2 respectively.

The power (thermal) developed across the coil is



$$e = E_0 \sin \omega t$$

$$e_{rms} = E$$

$$A. \frac{E - E_1^2}{2R}$$

$$B. \frac{E - E_1^2 - E_2^2}{2R}$$

$$C. \frac{E^2}{2R}$$

$$D. \frac{(E - E_1)^2}{2R}$$

Answer: 2



Watch Video Solution

18. A bulb is rated at 100V, 100W. It can be treated as a resistor. Find out the inductance of

an inductor (called choke coil) that should be connected in series with the bulb at its rated power with the help of an ac source of 200V and 50Hz.

A. $\frac{\pi}{\sqrt{3}}H$

B. $100H$

C. $\frac{\sqrt{2}}{\pi}H$

D. $\frac{\sqrt{3}}{\pi}H$

Answer: 4




Watch Video Solution

19. In the circuit shown in fig.

$X_C = 100\Omega$, $(X_L) = 200\Omega$ and $R = 100\Omega$. The

effective current through the source is

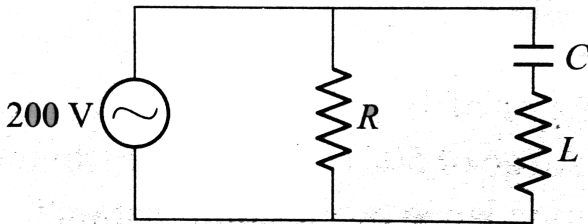

A. $2A$

B. $2\sqrt{2}A$

C. $0.5A$

D. $\sqrt{0.4}A$

Answer: 2



Watch Video Solution

20. When the rms voltages V_L , V_C and V_R are measured respectively across the inductor L , the capacitor C and the resistor R in a series LCR circuit connected to an AC source, it is found that the ratio $V_L : V_C : V_R = 1 : 2 : 3$. If the rms voltage of the AC sources is $100V$, the V_R is close to:

A. 50V

B. 70V

C. 90V

D. 100V

Answer: 3



Watch Video Solution

21. A sinusoidal voltage $V(t) = 100\sin(500t)$ is applied across a pure inductance of $L = 0.02H$.

The current through the coil is :

A. $10\cos(500t)$

B. $-10\cos(500t)$

C. $10\sin(500t)$

D. $-10\sin(500t)$


Answer: 2



Watch Video Solution

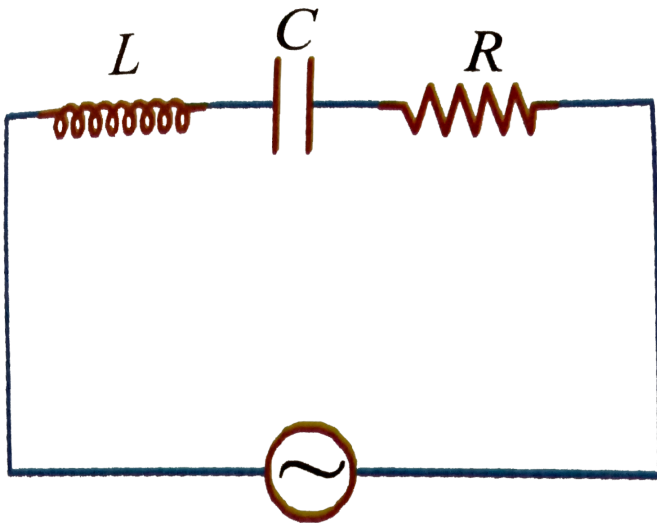22. For the LCR circuit, shown here, the current is observed to lead the applied voltage. An additional capacitor C' , when joined with the

capacitor C present in the circuit, makes the power factor of the circuit unity. The capacitor C' must have been connected in:



$$V = V_0 \sin t\omega$$

A. series with C and has magnitude

$$\frac{C}{(\omega^2 LC - 1)}$$

B. series with C and has a magnitude

$$\frac{1 - \omega^2 LC}{\omega^2 L}$$

C. parallel with C and has a magnitude

$$\frac{1 - \omega^2 LC}{\omega^2 L}$$

D. parallel with C and has a magnitude


$$\frac{C}{(\omega^2 LC - 1)}$$

Answer: 3







Watch Video Solution

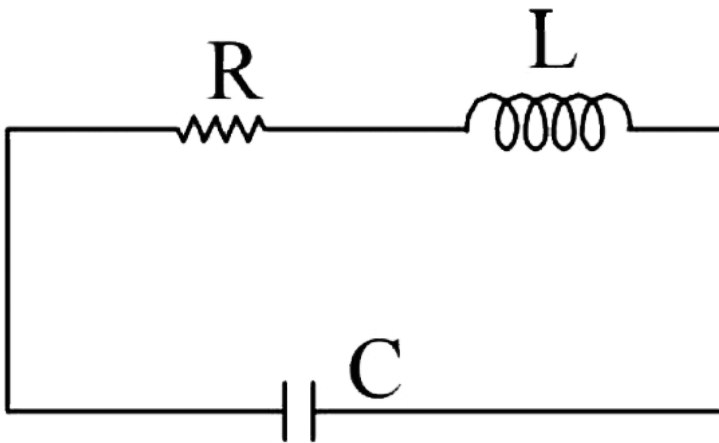23. An LCR circuit is equivalent to a damped pendulum. In an LCR circuit the capacitor is charged to (Q_0) and then connected to the L and R as shown below.



If a student plots graphs of the square of maximum charge (Q_{\max}^2) on the capacitor with time (t) for two different values

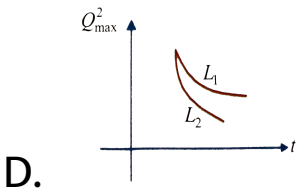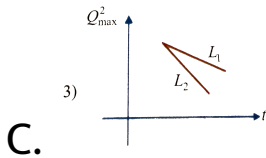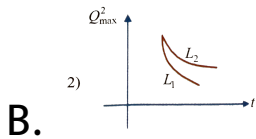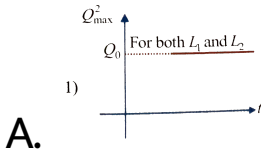L_1 and L_2 ($L_1 > L_2$) of L then which of the following represents this graph correctly?
 (plots are schematic and not drawn to scale).



Answer: 4



24. An arc lamp requires a direct current of 10A at 80V to function. If it is connected to a 220V(rms), 50 Hz AC supply, the series inductor needed for it to work is close to:

A. $80H$

B. $0.08H$

C. $0.044H$

D. $0.065H$


Answer: 4



Watch Video Solution

NCERT Based Question

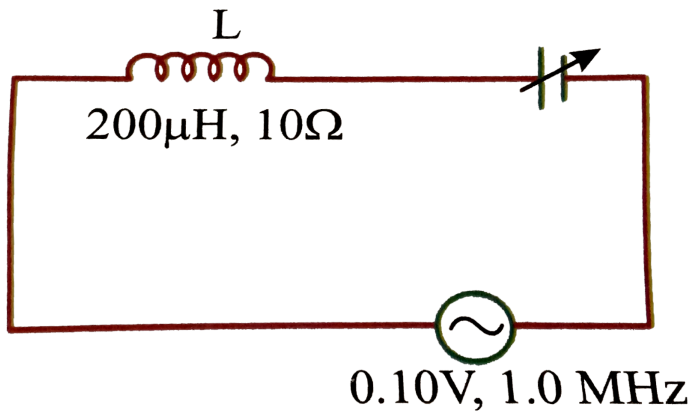1. At resonance, V_L and V_C both very much greater than the applied potential, V itself. The quantity factor for an LCR circuit in resonance is given by $Q = \frac{X_L}{R}$. In practice, $Q = 200$ has been achieved.



At resonance, the capacitor has been adjusted for

- (1). $200 \times 10^{-6}\mu\text{F}$
- (2) $0.00013\mu\text{F}$
- (3). $0.0012\mu\text{F}$
- (4). 0.0013F

At resonance, the potential difference across the inductance is

- (1) 1.3V

(2) 13V

(3). 0.3V

(d) none of these

The potential across the capacitor at resonance is

(1) 1.3V

(2) 13V

(3) $< 13V$

(4) none of these

The Q factor is

(1) $\frac{V_L}{V_C}$

(2) $\frac{V_C}{V_L}$

$$(3) \frac{V_C}{V}$$

$$(d) \frac{V_L}{V}$$

(e) choose the right statement.

(1) $V_L + V_C$ can be greater than V_{applied}

(2) $V_L + V_C = V_{\text{applied}}$

(3) $V_L + V_C < V_{\text{applied}}$

(4) none of these



[View Text Solution](#)

LEVEL - IV NCERT Based Questions

1. If the rms current in a 50 Hz ac circuit is 5 A, the value of the current $1/300$ second after its value becomes zero is

A. $5\sqrt{2}A$

B. $5\sqrt{\frac{3}{2}}A$

C. $\frac{5}{6}A$

D. $\frac{5}{\sqrt{2}}A$

Answer: 2



Watch Video Solution

2. An alternating current generator has an internal resistance R_g and an internal reactance X_g . It is used to supply power to a passive load consisting of a resistance R_g and a reactance X_L . For maximum power to be delivered from the generator to the load, the value of X_L is equal to

A. zero

B. X_g

C. $-X_g$

D. R_g

Answer: 3



Watch Video Solution

3. When a voltage measuring device is connected to a.c. mains the meter shows the steady input voltage of 220V. This means

A. input voltage cannot be a.c. voltage, but a.d.c voltage.

B. maximum input voltage is 220V

C. the meter reads not v but $\langle v^2 \rangle$ and is calibrated to read $\sqrt{\langle v^2 \rangle}$.

D. the pointer of the meter is stuck by some mechanical defect

Answer: 3



Watch Video Solution

4. To reduce the resonant frequency in an LCR series circuit with a generator

A. the generator frequency should be reduced

B. another capacitor should be added in parallel to the first

C. the iron core of the inductor should be removed

D. dielectric in the capacitor should be removed.

Answer: 2



Watch Video Solution

5. Which of the following combinations should be selected for better turning of an LCR circuit used for communication ?

A. $R = 20\Omega, L = 1.5H, C = 35\mu F$

B. $R = 25\Omega, L = 2.5H, C = 45\mu F$

C. $R = 15\Omega, L = 3.5H, C = 30\mu F$

D. $R = 25\Omega, L = 1.5H, C = 45\mu F$

Answer: 3



Watch Video Solution

6. A inductor of reactance 1Ω and a resistor of 2Ω are connected in series to the terminals of a 6 V (rms) a.c. source. The power dissipated in the circuit is

A. 8W

B. 12W

C. 14.4W

D. 18W

Answer: 3



Watch Video Solution

7. The output of a step-down transformer is measured to be $24V$ when connected to a 12 watt light bulb. The value of the peak current is

A. $\frac{1}{\sqrt{2}}$

B. $\sqrt{2}A$

C. $2A$

D. $2\sqrt{2}A$

Answer: 1



Watch Video Solution

8. As the frequency of an ac circuit increases, the current first increases and then decreases.

What combination of circuit elements is most likely to comprise the circuit ?

A. Inductor and capacitor

B. Resistor and inductor

C. Resistor and capacitor

D. Resistor, inductor and capacitor

Answer: 1,4



Watch Video Solution

9. In an alternating current circuit consisting of elements in series, the current increases on increasing the frequency of supply. Which of the following elements are likely to constitute the circuit ?

A. Only resistor

B. Resistor and an inductor

C. Resistor and a capacitor

D. Only a capacitor

Answer: 3,4



Watch Video Solution

10. Electrical energy is transmitted over large distances at high alternating voltages. Which of the following statements is (are) correct?

A. For a given power level, there is a lower current.

B. Lower current implies less power loss.

C. Transmission lines can be made thinner.

D. It is easy to reduce the voltage at the receiving end using step-down transformers

Answer: 1,2,4



Watch Video Solution

11. For an LCR circuit, the power transferred from the driving source to the driven oscillator is $P = I^2 Z \cos \phi$.

A. Here, the power factor $\cos \phi \geq 0$, $P \geq 0$.

B. The driving force can give no energy to the oscillator ($P = 0$) in some cases.

C. The driving force cannot syphone out ($P > 0$) the energy out of osillator.

D. The driving force take away energy out of the oscillator.

Answer: 1,2,3



Watch Video Solution

12. When an *A. C* voltage of $220V$ is applied to the capacitor C

A. The maximum voltage between plates is

$220V$

B. the current is in phase with the applied

voltage

C. the change on the plates is in phase with the applied voltage.

D. power delivered to the capacitor is zero.

Answer: 3,4



Watch Video Solution

13. The line that draws power supply to your house from street has

A. zero average current.

B. 220V average voltage

C. voltage and current out of phase by 90°

D. voltage and current possibly differing in

phase ϕ such that $|\phi| \leq \frac{\pi}{2}$

Answer: 1,4




Watch Video Solution

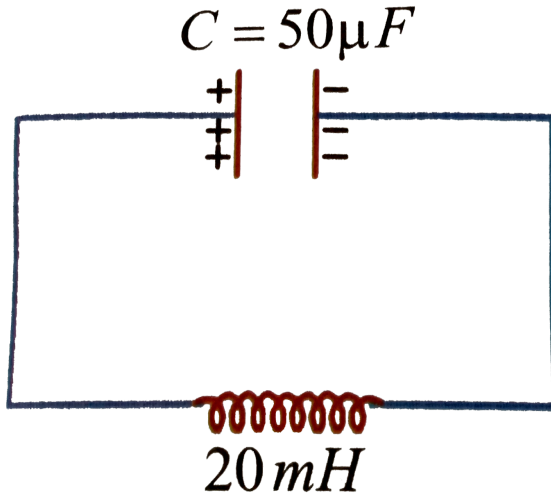14. An LC circuit contains a $20mH$ inductor and a $50\mu F$ capacitor with initial charge of $10mC$.

The resistance of the circuit is negligible. Let

the instant the circuit is closed be $t = 0$.



A. Energy stored in the circuit is completely

electrical at $t = \frac{n\pi}{2000}$

B. Energy stored in the circuit is completely

magnetic at $t = \frac{(2n + 1)\pi}{2000}$

C. Energy stored in the circuit is shared equally between the inductor and capacitor at $t = \frac{(2n + 1)\pi}{4000}$


D. Energy stored in the circuit is shared equally between the inductor and capacitor at $t = \frac{n\pi}{2000}$

Answer: 1,2,3



Watch Video Solution

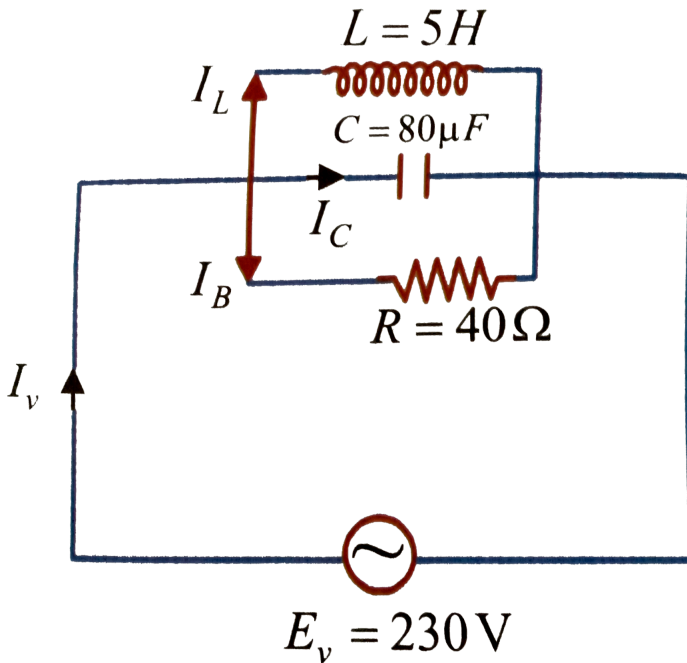15. If the three elements, L , C and R are arranged in parallel. Source has emf $230V$ and $L = 5.0H$, $C = 80\mu F$ and $R = 40\Omega$



A. The minimum impedance in the circuit is

40Ω

B. The maximum impedance in the circuit is

$$40\Omega$$

C. The impedance is minimum at

$$\omega = 50\text{rads}^{-1} \text{ of the source.}$$

D. The impedance is maximum at

$$\omega = 50\text{rads}^{-1} \text{ of the source}$$

Answer: 2,3



Watch Video Solution

1. The value of current in two series LCR circuits at resonance is same when connected across a sinusoidal voltage source. Then:

A. both circuits must be having same value of capacitance and inductor

B. in both circuits ratio of L and C will be same

C. for both the circuits X_L/X_C must be same at that frequency

D. both circuits must have same impedance
at all frequencies

Answer: C



Watch Video Solution

2. The series *RLC* circuit in resonance is called:

- A. Selector circuit
- B. rejector circuit
- C. amplifier circuit

D. oscillator circuit

Answer: A



Watch Video Solution

3. In a series R-L-C circuit, the frequency of the source is half of the resonance frequency. The nature of the circuit will be

A. capacitive

B. inductive

C. purely resistive

D. selective


Answer: A



Watch Video Solution

4. The graphs given below depict the dependence of two reactive impedances X_1 and X_2 on the frequency of the alternating e.m.f. applied individually to them. We can then say

that

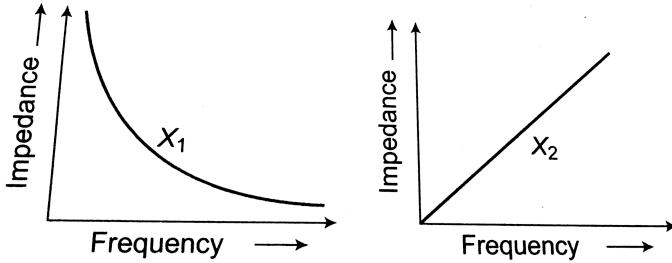

- A. X_1 is an inductor and X_2 is a capacitor
- B. X_L is a resistor and X_2 is a capacitor
- C. X_1 is a capacitor and X_2 is an inductor
- D. X_1 is an inductor and X_2 is a resistor

Answer: C



Watch Video Solution

5. In which of the following electrical appliances will *AC* fail to function where *DC* is normally used?

- A. electric light
- B. voltmeter
- C. solenoid for electromagnet
- D. a cathode ray tube

Answer: C



Watch Video Solution

6. Instantaneous values of current and e.m.f in an AC circuit are $I = I/\sqrt{2}\sin 314t$ amp and $E = \sqrt{2}\sin(314t - \pi/6)V$ respectively. The phase difference between E and I will be

A. $-\frac{\pi}{6}$ rad

B. $-\frac{\pi}{3}$

C. $\frac{\pi}{6}$

D. $\frac{\pi}{3}$ rad

Answer: A



Watch Video Solution

7. The rms value of an ac of 50Hz is 10A. The time taken by an alternating current in reaching from zero to maximum value and the peak value will be

A. 2×10^{-2} sec and 14.14 amp

B. 1×10^{-2} sec and 7.07 amp

C. 5×10^{-3} sec and 7.07 amp


D. 5×10^{-3} sec and 14.14 amp

Answer: D



Watch Video Solution

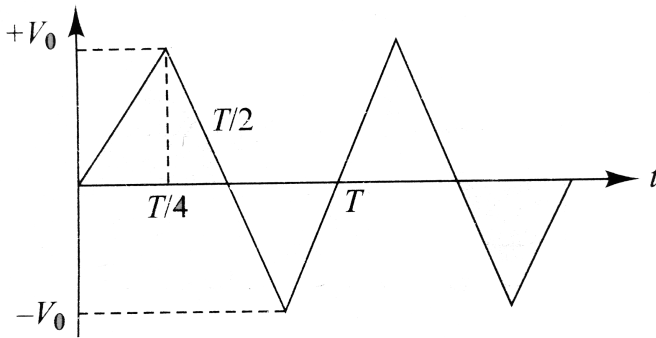8. The voltage time (V-t) graph for triangular wave having peak value (V_0) is as shown in fig.



A. $\frac{V_0}{3}$

B. $\frac{V_0}{2}$

C. $\frac{V_0}{\sqrt{2}}$

D. $\frac{V_0}{\sqrt{3}}$


Answer: D



Watch Video Solution

9. The average value for the saw-tooth voltage of peak value of V_0 over half the cycle as shown

in figure is

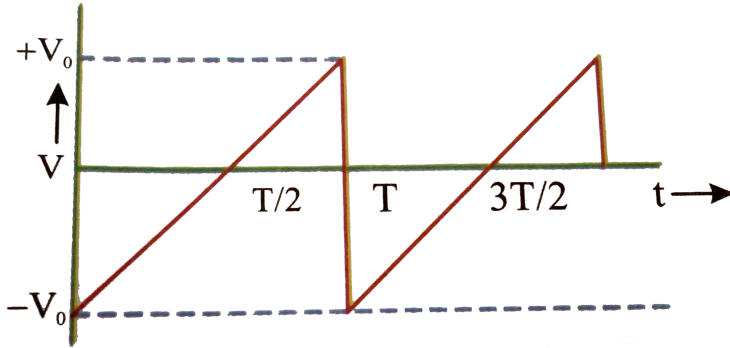

- A. $\frac{V_0}{\sqrt{3}}$
- B. $\frac{V_0}{\sqrt{2}}$
- C. $\frac{2V_0}{3}$
- D. $\frac{V_0}{3}$

Answer: D



10. An alternating voltage is given by:

$$e = e_1 \sin \omega t + e_2 \cos \omega t.$$

Then the root mean square value of voltage is given by:

A. $\sqrt{e_1^2 + e_2^2}$

B. $\sqrt{e_1 e_2}$

C. $\sqrt{\frac{e_1 e_2}{2}}$

D. $\sqrt{\frac{e_1^2 e_2^2}{2}}$

Answer: D



Watch Video Solution

11. If $i = t^2, 0 < t < T$ then *r.m.s.* value of current is

A. $\frac{T^2}{\sqrt{2}}$

B. $\frac{T^2}{2}$

C. $\frac{T^2}{\sqrt{5}}$

D. $\frac{T^2}{5}$


Answer: C



Watch Video Solution

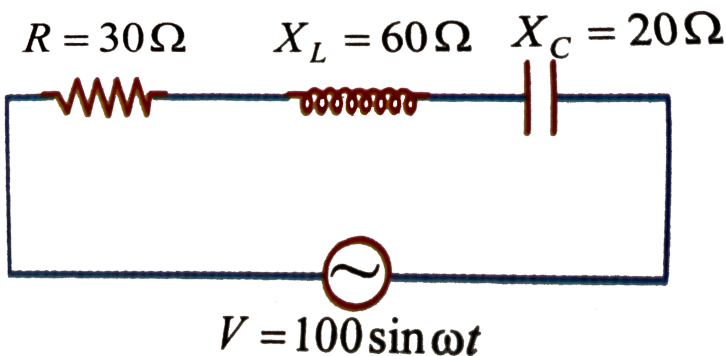12. An alternating voltage $V = 100\sin\omega t$ is applied across an LCR circuit as shown. At the instant when voltage drop across source is $50\sqrt{3}$ volts then at that instant

$$R = 30\Omega \quad X_L = 60\Omega \quad X_C = 20\Omega$$



A. voltage drop across inductor is

$$\left(120\cos 7^\circ\right) \text{ volts}$$

B. voltage drop across capacitor is

$$\left(40\cos 173^\circ\right) \text{ volts}$$

C. voltage drop across resistor is $\left(60\cos 7^\circ\right)$

volts


D. All the above

Answer: D



Watch Video Solution

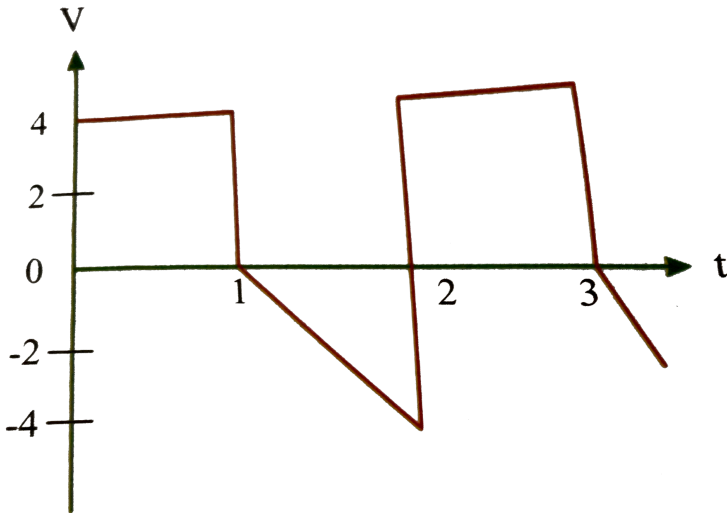13. The rms and the average value of the voltage wave shown in figure are



A. $\sqrt{\frac{32}{3}} \text{ V}, 1 \text{ V}$

B. $\sqrt{\frac{11}{3}} \text{ V}, 1 \text{ V}$

C. $\sqrt{\frac{11}{3}} \text{ V}, 3 \text{ V}$


D. $\sqrt{\frac{32}{3}} \text{ V}, 3 \text{ V}$

Answer: A



Watch Video Solution

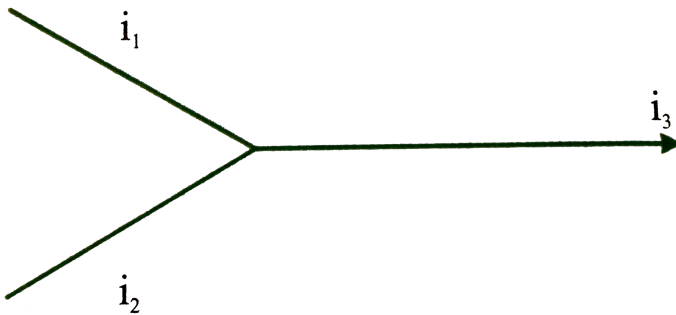14. If $i_1 = i_0 \sin(\omega t)$, $i_2 = i_{02} \sin(\omega t + \phi)$, then $i_3 =$



A. $\sqrt{i_{01}^2 + i_{02}^2} \sin\{\phi + \omega t\}$

B. $(i_{01} + i_{02}) \sin\left(\frac{\phi}{2} + \omega t\right)$

$$C. \left(\sqrt{i_{0_1}^2 + i_{0_2}^2 + 2i_{0_1}i_{0_2}\cos\phi} \right) \sin[\phi + \omega t]$$

$$D. \left(\sqrt{i_{0_1}^2 + i_{0_2}^2 + 2i_{0_1}i_{0_2}\cos\phi} \right) \sin[\alpha + \omega t]$$


$$\text{where } \alpha = \tan^{-1} \left[\frac{i_{0_2} \sin\phi}{i_{0_1} + i_{0_2} \cos\phi} \right]$$

Answer: D



Watch Video Solution

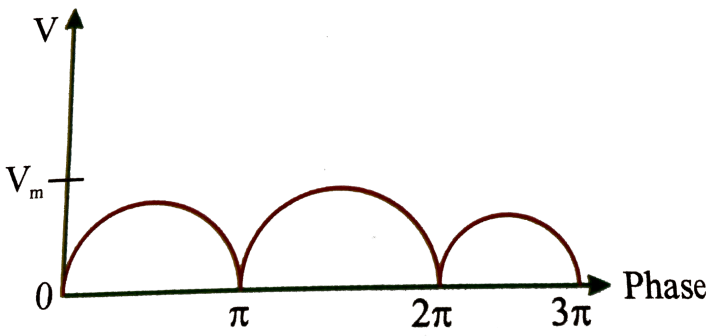15. The average and effective values for the waveshape shown in figure are:



A. $\frac{2}{\pi} V_m$ and $\frac{V_m}{2}$

B. $\frac{V_m}{\pi}$ and $\frac{V_m}{\sqrt{2}}$

C. $\frac{2}{\pi} V_m$ and $\frac{V_m}{\sqrt{2}}$

D. $\frac{V_m}{\pi\sqrt{2}}$ and $\frac{V_m}{\sqrt{2}}$

Answer: C



Watch Video Solution

16. Calculate the reading which will be given by a hot-wire voltmeter if it is connected across the terminals of generator whose voltage waveform is represented by

$$v = 200\sin\omega t + 100\sin 3\omega t + 50\sin\omega t$$

A. 110V

B. 162V

C. 200V


D. 220V


Answer: B




Watch Video Solution

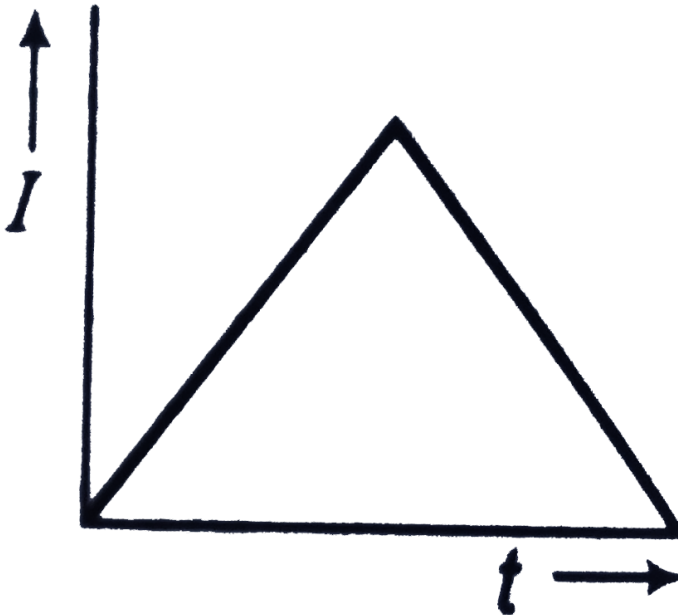17. An alternating current I in an inductance coil varies with time t according to the graph as shown: Which one of the following graph gives the variation of voltage with time?




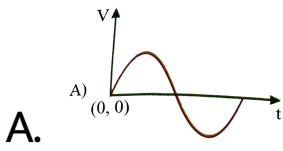


B.

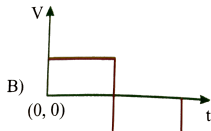

C.

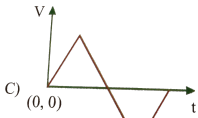

D.

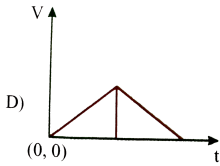


Answer: B



Watch Video Solution

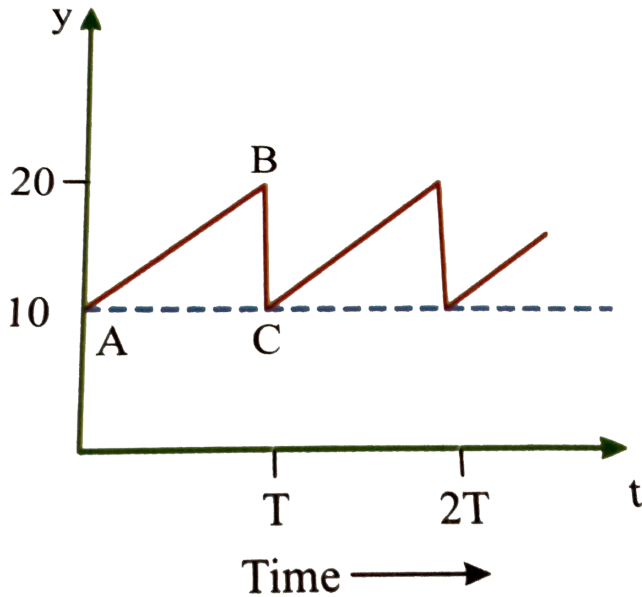18. Find the rms and average value of the waveform shown in figure



A. 8.5,10

B. 10.3,20

C. 15.2,15


D. 26,5

Answer: C



Watch Video Solution

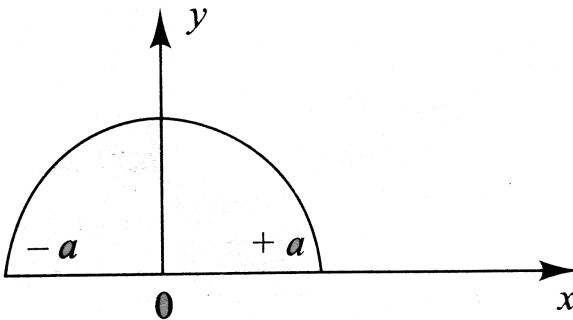19. Determine the rms value of a semi-circular current wave which has a maximum value of a .



A. 2.515 a

B. 1.815 a

C. 0.615 a

D. 0.816 a

Answer: D



Watch Video Solution

20. An electric bulb is designed to operate at 12 volts *DC*. If this bulb is connected to an AC

source and gives normal brightness, what would be the peak voltage of the source?

A. 37V

B. 17V

C. 18V

D. 10V

Answer: B



Watch Video Solution

21. The current in a discharging LR circuit is given by $I = i_0 e^{-\frac{t}{\tau}}$ where τ is the time constant of the circuit. Calculate the rms current for the period $t = 0$ to $t = \tau$.

A. $\frac{i_0}{e} \sqrt{\frac{(e^2 - 1)}{2}}$

B. $\frac{i_0}{e} \sqrt{\frac{(e^{-2} + 1)}{2}}$

C. $\frac{i_0}{e} \sqrt{\frac{(e + 2)}{3}}$

D. $\frac{i_0}{e} \sqrt{\frac{(e^2 - 1)}{2}}$





Answer: A




Watch Video Solution

22. The figure represents the voltage applied across a pure inductor. The diagram which correctly represents the variation of current i

with time t is given by

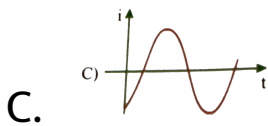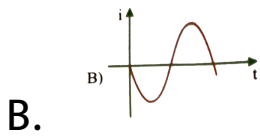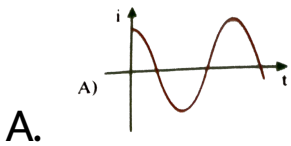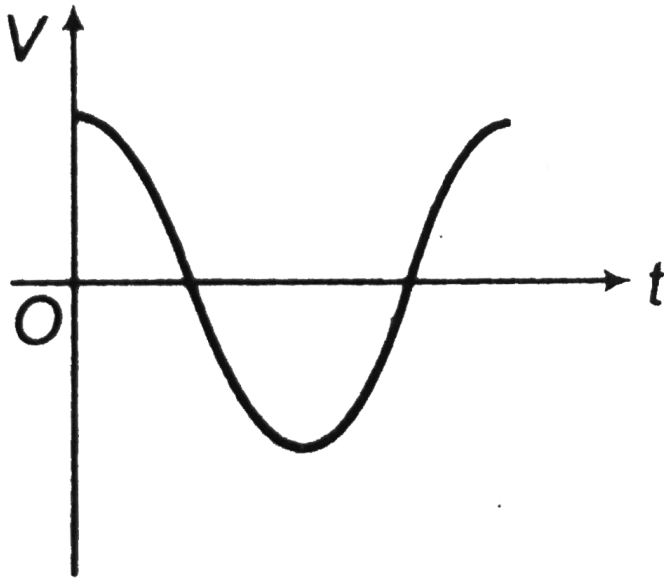

D.

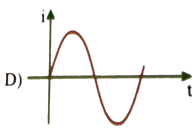


Answer: D






Watch Video Solution


23. A constant voltage at different frequencies is applied across a capacitance C as shown in the figure. Which of the following graphs correctly depicts the variation of current with

frequency

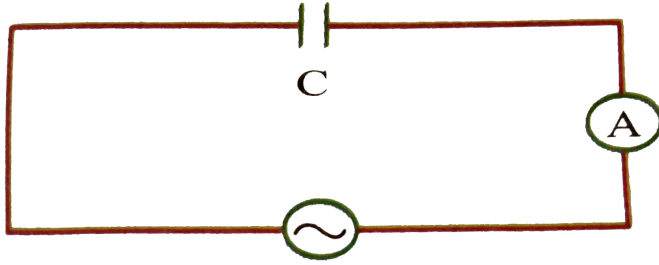

A.C. generator

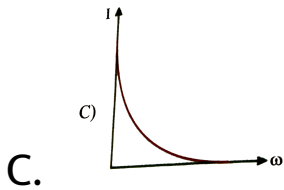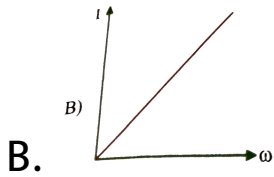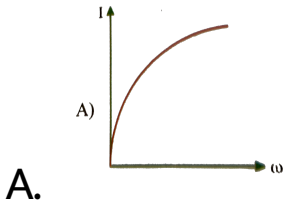

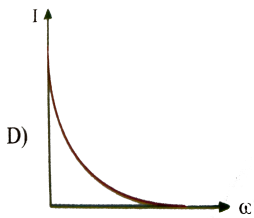


D.

Answer: B



Watch Video Solution

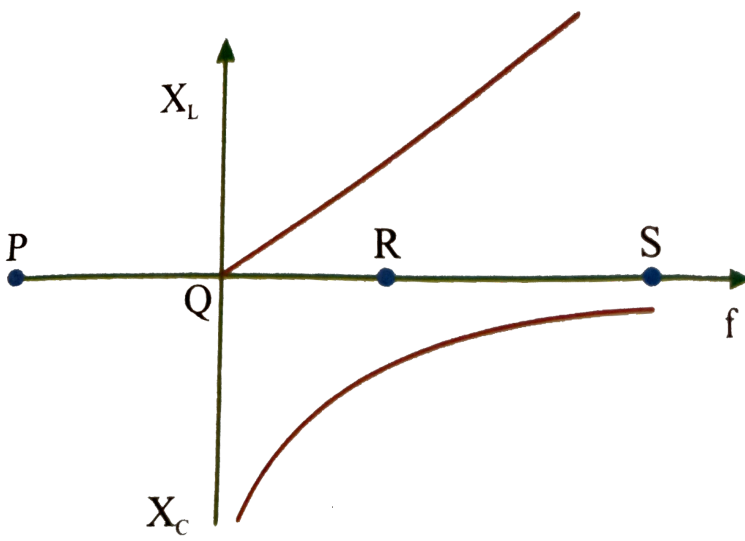24. The resonance point in $X_L - f$ and $X_C - f$ curves is



A. P

B. Q

C. R

D. S

Answer: C



Watch Video Solution

25. When $100V$ DC is applied across a solenoid, a current of $1.0A$ flows in it. When $100V$ AC is applied across the same coil. The current drops to $0.5A$. If the frequency of the ac source is $50Hz$, the impedance and inductance of the solenoid are

A. 200 ohm and 0.55 henry

B. 100 ohm and 0.86 henry

C. 100 ohm and 1.0 henry

D. 100 ohm and 0.93 henry.

Answer: A



Watch Video Solution

26. A coil having an inductance of $1/\pi$ henry is connected in series with a resistance of 300Ω . If 20 volt from a 200 cycle source are impressed across the combination, the value of the phase angle between the voltage and the current is :

A. $\tan^{-1} \frac{5}{4}$

B. $\tan^{-1} \frac{4}{5}$

C. $\tan^{-1} \frac{3}{4}$

D. $\tan^{-1} \frac{4}{3}$

Answer: D



Watch Video Solution

27. In a circuit containing an inductance of zero resistance, the current leads the applied a.c. voltage by a phase angle at

A. 90°

B. -90°

C. 0°

D. 180°

Answer: B



Watch Video Solution

28. In RLC circuit, at a frequency ν , the potential difference across each device are

$$\left(\Delta V_R\right)_{\max} = 8.8V, \left(\Delta V_L\right)_{\max} = 2.6V \quad \text{and}$$

$(\Delta V_C)_{\max} = 7.4V$. The composed potential difference $(\Delta V_C + \Delta V_L)_{\max}$ across inductor and capacitor is


- A. 10V
- B. 7.8V
- C. 7.4V
- D. 4.8V

Answer: D



Watch Video Solution

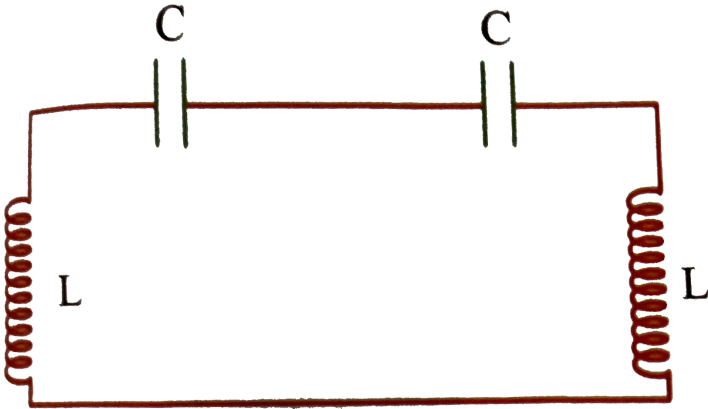29. The natural frequency of the circuit shown in the figure is



A. $\frac{1}{2\pi\sqrt{LC}}$

B. $\frac{1}{\pi\sqrt{LC}}$

C. $\frac{2}{\pi\sqrt{LC}}$

D. none

Answer: A



Watch Video Solution

30. If the phase difference between voltage and current is $\pi/6$ and the resistance in the circuit is $\sqrt{300}\Omega$, then the impedance of the circuit will be

A. 40Ω

B. 20Ω

C. 50Ω

D. 13Ω


Answer: B



Watch Video Solution

31. In the circuit as shown in the figure, if value of $R = 60\Omega$, then the current flowing through

the condenser will be

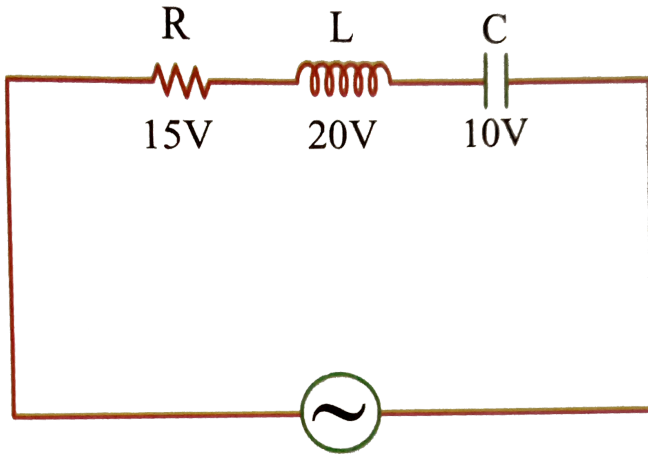

- A. 0.5A
- B. 0.25A
- C. 0.75A
- D. 1.0A

Answer: B



Watch Video Solution

32. The power in ac circuit is given by

$P = E_{rms} I_{rms} \cos \phi$. The value of $\cos \phi$ in series

LCR circuit at resonance is:

A. zero

B. 1

C. $\frac{1}{2}$


D. $\frac{1}{\sqrt{2}}$

Answer: B



Watch Video Solution

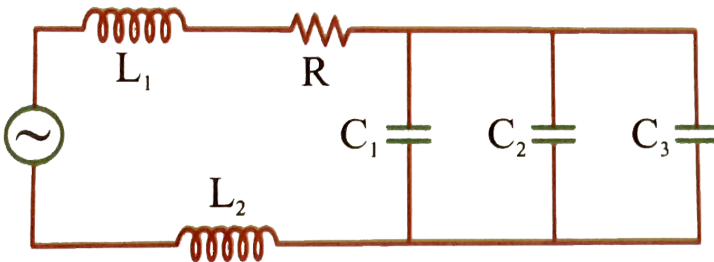33. A generator with an adjustable frequency of oscillation is connected to resistance, $R = 1000\Omega$, inductance, $L_1 = 1.7mH$ and $L_2 = 2.3mH$ and capacitance, $C_1 = 4\mu F$, $C_2 = 2.5\mu F$ and $C_3 = 3.5\mu F$. The resonant angular frequency of the circuit is



A. 0.5rad/s

B. $0.5 \times 10^4\text{rad/s}$

C. 2rad/s

D. $2 \times 10^{-4}\text{rad/s}$


Answer: B



Watch Video Solution

34. In the a.c circuit shown in figure, the supply voltage has a constant r.m.s value but variable

frequency f . Resonance frequency is

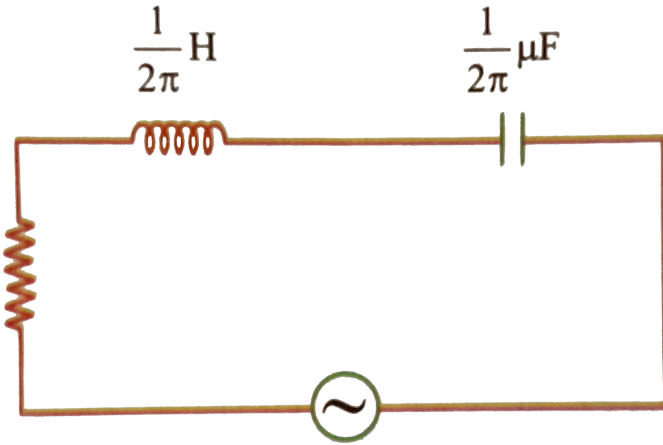

- A. 10Hz
- B. 100Hz
- C. 1000Hz
- D. 200Hz

Answer: C



Watch Video Solution

35. In a LCR circuit capacitance is changed from C to $2C$. For the resonant frequency to remain unchanged, the inductance should be changed from L to

A. $4L$

B. $2L$

C. $L/2$

D. $L/4$

Answer: C



Watch Video Solution

36. In an AC circuit, V and I are given by

$$V = 100\sin(100t) \text{ volt}, I = 100\sin\left(100t + \frac{\pi}{3}\right) \text{ mA}$$

. The power dissipated in circuit is

A. 10^4 watt

B. 10 watt

C. 2.5 watt

D. 5 watt

Answer: C



Watch Video Solution

37. A series combination of R, LC is connected to an a.c source. If the resistance is 3Ω and the reactance is 4Ω , the power factor of the circuit is

A. 0.4

B. 0.6

C. 0.8

D. 1.0

Answer: B



Watch Video Solution

38. In an a.c. Circuit the voltage applied is

$E = E_0 \sin(\omega)t$. The resulting current in the

circuit is $I = I_0 \sin\left((\omega)t - \left(\frac{\pi}{2}\right)\right)$. The power

consumption in the circuit is given by

A. $E_0 I_0 / \sqrt{2}$

B. $E_0 I_0 / 2$

C. $EI / \sqrt{2}$

D. zero


Answer: D



Watch Video Solution

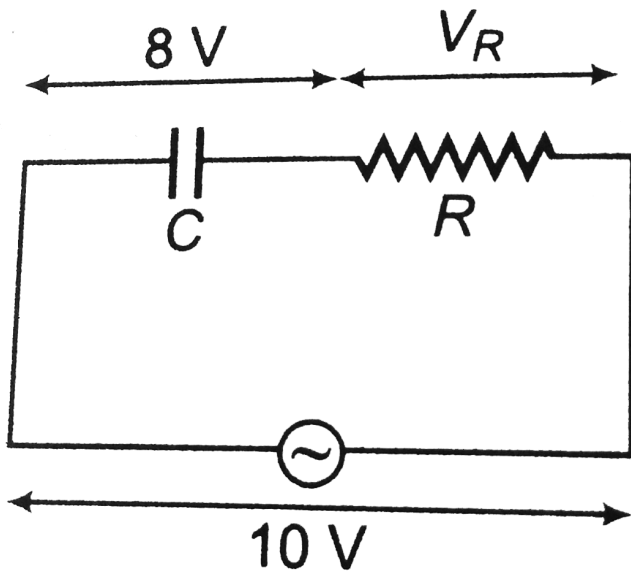39. In a series $C - R$ circuit shown in figureure, the applied voltage is $10V$ and the voltage across capacitor is found to $8V$. The voltage

across R , and the phase difference between current and the applied voltage will respectively be



A. $6V, \tan^{-1}\left(\frac{4}{4}\right)$

B. $3V, \tan^{-1}\left(\frac{3}{4}\right)$

C. $6V, \tan^{-1}\left(\frac{5}{3}\right)$

D. $3V, \tan^{-1}\left(\frac{4}{3}\right)$

Answer: A



Watch Video Solution

40. An inductor of inductance L and resistor of resistance R are joined in series and connected by a source of frequency ω . Power dissipated in the circuit is

A.
$$\frac{(R^2 + \omega^2 L^2)}{V}$$

$$\text{B. } \frac{V^2 R}{\left(R^2 + \omega^2 L^2\right)}$$

$$\text{C. } \frac{V}{\left(R^2 + \omega^2 L^2\right)}$$

$$\text{D. } \frac{\sqrt{R^2 + \omega^2 L^2}}{V^2}$$

Answer: B



Watch Video Solution

41. Power loss in AC circuit will be minimum when

A. Inductance is high, resistance is high

B. Inductance is low, resistance is high

C. Inductance is low, resistance is low

D. Inductance is high, resistance is low


Answer: D



Watch Video Solution

42. In the circuit, as shown in the figure, if the value of *R.M.S* current is 2.2 ampere, the

power factor of the box is ($E = 220V$)

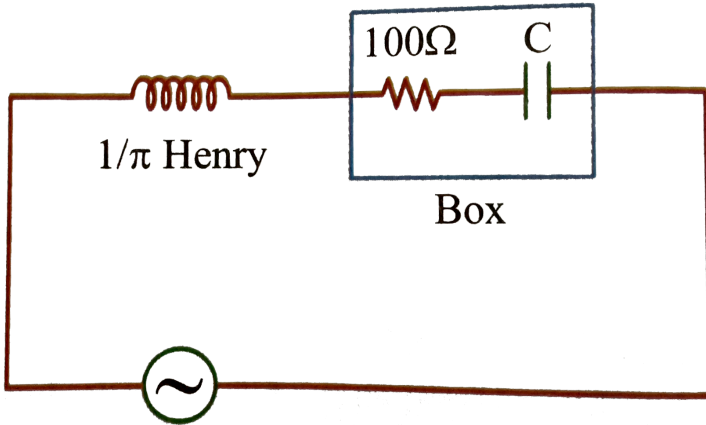

A. $\frac{1}{\sqrt{2}}$

B. 1

C. $\frac{\sqrt{3}}{3}$

D. $\frac{1}{2}$

Answer: A



Watch Video Solution

43. The impedance of a series RL circuit is same as the series RC circuit when connected to the same AC source separately keeping the same resistance. The frequency of the source is

A. $\frac{1}{\sqrt{LC}}$

B. $\frac{1}{2\pi\sqrt{LC}}$

C. $\frac{R}{L}$

D. $\frac{1}{RC}$


Answer: B



Watch Video Solution

44. A current source sends a current $I = (i_0)\cos(\omega t)$, When connected across an unknown load, it gives a voltages output of $v = v_0\sin[\omega t + (\pi/4)]$ across that load. Then the voltage across the current source may be brought in phase with the current through

it by

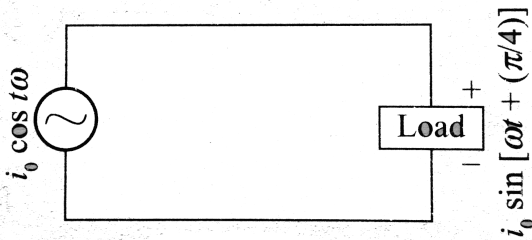

- A. Connecting an inductor in series with the load
- B. Connecting a capacitor in series with the load
- C. Connecting a capacitor in parallel with the load

D. Connecting a capacitor in parallel with the load

Answer: B




Watch Video Solution

45. A combination of elements is enclosed in a black box and the voltage and currents are measured across this black box. The expression for applied voltage, and the current flowing in it is $V = V_0 \sin \omega t$,

$$i = 2\sqrt{2}\sin(\omega + \pi/4) \quad \text{where} \quad \omega = 100\pi \text{ rad/sec}$$

Then the wrong statement is

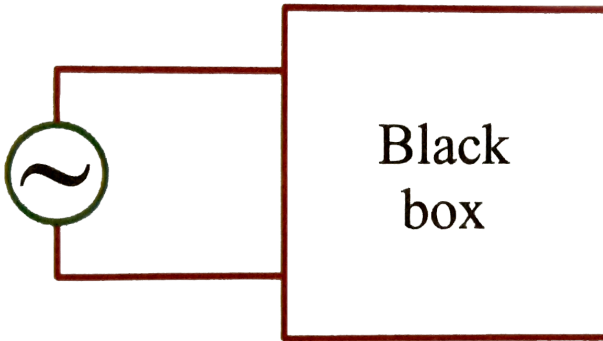

- A. There must be a capacitor in the black box
- B. Power factor of circuit = 0.707
- C. There must be a resistor in the box
- D. There must be an inductor in the box

Answer: D



Watch Video Solution

46. A high impedance AC voltmeter is connected in turn across the inductor, the capacitor and the resistor in a series circuit having an AC source of $100V$ (rms) and gives the same reading in volts in each case. This reading is:

A. $100V$

B. $141V$

C. $150V$

D. 200V


Answer: A



Watch Video Solution

47. In a black box of unknown elements (L or R or any other combination), an ac voltage $E = E_0 \sin(\omega t + \phi)$ is applied and current in the circuit was found to be $I = (I_0) \sin[\omega t + \phi + (\pi/4)]$. Then the unknown

elements in the box may be

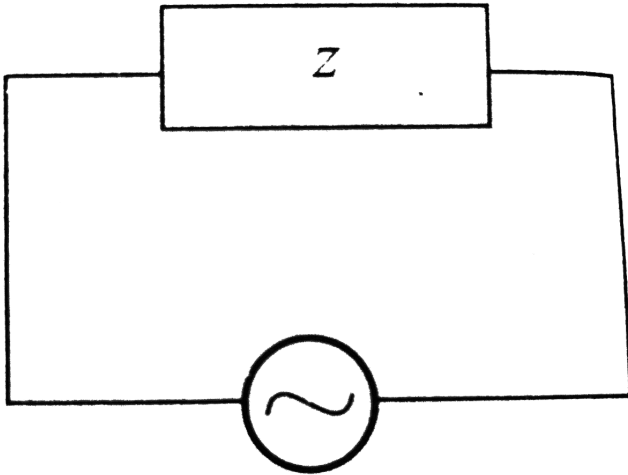

A. only capacitor

B. inductor and resistor both

C. either capacitor, resistor and inductor or

only capacitor and resistor

D. only resistor

Answer: C



Watch Video Solution

48. A given alternating current has an rms value of 5.6 ampere. If this current flows in a circuit containing 10Ω of resistance in series with 20Ω of inductive reactance, the power consumed in the circuit will be

A. 313.6W

B. 940.8W

C. 627.2W

D. 168W

Answer: A



Watch Video Solution

49. In an a.c circuit, V & I are given by

$$V = 100\sin(100t) \text{ volt.}$$

$$I = 100\sin\left(100t + \frac{\pi}{2}\right) \text{ mA}$$

The power dissipated in the circuit is:

A. 1 watt

B. 10 watt

C. zero

D. 5 watt

Answer: C



Watch Video Solution

50. In $R - L - C$ series circuit, we have same current at angular frequencies ω_1 and ω_2 . The resonant frequency of circuit is

A. $\frac{\omega_1^2}{\omega_2}$

B. $\frac{\omega_2^2}{\omega_1}$

C. $\sqrt{\omega_1\omega_2}$

D. $\omega_1 + \omega_2$

Answer: C



Watch Video Solution

51. A choke coil of resistance R and inductance L is connected to A.C source of frequency f and

maximum voltage V_0 . Then, the average power dissipated in the choke is proportional to:

A. f^2

B. f^{-2}

C. f^1

D. f^0

Answer: D



Watch Video Solution

52. When two A. C generators of emfs V_1 and V_2 and same frequency connected in series, the emf across A and B is ($\phi =$ phase angle difference between the generators):



A. $\frac{V_1 + V_2}{2}$

B. $\sqrt{V_1 + V_2}$

C. $\sqrt{V_1^2 + V_2^2 + 2V_1V_2\cos\phi}$


D. $\sqrt{V_1^2 + V_2^2}$

Answer: C



Watch Video Solution

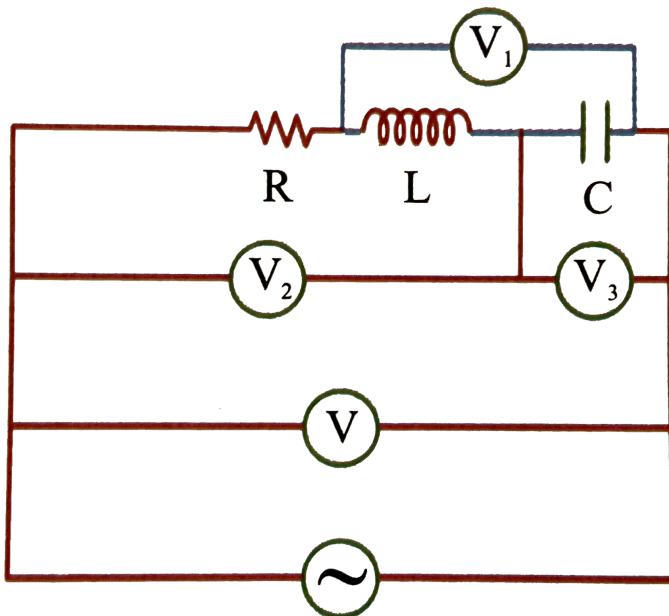53. At resonance of the given series $R - L - C$ circuit:



A. $V^2 = |V_1 - V_2|^2 + V_3^2$

B. $V_3 = 0$

C. $V_1 = 0$

D. $V_2 = 0$

Answer: C




Watch Video Solution

54. If the reading of the voltmeters vary with time as: $V_1 = 20\sin\omega t$ and

$V_2 = -20\cos\left(\omega t + \frac{\pi}{6}\right)$ then the unknown

circuit element x is a:

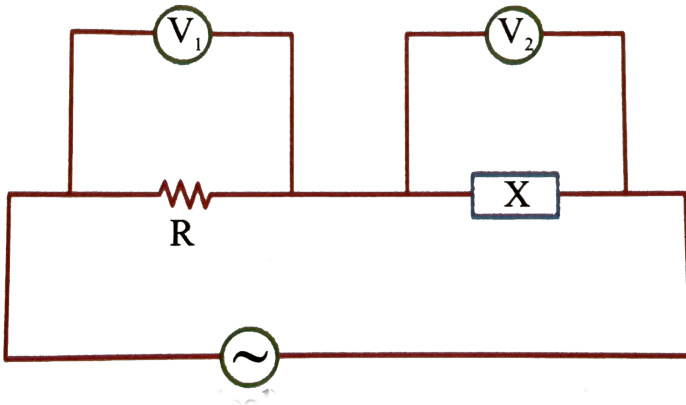

- A. pure (or ideal) inductor
- B. practical inductor
- C. pure (or ideal) capacitor
- D. practical capacitor

Answer: D



Watch Video Solution

55. In a series LCR circuit, at the frequencies f_1 and f_2 of AC source, the current amplitude falls to $\frac{1}{\sqrt{2}}$ of the current amplitude at resonance.

Then the value of $f_2 - f_1$ is

A. $\frac{R}{2\pi L}$

B. $\frac{R}{L}$

C. $\frac{R}{\pi L}$



D. $\frac{R}{\pi^2 L}$


Answer: A




Watch Video Solution

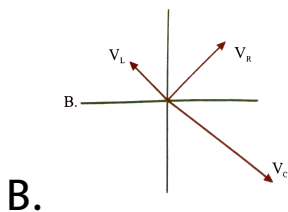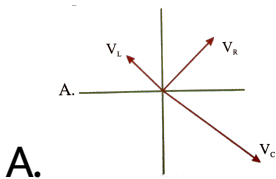56. In the figure, which of the phasor diagrams represents RLC circuit driven at resonance?



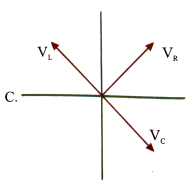

C.

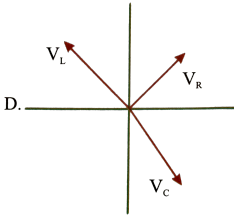

D.

Answer: C



Watch Video Solution

57. In LCR circuit at resonance current in the circuit is $10\sqrt{2}A$. If now frequency of the source is changed such that now current lags

by 45° that applied voltage in the circuit .

Which of the following is correct.

A. Frequency must be increased and current

after the change is 10A

B. Frequency must be decreases and current

after the change is 10A

C. Frequency must be decreased and

current is same as that of initial value

D. The given information is insufficient to

conclude anything

Answer: A



Watch Video Solution

58. A pure resistive circuit element X when connected to an sinusoidal AC supply peak voltage $200V$ gives a peak current of $5A$ which is in phase with the voltage. A second circuit element Y , when connected to the same AC supply also gives the same value of peak current but the current lags behind by 90^0 . If

the series combination of X and Y is connected to the same supply. the rms value of current is

A. $\frac{10}{\sqrt{2}}A$

B. $\frac{5}{\sqrt{2}}A$

C. $\frac{5}{2}A$

D. $5A$

Answer: C



Watch Video Solution

59. An A.C circuit contains a resistor ' R ' an inductor ' L ' and a capacitor ' C ' connected in series. When it is connected to an A.C generator of fixed output voltage and variable frequency, the current in the circuit is found to be leading the applied voltage $\frac{\pi}{4}$ rad, when the frequency is f_1 . when the frequency of the generator increased to f_2 the current is found to be lagging behind the applied voltage by $\frac{\pi}{4}$ rad. The resonant frequency of the circuit is

A. $\frac{f_1 f_2}{f_1 + f_2}$

B. $\frac{f_1 + f_2}{2}$

C. $\frac{2f_1f_2}{f_1 + f_2}$

D. $\sqrt{f_1f_2}$


Answer: D



Watch Video Solution

60. An alternative voltage $V = 10\sin\omega t$ (in volts) is applied across a parallel arrangement as shown current (in A) through the source is best

described by

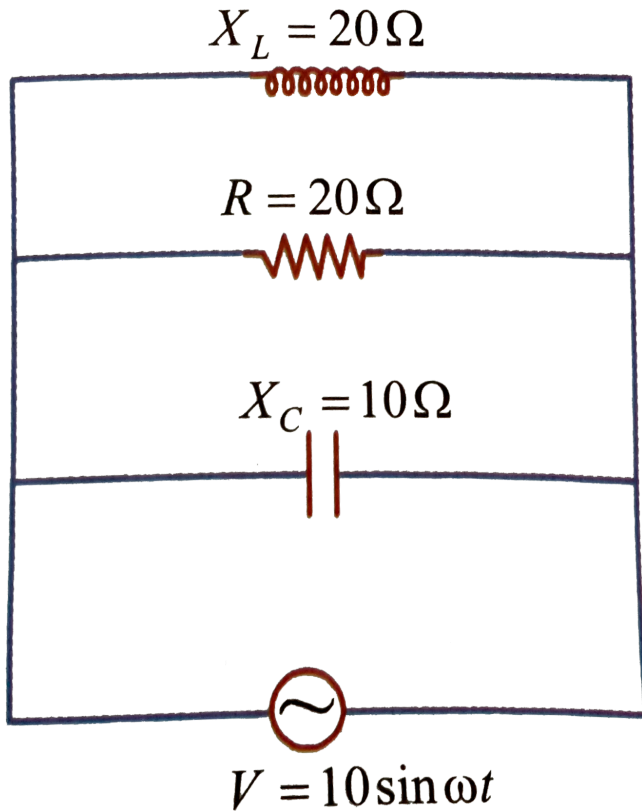

A. $i = 0.05\sin\omega t$

B. $i = 0.7\sin\left(\omega t + \frac{\pi}{6}\right)$

$$C. i = 0.7\sin\left(\omega t + \frac{\pi}{4}\right)$$

$$D. i = 0.05\sin\left(\omega t + \frac{\pi}{2}\right)$$

Answer: C



Watch Video Solution

61. A radio tuner has a frequency range from 500kHz to 5MHz . If its LC circuit has an effective inductance of $200\mu\text{H}$, what is the range of its variable capacitors? (Take $\pi^2 = 10$).

A. 2.5 pF to 250 pF

B. 5.0 pF to 500 pF

C. 7.5 pF to 750 pF

D. 10 pF to 1000 pF

Answer: A



Watch Video Solution

62. In a series *LCR* circuit the frequency of a 10V, AC voltage source is adjusted in such a fashion that the reactance of the inductor

measures 15Ω and that of the capacitor 11Ω . If $R = 3\Omega$, the potential difference across the series combination of L and C will be:

A. $8V$

B. $10V$

C. $22V$

D. $52V$

Answer: A



Watch Video Solution

63. A resistor of resistance 100Ω is connected to an AC source $\varepsilon = (12V)\sin(250\pi s^{-1})t$. Find the energy dissipated as heat during $t = 0$ to $t = 1.0ms$.

A. $0.61 \times 10^4 J$

B. $0.61 \times 10^{-4} J$

C. $2.61 \times 10^{-4} J$

D. $2.61 \times 10^{-6} J$

Answer: C



Watch Video Solution

64. A lamp consumes only 50 % of peak power in an *a. c.* circuit. What is the phase difference between the applied voltage and the circuit current

A. $\frac{\pi}{6}$

B. $\frac{\pi}{3}$

C. $\frac{\pi}{4}$

D. $\frac{\pi}{2}$

Answer: B





65. Voltage and current for a circuit with two elements in series are expressed as

$$V(t) = 170\sin\left(6280t + \frac{\pi}{3}\right) \text{ vo } <$$

$$i(t) = 8.5\sin\left(6280t + \frac{\pi}{2}\right) \text{ amp}$$

- (a) Plot the two waveforms.
- (b) Determine the frequency in Hz.
- (c) Determine the power factor starting its nature.
- (d) What are the values of the elements?

A. $R = 27.32\Omega, C = 25.92mF$

B. $R = 17.32\Omega, C = 15.92mF$

C. $R = 7.32\Omega, C = 5.92mF$

D. $R = 10.32\Omega, C = 5.92mF$


Answer: B



Watch Video Solution

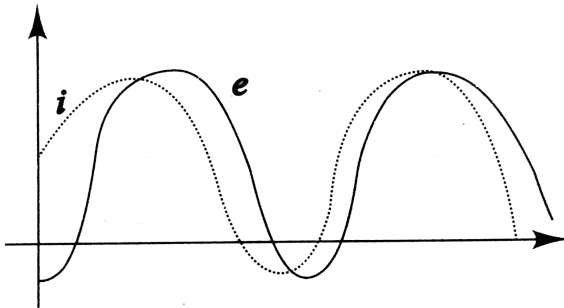66. When an ac source of emf $e = E_0 \sin(100t)$ is connected across a circuit, the phase difference between emf e and current I in the circuit is

observed to be $(\pi)/(4)$ as shown in fig. If the circuit consists possibly only of R-C or R-C of L-R series, find the relationship find the relationship between the two elements.



A. $R = 1k\Omega, C = 10\mu F$

B. $R = 1k\Omega, C = 1\mu F$

C. $R = 1k\Omega, H = 10H$

$$D. R = 1k\Omega, L = 1H$$


Answer: C



Watch Video Solution

67. The figure shows variation of R , X_L and X_C with frequency f in a series L, C, R circuit. Then for what frequency point, the circuit is

inductive ?

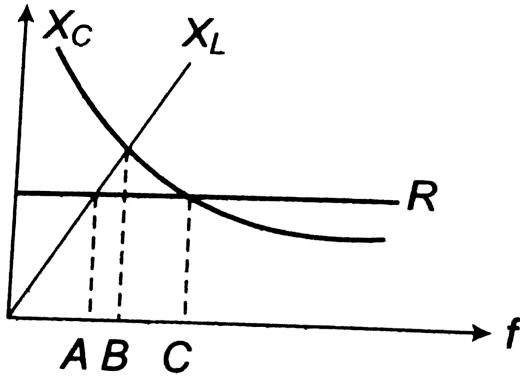

A. A

B. B

C. C


D. All points

Answer: C



Watch Video Solution

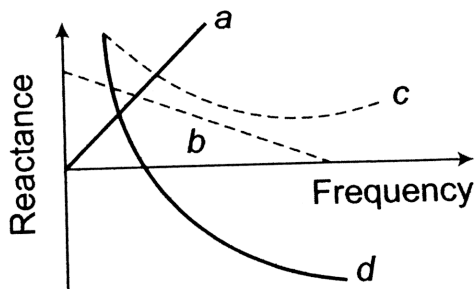68. Which of the following plots may represent the reactance of a series LC combination?



A. a

B. b

C. c

D. d

Answer: D



Watch Video Solution

69. An inductor-coil , a capacitor and an AC source of rms voltage $24V$ are connected in series. When the frequency of the source is varied, a maximum rms current of $6.0A$ is observed. If this inductor coil is connected to a battery of $emf 12V$ and internal resistance 4.0Ω , what will be the current?

A. $2A$

B. 1.5A

C. 0.5A

D. 2.5A

Answer: B



Watch Video Solution

70. A circuit consisting of a capacitor and a coil in series is connected to the mains. Varying the capacitance of the capacitor, the heat power generated in the coil was increased $n = 1.7$

times. How much (in per cent) was the value of $\cos\phi$ changed in the process ?

A. 80 %

B. 25 %

C. 50 %

D. 30 %

Answer: D



Watch Video Solution

71. An AC source producing *emf*

$$\varepsilon = \varepsilon_0 \left[\cos \left(100\pi s^{-1} \right) t + \cos \left(500\pi s^{-1} \right) t \right]$$

is connected in series with a capacitor and a resistor. The steady-state current in the circuit is found to be

$$I = i_1 \cos \left[\left(100\pi s^{-1} t + \phi_1 \right) \right] + i_2 \cos \left[\left(500\pi s^{-1} \right) t + \phi_2 \right]$$

.

A. $i_1 \geq i_2$

B. $i_1 = i_2$

C. $i_1 \leq i_2$

D. the information is insufficient to find the relation between i_1 and i_2 .


Answer: C



Watch Video Solution

72. In the circuit shown in figure the AC source gives a voltage $V = 20\cos(2000t)$. Neglecting source resistance, the voltmeter

and and ammeter readings will be

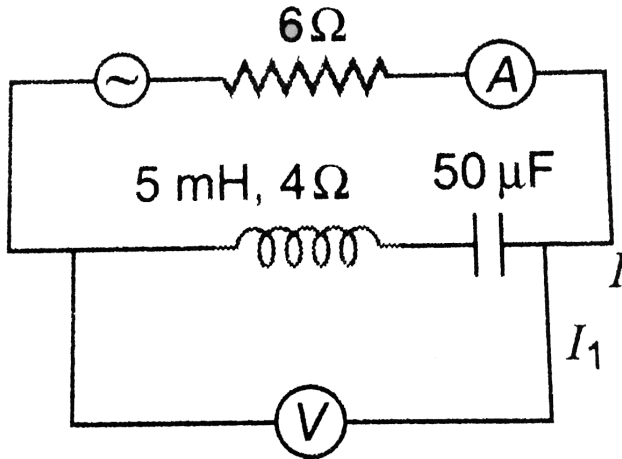

A. 0V , 0.47A


B. 1.68V , 0.47A

C. 0V , 1.4A

D. 5.6V , 1.4A

Answer: D

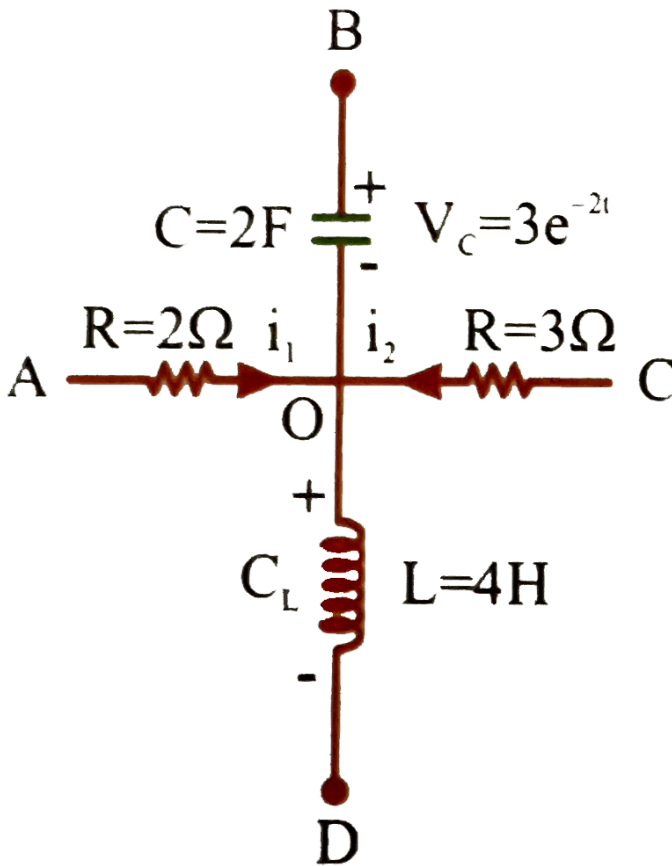73. In figure $i_1 = 10e^{-2t}A$, $i_2 = 4A$, $v_C = 3e^{-2t}V$



The current i_L is

A. $\left[2 - 2\left(1 - e^{-2t}\right)\right]A$

B. $\left[2 + 2\left(1 - e^{-2t}\right)\right]A$

C. $\left[3 - 2\left(1 - e^{-2t}\right)\right]A$


D. $\left[2 + 3\left(1 - e^{-2t}\right)\right]A$

Answer: B




Watch Video Solution

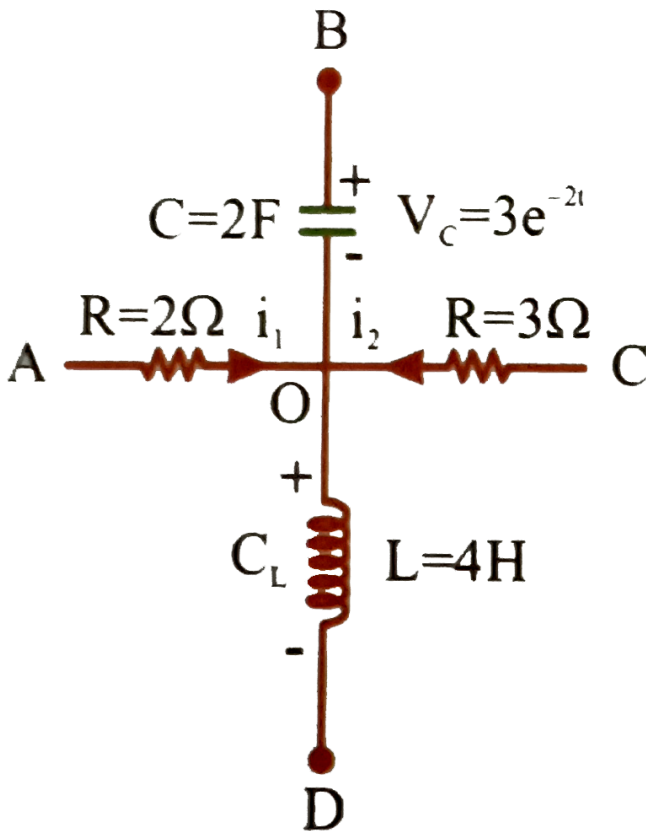74. In figure $i_1 = 10e^{-2t}A$, $i_2 = 4A$, $v_C = 3e^{-2t}V$




The variation of current in the inductor with time can be represented as :


A.

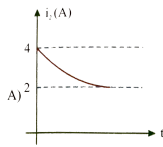


B.

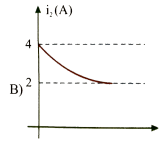

C.

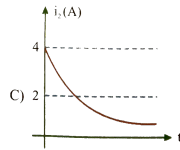

D.

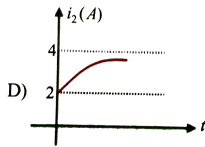


Answer: D



Watch Video Solution

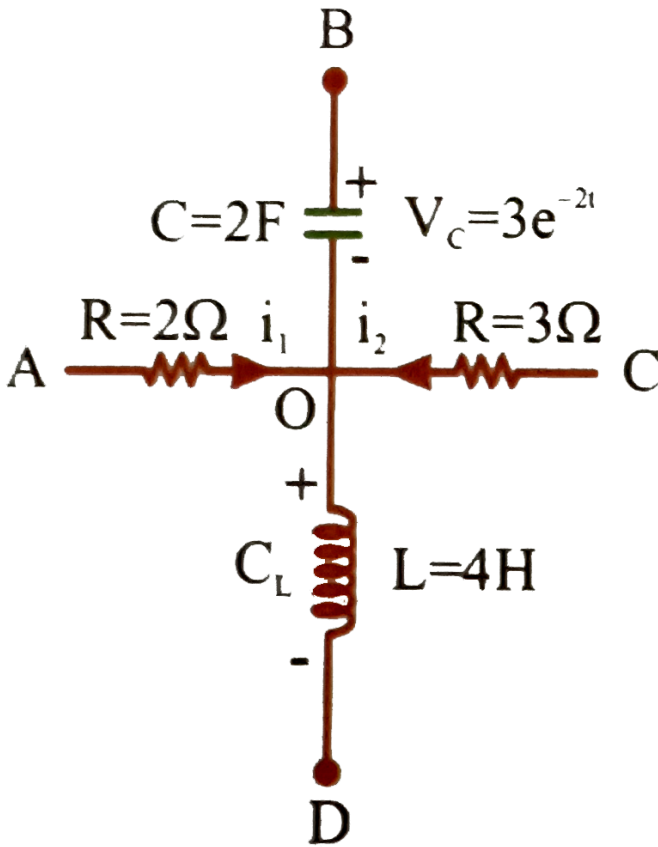75. In figure $i_1 = 10e^{-2t}A$, $i_2 = 4A$, $v_C = 3e^{-2t}V$



The potential difference across inductor V_L is :

A. $8e^{-2t}V$

B. $9e^{-2t}V$

C. $16e^{-2t}V$


D. $18e^{-2t}V$

Answer: C




Watch Video Solution

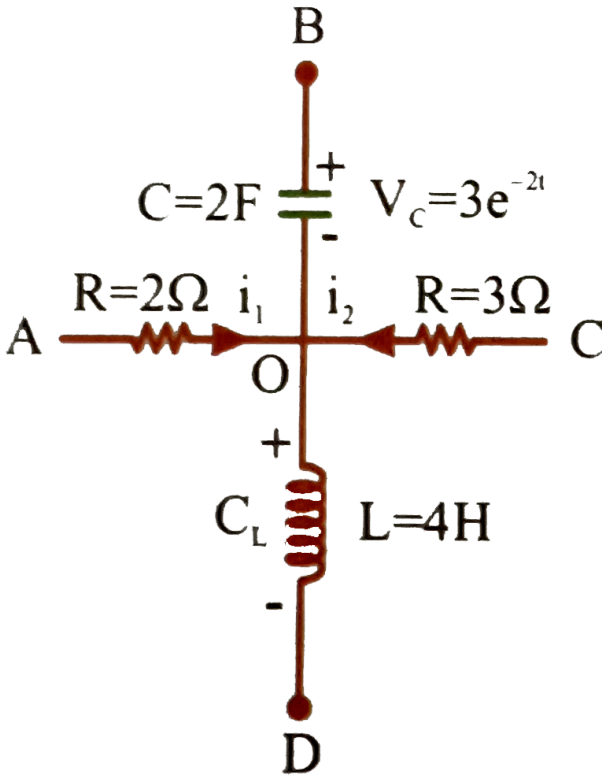
76. In figure $i_1 = 10e^{-2t}A$, $i_2 = 4A$, $v_C = 3e^{-2t}V$



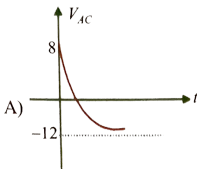
The variation of potential difference across A and C with time can be represented as




A.

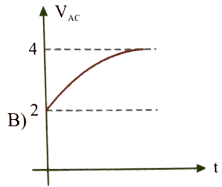

B.

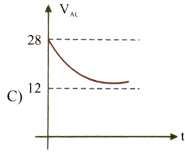

C.

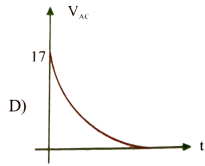


D.

Answer: A



Watch Video Solution

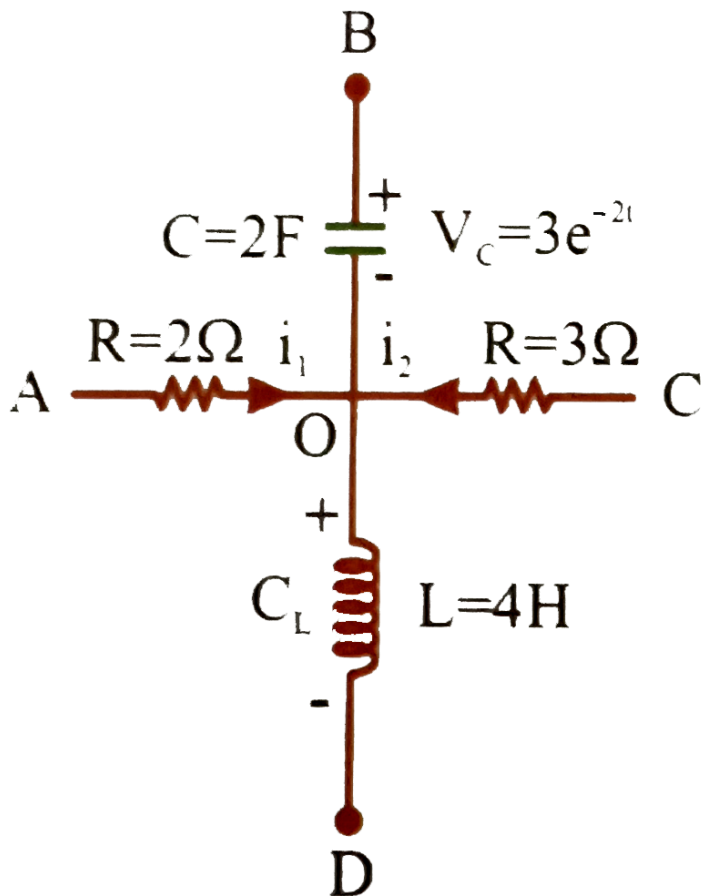77. In figure $i_1 = 10e^{-2t}\text{A}$, $i_2 = 4\text{A}$, $v_C = 3e^{-2t}\text{V}$



The potential difference across AB (V_{AB}) is:

A. $8e^{-2t}\text{V}$

B. $\frac{1}{2}e^{-3t}V$

C. $17e^{-2t}$


D. $16e^{-2t}V$

Answer: C




Watch Video Solution

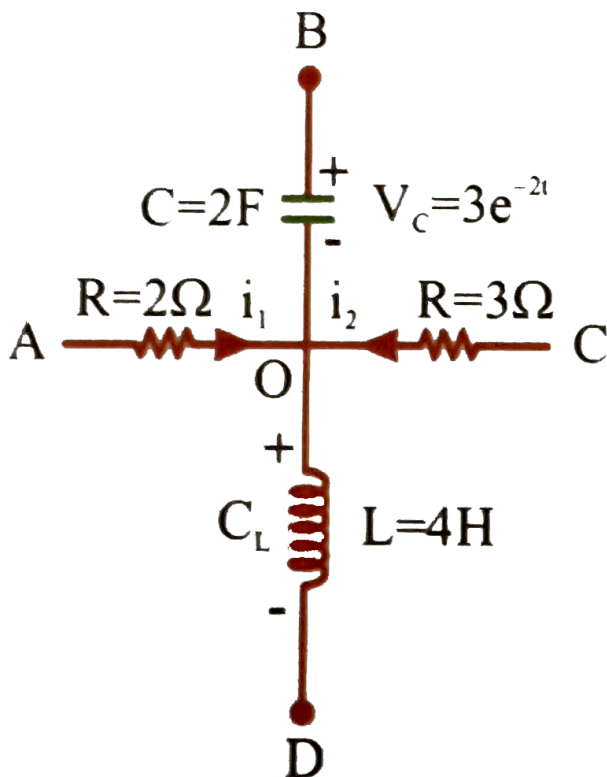
78. In figure $i_1 = 10e^{-2t}A$, $i_2 = 4A$, $v_C = 3e^{-2t}V$



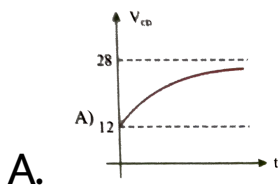
The variation of potential difference across A and C with time can be represented as




B.

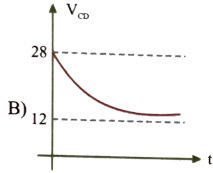

C.

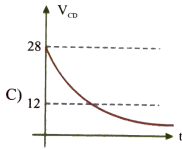

D.

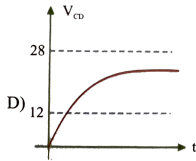


Answer: B



Watch Video Solution

79. An ac generator G with an adjustable frequency of oscillation is used in the circuit, as

shown.

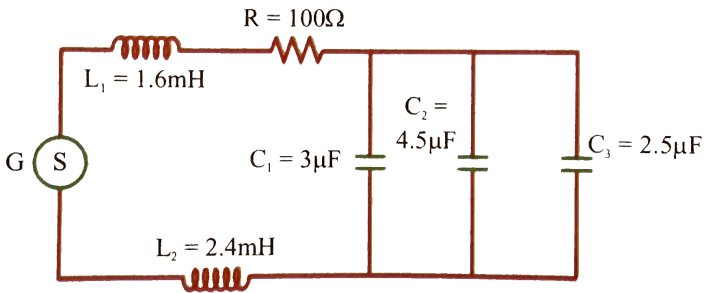

Current drawn from the ac source will be maximum if its angular frequency is


- A. 10^5rad/s
- B. 10^4rad/s
- C. 5000rad/s
- D. 50rad/s

Answer: C



Watch Video Solution

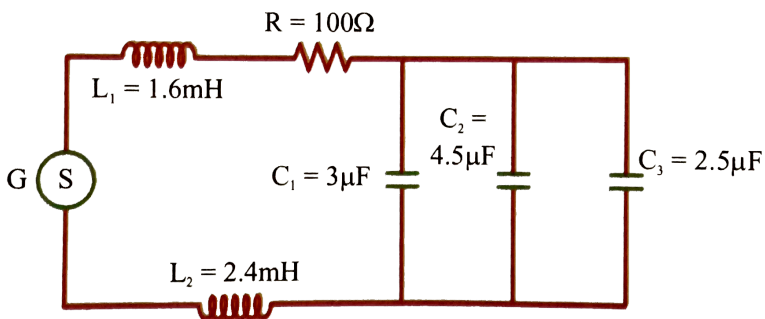80. An ac generator G with an adjustable frequency of oscillation is used in the circuit, as shown.



To increase resonant frequency of the circuit, some of the changes in the circuit are carried out. Which changes would certainly result in the increase in resonant frequency ?

A. R is increased

B. L_1 is increased and C_1 is decreased

C. L_2 is decreased and C_2 is increased


D. C_3 is removed from the circuit

Answer: D



Watch Video Solution

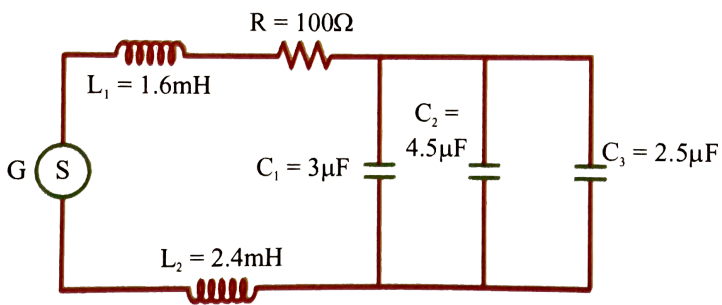81. An ac generator G with an adjustable frequency of oscillation is used in the circuit, as shown.



If the ac source G is 100V rating at resonant frequency of the circuit, then average power supplied by the source is


- A. 50W
- B. 100W
- C. 500W
- D. 1000W

Answer: B



Watch Video Solution

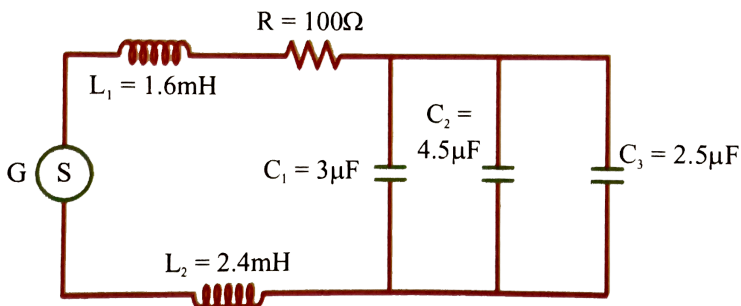82. An ac generator G with an adjustable frequency of oscillation is used in the circuit, as shown.



Average energy stored by the inductor L_2 (source is at resonance frequency) is equal to

A. zero

B. $1.2mJ$

C. $2.4mJ$


D. $4mJ$

Answer: B



Watch Video Solution

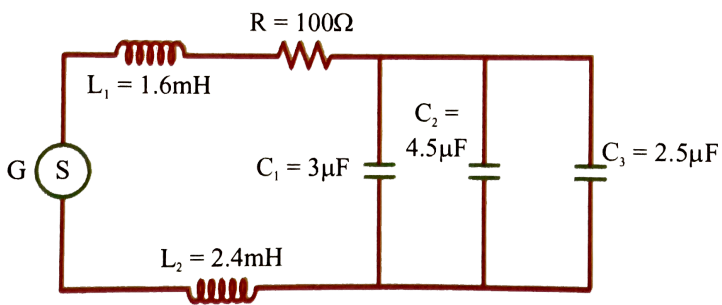83. An ac generator G with an adjustable frequency of oscillation is used in the circuit, as shown.



If the ac source G is 100V rating at resonant frequency of the circuit, then average power supplied by the source is

A. 0J

B. 1mJ

C. 100mJ

D. not possible to calculate from the given information

Answer: D




Watch Video Solution

LEVEL - VI

1. If a direct current of value ' a ' ampere is superimposed on an alternating current $I = b\sin\omega t$ flowing through a wire, what is the effective value of the resulting current in the

circuit?

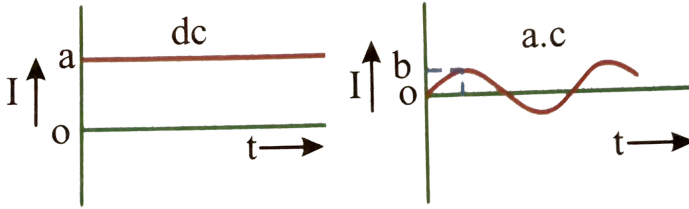

A. $\sqrt{a^2 + b^2}$

B. $\sqrt{a^2 + \frac{b^2}{2}}$

C. $\sqrt{\frac{a^2}{2} + b^2}$

D. $\sqrt{a^2 + \frac{b^2}{3}}$

Answer: B



Watch Video Solution

2. The secondary coil of an ideal step down transformer is delivering 500 watt power at 12.5A current. If the ratio of turns in the primary to the secondary is 5:1 then the current flowing in the primary coil will be:

A. 62.5A

B. 2.5A

C. 6A

D. 0.4A

Answer: B



Watch Video Solution

3. In a step-up transformer the turn's ratio is 10. If the frequency of the current in the primary coil is 50Hz then of the frequency of the current in the second ary coil will be

A. 500Hz

B. 5Hz

C. 60Hz

D. 50Hz

Answer: D



Watch Video Solution

4. An alternating voltage of 200 volt, at 400 cycles/sec is applied in a circuit containing an inductance of 0.01 henry in series with a resistance of 22.8 ohms. The voltage across the inductance is

A. 148.2 volt

B. 392.4 volt

C. 74.1 volt


D. 196.2 volt

Answer: A



Watch Video Solution

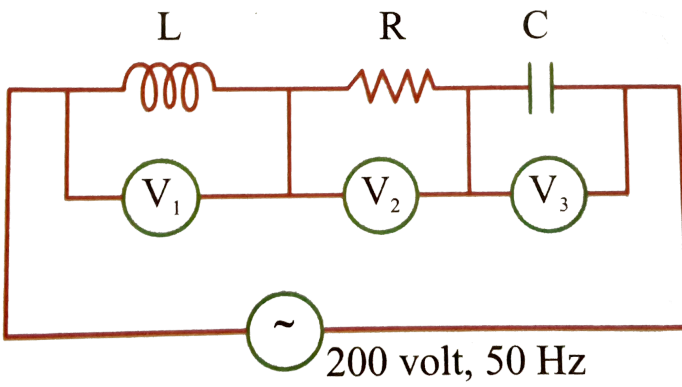5. If the readings V_1 and V_3 are 10. volt each, then reading of V_2 is:



A. 0 volt

B. 100 volt

C. 200 volt


D. cannot be determined by given information

Answer: C



Watch Video Solution

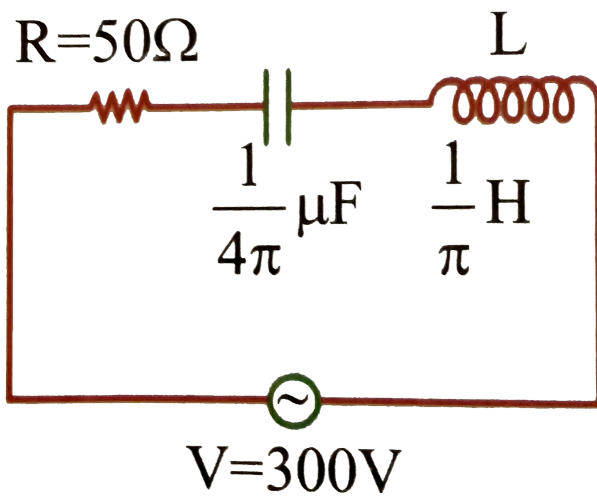6. In the a.c. circuit shown in the figure. The supply voltage has a constant r.m.s value V but variable frequency f . Resonance frequency in hertz is



A. 10

B. 100

C. 1000

D. 200

Answer: C



Watch Video Solution

7. If the power factor is $1/2$ in a series RL circuit with $R = 100\Omega$. If AC mains, $50Hz$ is used then L is

A. $\frac{\sqrt{3}}{\pi}$ henry

B. π henry

C. $\sqrt{3}$ henry

D. $\sqrt{3}\pi$ henry


Answer: A



Watch Video Solution

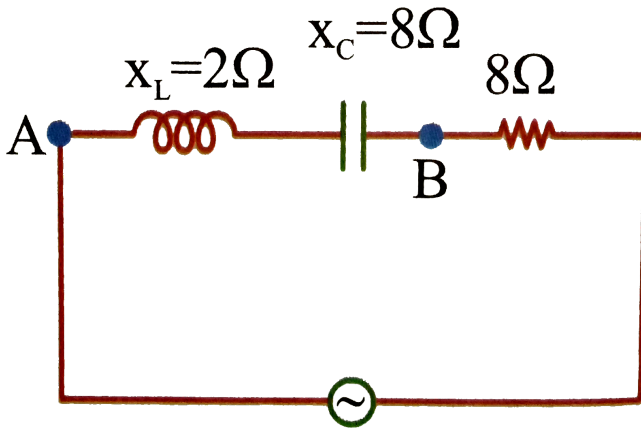8. An inductor ($X_L = 2\Omega$) a capacitor ($X_C = 8\Omega$) and a resistance (8Ω) are

connected in series with an ac source. The voltage output of A.C source is given by $v = 10\cos 100\pi t$. The instantaneous p.d. between A and B when is half of the voltage output from source will be:



- A. $\frac{24}{7}$ volt
- B. $\frac{24}{5}$ volt

C. $\frac{7}{24}$ volts

D. $\frac{5}{24}$ volts

Answer: B



Watch Video Solution

9. A resistor of resistance 100Ω is connected to an AC source $\varepsilon = (12V)\sin(250\pi s^{-1})t$. Find the energy dissipated as heat during $t = 0$ to $t = 1.0ms$.

A. $0.61 \times 10^4 J$

B. $0.61 \times 10^{-4} J$

C. $2.61 \times 10^{-4} J$


D. $2.61 \times 10^{-6} J$

Answer: C



Watch Video Solution

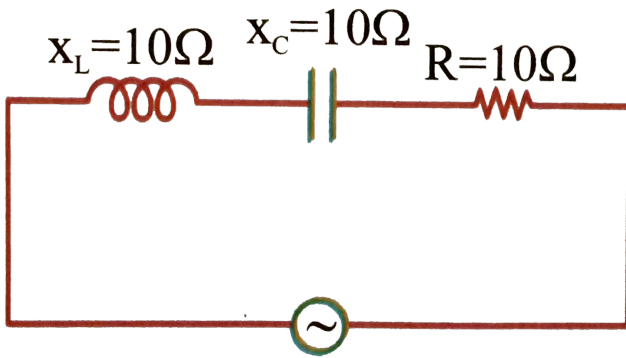10. In the given AC, circuit, which of the following is incorrect:



$$\varepsilon = 100 \sin (100\pi t + \pi/2)$$

- A. Voltage across resistance is lagging by 90° than the voltage across capacitor
- B. Voltage across capacitor is lagging by 180° than voltage across inductor
- C. Voltage across inductor is leading by 90° than voltage across resistance

D. resistance of the circuit is equal to
impedance reactance of circuit


Answer: A



Watch Video Solution

11. In the series circuit shown in the figure the
voltmeter reading will be (all the meters are

ideal).

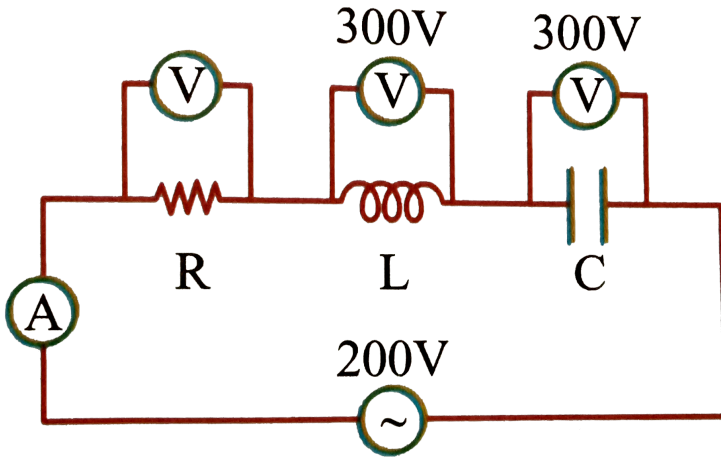

A. 300V

B. 200V

C. 100V


D. 600V

Answer: B

12. In the circuit shown in fig.

$X_C = 100\Omega$, $(X_L) = 200\Omega$ and $R = 100\Omega$. The

effective current through the source is

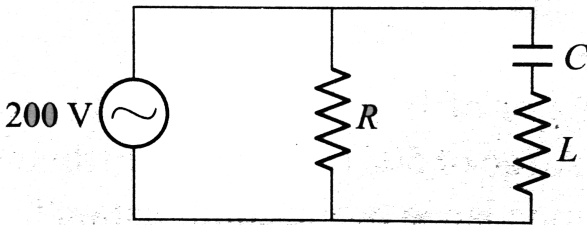

A. $2A$

B. $2\sqrt{A}$

C. $0.5A$

D. $\sqrt{0.4A}$


Answer: B



Watch Video Solution

13. In the given circuit assuming inductor and source to be ideal, the phase difference between

current I_1 and I_2 :

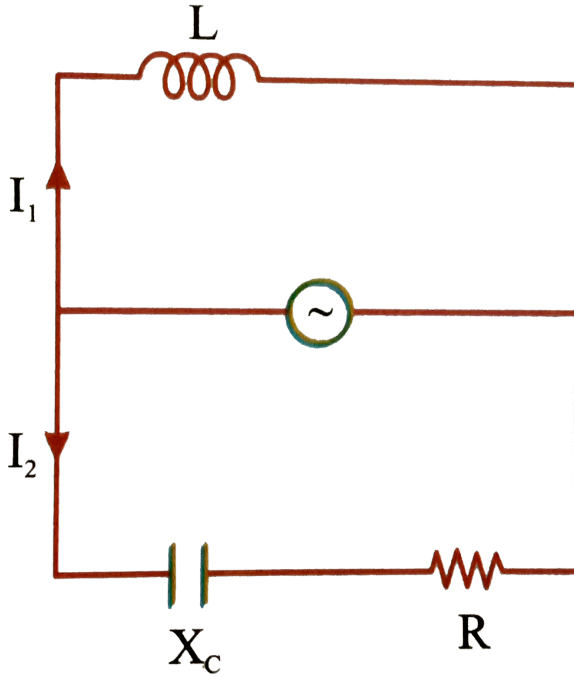

A. $\tan^{-1} \left(\frac{X_C}{R} \right) - \frac{\pi}{2}$

B. $\tan^{-1} \left(\frac{X_C}{R} \right)$

C. $\tan^{-1}\left(\frac{X_C}{R}\right) + \frac{\pi}{2}$

D. $\frac{\pi}{2}$

Answer: C




Watch Video Solution

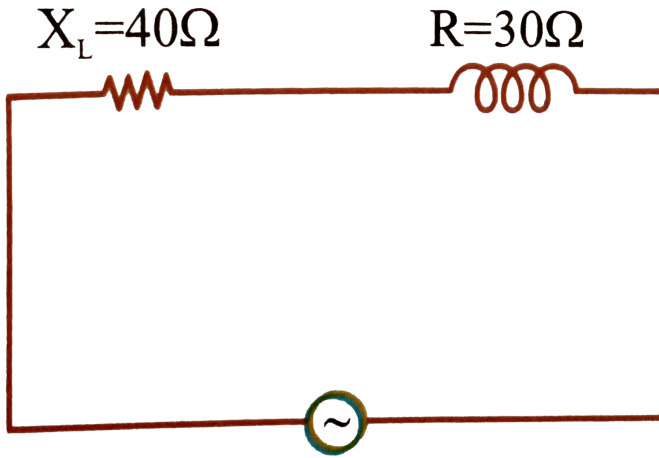14. In the circuit current through source will be

[Given $(\cos^{-1}(0.6) = 53^\circ)$]

$$V = 10 + 10\sqrt{2}\sin(100\pi + 45^\circ)$$




- A. $\frac{1}{3} + \frac{\sqrt{2}}{5}\sin(100\pi t - 8^\circ)$
- B. $\frac{1}{5} + \frac{\sqrt{2}}{5}\sin(100\pi t - 8^\circ)$
- C. $\frac{1}{3} + \frac{\sqrt{2}}{5}\sin(100\pi t - 98^\circ)$
- D. $\frac{1}{3} + \frac{\sqrt{2}}{5}\sin(100\pi t + 98^\circ)$

Answer: B



Watch Video Solution

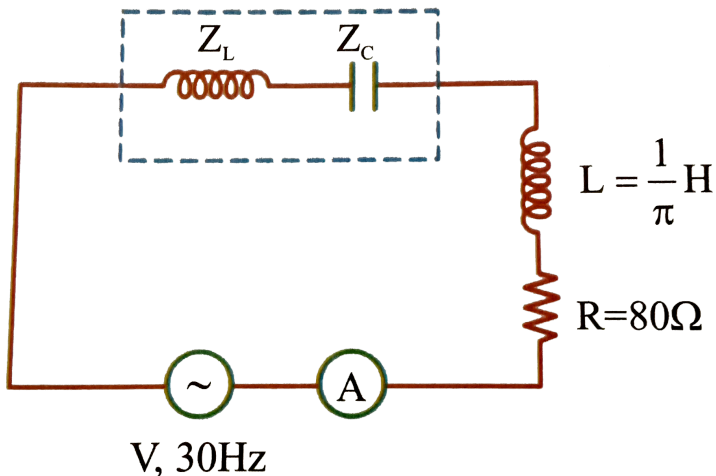15. In figure below if $Z_L = Z_C$ and reading of ammeter is 1A. Find value of source voltage V .



A. 80 volt

B. 60 volt

C. 100 volt


D. None

Answer: C



Watch Video Solution

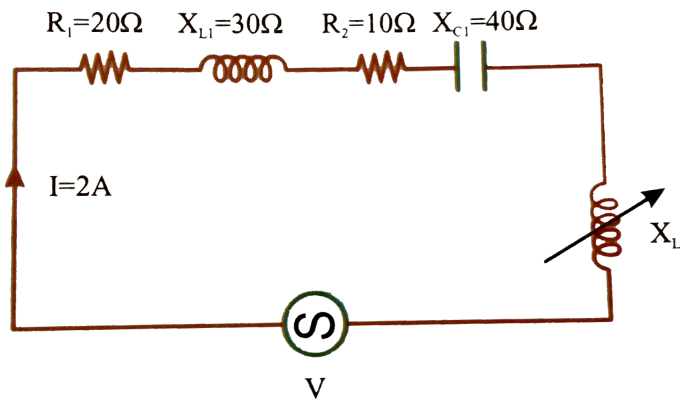16. As shown in figure value of inductive reactance X_L will be (source voltage is 100 volt)




- A. 40Ω
- B. 30Ω
- C. 50Ω
- D. Can have any value

Answer: C



Watch Video Solution

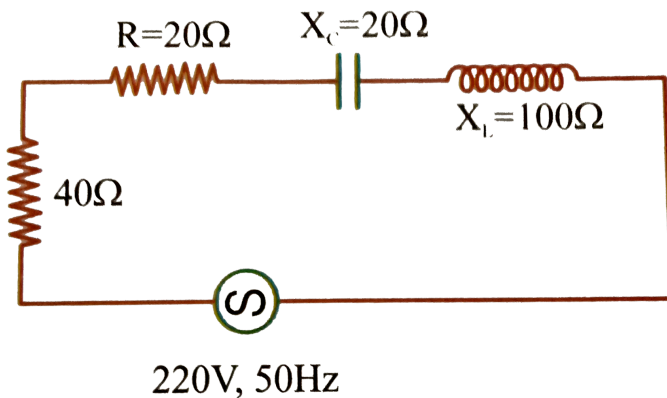17. The power factor of the circuit shown in the figure is



A. 0.4

B. 0.2

C. 0.8

D. 0.6

Answer: D



Watch Video Solution

18. In an $L - R - C$ circuit the current is given by $i = I \cos \omega t$. The voltage amplitudes for the resistor, inductor and capacitor are V_R , V_L and V_C respectively.

(a) The instantaneous power into the resistor is

$$P_R = V_R I \cos^2 \omega t.$$

(b) The instantaneous power into the inductor is

$$P_L = -V_L I \sin \omega t \cos \omega t$$

(c) The instantaneous power into the capacitor

is $P_c = V_c I \sin \omega t \cos \omega t$.

(d) $p_R + p_L + P_c$ equals total power p supplied by the source at each instant of time.

A. (a),(c),(d) are correct

B. (b),(c) are correct

C. (a) is correct

D. (a),(b),(c),(d) are correct


Answer: D



Watch Video Solution

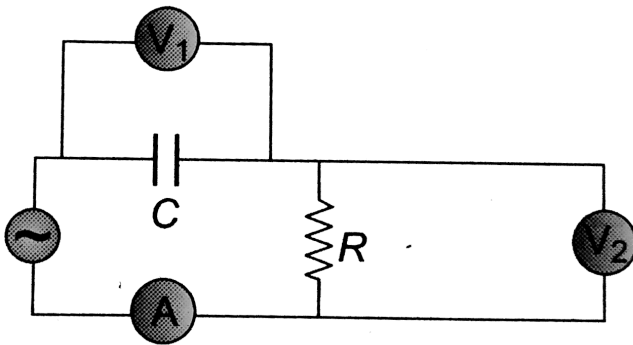19. The diagram shows a capacitor C and a resistor R connected in series to an AC source.

V_1 and V_2 are voltmeters and A is ammeter



Now, consider the following statements :

(I) Reading in A and V_2 are always in phase.

(II) Reading in V_1 is ahead in phase with reading in V_2 ,

(III) Reading in A and V_1 are always in phase.

Which of these statements are/is correct

A. I only

B. II only

C. I and II only

D. II and III only

Answer: A



Watch Video Solution

20. Two impedances Z_1 and Z_2 when connected separately across a 230V, 50Hz supply consume 100W and 60W at power factor of 0.5 lagging

and 0.6 leading respectively. If these impedances are now connected in series across the same supply, find

(a) total power absorbed and overall power factor

(b) the value of reactance to be added in series so as to raise the overall power factor to unity.

A. 19W, 295 Ω

B. 19W, 95 Ω

C. 99W, 195 Ω


D. 75W, 195 Ω

Answer: C



Watch Video Solution

21. In the *LCR* circuit shown in figure

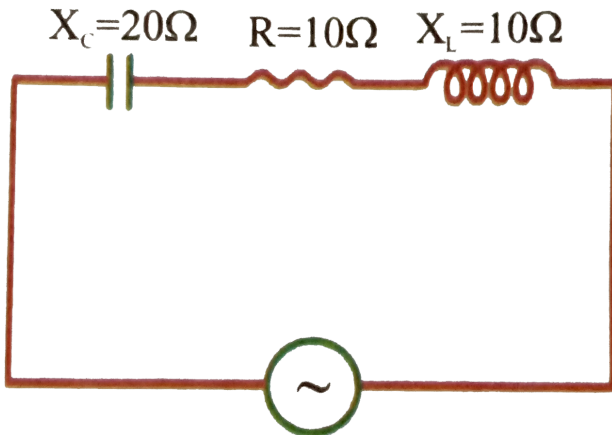

$$V = 200\sqrt{2} \sin \omega t$$

(a) current will lead the voltage

(2) rms value of current in 20A

(3) power factor of the circuit is $\frac{1}{\sqrt{2}}$

(4) voltage drop across resistance is 100V

A. (1) and (3) are correct

B. (1) and (4) are correct

C. (2) and (3) are correct


D. (3) and (4) are correct

Answer: A



Watch Video Solution

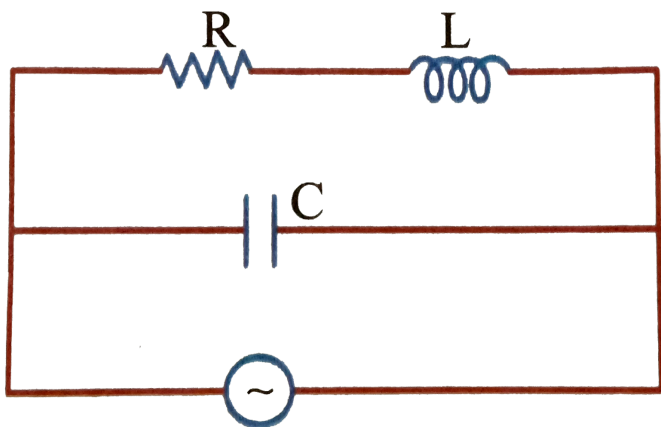22. The A. C circuit shown in figure. Find the frequency (ω_0) of the AC voltage source so that current through the source will be in same phase with the voltage of source.



$$\text{A. } \omega_0 = \sqrt{\frac{1}{LC} + \frac{R^2}{L^2}}$$

$$\text{B. } \omega_0 = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$C. W_0 = \frac{1}{\sqrt{LC}}$$

$$D. W_0 = \sqrt{\frac{1}{LC} + \frac{R^2}{4L} + \frac{R}{2L}}$$


Answer: B



Watch Video Solution

23. A resistance & ideal inductor is connected in the *A.C* circuit. Here V_1, V_2 & V_3 are the

reading of three hotwire ideal voltmeter

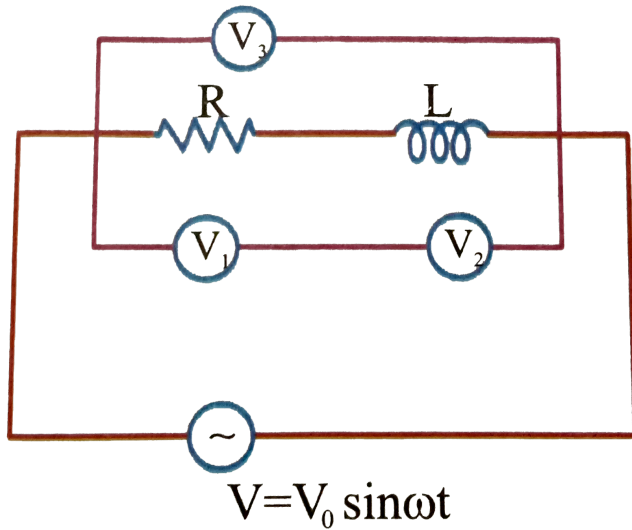

A. $V_3 = V_2 + V_1$

B. $V_3 > (V_1 + V_2)$

C. $V_3 < (V_1 + V_2)$

D. informations are insufficients to decide

Answer: C



Watch Video Solution

24. In an AC series circuit, the instantaneous current is zero when the instantaneous voltage is maximum. Connected to the source may be a

A. pure inductors

B. pure capacitor

C. pure resistor

D. combination of an inductor and a capacitor

Answer: A,B,D



Watch Video Solution

25. Which statement(s) is False for the series resonant condition

A. current maximum and phase difference between E and i is $\pi/2$

B. current maximum and phase difference between E and i is zero

C. voltage maximum and phase difference

between E and i is zero

D. voltage maximum and phase difference

between E and i is $\pi/2$

Answer: A,C,D



Watch Video Solution

26. An alternating EMF of frequency $\frac{1}{2\pi\sqrt{LC}}$ is applied to a series LCR circuit. For this

frequency of the applied EMF,

A. The circuit is at resonance and its impedance is made up only of a resistive part

B. The current in the circuit is in phase with the applied e.m.f and the voltage across R equal this applied emf

C. The sum of the p.d'a across the inductance and capacitance equals the

applied e.m.f which is 180° ahead of phase of the current in the circuit

D. The quality factor of the circuit is $\omega L/R$ or $1/\omega CR$ and this is a measure of the voltage magnification (produced by the circuit at resonance) as well as the sharpness of resonance of the circuit.

Answer: A,B,C



Watch Video Solution

27. An LC source rated $100V$ (rms) supplies a current of $10A$ (rms) to a circuit. The average power delivered by the source

A. must be $1000W$

B. may be $1000W$

C. may be greater than $1000W$

D. may be less than $1000W$

Answer: B,D



Watch Video Solution

28. In a $L - R$ circuit, the value of L is $\left(\frac{0.4}{\pi}\right)$ henry and the value of R is 30 ohm. If in the circuit, an alternating e.m.f of 200 vol at 50 cycles per sec is connected, the impedance of the circuit will be

A. 50 ohm

B. 60 ohm

C. 2 ampere

D. 4 ampere

Answer: A,D



Watch Video Solution

29. A circuit has three elements, a resistance of 11Ω , a coil of inductive reactance 120Ω and a capacitive reactance of 120Ω in series and connected to an A.C source of $110V, 60Hz$. Which of the three elements have minimum potential difference?

A. Resistance

B. Capacitance

C. Inductor

D. All will have equal potential difference

Answer: A



Watch Video Solution

30. An inductor 20×10^{-3} henry, a capacitor $100\mu F$ and a resistor 50Ω are connected in series across a source of emf $V = 10\sin 314t$.

(a) The energy dissipated in the circuit in 20 minutes is $951J$.

(b) If resistance is removed from the circuit and the value of inductance is doubled, then the

variation of current with time in the new circuit
is $0.52\cos(314t)$


- A. Both (a) and (b) are correct
- B. Both (a) and (b) are false
- C. Only (a) is corrects
- D. Only (b) is correct

Answer: A



Watch Video Solution

31. In a series *LCR* circuit

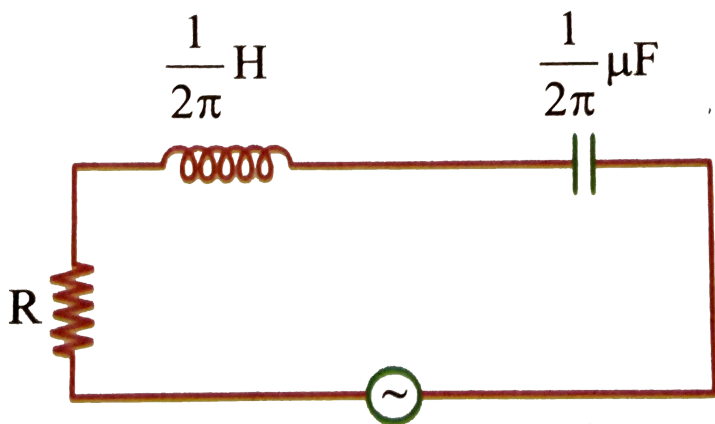

A. the voltage V_L across the inductance

leads the current in the circuit by a phase

angle of $\pi/2$

B. the voltage V_C across the capacitance

lags behind the current by a phase angle

of $\pi/2$

C. the voltage V_R across the resistance is in phase with the current


D. the voltage across series combination of L , C and R is $V = V_L + V_C + V_R$

Answer: A,B,C



Watch Video Solution

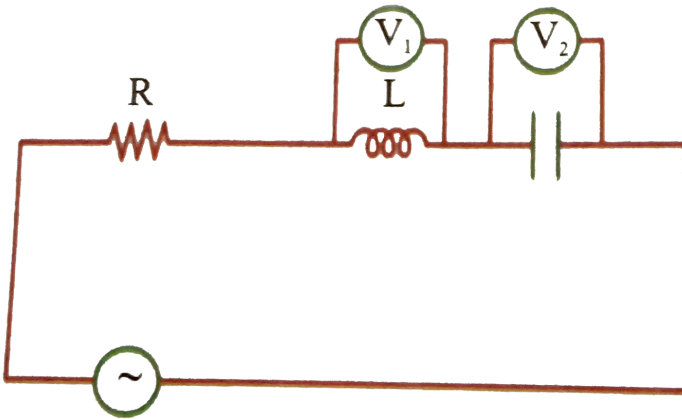32. In the figure shown $R = 100\Omega$, $L = \frac{2}{\pi}H$ and $C = \frac{8}{\pi}\mu F$ are connected in series with a.c source of 200 volt and frequency ' f '. V_1 and V_2 are two hot-wire voltmeters. If the readings of V_1 and V_2 are same then:



A. $f = 125Hz$

B. $f = 250Hz$

C. Current through R is $2A$


D. $V_1 = V_2 = 1000$ volt

Answer: A,C,D



Watch Video Solution

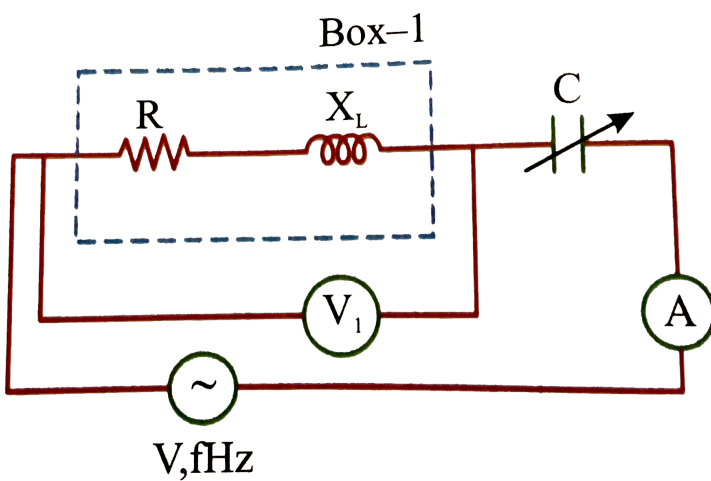33. Choose correct statement if capacitance increases from zero (0) to infinity ∞



- A. Current increases from 0 (Zero) to maximum then decreases to zero
- B. Reading of voltmeter first increases and it will be maximum when $X_L = X_C$
- C. Power factor of circuit first increases then decreases

D. V_1 may be greater than V , V_1 may be equal V , V_1 maybe less than V , where V_1 is reading of volmeter and V is source voltage.

Answer: A,B,C,D



Watch Video Solution

34. A box P and a coil Q are connected in series with an AC source of variable frequency. The emf of the source is constant at $10V$. Box P


contains a capacitance of $1\mu F$ in series with a resistance of 32Ω . Coil Q has a self-inductance 4.9 mH and a resistance of 68Ω in series. The frequency is adjusted to that the maximum current flows in P and Q . At this frequency

(a) The impedance of P is 77Ω

(b) The impedance of Q is 85Ω

(c) Voltage across P is $7.7V$

(d) Voltage across Q is 9.7V

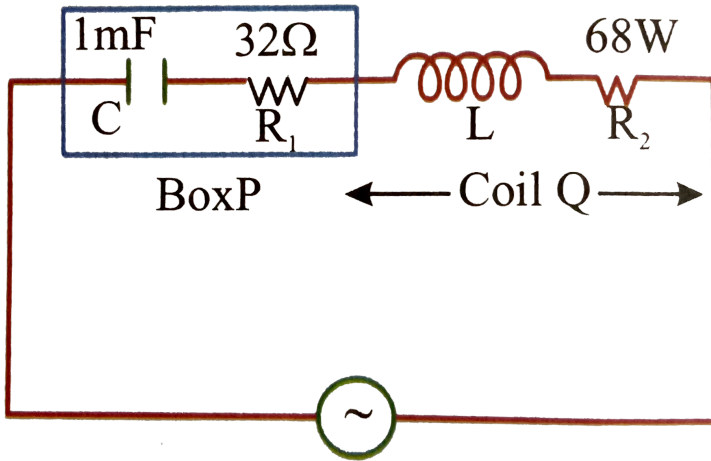

- A. Only (a),(c) are correct
- B. Only (a),(d) are correctd
- C. Only (c), (d) are correct
- D. (a),(c),(d) are correct

Answer: D



35. A series LCR circuit containing a resistance of 120Ω has angular resonance frequency $4 \times 10^5 \text{rads}^{-1}$. At resonance the voltages across resistance and inductance are $60V$ and $40V$ respectively.

(a) The value of L and C are 0.2 mH , $\frac{1}{32} \mu F$

(b) If angular frequency is changed to $8 \times 10^5 \text{rad/s}$, the current lags the voltage by 45°

(c) If angular frequency is changed to

$6 \times 10^5 \text{ rad/s}$, the current lags the voltage by 45°

- A. (a),(c) are correct
- B. (a),(b) are correct
- C. (a),(b) (c) are correct
- D. (a),(b),(c) are wrong

Answer: B



Watch Video Solution

36. A current of $4A$ flows in a coil when connected to a $12VDC$ source. If the same coil is connected to a $12V, 50rad/sAC$ source, a current of $2.4A$ flows in the circuit. Determine the inductance of the coil. Also, find the power developed in the circuit if a $2500\mu F$ capacitor is connected in series with the coil.

- A. (a), (c) are correct
- B. (b), (c) are correct
- C. (a), (b), (c) are correct
- D. Only (b) is correct

Answer: (A),(B),(C) are correct



Watch Video Solution

37. In the given series $R - L - C$ circuit,


$$R = 100\Omega, L = 10^{-3}H, C = 0.1\mu F, V_0 = 200V$$

(a) The resonant frequency is $15924Hz$

(b) The current at resonance is $1A$

(c) The power dissipated in the circuitd at

resonance is 100W

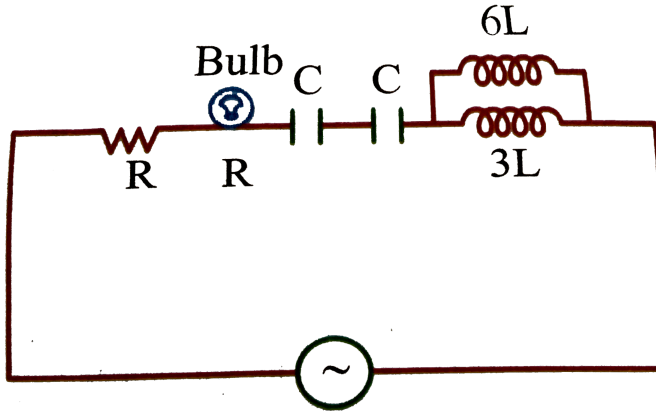

$$V = 200 \sin \omega t$$

- A. (a),(b),(c) are correct
- B. (a),(b),(c) are wrong
- C. Only (a),(b) are correct
- D. Only (b),(c) are correct

Answer: A



38. An alternating emf of frequency $f = 50\text{Hz}$ peak voltage $V_0 = 21$ volt is applied to a series circuit of resistance $R = 20$ ohm, an inductance $L = 100\text{mH}$ and a capacitor of $C = 30\mu\text{F}$.

(a) The maximum current is 3A

The phase difference between current and applied voltage is 75°

(c) The current i as a function of time ' t ' is

$$i = 3\sin(314t + 75^\circ)$$

A. Only (a),(b) are correct

B. Only (b),(c) are correct

C. (a),(b),(c) are correct

D. (a),(b),(c) are wrong

Answer: C



Watch Video Solution

39. A resistor R is connected in series with a coil. The system is subjected to an AC supply of peak voltage V_0 . If the peak voltages dropped across the resistor R and the coil are V_1 and V_2


respectively

(a) The power dissipated in the coil is

$$\frac{V_0^2 - V_1^2 - V_2^2}{2R}$$

The power dissipated in the circuit is

$$\frac{V_0^2 + V_1^2 - V_2^2}{2R}$$

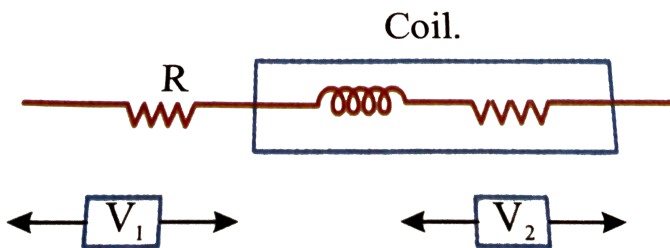

A. Only (a) is correct

B. Only (b) is correct

C. (a),(b) are wrong

D. (a),(b) are correct


Answer: D



Watch Video Solution

40. For the *AC* circuit shown, the reading of ammeter and voltmeter are $5A$ and $50\sqrt{5}$ volts

respectively, then

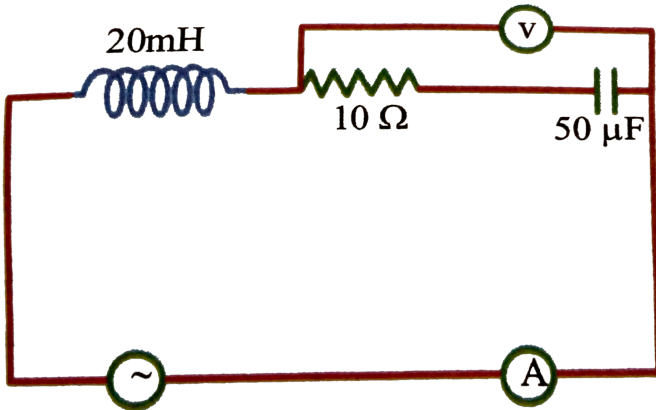

A. average power delivered by the source is

250W

B. rms value of AC source is 50 volts

C. voltage gain is 2


D. frequency of ac source is 1000rad/s

Answer: A,B,C,D



Watch Video Solution

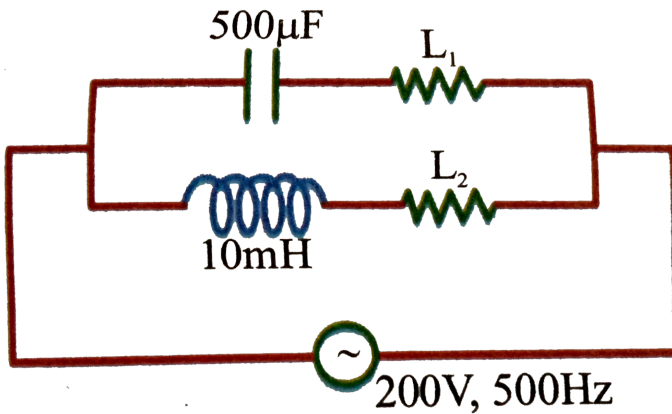41. In the circuit shown in Fig. If both the lamps L_1 and L_2 are identical.



A. their brightness will be same

B. L_1 will be brighter than L_2

C. As the frequency of supply voltage is increased, brightness of L_1 will increase and that of L_2 will decrease

D. Only L_2 will glow because the capacitor has infinite resistance

Answer: B,C



Watch Video Solution

42. A series LCR circuit with $L = 0.12H$, $C = 480nF$, and $R = 23\Omega$ is connected to a $230V$ variable frequency supply.

(a) What is the source frequency for which current amplitude is maximum? Find this maximum value.

(b) What is the source frequency for which average power absorbed by the circuit is maximum? Obtain the value of maximum power.

(c) For which frequencies of the source is the power transferred to the circuit half the power

at resonant frequency?

(d) What is the Q-factor of the circuit?

A. The source frequency 663Hz , current amplitude is maximum and this maximum value is 14.1A .

B. At the source frequency 663Hz average power absorbed by the circuit is maximum and the value of this maximum power is 2300W

C. At the frequencies 648Hz , 678Hz of the source, the power transferred to the circuit is half the power at resonant frequency. The current amplitude at these frequencies is 10A

D. The Q -factor of the given circuit is 21.7

Answer: A,B,C,D



Watch Video Solution

43. An ac source of angular frequency ω is fed across a resistor R and a capacitor C in series. The current registered is I . If now the frequency of source is changed to $\omega/3$ (but maintaining the same voltage), the current in the circuit is found to be halved. Calculate the ratio of the reactance to resistance at the original frequency ω .

A. $\sqrt{\frac{3}{5}}$

B. $\sqrt{\frac{5}{3}}$

C. $\sqrt{\frac{3}{4}}$

D. $\sqrt{\frac{4}{3}}$

Answer: A



Watch Video Solution

44. A circuit has a coil of resistance 60 ohm and inductance 3 henry. It is connected in series with a capacitor of $4\mu F$ and A.C supply voltage of 200V and 50 cycle/sec

A. the impedance of the coil is 943Ω

B. the impedance of the coil is 843Ω

C. the p.d. across the inductor coil is $1110V$

D. the p.d. across the capacitor is $924V$

Answer: A,C,D



Watch Video Solution

45. A circuit consists of a noninductive resistor of 50Ω , a coil of inductance $0.3H$ and resistance 2Ω , and a capacitor of $40\mu F$ in series and is

supplied with 200 volt rms at 50 cycles / sec.

Then

A. the current lag or lead by an angle $15^\circ 51'$

B. the power in the circuit is 710.4W

C. the power in th circuit is 640W

D. the current lag or lead by an angle $12^\circ 51'$

Answer: A,B



Watch Video Solution

46. A coil of resistance 300Ω and inductance 1.0 henry is connected across an voltages source of frequency $300/2\pi\text{Hz}$. The phase difference between the voltage and current in the circuit is

A. $\frac{\pi}{2}$

B. $\frac{\pi}{4}$

C. $\frac{\pi}{3}$

D. $\frac{\pi}{6}$

Answer: B



Watch Video Solution

47. A circuit draws a power of 550 watt from a source of 220 volt, 50Hz. The power factor of the circuit is 0.8 and the current lags in phase behind the potential difference. To make the power factor of the circuit as 1.0, The capacitance should be connected in series with it is

A. $75\mu F$

B. $60\mu F$

C. $50\mu F$

D. $65\mu F$


Answer: A



Watch Video Solution

48. In the figure shown V_1, V_2, V_3 are AC voltmeters and A is AC ammeter. The readings of V_1, V_2, V_3 and $10V, 20V, 20V, 2A$ respectively.

If the inductor is short circuited, then

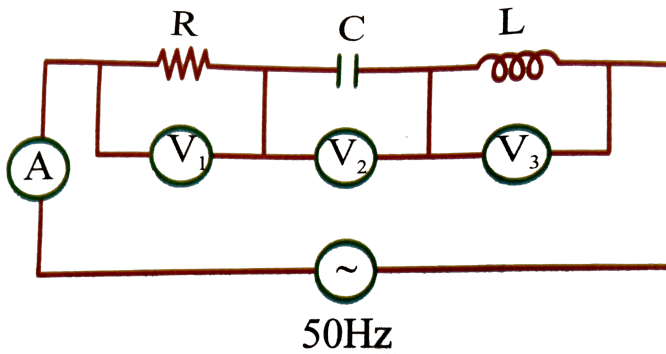

A. the reading of V_1 is $2\sqrt{5}V$

B. the reading of V_2 is $4\sqrt{5}V$

C. the reading of V_2 is $2\sqrt{5}V$

D. the value of A is $\frac{2}{\sqrt{5}}A$

Answer: A,B,D



Watch Video Solution

49. In a series LCR circuit with an ac source of $50V$, $R = 300\Omega$, frequency $\nu = \frac{50}{\pi} Hz$. The average electric field energy, stored in the capacitor and average magnetic energy stored in the coil are $25mJ$ and $5mJ$ respectively. The RMS current in the circuit is $0.10A$. Then find

A. capacitance C of capacitor is $20\mu F$

B. inductance L of inductor is $2H$

C. peak voltage of source is $50V$

D. the sum of rms voltage across the three elements is $35.4V$

Answer: A,B,C,D



Watch Video Solution

50. An $L - C - R$ series circuit with 100Ω resistance is connected to an AC source of $200V$ and angular frequency $300rad/s$. When only the capacitance is removed, the current lags behind the voltage by 60° . When only the

inductance is removed the current leads the voltage by 60° . Calculate the current and the power dissipated in the $L - C - R$ circuit

A. 200W

B. 100W

C. 50W

D. 400W


Answer: D



Watch Video Solution

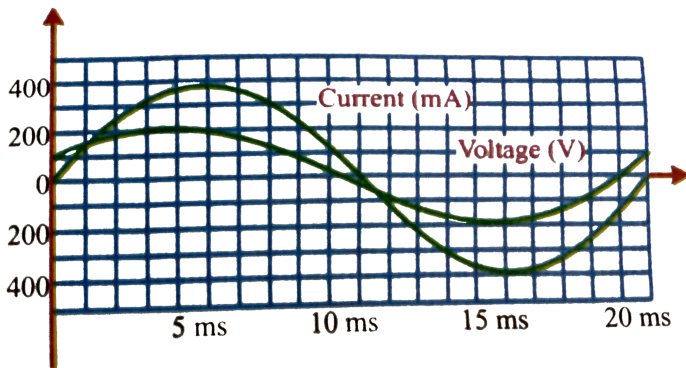51. The given graph shows variation with time in the source voltage and steady state current drawn by a series RLC circuit. Given curve through origin is the current variation.

Which of the following statements is/are correct ?



A. current lag the voltage

B. Resistance in the circuits is $250\sqrt{3}\Omega$

C. If capacitive reactance is 74Ω , inductance in the circuit is approximately $560mH$.

D. Average power dissipation in the circuit is $20\sqrt{3}W$.

Answer: A,B,D



Watch Video Solution

52. A 100Ω resistance is connected in series with a $4H$ inductor. The voltage across the

resistor is, $V_R = (2.0\text{V})\sin(10^3t)$.

Find the expression of circuit current

A. $(2 \times 10^{-2}\text{A})\sin(10^3t)$

B. $(2 \times 10^{-3}\text{A})\sin(10^2t)$

C. $(2 \times 10^{-3}\text{A})\sin(10^3t)$

D. $(2 \times 10^{-2}\text{A})\sin(10^2t)$

Answer: A



Watch Video Solution

53. A 100Ω resistance is connected in series with a $4H$ inductor. The voltage across the resistor is, $V_R = (2.0V)\sin(10^3t)$.

Find the inductive reactance

A. 2×10^3 ohm

B. 3×10^3 ohm

C. 4×10^3 ohm

D. 5×10^3 ohm

Answer: C



Watch Video Solution

54. A 100Ω resistance is connected in series with a $4H$ inductor. The voltage across the resistor is, $V_R = (2.0V)\sin(10^3t)$.

Find amplitude of the voltage across the inductor.

A. $40V$

B. $60V$

C. $80V$

D. $90V$

Answer: C



Watch Video Solution

55. If various elements, i.e., resistance capacitance and inductance which are in series and having values 1000Ω , $1\mu F$ and $2.0H$ respectively. Given emf as, $V = 100\sqrt{2}\sin 1000t$ volts

Voltage across the resistor is

A. 70.7 Volts

B. 100 Volts

C. 141.4 Volts

D. 270.7 Volts

Answer: A



Watch Video Solution

56. If various elements, i.e., resistance capacitance and inductance which are in series and having values 1000Ω , $1\mu F$ and $2.0H$ respectively. Given emf as, $V = 100\sqrt{2}\sin 1000t$

volts

voltage across the inductor is

A. 70.7 Volts

B. 101 Volts

C. 141.4 Volts

D. 270.7 Volts

Answer: C



Watch Video Solution

57. If various elements, i.e., resistance capacitance and inductance which are in series and having values 1000Ω , $1\mu F$ and $2.0H$ respectively. Given emf as, $V = 100\sqrt{2}\sin 1000t$ volts

voltages across the capacitor is

A. 70.7 Volts

B. 102 Volts

C. 141.4 Volts


D. 270.7 Volts

Answer: A



Watch Video Solution

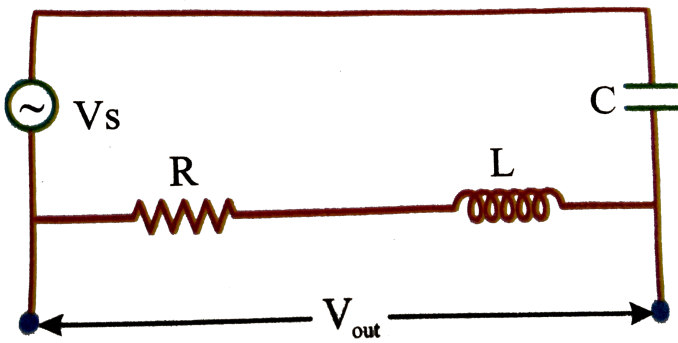58. One application of $L - R - C$ series circuit is in high pass or low pass filter, which out either the low or high frequency components of a signal. A has pass filter is shown in figure where the output voltage is taken across the $L - R$ where $L - R$ combination represents and inductive coil that also has resistance due to the large length of the wire in the coil.



Find the ratio V_{out}/V_s as a function of the angular frequency ω of the source

A.
$$\sqrt{\frac{R^2 + \omega L^2}{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

B.
$$\sqrt{\frac{R^2 + \omega^2 L^2}{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

C. $\sqrt{\frac{R^2 + \omega^2 L}{R^2 + \left(\omega C - \frac{1}{\omega L}\right)^2}}$

D. 1


Answer: B



Watch Video Solution

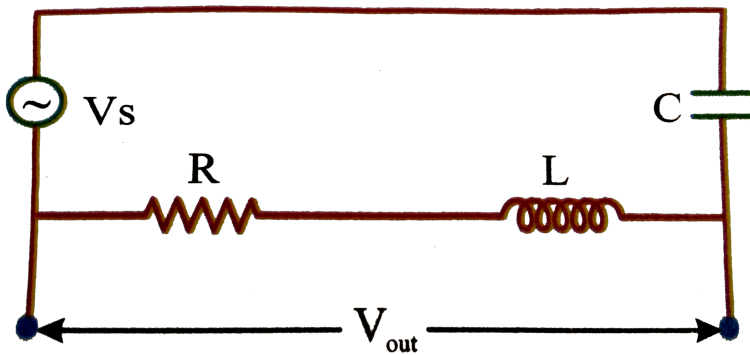59. One application of $L - R - C$ series circuit is in high pass or low pass filter, which out either the low or high frequency components of a signal. A has pass filter is shown in figure where

the output voltage is taken across the $L - R$ where $L - R$ combination represents and inductive coil that also has resistance due to the large length of the wire in the coil.



which of the following statements is correct when ω is small in the case of V_{out}/V_s

A. ωRC

B. $\frac{\omega R}{L}$

C. ωRL

D. $\frac{\omega R}{C}$


Answer: A



Watch Video Solution

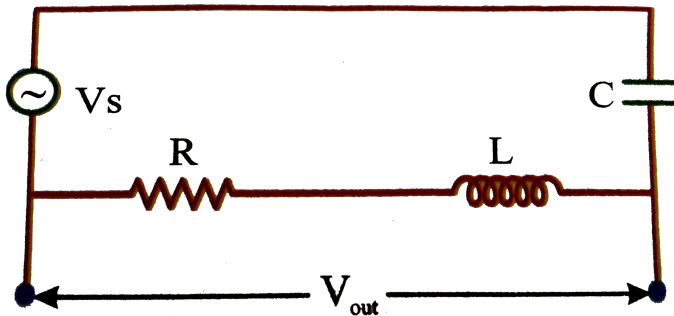60. One application of $L - R - C$ series circuit is in high pass or low pass filter, which out either the low or high frequency components of a signal. A has pass filter is shown in figure where the output voltage is taken across the $L - R$

where $L - R$ combination represents an inductive coil that also has resistance due to the large length of the wire in the coil.



Which statement is correct in the limit of large frequency is reached? (for V_{out}/V_s)

A. 1

B. ωRC

C. ωRL

D. $\frac{\omega R}{L}$

Answer: A



Watch Video Solution

61. In *A.C* source peak value of *A.C* is the maximum value of current in either direction of the cycle. Root mean square (*RMS*) is also defined as the direct current which produces the same heating effect in a resistor as the actual *A.C*

A.C measuring instrument measures its

A. rms value

B. Peak value

C. Average value

D. Square of current

Answer: A







Watch Video Solution

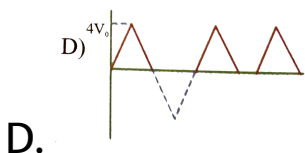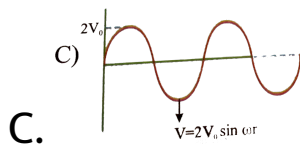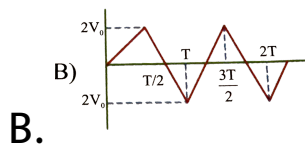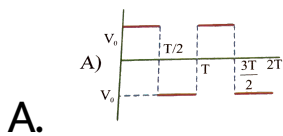62. In *A.C* source peak value of *A.C* is the maximum value of current in either direction of the cycle. Root mean square (*RMS*) is also

defined as the direct current which produces the same heating effect in a resistor as the actual A.C

Current time graph of different source is given which one will have R.M.S value V_0




Answer: A



Watch Video Solution

63. In A.C source peak value of A.C is the maximum value of current in either direction of the cycle. Root mean square (*RMS*) is also defined as the direct current which produces the same heating effect in a resistor as the actual A.C

Average voltage for the given source is

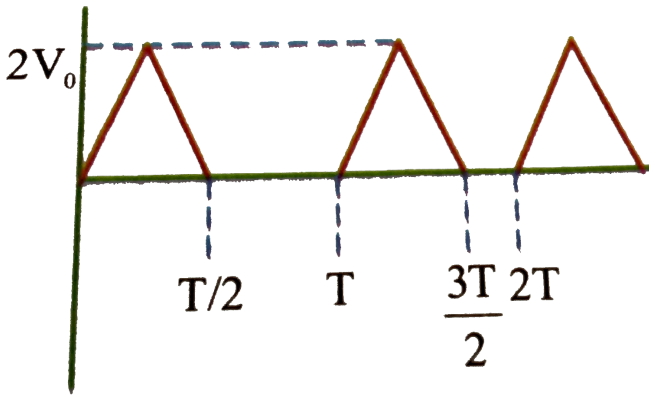

A. V_0

B. $2V_0$


C. $\frac{V_0}{2}$

D. $\frac{3V_0}{2}$

Answer: C



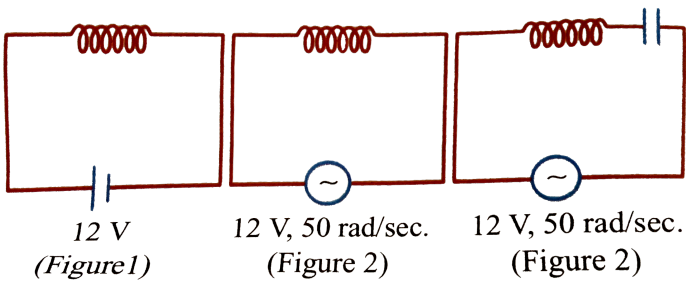64. A steady 4A flows in an inductor coil when connected to a 12V source as shown in figure. If the same coil is connected to an ac source of 12V, 50rad/s a currentd of 2.4A flows in the circuit as shown in figure2. Now after these observations , a capacitor fo capacitance $\frac{1}{50}F$ is connected in series with the coil and with same AC source as shown in figure 3.




The resistance of the coil is:

- A. $0.01H$
- B. $0.02H$
- C. $0.04H$
- D. $0.08H$

Answer: A

 [Watch Video Solution](#)

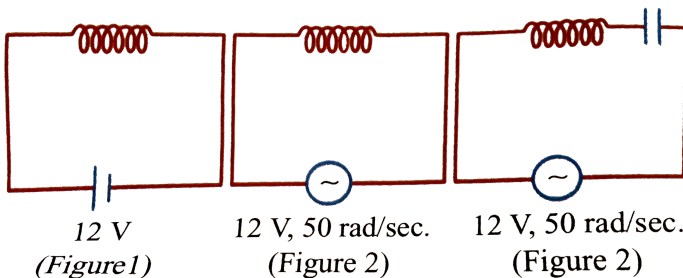65. A steady 4A flows in an inductor coil when connected to a 12V source as shown in figure. If the same coil is connected to an ac source of 12V, 50rad/s a current of 2.4A flows in the circuit as shown in figure2. Now after these observations, a capacitor of capacitance $\frac{1}{50}F$ is connected in series with the coil and with same AC source as shown in figure 3.



The resistance of the coil is:

A. 1Ω

B. 2Ω

C. 3Ω

D. 4Ω


Answer: C



Watch Video Solution

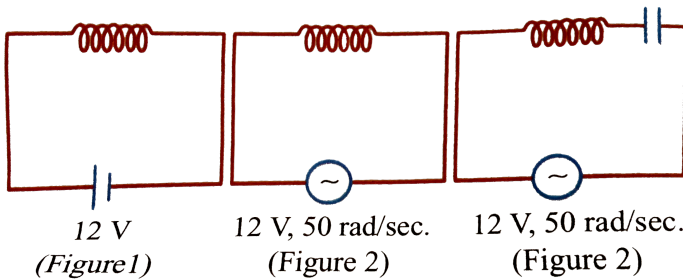66. A steady $4A$ flows in an inductor coil when connected to a $12V$ source as shown in figure. If the same coil is connected to an ac source of

12V, 50rad/s a current of 2.4A flows in the circuit as shown in figure 2. Now after these observations, a capacitor of capacitance $\frac{1}{50}F$ is connected in series with the coil and with same AC source as shown in figure 3.



The resistance of the coil is:

- A. 24W
- B. 72W
- C. 144W

D. 18.2W

Answer: D



Watch Video Solution

67. In a series L-R circuit, connected with a sinusoidal ac source, the maximum potential difference across L and R are respectively 3 volts and 4 volts.

At an instant the potential difference across resistor is 2 volts. The potential difference in

volt, across the inductor at the same instant will be:

A. $3\cos 30^\circ$

B. $3\cos 60^\circ$

C. $6\cos 45^\circ$

D. 6

Answer: A



Watch Video Solution

68. In a series $L - R$ circuit, connected with a sinusoidal ac source, the maximum potential difference across L and R are respectively 3 volts and 4 volts

At the same instant, the magnitude of the potential difference in volt, across the ac source will be

A. $3\cos 67^\circ$

B. $5\sin 37^\circ$

C. $4\cos 97^\circ$

D. 0

Answer: B



Watch Video Solution

69. In a series $L - R$ circuit, connected with a sinusoidal ac source, the maximum potential difference across L and R are respectively 3 volts and 4 volts

If the current at this instant is decreasing the magnitude of potential difference at that instant across the ac source is

A. increasing

B. decreasing

C. Constant

D. Can't be said

Answer: A



Watch Video Solution

70. A constant voltage at a frequency of 1MHz is applied to an inductor in series with variable capacitor, when capacitor is 500pF , the current has its maximum value, while it is reduced to

half when capacitance is 600pF . Find

Resistance (R)

A. 30Ω

B. 20Ω

C. 40Ω

D. 50Ω

Answer: A



Watch Video Solution

71. A constant voltage at a frequency of 1MHz is applied to an inductor in series with variable capacitor, when capacitor is 500pF , the current has its maximum value, while it is reduced to half when capacitance is 600pF . Find

The inductance L

A. 0.05mH

B. 0.5mH

C. 0.005mH

D. 5mH

Answer: A



Watch Video Solution

72. A constant voltage at a frequency of 1MHz is applied to an inductor in series with variable capacitor, when capacitor is 500pF , the current has its maximum value, while it is reduced to half when capacitance is 600pF . Find Q factor of the circuit is

A. 10.4

B. 20.8

C. 5.2

D. 9.4

Answer: A



Watch Video Solution

73. When $1A$ is passed through three coils A, B, C in series the voltage drops are respectively $6,3$ and 8 volt on direct current source and $7,5$ and 10 volt on Alternating

current source

Power factor of coil B , will be

A. 0.6

B. 0.8

C. 0.7

D. None

Answer: A



Watch Video Solution

74. When 1A is passed through three coils A, B, C in series the voltage drops are respectively 6,3 and 8 volt on direct current source and 7,5 and 10 volt on Alternating current source

Power dissipated in coil C

A. 10 watt

B. 6 watt

C. 5 watt

D. 8 watt

Answer: D



Watch Video Solution

75. When $1A$ is passed through three coils A, B, C in series the voltage drops are respectively $6,3$ and 8 volt on direct current source and $7,5$ and 10 volt on Alternating current source

Power factor of whole circuit when alternating current flow

A. 0.6

B. 0.8

C. 0.78

D. 1


Answer: C



Watch Video Solution

76. A series circuit connected across a 200V, 60Hz line consists of a capacitive reactance 30Ω non inductive resistor of 44Ω and a coil of inductive reactance 90Ω and

resistance 36Ω as shown in the diagram

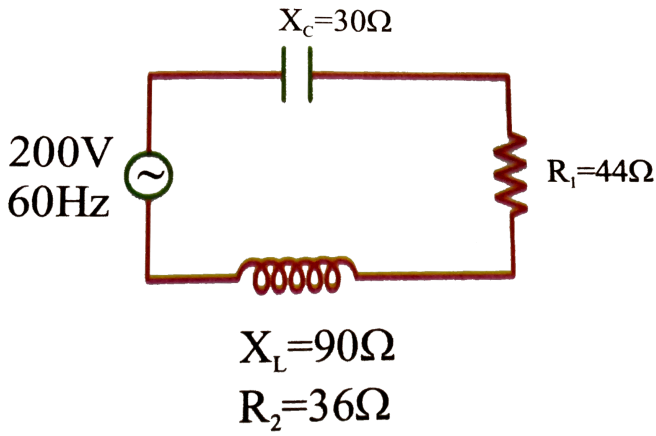

The potential difference across the coil is


- A. 100v
- B. 194V
- C. 97V
- D. zero

Answer: B



Watch Video Solution

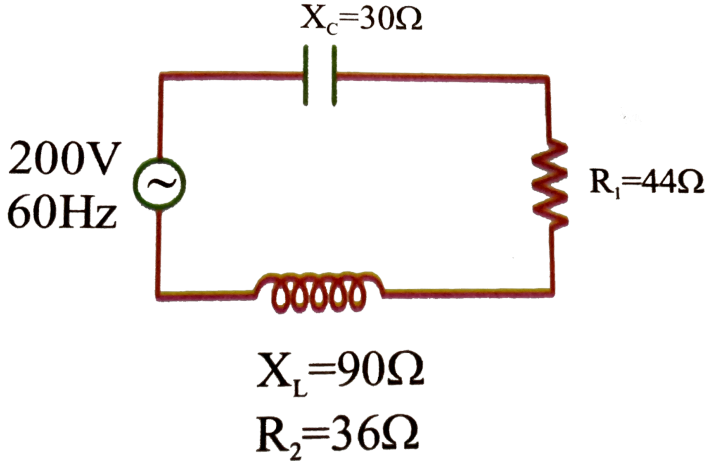77. A series circuit connected across a 200V, 60Hz line consists of a capacitive reactance 30Ω non inductive resistor of 44Ω and a coil of inductive reactance 90Ω and resistance 36Ω as shown in the diagram




The power used in the circuit is

- A. 320W
- B. 144W
- C. 160W
- D. 96W

Answer: A

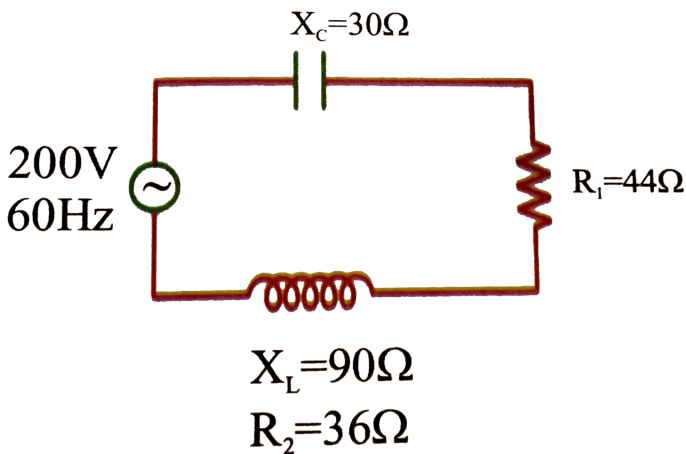78. A series circuit connected across a 200V, 60Hz line consists of a capacitive reactance 30Ω non inductive resistor of 44Ω and a coil of inductive reactance 90Ω and resistance 36Ω as shown in the diagram



The power dissipated in the inductance coil is

A. zero

B. 320W

C. 144W

D. 160W


Answer: C



Watch Video Solution

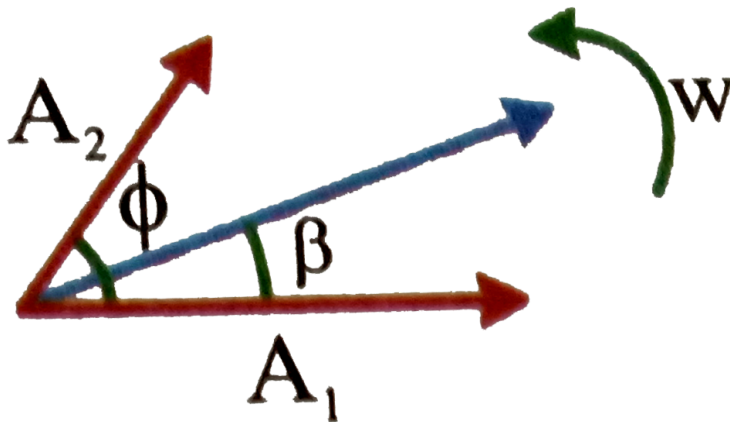79. The maximum values of the phasors (currents and voltage) in *AC* circuits can be treated as vectors rotating with an angular

frequency equal to the angular frequency of the rotor of the generator. If the phase difference between two phasors A_1 and A_2 is ϕ the resultant phasor is :



$$A = \sqrt{A_1^2 + A_2^2 + 2A_1A_2\cos\phi}$$

and the phase of \vec{A} with respects to A_1 is

$$\beta = \tan^{-1} \frac{A_2 \sin\phi}{A_1 + A_2 \cos\phi}$$

RHS value

The rms value of $y = f(t)$ is

$$y_{\text{rms}} = \left\{ \frac{\int_0^T [f(t)]^2 dt}{T} \right\}^{\frac{1}{2}}$$

Average value


The average value of $y = f(t)$ is $y_{\text{av}} = \frac{\int_0^T y dt}{T}$

Using the above concept, answer the following questions.

The current i_1 and i_2 in A. C circuit are given as:

$$i_1 = 4\sin\left(\omega t - \frac{\pi}{3}\right) \text{ and } i_2 = 4\sin\left(\omega t + \frac{\pi}{3}\right)$$

The current i_3 can be given as :

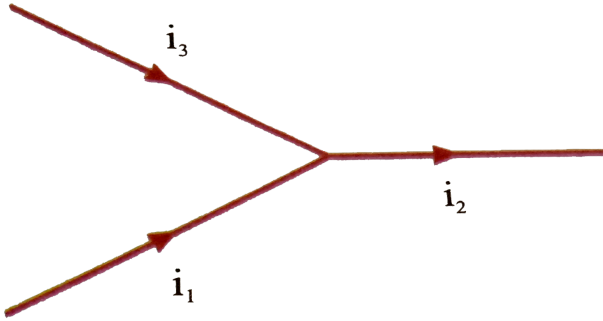

A. $4\sqrt{3}\sin\left(\omega t - \frac{2\pi}{3}\right)$

B. $2\sqrt{3}\cos\left(\omega t + \frac{\pi}{3}\right)$

C. $4\sin(\omega t)$


D. $4\cos(\omega t)$

Answer: C



Watch Video Solution

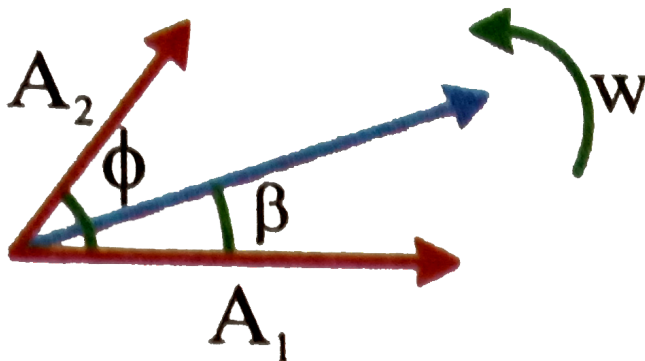80. The maximum values of the phasors (currents and voltage) in AC circuits can be treated as vectors rotating with an angular frequency equal to the angular frequency of the rotor of the generator. If the phase difference between two phasors \vec{A}_1 and \vec{A}_2 is ϕ the resultant phasor is :



$$A = \sqrt{A_1^2 + A_2^2 + 2A_1A_2\cos\phi}$$

and the phase of \vec{A} with respects to A_1 is

$$\beta = \tan^{-1} \frac{A_2 \sin\phi}{A_1 + A_2 \cos\phi}$$

RHS value

The rms value of $y = f(t)$ is

$$y_{\text{rms}} = \left\{ \frac{\int_0^T [f(t)]^2 dt}{T} \right\}^{\frac{1}{2}}$$

Average value

The average value of $y = f(t)$ is $y_{av} = \frac{\int_0^T y dt}{T}$

Using the above concept, answer the following questions.

The rms value of i_3 is

A. $2\sqrt{6}$

B. $\sqrt{6}$

C. $3\sqrt{2}$

D. $2\sqrt{2}$


Answer: D



Watch Video Solution

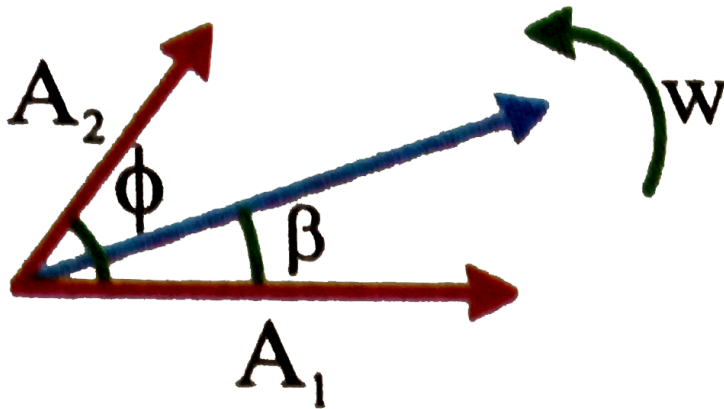81. The maximum values of the phasors (currents and voltage) in *AC* circuits can be treated as vectors rotating with an angular

frequency equal to the angular frequency of the rotor of the generator. If the phase difference between two phasors A_1 and A_2 is ϕ the resultant phasor is :



$$A = \sqrt{A_1^2 + A_2^2 + 2A_1A_2\cos\phi}$$

and the phase of \vec{A} with respects to A_1 is

$$\beta = \tan^{-1} \frac{A_2 \sin \phi}{A_1 + A_2 \cos \phi}$$

RHS value

The rms value of $y = f(t)$ is

$$y_{\text{rms}} = \left\{ \frac{\int_0^T [f(t)]^2 dt}{T} \right\}^{\frac{1}{2}}$$


Average value

The average value of $y = f(t)$ is $y_{av} = \frac{\int_0^T y dt}{T}$

Using the above concept, answer the following questions.

The average value of i in $i-t$ graph (Semi

circular) is

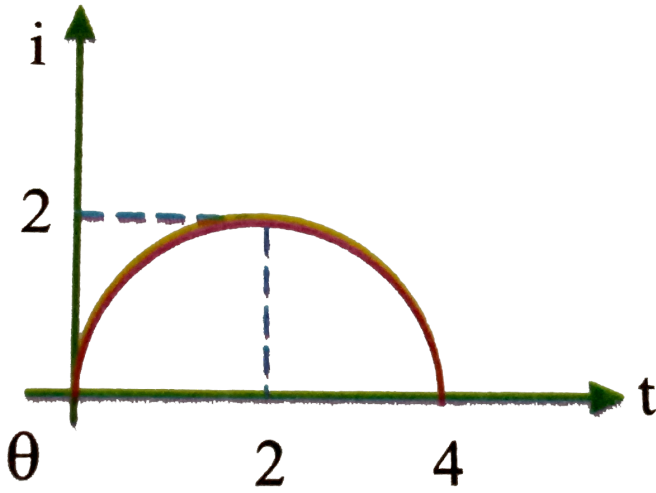

A. π

B. $\frac{\pi}{2}$

C. $\frac{\pi}{3}$

D. $\frac{\pi}{\sqrt{2}}$

Answer: B



Watch Video Solution

82. A series $R - L - C$ circuit has $R = 100$ ohm.

$L = 0.2mH$ and $C = \frac{1}{2}\mu F$. The applied voltage

$V = 20\sin\omega t$. Then

At resonant frequency ω_0 , $\frac{(V_R)_{\max}}{(V_L)_{\max}} =$

A. 2

B. 5

C. 3

D. 4

Answer: B



Watch Video Solution

83. A series $R - L - C$ circuit has $R = 100$ ohm.

$L = 0.2mH$ and $C = \frac{1}{2}\mu F$. The applied voltage

$V = 20\sin\omega t$. Then

When the current lags the applied voltage by

45° , the value of ω is approximately

A. 5×10^5 rad/s

B. $3 \times 10^5 \text{rad/s}$

C. $4 \times 10^5 \text{rad/s}$

D. $4 \times 10^{10} \text{rad/s}$

Answer: A



Watch Video Solution

84. A series $R - L - C$ circuit has

$R = 100\Omega$, $L = 0.2\text{mH}$ and $C = \frac{1}{2}\mu\text{F}$. The

applied voltage $V = 20\sin\omega t$.

When the current lags the applied voltage by 45° , the equation of the current is

A. $0.2\sin(\omega t + \tan^{-1}0.3)$

B. $0.2\sin(\omega t - \tan^{-1}0.3)$

C. $0.3\sin(\omega t + \tan^{-1}0.3)$

D. $0.3\sin(\omega t - \tan^{-1}0.3)$


Answer: B



View Text Solution

85. The potential difference across a $2H$ inductor as a function of time is shown in figure. At time $t = 0$, current is zero

Current $t = 2$ second is

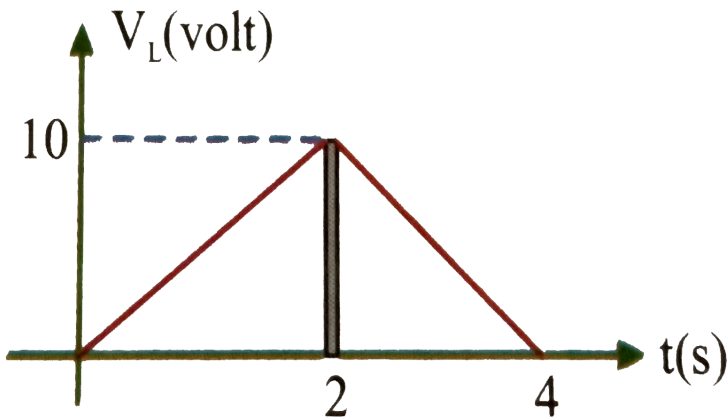

A. 1A

B. 3A

C. 4A

D. 5A

Answer: D




Watch Video Solution


86. The potential difference across a $2H$ inductor as a function of time is shown in figure. At time $t = 0$, current is zero

Current versus time graph across the inductor will be


A.

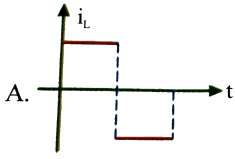


B.

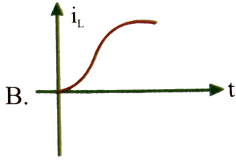

C.

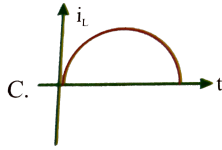

D.

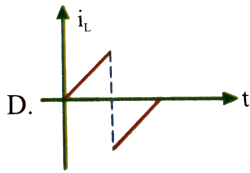


Answer: B



Watch Video Solution

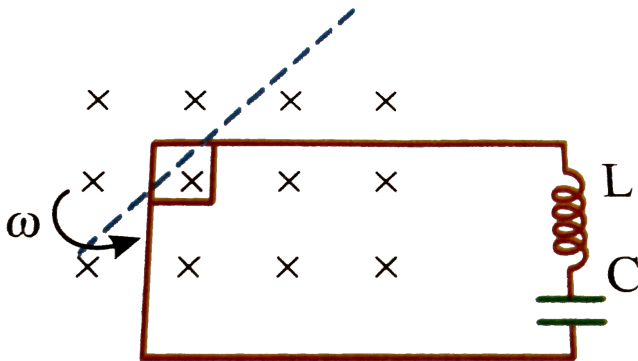87. In the given arrangement the square loop of area 10cm^2 rotates with an angular velocity ω about its diagonal. The loop is connected to an inductance of $L = 100\text{mH}$ and a capacitance of 10mF in series. The lead wires have a net resistance of 10Ω . Given that $B = 0.1\text{T}$ and $\omega = 63\text{rad/s}$



Find the rms current

A. $6 \times 10^5 A$

B. $5 \times 10^{-5} A$

C. $4 \times 10^{-5} A$

D. $7 \times 10^{-5} A$


Answer: C



Watch Video Solution

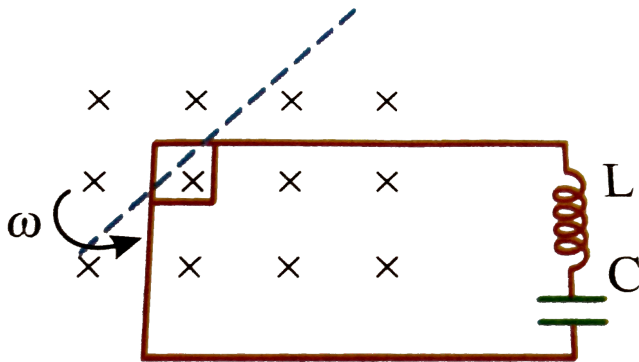88. In the given arrangement the square loop of area 10cm^2 rotates with an angular velocity ω about its diagonal. The loop is connected to

a inductance of $L = 100\text{mH}$ and a capacitance of 10mF in series. The lead wires have a net resistance of 10Ω . Given that $B = 0.1\text{T}$ and $\omega = 63\text{rad/s}$



Find the rms current

A. $6.12 \times 10^{-6}\text{A}$

B. $8.12 \times 10^{-5}\text{A}$

C. $5.12 \times 10^{-5}\text{A}$


$$D. 8.12 \times 10^6 J$$

Answer: B



Watch Video Solution

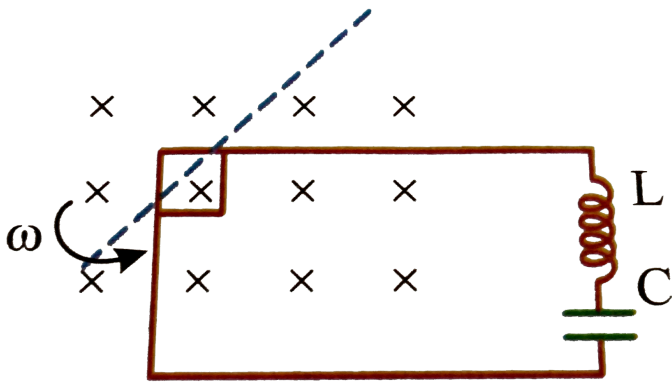89. In the given arrangement the square loop of area 10cm^2 rotates with an angular velocity ω about its diagonal. The loop is connected to an inductance of $L = 100\text{mH}$ and a capacitance of 10mF in series. The lead wires have a net resistance of 10Ω . Given that $B = 0.1\text{T}$ and $\omega = 63\text{rad/s}$



If the current is in phase with voltage, what should be the frequency of rotation of the coil.

- A. 31.6rad/s
- B. 29.5rad/s
- C. 25.6rad/s
- D. 20.5rad/s

Answer: A



90. A $20V$ 5 watt lamp is used in ac main $220V$ and frequency 50 c.p.s.

Capacitance of capacitor, to be put in series to run the lamp

A. $2 \cdot F$

B. $4 \cdot F$

C. $6 \cdot F$

D. $8 \cdot F$

Answer: B



Watch Video Solution

91. A 20V 5 watt lamp is used in ac main 220V and frequency 50 c.p.s.

Inductance of inductor, to be put in series to run the lamp.

A. $2.53H$

B. $5H$

C. $7.5H$

D. $9H$

Answer: A



Watch Video Solution

92. A $20V$ 5 watt lamp is used in ac main $220V$ and frequency 50 c.p.s.

What pure resistance should be included in place of the above passive elements so that the lamp can run on its rated voltage?

A. 120Ω

B. 240Ω

C. 800Ω

D. 720Ω

Answer: C




Watch Video Solution

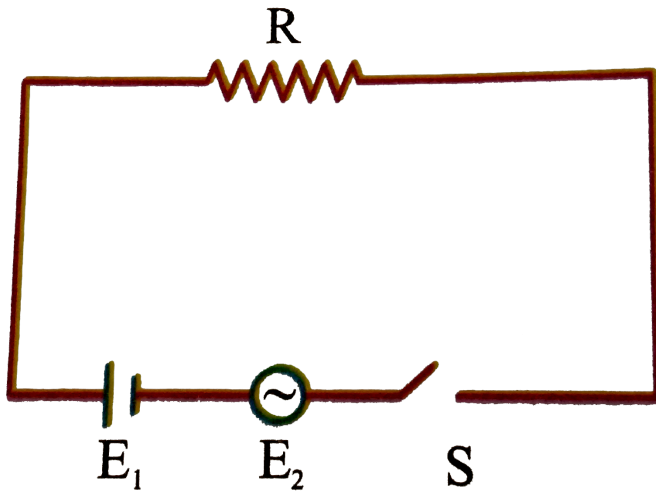93. In the circuit shown in the figure $R = 50\Omega$, $E_1 = 25\sqrt{3}$ volt and $E_2 = 25\sqrt{6}\sin\omega t$ volt where $\omega = 100\pi s^{-1}$. The switch is closed at time $t = 0$ and remains closed for 14 minutes,

then it is opened.

Find the amount of heat produced in the resistor



A. $64000J$

B. $56000J$

C. $63000J$

D. $75000J$

Answer: C



Watch Video Solution

94. In the circuit shown in the figure $R = 50\Omega$, $E_1 = 25\sqrt{3}$ volt and $E_2 = 25\sqrt{6}\sin\omega t$ volt where $\omega = 100\pi\text{s}^{-1}$. The switch is closed at time $t = 0$ and remains closed for 14 minutes, then it is opened.

If total heat produced is used to raise the temperature of 3 kg of water at 20°C , what would be the final temperature of water ?

A. 15°C

B. 25°C

C. 45°C

D. 75°C

Answer: B



View Text Solution

95. In the circuit shown in the figure

$R = 50\Omega$, $E_1 = 25\sqrt{3}$ volt and $E_2 = 25\sqrt{6}\sin\omega t$

volt where $\omega = 100\pi\text{s}^{-1}$. The switch is closed at

time $t = 0$ and remains closed for 14 minutes, then it is opened.

Find the value of the direct current I_{DC} that will produce same amount of heat in the resistor in same time as combination of AC source and AC source produce. Specific heat of water $= 4200 J/kg - ^\circ C$.

A. 1.23A

B. 1.22A

C. 2.24A

D. 3.25A

Answer: C




View Text Solution

96. A physics lab is designed to study the transfer of electrical energy from one circuit to another by means of a magnetic field using simple transformers. Each transformer has two coils of wire electrically insulated from each other but wound around a common core of ferromagnetic material. The two wires are close together but do not touch each other

The primary (1°) coil is connected to a source of alternating (AC) current. The secondary (2°) coil is connected to resistor such as a light bulb. The AC source produces an oscillating voltage and current in the primary coil that produces an oscillating magnetic field in the core material. This in turn induces an oscillating voltage and AC current in the secondary coil

Students collected the following data comparing the number of turns per coil (N), the voltage (V) and the current (I) in the coils of three transformers.

Transformer	primary coil	secondary coil
1	100. 10V.10A	200.20V.5A
2	100.10V.10A	50.5V.5A
3	100.10V.10A	100.5V.20A

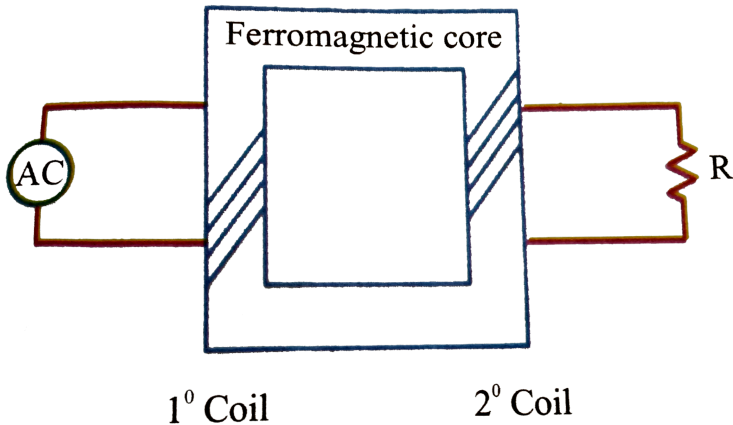

The primary coil of a transformer has 100 turns and is connected to a 120VAC source. How many turns are in the secondary coil if there is 2400V across it

A. 5

B. 50

C. 200

D. 2000

Answer: D



Watch Video Solution


97. A physics lab is designed to study the transfer of electrical energy from one circuit to another by means of a magnetic field using simple transformers. Each transformer has two

coils of wire electrically insulated from each other but wound around a common core of ferromagnetic material. The two wires are close together but do not touch each other

The primary (1°) coil is connected to a source of alternating (AC) current. The secondary (2°) coil is connected to resistor such as a light bulb. The AC source produces an oscillating voltage and current in the primary coil that produces an oscillating magnetic field in the core material. This in turn induces an oscillating voltage and AC current in the secondary coil

Students collected the following data comparing the number of turns per coil (N), the voltage (V) and the current (I) in the coils of three transformers.

Transformer	primary coil	secondary coil
1	100. 10V.10A	200.20V.5A
2	100.10V.10A	50.5V.5A
3	100.10V.10A	100.5V.20A

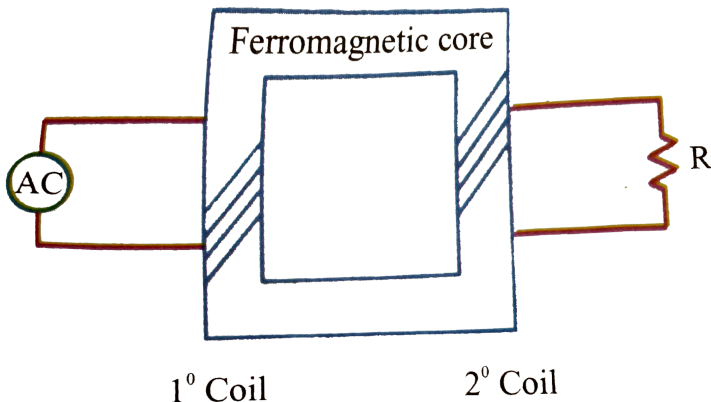

A transformer with 40 turns in its primary coil

is connected to a 120VAC source. If 20W of power is supplied to the primary coil, how much power is developed in the secondary coil ?

A. 10W

B. 20W

C. 80W

D. 160W

Answer: B



Watch Video Solution


98. A physics lab is designed to study the transfer of electrical energy from one circuit to another by means of a magnetic field using simple transformers. Each transformer has two coils of wire electrically insulated from each other but wound around a common core of ferromagnetic material. The two wires are close together but do not touch each other

The primary (1°) coil is connected to a source of alternating (AC) current. The secondary (2°) coil is connected to resistor such as a light bulb. The AC source produces an oscillating voltage and current in the primary

coil that produces an oscillating magnetic field in the core material. This in turn induces an oscillating voltage and AC current in the secondary coil

Students collected the following data comparing the number of turns per coil (N), the voltage (V) and the current (I) in the coils of three transformers.

Transformer	primary coil	secondary coil
1	100. 10V.10A	200.20V.5A
2	100.10V.10A	50.5V.5A
3	100.10V.10A	100.5V.20A

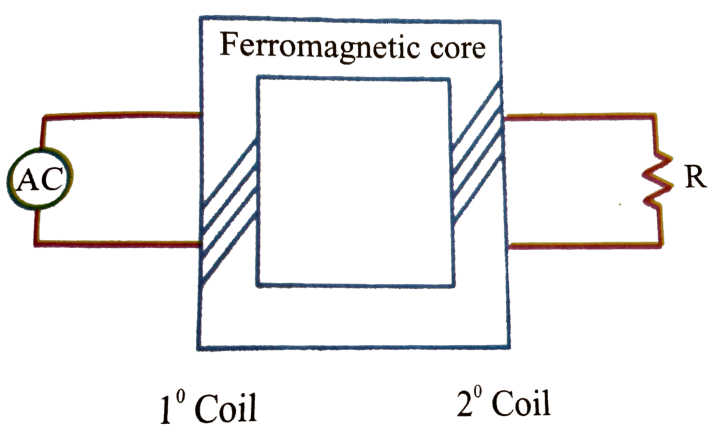

Which of the following is a correct expression for R , the resistance of the load connected to the secondary coil

A. $\left(\frac{V_1^\circ}{I_1^\circ}\right)\left(\frac{N_2^\circ}{N_1^\circ}\right)$

B. $\left(\frac{V_1^\circ}{I_1^\circ}\right)\left(\frac{N_2^\circ}{N_1^\circ}\right)^2$

C. $\left(\frac{V_1^\circ}{I_1^\circ}\right)\left(\frac{N_1^\circ}{N_2^\circ}\right)$

$$D. \left(\frac{V_1^\circ}{I_1^\circ} \right) \left(\frac{N_1^\circ}{N_2^\circ} \right)^2$$

Answer: D



Watch Video Solution

99. A physics lab is designed to study the transfer of electrical energy from one circuit to another by means of a magnetic field using simple transformers. Each transformer has two coils of wire electrically insulated from each other but wound around a common core of


ferromagnetic material. The two wires are close together but do not touch each other

The primary (1°) coil is connected to a source of alternating (AC) current. The secondary (2°) coil is connected to resistor such as a light bulb. The AC source produces an oscillating voltage and current in the primary coil that produces an oscillating magnetic field in the core material. This in turn induces an oscillating voltage and AC current in the secondary coil

Students collected the following data comparing the number of turns per coil (N),

the voltage (V) and the current (I) in the coils of three transformers.

Transformer	primary coil	secondary coil
1	100. 10V.10A	200.20V.5A
2	100.10V.10A	50.5V.5A
3	100.10V.10A	100.5V.20A

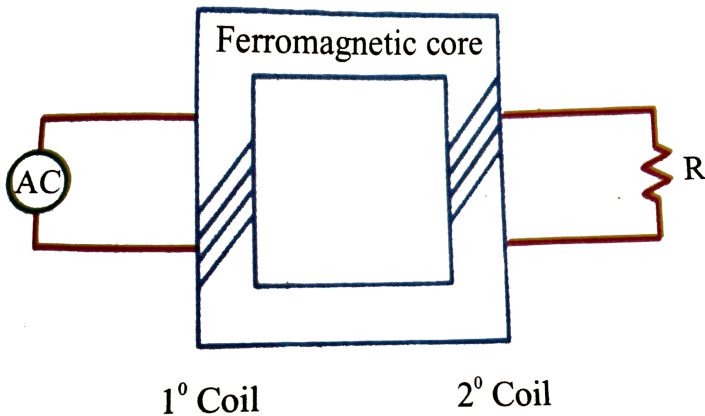

A 12V battery is used to supply 2.0mA of current to the 300 turns in the primary coil of a given transformer. What is the current in the secondary coil if $N_2 = 150$ turns.

A. zero

B. 1.0mA

C. 2.0mA

D. 4.0mA

Answer: A




Watch Video Solution

100. In the circuit shown in figure :

$$R = 10\Omega, L = \frac{\sqrt{3}}{10}\text{H}, R_2 = 20\Omega \quad \text{and} \quad C = \frac{\sqrt{3}}{2}\text{mF}.$$

Current in $L - R_1$ circuit is I_1 in $C - R_2$ circuit is

I_2 and the main current is I

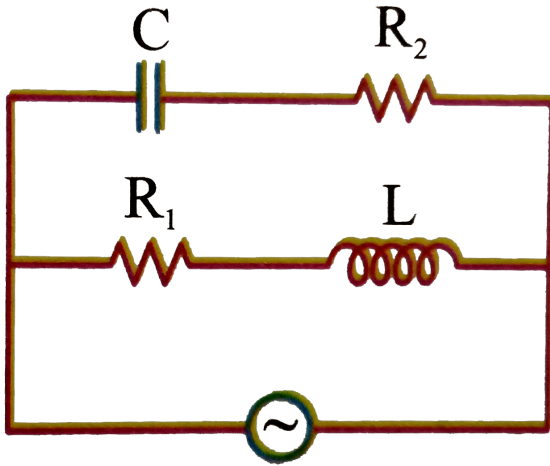

$$V = 200\sqrt{2} \sin(100t) \text{ V}$$

Phase difference between I_1 and I_2 is

- A. 0°
- B. 90°
- C. 180°

D. 60°

Answer: B




Watch Video Solution

101. In the circuit shown in figure :

$$R = 10\Omega, L = \frac{\sqrt{3}}{10}H, R_2 = 20\Omega \text{ and } C = \frac{\sqrt{3}}{2}mF.$$

Current in $L - R_1$ circuit is I_1 in $C - R_1$ circuit is

I_2 and the main current is I

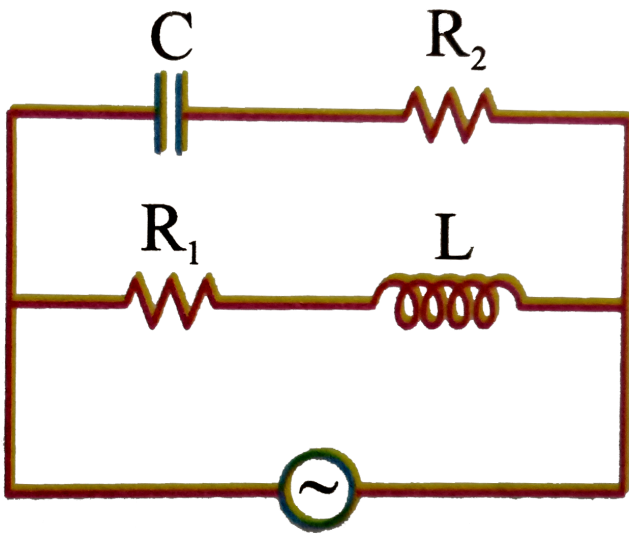

$$V = 200\sqrt{2} \sin(100t) \text{ V}$$

At some instant current in $L - R_1$ circuit is 10A.

At the same instant current in $C - R_2$ branch will be

- A. 5A
- B. $5\sqrt{2} \text{ A}$
- C. $5\sqrt{6} \text{ A}$

$$D. 5\sqrt{3}A$$

Answer: D




Watch Video Solution

102. In the circuit shown in figure :

$$R = 10\Omega, L = \frac{\sqrt{3}}{10}H, R_2 = 20\Omega \text{ and } C = \frac{\sqrt{3}}{2}mF.$$

Current in $L - R_1$ circuit is I_1 in $C - R_1$ circuit is

I_2 and the main current is I

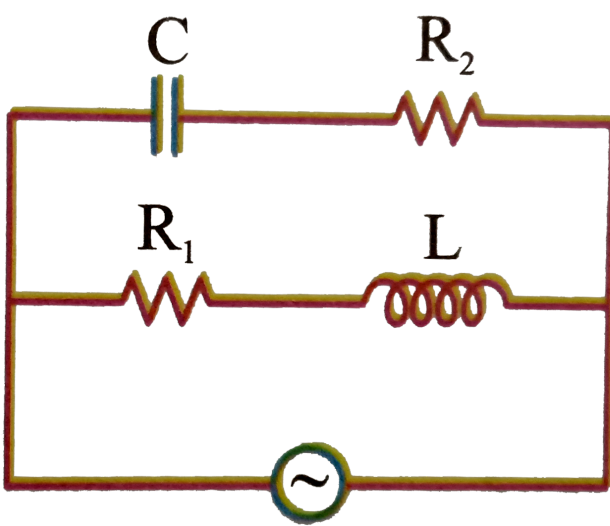

$$V = 200\sqrt{2} \sin(100t) \text{ V}$$

At some instant I_1 in the circuit is $10\sqrt{2} \text{ A}$, then at this instant current I will be

- A. 20A
- B. $10\sqrt{2} \text{ A}$
- C. $20\sqrt{2} \text{ A}$
- D. 25A

Answer: B



Watch Video Solution

103. A solenoid with inductance $L = 7\text{mH}$ and active resistance $R = 44\Omega$ is first connected to a source of direct voltage V_0 and then to a source of sinusoidal voltage with effective value $V = V_0$. At what frequency of the oscillator will be power consumed by the solenoid be $\eta = 5.0$ times less than in the former case?



Watch Video Solution

104. An LCR circuit has $L = 10 \text{ mH}$, $R = 3\Omega$ and $C = 1\mu\text{F}$ connected in series to a source of $15\cos\omega t$. volt. Calculate the current amplitude and the average power dissipated per cycle at a frequency 10% lower than the resonance frequency.



Watch Video Solution

105. A series LCR circuit with $R = 20\Omega$, $L = 1.5H$ and $C = 35\mu F$ is connected to a variable frequency $200V$ ac supply. When the frequency of the supply equals the natural frequency of the circuit, what is the average power in Kw transferred to the circuit in one complete cycle?



Watch Video Solution

106. A sinusoidal voltage of peak value $283V$ and frequency $50Hz$ is applied to a series LCR


circuit in which $R = 3\Omega$, $L = 25.48mH$, and $C = 796\mu F$. Find the impedance of the circuit.



[Watch Video Solution](#)

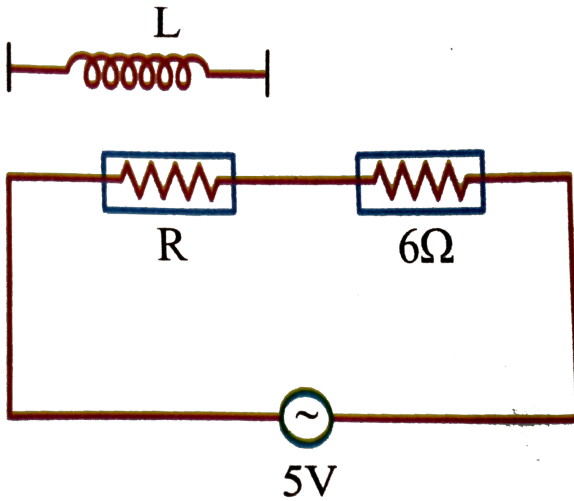107. Two resistors are connected in series across $5V$ rms source of alternating potential. The potential difference across 6Ω resistor is $3V_m$. If R is replaced by a pure inductor L of such magnitude that current remains same,

then the potential difference across L is



[Watch Video Solution](#)

108. In LCR circuit current resonant frequency is 600Hz and half power points are at 650 and 550Hz . The quality factor is



[Watch Video Solution](#)

109. An ac ammeter is used to measure current in a circuit. When a given direct current passes through the circuit. The ac ammeter reads 3 A. When another alternating current passes through the circuit, the ac ammeter reads 4A. Then find the reading of this ammeter (inA), if dc and ac flow through the circuit simultaneously.



Watch Video Solution

110. In a series LCR circuit the voltage across the resistance, capacitance and inductance is 10 V each. If the capacitance is short circuited, the voltage across the inductance will be $\frac{10^x}{\sqrt{2}}$

what is value of x



Watch Video Solution

111. An ideal choke takes a current of 10 A when connected to an ac supply of 125 V and 50 Hz . A pure resistor under the same conditions takes a current of 12.5 A . If the two are connected to an

ac supply of $100V$ and $40Hz$, then the current in series combination of above resistor and inductor is $\frac{10^x}{\sqrt{2}}$ what is the value of x



[Watch Video Solution](#)

112. In a region of uniform magnetic induction $B = 10^2$ tesla, a circular coil of radius $30cm$ and resistance π^2 ohm is rotated about an axis which is perpendicular to the direction of B and which form a diameter of the coil. If the coil

rotates at 200rpm the amplitude of the alternating current induced in the coil is



[Watch Video Solution](#)

113. An inductor of inductance 2.0mH is connected across a charged capacitor of capacitance $5.0\mu\text{F}$ and the resulting LC circuit is set oscillating at its natural frequency. Let Q denote the instantaneous charge on the capacitor and I the current in the circuit. It is found that the maximum value of charge Q is $200\mu\text{C}$.

a. When $Q = 100\mu\text{C}$, what is the value of $\left|\frac{dI}{dt}\right|$?

b. When $Q = 200\mu\text{C}$, what is the value of I ?

c. Find the maximum value of I .

d. When I is equal to one-half its maximum value, what is the value of $|Q|$?

A. When $Q = 100\mu\text{C}$, what is the value of $|dI/dt|$?

B. when $Q = 200\mu\text{C}$ what is the value of I ?

C. Find the maximum value of I ?

D. When I is equal to one-half its maximum value, what is the value of $|Q|$?


Answer: A::B::C::D



Watch Video Solution

114. When an ac source of emf $e = E_0 \sin(100t)$ is connected across a circuit, the phase difference between emf e and current I in the circuit is observed to be $(\pi)/4$ as shown in fig. If the circuit consists possibly only of R-C or R-C of L-R series, find the relationship find the

relationship between the two elements.

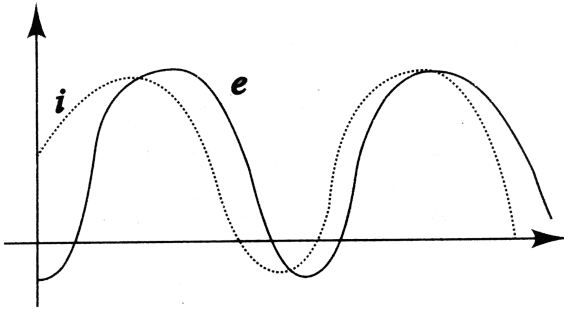

A. $R = 1k\Omega, C = 10\mu F$

B. $R = 1k\Omega, C = 1\mu F$

C. $R = 1k\Omega, L = 10H$


D. $R = 1k\Omega, L = 1H$

Answer: A



115. In a series L-R circuit ($L = 35\text{mH}$ and $R = 11\Omega$), a variable emf source ($V = V_0\sin\omega t$) of $V_{rms} = 220\text{V}$ and frequency 50 Hz is applied. Find the current amplitude in the circuit and phase of current with respect to voltage. Draw current-time graph on given

graph $\left(\pi = \frac{22}{7}\right)$.

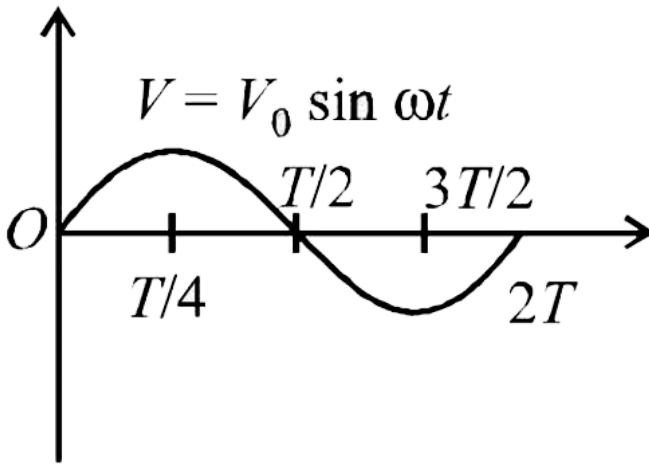

[Watch Video Solution](#)

116. An AC voltage source of variable angular frequency (ω) and fixed amplitude V_0 is connected in series with a capacitance C and an

electric bulb of resistance R (inductance zero).

When (ω) is increased

- A. The bulb glows dimmer
- B. the bulb glows brighter
- C. total impedance of the circuit is unchanged
- D. total impedance of the circuit increases


Answer: A::B::D



Watch Video Solution

117. At time $t = 0$, terminal A in the circuit shown in the figure is connected to B by a key and an alternating current $I(t) = I_0 \cos(\omega t)$, with $I_0 = 1A$ and $(\omega) = 500 \text{rads}^{-1}$ starts flowing in it with the initial direction shown in the figure. At $t = (7\pi/6\omega)$, the key is switched from B to D. Now onwards only A and D are connected. A total charge Q flows from the battery to charge the capacitor fully. If $C=20(\mu)F$, $R = 10(\Omega)$ and the battery is ideal with emf of 50 V,

identify the correct statement(s).

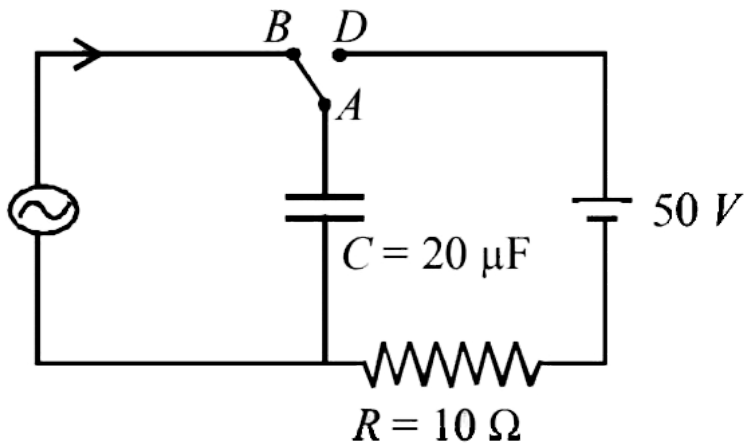

A. Magnitude of the maximum charge on

the capacitor before $t = \frac{7\pi}{6\omega}$ is $1 \times 10^{-3} \text{C}$

B. The current in the left part of the circuit

just before $t = \frac{7\pi}{6\omega}$ is clockwise

C. Immediately after A is connected to D ,

the current in R is 10A

$$D. Q = 2 \times 10^{-3}C$$


Answer: B



Watch Video Solution

118. In the given circuit, the AC source has $(\omega) = 100\text{rad/s}$. Considering the inductor and capacitor to be ideal, the correct choice(s) is

(are)

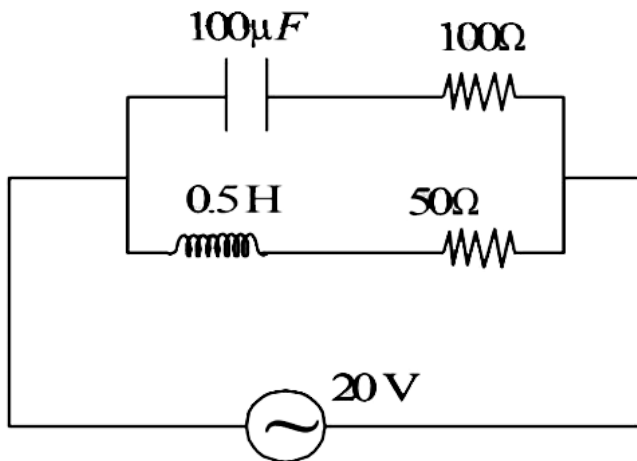

A. the current through the circuit, I is $0.3A$

B. the current through the circuit, I is

$$0.3\sqrt{2}A$$

C. the voltage across 1000Ω resistor

$$= 10\sqrt{2}V$$

D. the voltage across 50Ω resistor = $10V$

Answer: C::D



Watch Video Solution

119. A series R-C circuit is connected to AC voltage source. Consider two cases, (A) when C is without a dielectric medium and (B) when C is filled with dielectric of constant 4. The current I_R through the resistor and voltage V_C across the capacitor are compared in the two cases. Which of the following is/ are true?

A. $I_R^A > I_R^B$

B. $I_R^A < I_R^B$

C. $V_C^A > V_C^B$

D. $V_C^A < V_C^B$

Answer: A::C



Watch Video Solution

120. A series R-C combination is connected to an AC voltage of angular frequency $\omega = 500 \text{radian/s}$. If the impedance of the R-C

circuit is $R\sqrt{1.25}$, the time constant (in millisecond) of the circuit is



[Watch Video Solution](#)

LEVEL - I (H.W)

1. For a given AC source the average emf during the positive half cycle

A. depends on E_0

B. depends on shape of wave

C. both 1 and 2

D. depends only on peak value of E_0

Answer: 4



Watch Video Solution

2. The peak value of an alternating emf E given by

$$E = (E_0) \cos \omega t$$

is 10V and frequency is 50 Hz. At time $t = (1/600)s$ the instantaneous value of emf is

A. $10V$

B. $5\sqrt{3}V$

C. $5V$

D. $1V$

Answer: 3



Watch Video Solution

3. The equation of $A. C$ of frequency $75Hz$, if it's

RMS value is $20A$ is

A. $I = 20\sin(150\pi t)$

B. $I = 20\sqrt{2}\sin(150\pi t)$

C. $I = \frac{20}{\sqrt{2}}\sin(150\pi t)$

D. $I = 20\sqrt{2}\sin(75\pi t)$

Answer: 2



Watch Video Solution

4. The voltage of an A.C source varies with time according to the equation

$$V = 50\sin 100\pi t \cos 100\pi t.$$

Where 't' is in and 'V' is in volt. Then

A. The peak voltage of the source is 100V

B. The peak voltage of the source is

$$100/\sqrt{2}V$$

C. The peak voltage of the source is 25V

D. The frequency of the source is 50Hz

Answer: 3



Watch Video Solution

5. The form factor for a sinusoidal A. C is

A. $2\sqrt{2}$

B. $\pi: 2\sqrt{2}$

C. $\sqrt{2}: 1$

D. $1: \sqrt{2}$

Answer: 2



Watch Video Solution

6. At resonance the peak value of current in

$L - C - R$ series circuit is

A. E_0/R

B.
$$\frac{E_0}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

C.
$$\frac{E_0}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega^2 C}\right)^2}}$$

D.
$$\frac{E_0}{\sqrt{2}R}$$

Answer: 1

7. In an AC circuit, the mass value of the current I_{rms} is related to the peak current I_0 as

A. $I_{\text{rms}} = \frac{1}{\pi} I_0$

B. $I_{\text{rms}} = \frac{1}{\sqrt{2}} I_0$

C. $I_{\text{rms}} = \sqrt{2} I_0$

D. $I_{\text{rms}} = \pi I_0$

Answer: 2

8. A voltmeter connected in an A.C circuit reads 220V. It represents,

A. peak voltage

B. *RMS* voltage

C. Average voltage

D. Mean square voltage

Answer: 2



Watch Video Solution

9. If the instantaneous current in a circuit is given by $I = 20\cos(\omega t + \phi)A$, the rms value of the current is

A. $2A$

B. $\sqrt{2}A$

C. $2\sqrt{2}A$

D. zero

Answer: 2



Watch Video Solution

10. The time taken by an *AC* of 50Hz in reaching from zero to its maximum value will be

A. 0.5s

B. 0.005s

C. 0.05s

D. 5s

Answer: 2



Watch Video Solution

11. A generator produces a time varying voltage given by $V = 240\sin 120t$, where t is in second.

The rms voltage and frequency are

A. 60Hz and 240V

B. 19Hz and 120V

C. 19Hz and 170V

D. 754Hz and 170V

Answer: 3



Watch Video Solution

12. A 220V, 50Hz AC supply is connected across a resistor of $50k\Omega$. The current at time t second.

Assuming that it is zero at $t = 0$, is

A. $4.4\sin(314t)mA$

B. $6.2\sin(314t)mA$

C. $4.4\sin(157t)mA$

D. $6.2\sin(157t)mA$

Answer: 2



Watch Video Solution

13. A resistance of 20Ω is connected to a source of alternating current rated $110V, 50Hz$. Find (a) the *rms* current, (b) the maximum instantaneous current in the resistor and the time taken by the current to change from its maximum value to the rms value.

A. $2.5 \times 10^{-3}\text{sec}$

B. $2.5 \times 10^{-2}\text{sec}$

C. $5 \times 10^{-3}\text{sec}$

D. $25 \times 10^{-3}\text{sec}$

Answer: 1



Watch Video Solution

14. A conductor of capacity $1\mu\text{F}$ is connected to an *A.C* source of 220V and 50Hz frequency. The current flowing in the circuit will be

A. $6.9 \times 10^{-8}\text{A}$

B. 6.9A

C. $6.9 \times 10^{-6}\text{A}$

D. zero

Answer: 1



Watch Video Solution

15. In a circuit, the frequency is $f = \frac{1000}{2\pi} \text{ Hz}$ and the inductance is 2 henry, then the reactance will be

A. 200Ω

B. $200\mu\Omega$

C. 2000Ω

D. $2000\mu\Omega$

Answer: 3



Watch Video Solution

16. The transformer ratio of transformer is 10 : 1 . The current in the primary circuit if the secondary current required is 100A assuming the transformer be ideal, is

A. 500A

B. 200A

C. 1000A

D. 2000A

Answer: 3



Watch Video Solution

17. The transformer ratio of transformer is 10 : 1
. If the primary voltage is 440 V, secondary emf
is

A. 44V

B. 440V

C. $4400V$

D. $44000V$

Answer: 3



Watch Video Solution

18. The frequency at which the inductive reactance of $2H$ inductance will be equal to the capacitive reactance of $2\mu F$ capacitance (nearly)

A. $80Hz$

B. 40Hz

C. 60Hz

D. 20Hz

Answer: 1



Watch Video Solution

19. In a series LCR circuit, resistance $R = 10\Omega$ and the impedance $Z = 20\Omega$ the phase difference between the current and the voltage is

A. 60°

B. 20°

C. 45°

D. 90°

Answer: 1



Watch Video Solution

20. In an $L - C - R$ series circuit,

$R = \sqrt{5}\Omega$, $X_L = 9\Omega$, $X_C = 7\Omega$. If applied voltage in

the circuit is $50V$ then impedance of the circuit
in ohm will be

A. 2

B. 3

C. $2\sqrt{5}$

D. $3\sqrt{5}$

Answer: 2



Watch Video Solution

21. In an ac circuit the potential differences across an inductance and resistance joined in series are, respectively, 16 V and 20 V. The total potential difference across the circuit is

A. 20V

B. 25.6V

C. 31.0V

D. 53.5V

Answer: 2



Watch Video Solution

22. Current in an ac circuit is given by

$$I = 3\sin\omega t + 4\cos\omega t, \text{ then}$$

A. rms value fo current is 5A

B. mean value of this current in one half
period will be $6/\pi$

C. if voltage applied is $V = V_m \sin\omega t$ then the
circuit must be containing resistance and
capacitance

D. ir voltage applied is $V = V_m \sin \omega t$, the circuit may contains resistance and inductance

Answer: 3



Watch Video Solution

23. A fully charged capacitor C with initial charge q_0 is connected to a coil of self inductance L at $t=0$. The time at which the

energy is stored equally between the electric and the magnetic fields is

A. $\frac{\pi}{4}\sqrt{LC}$

B. $2\pi\sqrt{LC}$

C. \sqrt{LC}

D. $\pi\sqrt{LC}$

Answer: 1



Watch Video Solution

1. An alternating current ' I ' is given by

$I = i_0 \sin 2\pi(t/T + 1/4)$. Then the average current

in the first one quarter time period to

A. $\frac{2i_0}{\pi}$

B. $\frac{i_0}{\pi}$

C. $\frac{i_0}{2\pi}$

D. $\frac{3i_0}{\pi}$

Answer: 1



Watch Video Solution

2. In an LR circuit, $R = 100\Omega$ and $L = 2H$. If an alternating voltage of $120V$ and $60Hz$ is connected in this circuit, then the value of current flowing in it will be _____ A nearly

A. 0.32

B. 0.16

C. 0.48

D. 0.8

Answer: 2



3. The equation of an alternating current is

$$I = 50\sqrt{2}\sin 400\pi t \text{ A},$$
 then the frequency and the

root mean square value of current are respectively.

A. 200Hz , 50A

B. 400Hz , $50\sqrt{2}\text{A}$

C. 200Hz , $50\sqrt{2}\text{A}$

D. 500Hz , 200A

Answer: 1



Watch Video Solution

4. A circuit operating at $\frac{360}{2\pi}$ Hz contains a $1\mu F$ capacitor and a 20Ω . resistor. How large an inductor must be added in series to make the phase angle for the circuit zero? Calculate the current in the circuit if the applied voltage is 120V.

A. $7.7H$

B. $10H$

C. $3.5H$

D. $15H$

Answer: 1



Watch Video Solution

5. A resistor R and the capacitor C are connected in series across an ac source of rms voltage $5V$ if the rms voltage across C is $3V$ then that across R is .

A. $1V$

B. $2V$

C. $3V$

D. $4V$

Answer: 4



Watch Video Solution

6. An LCR series circuit containing a resistance of 12Ω has angular resonance frequency $4 \times 10^5 \text{radS}^{-1}$. At resonance the voltage across

resistance and inductance are 60Ω and 40Ω respectively. Then the values of L and C are respectively.

A. 0.2mH , $1/32\mu\text{F}$

B. 0.4mH , $1/16\mu\text{F}$

C. 0.2μ , $1/16\mu\text{F}$

D. 0.4mH , $1/32\mu\text{F}$

Answer: 1



Watch Video Solution

7. The natural frequency of an LC - circuit is 1,25,000 cycles per second. Then the capacitor C is replaced by another capacitor with a dielectric medium of dielectric constant k . In this case, the frequency decreases by 25 kHz. The value of k is

A. 3.0

B. 2.1

C. 1.56


D. 1.7

Answer: 3



Watch Video Solution

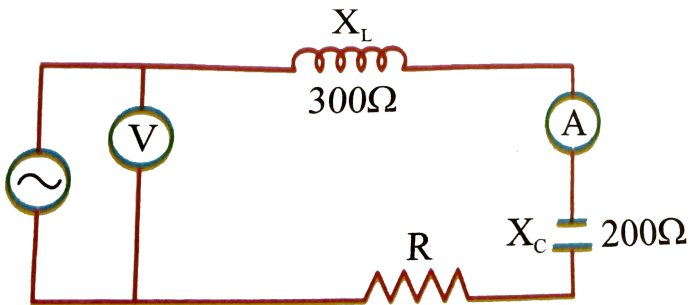8. In the given figure, the instantaneous value of alternating e.m.f. is $e = 14.14\sin\omega t$. The reading of voltmeter in volt will be



A. 141.0

B. 10

C. 200

D. 70.7

Answer: 2



Watch Video Solution

9. A coil of inductance $0.1H$ is connected to $50V, 100Hz$ generator and current is found to be $0.5A$. The potential difference across resistance of coil is:

A. $15V$

B. $20V$

C. 25V

D. 39V

Answer: 4



Watch Video Solution

10. The voltage of A.C source varies with time according to equation. $V = 120\sin 100\pi t \cos 100\pi t$. Then the frequency of source is

A. 50Hz

B. 100Hz

C. 150Hz

D. 200Hz

Answer: 2



Watch Video Solution

11. The current in a coil of self inductance 5 henry is increasing according to $I = 2\sin^2 t$. The amount of energy spent during the period when current changes from 0 to 2 amperes is

A. $10J$

B. $5J$

C. $100J$

D. $2J$

Answer: 4



Watch Video Solution

12. In an *AC* circuit the voltage applied is $E = E_0 \sin \omega t$. The resulting current in the circuit

is $I = I_0 \sin\left(\omega t - \frac{\pi}{2}\right)$. The power consumption in the circuit is given by

A. $P = \frac{E_0 I_0}{\sqrt{2}}$

B. $P = \text{zero}$

C. $P = \frac{E_0 I_0}{2}$

D. $P = \sqrt{2} E_0 I_0$

Answer: 2



Watch Video Solution

13. The efficiency of a transformer is 98%. The primary voltage and current are 200V and 6A. If the secondary voltage is 100V, the secondary current

A. 11.76A

B. 12.25A

C. 3.06A

D. 2.94A

Answer: 3



Watch Video Solution

ILLUSTRATION

1. The peak value of alternating current is 5A and its frequency is 60Hz. Find its rms value. How long will the current take to reach the peak starting from zero?



[Watch Video Solution](#)

2. The electric current in a circuit is given by

$I = i_0 \left(\frac{t}{\tau} \right)$ for some time. Calculate the rms current for the period $t = 0$ to $t = (\tau)$.



[Watch Video Solution](#)

3. An alternating emf is represented by

$E = 100\sin(120\pi t + \pi/4)$ volt. Calculate

(i) Average or mean value of emf

(ii) RMS value of emf

(iii) Frequency of alternating emf

(iv) the shortest time interval after start at which emf is zero.




[Watch Video Solution](#)

4. A pure inductor of 25.0 mH is connected to a source of 220 V. Find the inductive reactance and rms current in the circuit if the frequency of the source is 50 Hz.



[Watch Video Solution](#)

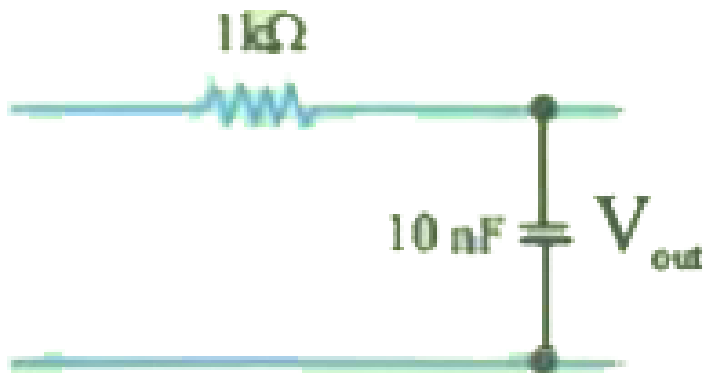5. If an input of 50mV is applied as V_{in} then V_{out} at 100kHz will be



[Watch Video Solution](#)

6. A $15.0\mu\text{F}$ capacitor is connected to a 220 V, 50 Hz source. Find the capacitive reactance and the current (rms and peak) in the circuit. If the


frequency is doubled, what happens to the capacitive reactance and the current ?



[Watch Video Solution](#)

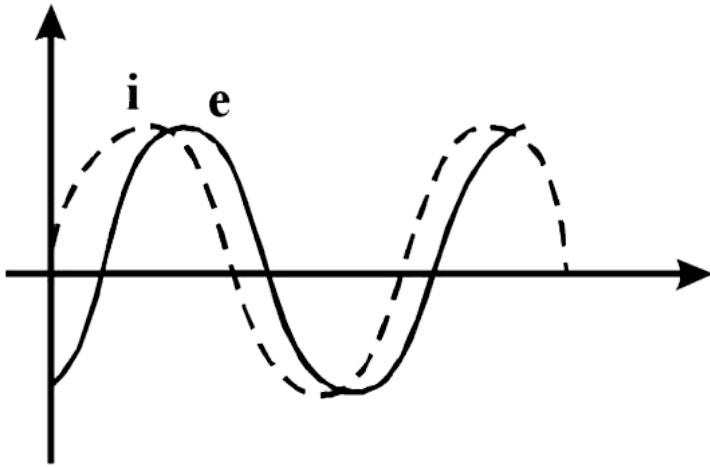7. When an AC source of $emf e = E_0 \sin(100t)$ is connected across a circuit i in the circuit, the phase difference between the emf e and the current i in the circuit is observed to be $(\pi/4)$, as shown in the diagram. If the circuit consists possibly only of R-C or R-L or L-C in series, find

the relationship between the two elements



[Watch Video Solution](#)

8. An LCR circuit contains resistance of 100Ω and a supply of $200V$ at 300rads^{-1} angular frequency. If only capacitance is taken out from the circuit and the rest of the circuit is joined,

current lags behind the voltage by 60° . If, on the other hand, only inductor is taken out, the current leads the voltage by 60° . The current flowing in the circuit is




[Watch Video Solution](#)

9. In a series resonant circuit, the ac voltage across resistance R , inductance L and capacitance C are $V_R = 4V$, $V_L = 10V$ and $V_C = 7V$ respectively. Find the voltage applied to the circuit.



[Watch Video Solution](#)

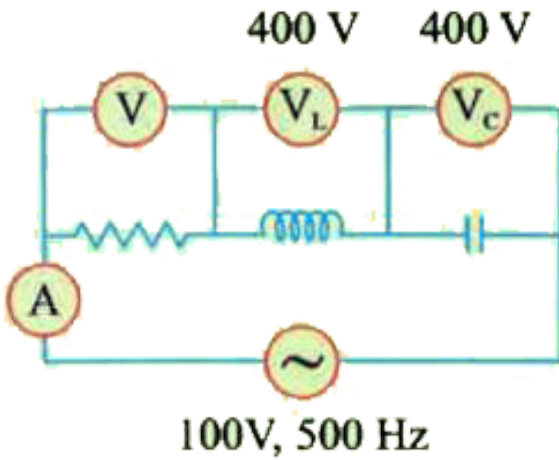10. Find the power factor of the circuit shown in figure.



[Watch Video Solution](#)


11. A 750Hz , 20V source is connected to a resistance of 100Ω an inductance of 0.1803H and a capacitance of $10\mu\text{F}$ all in series. Calculate the time in which the resistance (thermal capacity $2\text{J}/^\circ\text{C}$) will get heated by 10°C .



Watch Video Solution

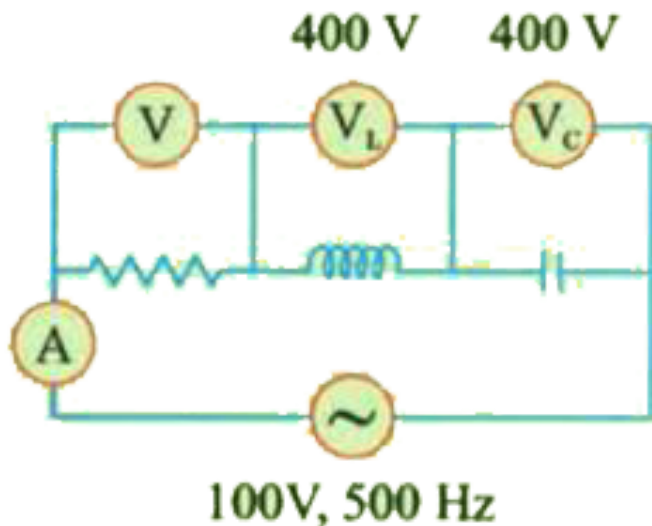12. In the LCR series circuit find the voltmeter and ammeter reading in the figure shown

below. Also find the quality factor of circuit.



[Watch Video Solution](#)

13. An inductance of $2.0H$, a capacitance of $18\mu F$ and a resistance of $10k\Omega$ are connected to an AC source of $20V$ with adjustable frequency.

(a) What frequency should be chosen to maximise the current in the circuit? (b) What is the value of this maximum current?



[Watch Video Solution](#)

14. A 50Ω electric iron is connected to an ac supply of 200V, 50 Hz. Calculate (i) average power delivered to iron (ii) peak power and (iii) energy spent in one minute.



[Watch Video Solution](#)

15. The LCR series circuit is connected to an external emf $e = 200\sin 100\pi t$. The values of the capacitance and resistance in the circuit are $1\mu F$ and 100Ω respectively. The amplitude of the current in the circuit will be maximum when the inductance is



Watch Video Solution

16. The potential difference V across and the current I flowing through an instrument in an AC circuit are given by:

$$V = 5\cos\omega t \text{ volt}$$

$$I = 2\sin\omega t \text{ Amp.}$$



[Watch Video Solution](#)

17. A capacitor, an inductor and an electric bulb are connected in series to an AC supply of variable frequency. If the frequency of the supply is increased gradually, what will happen to brightness of bulb.



[Watch Video Solution](#)

18. A power transformer is used to step up an alternating emf of 200V to 4 KV and to transmits 5KW power. If the primary is of 1000 turns, calculate, assuming the transformer to be ideal.

(i) The number of turns in the secondary

(ii) The current rating of the secondary



Watch Video Solution

19. A $1\mu F$ condenser is charged to 50V. The charging battery is then disconnected and a

10mH coil is connected across capacitor so that the LC oscillations occur. Find the maximum current in the coil?



[Watch Video Solution](#)

20. An inductance of $2H$ carries a current of $2A$. To prevent sparking when the circuit is broken a capacitor of $4\mu F$ is connected across the inductance. The voltage rating of the capacitor is of the order of



[Watch Video Solution](#)

21. The peak value of an alternating current is 5A and its frequency is 60Hz. Find its rms value.

How long will the current be 5 A and its frequency is 60 Hz. Find its rms value.



[Watch Video Solution](#)

22. The electric current in a circuit is given by

$$I = i_0 \left(\frac{t}{\tau} \right)$$

for some time. Calculate the rms

current for the period $t = 0$ to $t = (\tau)$.



[Watch Video Solution](#)

23. An alternating emf is represented by

$$E = 100\sin(120\pi t + \pi/4) \text{ volt. Calculate}$$

(i) Average or mean value of emf

(ii) RMS value of emf

(iii) Frequency of alternating emf

(iv) the shortest time interval after start at which emf is zero.




Watch Video Solution

24. A pure inductor of 25.0 mH is connected to a source of 220 V. Find the inductive reactance and rms current in the circuit if the frequency of the source is 50 Hz.



Watch Video Solution

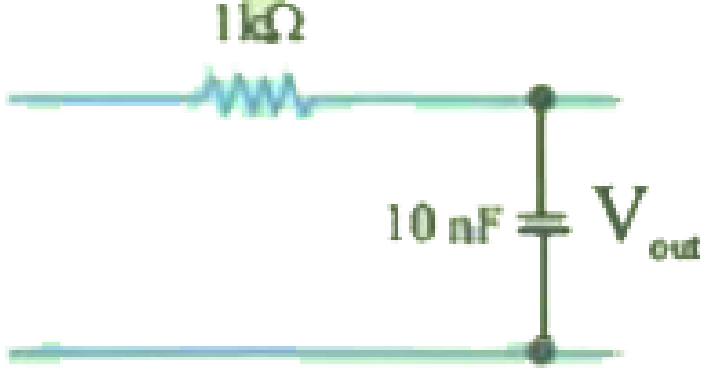25. If an input of 50mV is applied as V_{in} then V_{out} at 100kHz will be




 [Watch Video Solution](#)

26. A $30\mu\text{F}$ capacitor is connected to a 220 V, 50 Hz. Source. Find its capacitive reactance, rms current, peak current and impedance of the circuit.

 [Watch Video Solution](#)

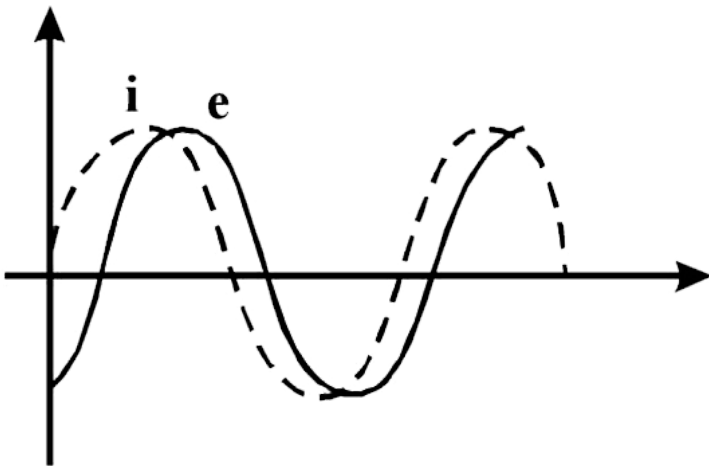27. When an AC source of $emf = E_0 \sin(100t)$ is connected across a circuit in the circuit, the phase difference between the emf e and the current i in the circuit is observed to be $(\pi/4)$, as shown in the diagram. If the circuit consists possibly only of R-C or R-L or L-C in series, find the relationship between the two elements



 [Watch Video Solution](#)

28. An LCR circuit contains resistance of 100Ω and a supply of $200V$ at 300rads^{-1} angular frequency. If only capacitance is taken out from the circuit and the rest of the circuit is joined, current lags behind the voltage by 60° . If, on the other hand, only inductor is taken out, the current leads the voltage by 60° . The current flowing in the circuit is


 [Watch Video Solution](#)

29. In a series resonant circuit, the ac voltage across resistance R , inductance L and capacitance C are $V_R = 4V$, $V_L = 10V$ and $V_C = 7V$ respectively. Find the voltage applied to the circuit.



Watch Video Solution

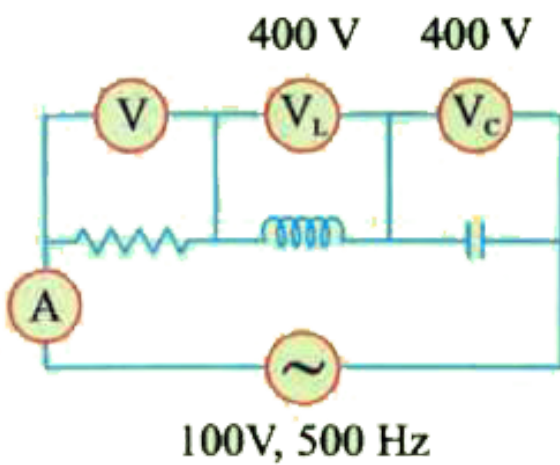30. Find the power factor of the circuit shown in figure.



[▶ Watch Video Solution](#)

31. A 750Hz , 20V source is connected to a resistance of 100Ω , an inductance of 0.1803H and a capacitance of $10\mu\text{F}$ all in series. Calculate the time in which the resistance


(thermal capacity $2J/^\circ C$) will get heated by $10^\circ C$.



[Watch Video Solution](#)

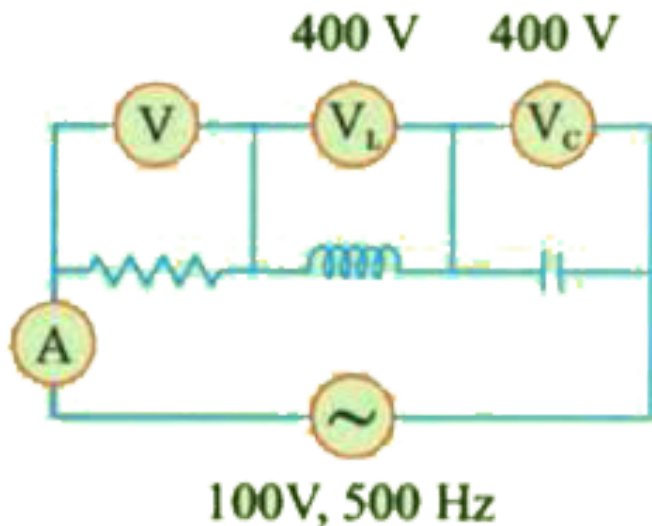32. In the LCR series circuit find the voltmeter and ammeter reading in the figure shown

below. Also find the quality factor of circuit.



[Watch Video Solution](#)

33. An inductance of $2.0H$, a capacitance of $18\mu F$ and a resistance of $10k\Omega$ are connected to an AC source of $20V$ with adjustable frequency.

(a) What frequency should be chosen to maximise the current in the circuit? (b) What is the value of this maximum current?



[Watch Video Solution](#)

34. A 50Ω electric iron is connected to an ac supply of 200V, 50 Hz. Calculate (i) average power delivered to iron (ii) peak power and (iii) energy spent in one minute.



[Watch Video Solution](#)

35. The LCR series circuit is connected to an external emf $e = 200\sin 100\pi t$. The values of the capacitance and resistance in the circuit are $1\mu F$ and 100Ω respectively. The amplitude of the current in the circuit will be maximum when the inductance is



Watch Video Solution

36. The potential difference V across and the current I flowing through an instrument in an AC circuit are given by:

$$V = 5\cos\omega t \text{ volt}$$

$$I = 2\sin\omega t \text{ Amp.}$$



[Watch Video Solution](#)

37. A capacitor, an inductor and an electric bulb are connected in series to an AC supply of variable frequency. If the frequency of the supply is increased gradually, what will happen to brightness of bulb.



[Watch Video Solution](#)

38. A $1\mu F$ condenser is charged to 50V. The charging battery is then disconnected and a 10mH coil is connected across capacitor so that the LC oscillations occur. Find the maximum current in the coil?



Watch Video Solution

39. An inductance of $2H$ carries a current of $2A$. To prevent sparking when the circuit is broken a capacitor of $4\mu F$ is connected across the

inductance. The voltage rating of the capacitor is of the order of



[Watch Video Solution](#)

EVALUATE YOURSELF-1

1. If E_0 represents the peak value of the voltage in an ac circuit, the r.m.s. value of the voltage will be



[Watch Video Solution](#)

2. The electric current in a circuit is given by $I = 2i_0/\tau$ for some time. What is the rms current for the period $t = 0$ to $t = \tau$?



[Watch Video Solution](#)

3. The frequency of A.C. is 50 Hz. How many times the current becomes zero in one second?



[Watch Video Solution](#)

4. If the instantaneous current in a circuit is given by $I = 2\cos(\omega t + \phi)$ amperes, the rms value of the current is



[Watch Video Solution](#)

5. The equation of alternating current is given by $E = 158 \sin 200 \pi t$. The value of voltage at time $t = 1/400$ sec is



[Watch Video Solution](#)

6. A generator produces a time varying voltage given by $V = 240\sin 120t$, where t is in second.

The rms voltage and frequency are



[Watch Video Solution](#)

7. If E_0 represents the peak value of the voltage in an ac circuit, the r.m.s. value of the voltage will be



[Watch Video Solution](#)

8. The electric current in a circuit is given by

$I = 2i_0/\tau$ for some time. What is the rms

current for the period $t = 0$ to $t = \tau$?



[Watch Video Solution](#)

9. The frequency of A.C. is 50 Hz. How many

times the current becomes zero in one second?



[Watch Video Solution](#)

10. If the instantaneous current in a circuit is given by $I = 2\cos(\omega t + \phi)$ amperes, the rms value of the current is



[Watch Video Solution](#)

11. The equation of alternating current is given by $E = 158 \sin 200 \pi t$. The value of voltage at time $t = 1/400$ sec is



[Watch Video Solution](#)

12. A generator produces a voltage that is given by $V = 240 \sin 120 t$ volt, where t is in second. The frequency and r.m.s. voltage are



[Watch Video Solution](#)

EVALUATE YOURSELF-2

1. Assertion (A) : An electric lamp is connected in series with a long solenoid of copper with air core and then connected to AC source. If an iron rod is inserted in solenoid the lamp will

become dim.

Reason (R) : If iron rod is inserted in solenoid, the induction of solenoid increases.



[Watch Video Solution](#)

2. A resistor, an inductance and a capacitance are connected in series to an a.c. supply. When measured with the help of an a.c. voltmeter, the p.d. across the resistor is found to be 40V, across the inductance 30V, and across the capacitance 60V. What is the supply voltage?



[Watch Video Solution](#)



[Watch Video Solution](#)

3. A 60 volt-10 watt bulb is operated at 100 volt-60 Hz ac. The inductance required is



[Watch Video Solution](#)

4. In L-R circuit, the A.C. source has voltage 220V. If potential difference across inductor is 176V, the potential difference across the resistor (in Volts) is $K \times 33$. Find the value of K



[Watch Video Solution](#)

5. A coil having an inductance of $1/\pi$ henry is connected in series with a resistance of 300Ω . If 20 volt from a 200 cycle source are impressed across the combination, the value of the phase angle between the voltage and the current is :



[Watch Video Solution](#)

6. A 20volts *AC* is applied to a circuit consisting of a resistance and a coil with negligible

resistance. If the voltage across the resistance is $12V$, the voltage across the coil is




[Watch Video Solution](#)

7. Alternating voltage $V = 400 \sin (500\pi t)$ is applied across a resistance of $0.2k\Omega$. The r.m.s. value of current will be equal to




[Watch Video Solution](#)

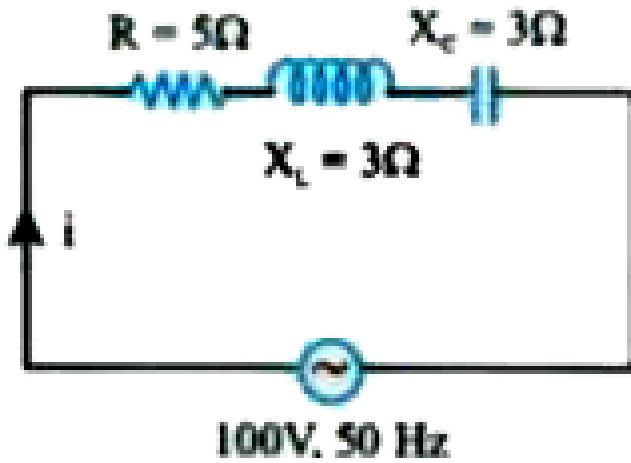8. A series L-C-R circuit is given in figure . The current through the circuit is



[Watch Video Solution](#)

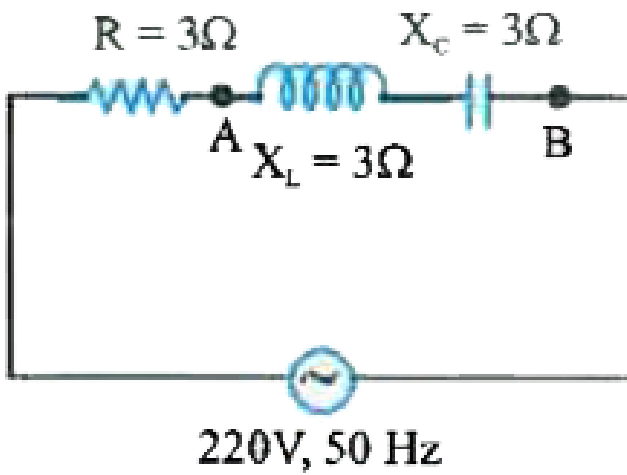9. In serial L-C-R circuit as shown in figure. The potential difference across A & B is



[Watch Video Solution](#)

10. If resistance of 100Ω , inductance of 0.5 henry and capacitor of $10 \times 10^{-6}F$ are connected in series through 50Hz AC supply, then impedance is

[Watch Video Solution](#)

11. The values of current and voltage in an AC circuits are respectively $i=4 \sin \omega t$ and $e = 100\cos[\omega t + (\pi/3)]$. The phase difference between voltage and current is



Watch Video Solution

12. Assertion (A) : An electric lamp is connected in series with a long solenoid of copper with air core and then connected to AC source. If an

iron rod is inserted in solenoid the lamp will become dim.

Reason (R) : If iron rod is inserted in solenoid, the induction of solenoid increases.



[Watch Video Solution](#)

13. A resistor, an inductance and a capacitance are connected in series to an a.c. supply. When measured with the help of an a.c. voltmeter, the p.d. across the resistor is found to be 40V, across the inductance 30V, and across the capacitance 60V. What is the supply voltage?



[Watch Video Solution](#)

14. A 60 volt-10 watt bulb is operated at 100 volt-60 Hz ac. The inductance required is



[Watch Video Solution](#)

15. In L-R circuit, the a.c. source has voltage 220 volt. If the potential difference across the inductance is 176 volt, the p.d. across the resistance will be



[Watch Video Solution](#)

 [Watch Video Solution](#)

16. Alternating voltage $V = 400 \sin (500\pi t)$ is applied across a resistance of $0.2k\Omega$. The r.m.s. value of current will be equal to



[Watch Video Solution](#)

17. If resistance of 100Ω , inductance of 0.5 henry and capacitor of $10 \times 10^{-6}F$ are connected in series through $50Hz$ AC supply, then impedance is



Watch Video Solution


18. The instantaneous values of current and voltage in an A.C. circuit are respectively $I = 4\sin\omega t$ and $E = 100\cos(\Omega t + \pi/3)$. The phase difference between voltage and current is



Watch Video Solution


EVALUATE YOURSELF-3

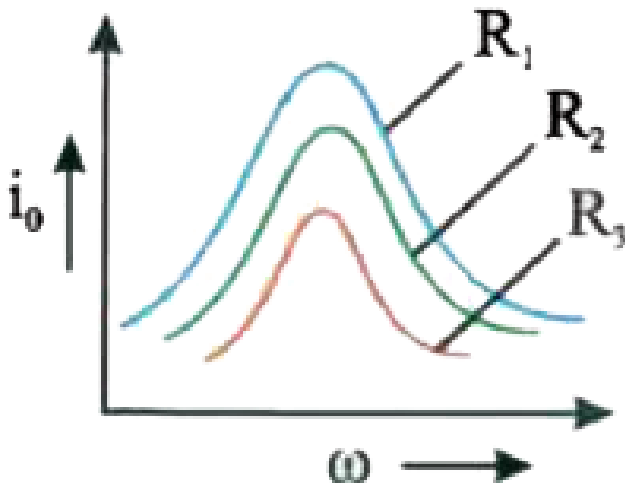1. The graph between current and frequency for LCR series circuit is drawn for three different resistor R_1, R_2 & R_3 . Which one is correct regarding resistance.




[Watch Video Solution](#)

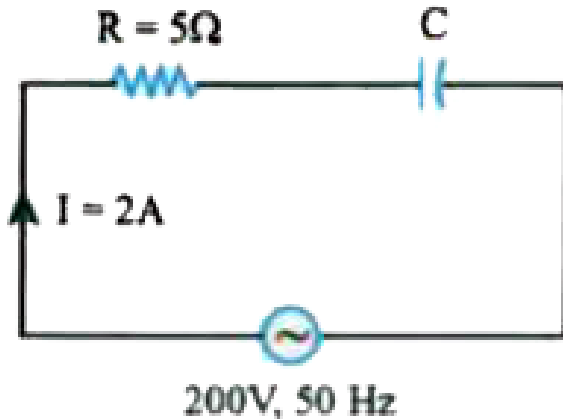2. In the given A.C. circuit the average power consumed in the circuit is




 [Watch Video Solution](#)

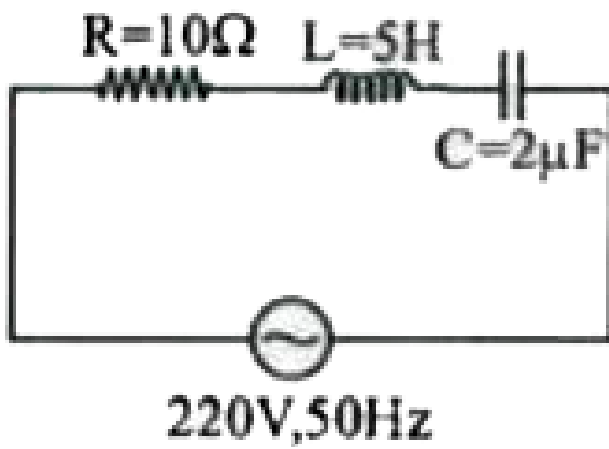3. The circuit shown in the diagram is in resonance. Power factor of the circuit is



[Watch Video Solution](#)

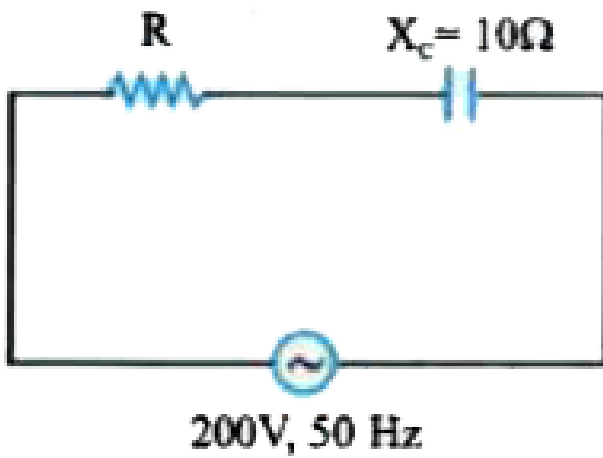4. Power factor of the A.C. circuit given in figure is 0.6 . The value of R is



[Watch Video Solution](#)

5. A 30 mH pure inductor is connected to 220V, 50 Hz A.C. supply .Net power absorbed by the circuit over a complete cycle is




[Watch Video Solution](#)

6. A resistor, a capacitor of $100\mu F$ capacitance and an inductor are in series with an AC source of frequency 50Hz . If the current in the circuit is in phase with the applied voltage. The inductance of the inductor is



[Watch Video Solution](#)

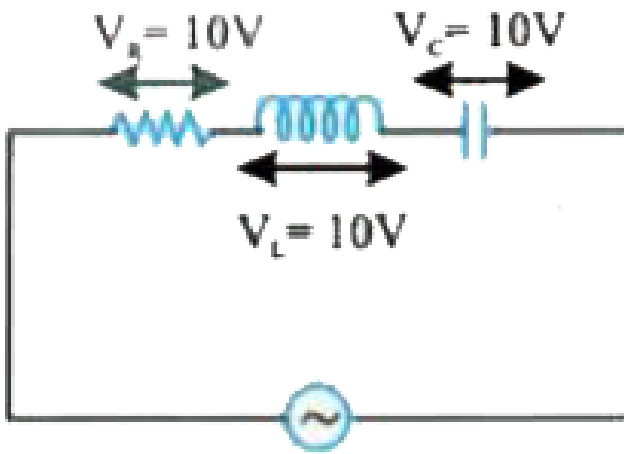7. In series L-C-R circuit as shown in figure the voltage of the source is



[Watch Video Solution](#)

8. In series L-C-R circuit the quality factor is


[Watch Video Solution](#)

9. The average power delivered to a series AC circuit is given by (symbols have their usual meaning):




Watch Video Solution

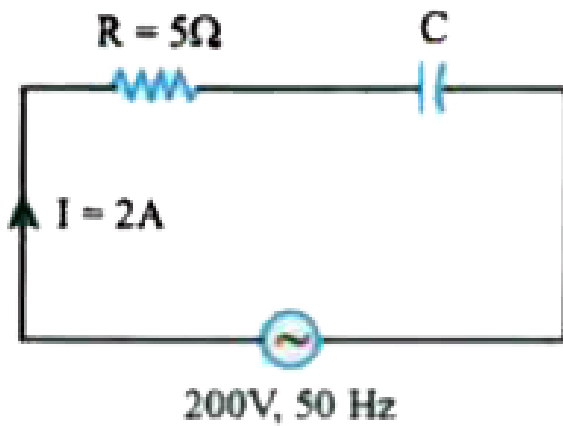10. In the given A.C. circuit the average power consumed in the circuit is




[Watch Video Solution](#)

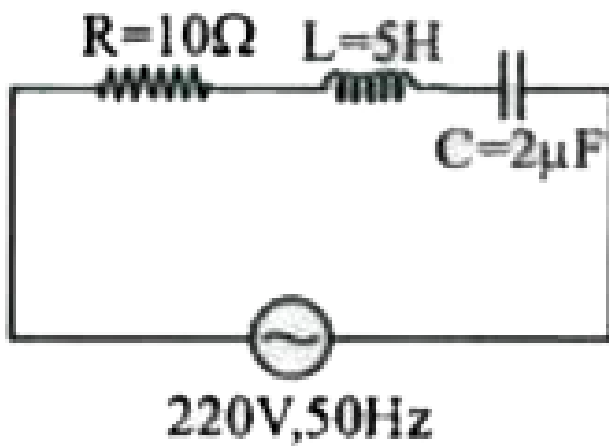11. The circuit shown in the diagram is in resonance. Power factor of the circuit is



[Watch Video Solution](#)

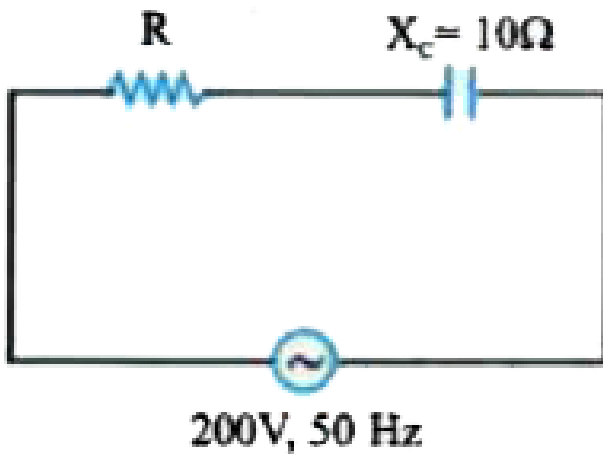12. Power factor of the A.C. circuit given in figure is 0.6 . The value of R is



 [Watch Video Solution](#)

13. A 30 mH pure inductor is connected to 220V, 50 Hz A.C. supply .Net power absorbed by the circuit over a complete cycle is


 [Watch Video Solution](#)

14. A resistor 10Ω , a capacitor of $100\mu F$ capacitance and an inductor are in series with an AC source of frequency 50Hz . If the current in the circuit is in phase with the applied voltage. The inductance of the inductor is



[Watch Video Solution](#)

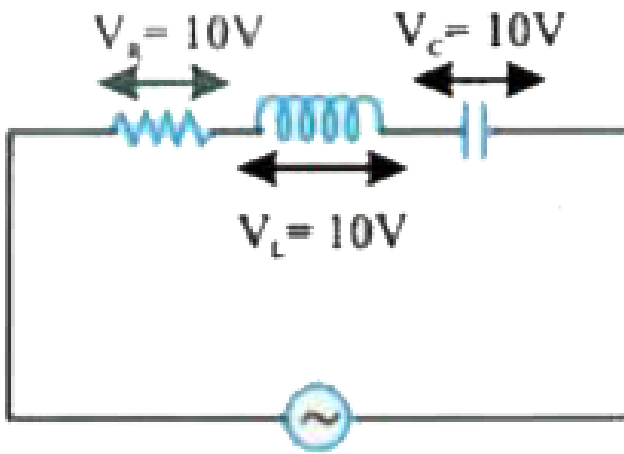15. In series L-C-R circuit as shown in figure the voltage of the source is



[Watch Video Solution](#)

16. In series L-C-R circuit the quality factor is

[Watch Video Solution](#)

17. The average power in LCR series circuit is



[Watch Video Solution](#)

EVALUATE YOURSELF-4

1. A transformer is used to illuminate a bulb of (36W and 12 V) with the help of 220 volt mains. If the efficiency of the transformer is 75%, then current in primary coil is



[Watch Video Solution](#)

2. The primary winding of a transformer has 100 turns and its secondary winding has 200 turns. The primary is connected to an ac supply of 120V and the current flowing in it is 10A. The voltage and the current in the secondary are



[Watch Video Solution](#)

3. A transformer has an efficiency of 80% and works at 100 volt and 4 kw. If the secondary voltage is 240 V. The current in secondary is



[Watch Video Solution](#)

4. A small town with a demand of 800 kW of electric power at 220 V is situated 15 km away from an electric plant generating power at 440 V. The resistance of the two line wires carrying power is 0.5Ω per km. The town gets power from the lines through a 4000-220 V step down transformer at a substation in the town.

Estimate the line power loss in the form of heat.

(b) How much power must the plant supply, assuming there is negligible power loss due to

leakage?

(c) Characterize the step up transformer at the plant.



Watch Video Solution

5. The core of a transformer is laminated to reduce



Watch Video Solution

6. In step down transformer 220 / 110 V the primary is connected to 10V battery. The output voltage is



[Watch Video Solution](#)

7. In an LCR series circuit the capacitance is changed from C to $4C$ For the same resonant frequency the inductance should be changed from L to .



[Watch Video Solution](#)

8. A transformer is used to illuminate a bulb of (36W and 12 V) with the help of 220 volt mains. If the efficiency of the transformer is 75%, then current in primary coil is



Watch Video Solution

9. The primary winding of a transformer has 100 turns and its secondary winding has 200 turns. The primary is connected to an ac supply of 120V and the current flowing in it is 10A. The voltage and the current in the secondary are



[Watch Video Solution](#)

10. A transformer with efficiency 80 % works at 4 kW and 100 V . If the secondary voltage is 200 V , then the primary and secondary currents are respectively



[Watch Video Solution](#)

11. A small town with a demand of 800 kW of electric power at 220 V is situated 15 km away from an electric plant generating power at 440

V. The resistance of the two line wires carrying power is 0.5Ω per km. The town gets power from the lines through a 4000-220 V step down transformer at a substation in the town.

Estimate the line power loss in the form of heat.

(b) How much power must the plant supply, assuming there is negligible power loss due to leakage?

(c) Characterize the step up transformer at the plant.



Watch Video Solution

12. The core of any transformer is laminated so as to



Watch Video Solution

13. In step down transformer 220 / 110 V the primary is connected to 10V battery. The output voltage is



Watch Video Solution

14. In an LCR series circuit the capacitance is changed from C to $4C$ For the same resonant frequency the inductance should be changed from L to .



[Watch Video Solution](#)

EXERCISE-1(C.W)

1. The r.m.s. value of $I = I_1 \sin \omega t + I_2 \cos \omega t$ is



[Watch Video Solution](#)

2. The frequency of A.C. is 50 Hz. How many times the current becomes zero in one second?



[Watch Video Solution](#)

3. The values of current and voltage in an AC circuits are respectively $i = 4 \sin \omega t$ and $e = 100 \cos[\omega t + (\pi/3)]$. The phase difference between voltage and current is



[Watch Video Solution](#)

4. An a.c. source is of 120 volts, 60 Hz . The value of the voltage after $1/360$ sec. from the start will be



[Watch Video Solution](#)

5. In general in an alternating current circuit



[Watch Video Solution](#)

6. The voltage of an AC supply varies with time (t) as $V = 120 \sin 100\pi t \cos 100\pi t$. The maximum voltage and frequency respectively are



[Watch Video Solution](#)

7. An inductance of negligible resistance, whose reactance is 22 ohm at 200 Hz is connected to a 220 V V, 50 Hz power line. What is the value of inductance and reactance ?



[Watch Video Solution](#)

8. In L-R circuit, the A.C. source has voltage 220V. If potential difference across inductor is 176V, the potential difference across the resistor (in Volts) is $K \times 33$. Find the value of K



[Watch Video Solution](#)

9. A pure resistance and a pure inductance are connected in series across a 100 volt. A.C. line. A voltmeter gives same reading whether connected across resistance or inductance. What does it read ?



[Watch Video Solution](#)

10. A direct current of 10A is superimposed on an alternating current $I = 40 \cos \omega t$. Amperes flowing through a wire. The effective value of the resulting current will be



[Watch Video Solution](#)

11. In an AC circuit resistance, inductance and capacitance are connected in series. The values of potential differences across the three are 70

V, 90 V and 65 V respectively. The value of the potential difference of the AC source is



[Watch Video Solution](#)

12. A $10\mu F$ capacitor is connected across a 200V, 50Hz A.C. supply. The peak current through the circuit is



[Watch Video Solution](#)

13. In a LCR circuit having $L = 8.0$ henry, $C = 0.5\mu F$ and $R = 100$ ohm in series. The resonance frequency in per second is



[Watch Video Solution](#)

14. An $L - C - R$ series circuit has a maximum current of $5A$. If $L = 0.5H$ and $C = 8\mu F$, then the angular frequency of AC voltage is



[Watch Video Solution](#)

15. The current in series *LCR* circuit will be the maximum when ω is



[Watch Video Solution](#)

16. The resonant frequency of a circuit of negligible resistance containing an inductance of 50 mH and a capacitance of 500 pf is



[Watch Video Solution](#)

17. A series LCR circuit is tuned to resonance.

The impedance of the circuit now is



Watch Video Solution

18. In a resonant LCR circuit,



Watch Video Solution

19. Energy required to establish a current of 4 A

in a coil of self-inductance $L=200$ mH is



[Watch Video Solution](#)

20. If a power of 100 W is being supplied across a potential difference of 200 V , current flowing is



[Watch Video Solution](#)

21. In an AC circuit voltage applied is $e=220 \sin 100 t$. if the impedance is 110Ω and phase difference between the current and voltage is 60° the power consumption is equal to



[Watch Video Solution](#)

22. An alternating voltage is applied across the R-L combination $V = 220 \sin 120 t$ and the current $I = 4 \sin (120 t - 60^\circ)$ develops. The power consumption is



[Watch Video Solution](#)

23. In an A.C. circuit , e and I are given by,

$$e = 100\sin(100t) \text{ volt, } I = 100\sin\left(100t + \frac{\pi}{3}\right) \text{ mA.}$$

The power dissipated in circuit is



[Watch Video Solution](#)

24. In an *AC* circuit with voltage V and current I , the power dissipated is



[Watch Video Solution](#)

25. An rms voltage of 110 V is applied across a series circuit having a resistance 11Ω and an impedance 22Ω . The power consumed is



Watch Video Solution

26. Power factor is one for



Watch Video Solution

27. A coil of inductive reactance 31Ω has a resistance of 8ohm . It is placed in series with a condenser of capacitive reactance 25Ω . The combination is connected to an *ac* source of 110V . The power factor of the circuit is



Watch Video Solution

28. An ac ammeter is used to measure current in a circuit. When a given direct current passes through the circuit. The ac ammeter reads 3 A. When another alternating current passes through the circuit, the ac ammeter reads 4A. Then find the reading of this ammeter (inA), if dc and ac flow through the circuit simultaneously.



Watch Video Solution

29. A transformer steps an *A. C* voltage from 230V to 2300V. If the number of turns in the secondary coil is 1000, the number of turns in the primary coil will be



Watch Video Solution

30. The transformer ratio of a transformer is 5. If the primary voltage of the transformer is 400V, 50Hz the secondary voltage will be



Watch Video Solution

31. A step-up transformer works on $220V$ and gives $2A$ to an external resistor. The turn ratio between the primary and secondary coils is $2 : 25$. Assuming 100% efficiency, find the secondary voltage, primary current and power delivered respectively



Watch Video Solution

32. The transformer ratio of transformer is $10:1$. The current in the primary circuit if the

secondary current required is 100A assuming the transformer be ideal, is



[Watch Video Solution](#)

33. The transformer ratio of transformer is 10:1. If the primary voltage is 440 V, secondary emf is



[Watch Video Solution](#)

34. A fully charged capacitor C with initial charge q_0 is connected to a coil of self inductance L at $t=0$. The time at which the energy is stored equally between the electric and the magnetic fields is



[Watch Video Solution](#)

35. The r.m.s. value of $I = I_1 \sin \omega t + I_2 \cos \omega t$ is



[Watch Video Solution](#)

36. The frequency of A.C. is 50 Hz. How many times the current becomes zero in one second?



[Watch Video Solution](#)

37. The instantaneous values of current and voltage in an A.C. circuit are respectively $I = 4\sin\omega t$ and $E = 100\cos(\omega t + \pi/6)$. The phase difference voltage and current is



[Watch Video Solution](#)

38. An a.c. source is of 120 volts, 60 Hz . The value of the voltage after $1/360$ sec. from the start will be



Watch Video Solution

39. In general in an alternating current circuit



Watch Video Solution

40. The voltage of an AC supply varies with time (t) as $V = 120 \sin 100\pi t \cos 100\pi t$. The maximum voltage and frequency respectively are



[Watch Video Solution](#)

41. An inductance of negligible resistance, whose reactance is 22 ohm at 200 Hz is connected to a 220 V V, 50 Hz power line. What is the value of inductance and reactance ?



[Watch Video Solution](#)

42. In L-R circuit, the A.C. source has voltage $220V$. If potential difference across inductor is $176V$, the potential difference across the resistor (in Volts) is $K \times 33$. Find the value of K



Watch Video Solution

43. A pure resistance and a pure inductance are connected in series across a 100 volt. A.C. line. A voltmeter gives same reading whether connected across resistance or inductance. What does it read ?



Watch Video Solution

44. In an oscillating system, a restoring force is a must. In a L-C circuit, restoring force is provided by a/ An

A. Inductor

B. Resistor

C. Both 1 and 2

D. Capacitor



[Watch Video Solution](#)

45. A direct current of 5A is superimposed on an alternating current $I = 10 \sin\omega t$ flowing through a wire . The effective value of the resulting current will be



[Watch Video Solution](#)

46. In an AC circuit resistance, inductance and capacitance are connected in series. The values of potential differences across the three are 70

V, 90 V and 65 V respectively. The value of the potential difference of the AC source is



[Watch Video Solution](#)

47. A $10\mu F$ capacitor is connected across a $200V$, $50Hz$ A.C. supply. The peak current through the circuit is



[Watch Video Solution](#)

48. In a LCR circuit having $L = 8.0$ henry, $C = 0.5\mu F$ and $R = 100$ ohm in series. The resonance frequency in per second is



[Watch Video Solution](#)

49. An $L - C - R$ series circuit has a maximum current of $5A$. If $L = 0.5H$ and $C = 8\mu F$, then the angular frequency of AC voltage is



[Watch Video Solution](#)

50. The current in series LCR circuit will be the maximum when ω is



[Watch Video Solution](#)

51. The resonant frequency of a circuit of negligible resistance containing an inductance of 50 mH and a capacitance of 500 pf is



[Watch Video Solution](#)

52. A series LCR circuit is tuned to resonance.

The impedance of the circuit now is



Watch Video Solution

53. Energy needed to establish an alternating

current I in a coil of self inductance L is



Watch Video Solution

54. If a power of 100 W is being supplied across a potential difference of 200 V , current flowing is



[Watch Video Solution](#)

55. In an AC circuit voltage applied is $e=220 \sin 100 t$. if the impedance is 110Ω and phase difference between the current and voltage is 60° the power consumption is equal to



[Watch Video Solution](#)

56. An alternating voltage is applied across the R-L combination $V = 220 \sin 120 t$ and the current $I = 4 \sin (120 t - 60^\circ)$ develops. The power consumption is



[Watch Video Solution](#)

57. In an A.C. circuit, V and I are given by $V = 100 \sin (100t)$ volt.

$$I = 100 \sin (100 t + \pi/4) \text{ mA}$$

The power dissipated in the circuit is



[Watch Video Solution](#)

58. An rms voltage of 110 V is applied across a series circuit having a resistance 11Ω and an impedance 22Ω . The power consumed is



Watch Video Solution

59. Power factor is one for



Watch Video Solution

60. A coil of inductive reactance 31Ω has a resistance of 8Ω . It is placed in series with a condenser of capacitive reactance 25Ω . The combination is connected to an a.c. source of 110 volt. The power factor of the circuit is



Watch Video Solution

61. An ac ammeter is used to measure current in a circuit. When a given direct current passes through the circuit. The ac ammeter reads 3 A. When another alternating current passes

through the circuit, the ac ammeter reads 4A. Then find the reading of this ammeter (inA), if dc and ac flow through the circuit simultaneously.



[Watch Video Solution](#)

62. A transformer steps up an A.C. voltage from 230 V to 2300 V. If the number of turns in the secondary coil is 1000, the number of turns in the primary coil will be



[Watch Video Solution](#)

63. The transformer ratio of a transformer is 5. If the primary voltage of the transformer is 400V, 50Hz the secondary voltage will be



Watch Video Solution

64. A step-up transformer works on 220V and gives 2A to an external resistor. The turn ratio between the primary and secondary coils is 2 : 25. Assuming 100% efficiency, find the

secondary voltage, primary current and power delivered respectively



[Watch Video Solution](#)

65. The transformer ratio of transformer is 10:1. The current in the primary circuit if the secondary current required is 100A assuming the transformer be ideal, is



[Watch Video Solution](#)

66. The transformer ratio of transformer is 10:1. If the primary voltage is 440 V, secondary emf is



[Watch Video Solution](#)

67. A fully charged capacitor C with initial charge q_0 is connected to a coil of self inductance L at $t=0$. The time at which the energy is stored equally between the electric and the magnetic fields is



[Watch Video Solution](#)

EXERCISE-1(H.W)

1. An inductor has a resistance R inductance L . It is connected to an A.C source of e.m.f. E_v and angular frequency ω then the current I_v in the circuit is



[Watch Video Solution](#)

2. The rms value of an ac of 50Hz is 10A. The time taken by an alternating current in reaching from zero to maximum value and the peak value will be



[Watch Video Solution](#)

3. The peak value A. C is $2\sqrt{2}A$. It's apparent value will be



[Watch Video Solution](#)

4. Alternating current in circuit is given by

$I = I_0 \sin 2\pi nt$. Then the time by the current to

rise from zero to r.m.s value is equal to



[Watch Video Solution](#)

5. The form factor for a sinusoidal A. C is



[Watch Video Solution](#)

6. The voltage of an A. C source varies with

time according to the equation

$$V = 50\sin 100\pi t \cos 100\pi t.$$

Where ' t ' is in second and ' V ' is in volt. Then



[Watch Video Solution](#)

7. A coil of self-inductance $\left(\frac{1}{\pi}\right)H$ is connected in series with a 300Ω resistance. A voltage of $200V$ at frequency $200Hz$ is applied to this combination. The phase difference between the voltage and the current will be



[Watch Video Solution](#)

8. In an LCR series circuit the rms voltages across R , L and C are found to be $10V$, $10V$ and $20V$ respectively. The rms voltage across the entire combination is



[Watch Video Solution](#)

9. An alternating voltage of $e = 100\sqrt{2}\sin(100t)$ volt is connected to a condenser of $0.5\mu F$ through an A.C. ammeter. The reading of the ammeter will be



[Watch Video Solution](#)

[Watch Video Solution](#)

10. In a circuit, the frequency is $f = \frac{1000}{2\pi} \text{ Hz}$ and the inductance is 2 henry, then the reactance will be



[Watch Video Solution](#)

11. A conductor of capacity 1pF is connected to an A. C source of 220V and 50Hz frequency. The current flowing in the circuit will be



[Watch Video Solution](#)

12. The frequency at which the inductive reactance of $2H$ inductance will be equal to the capacitive reactance of $2\mu F$ capacitance (nearly)



[Watch Video Solution](#)

13. If the instantaneous current in a circuit is given by $I = 2\cos(\omega t + \phi)$ amperes, the rms value of the current is



[Watch Video Solution](#)

14. A 100km telegraph wire hasd capacity of $0.02\mu\text{F}/\text{km}$, if it carries an alternating current of frequency 5kHZ . The value of an inductrance required to be connected in series so that the impedance is minimum.



[Watch Video Solution](#)

15. In a series LCR circuit, resistance $R = 10\Omega$ and the impedance $Z = 20\Omega$ the phase difference between the current and the voltage is



[Watch Video Solution](#)

16. In an $L - C - R$ series circuit,

$R = \sqrt{5}\Omega$, $X_L = 9\Omega$, $X_C = 7\Omega$. If applied voltage

in the circuit is $50V$ then impedance of the

circuit in ohm will be




[Watch Video Solution](#)

17. In the following circuit, the values of current

flowing in the circuit at $f = 0$ and $f = \infty$ will

respectively be

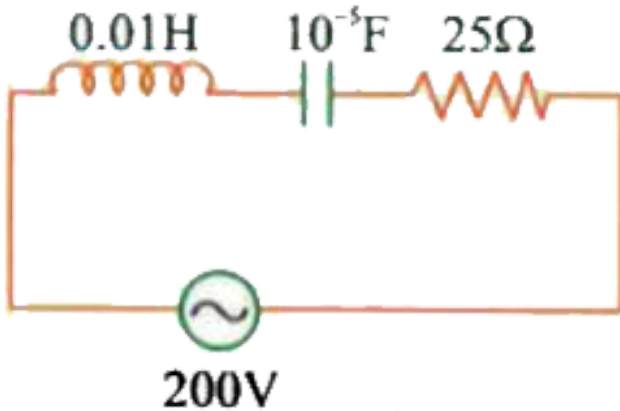

[▶ Watch Video Solution](#)

18. Radio receiver receives a message at 300m band, If the available inductance is 1mH , then calculate required capacitance.

[▶ Watch Video Solution](#)

19. In oscillating Lc circuit, the total stored energy is U and maximum charge upon capacitor is $\frac{Q}{2}$, the energy stored in the inductor is



Watch Video Solution

20. A voltage 10V and frequency 10^3 Hz is applied to $\frac{1}{\pi}\mu F$ capacitor is series with a resistor of 500Ω . Find the power factor of the circuit and the power dissipated



[Watch Video Solution](#)

21. If power factor of a R-L series circuit is $\frac{1}{2}$ when applied voltage is $V = 100\sin 100\pi t$ volt and resistance of circuit is 200Ω then the inductance of the circuit is



[Watch Video Solution](#)


22. A circuit consisting of an inductance and a resistance joined to a 200 volt supply (A.C.) It

draws a current of 10 ampere. If the power used in the circuit is 1500 watt, then the watt less current component is



[Watch Video Solution](#)

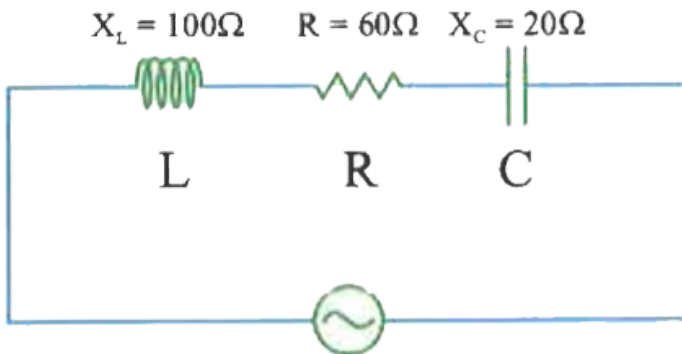23. The power factor for the circuit shown below is



220 V, 50 Hz



[Watch Video Solution](#)

24. A series L-C-R circuit is connected across an

AC source $E = 10\sin\left[100\pi t - \frac{\pi}{6}\right]$. Current from

the supply is $I = 2\sin\left[100\pi t + \frac{\pi}{12}\right]$, What is the

average power dissipated?



[Watch Video Solution](#)

25. If power factor is $1/2$ in a series RL , circuit

$R = 100\Omega$. AC mains is used then L is



Watch Video Solution

26. An LC circuit contains a 20 mH inductor and a $50\mu\text{F}$ capacitor with an initial charge of 10 mC. The resistance of the circuit is negligible.

Let the instant the circuit is closed be $t = 0$.

(a) What is the total energy stored initially ? Is it conserved during the oscillations?

(b) What is the natural frequency of the circuit?

(c) At what time is the energy stored? (i) Completely electrical ? (ii) Completely magnetic ?

(d) At what time is the total energy shared equally between the inductor and the capacitor ?

(e) If a resistor is inserted in the circuit, how much energy is eventually dissipated as heat ?



[Watch Video Solution](#)

27. In a step up transformer, if ratio of turns of primary to secondary is 1:10 and primary voltage is 230V. If the load current is 2A. Then the current in primary is



[Watch Video Solution](#)

 [Watch Video Solution](#)

28. In a transformer, number of turns in the primary coil are 140 and that in the secondary coil are 280. If current in primary coil is 4A, then that in the secondary coil is



[Watch Video Solution](#)

29. The number of turns in the primary and secondary coils of a transformer are 200 and 800 respectively. If the voltage developed

across the secondary is 240 V, then the potential difference across each turn of the primary will be



[Watch Video Solution](#)

30. The number of turns in primary and secondary coils of a transformer is 50 and 200, respectively. If the current in the primary coil is 4 A, then current in the secondary coil is



[Watch Video Solution](#)

31. A transformer has 1500 turns in the primary coil and 1125 turns in the secondary coil. If a voltage of 200V is applied across the primary coil, then the voltage in the secondary coil is :



[Watch Video Solution](#)

32. In a primary coil 5A current is flowing on 220 volts. In the secondary coil 2200V voltage produces. Then ratio of number of turns in secondary coil and primary coil will be



[Watch Video Solution](#)

33. The turn ratio of a transformers is given as 2:3. If the current through the primary coil is 3A, thus calculate the current through load resistance



Watch Video Solution

34. In a electrical circuit consisting of an inductance 'L' and a capacitance 'C' at resonance. The time period of oscillations of charge is



Watch Video Solution

35. An A.C circuit contains a resistor ' R ' an inductor ' L ' and a capacitor ' C ' connected in series. When it is connected to an A.C generator of fixed output voltage and variable frequency, the current in the circuit is found to be leading the applied voltage $\frac{\pi}{4}$ rad, when the frequency is f_1 . when the frequency of the generator increased to f_2 the current is found to be lagging behind the applied voltage by $\frac{\pi}{4}$ rad. The resonant frequency of the circuit is



[Watch Video Solution](#)

36. An inductor has a resistance R inductance L . It is connected to an *A.C* source of e.m.f. E_V and angular frequency ω then the current I_V in the circuit is



[Watch Video Solution](#)

37. The r.m.s value of an a.c of 59Hz is 10A . The time taken by the alternating current in

reaching from zero to maximum value and the peak value of current will be



[Watch Video Solution](#)

38. The peak value A. C is $2\sqrt{2}A$. It's apparent value will be



[Watch Video Solution](#)

39. The electric current in an AC circuit is given by $I = I_0 \sin \omega t$. What is the time taken by the

current to change from its maximum value to the *rms* value?



[Watch Video Solution](#)

40. The form factor for a sinusoidal *A. C* is



[Watch Video Solution](#)

41. The voltage of an *A. C* source varies with time according to the equation

$$V = 50\sin 100\pi t \cos 100\pi t.$$

Where ' t ' is in second and ' V ' is in volt. Then

 [Watch Video Solution](#)

42. A coil of self-inductance $\left(\frac{1}{\pi}\right)H$ is connected in series with a 300Ω resistance. A voltage of $200V$ at frequency $200Hz$ is applied to this combination. The phase difference between the voltage and the current will be

 [Watch Video Solution](#)

43. In an LCR series circuit the rms voltages across R , L and C are found to be $10V$, $10V$ and $20V$ respectively. The rms voltage across the entire combination is



Watch Video Solution

44. An alternating voltage $E = 200\sqrt{2}\sin(100t)V$ is applied to a $2\mu F$ capacitor through an A.C. ammeter. The reading of the ammeter is



Watch Video Solution

45. In a circuit, the frequency is $f = \frac{1000}{2\pi} \text{ Hz}$ and the inductance is 2 henry, then the reactance will be



Watch Video Solution

46. A conductor of capacity 1pF is connected to an A. C source of 220V and 50Hz frequency. The current flowing in the circuit will be



Watch Video Solution

47. The frequency at which the inductive reactance of $2H$ inductance will be equal to the capacitive reactance of $2\mu F$ capacitance (nearly)



[Watch Video Solution](#)

48. If the instantaneous current in a circuit is given by $I = 2\cos(\omega t + \phi)A$, the rms value of the current is



[Watch Video Solution](#)

49. A 100km telegraph wire hasd capacity of $0.02\mu\text{F}/\text{km}$, if it carries an alternating current of frequency 5kHZ . The value of an inductance required to be connected in series so that the impedance is minimum.



Watch Video Solution

50. In a series LCR circuit, resistance $R = 10\Omega$ and the impedance $Z = 20\Omega$ the phase difference between the current and the voltage is



[Watch Video Solution](#)

51. In an $L - C - R$ series circuit,


$R = \sqrt{5}\Omega$, $X_L = 9\Omega$, $X_C = 7\Omega$. If applied voltage in the circuit is $50V$ then impedance of the circuit in ohm will be



[Watch Video Solution](#)

52. In the following circuit, the values of current flowing in the circuit at $f = 0$ and $f = \infty$ will

respectively be

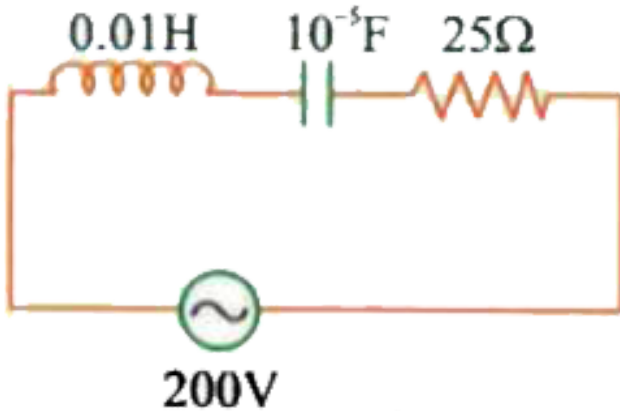

[▶ Watch Video Solution](#)

53. Radio receiver receives a message at 300m band, If the available inductance is 1mH , then calculate required capacitance.

[▶ Watch Video Solution](#)

54. In oscillating Lc circuit, the total stored energy is U and maximum charge upon capacitor is $\frac{Q}{2}$, the energy stored in the inductor is



[Watch Video Solution](#)

55. A voltage 10V and frequency 10^3 Hz is applied to $\frac{1}{\pi}\mu F$ capacitor is series with a resistor of 500Ω . Find the power factor of the circuit and the power dissipated



[Watch Video Solution](#)

56. If power factor of a R-L series circuit is $\frac{1}{2}$ when applied voltage is $V = 100\sin 100\pi t$ volt and resistance of circuit is 200Ω then the inductance of the circuit is



[Watch Video Solution](#)


57. A circuit consisting of an inductance and a resistance joined to a 200 volt supply (A.C.) It

draws a current of 10 ampere. If the power used in the circuit is 1500 watt, then the wattless current component is



[Watch Video Solution](#)

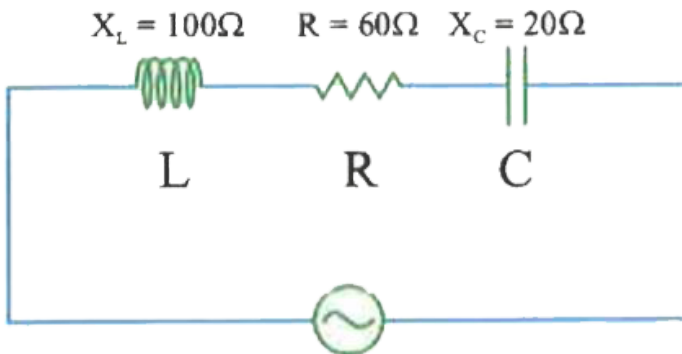58. The power factor for the circuit shown below is



220 V, 50 Hz



[Watch Video Solution](#)

59. A series L-C-R circuit is connected across an

AC source $E = 10\sin\left[100\pi t - \frac{\pi}{6}\right]$. Current from

the supply is $I = 2\sin\left[100\pi t + \frac{\pi}{12}\right]$, What is the

average power dissipated?



[Watch Video Solution](#)

60. If power factor is $1/2$ in a series RL , circuit

$R = 100\Omega$. AC mains is used then L is



[Watch Video Solution](#)

61. An LC circuit contains a 20 mH inductor and $25\mu\text{F}$ capacitor with an initial charge of 5 mC. The total energy stored in the circuit initially is



[Watch Video Solution](#)

62. In a step up transformer, if ratio of turns of primary to secondary is 1:10 and primary voltage is 230V. If the load current is 2A. Then the current in primary is



[Watch Video Solution](#)

63. In a transformer, number of turns in the primary coil are 140 and that in the secondary coil are 280. If current in primary coil is 4A, then that in the secondary coil is



[Watch Video Solution](#)

64. The number of turns in the primary and secondary coils of a transformer are 200 and 800 respectively. If the voltage developed

across the secondary is 240 V, then the potential difference across each turn of the primary will be



[Watch Video Solution](#)

65. The number of turns in primary and secondary coils of a transformer is 50 and 200, respectively. If the current in the primary coil is 4 A, then current in the secondary coil is



[Watch Video Solution](#)

66. A transformer has 1500 turns in the primary coil and 1125 turns in the secondary coil. If a voltage of 200V is applied across the primary coil, then the voltage in the secondary coil is :



Watch Video Solution

67. In a primary coil 5A current is flowing on 220 volts. In the secondary coil 2200V voltage produces. Then ratio of number of turns in secondary coil and primary coil will be



Watch Video Solution

68. The turn ratio of a transformers is given as 2:3. If the current through the primary coil is 3A, thus calculate the current through load resistance



Watch Video Solution

69. In a electrical circuit consisting of an inductance 'L' and a capacitance 'C' at resonance. The time period of oscillations of charge is



Watch Video Solution

70. An $A.C$ circuit contains a resistor ' R ' an inductor ' L ' and a capacitor ' C ' connected in series. When it is connected to an $A.C$ generator of fixed output voltage and variable frequency, the current in the circuit is found to be leading the applied voltage $\frac{\pi}{4}$ rad, when the frequency is f_1 . when the frequency of the generator increased to f_2 the current is found to be lagging behind the applied voltage by $\frac{\pi}{4}$ rad. The resonant frequency of the circuit is



[Watch Video Solution](#)

EXERCISE-2(C.W)

1. The rms value of an ac of 50Hz is 10A. The time taken by an alternating current in reaching from zero to maximum value and the peak value will be



[Watch Video Solution](#)

2. Two alternating voltage generators produce emfs of the same amplitude (E_0) but with a phase difference of $(\pi)/3$. The resultant emf is



[Watch Video Solution](#)

3. A resistance of 20Ω is connected to a source of an alternating potential $V = 220\sin(100\pi t)$. The time taken by the current to change from the peak value to rms value is



[Watch Video Solution](#)

4. An inductor, a capacitor and a resistor are connected in series to an a.c. supply. When measured with an a.c. voltmeter, the potential difference across the inductor, capacitor and resistor are respectively 90 volt, 60 volt and 40 volt. Then the supply voltage is



[Watch Video Solution](#)

5. The magnetic field energy in an inductor changes from maximum value to minimum

value in 5.0ms when connected to an AC source.

The frequency of the source is



[Watch Video Solution](#)

6. In an L-R circuit, an inductance of 0.1 H and a resistance of 1Ω are connected in series with an ac source of voltage $V = 5 \sin 10 t$. The phase difference between the current and applied voltage will be



[Watch Video Solution](#)

7. The coil of choke in a circuit



[Watch Video Solution](#)

8. In a circuit, the current lags behind the voltage by a phase difference of $\pi/2$, the circuit will contain which of the following ?



[Watch Video Solution](#)

9. The reactance of a capacitor of capacitance C is X. If both the frequency and capacitance be


doubled, then new reactance will be



[Watch Video Solution](#)

10. A pure inductor and a pure resistor are connected in series and an ac supply is connected across this combination. Ideal ac volt meters v_1 and v_2 show 120 volt and 160 volt respectively . What is the phase difference

between V_1 and V_2 .

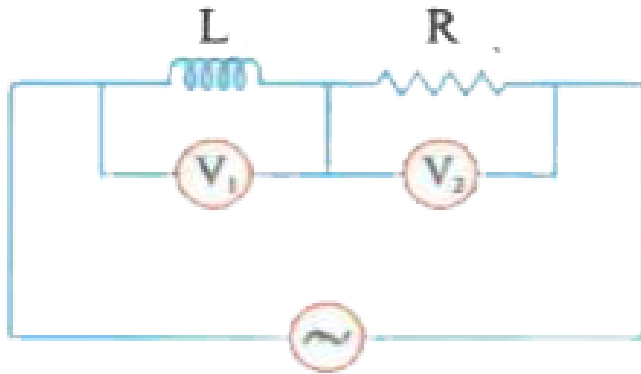

[▶ Watch Video Solution](#)

11. In L-R circuit, the A.C. source has voltage 220V. If potential difference across inductor is 176V, the potential difference across the resistor (in Volts) is $K \times 33$. Find the value of K

[▶ Watch Video Solution](#)

12. In an LCR circuit, the capacitance is made one-fourth, when in resonance. Then what should be the change in inductance, so that the circuit remains in resonance?



Watch Video Solution

13. A coil of inductance 5.0 mH and negligible resistance is connected to an alternating voltage $V = 10\sin(100t)$. The peak current in the circuit will be:



[Watch Video Solution](#)

14. An alternating e.m.f. $100 \cos 100 t$ volt is connected in series to a resistance of 10 ohm and inductance 100mH. The phase difference between the current in the circuit and the e.m.f. is



[Watch Video Solution](#)

15. Which increase in frequency of an AC supply, the impedance of an L-C-R series circuit



[Watch Video Solution](#)


16. An e.m.f. $E = 4\cos(1000t)$ volt is applied to an LR circuit of inductance $3mH$ and resistance $4ohm$. The amplitude of current in the circuit is



[Watch Video Solution](#)

17. The figure shows variation of R , X_L and X_C with frequency f in a series L, C, R circuit. Then for what frequency point, the circuit is

inductive ?

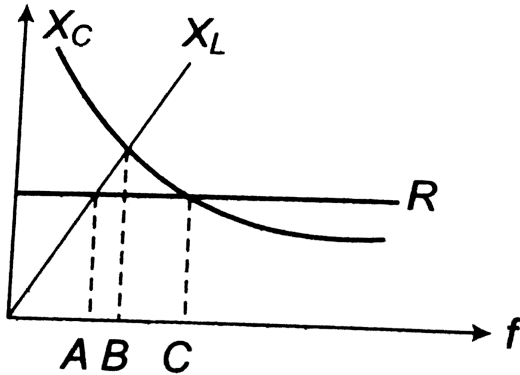

[▶ Watch Video Solution](#)

18. In a circuit L , C and R are connected in series with an alternating voltage source of frequency f . The current lead the voltages by 45° . The value of C is :

[▶ Watch Video Solution](#)

 [Watch Video Solution](#)

19. In an LCR circuit, the capacitance is made one-fourth, when in resonance. Then what should be the change in inductance, so that the circuit remains in resonance?



[Watch Video Solution](#)

20. A lamp consumes only 50 % of peak power in an *a. c.* circuit. What is the phase difference

between the applied voltage and the circuit current



[Watch Video Solution](#)

21. For a series L C R circuit, the power loss at resonance is



[Watch Video Solution](#)

22. Radiowaves of wavelength 360 m are transmitted from a transmitter. The inductance

of the coil which must be connected with capacitor of capacity $3.6\mu F$ in a resonant circuit to receive these waves will be approximately



[Watch Video Solution](#)

23. The potential difference V across and the current I flowing through an instrument in an AC circuit are given by:

$$V = 5\cos\omega t \text{ volt}$$

$$I = 2\sin\omega t \text{ Amp.}$$



[Watch Video Solution](#)

24. Power loss in *AC* circuit will be minimum when



Watch Video Solution

25. A direct current of 5 amp is superimposed on an alternating current $I = 10\sin\omega t$ flowing through a wire. The effective value of the resulting current will be:



Watch Video Solution

26. An LCR circuit has $L = 10mL$, $R = 3\Omega$, and $C = 1\mu F$ connected in series to a source of $15\cos\omega t$ volt. The current amplitude at a frequency that is 10% lower than the resonant frequency is



Watch Video Solution

27. An AC source of angular frequency ω is fed across a resistor R and a capacitor C in series. The current registered is I . If now the frequency of source is changed to $\omega/3$ (but maintaining

the same voltage), the current in the circuit is found to be halved. The ratio of reactance to resistance at the original frequency ω will be.



[Watch Video Solution](#)

28. in a step-up transformer, the turn ratio is 1:2 leclanche cell (e.m.f. 1.5V) is connected across the primary. The voltage developed in the secondary would be



[Watch Video Solution](#)

29. The efficiency of a transformer is 98%. The primary voltage and current are 200V and 6A. If the secondary voltage is 100V, the secondary current



Watch Video Solution

30. The rms value of an AC of 50Hz is 20 amp. The time taken by an alternating current in reaching from zero to maximum value and the peak value of current will be



Watch Video Solution

31. Two alternating voltage generators produce emfs of the same amplitude (E_0) but with a phase difference of $(\pi)/3$. The resultant emf is



[Watch Video Solution](#)

32. A resistance of 20Ω is connected to a source of an alternating potential $V = 220\sin(100\pi t)$. The time taken by the current to change from the peak value to rms value is



[Watch Video Solution](#)

[Watch Video Solution](#)

33. An inductor, a capacitor and a resistor are connected in series to an a.c. supply. When measured with an a.c. voltmeter, the potential difference across the inductor, capacitor and resistor are respectively 90 volt, 60 volt and 40 volt. Then the supply voltage is



[Watch Video Solution](#)

34. The magnetic field energy in an inductor changes from maximum value to minimum value in 5.0ms when connected to an AC source.

The frequency of the source is



Watch Video Solution

35. In an L-R circuit, an inductance of 0.1 H and a resistance of 1Ω are connected in series with an ac source of voltage $V = 5 \sin 10 t$. The phase difference between the current and applied voltage will be



[Watch Video Solution](#)

36. In a circuit, the current lags behind the voltage by a phase difference of $\pi/2$, the circuit will contain which of the following ?




[Watch Video Solution](#)

37. The reactance of a capacitor of capacitance C is X . If both the frequency and capacitance be doubled, then new reactance will be



[Watch Video Solution](#)

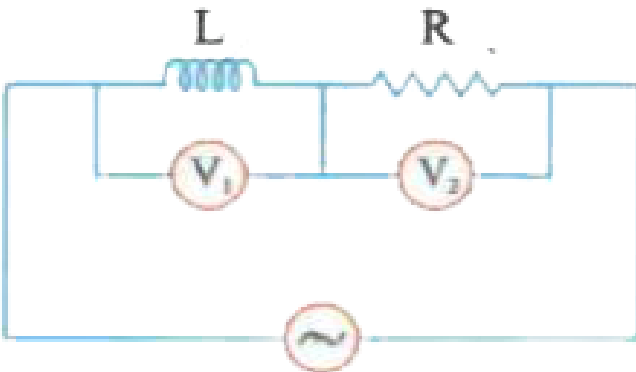38. A pure inductor and a pure resistor are connected in series and an ac supply is connected across this combination. Ideal ac voltage meters v_1 and v_2 show 120 volt and 160 volt respectively . What is the phase difference between V_1 and V_2 .



39. In L-R circuit, the A.C. source has voltage $220V$. If potential difference across inductor is $176V$, the potential difference across the resistor (in Volts) is $K \times 33$. Find the value of K



Watch Video Solution

40. In an LCR circuit, the capacitance is made one-fourth, when in resonance. Then what should be the change in inductance, so that the circuit remains in resonance?



[Watch Video Solution](#)

41. A coil of inductance 5.0 mH and negligible resistance is connected to an alternating voltage $V = 10\sin(100t)$. The peak current in the circuit will be:



[Watch Video Solution](#)

42. An alternating e.m.f. $100 \cos 100 t$ volt is connected in series to a resistance of 10 ohm and inductance 100mH. The phase difference

between the current in the circuit and the e.m.f.
is



[Watch Video Solution](#)

43. Which increase in frequency of an AC supply
, the impedance of an L-C-R series circuit




[Watch Video Solution](#)

44. An e.m.f. $E = 4\cos(1000t)$ volt is applied to an
 LR circuit of inductance $3mH$ and resistance

40hm. The amplitude of current in the circuit is

[▶ Watch Video Solution](#)

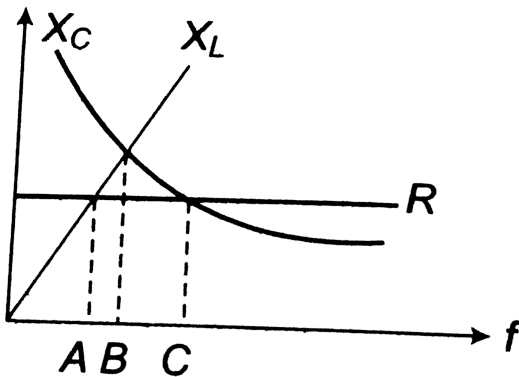45. The figure shows variation of R , X_L and X_C with frequency f in a series L, C, R circuit. Then for what frequency point, the circuit is inductive ?



[▶ Watch Video Solution](#)

 Watch Video Solution

46. In a circuit L , C and R are connected in series with an alternating voltage source of frequency f . The current lead the voltages by 45° . The value of C is :



Watch Video Solution

47. In an LCR circuit, the capacitance is made one-third, then what should be change in

inductance, so that the circuit remains in resonance ?



[Watch Video Solution](#)

48. A lamp consumes only 50 % of peak power in an *a. c.* circuit. What is the phase difference between the applied voltage and the circuit current



[Watch Video Solution](#)

49. For a series L C R circuit, the power loss at resonance is



Watch Video Solution

50. Radiowaves of wavelength 360 m are transmitted from a transmitter. The inductance of the coil which must be connected with capacitor of capacity $3.6\mu F$ in a resonant circuit to receive these waves will be approximately



Watch Video Solution

51. The potential difference V across and the current I flowing through an instrument in an AC circuit are given by:

$$V = 5\cos\omega t \text{ volt}$$

$$I = 2\sin\omega t \text{ Amp.}$$



Watch Video Solution

52. Power loss in AC circuit will be minimum when



Watch Video Solution

53. A direct current of $5\sqrt{2}$ amp, is superimposed on an alternating current $I = 10\sin\omega t$ flowing through a wire. The effective value of the resulting current will be



Watch Video Solution

54. An LCR circuit has $L = 10mL$, $R = 3\Omega$, and $C = 1\mu F$ connected in series to a source of $15\cos\omega t$ volt. The current amplitude at a frequency that is 10% lower than the resonant frequency is



[Watch Video Solution](#)

55. An AC source of angular frequency ω is fed across a resistor R and a capacitor C in series. The current registered is I . If now the frequency of source is changed to $\omega/3$ (but maintaining the same voltage), the current in the circuit is found to be halved. The ratio of reactance to resistance at the original frequency ω will be.



[Watch Video Solution](#)

56. in a step-up transformer, the turn ratio is 1:2 leclanche cell (e.m.f. 1.5V) is connected across the primary. The voltage developed in the secondary would be



Watch Video Solution

57. The efficiency of a transformer is 98%. The primary voltage and current are 200V and 6A. If the secondary voltage is 100V, the secondary current



Watch Video Solution

EXERCISE-2(H.W)

1. The voltage over a cycle varies as

$$V = V_0 \sin \omega t \text{ for } 0 \leq t \leq \frac{\pi}{\omega}$$
$$= -V_0 \sin \omega t \text{ for } \frac{\pi}{\omega} \leq t \leq \frac{2\pi}{\omega}$$

The average value of the voltage one cycle is



[Watch Video Solution](#)


2. A pure inductor of 25.0 mH is connected to a source of 220 V. Find the inductive reactance

and rms current in the circuit if the frequency of the source is 50 Hz.




[Watch Video Solution](#)

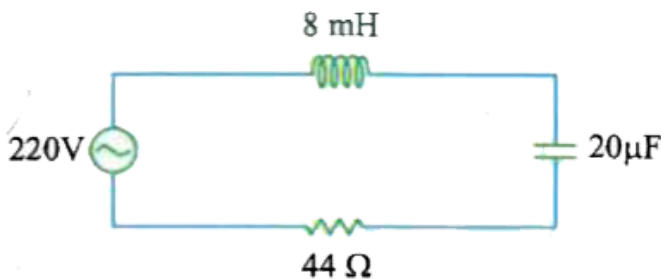3. For the series LCR circuit shown in figure, the resonating frequency and current amplitude at resonance respectively are



[Watch Video Solution](#)

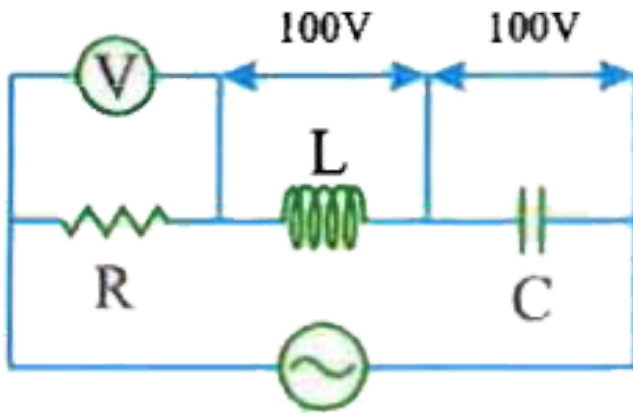4. In the circuit shown in figure, what will be the reading of the voltmeter ?



200 V, 100 Hz



[Watch Video Solution](#)

5. In a series LCR circuit the voltage across the resistance, capacitance and inductance is 10 V each. If the capacitance is short circuited, the voltage across the inductance will be $\frac{10^x}{\sqrt{2}}$ what is value of x



[Watch Video Solution](#)

6. If a circuit made up of a resistance $1\ \Omega$ and inductance 0.01 H , an alternating emf of 200 volt at 50 Hz is connected, then find the phase

difference between the current and the emf in the circuit.



[Watch Video Solution](#)

7. An e.m.f. $E = 4\cos(1000t)$ volt is applied to an LR circuit of inductance $3mH$ and resistance $4ohm$. The amplitude of current in the circuit is



[Watch Video Solution](#)

8. In a LCR circuit the $P.D$ between the terminals of the inductance is $60V$, between the terminals of the capacitor is $30V$ and that between the terminals of resistance is $40V$. The supply voltage will be equal to.....



[Watch Video Solution](#)

9. A series LCR circuit has $R = 5\Omega$, $L = 40mH$ and $C = 1\mu F$, the bandwidth of the circuit is



[Watch Video Solution](#)

10. A pure resistive circuit element X when connected to an ac supply of peak voltage 400 V gives a peak current of 5 A which is in phase with the voltage. A second circuit element Y, when connected to the same ac supply also gives the same value of peak current but the current lags behind by 90° . If the series combination of X and Y is connected to the same supply, what will be the rms value of current?



[Watch Video Solution](#)

11. In a series resonant LCR circuit the voltage across R is 100 volts and $R = 1k(\Omega)$ with $C = 2(\mu)F$. The resonant frequency (ω) is $200rad/s$. At resonance the voltage across L is



Watch Video Solution

12. A charged capacitor discharges through a resistance R with time constant τ . The two are now placed in series across an AC source of angular frequency $\omega = \frac{1}{\tau}$. The impedance of the circuit will be



[Watch Video Solution](#)


13. An inductor of inductance 2H and a resistance of 10Ω are connected in series to an ac source of 1109 V , 60 Hz . The current in the circuit will be



[Watch Video Solution](#)

14. An ideal resistance R , ideal inductance L , ideal capacitance C and AC voltmeters V_1 , V_2 , V_3 and V_4 are connected to an AC source as


shown . At resonance

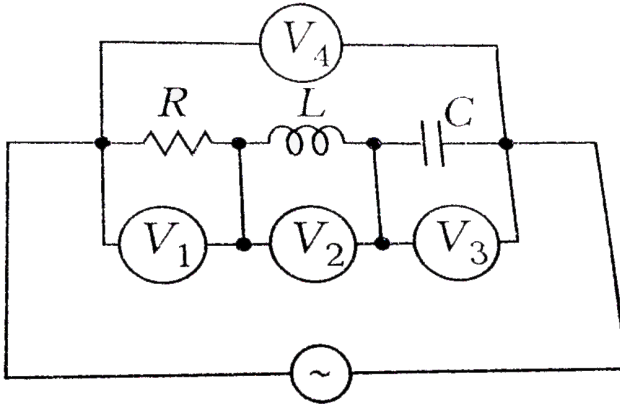

[Watch Video Solution](#)

15. In the series LCR circuit as shown in the figure, the voltmeter V and ammeter A reading


are

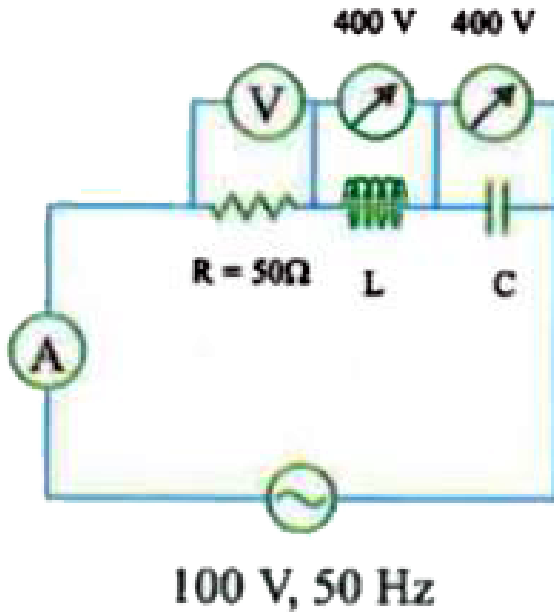

[▶ Watch Video Solution](#)

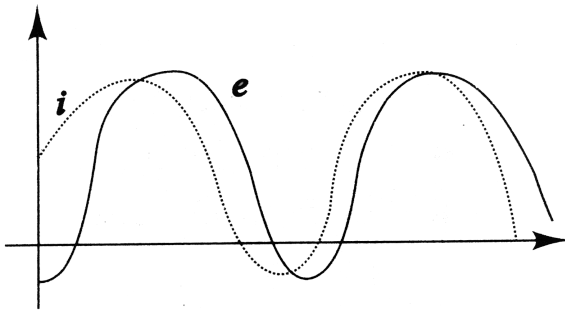16. When an ac source of emf $e = E_0 \sin(100t)$ is connected across a circuit, the phase difference

between emf e and current I in the circuit is observed to be $(\pi)/4$ as shown in fig. If the circuit consists possibly only of R-C or R-C of L-R series, find the relationship find the relationship between the two elements.



[Watch Video Solution](#)


17. An inductance of $\frac{200}{\pi}mH$ a capacitance of $\frac{10^{-3}}{\pi}$ and a resistance of 10Ω are connected in series with an AC source of $220V, 50Hz$. The phase angle of the circuit is



[Watch Video Solution](#)


18. An LCR series ac circuit is at resonance with $10V$ each across L,C and R. If the resistance is halved, the respective voltages across L,C and R

are

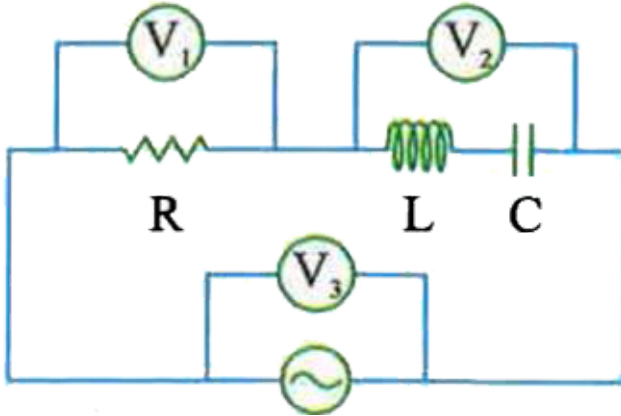

[Watch Video Solution](#)

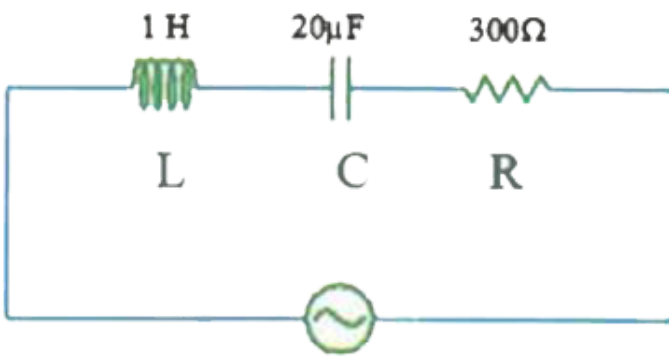19. In the series LCR circuit shown, the impedance is



50V, 50Hz



Watch Video Solution

20. In a series resonant LCR circuit, the voltage across R is 100V and the value of $R = 1000\Omega$. The capacitance of the capacitor is $5 \times 10^{-6}F$, angular frequency of ac is 200rads^{-1} . Then the


potential difference across the inductance coil is



[Watch Video Solution](#)

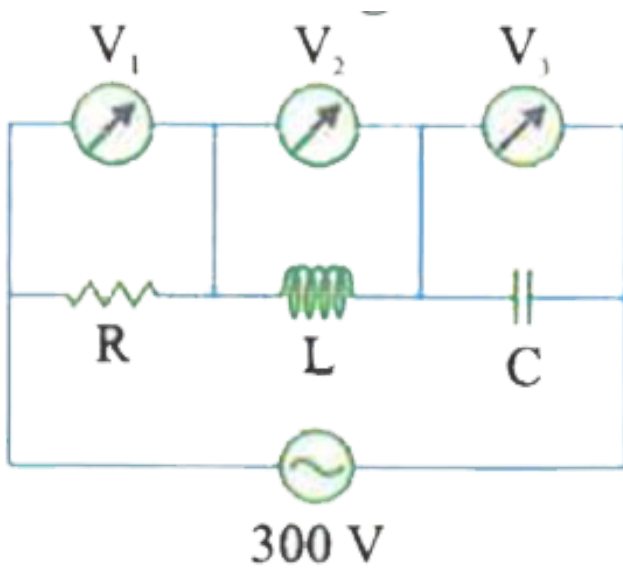21. The figure shows a LCR network connected to 300V ac supply. The circuit elements are such that $R = X_L = X_C = 10\Omega$ V_1 , V_2 and V_3 are three ac voltmeters connected as shown in the figure. Which of the following represents the


correct set of readings of the voltmeters ?



[▶ Watch Video Solution](#)

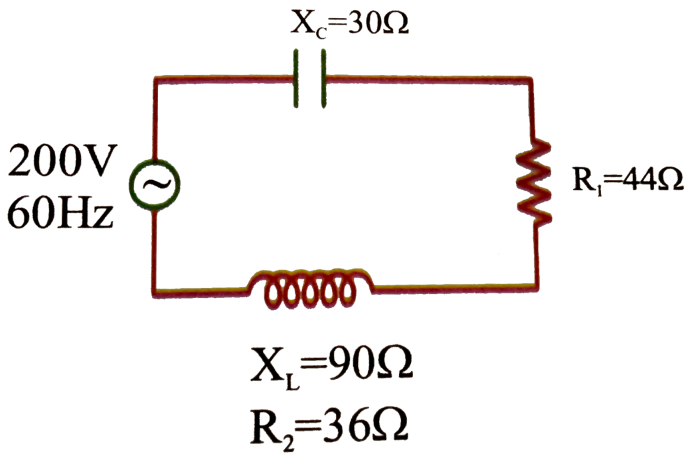22. A series circuit connected across a 200V, 60Hz line consists of a capacitive reactance 30Ω non inductive resistor of 44Ω

and a coil of inductive reactance 90Ω and resistance 36Ω as shown in the diagram



The power dissipated in the inductance coil is

 [Watch Video Solution](#)

23. In an AC circuit, the reactance is equal to the resistance. The power factor of the circuit

will be



[Watch Video Solution](#)

24. An inductance L , a capacitance C and a resistance R may be connected to an AC source of angular frequency ω in three different combinations of RC , RL and LC in series. Assume that $\omega L = \frac{1}{\omega C}$. The power drawn by the three combinations are P_1, P_2, P_3 respectively. Then



[Watch Video Solution](#)

25. An LC circuit contains a 40 mH inductor and a $25\mu\text{F}$ capacitor. The resistance of the circuit is negligible. The time is measured from the instant the circuit is closed. The energy stored in the circuit is completely magnetic at time (in milliseconds)



Watch Video Solution

26. An alternating supply of 220 V is applied across a circuit with resistance 22Ω and

impedance 44Ω . The power dissipated in the circuit is



[Watch Video Solution](#)

27. In an AC circuit, the current is given by

$$i = 5\sin\left(100t - \frac{\pi}{2}\right) \text{ and the AC potential is}$$

$V = 200\sin(100t)\text{volt}$. Then the power

consumption is



[Watch Video Solution](#)

28. A capacitor of capacitance $1\mu F$ is charged to a potential of $1V$, it is connected in parallel to an inductor of inductance $10^{-3}H$. The maximum current that will flow in the circuit has the value



Watch Video Solution

29. A coil of inductance $0.1H$ is connected to $50V, 100Hz$ generator and current is found to be $0.5A$. The potential difference across resistance of coil is:



[Watch Video Solution](#)

30. An alternating voltage (in volts) given by $V = 200\sqrt{2}\sin(100t)$ is connected to $1\mu F$ capacitor through an ideal ac ammeter in series. The reading of the ammeter and the average power consumed in the circuit shall be



[Watch Video Solution](#)

31. In an circuit, V and I are given by

$$V = 150\sin(150t)V \quad \text{and} \quad I = 150\sin\left(150t + \frac{\pi}{3}\right)A.$$

The power dissipated in the circuit is



[Watch Video Solution](#)

32. A series resonant LCR circuit has a quality factor (Q -factor)=0.4. If $R = 2k\Omega$, $C = 0.1\mu F$ then the value of inductance is



[Watch Video Solution](#)

33. A resistor of 500Ω and an inductance of 0.5 H are in series with an ac source which is given by $V = 100\sqrt{2}\sin(1000t)$. The power factor of the combination is



[Watch Video Solution](#)

34. A transformer is used to light a 140 W, 24 V lamp from 240 V AC mains. The current in mains cable is 0.7 A, find the efficiency of transformer.



[Watch Video Solution](#)

35. A transformer has 100 turns in the primary coil and carries 8A current. If input power is one kilowatt, the number of turns required in the secondary coil to have 500V output will be



Watch Video Solution

36. A transmitting station transmits radiowave of wavelength 360 m. What is the inductance of a coil required with a condenser of capacity

1.20 μF in the resonant circuit to receive the radiowaves ? (Use $\pi^2=10$)



Watch Video Solution

37. A step-down transformer is used on a 1000V line to deliver 20A at 120V at the secondary coil. If the efficiency of the transformer is 80 % the current drawn from the line is.




Watch Video Solution

38. A power transmission line feeds input power at 2300 V to a step down transformer with its primary windings having 4000 turns. What should be the number of turns in the secondary windings in order to get output power at 230 V?



Watch Video Solution

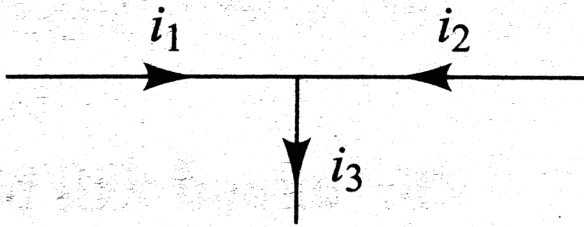39. If $i_1 = 3\sin\omega t$ and $(i_2) = 4\cos\omega t$, then (i_3) is



[Watch Video Solution](#)

40. The voltage over a cycle varies as

$$V = V_0 \sin \omega t \text{ for } 0 \leq t \leq \frac{\pi}{\omega}$$
$$= -V_0 \sin \omega t \text{ for } \frac{\pi}{\omega} \leq t \leq \frac{2\pi}{\omega}$$

The average value of the voltage one cycle is



[Watch Video Solution](#)


41. A pure inductor of 25.0 mH is connected to a source of 220 V . Find the inductive reactance and rms current in the circuit if the frequency of the source is 50 Hz .



Watch Video Solution


42. For the series LCR circuit shown in figure, the resonating frequency and current

amplitude at resonance respectively are

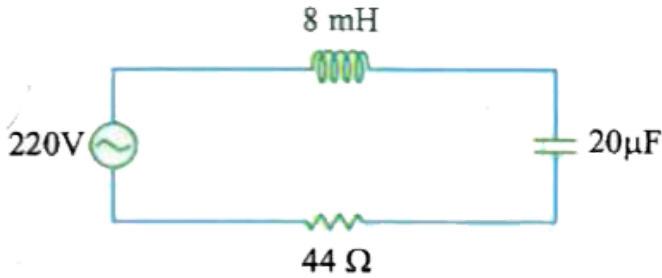

[Watch Video Solution](#)

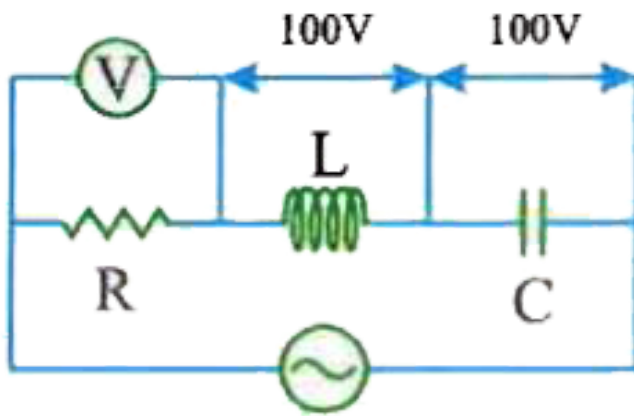43. In the circuit shown in figure, what will be the reading of the voltmeter ?



200 V, 100 Hz



[Watch Video Solution](#)

44. In a series LCR circuit the voltage across the resistance, capacitance and inductance is 10 V each. If the capacitance is short circuited,

the voltage across the inductance will be $\frac{10^x}{\sqrt{2}}$

what is value of x



[Watch Video Solution](#)

45. If a circuit made up of a resistance 1Ω and inductance 0.01 H , an alternating emf of 200 volt at 50 Hz is connected, then find the phase difference between the current and the emf in the circuit.



[Watch Video Solution](#)

46. An e.m.f. $E = 4\cos(1000t)$ volt is applied to an LR circuit of inductance $3mH$ and resistance $4ohm$. The amplitude of current in the circuit is



[Watch Video Solution](#)

47. In a LCR circuit the $P.D$ between the terminals of the inductance is $60V$, between the terminals of the capacitor is $30V$ and that between the terminals of resistance is $40V$. The supply voltage will be equal to.....



[Watch Video Solution](#)

48. A series LCR circuit has $R = 5\Omega$, $L = 40mH$ and $C = 1\mu F$, the bandwidth of the circuit is



Watch Video Solution

49. A pure resistive circuit element X when connected to an ac supply of peak voltage 400 V gives a peak current of 5 A which is in phase with the voltage. A second circuit element Y, when connected to the same ac supply also

gives the same value of peak current but the current lags behind by 90° . If the series combination of X and Y is connected to the same supply, what will be the rms value of current?



[Watch Video Solution](#)

50. In a series resonant LCR circuit the voltage across R is 100 volts and $R = 1k(\Omega)$ with $C = 2(\mu)F$. The resonant frequency (ω) is $200rad/s$. At resonance the voltage across L is



[Watch Video Solution](#)

 [Watch Video Solution](#)

51. A charged capacitor discharges through a resistance R with time constant τ . The two are now placed in series across an AC source of angular frequency $\omega = \frac{1}{\tau}$. The impedance of the circuit will be



[Watch Video Solution](#)

52. An inductor of inductance $2H$ and a resistance of 10Ω are connected in series to an


ac source of 1109 V, 60 Hz. The current in the circuit will be



[Watch Video Solution](#)

53. An ideal resistance R , ideal inductance L , ideal capacitance C and AC voltmeters V_1 , V_2 , V_3 and V_4 are connected to an AC source as


shown . At resonance

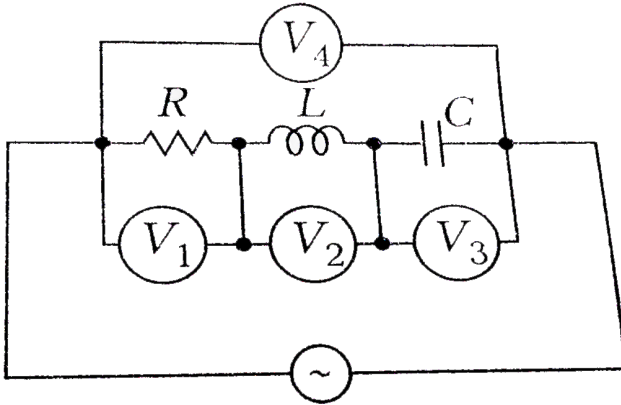


 [Watch Video Solution](#)

54. A series LCR circuit is connected to an ac source of variable frequency. When the frequency is increased continuously, starting from a small value, the power factor

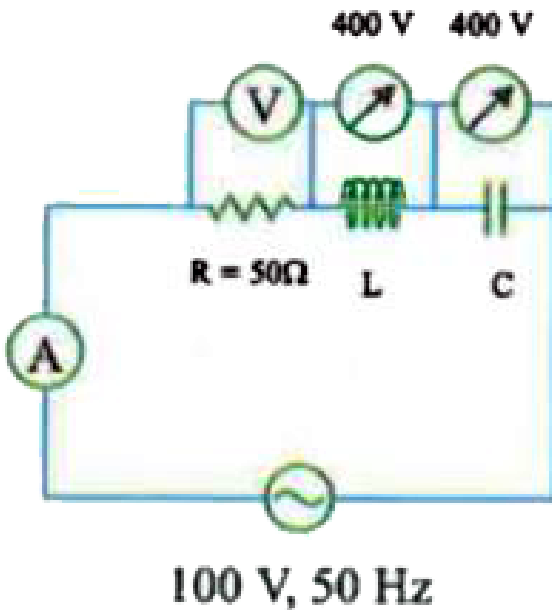55. In the series LCR circuit as shown in the figure, the voltmeter V and ammeter A reading are



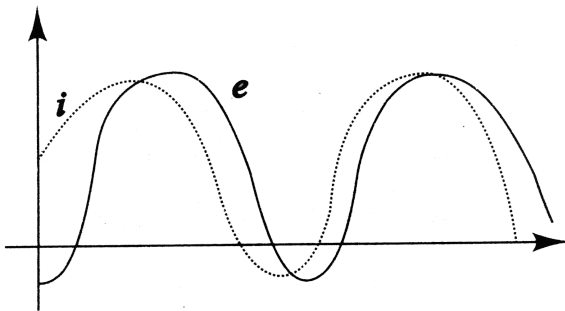56. When an ac source of emf $e = E_0 \sin(100t)$ is connected across a circuit, the phase difference between emf e and current i in the circuit is observed to be $(\pi)/4$ as shown in fig. If the circuit consists possibly only of R-C or R-L or L-R series, find the relationship between the two elements.





[Watch Video Solution](#)


57. An inductance of $\frac{200}{\pi} mH$ a capacitance of $\frac{10^{-3}}{\pi}$ and a resistance of 10Ω are connected in series with an AC source of $220V, 50Hz$. The phase angle of the circuit is



[Watch Video Solution](#)

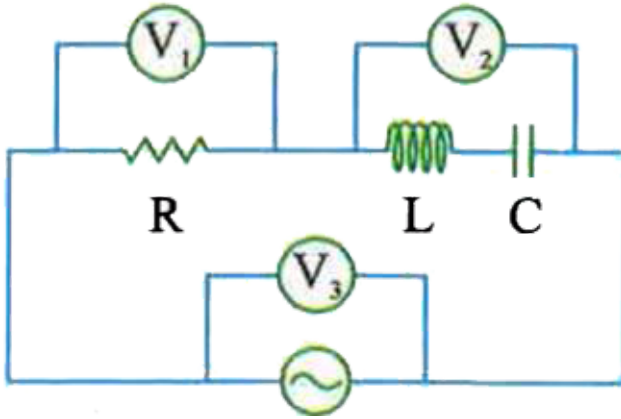
58. An LCR series ac circuit is at resonance with $10 V$ each across L.C and R. If the resistance is

halved, the respective voltages across L,C and R are



[▶ Watch Video Solution](#)

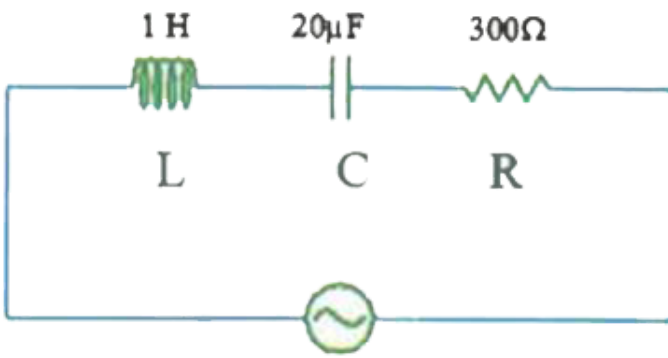59. In the series LCR circuit shown, the impedance is



50V, 50Hz



Watch Video Solution

60. In a series resonant LCR circuit, the voltage across R is 100V and the value of $R = 1000\Omega$. The capacitance of the capacitor is $5 \times 10^{-6}F$, angular frequency of ac is 200rads^{-1} . Then the


potential difference across the inductance coil is



[Watch Video Solution](#)

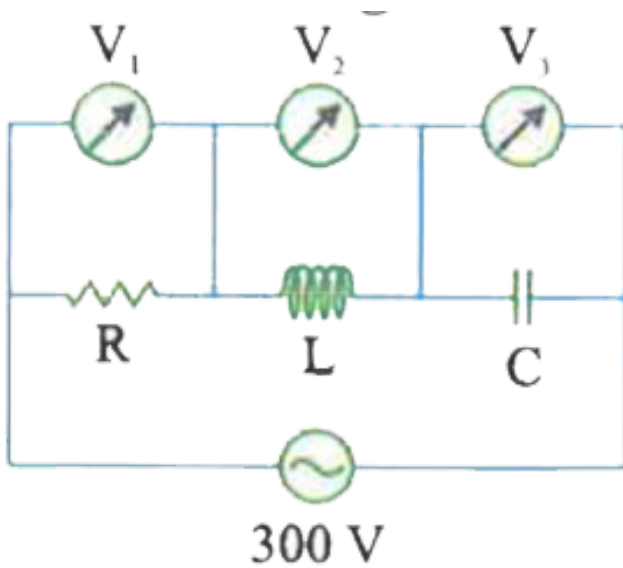61. The figure shows a LCR network connected to 300V ac supply. The circuit elements are such that $R = X_L = X_C = 10\Omega$ V_1 , V_2 and V_3 are three ac voltmeters connected as shown in the figure. Which of the following represents the


correct set of readings of the voltmeters ?



[Watch Video Solution](#)

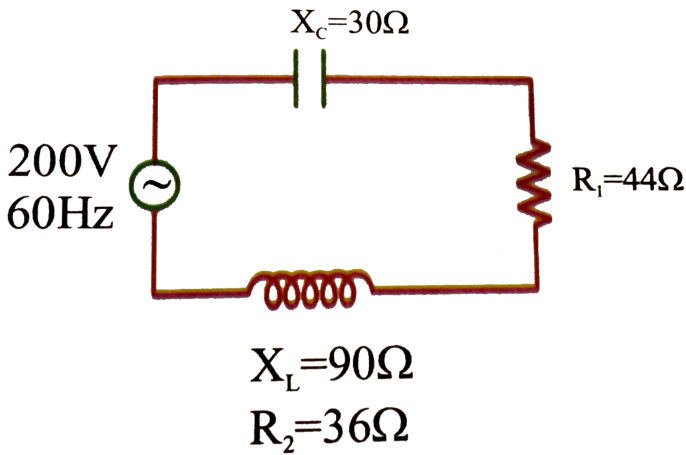62. A series circuit connected across a 200V, 60Hz line consists of a capacitive reactance 30Ω non inductive resistor of 44Ω

and a coil of inductive reactance 90Ω and resistance 36Ω as shown in the diagram



The power dissipated in the inductance coil is

[Watch Video Solution](#)

63. In an AC circuit, the reactance is equal to the resistance. The power factor of the circuit

will be



[Watch Video Solution](#)

64. An inductance L , a capacitance C and a resistance R may be connected to an AC source of angular frequency ω in three different combinations of RC , RL and LC in series. Assume that $\omega L = \frac{1}{\omega C}$. The power drawn by the three combinations are P_1, P_2, P_3 respectively. Then



[Watch Video Solution](#)

65. An Lc circuit contains a 40 mH inductor and a $25\mu F$ capacitor. The resistance of the circuit is negligible. The time is measured from the instant the circuit is closed. The energy stored in the circuit is completely magnetic at time (in milliseconds)



Watch Video Solution

66. An alternating supply of 220 V is applied across a circuit with resistance 22Ω and

impedance 44Ω . The power dissipated in the circuit is



[Watch Video Solution](#)

67. In an A.C. circuit, the current flowing in inductance is $I = 5\sin(100t - \pi/2)$ amperes and the potential difference is $V = 200\sin(100t)$ volts. The power consumption is equal to



[Watch Video Solution](#)

68. A capacitor of capacitance $1\mu F$ is charged to a potential of $1V$, it is connected in parallel to an inductor of inductance $10^{-3}H$. The maximum current that will flow in the circuit has the value



Watch Video Solution

69. A coil of inductance $0.1H$ is connected to $50V, 100Hz$ generator and current is found to be $0.5A$. The potential difference across resistance of coil is:



[Watch Video Solution](#)

70. An alternating voltage (in volts) given by $V = 200\sqrt{2}\sin(100t)$ is connected to $1\mu F$ capacitor through an ideal ac ammeter in series. The reading of the ammeter and the average power consumed in the circuit shall be



[Watch Video Solution](#)

71. In an A.C. circuit , e and I are given by,

$$e = 100\sin(100t) \text{ volt, } I = 100\sin\left(100t + \frac{\pi}{3}\right) \text{ mA.}$$

The power dissipated in circuit is



[Watch Video Solution](#)

72. A series resonant LCR circuit has a quality factor (Q-factor)=0.4. If $R = 2k\Omega$, $C = 0.1\mu F$ then the value of inductance is



[Watch Video Solution](#)

73. A resistor of 500Ω and an inductance of 0.5 H are in series with an ac source which is given by $V = 100\sqrt{2}\sin(1000t)$. The power factor of the combination is



[Watch Video Solution](#)

74. A transformer is used to light a 140 W, 24 V lamp from 240 V AC mains. The current in mains cable is 0.7 A, find the efficiency of transformer.



[Watch Video Solution](#)

75. A transformer has 100 turns in the primary coil and carries 8A current. If input power is one kilowatt, the number of turns required in the secondary coil to have 500V output will be



Watch Video Solution

76. A transmitting station transmits radiowave of wavelength 360 m. What is the inductance of a coil required with a condenser of capacity

1.20 μF in the resonant circuit to receive the radiowaves ? (Use $\pi^2=10$)



Watch Video Solution

77. A step-down transformer is used on a 1000V line to deliver 20A at 120V at the secondary coil. If the efficiency of the transformer is 80 % the current drawn from the line is.




Watch Video Solution

78. A power transmission line feeds input power at 2300 V to a step down transformer with its primary windings having 4000 turns. What should be the number of turns in the secondary windings in order to get output power at 230 V?



Watch Video Solution

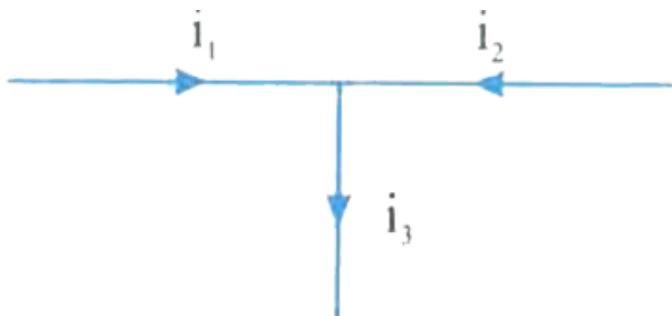79. If $i_1 = 3\sin\omega t$ and $i_2 = 6\cos\omega t$, then i_3 is



Watch Video Solution

EXERCISE - 3

1. What is the value of inductance L for which the current is a maximum in series LCR circuit

with $C = 10\mu F$ and $\omega = 1000 \frac{\text{rad}}{\text{s}}$?



[Watch Video Solution](#)

2. In any AC circuit the emf (e) and the current (i) at any instant are given respectively by

$$e = E_0 \sin \omega t$$

$$i = I_0 \sin(\omega t - \phi)$$

The average power in the circuit over one cycle of AC is



[Watch Video Solution](#)

3. A wire of resistance R is connected in series with an inductor of reactance ωL . Then quality factor of RL circuit is




[Watch Video Solution](#)

4. An LCR series circuit having 220 V ac source, inductance $L = 25mH$ and resistance $R = 100\Omega$. If voltage across inductor is just double of voltage across resistor then find out frequency of source.



[Watch Video Solution](#)

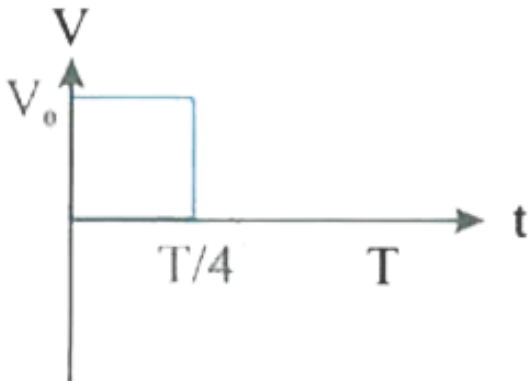5. A periodic voltage V varies with time t as shown in figure. T is the time period. Find the rms value of the voltage.



[Watch Video Solution](#)

6. An a.c. voltage is applied to a pure inductor L , drives a current in the inductor. The current in the inductor would be




[Watch Video Solution](#)

7. Power dissipated in an $L - C - R$ series circuit connected to an AC source of emf ε is



[Watch Video Solution](#)

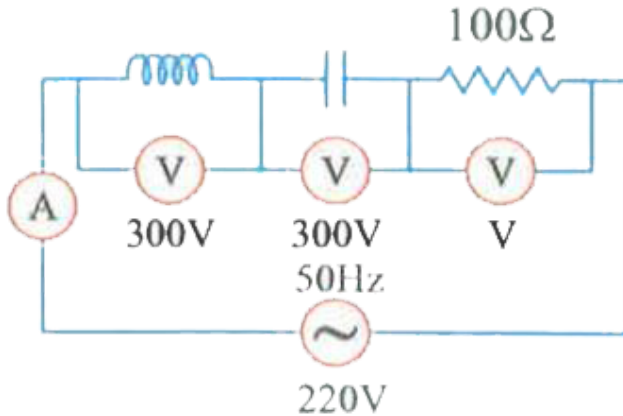8. In the circuit shown below what will be the reading of the voltmeters and ammeter?



[▶ Watch Video Solution](#)

9. In an AC circuit , an alternating voltage $e = 200\sin 100t$ V is connected to a capacitor of

capacity $1\mu F$. The rms value of the current in the circuit is




[Watch Video Solution](#)

10. An AC voltage is applied to a resistance R and an inductance L in series. If R and the inductive reactance are both equal to 3Ω , the phase difference between the applied voltage and the current in the circuit is



[Watch Video Solution](#)

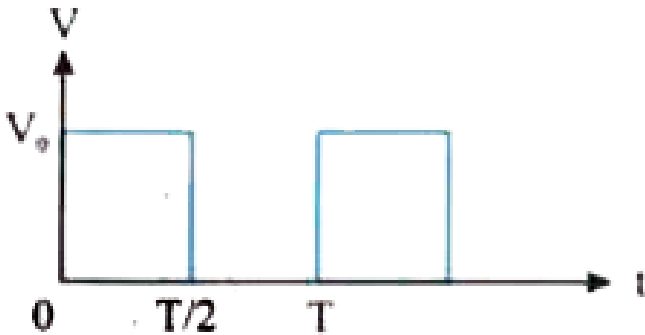11. The rms value of potential difference V shown in the Fig. is



[Watch Video Solution](#)

12. In an electrical circuit R, L, C and an AC voltage source are all connected in series. When L is removed from the circuit, the phase difference between the voltage and the current

in the circuit is $\pi/3$. If instead, C is removed from the circuit, difference the phase difference is again $\pi/3$. The power factor of the circuit is



[Watch Video Solution](#)

13. A coil of self-inductance L is connected in series with a bulb B and an AC source. Brightness of the bulb decreases when



[Watch Video Solution](#)

14. A series $R - C$ circuit is connected to an alternating voltage source. Consider two situations

(a) When capacitor is air filled.

(b) When capacitor is mica filled.

current through resistor is i and voltage across capacitor is V then



[Watch Video Solution](#)

15. A resistance R draws power P when connected to an AC source. If an inductance is

now placed in series with the resistance, such that the impedance of the circuit becomes Z , the power drawn will be



[Watch Video Solution](#)

16. An inductor 20 mH , a capacitor $50 \mu\text{F}$ and a resistor 40Ω are connected in series across a source of emf $V = 10 \sin 340 t$. The power loss in A.C. circuit is :



[Watch Video Solution](#)

17. A small signal voltage $V(t) = V_0 \sin \omega t$ is applied across an ideal capacitor C :



[Watch Video Solution](#)

18. The potential differences across the resistance, capacitance and inductance are $80V$, $40V$ and $100V$ respectively in an L-C-R circuit. The power factor of this circuit is



[Watch Video Solution](#)

19. A 100Ω resistance and a capacitor of 100Ω reactance are connected in series across a 220 V source. When the capacitor is 50 % charged, the peak value of the displacement current is



[Watch Video Solution](#)

20. What is the value of inductance L for which the current is a maximum in series LCR circuit with $C = 10\mu F$ and $\omega = 1000 \frac{rad}{s}$?



[Watch Video Solution](#)

21. In any AC circuit the emf (e) and the current (i) at any instant are given respectively by

$$e = E_0 \sin \omega t$$

$$i = I_0 \sin(\omega t - \phi)$$

The average power in the circuit over one cycle of AC is



Watch Video Solution

22. A wire of resistance R is connected in series with an inductor of reactance ωL . Then quality

factor of RL circuit is




[Watch Video Solution](#)

23. An LCR series circuit having 220 V ac source, inductance $L = 25mH$ and resistance $R = 100\Omega$. If voltage across inductor is just double of voltage across resistor then find out frequency of source.



[Watch Video Solution](#)

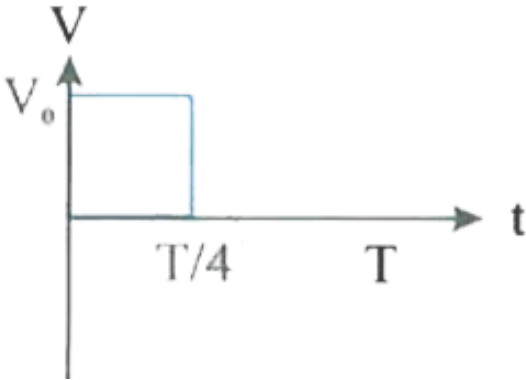24. A periodic voltage V varies with time t as shown in figure. T is the time period. Find the rms value of the voltage.



[Watch Video Solution](#)

25. An a.c. voltage is applied to a pure inductor L , drives a current in the inductor. The current

in the inductor would be

- A. ahead voltage by $\pi/2$
- B. lagging voltage by $\pi/2$
- C. ahead voltage by $3\pi/2$
- D. lagging voltage by $3\pi/2$

Answer: B




Watch Video Solution

26. Power dissipated in an $L - C - R$ series circuit connected to an AC source of emf ε is

 [Watch Video Solution](#)

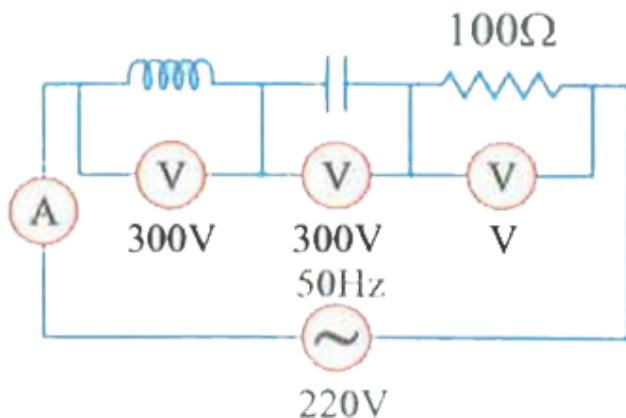27. In the circuit shown below what will be the reading of the voltmeters and ammeter?



 [Watch Video Solution](#)

28. In an AC circuit , an alternating voltage $e = 200\sin 100t$ V is connected to a capacitor of capacity $1\mu F$. The rms value of the current in the circuit is



Watch Video Solution


29. An AC voltage is applied to a resistance R and an inductance L in series. If R and the inductive reactance are both equal to 3Ω , the

phase difference between the applied voltage and the current in the circuit is



[Watch Video Solution](#)

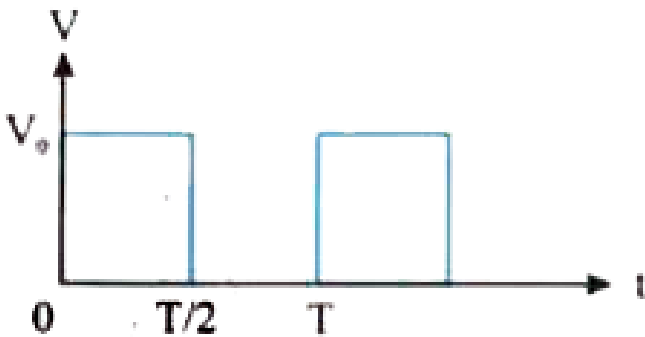30. The rms value of potential difference V shown in the Fig. is



[Watch Video Solution](#)

31. In an electrical circuit R, L, C and an AC voltage source are all connected in series. When L is removed from the circuit, the phase difference between the voltage and the current in the circuit is $\pi/3$. If instead, C is removed from the circuit, difference the phase difference is again $\pi/3$. The power factor of the circuit is



Watch Video Solution

32. A coil of self-inductance L is connected in series with a bulb B and an AC source.

Brightness of the bulb decreases when



[Watch Video Solution](#)

33. A series $R - C$ circuit is connected to an alternating voltage source. Consider two situations

(a) When capacitor is air filled.

(b) When capacitor is mica filled.

current through resistor is i and voltage across capacitor is V then



[Watch Video Solution](#)

34. A resistance R draws power P when connected to an AC source. If an inductance is now placed in series with the resistance, such that the impedance of the circuit becomes Z , the power drawn will be



Watch Video Solution

35. An inductor 20 mH , a capacitor $50 \mu\text{F}$ and a resistor 40Ω are connected in series across a

source of emf $V = 10 \sin 340 t$. The power loss in

A.C. circuit is :



[Watch Video Solution](#)

36. A small signal voltage $V(t) = V_0 \sin \omega t$ is applied across an ideal capacitor C :



[Watch Video Solution](#)

37. The potential differences across the resistance, capacitance and inductance are 80V,

40V and 100V respectively in an L-C-R circuit.

The power factor of this circuit is



[Watch Video Solution](#)

38. A 100Ω resistance and a capacitor of 100Ω reactance are connected in series across a 220 V source. When the capacitor is 50 % charged, the peak value of the displacement current is



[Watch Video Solution](#)

1. If the rms current in a 50 Hz ac circuit is 5 A, the value of the current $1/300$ second after its value becomes zero is



[Watch Video Solution](#)

2. An alternating current generator has an internal resistance R_g and an internal reactance X_g . It is used to supply power to a passive load consisting of a resistance R_g and a reactance X_L . For maximum power to be

delivered from the generator to the load, the value of X_L is equal to



[Watch Video Solution](#)

3. When a voltage measuring device is connected to a.c. mains the meter shows the steady input voltage of 220V. This means



[Watch Video Solution](#)

4. To reduce the resonant frequency in an LCR series circuit with a generator



[Watch Video Solution](#)

5. Which of the following combinations should be selected for better tuning of an LCR circuit used for communication ?



[Watch Video Solution](#)

6. A inductor of reactance 1Ω and a resistor of 2Ω are connected in series to the terminals of a 6 V (rms) a.c. source. The power dissipated in the circuit is



[Watch Video Solution](#)

7. The output of a step-down transformer is measured to be 24V when connected to a 12 watt light bulb. The value of the peak current is




[Watch Video Solution](#)

8. The potential difference across a $2H$ inductor as a function of time is shown in figure. At time

$t = 0$, current is zero


Current $t = 2$ second is

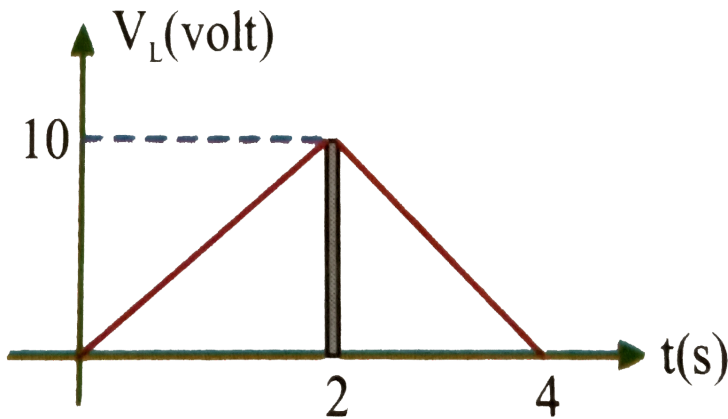

[Watch Video Solution](#)

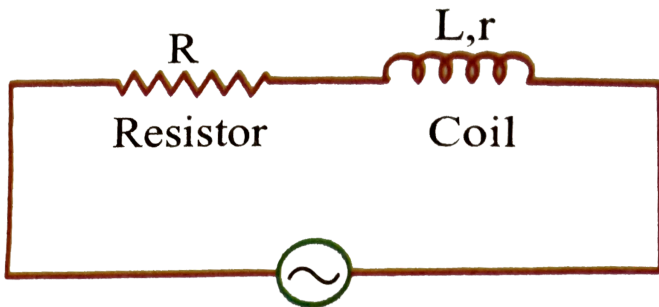9. For the circuit shown in the figure the rms value of voltage across R and coil are E_1 and E_2 respectively.

The power (thermal) developed across the coil is



$$e = E_0 \sin \omega t$$

$$e_{rms} = E$$



[Watch Video Solution](#)

10. A bulb is rated at $100V$, $100W$. It can be treated as a resistor. Find out the inductance of an inductor (called choke coil) that should be connected in series with the bulb at its rated power with the help of an ac source of $200V$ and $50Hz$.



Watch Video Solution

11. In LCR circuit current resonant frequency is $600Hz$ and half power points are at 650 and $550Hz$. The quality factor is



Watch Video Solution

12. A group of electric lamps having a total power rating of 1000 watt is supplied by an AC voltage $E = 200\sin(310t + 60^\circ)$. Then the r.m.s value of the circuit current is



Watch Video Solution

13. In a $L - R$ circuit, the value of L is $\left(\frac{0.4}{\pi}\right)$ henry and the value of R is 30 ohm. If in the

circuit, an alternating e.m.f of 200 vol at 50 cycles per sec is connected, the impedance of the circuit will be



[Watch Video Solution](#)

14. In a transformer the output current and voltage are respectively 4A and 20V. If the ratio of number of turns in the primary to secondary is 2:1 what is the input current and voltage?



[Watch Video Solution](#)

15. The self inductance of the motor of an electric fan is 10H . In order to impart maximum power at 50 Hz , it should be connected to a capacitance of



Watch Video Solution

16. A current of 5A is flowing at 220V in the primary coil of a transformer. If the voltage produced in the secondary coil is 2200V and 50% of power is lost, then the current in the secondary coil will be –




[Watch Video Solution](#)

17. The value of L, C and R for a circuit are 1H, 9F and 3Ω . What is the quality factor for the circuit at resonance ?




[Watch Video Solution](#)

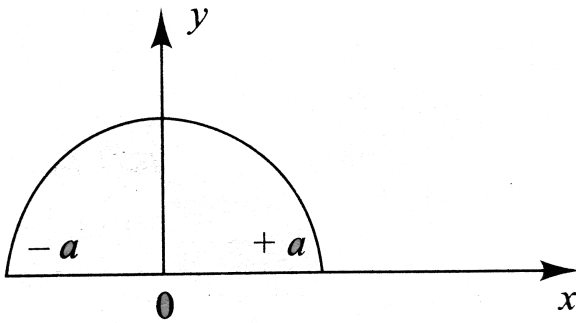18. Determine the rms value of a semi-circular current wave which has a maximum value of a.



[Watch Video Solution](#)

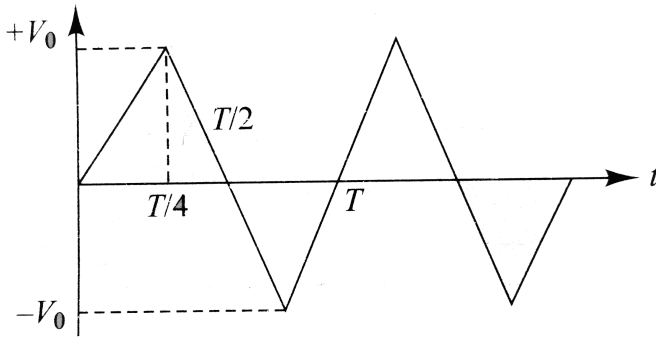19. The voltage time (V-t) graph for triangular wave having peak value (V_0) is as shown in fig.



[Watch Video Solution](#)

20. Two series resonant circuits with component values L_1C_1 and L_2C_2 , respectively have the same resonant frequency, They are then connected in series, so that the combination has the same resonant frequency



[Watch Video Solution](#)

21. A circuit containing resistance R_1 , Inductance L_1 and capacitance C_1 connected in series resonates at the same frequency n' as a second combination of R_2, L_2 and C_2 . If the two are connected in series. Then the circuit will resonate at



[Watch Video Solution](#)

22. An AC source of variable frequency is applied across a series $L - C - R$ circuit. At a frequency double the resonance frequency. The impedance is $\sqrt{10}$ times the minimum impedance. . The inductive reactance is



Watch Video Solution

23. An LCR circuit has $L = 10mL$, $R = 3\Omega$, and $C = 1\mu F$ connected in series to a source of $15\cos\omega t$ volt. The current amplitude at a

frequency that is 10% lower than the resonant frequency is



[Watch Video Solution](#)

24. A 100V a.c. source of frequency 500Hz is connected to a LCR circuit with $L = 8.1$ millihenry, $C = 12.5\mu F$ and $R = 10$ ohm, all connected in series. What is the potential difference across the resistance?



[Watch Video Solution](#)

25. If the rms current in a 50 Hz ac circuit is 5 A, the value of the current $1/300$ second after its value becomes zero is



Watch Video Solution

26. An alternating current generator has an internal resistance R_g and an internal reactance X_g . It is used to supply power to a passive load consisting of a resistance R_g and a reactance X_L . For maximum power to be

delivered from the generator to the load, the value of X_L is equal to



[Watch Video Solution](#)

27. When a voltage measuring device is connected to a.c. mains the meter shows the steady input voltage of 220V. This means



[Watch Video Solution](#)

28. To reduce the resonant frequency in an *LCR* series circuit with a generator



Watch Video Solution

29. Which of the following combinations should be selected for better tuning of an LCR circuit used for communication ?



Watch Video Solution

30. A inductor of reactance 1Ω and a resistor of 2Ω are connected in series to the terminals of a 6 V (rms) a.c. source. The power dissipated in the circuit is



Watch Video Solution


31. The output of a step-down transformer is measured to be 24V when connected to a 12 watt light bulb. The value of the peak current is



Watch Video Solution

32. The potential difference across a $2H$ inductor as a function of time is shown in figure. At time $t = 0$, current is zero


Current $t = 2$ second is

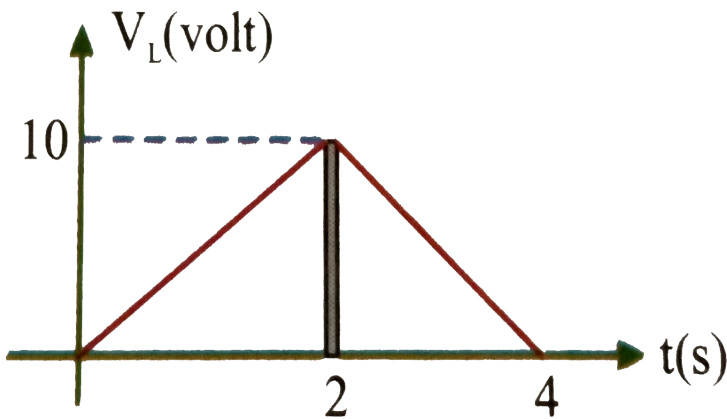

[Watch Video Solution](#)

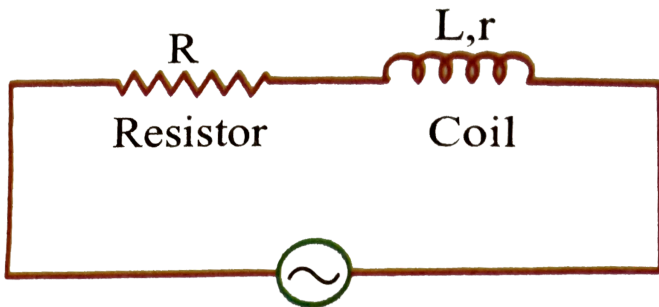33. For the circuit shown in the figure the rms value of voltage across R and coil are E_1 and E_2 respectively.

The power (thermal) developed across the coil is



$$e = E_0 \sin \omega t$$

$$e_{rms} = E$$



Watch Video Solution

34. A bulb is rated at 100V , 100W . It can be treated as a resistor. Find out the inductance of an inductor (called choke coil) that should be connected in series with the bulb at its rated power with the help of an ac source of 200V and 50Hz .



Watch Video Solution

35. In LCR circuit current resonant frequency is 600Hz and half power points are at 650 and 550Hz . The quality factor is



Watch Video Solution

36. A group of electric lamps having a total power rating of 1000 watt is supplied by an AC voltage $E = 200\sin(310t + 60^\circ)$. Then the r.m.s value of the circuit current is



Watch Video Solution

37. In a $L - R$ circuit, the value of L is $\left(\frac{0.4}{\pi}\right)$ henry and the value of R is 30 ohm. If in the

circuit, an alternating e.m.f of 200 vol at 50 cycles per sec is connected, the impedance of the circuit will be



[Watch Video Solution](#)

38. In a transformer the output current and voltage are respectively 4A and 20V. If the ratio of number of turns in the primary to secondary is 2:1 what is the input current and voltage?



[Watch Video Solution](#)

39. The self inductance of the motor of an electric fan is 10H , in order to impart maximum power at 10Hz , it should be connected to a capacitance of



Watch Video Solution

40. A current of 5A is flowing at 220V in the primary coil of a transformer. If the voltage produced in the secondary coil is 2200V and 50% of power is lost, then the current in the secondary coil will be –




[Watch Video Solution](#)

41. The value of L,C and R for a circuit are 1H, 9F and 3Ω . What is the quality factor for the circuit at resonance ?




[Watch Video Solution](#)

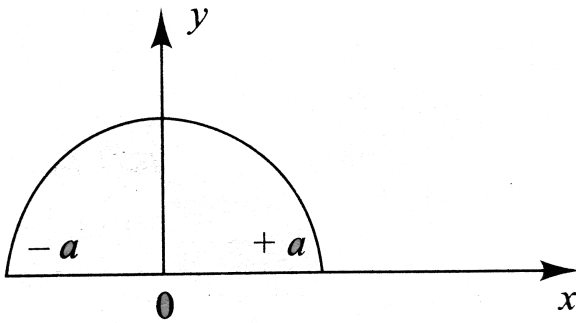42. Determine the rms value of a semi-circular current wave which has a maximum value of a.



[Watch Video Solution](#)

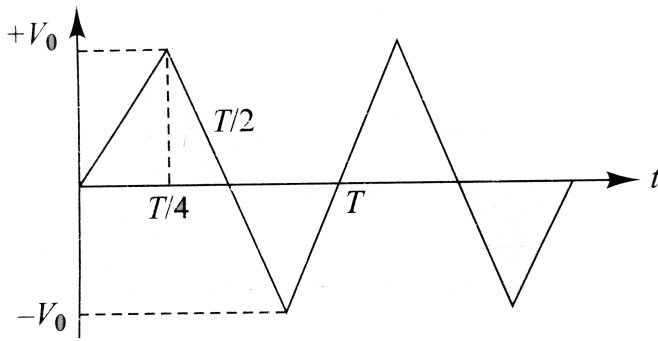43. The voltage time (V-t) graph for triangular wave having peak value (V_0) is as shown in fig.



[Watch Video Solution](#)

44. A circuit containing resistance R_1 inductance L_1 and capacitance C_1 connected in series gives resonance at the same frequency ν as a second similar combination of R_2, L_2 and C_2 . If the two circuits are connected in series,

shown that the whole circuit will resonate with the same frequency.



[Watch Video Solution](#)

45. A circuit containing resistance R_1 , Inductance L_1 and capacitance C_1 connected in series resonates at the same frequency n' as a second combination of R_2, L_2 and C_2 . If the two are connected in series. Then the circuit will resonate at



[Watch Video Solution](#)

46. An AC source of variable frequency is applied across a series $L - C - R$ circuit. At a frequency double the resonance frequency. The impedance is $\sqrt{10}$ times the minimum impedance. . The inductive reactance is



Watch Video Solution

47. An LCR circuit has $L = 10mL$, $R = 3\Omega$, and $C = 1\mu F$ connected in series to a source of $15\cos\omega t$ volt. The current amplitude at a

frequency that is 10% lower than the resonant frequency is



[Watch Video Solution](#)

48. A 100V a.c. source of frequency 500Hz is connected to a LCR circuit with $L = 8.1$ millihenry, $C = 12.5\mu F$ and $R = 10$ ohm, all connected in series. What is the potential difference across the resistance?



[Watch Video Solution](#)