

## PHYSICS

### FOR IIT JEE ASPIRANTS OF CLASS 12 FOR PHYSICS

#### SEMI CONDUCTOR DEVICES

##### Solved Example

1. The number of silicon atoms per  $m^3$  is  $5 \times 10^{28}$ . This is doped simultaneously with  $5 \times 10^{22}$  atoms per  $m^3$  of Arsenic and  $5 \times 10^{20}$  atoms per  $m^3$  of indium. Calculate the number of electrons and holes. Given that  $n_i = 1.5 \times 10^{16} m^{-3}$ . Is the material n-type or p-type?



Watch Video Solution

2. A semiconductor has an electron concentration of  $0.45 \times 10^{12} m^{-3}$  and a hole concentration of  $5.0 \times 10^{20} m^{-3}$ . Calculate its conductivity. Given electron mobility  $= 0.135 m^2 V^{-1} s^{-1}$ , hole mobility  $= 0.048 m^2 V^{-1} s^{-1}$ ,



[Watch Video Solution](#)

3. A *N*-type silicon sample of width  $4 \times 10^{-3} m$ , thickness and length  $6 \times 10^{-2} m$  carries a current of  $4.8 mA$ , when the voltage is applied across the length of the sample. The free electron density is  $10^{22} m^{-3}$



[Watch Video Solution](#)

4. The energy gap of pure *Si* is  $1.1\text{eV}$ . The mobilities of electrons and holes are respectively  $0.135\text{m}^2\text{V}^{-1}\text{s}^{-1}$  and  $0.048\text{m}^2\text{V}^{-1}\text{s}^{-1}$  and can be taken as independent of temperature. The intrinsic carrier concentration is given by  $n_i = n_0 e^{-E_g/2kT}$ .

Where  $n_0$  is a constant,  $E_g$  The gap width and  $k$  The Boltmann's constant whose value is  $1.38 \times 10^{-23}\text{JK}^{-1}$ . The ratio of the electrical conductivities of *Si* at  $600\text{K}$  and  $300\text{K}$  is.



[Watch Video Solution](#)

5. In a  $p - n$  junction diode, the current  $I$  can be expressed as  $I = I_0 \exp\left(\frac{eV}{2k_B T} - 1\right)$  where  $I_0$  is called the reverse saturation current,  $V$  is the voltage across the diode and is positive for forward bias and negative for reverse bias, and  $I$  is

the current through the diode,  $K_B$  is the Boltzmann constant ( $8.6 \times 10^{-5} eV/K$ ) and  $T$  is the absolute temperature. If for a given diode  $I_o = 5 \times 10^{-12} A$  and  $T = 300K$ , then

- (a) What will be the forward current at a forward voltage of  $0.6V$  ?
- (b) What will be the increase in the current if the voltage across the diode is increased to  $0.7V$  ?
- (c) What is the dynamic resistance ?
- (d) What will be current if reverse bias voltage changes from  $1V$  to  $2V$  ?



[Watch Video Solution](#)

6. The energy of a photon of sodium light ( $\lambda = 589nm$ ) equal the band gap of a semiconducting material.(a)Find the



minimum energy  $E$  required to create a hole-electron pair.


(b) Find the value of  $E/kT$  at a temperature of 300K.

 **Watch Video Solution**


7. The  $V - I$  characteristic of a silicon diode is shown in the Fig. Calculate the resistance of the diode at

(a)  $I_D = 15mA$  and

(b)  $V_D = -10V$ .

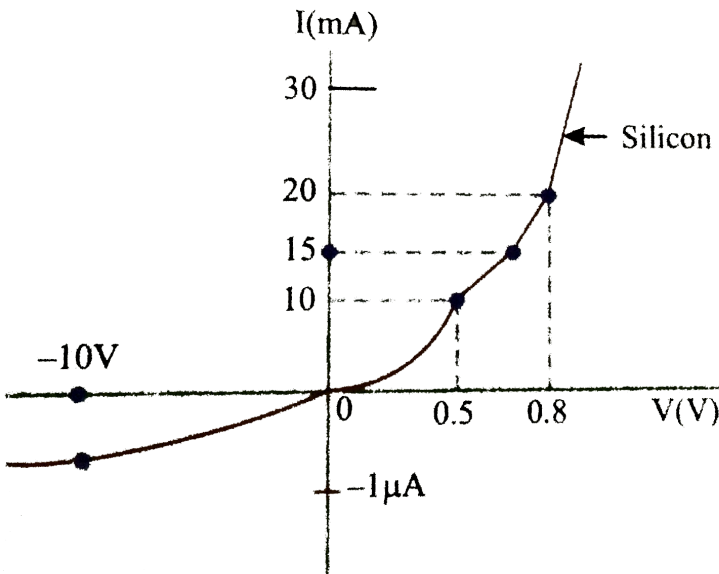


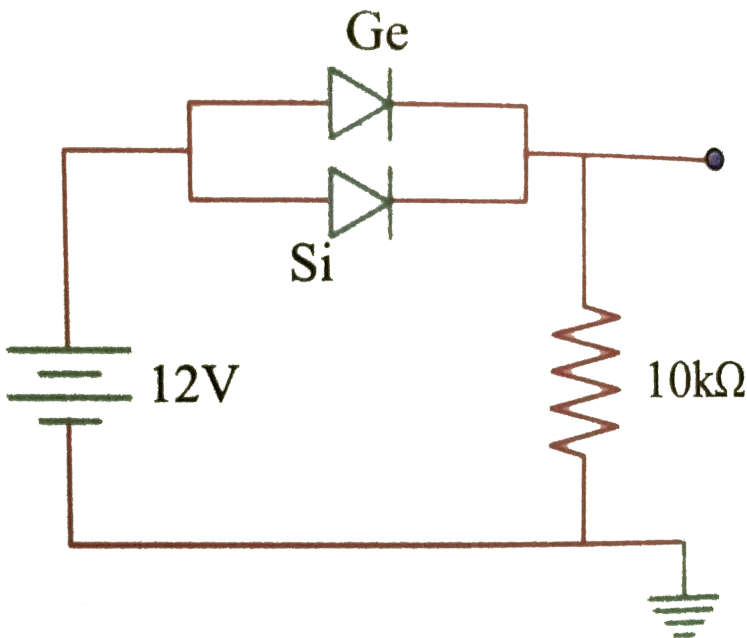8. Two junction diodes, one of germanium ( $Ge$ ) and other of silicon ( $Si$ ) are connected as shown in fig to a battery of  $12V$  and a load resistance  $10k\Omega$ . The germanium diode conducts at  $0.3V$  and silicon diode at  $0.7V$ . When current flows in the circuit, the potential of terminal  $Y$  will be



9. Find the maximum voltage across  $AB$  in the circuit shown in


Fig. Assume that diode is ideal.

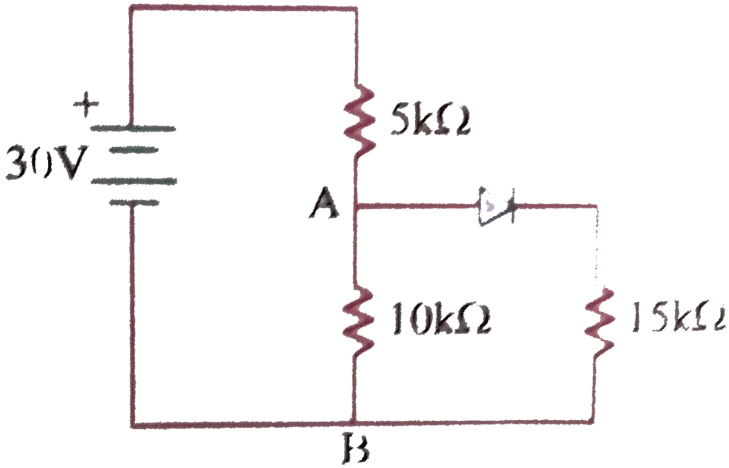

Watch Video Solution

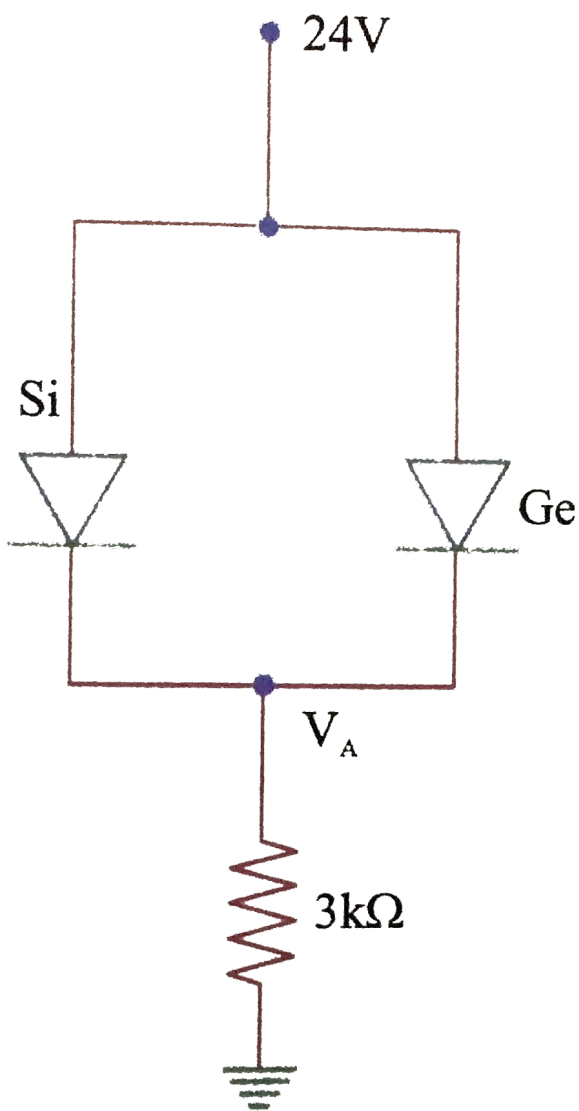
10. Find the voltage  $V_A$  in the circuit shown in figure. The

potential barrier for  $Ge$  is  $0.3V$  and for  $Si$  is  $0.7V$




Watch Video Solution

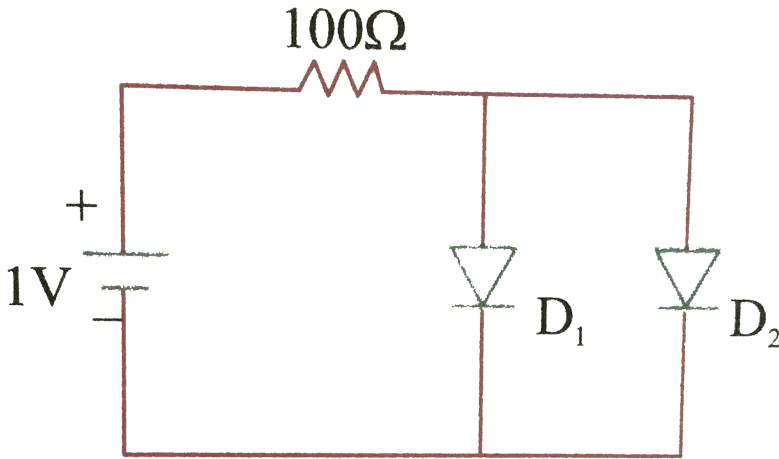11. Considering the circuit and data given in the diagram, calculate the currents flowing in the diodes  $D_1$  and  $D_2$ . Forward resistance of  $D_1$  and  $D_2$  is  $20\Omega$ .



[▶ Watch Video Solution](#)

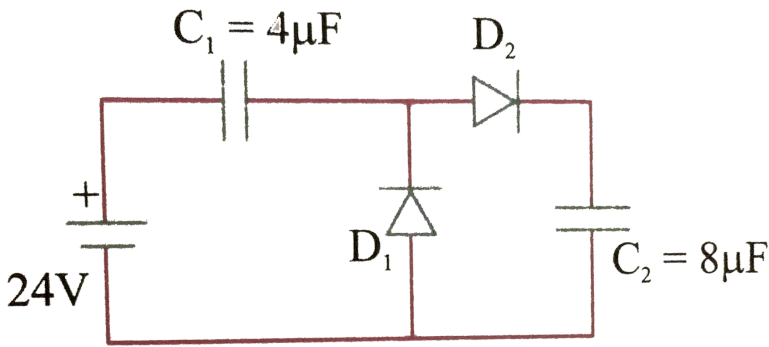12. In the circuit shown. The potential drop across each capacitor is (assuming the two diodes are ideal).



[▶ Watch Video Solution](#)

13. A potential barrier of 0.50V exists across a p-n junction.(a) If the depletion region is  $5.0 \times 10^{-7}\text{m}$  wide, what is the intensity of the electric field in this region?(b) An electron with speed  $5.0 \times 10^5\text{ms}^{-1}$  approaches the p-n junction from the n-side. With what speed will it enter the p-side?

[▶ Watch Video Solution](#)

**14.** A  $p - n$  diode is used in a half wave rectifier with a load resistance of  $1000\Omega$ . If the forward resistance ( $r_f$ ) of diode is  $10\Omega$ , calculate the efficiency of this half wave rectifier.




**Watch Video Solution**

**15.** A full wave rectifier uses two diodes with a load resistance of  $100\Omega$ . Each diode is having negligible forward resistance. Find the efficiency of this wave rectifier.




**Watch Video Solution**

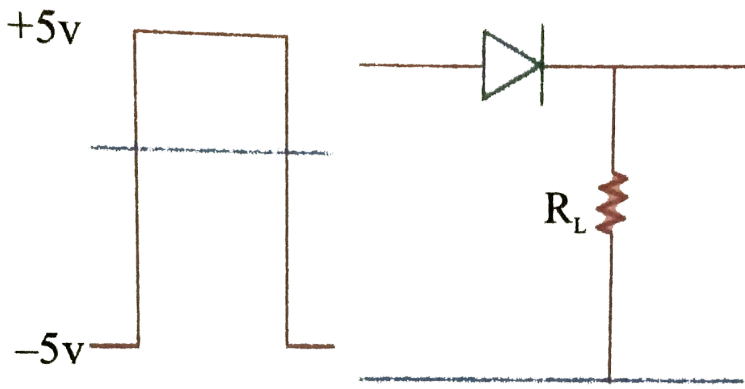**16.** If a  $p - n$  junction diode, a square input signal of  $10V$  is applied as shown.



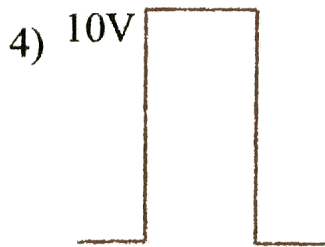Then the out put signal across  $R_L$  will be



Watch Video Solution




17. For the circuit shown in figure, Find

(1) the output voltage ,

(2) the voltage drop across series resistance ,

(3) the current through Zener diode.

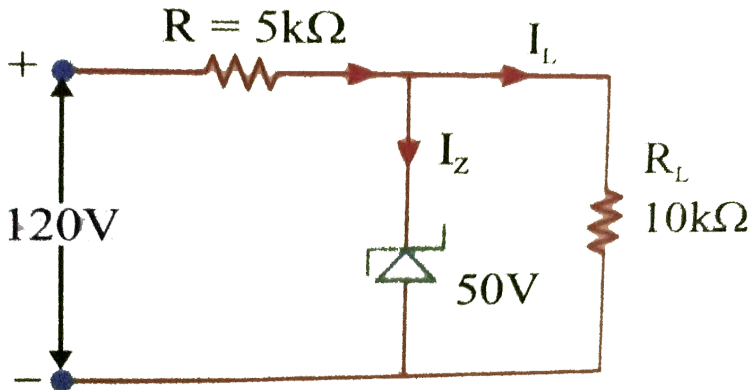

[Watch Video Solution](#)

18. Current amplification factor of a common base configuration is 0.88. Find the value of base current when the emitter current is  $1\text{mA}$ .



Watch Video Solution


19. In a transistor, the emitter circuit resistance is  $100\Omega$  and the collector resistance is  $100\Omega$ . The power gain. If the emitter and collector currents are assumed to be equal, will be.



Watch Video Solution

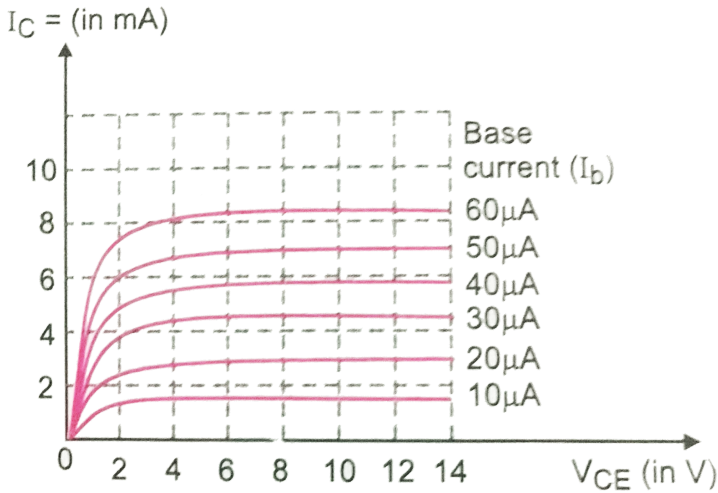20. From the output characteristics of common emitter circuit shown in Fig., calculate the value of  $\beta_{ac}$  and  $\beta_{dc}$  of the


transistor when  $V_{CE}$  is  $10V$  and  $I_c = 4.0mA$ .



Watch Video Solution

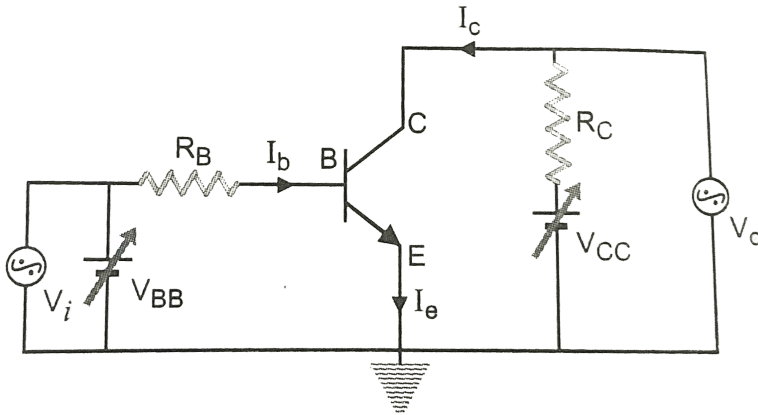21. In common emitter transistor as shown in Fig., the  $V_{BB}$  supply can be varied from 0 V to 5.0V. The Si. Transistor has  $\beta_{ac} = 250$  and  $R_B = 100k\Omega$ ,  $R_c = 1k\Omega$ ,  $V_{CC} = 5.0V$ . Assume that when the transistor is saturated,  $V_{CE} = 0V$  and  $V_{BE} = 0.8V$ . Calculate the minimum base current, for which the transistor will reach saturation. Hence, determine  $V_i$  when

the transistor is 'switched on' find ranges of  $V_i$  for which the transistor is switched off and switched on.



[Watch Video Solution](#)

22. Two amplifiers are connected one after the other in series (cascaded). The first amplifier has a voltage gain of 10 and the second has a voltage gain of 20 . If the input signal is 0.01 V , calculate the output AC signal .

[Watch Video Solution](#)

**23.** In a single stage transistor amplifier, when the signal changes by  $0.02V$  the base current by  $10\mu A$  and collector current by  $1mA$ . If collector load  $R_C = 2k\Omega$  and  $R_L = 10k\Omega$ ,

Calculate :

- (i) Current Gain
- (ii) Input Impedance,
- (iii) Effective  $AC$  load,
- (iv) Voltage gain and
- (v) Power gain.



[Watch Video Solution](#)

**24.** An n-p-n transistor in a common - emitter mode is used as a simple voltage amplifier with a collector current of  $4\text{ mA}$ . The positive terminal of a  $8\text{ V}$  battery is connected to the collector through a load resistance  $R_L$  and to the base through a

resistance  $R_B$ . The collector - emitter voltage  $V_{CE} = 4V$ , the base - emitter voltage  $V_{BE} = 0.6V$  and the current amplification factor  $\beta = 100$ . Calculate the values of  $R_L$  and  $R_B$ .



[Watch Video Solution](#)

**25.** In a negative feedback amplifier, the gain without feedback is 100, feedback ratio is  $1/25$  and input voltage is  $50mV$ .

Calculate


- (i) gain with feedback
- (ii) feedback factor
- (iii) output voltage
- (iv) feedback voltage
- (v) new input voltage so that output voltage with feedback equals the output voltage without feedback.

[▶ Watch Video Solution](#)

26. Convert binary number 10111 into decimal number.


[▶ Watch Video Solution](#)

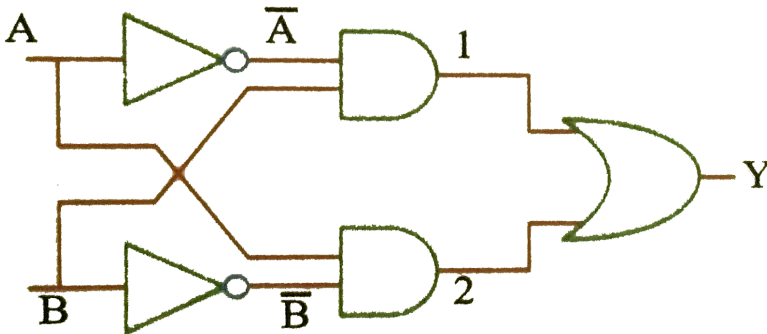27. The Boolean expression of the output  $Y$  of the inputs  $A$  and  $B$  for the circuit shown in the fig.



[▶ Watch Video Solution](#)

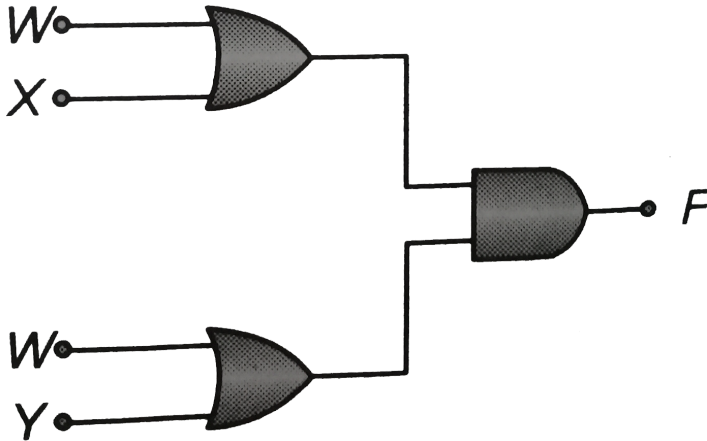28. The diagram of a logic circuit is given below. The output  $F$  of the circuit is represented by




[Watch Video Solution](#)

29. The logic circuit and its truth table are given, what is the gate  $X$  in the diagram




A	B	Y
1	1	1
1	0	1
0	1	1
0	0	0

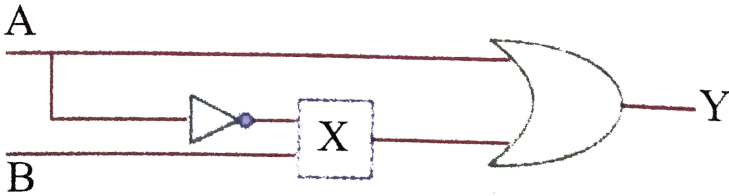


Watch Video Solution

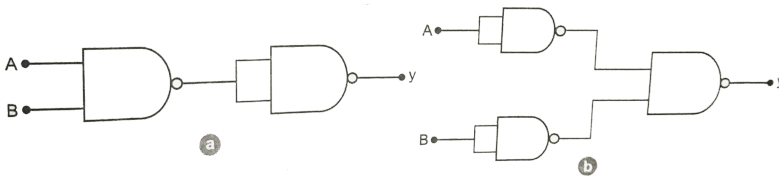30. You are given two circuit as shown in Fig. and . Which consists of NAND gates. Identify the logic operation carried out by the two circuits.



Watch Video Solution

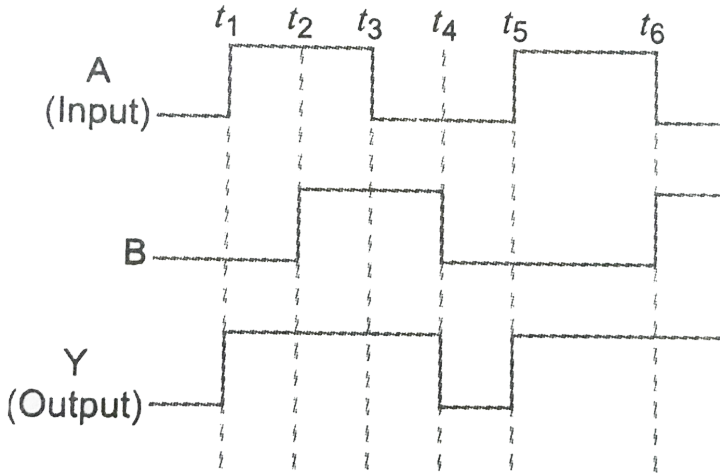31. Justify the output waveform (y) of the OR gate for input and as gives in Fig.



[Watch Video Solution](#)

32. Draw logic diagrams for the Boolean expressions given below :

$$(i) A \cdot \bar{B} + \bar{A} \cdot B = Y$$

$$(ii) (A + \bar{B}) \cdot (\bar{A} + B) = Y.$$



Watch Video Solution

CUQ

1. Which property makes the crystalline solids to have sharp melting point ?

- A. Equal strength of all the interatomic bonds
- B. anisotropic
- C. long range order
- D. short range order

**Answer: A**



[Watch Video Solution](#)

2. Which of the following is not a property of crystalline substance

- A. sharp melting point
- B. bounded by flat surface
- C. isotropic
- D. long range order

**Answer: C**



[Watch Video Solution](#)

3. A piece of copper and another of germanium are cooled from room temperature to  $80K$ . The resistance of

- A. each of these decreases
- B. copper strip decreases and that of germanium decreases
- C. copper strip decreases and that of germanium increases
- D. each of these increases

**Answer: C**



[Watch Video Solution](#)

4. The difference in the variation of resistance with temperature in a metal and a semiconductor arises essentially due to the difference in the

A. crystal structure

B. variation of the number of charge carries with temperature

C. type of bonding

D. variation of scattering mechanism with temperature

**Answer: B**



[Watch Video Solution](#)

5. The manifestation of band structure in solids is due to

A. Heisenberg's uncertainty principle

B. Pauli's exclusive principle

C. Bohe's correspondence principle

D. Boltzman's law

**Answer: B**

 [Watch Video Solution](#)

6. A solid which is not transparent to visible light and whose conductivity increase with temperature is formed by

- A. ionic bonding
- B. covalent bonding
- C. vander Wall's bonding
- D. metallic bonding

**Answer: B**

 [Watch Video Solution](#)

7. To a germanium sample, traces of gallium are added as an impurity. The resultant sample would behave like

- A. A conductor
- B. An p-type semiconductor
- C. A n-type semiconductor
- D. An insulator

**Answer: B**



[Watch Video Solution](#)

8. In semiconductors at a room temperature



- A. The valence band is partially empty and the conduction band is partially filled.
- B. The valence band is completely filled and the conduction band is partially filled
- C. The valence band is completely filled
- D. The conduction band is completely filled

**Answer: A**



[Watch Video Solution](#)

9. Identify the property which is not characteristic for a semiconductor ?

- A. at a very low temperatures, it behaves like an insulator

- B. at higher temperatures two types of charge carriers will cause conductivity
- C. the charge carriers are electrons and holes in the valence band at higher temperatures.
- D. the semiconductor is electrically neutral.

**Answer: C**



[Watch Video Solution](#)

**10.** Carbon , silicon and germanium have four valence electrons each . At room temperature which one of the following statements is most appropriate ?

- A. The number of free conduction electrons is negligibly small in all the three
- B. The number of free electrons for conduction is significant in all the three.
- C. The number of free electrons for conduction is significant only in *Si* and *Ge* but small in *C*.
- D. The number of free conductor electrons is significant in *C* but small in *Si* and *Ge*.

**Answer: C**



**Watch Video Solution**

**11.** The relation between number of free electrons ( $n$ ) in a semiconductor and temperature ( $T$ ) is given by

A.  $n \propto T$

B.  $n \propto T^2$

C.  $n \propto \sqrt{T}$

D.  $n \propto T^{3/2}$

**Answer: D**



**Watch Video Solution**

12. An electrically neutral semiconductor has

A. equal amounts of negative and positive charge

B. no minority charge carries

C. no majority charge carriers

D. no free charges

**Answer: A**



**Watch Video Solution**

**13.** There is no hole current in conductors because they have

A. high conductivity

B. high electron density

C. no valence band

D. overlapping of valence and conduction bands.

**Answer: D**



**Watch Video Solution**

14. In the insulators

- A. the valence band is partially filled with electrons
- B. the conduction band is partially filled with electrons
- C. the conduction band is partially filled with electrons and valence band is empty
- D. the conduction band is empty and the valence band is filled with electrons.

**Answer: D**



[Watch Video Solution](#)

15. In semiconductors the forbidden energy gap between  $V$ .  $B$  and  $C$ .  $B$  is of the order of

A. 1 eV

B. 5 eV

C. 1 KeV

D. 1 MeV

**Answer: A**



**Watch Video Solution**

**16.** The level formed due to impurity atom, in the for hidden energy gap, very near to the valence band in a p-type semiconductor is called

A. acceptor level

B. donar level

C. conduction level

D. forbidden level

**Answer: A**



**Watch Video Solution**

17. The bond in semiconductors is

A. covalent

B. ionic

C. metallic

D. hydrogen

**Answer: A**



**Watch Video Solution**



18. On increasing temperature, the conductivity of pure semiconductors

A. decreases

B. increases

C. remains unchanged

D. becomes zero

**Answer: B**



[Watch Video Solution](#)

19. The mobility of free electrons is greater than that of free holes because

- A. they carry negative charge
- B. they are light
- C. their mutual collisions are less
- D. they require low energy to continue their motion

**Answer: D**



**Watch Video Solution**

**20.** A semiconductor at  $0K$  behaves as

- A. conductor
- B. insulator
- C. super conductor
- D. extrinsic semiconductor

**Answer: B**



**Watch Video Solution**

**21.** Carbon , silicon and germanium have four valence electrons each . These are characterised by valence and conduction bands separated by energy band - gap respectively equal to  $(E_g)_C$ ,  $(E_g)_{Si}$  and  $(E_g)_{Ge}$ . Which of the following statements are true ?

A.  $(E_g)_{Si} < (E_g)_{Ge} < (E_g)_C$

B.  $(E_g)_C < (E_g)_{Ge} > (E_g)_{Si}$

C.  $(E_g)_C > (E_g)_{Si} > (E_g)_{Ge}$

D.  $(E_g)_C = (E_g)_{Si} = (E_g)_{Ge}$

**Answer: C**



[Watch Video Solution](#)

22. The valency of impurity element for making p-type semiconductors is

A. 5

B. 4

C. 3

D. 7

**Answer: C**



[Watch Video Solution](#)

23. In n-type semiconductors the electron concentration is equal to

- A. density of donor atoms
- B. density of acceptor atoms
- C. density of both type of atoms
- D. neither density of acceptor atoms nor density of donor atoms

**Answer: A**



**Watch Video Solution**

24. Which of the following statements is not true ?

- A. the resistance of intrinsic semiconductors decreases with increase of temperature
- B. doping pure  $Si$  with trivalent impurities gives p-type semiconductors
- C. the majority charge carries in n-type semiconductors are holes
- D. a  $p - n$  junction can act as a semiconductor diode

**Answer: C**



**Watch Video Solution**

**25. p-type semiconductor is**

- A. negativity charged

B. positively charged

C. neutral

D. may be positive or negative

**Answer: C**



**Watch Video Solution**

**26. n-type semiconductor is**

A. negativity charged

B. positively charged

C. neutral

D. may be positive or negative

**Answer: C**



Watch Video Solution

27. An electric field is applied across a semiconductor. Let  $n$  be the number of charge carriers. As temperature increases,  $n$  will

- A. increase
- B. decrease
- C. does not change
- D. may increase or decrease

**Answer: A**



Watch Video Solution

28. In a n-type semiconductor, the fermi energy level lies



- A. in the forbidden energy gap nearer to the conduction band.
- B. in the forbidden energy gap nearer to the valence band.
- C. in the middle of forbidden energy gap
- D. outside the forbidden energy gap

**Answer: A**



**Watch Video Solution**

**29.** An n-type and p-type silicon can be obtained by doping pure silicon with.

- A. Arsenic and phosphorous
- B. Indium and aluminium

C. Phosphorous and indium

D. aluminium and boron

**Answer: C**



**Watch Video Solution**

**30.** The width of forbidden gap in silicon crystal is  $1.2\text{eV}$ . When the crystal is converted into a n-type semiconductor the distance of fermi level from conduction band is Greater than  $0.55\text{eV}$

A. Greater than  $0.55\text{eV}$

B. Equal to  $0.55\text{eV}$

C. lesser than  $0.55\text{eV}$

D. Equal to  $1.1\text{eV}$

**Answer: C**



**Watch Video Solution**

**31. In extrinsic semiconductors**

- A. the conduction band and valence band overlap
- B. the gap between conduction band and valence band is near about  $16eV$
- C. the gap between conduction band and valence band is near about  $1eV$
- D. The gap between conduction band and valence band will be  $100eV$  and more

**Answer: C**



[Watch Video Solution](#)

**32.** The element that can be used as acceptor impurity to dope silicon is

- A. Antimony
- B. Arsenic
- C. Boron
- D. phosphorous

**Answer: C**



[Watch Video Solution](#)

**33.** Among the following, the wrong statement on the case of semiconductor is

- A. Resistivity is in between that of a conductor and insulator
- B. Temperature coefficient of resistance is negative
- C. Doping increases conductivity
- D. At absolute zero temperature it behaves like a conductor.

**Answer: D**



**Watch Video Solution**

**34.** The value indicated by fermi energy level in an intrinsic semiconductor is

- A. the average energy of electrons and holes
- B. the energy of electrons in conduction band
- C. the energy of holes in valence band
- D. the energy of forbidden region

**Answer: A**



**Watch Video Solution**

**35.** The conduction band and valency band of a good conductors are

- A. well separated
- B. just touch
- C. very close

D. overlap

**Answer: D**



[Watch Video Solution](#)

**36.** Two pieces one of germinium and the other of aluminium are cooled from  $T_1K$  to  $T_2K$ . The resistance of

- A. aluminium increases and that of gertmanium decreases
- B. each of them decreases
- C. aluminium decreases and that of germanium increases
- D. each of them increases

**Answer: C**



[Watch Video Solution](#)

37. In intrinsic semiconductor at room temperature the no. of electrons and holes are

- A. equal
- B. zero
- C. unequal
- D. infinite

**Answer: A**



**Watch Video Solution**

38. Band gap in insulator is of the order

- A.  $6eV$



B.  $0.60eV$

C.  $-6eV$

D.  $0eV$

**Answer: A**



**Watch Video Solution**

**39.** In p-type semiconductor conduction is due to

A. greater number of holes and less number of electrons

B. only electrons

C. only holes

D. greater number of electrons and less number of holes

**Answer: A**



[Watch Video Solution](#)

**40.** In an intrinsic semiconductor, the fermi energy level is

- A. nearer to valence band than conduction band
- B. equidistant from conduction band and valence band
- C. nearer to conduction band than valence band
- D. bisecting the conduction band

**Answer: B**



[Watch Video Solution](#)

**41.** With increase in temperature in an intrinsic semiconductor the ration of conduction electrons and holes is

A. 1:1

B. 1:2

C. 2:1

D. 1:3

**Answer: A**



**Watch Video Solution**

**42.** To obtain n-type extrinsic semiconductor, the impurity element to be added to germanium should be of valency

A. 2

B. 5

C. 4

D. 3

**Answer: B**



**Watch Video Solution**

**43.** The majority carries in a p-type semiconductor are....

A. Electrons

B. Holes

C. Both

D. Impurities

**Answer: B**



**Watch Video Solution**

**44.** The objective of adding impurities in the extrinsic semiconductor is

A. to increase the conductivity of the semiconductor

B. to increase the density of total current carries

C. to increase the density of either holes or electrons but not both

D. to eliminate the electron-hole pairs produced in intrinsic semiconductor.

**Answer: C**



**Watch Video Solution**

**45.** In intrinsic semiconductor conductivity is

A. low

B. average

C. high

D. very low

**Answer: A**



**Watch Video Solution**

**46.** In intrinsic semiconductor conductivity is due to.

A. doping

B. breaking of covalent bonds

C. free electrons

D. holes

**Answer: B**



**Watch Video Solution**

**47.** When the conductivity of a semiconductor is only due to breaking of covalent bonds, the semi conductor is called.

A. n-type

B. p-type

C. intrinsic

D. extrinsic

**Answer: C**



**Watch Video Solution**

**48.** Assertion ( $A$ ) :  $C$ ,  $Si$  and  $Ge$  have 4 Valency each both but  $C$  is an insulator where as  $Si$  and  $Ge$  are semi conductors  
Reason ( $R$ ) : Energy gap is least for  $Ge$ , less for  $Si$  compared to  $C$ , So that free electrons for conduction in  $Ge$  and  $Si$  are significant but negligible small for  $C$ .

- A.  $A$ ,  $R$  are true and  $R$  explains  $A$  correctly
- B.  $A$ ,  $R$  are true and  $R$  do not explain  $A$  correctly
- C.  $A$  is true, but  $R$  is false
- D.  $R$  is true, but  $A$  is false

**Answer: A**



**Watch Video Solution**

**49.** The potential barrier at  $PN$  junction is due to



- A. fixed acceptor and donor ions on either side of the junction
- B. minority carriers on either side of the junction
- C. majority carriers on either side of the junction
- D. both majority and minority carriers on either side of junction

**Answer: A**



**Watch Video Solution**

**50.** A  $PN$  junction diode cannot be used

- A. as rectifier
- B. for converting light energy to electric energy

C. for getting light radiation


D. both majority and minority carriers on either side of junction



**Answer: D**



**Watch Video Solution**

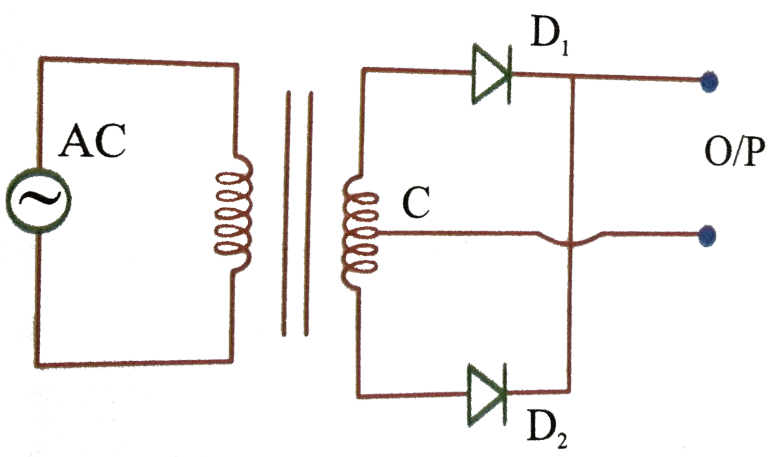51. A full wave rectifier with the output is shown in fig. the contributions from the diode (2) are.



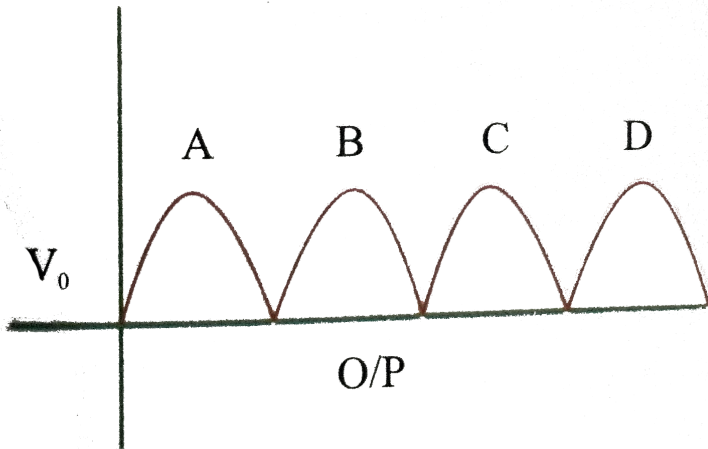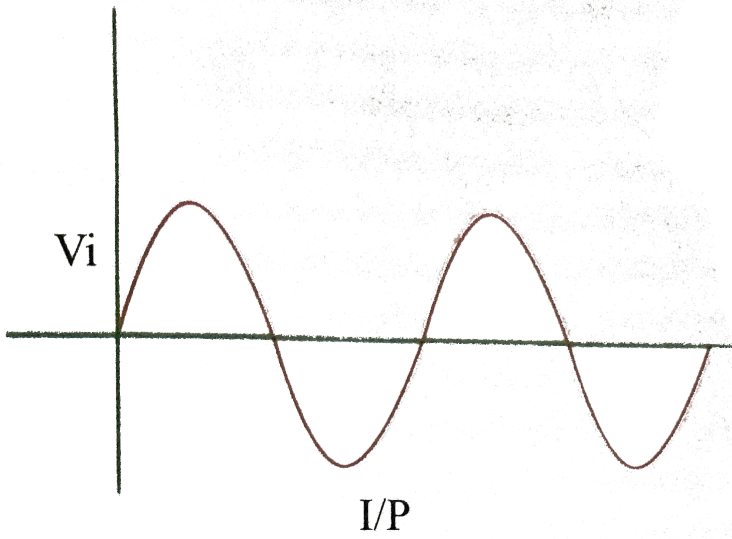

A. C

B. A,C

C. B,D

D. A,B,C,D

**Answer: C**



**Watch Video Solution**

**52.** A full-wave rectifier is used to convert ' $n$ '  $Hz$  a. c into  $d. c$ , then the number of pulses per second present in the rectified voltage is.

A.  $n$

B.  $n/2$

C.  $2n$

D.  $4n$

**Answer: C**

 [Watch Video Solution](#)

53. If the input frequency of half-wave rectifier is  $nHz$ , then its output is

- A. a constant  $dc$
- B.  $n/2Hz$  pulsating  $dc$
- C.  $nHz$  pulsating  $dc$
- D.  $2nHz$  pulsating  $dc$

**Answer: C**

 [Watch Video Solution](#)

54.  $p - n$  junction diode acts as

- A. ohmic resistance
- B. non-ohmic resistance
- C. both 1 and 2
- D. amplifier

**Answer: B**



**Watch Video Solution**

**55.** The process of converting alternating current into direct current is known as

- A. modulation
- B. amplification
- C. detection

D. rectification

**Answer: D**



**Watch Video Solution**

**56.** On increasing reverse voltage in a  $p - n$  junction diode the value of reverse current will

- A. gradually increases
- B. first remains constant and then suddenly increase
- C. remains constant
- D. gradually decrease

**Answer: B**



**Watch Video Solution**



57. In forward bias the depletion layer behaves like

- A. an insulator
- B. a conductor
- C. a semiconductor
- D. capacitor

**Answer: B**



**Watch Video Solution**

58.  $p - n$  junction in reverse bias behaves like

- A. an inductor
- B. a condenser

C. amplifier

D. an off switch

**Answer: D**



**Watch Video Solution**

**59.** The main cause of avalanche breakdown is

A. collision by ionisation

B. high doping

C. recombination of electrons and holes

D. low doping

**Answer: A**



**Watch Video Solution**

60. The main cause of Zener breakdown is.

- A. the base semiconductor being germanium
- B. production of electron - hole pairs due to thermal excitation
- C. low doping
- D. high doping

**Answer: D**



[Watch Video Solution](#)

61. When  $p - n$  junction is forward biased, the current across the junction is mainly due to

- A. diffusion of charges
- B. drifting of charges
- C. both diffusion and drifting of charges
- D. holes only

**Answer: A**



**Watch Video Solution**

**62.** The current through any  $p - n$  junction is due to

- (a) drift of charge carriers
- (b) diffusion of charge carriers
- (c) different concentrations of same type of charge carriers in different regions.
- (d) Same concentrations of same type of charge carriers in different regions

A.  $a$ ,  $b$  and  $c$

B.  $a$  and  $b$  only

C. only  $d$

D.  $a$ ,  $b$ ,  $c$ ,  $d$

**Answer: A**



**Watch Video Solution**

**63.** The thickness of depletion layer is approximately

A.  $1\mu m$

B.  $1mm$

C.  $1cm$

D.  $1m$

**Answer: A**



**Watch Video Solution**

**64.** The depletion region is

- A. region of opposite charges
- B. neutral region
- C. region of infinite energy
- D. region of free current carriers

**Answer: D**



**Watch Video Solution**

65. Diffusion current in a p-n junction is greater than the drift current in magnitude

A. forward biased

B. reverse biased

C. un biased

D. both forward and reverse biased

**Answer: A**



[Watch Video Solution](#)

66. Germanium diode.

A. may be used as rectifier because it offers a relatively low resistance for forward bias and very high resistance for reverse bias.

B. may be used as a rectifier because it offers a relatively high resistance for forward bias and very low resistance for reverse bias.

C. cannot be used as a rectifier

D. may be used as an amplifier


**Answer: A**



**Watch Video Solution**



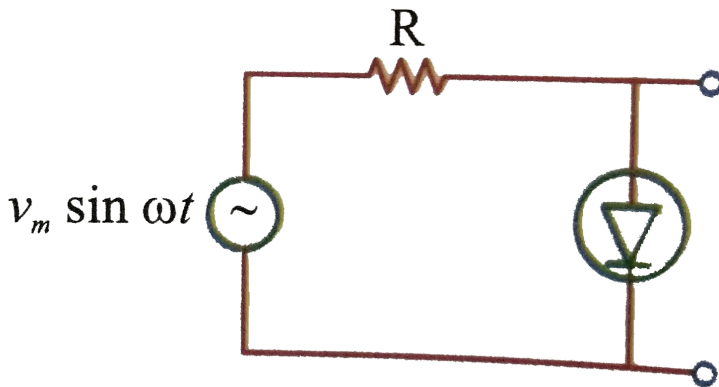67. The output of the given circuit in Fig.



A. would be zero at all times

B. would be like a half-wave rectifier with positive cycles in output

C. would be like a half-wave rectifier with negative cycles in output

D. would be like that of a full-wave rectifier.

**Answer: C**



Watch Video Solution

**68.** Diode is forward biased and the applied voltage is greater than the potential barrier then

(I) resistance of the junction in the forward bias decreases

(II) potential barrier remains same

(III) width barrier remains decreases

(IV) p-type is at higher potential than the n-type.

A. all are true

B. all are false

C. *I, III, IV* are true

D. *I, II, III* are true

**Answer: C**



Watch Video Solution

69. When a junction diode is reverse biased, then current called drift current is due to

- A. majority charge carriers of both  $n$  &  $p$  sides
- B. minority charge carriers of both  $n$  &  $p$  sides
- C. holes of both  $n$  &  $p$  sides
- D. conduction band electrons of  $n$ -side only

**Answer: B**



[Watch Video Solution](#)

70. Among the following one statement is not correct when a junction diode is forward bias

- A. the width of depletion region decreases
- B. free electron on n-side will move towards the junction
- C. holes on p-side move towards the junction
- D. electron on n-side and holes on p-side will move away from junction

**Answer: D**



**Watch Video Solution**

**71.** Considering a  $p - n$  junction as a capacitor, forward with  $p$  and  $n$  material acting as thin metal electrodes and depletion layer width acting as separation between them. Basing on this assume that a  $n - p - n$  transistor is working as an amplifier

in  $CE$  configuration. If  $C_1$  and  $C_2$  are base-emitter and collector emitter junction capacitances, then :

A.  $C_1 > C_2$

B.  $C_1 < C_2$

C.  $C_1 = C_2$

D.  $C_1 = C_2 = 0$

**Answer: A**



**Watch Video Solution**

**72.** Consider the following statements  $A$  and  $B$  and identify the correct answer

(1) : Germanium is preferred over silicon in the construction of zener diode.

(2) : Germanium has high thermal stability than silicon in the construction of Zener diode.

- A. Both 1 & 2 are true
- B. Both 1 & 2 are false
- C. 1 is true 2 is false
- D. 1 is false but 2 is true

**Answer: B**



**Watch Video Solution**

**73.** A Zener diode when used as a voltage regulator is connected

- (a) in forward bias
- (b) in reverse bias

( c ) in parallel to the load

(d) in series to the load.

A. (a) and (b) are correct

B. (b) and ( c ) are correct

C. (a) only is correct

D. (d) only is correct

**Answer: B**



**Watch Video Solution**

**74.** Consider the following statements  $A$  and  $B$  and identify the correct answer

(A) A Zener diode is always connected in reverse bias to use it as voltage regulator.

(B) The potential barrier of a  $p - n$  junction lies between 0.1 to 0.3V, approximately.

- A.  $A$  and  $B$  are correct
- B.  $A$  and  $B$  are wrong
- C.  $A$  is correct but  $B$  is wrong
- D.  $A$  is wrong but  $B$  is correct.

**Answer: C**



**Watch Video Solution**

**75.** Consider the following statement  $A$  and  $B$  and identify the correct choice of the given answers

$A$ : The width of the depletion layer in a  $P - N$  junction diode increases in forwards biase



$B$ : In an intrinsic semiconductor the fermi energy level is exactly in the middle of the forbidden gap

- A.  $A$  is true and  $B$  is false
- B. Both  $A$  and  $B$  are false
- C.  $A$  is false and  $B$  is true
- D. Both  $A$  and  $B$  are true

**Answer: C**



**Watch Video Solution**

**76.** The potential in the depletion layer due to.

- A. Electrons
- B. Holes

C. Ions

D. Forbidden band

**Answer: C**



**Watch Video Solution**

77. Pickout the incorrect statement regarding reverse saturation current in the  $p - n$  junction diode.

A. this current doubles for every  $100^\circ C$  rise of temperature

B. the current is due to minority carriers

C. the current carriers are produced by thermal agitation

D. reverse saturation current is also known as leakage current

**Answer: A**



**Watch Video Solution**

**78.** When the  $p - n$  junction diode is reverse biased, the thickness of the depletion layer

- A. increase
- B. decrease
- C. becomes zero
- D. remains constant

**Answer: A**



**Watch Video Solution**

79.  $p - n$  junction diode can be used as

A. amplifier

B. detector

C. oscillator

D. capacitor

**Answer: B**



**Watch Video Solution**

80. A  $p - n$  junction diode is reverse biased. Then

A. more current flows

B. the barrier potential decreases

C. the barrier potential increases

D. resistance offered is low

**Answer: C**



[Watch Video Solution](#)

**81.** In the middle of the depletion layer of a reverse - biased  $p - n$  junction , the

- A. electric field is zero
- B. potential is maximum
- C. electric field is maximum
- D. potential is zero

**Answer: C**



[Watch Video Solution](#)

82. When  $p - n$  junction diode is forward biased then

- A. the depletion region is reduced and barrier height is increased
- B. the depletion region is widened and barrier height is reduced
- C. both the depletion region and barrier height are reduced
- D. both the depletion region and barrier height are increased

**Answer: C**



**Watch Video Solution**

83. In a  $p - n$  junction photo cell, the value of the photo electromotive force produced by monochromatic light is proportional to

- A. The barrier voltage at the  $p - n$  junction
- B. The intensity of the light falling on the cell
- C. The frequency of the light falling on the cell
- D. The voltage applied at the  $p - n$  junction

**Answer: B**



[Watch Video Solution](#)

84. There is a sudden increase in current in zener diode is

- A. Due to rupture of bonds

B. Resistance of depletion layer becomes less

C. Due to high doping

D. Due to less doping

**Answer: A**



**Watch Video Solution**

**85.** Application of a forward bias to a  $p - n$  junction:

A. increases the number of donors on the n-side

B. increases the electric field in the depletion zone

C. increases the potential difference across the depletion zone

D. widens the depletion zone



**Answer: A**



**Watch Video Solution**

**86.** In a p- n junction diode not connected to any circuit,

A. the potential is the same everywhere

B. then p-type side is at a higher potential than the n-type side.

C. there is an electric field at the junction directed from the n-type side to the p-type side.

D. there is an electric field at the junction directed from the p-type side to then n-type side.

**Answer: C**



Watch Video Solution

87. Select the correct statement from the following :

- A. A diode can be used as a rectifier
- B. A triode cannot be used as a rectifier
- C. The current in a diode is always proportional to the applied voltage
- D. The linear portion of the  $I - V$  characteristic of a triode is used for amplification without distortion.

**Answer: A**



Watch Video Solution

88. When a  $PN$  junction diode is forwards biased, energy is released at the junction due to the recombination of electrons and holes. This energy is in

- A. Visible region
- B. Infrared region
- C.  $UV$  region
- D. X-ray region

**Answer: B**



[Watch Video Solution](#)

89. A  $Si$  and a  $Ge$  diode has identical physical dimensions. The band gap in  $Si$  is larger than that in  $Ge$ . An identical reverse

bias is applied across the diodes.

- A. The reverse current in  $Ge$  is larger than that in  $Si$
- B. The reverse current in  $Si$  is larger than that in  $Ge$
- C. The reverse current is identical in the two diodes
- D. The relative magnitude of the reverse currents cannot be determined from the given data only.


**Answer: C**



**Watch Video Solution**

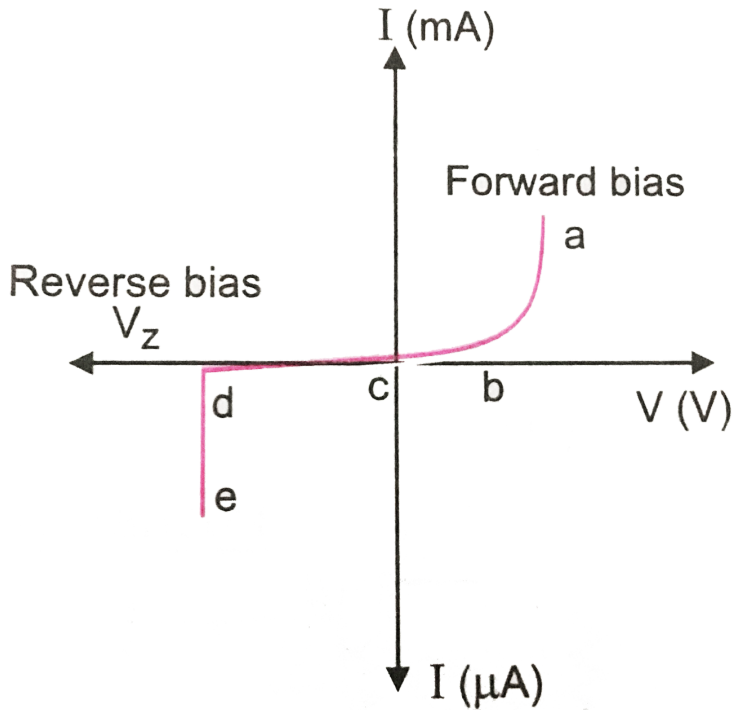**90.** The graph shown in Fig. represents the I-V characteristics of a zener diode. Which part of the characteristics curve is

most relevant for its operation as a voltage regular?



- A.  $A$ ,  $R$  are true and  $R$  explains  $A$  correctly
- B.  $A$ ,  $R$  are true and  $R$  do not explain  $A$  correctly
- C.  $A$  is true, but  $R$  is false
- D.  $R$  is true, but  $A$  is false

**Answer: D**



**Watch Video Solution**

**91.** Assertion (A) : *Si* and *GaAs* are preferred materials for solar cells

Reason (R) : Energy gap of *Si* is  $1.1eV$  and that of *GaAs* is  $1.53eV$  which gives maximum irradiance where as other materials like *CdS* or *CdSe* ( $E_g = 2.4eV$ ) and *PbS* ( $E_g = 0.4eV$ ) given minimum irradiance.



**Watch Video Solution**

**92.** Assertion (A) : Putting p-type semiconductor slabs directly in physical contact can not form  $p - n$  junction

Reason (R) : The roughness at contact will be much more than

inter atomic crystal spacing ( $= 2\text{\AA} \rightarrow 3\text{\AA}$ ) and continuous flow of charge carriers is not possible.



[Watch Video Solution](#)

**93.** Assertion (A) : Eventhough forward bias is known to be more ( $mA$ ) than the current in the reverse bias ( $\mu A$ ), photodiodes are still used in reverse bias.

Reason ( R ) : The fractional change in majority charge carriers would be much less than that in minority charge carriers due to photo-effects so that minority carrier reverse bias current is more easily to measure with photo diodes than majority carrier forward current.



[View Text Solution](#)

94. The correct relation between current gains  $\alpha$  and  $\beta$  is

A.  $\beta = \frac{\alpha}{1 - \alpha}$

B.  $\beta = \frac{\alpha}{1 + \alpha}$

C.  $\beta = \alpha(1 - \alpha)$

D.  $\beta = \frac{1 - \alpha}{\alpha}$

**Answer: A**



[Watch Video Solution](#)

95. Transistors are made of.

A. insulators

B. conductors



C. alloys

D. doped semi-conductors

**Answer: D**



**Watch Video Solution**

**96.** In  $n - p - n$  transistor the arrow head on emitter represents that the conventional current flows from

A. base to emitter

B. emitter to base

C. emitter to collector

D. base to collector

**Answer: A**



[Watch Video Solution](#)

**97.** In a junction transistor the emitter, base and collector are made of.

- A. extrinsic semi conductors
- B. intrinsic semi conductors
- C. both 1 and 2
- D. metal

**Answer: A**



[Watch Video Solution](#)

**98.** In a transistor.

- A. both emitter and the collector are equally doped
- B. base is more heavily doped than collector
- C. collector is more heavily doped than the emitter
- D. the base is made very thin and is lightly doped

**Answer: D**



**Watch Video Solution**

**99.** In a transistor

- A. length of emitter is greater than that of collector
- B. length of collector is greater than that of emitter
- C. both emitter and collector have same length
- D. any one of emitter and collector can have greater length

**Answer: B**



**Watch Video Solution**

**100.** In transistor the emitter current is.

- A. slightly more than the collector current
- B. slightly less than the collector current
- C. equal to the collector current
- D. equal to the base current

**Answer: A**



**Watch Video Solution**

**101.** In the use of transistor as an amplifier

- A. the emitter - base junction is reverse biased and the collector base junction is also reverse biased
- B. the emitter - base junction is forward biased and the collector -base junction is reverse biased
- C. both the junctions are forward biased
- D. any of the two junctions may be forward biased

**Answer: B**



[Watch Video Solution](#)

**102.** One way in which the operation of an *nnp* transistor differ from that of a *pnp* transistor is that

- A. the emitter junction is reverse biased in  $npn$
- B. the emitter junction injects minority carriers into the base region of the  $pnp$ .
- C. the emitter injects holes into the base of the  $pnp$  and electrons into the base region of  $npn$
- D. the emitter injects holes into the base of  $npn$ .

**Answer: C**



[Watch Video Solution](#)

**103.**  $npn$  transistors are preferred to  $pnp$  transistors because they have

- A. low cost

B. low dissipation energy

C. capable of handling large power

D. electrons have high mobility than holes and hence high mobility of energy.

**Answer: D**



**Watch Video Solution**

**104.** A  $CE$  transistor amplifies weak current signal because collector current is.

A.  $\beta$  times  $I_b$

B.  $\beta$  times  $I_C$

C.  $\alpha$  times  $I_b$

D.  $\alpha$  times  $I_C$

**Answer: A**



**Watch Video Solution**

**105.** When a positive voltage signal is applied to the base of a common emitter *npn* amplifier

- A. The emitter current decreases
- B. The collector voltage becomes more positive
- C. The collector voltage becomes less positive
- D. The collector current decreases

**Answer: C**



**Watch Video Solution**



**106.** In case of common emitter  $p - n - p$  transistor input characteristic is a graph drawn.

- A. With  $I_C$  on y-axis and  $V_{CE}$  on x-axis keeping  $I_B$  constant
- B. With  $I_B$  on y-axis and  $V_{BE}$  on x-axis keeping  $V_{CE}$  constant
- C. With  $I_C$  on y-axis and  $I_B$  on x-axis keeping  $V_{CE}$  constant
- D. With  $V_{BE}$  on y-axis and  $V_{CE}$  x- axis keeping  $I_B$  constant.

**Answer: B**



**Watch Video Solution**

107. The output characteristics of an  $n - p - n$  transistor represent, [ $I_C$  = Collector current,  $V_{CE}$  = potential difference between collector and emitter,  $I_B$  = Base current,  $V_{BB}$  = voltage given base,  $V_{BE}$  = the potential difference between base and emitter].

- A. change in  $I_C$  as  $I_B$  and  $V_{BB}$  are changed
- B. Changes in  $I_C$  with changes in  $V_{CE}$  ( $I_B = \text{constant}$ ).
- C. changes in  $I_B$  with changes in  $V_{CE}$ .
- D. Changes in  $I_C$  as  $V_{BE}$  is changed.

**Answer: B**



**Watch Video Solution**

**108.** In a transistor the base is made very thin and is lightly doped with an impurity, because.

- A. to enable the collector to collect about 95% of the holes or electrons coming from the emitter side
- B. to enable the emitter to emit small number of holes or electrons
- C. to save the transistors from high current effects
- D. to enable the base to collect about 95% of holes or electrons coming from the emitter side.

**Answer: A**



**Watch Video Solution**

109. A  $p - n - p$  transistor is said to be in active region of operation, When

- A. Both emitter junction and collector junction are forward biased
- B. Both emitter junction and collector junction are reverse biased
- C. Emitter junction is forward biased and collector junction is reverse biased
- D. Emitter junction is reverse biased and collector junction is forward biased.

**Answer: C**



**Watch Video Solution**

110. An  $n - p - n$  transistor power amplifier in  $C - E$  configuration gives.

- A. Voltage amplification only
- B. Current amplification only
- C. Both current and voltage amplification
- D. Only power gain of unity

**Answer: C**



[Watch Video Solution](#)

111. When N-P-N transistor is used as an amplifier-

- A. electrons move from base to collector

B. holes moves from emitter to base

C. holes move from collector to base

D. holes move from base to emitter

**Answer: A**



**Watch Video Solution**

**112.** The part of a transistor which is heavily doped to produce a large number of majority carriers, is

A. emitter

B. base

C. collector

D. can be any of the above three

**Answer: A**



**Watch Video Solution**

**113.** When N-P-N transistor is used as an amplifier-

- A. electrons move from collector to base
- B. holes move from collector to base
- C. electrons move from base to emitter
- D. holes move from base to emitter

**Answer: D**



**Watch Video Solution**

114. A  $n - p - n$  transistor conducts when

- A. both collector and emitter are positive when respect to the base
- B. collector is positive and emitter is negative with respect to the base
- C. collector is positive and emitter is at same potential as the base
- D. both collector and emitter are negative with respect to the base

**Answer: B**



**Watch Video Solution**



**115.** In a common-base amplifier, the phase difference between the input signal voltage and output voltage is :

A.  $\frac{\pi}{4}$

B.  $\pi$

C. zero

D.  $\frac{\pi}{2}$

**Answer: C**



**Watch Video Solution**

**116.** In a common emitter amplifier, the phase difference between the input signal voltage and output voltage is.

A.  $\frac{\pi}{2}$

B. 0

C.  $\pi$

D.  $\frac{\pi}{4}$

**Answer: C**



**Watch Video Solution**

**117.** When  $n - p - n$  transistor is used as an amplifier :

A. Electrons move from emitter to collector

B. Holes move from emitter to base

C. Electrons move from collector to base

D. Holes move from base to collector

**Answer: A**



Watch Video Solution

118. In a  $PNP$  transistor the base is the N-region. Its width relative to the P-region is

- A. smaller
- B. larger
- C. same
- D. not related

**Answer: A**



Watch Video Solution

119. A three terminal device with one terminal common to both the output and input is called.

- A. rectifier
- B. transistor
- C. diode
- D. triode

**Answer: B**



[Watch Video Solution](#)

120. Input and output signal of an amplifier in  $CE$  configuration are always

- A. Equal

B. Inphase

C. Having a phase difference

D. Out of phase

**Answer: D**



**Watch Video Solution**

**121.** *Ge* transistor can be operated at a temperature

A. upto  $90^{\circ} C$

B. upto  $40^{\circ} C$

C. upto  $100^{\circ} C$

D. upto  $20^{\circ} C$

**Answer: A**



[Watch Video Solution](#)

122. Transistor amplifier circuit with a feed back circuit is called

- A. oscillator
- B. detector
- C. modulator
- D. all

**Answer: A**



[Watch Video Solution](#)

123. A pulsating voltage is a mixture of an *a. c* componet and *a. d. c* compenent. The circuit used to separate *a. c* and *d. c*

component is called

- A. an oscillator
- B. an amplifier
- C. a rectifier
- D. a filter

**Answer: D**



**Watch Video Solution**

**124.** The  $\alpha$  and  $\beta$  of a transistor are always

- A.  $\alpha > 1, \beta < 1$
- B.  $\alpha < 1, \beta > 1$
- C.  $\alpha = \beta$

D.  $\alpha\beta = 1$

**Answer: B**



**Watch Video Solution**

**125.** In case of *NPN* transistor, emitter current is always greater than collector current, because :

- A. Collector side is reverse biased and emitter side is forward biased
- B. Collector being reverse biased attracts more electrons
- C. Some electrons are lost in base
- D. Collector side is forward biased and emitter side is reverse biased.



**Answer: C**



**Watch Video Solution**

**126.** When a transistor amplifier having current gain of 75 is given an input signal,  $V_I = 2 \sin(157t + \pi/2)$ , the output signal is found to be  $V_o = 200 \sin(157t + 3\pi/2)$ . The transistor is connected as :

- A. A common collector amplifier
- B. A common base amplifier
- C. A common emitter amplifier
- D. An oscillator

**Answer: C**



**Watch Video Solution**

**127.** An oscillator is an amplifier with

- A. A large gain
- B. Negative oscillator
- C. Positive feedback
- D. No feedback

**Answer: C**



**Watch Video Solution**

**128.** In which of the transistor configurations, the voltage gain is highest ?

- A. Common-base
- B. Common-emitter
- C. Common-collector
- D. Same in all three

**Answer: B**



[Watch Video Solution](#)

**129.** A working transistor with its three legs marked  $P$ ,  $Q$  and  $R$  is tested using a multimeter. No conduction is found between  $P$ ,  $Q$  by connecting the common (negative) terminal of the multimeter to  $R$  and the other (positive) terminal to or  $Q$  some resistance is seen on the multimeter. Which of the following is true for the transistor ?

- A. It is a *pn*p transistor with  $R$  as emitter
- B. It is an *np*n transistor with  $R$  as collector
- C. It is an *np*n transistor with  $R$  as base
- D. It is *pn*p transistor with  $R$  as collector.

**Answer: D**



**Watch Video Solution**

**130.** Common emitter mode of a transistor is widely used.

Current gain, voltage gain, and power gain are maximum in

*C. E* mode of a transistors.

- A. If both  $A$  and  $R$  are correct and  $R$  is the correct explanation of  $A$

B. If both  $A$  and  $R$  are correct and  $R$  is not the correct explanation of  $A$

C. If 'A' is correct and 'R' is incorrect

D. If 'A' is incorrect and 'R' is correct.

**Answer: A**



**Watch Video Solution**

**131.** Transistor in  $C. E$  mode can be used as amplifier

A small change in base current produces a relatively large change in collector current.

A. If both  $A$  and  $R$  are correct and  $R$  is the correct explanation of  $A$

B. If both  $A$  and  $R$  are correct and  $R$  is not the correct explanation of  $A$

C. If 'A' is correct and 'R' is incorrect

D. If 'A' is incorrect and 'R' is correct.

**Answer: A**



**Watch Video Solution**

**132.** In the Binary number system the number 100 represents :

A. one

B. three

C. four

D. hundred

**Answer: C**



**Watch Video Solution**

**133.** Among the following is not the function of *NOT* gate is

- A. stop a signal
- B. invert an input signal
- C. complement a signal
- D. change the logic in a digital circuit

**Answer: A**



**Watch Video Solution**

134. Digital circuit can be made by repetitive use of

A. *OR* gates

B. *AND* gates

C. *NOT* gates

D. *NAND* gates

**Answer: D**



**Watch Video Solution**

135. Among the following one gives output 1 in the *AND* gate.

A.  $A = 0, B = 0$

B.  $A = 1, B = 1$



C.  $A = 1, B = 0$

D.  $A = 0, B = 1$

**Answer: B**



**Watch Video Solution**

**136.** Person who use Boolean algebra for describing the operation of logic gates first was

A. Boole

B. Shannon

C. Schottky

D. Zener

**Answer: B**



Watch Video Solution

**137.** *NAND* and *NOR* gates are called universal gates because they

- A. are universally available
- B. can be combined to produce *OR*, *AND* and *NOT* gates
- C. are widely used in the Integrated circuits
- D. can be easily manufactured

**Answer: B**



Watch Video Solution

**138.** In positive logic, the logic state 1 corresponds to

- A. positive voltage
- B. zero voltage
- C. lower voltage level
- D. higher voltage level.

**Answer: D**



**Watch Video Solution**

**139.** In Boolean algebra  $A + B = Y$  implies that :

- A. sum of  $A$  and  $B$  is  $Y$
- B.  $Y$  exists when  $A$  exists or  $B$  exists or both  $A$  and  $B$  exist
- C.  $Y$  exists only when  $A$  and  $B$  both exist

D.  $Y$  exists when  $A$  or  $B$  exist but not when both  $A$  and  $B$  exist.

**Answer: B**



[Watch Video Solution](#)

**140.** In the Boolean algebra, the following one is wrong

A.  $1 + 0 = 1$

B.  $0 + 1 = 1$

C.  $1 + 1 = 1$

D.  $0 + 0 = 1$

**Answer: D**



[Watch Video Solution](#)

141. In Boolean algebra  $A \cdot B = Y$  implies that :

A. product of  $A$  and  $B$  is  $Y$

B.  $Y$  exists when  $A$  exists or  $B$  exists

C.  $Y$  exists when both  $A$  and  $B$  exist but not when only  $A$   
or  $B$  exists

D.  $Y$  exists when  $A$  or  $B$  exists but not both  $A$  and  $B$  exist.

**Answer: C**



[Watch Video Solution](#)

142. In the Boolean algebra, the following one is wrong

A.  $1.0 = 0$

B.  $0.1 = 0$

C.  $1.1 = 0$

D.  $1.1 = 1$

**Answer: C**



**Watch Video Solution**

**143.** The following truth table is for

<i>A</i>	<i>B</i>	<i>Y</i>
1	1	0
1	0	1
0	1	1
0	0	1

A. *NAND* gate

B. *AND* gates

C. *XOR* gate

D. *NOT* gate

**Answer: A**



[Watch Video Solution](#)

**144.** The output of a 2-input *OR* gate is zero only when its

A. both inputs are 0

B. either input is 1

C. both inputs are 1

D. either input is zero

**Answer: A**



[Watch Video Solution](#)

145. Boolean algebra is essentially based on

A. symbols

B. logic

C. truth

D. numbers

**Answer: B**



[Watch Video Solution](#)

146. The value of  $\bar{A} + A$  in the Boolean algebra is

A.  $A$



B.  $\bar{A}$

C. 0

D. 1

**Answer: D**



**Watch Video Solution**

**147.** The value of  $A \cdot \bar{A}$  in Boolean algebra is.

A. 0

B. 1

C.  $A$

D.  $\bar{A}$

**Answer: A**



Watch Video Solution

148. The following is *NOT* equal to 0 in the Boolean algebra is

A.  $\overline{\overline{A}} \cdot 0$

B.  $A \cdot \overline{A}$

C.  $A \cdot 0$

D.  $\overline{A + \overline{A}}$

Answer: A



Watch Video Solution

149. An *AND* gate is following by a *NOT* gate in series. With two inputs  $A$  &  $B$ , the Boolean expression for the out put  $Y$

will be :

A.  $A \cdot B$

B.  $A + B$

C.  $\overline{A + B}$

D.  $\overline{A \cdot B}$

**Answer: D**



[Watch Video Solution](#)

**150.** *NOR* gate is the series combination of

A. *NOT* gate following by *OR* gate

B. *OR* gate following by *NOT* gate

C. *AND* gate followed by *OR* gate

D. *OR* gate followed by *AND* gate

**Answer: B**



**Watch Video Solution**

**151.** The gate that has only one input terminal

A. *NOT*

B. *NOR*

C. *NAND*

D. *XOR*

**Answer: A**



**Watch Video Solution**

152. *AND* gate :

- A. It has no equivalence to switching circuit.
- B. It is equivalent to series switching circuit
- C. It is equivalent to parallel switching circuit
- D. It is mixture of series and parallel switching circuit

**Answer: B**



[Watch Video Solution](#)

153. The gate that can act as a building block for the digital circuits is

- A. *OR*
- B. *NOT*

C. *AND*

D. *NAND*

**Answer: D**



**Watch Video Solution**

**154.** Assertion: *NAND* or *NOR* gates are called digital building blocks.

Reason: The repeated use of *NAND* (or *NOR*) gates can produce all the basic or complicated gates.

A. Statement – 1 is false, statement – 2 is true

B. statement 1 – is true statement – 2 is true statement

– 2 is correct explanation of statement – 1.

- C. statement 1 – is true statement – 2 is true statement  
– 2 is not correct explanation of statement – 1
- D. statement 1 – is true statement – 2 is false.

**Answer: B**



[Watch Video Solution](#)

**155.** *NOT* gate is also called invertor circuit.

*NOT* gate inverts the input order.

- A. Statement – 1 is false, statement – 2 is true
- B. statement 1 – is true statement – 2 is true statement  
– 2 is correct explanation of statement – 1.

C. statement 1 – is true statement – 2 is true statement

– 2 is not correct explanation of statement – 1

D. statement 1 – is true statement – 2 is false.

**Answer: B**



[Watch Video Solution](#)

Level I C W

1. The electrical conductivity of a semiconductor increases when electromagnetic radiation of wavelength shorter than 2480 nm is incident on it. The band gap (in eV) for the semiconductor is  $[hc = 1242eVnm]$

A.  $0.7eV$



B.  $0.5eV$

C.  $2.5eV$

D.  $1.2eV$

**Answer: B**



[Watch Video Solution](#)

2. Pure *Si* at  $300K$  has equal electron ( $n_i$ ) concentrations of  $1.5 \times 10^{16} m^{-3}$ . Doping by indium increases  $n_h = 4.5 \times 10^{22} m^{-3}$ .  $N_e$  in the doped *Si* is

A.  $5 \times 10^9$

B.  $7 \times 10^9$

C.  $9 \times 10^9$

D.  $8 \times 10^9$

**Answer: A**



**View Text Solution**

3. In a  $p - n$  junction the depletion region is  $400nm$  wide and electric field of  $5 \times 10^5 Vm^{-1}$  exists in it. The minimum energy of a conduction electron, which can diffuse from n-side to the p-side is.

A.  $4eV$

B.  $5eV$

C.  $0.4eV$

D.  $0.2eV$

**Answer: D**



**Watch Video Solution**

4. The reverse bias in a junction diode is changed from  $5V$  to  $15V$  then the value of current changes from  $38\mu A$  to  $88\mu A$ . The resistance of junction diode will be.

A.  $4 \times 10^5 \Omega$

B.  $3 \times 10^5 \Omega$

C.  $2 \times 10^5 \Omega$

D.  $10^6 \Omega$

**Answer: C**



**Watch Video Solution**

5. A diode made of silicon has a barrier potential of  $0.7V$  and a current of  $20mA$  passes through the diode when a battery of  $emf 3V$  and a resistor is connected to it. The wattage of the resistor and diode are

A.  $0.046W$ ,  $0.014W$

B.  $4.6W$ ,  $0.14W$

C.  $0.46W$ ,  $0.14W$

D.  $46W$ ,  $14W$

**Answer: A**



**Watch Video Solution**

6. In a half wave rectifier output is taken across a  $90\Omega$  load resistor. If the resistance of diode in forward biased condition is  $10\Omega$ , the efficiency of rectification of  $ac$  power into  $dc$  power is.

A. 40.6 %

B. 81.2 %

C. 73.08 %

D. 36.54 %

**Answer: D**



**Watch Video Solution**

7. In a full wave rectifier output is taken across a load resistor of  $800\text{ohm}$ . If the resistance of diode in forward biased condition is  $200\text{ohm}$ , the efficiency of rectification of  $ac$  power into  $dc$  power is.

A. 64.96 %

B. 40.6 %

C. 81.2 %

D. 80 %

**Answer: A**



**Watch Video Solution**

8. In a  $P - N - P$  transistor, the collector current is  $10\text{mA}$ . If 90% of the holes reach the collector, then emitter current will be :

A.  $13\text{mA}$

B.  $12\text{mA}$

C.  $11\text{mA}$

D.  $10\text{mA}$

**Answer: C**



**Watch Video Solution**

9. A transistor has a base current of  $1\text{mA}$  and emitter current  $100\text{mA}$ . The current transfer ratio will be

A. 0.9

B. 0.99

C. 1.1

D. 10.1

**Answer: B**



**Watch Video Solution**

**10.** When base-emitter voltage of a transistor connected in the common-emitter mode is changed by  $20mV$  the collector current is changed by  $25mA$ . Find the transconductance.

A.  $1.25\Omega^{-1}$

B.  $2.50\Omega^{-1}$



C.  $0.5\Omega^{-1}$

D.  $5.5\Omega^{-1}$

**Answer: A**



**Watch Video Solution**

**11.** In a transistor circuit the base current changes from  $30\mu A$  to  $90\mu A$ . If the current gain of the transistor is 30, the change in the collector current is.

A.  $4mA$

B.  $2mA$

C.  $3.6mA$

D.  $1.8mA$

**Answer: D**



**Watch Video Solution**

12. The circuit gain of transistor in a common emitter circuit is 40. The ratio of emitter current to base current is.

A. 40

B. 41

C. 42

D. 43

**Answer: B**



**Watch Video Solution**

13. In a common base configuration the emitter current changes by  $5\text{mA}$  when emitter voltage is changed by  $200\text{mV}$  at a fixed collector to base voltage. The input resistance is.

- A.  $40\Omega$
- B.  $1000\Omega$
- C.  $2.5\Omega$
- D.  $4\Omega$

**Answer: A**



**Watch Video Solution**

14. For a common base amplifier, The values of resistance gain and voltage gain are 3000 and 2800 respectively. The current gain will be.

A. 0.93

B. 0.83

C. 0.73

D. 0.63

**Answer: A**



**Watch Video Solution**

**15.** In a transistor amplifier  $\beta = 62$ ,  $R_L = 5000\Omega$  and internal resistance of the transistor is  $500\Omega$ . Its power amplification will be.

A. 25580

B. 33760

C. 38440

D. 55280

**Answer: C**



[Watch Video Solution](#)

**16.** Decimal number 15 is equivalent to the binary number :

A. 110001

B. 000101

C. 101101

D. 001111

**Answer: D**



[Watch Video Solution](#)

17. Binary number 1001001 is equivalent to the decimal number :

A. 37

B. 73

C. 41

D. 32

**Answer: B**



[Watch Video Solution](#)

18. In the Binary number system  $1 + 1 =$

A. 2

B. 1

C. 10

D. 100

**Answer: C**



**Watch Video Solution**

**19.** If  $A = B = 1$ , then in terms of Boolean algebra the value of  $A \cdot B + A$  is not equal to.

A.  $B \cdot A + B$

B.  $B + A$

C.  $B$

D.  $\bar{A} \cdot B$

**Answer: D**



**Watch Video Solution**

**20.** In the Boolean algebra, the following one which is not equal to  $A$  is.

A.  $A \cdot A$

B.  $A + A$

C.  $\bar{A} \cdot A$

D.  $\overline{\bar{A} + \bar{A}}$

**Answer: C**



**Watch Video Solution**



21. The logic expression which is *NOT* true in Boolean algebra is.

A.  $(\bar{1} + \bar{1}) \cdot 1 = 0$

B.  $(\bar{1} + 0) \cdot 1 = 0$

C.  $(\bar{1} + 0) \cdot \bar{1} = 0$

D.  $(1 + 1) \cdot 1 = 0$

**Answer: D**



**Watch Video Solution**

**Level II C W**

1. Mobilities of electrons and holes in a sample of intrinsic germanium at room temperature are  $0.36m^2/Vs$  and

$0.17m^2 / Vs$ . The electron and hole densities are each equal to  $2.5 \times 10^{19}m^{-3}$ . The electrical conductivity of germanium is.

A.  $0.47S / m$

B.  $5.18S / m$

C.  $2.12S / m$

D.  $1.09S / m$

**Answer: C**



**Watch Video Solution**

2. In a  $p - n$  junction diode the thickness of depletion layer is  $2 \times 10^{-6}m$  and barrier potential is  $0.3V$ . The intensity of the electrical field at the junction is.

A.  $0.6 \times 10^{-6}Vm^{-1}$  from  $n$  to  $p$  side

B.  $0.6 \times 10^{-6} \text{Vm}^{-1}$  from  $p$  to  $n$  side

C.  $1.5 \times 10^5 \text{Vm}^{-1}$  from  $n$  to  $p$  side

D.  $1.5 \times 10^5 \text{Vm}^{-1}$  from  $p$  to  $n$  side.

**Answer: C**



**Watch Video Solution**

**3.** A potential barrier  $V$  volts exists across a  $P - N$  junction.

The thickness of the depletion region is 'd'. An electron with

velocity 'v' approaches  $P - N$  junction from N-side. The velocity

of the electron acrossing the junction is.

A.  $\sqrt{v^2 + \frac{2Ve}{m}}$

B.  $\sqrt{v^2 - \frac{2Ve}{m}}$




C.  $v$


D.  $\sqrt{\frac{2Ve}{m}}$

Answer: B

 Watch Video Solution

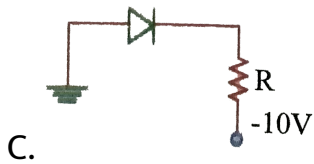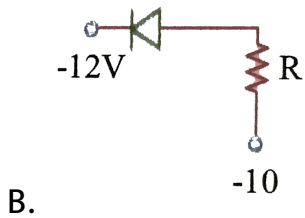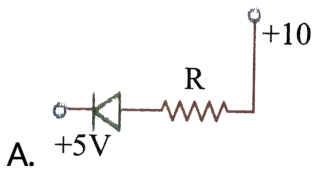4. In the following, reverse biased diode is.



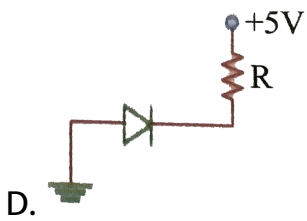


**Answer: D**

[Watch Video Solution](#)

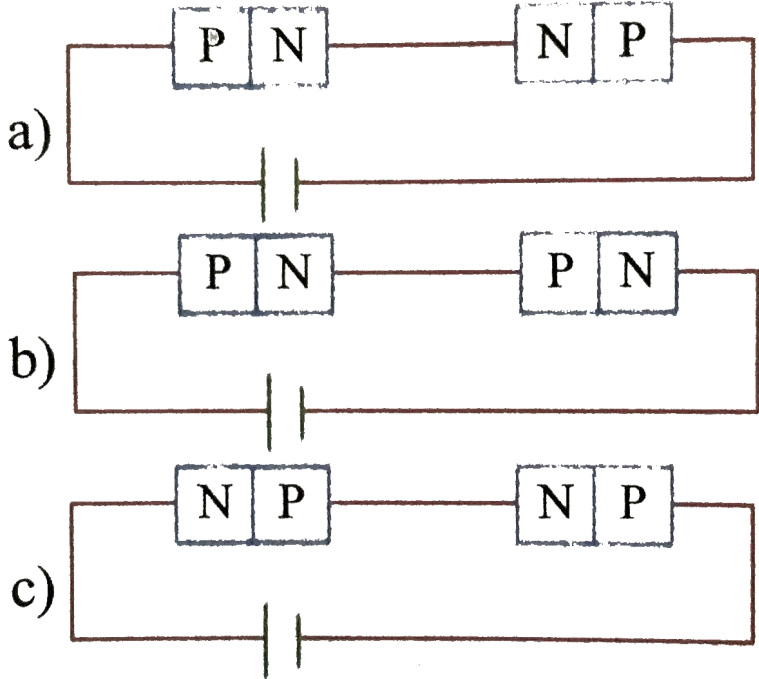5. Two similar  $p - n$  junctions can be connected in three different ways as shown in the figure. The two connections

across which the potential difference is same are.




(a)

- A. circuit *a* and *b*
- B. circuit *b* and *c*
- C. circuits *a* and *c*
- D. all the circuits

**Answer: B**



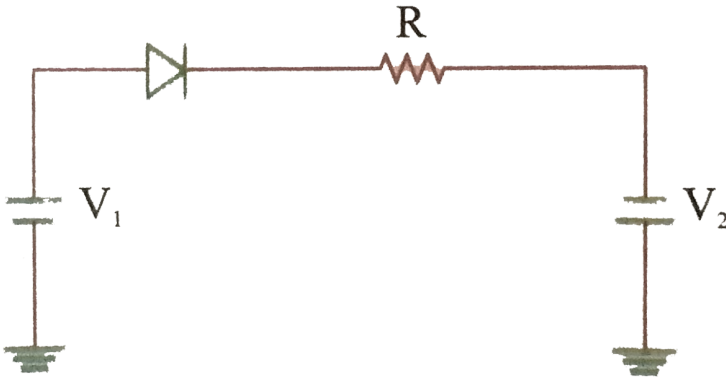6. If  $V_1 > V_2$ ,  $r$  is resistance offered by diode in forward bias then current through the diode is.



A. 0


B.  $\frac{V_1 + V_2}{R + r}$

C.  $\frac{V_1 - V_2}{R + r}$

D. None

Answer: B

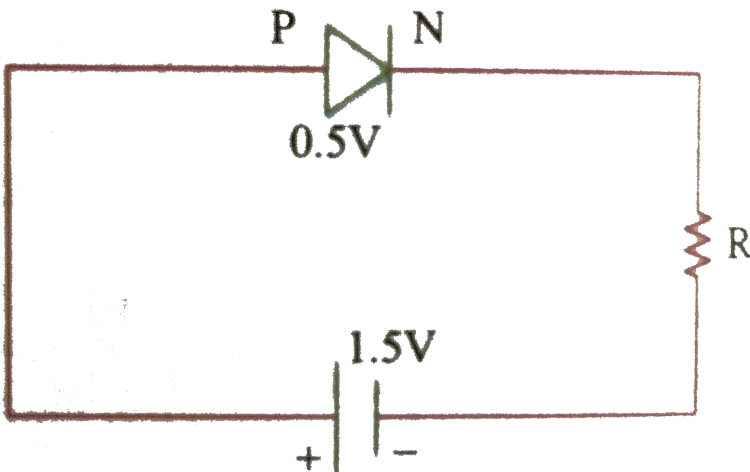7. A  $PN$  junction diode when forward biased has a drop of  $0.5V$  which is assumed to be independent of current. The current in excess of  $10mA$  through the diode produces large joule heating which damages the diode. If we diode, the resistor used in series with the diode so that the maximum current does not exceed  $5mA$  is.



A.  $2 \times 10^2 \Omega$



B.  $2 \times 10^5 \Omega$

C.  $2 \times 10^3 \Omega$

D.  $2 \times 10^4 \Omega$


**Answer: A**



**Watch Video Solution**

8. The circuit shown in figure (1) Contains two diodes each with a forward resistance of  $50\Omega$  and with infinite reverse resistance. If the battery voltage is  $6V$ , the current through

the  $100\text{ohm}$  resistance is.

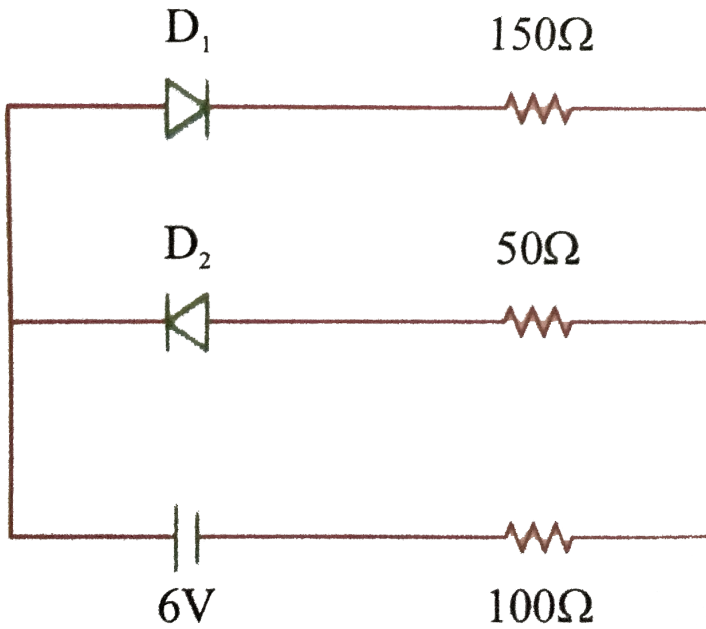


- A.  $0.01A$
- B.  $0.02A$
- C.  $0.03A$
- D.  $0.04A$

**Answer: B**



**Watch Video Solution**

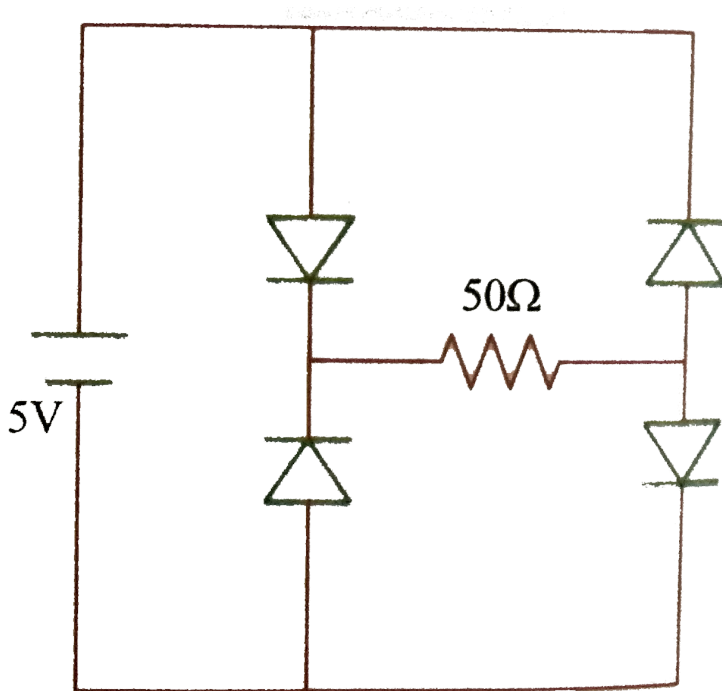9. 4 ideal diodes are connected as shown in the circuit the current through  $50\Omega$  is.



A.  $0.1A$

B.  $0.5A$


C.  $0.6A$

D. 1A

Answer: A

 Watch Video Solution

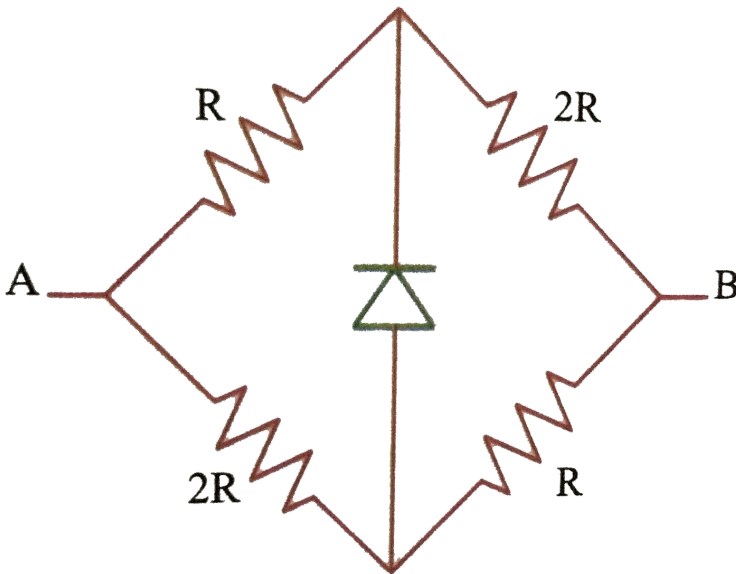10. Find the effective resistance between  $A$  &  $B$



A.  $\frac{2}{3R}$

B.  $\frac{3R}{2}$

C.  $\frac{2R}{2}$


D.  $R$

Answer: B



Watch Video Solution

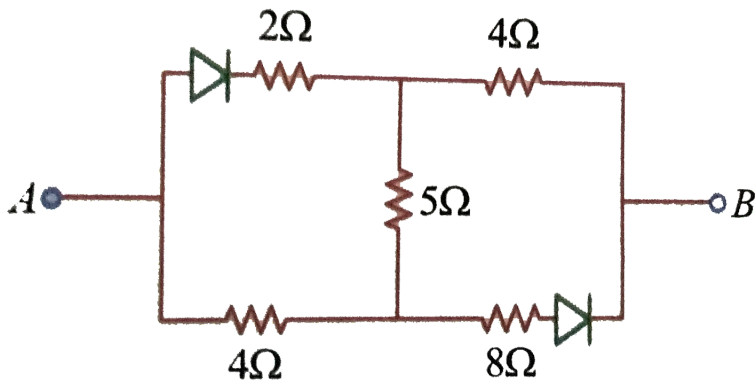11. The equivalent resistance of the circuit across  $AB$  is given by



A.  $4\Omega$

B.  $13\Omega$


C.  $4\Omega$  or  $13\Omega$

D.  $4\Omega$  or zero

**Answer: C**

 [Watch Video Solution](#)

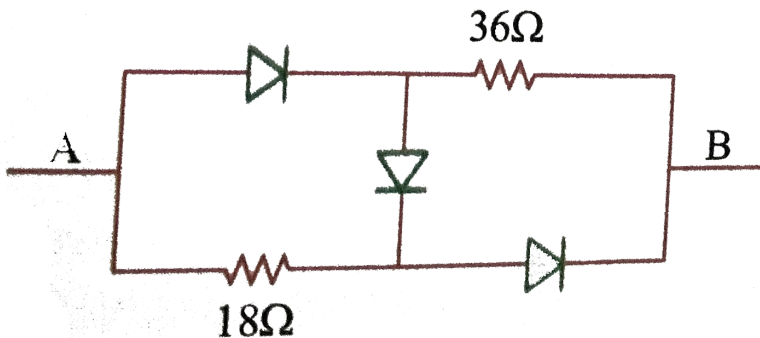12. The equivalent resistance between  $A$  and  $B$  is



A.  $36\Omega$  if  $V_A > V_B$

B.  $18\Omega$  if  $V_A < V_B$

C. Zero if  $V_A < V_B$  and  $54\Omega$  if  $V_A > V_B$

D. Zero if  $V_A > V_B$  and  $54\Omega$  if  $V_A < V_B$

**Answer: D**



[Watch Video Solution](#)

**13.** A junction diode is connected to a  $10V$  source and  $10^3\Omega$  rheostat. The slope of load line on the characteristic curve of diode by ( $\text{inA} / V$ ).

A.  $10^{-1}$

B.  $10^{-2}$


C.  $10^{-3}$

D.  $10^{-4}$




Answer: C

 Watch Video Solution

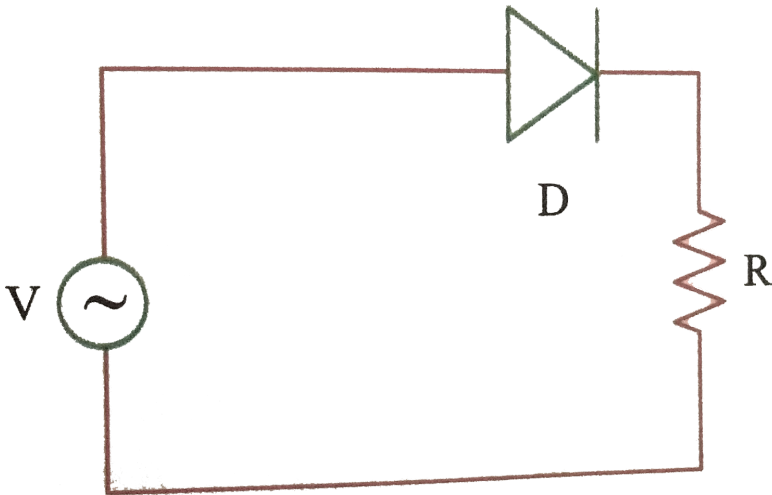14. A  $p - n$  junction ( $D$ ) shown in the figure can act as a rectifier. An alternating current source ( $V$ ) is connected in the circuit.





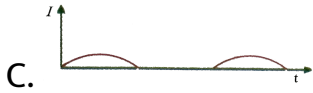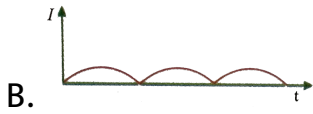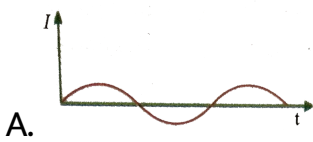


**Answer: C**



**Watch Video Solution**

**15.** In the diagram, the input is across the terminals  $A$  and  $C$  and the output is across the terminals  $B$  and  $D$ , then the





outputs is

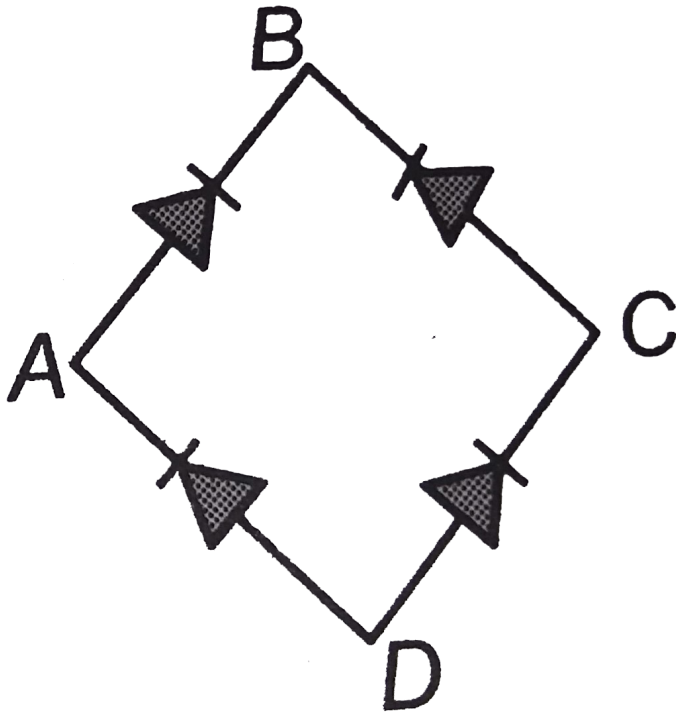

- A. Zero
- B. Same as the input
- C. Full wave rectified
- D. Half-wave rectified

**Answer: C**

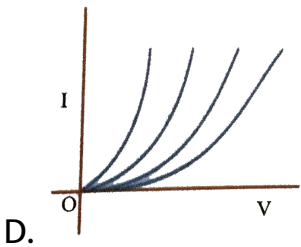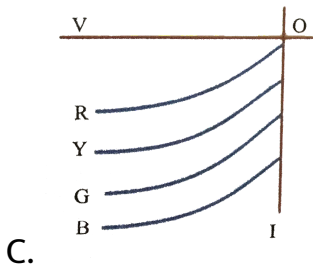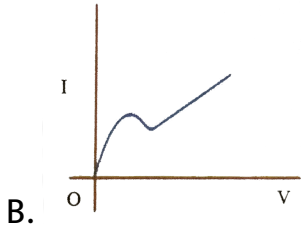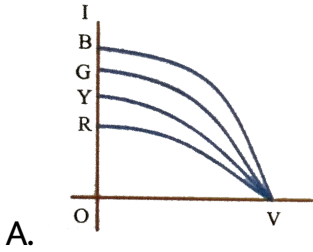
16. The  $I - V$  characteristic of an  $LED$  is.



Answer: D

 Watch Video Solution

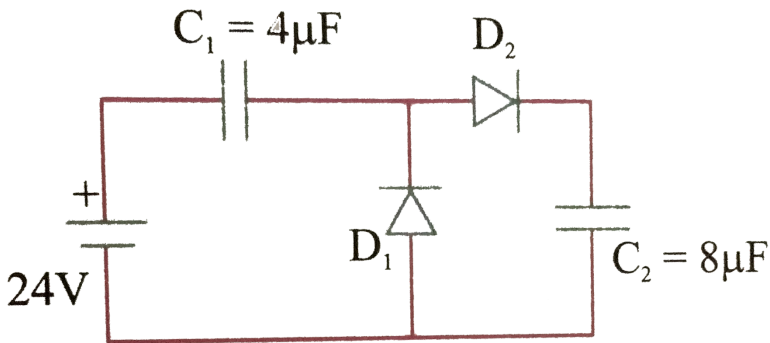17. In the circuit shown. The potential drop across each capacitor is (assuming the two diodes are ideal).



A. 12 V, 12 V

B. 16 V, 8 V


C. zero, 24 V

D. 8 V, zero

Answer: B

 Watch Video Solution

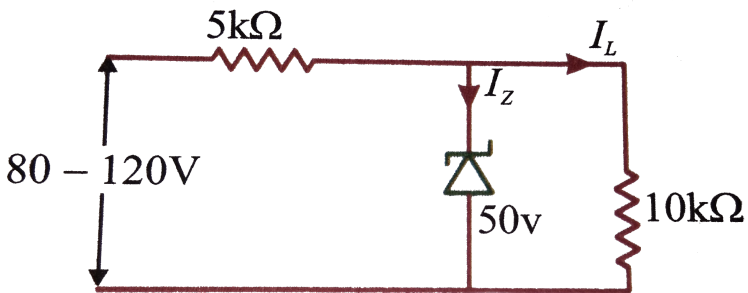18. The maximum and minimum values of zener diode current are



A. 6mA,5mA

B. 14mA,5mA

C. 9mA,1mA

D. 3mA,2mA

**Answer: C**



[Watch Video Solution](#)

19. In an n-p-n transistor circuit, the collector current is 10 mA.

If 90% of the electrons emitted reach the collector.

A. the emitter current, the will be  $9mA$

B. the base current will be  $1mA$

C. the emitter current will be  $11mA$

D. both 2 & 3

**Answer: D**



[Watch Video Solution](#)

20. The constant  $\alpha$  of a transistor is 0.9 What would be the change in the collector current corresponding to a change of  $4mA$  in the base current in a common emitter arrangement ?

A.  $30mA$

B.  $63mA$

C.  $36mA$

D.  $3.6mA$

**Answer: C**



**Watch Video Solution**

21. A voltage amplifier operated from a 12volt battery has a collector load  $6k\Omega$ . Calculate the maximum collector current in the circuit.

A.  $0.5mA$

B.  $1mA$

C.  $3mA$

D.  $2mA$

**Answer: D**




[Watch Video Solution](#)

22. In a transistor circuit shown here the base current is  $35\mu A$ .

The value of the resistor  $R_b$  is



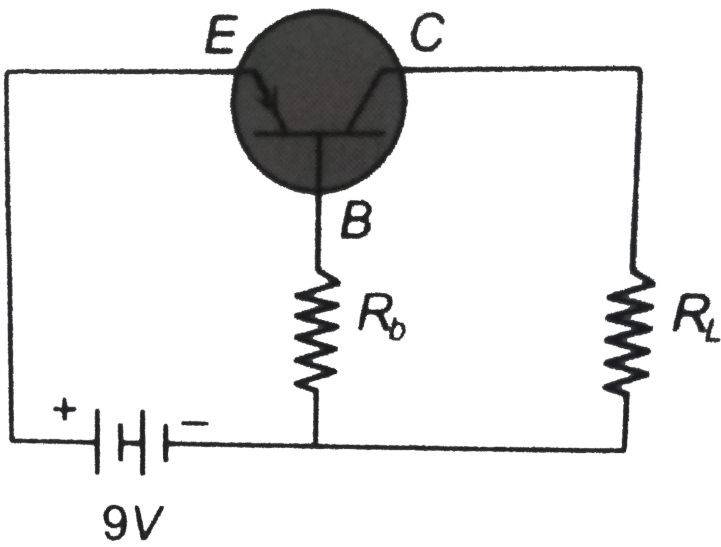

- A.  $124k\Omega$
- B.  $257k\Omega$
- C.  $352k\Omega$
- D. None of these

**Answer: B**



**Watch Video Solution**

23. In a single stage transistor amplifier, when the signal changes by  $0.02V$  the base current by  $10\mu A$  and collector current by  $1mA$ . If collector load  $R_C = 2k\Omega$  and  $R_L = 10k\Omega$ ,

Calculate :

(i) Current Gain

(ii) Input Impedance,

(iii) Effective AC load,

(iv) Voltage gain and

(v) Power gain.

A. 50,  $2k\Omega$ ,  $1.66k\Omega$ , 83, 8300

B. 100,  $1k\Omega$ ,  $1.66\Omega$ , 83, 8300

C. 100,  $2k\Omega$ ,  $1.66k\Omega$ , 83, 830

D. 100,  $2k\Omega$ ,  $1.66k\Omega$ , 83, 8300

**Answer: D**



[Watch Video Solution](#)

24. On subtracting 010101 from 101010, we get :

A. 001011

B. 001100

C. 010101

D. 011111

**Answer: C**



[Watch Video Solution](#)

25. The minimum number of gates required to realise this expression  $Z = DABC + D\overline{A}\overline{B}C$  is.

A. One

B. Two

C. Eight


D. Five

**Answer: A**



**Watch Video Solution**

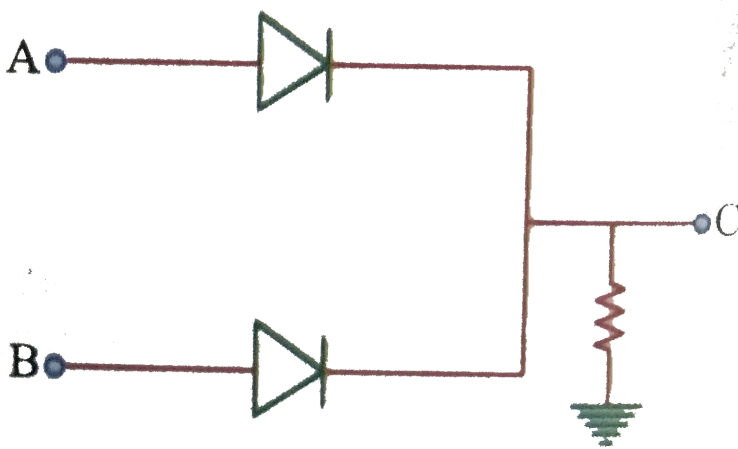**26.** In the circuit below,  $A$  and  $B$  represents two inputs and  $C$  represents the output, the circuit represents.



A. *NOR* gate

B. *AND* gates

C. *NAND*gate


D. *OR*gate

**Answer: D**



**Watch Video Solution**

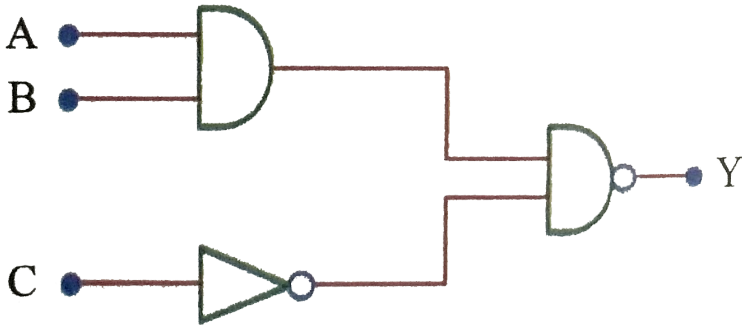27. In the following circuit the output  $Y$  becomes zero for the inputs



A.  $A = 1, B = 0, C = 0$

B.  $A = 0, B = 1, C = 1$


C.  $A = 0, B = 0, C = 0$

D.  $A = 1, B = 1, C = 0$

**Answer: D**

 [Watch Video Solution](#)

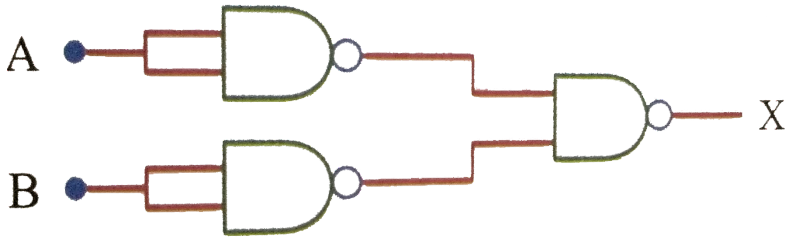28. The combination of gates shown below yields



A. *NAND* gate

B. *OR* gate

C. *NOT* gates





D. *XOR* gate

**Answer: B**



**Watch Video Solution**

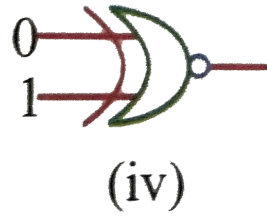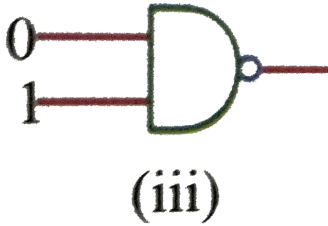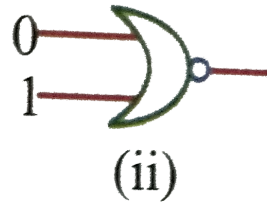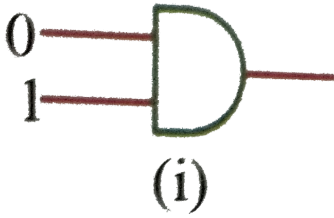29. The logic gate having an output of 1 is.



(i)

A. (iv)

B. (i)

C. (ii)

D. (iii)


**Answer: D**





**Watch Video Solution**




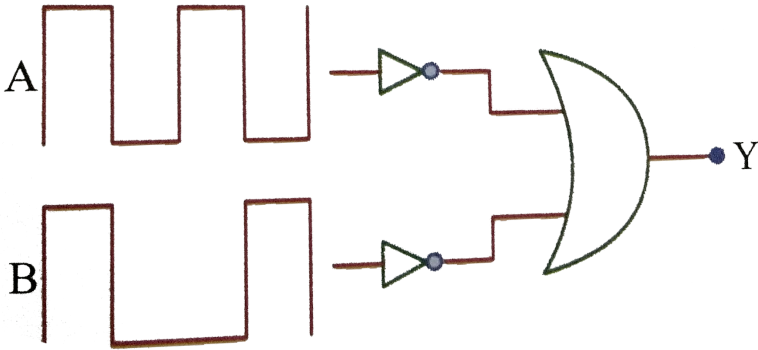30. In a given circuit as shown the two input wave forms  $A$  and  $B$  are applied simultaneously.



The resultant wave format at  $Y$  is.

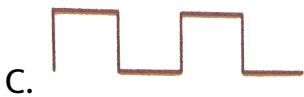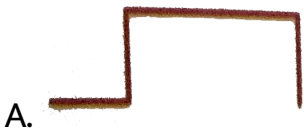


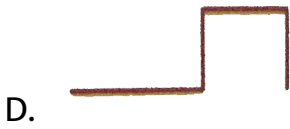

Answer: A

 [Watch Video Solution](#)

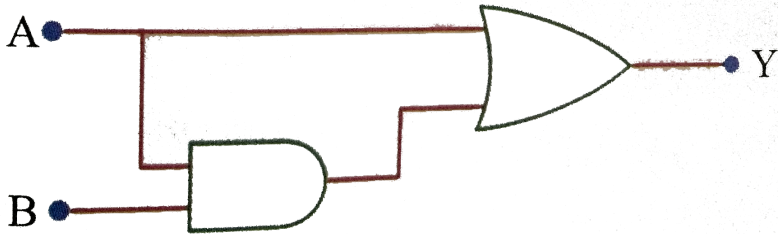31. The output of the combination of the gates shown in the figure below is



A.  $A + A \cdot B$

B.  $(A + B)A + \bar{B}$


C.  $(A \cdot B) + (\bar{A} \cdot \bar{B})$

D.  $(A + B)(\overline{A \cdot B})$

Answer: A

 Watch Video Solution

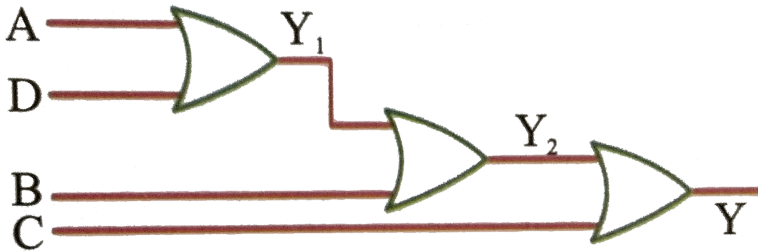32. The expression of  $Y$  in following circuit is



A.  $ABCD$

B.  $A + BCD$

C.  $A + B + C + D$

D.  $AB + CD$

**Answer: C**



**Watch Video Solution**

**33.** How many *NAND* gate are used to from *AND* gate?

- A. four
- B. two
- C. three
- D. Five

**Answer: C**



**Watch Video Solution**

1. If the ratio of the concentration of electron to that of holes in a semiconductor is  $\frac{7}{5}$  and the ratio of current is  $\frac{7}{4}$  then what is the ratio of their drift velocities ?

A.  $5/8$

B.  $4/8$

C.  $5/4$

D.  $4/7$

**Answer: C**



**Watch Video Solution**

2. If the resistivity of copper is  $1.7 \times 10^{-6} \Omega cm$ , then the mobility of electrons in copper, if each atom of copper

contributes one free electron for conduction, is [The atomic weight of copper is 63.54 and its density is  $8.96\text{g/cc}$ ]:

A.  $23.36\text{cm}^2 / \text{Vs}$

B.  $503.03\text{cm}^2 / \text{Vs}$

C.  $43.25\text{cm}^2 / \text{Vs}$

D.  $88.0\text{cm}^2 / \text{Vs}$

**Answer: C**



**Watch Video Solution**

3. A pure silicon crystal of length  $l(0.1\text{m})$  and area  $A(10^{-4}\text{m}^2)$  has the mobility of electron ( $\mu_e$ ) and holes ( $\mu_h$ ) as  $0.135\text{m}^2 / \text{Vs}$  and  $0.48\text{m}^2 / \text{Vs}$ , respectively, If the voltage applied across it is  $2\text{V}$  and the intrinsic charge concentration

it is  $2V$  and the intrinsic charge concentration is  $n_i = 1.5 \times 10^6 m^{-3}$ , then the total current flowing through the crystal is.

A.  $8.78 \times 10^{17} A$

B.  $6.25 \times 10^{-17} A$

C.  $7.89 \times 10^{-17} A$

D.  $2.456 \times 10^{-17} A$

**Answer: A**



**Watch Video Solution**

4. Find the current produced at room temperature in a pure germanium plate of area  $2 \times 10^{-4} m^2$  and of thickness  $1.2 \times 10^{-3} m$  when a potential of  $5V$  is applied across the

faces. Concentration of carries in germanium at room temperature is  $1.6 \times 10^6$  per cubic metre. The mobilities of electrons and holes are  $0.4m^2V^{-1}s^{-1}$  and  $0.2m^2V^{-1}s^{-1}$  respectively. The heat energy generated in the plate in 100 second is.

A.  $2.4 \times 10^{-11} J$

B.  $3.4 \times 10^{-11} J$

C.  $5.4 \times 10^{-11} J$

D.  $6.4 \times 10^{-11} J$

**Answer: D**



**Watch Video Solution**



5. An n-type semiconductor has impurity level  $20meV$  below the conduction band. In a thermal collision, transferable energy is  $KT$ . The value of  $T$  for which electrons start to jump in conduction band is :

A. 232 K

B. 348 K

C. 400 K

D. 600 K

**Answer: A**



**Watch Video Solution**

6. Assume that the number of hole-electron pair in an intrinsic semiconductor is proportional to  $e^{-\Delta E/2kT}$ . Here  $\Delta E$  = energy gap and  $k = 8.62 \times 10^{-5} eV / \text{kelvin}$

The energy gap for silicon is  $1.1 eV$ . The ratio of electron hole pairs at  $300K$  and  $400K$  is :

A.  $e^{-5.31}$

B.  $e^{-5}$

C.  $e$


D.  $e^2$

**Answer: A**



**Watch Video Solution**

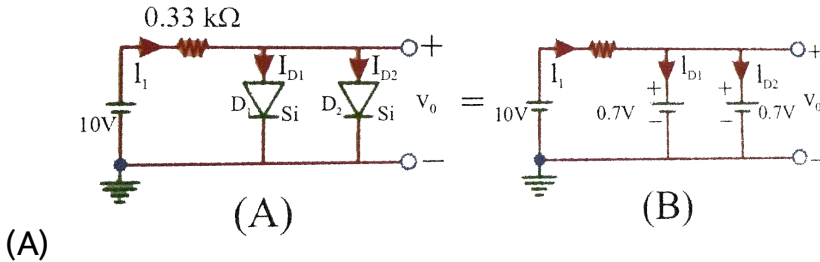7. In the circuit shown in figure (1), the  $V_0$ ,  $I_1$ ,  $I_{D_1}$ , and  $I_{D_2}$  are respectively.



- A.  $0.5\text{V}$ ,  $25\text{mA}$ ,  $15\text{mA}$
- B.  $0.7\text{V}$ ,  $28\text{mA}$ ,  $14.09\text{mA}$
- C.  $0.4\text{V}$ ,  $15\text{mA}$ ,  $20\text{mA}$
- D.  $0.3\text{V}$ ,  $15.06\text{mA}$ ,  $20.18\text{mA}$

**Answer: B**

 [Watch Video Solution](#)

8. For a junction diode, the ratio of forward current ( $I_f$ ) and reverse current is.

[ $I_e$  = electronic charge,

$V$  = voltage applied across junction,

$k$  = Boltzmann constant

$T$  = temperature in kelvin].

A.  $e^{-v/kT}$

B.  $e^{V/kT}$

C.  $\left(e^{eV/kT}\right)$



D.  $\left(e^{V/kT} - 1\right)$

**Answer: C**




**Watch Video Solution**

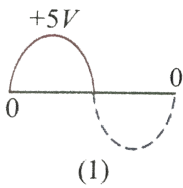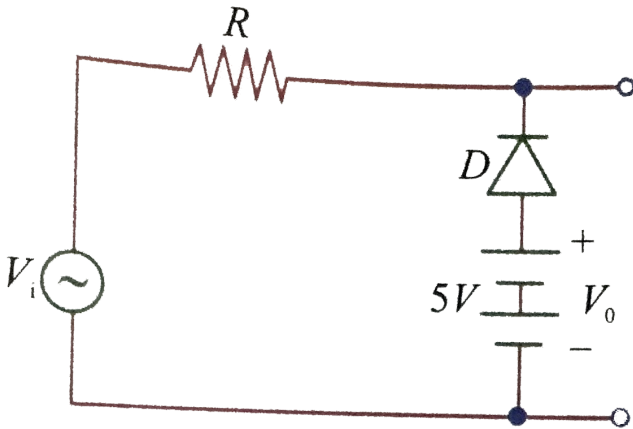
9. In the diagram  $D$  an ideal diode and an alternating voltage of peak value  $10V$  is connected as input  $V_1$ . Which of the following diagram represents the correct wavelength of output voltage  $V_0$  ?




A.

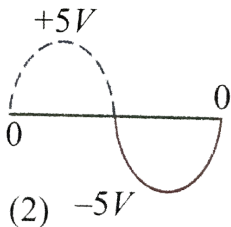

B.

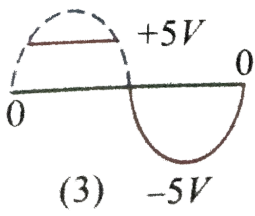

C.

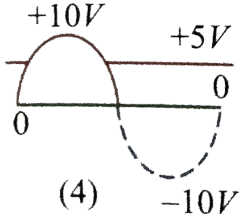

D.

**Answer: D**

 [Watch Video Solution](#)

**10.** For a *CE*-transistor amplifier, the audio signal voltage across the collector resistance of  $2k\Omega$  is  $2V$ . Suppose the current amplification factor of the transistor is 100. Find the input signal voltage and base current, if the base resistance is  $1k\Omega$ .

A.  $0.02V$

B.  $0.01V$

C.  $0.03V$

D.  $0.04V$


**Answer: B**



**Watch Video Solution**

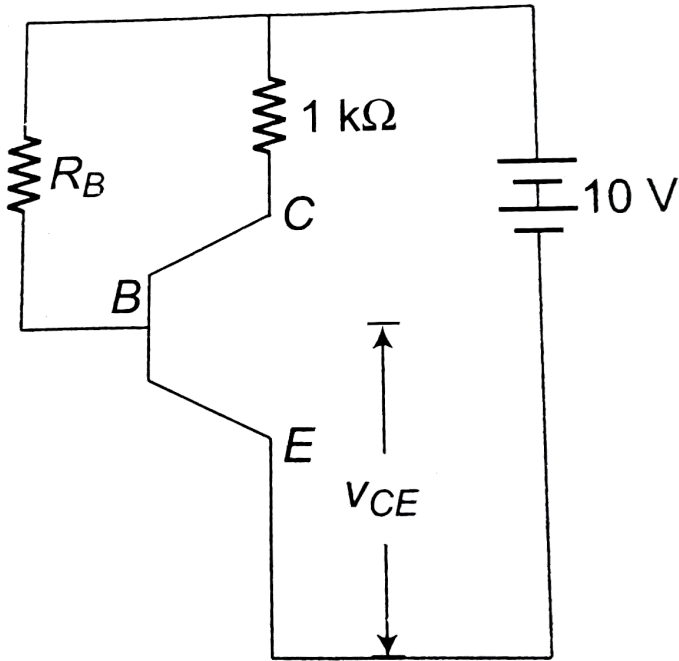**11.** In the circuit shown here the transistor used has a current gain  $\beta = 100$ . What should be the bias resistor  $R_{BE}$  so that

$$V_{CE} = 5V \text{ (neglect } V_{BE})$$



- A.  $200\text{ k}\Omega$
- B.  $1\text{ k}\Omega$
- C.  $500\text{ k}\Omega$
- D.  $2\text{ k}\Omega$

**Answer: A**



Watch Video Solution



12. An n - p- n transistor is connected in common - emitter configuration in which collector supply is 8 V and the voltage drop across the load resistance of  $800\Omega$  connected in the collector circuit is 0.8 V . If current amplification factor is 25 , determine collector - emitter voltage and base current . If the internal resistance of the transistor is  $200\Omega$  , calculate the voltage gain and the power gain.

A.  $5.2V$ , 1.86, 3

B.  $6.2V$ , 186, 5.5

C.  $7.2V$ , 3.86, 3.698

D.  $8.2V$ , 4.91, 3.15


**Answer: C**

13. For a  $CE$  transistor amplifier, the audio signal voltage across the collector resistance of  $2k\Omega$  is  $2V$ . Suppose the current amplification factor of the transistor is 100. The value of  $R_B$  in series with  $V_{BB}$  supply of  $2V$ , if the  $DC$  base current has to be 10 times the signal current is.

- A.  $4k\Omega$
- B.  $14k\Omega$
- C.  $28k\Omega$
- D.  $54k\Omega$

**Answer: B**

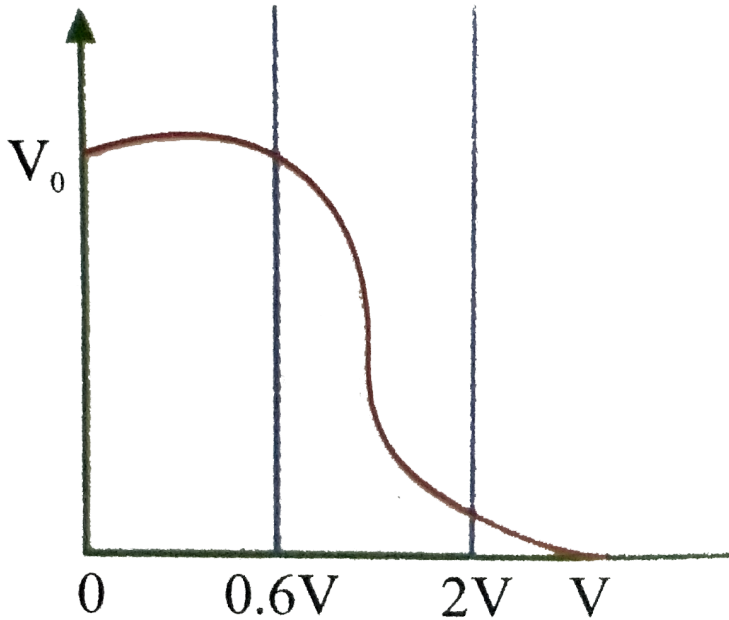14. Figure shows the transfer characteristics of a base biased  $CE$  transistor. Which of the following statements are true ?



- (A) At  $V_1 = 0.14V$  transistors is in active state
- (B) At  $V_1 = 1V$  it can be used as an amplifier
- (C) At  $V_1 = 0.5V$ , it can be used as a switch turned off
- (D) At  $V_1 = 2.5V$ , it can be used as switch turned on

A.  $A, B, C$

B.  $B, C, D$


C.  $A, C, D$

D.  $A, B, D$

Answer: B

 Watch Video Solution

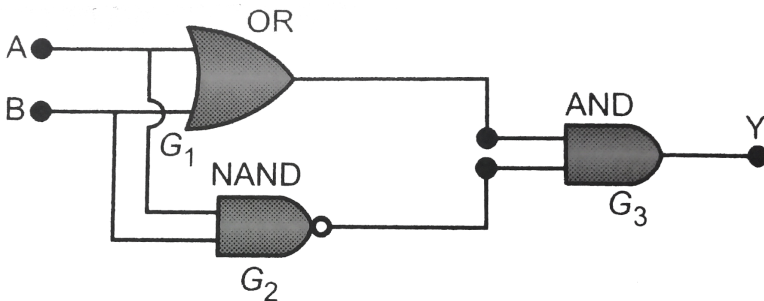15. The following configuration of gate is equivalent to



A.  $NAND$  gate

B.  $XOR$  gate


C.  $OR$  gate

D. *NOR* gate

Answer: B

 Watch Video Solution

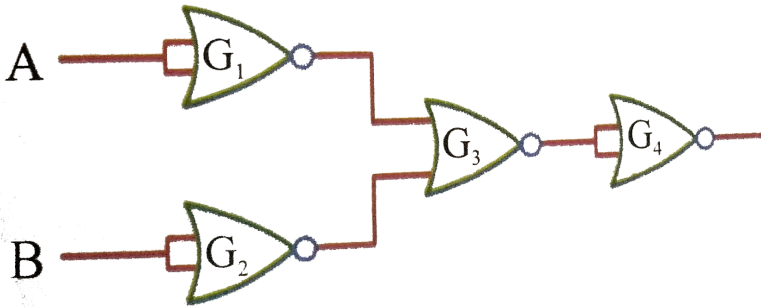16. The combination of the gates shown below produces



A. *AND* gate

B. *XOR* gate


C. *NOR* gate

D. *NAND* gate

Answer: D

 Watch Video Solution

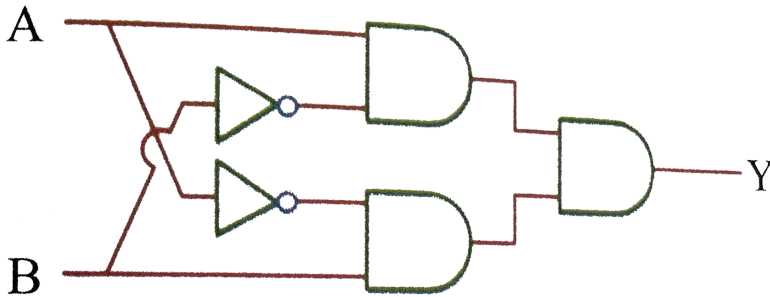17. Which of the following truth tables is true ?



- |    | A | B | Y |
|----|---|---|---|
|    | 0 | 0 | 0 |
| A. | 1 | 0 | 0 |
|    | 0 | 1 | 0 |
|    | 1 | 1 | 0 |
- 
- |    | A | B | Y |
|----|---|---|---|
|    | 0 | 0 | 0 |
| B. | 1 | 0 | 0 |
|    | 0 | 1 | 1 |
|    | 1 | 1 | 1 |

A B Y

0 0 0

C. 1 0 1

0 1 1

1 1 1

A B Y

0 0 0

D. 1 0 1

0 1 1


1 1 0

Answer: A



Watch Video Solution

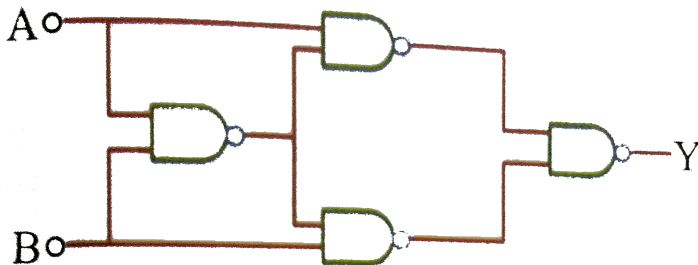18. Truth table for system of four *NAND* gates as shown in figure is :



*A B Y*

0 0 0

A. 0 1 1

1 0 1

1 1 0

*A B Y*

0 0 0

B. 0 1 0

1 0 1

1 1 1

*A B Y*

0 0 1

C. 0 1 1

1 0 0

1 1 0

*A B Y*

0 0 1

D. 0 1 0

1 0 0

1 1 1







**Answer: A**



**Watch Video Solution**



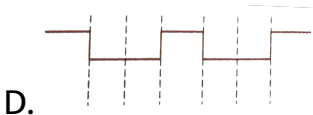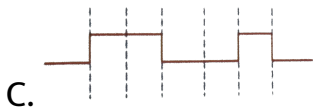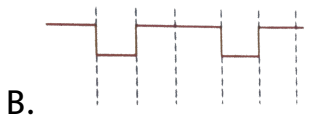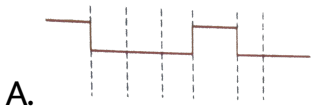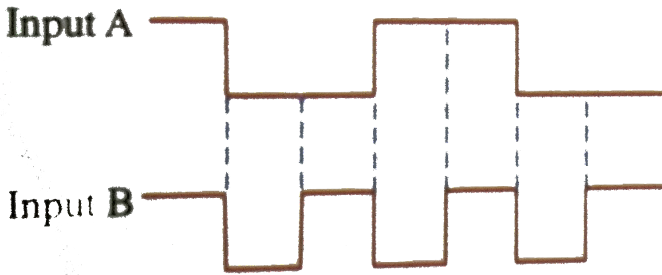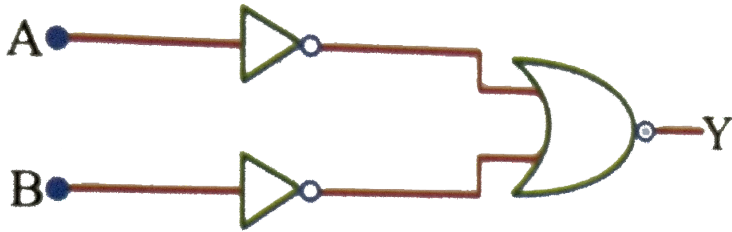19. The logic circuit shown below has the input waveforms 'A' and 'B' as shown. Pick out the correct output waveform




Answer: A



Watch Video Solution

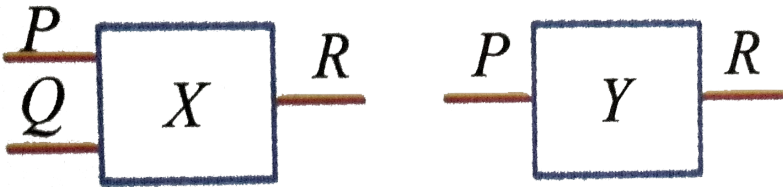20. Logic gates  $X$  and  $Y$  have the truth tables shown below



$P$	$Q$	$R$	$P$	$R$
0	0	0	0	1
1	0	0	1	0
0	1	0		
1	1	1		

When the output of  $X$  is connected to the input of  $Y$ , the resulting combination is equivalent to a single.

A. *NOT* gate

B. *OR* gate

C. *NOR* gate

D. *NAND* gate

**Answer: D**

 [Watch Video Solution](#)

### Ncert Comprehension

1. A block of pure silicon at  $300K$  has a length of  $10cm$  and an area of  $1.0cm^2$ . A battery of emf  $2V$  is connected across it. The mobility of electron is  $0.14m^2v^{-1}S^{-1}$  and their number density is  $1.5 \times 10^{16}m^{-3}$ . The mobility of holes is  $0.05m^2v^{-1}S^{-1}$ .

The electron current is

A.  $6.72 \times 10^{-4} A$

B.  $6.72 \times 10^{-5} A$

C.  $6.72 \times 10^{-6} A$

D.  $6.72 \times 10^{-7} A$

**Answer: D**



**Watch Video Solution**

2. A block of pure silicon at  $300K$  has a length of  $10cm$  and an area of  $1.0cm^2$ . A battery of emf  $2V$  is connected across it. The mobility of electron is  $0.14m^2v^{-1}S^{-1}$  and their number density is  $1.5 \times 10^{16}m^{-3}$ . The mobility of holes is  $0.05m^2v^{-1}S^{-1}$ .

The hole current is

A.  $2.0 \times 10^{-7} A$

B.  $2.2 \times 10^{-7} A$

C.  $2.4 \times 10^{-7} A$

D. 2.6

**Answer: C**



**Watch Video Solution**

3. A block of pure silicon at  $300K$  has a length of  $10cm$  and an area of  $1.0cm^2$ . A battery of emf  $2V$  is connected across it. The mobility of electron is  $0.14m^2v^{-1}S^{-1}$  and their number density is  $1.5 \times 10^{16}m^{-3}$ . The mobility of holes is  $0.05m^2v^{-1}S^{-1}$ .

The total current in the block is

A.  $2.4 \times 10^{-7} A$

B.  $6.72 \times 10^{-7} A$

C.  $4.32 \times 10^{-7} A$

D.  $9.12 \times 10^{-7} A$

**Answer: D**



**Watch Video Solution**

4. The input and output resistances in a common base amplifier circuits are  $400\Omega$  and  $400K\Omega$  respectively. The emitter current is  $2mA$  and current gain is 0.98.

The collector current is

A.  $1.84mA$

B.  $1.96mA$

C.  $1.2mA$

D.  $2.04mA$

**Answer: B**



[Watch Video Solution](#)

5. The input and output resistances in a common base amplifier circuits are  $400\Omega$  and  $400K\Omega$  respectively. The emitter current is  $2mA$  and current gain is 0.98.

The base current is

A.  $0.012mA$

B.  $0.022mA$

C.  $0.032mA$

D.  $0.042mA$

**Answer: D**



**Watch Video Solution**

6. The input and output resistances in a common base amplifier circuits are  $400\Omega$  and  $400K\Omega$  respectively. The emitter current is  $2mA$  and current gain is 0.98.

Voltage gain of transistor is

A. 960

B. 970

C. 980

D. 990

**Answer: C**



**Watch Video Solution**



7. The input and output resistances in a common base amplifier circuits are  $400\Omega$  and  $400K\Omega$  respectively. The emitter current is  $2mA$  and current gain is 0.98.

Power gain of transistor is

A. 950

B. 960

C. 970


D. 980

**Answer: B**



[Watch Video Solution](#)

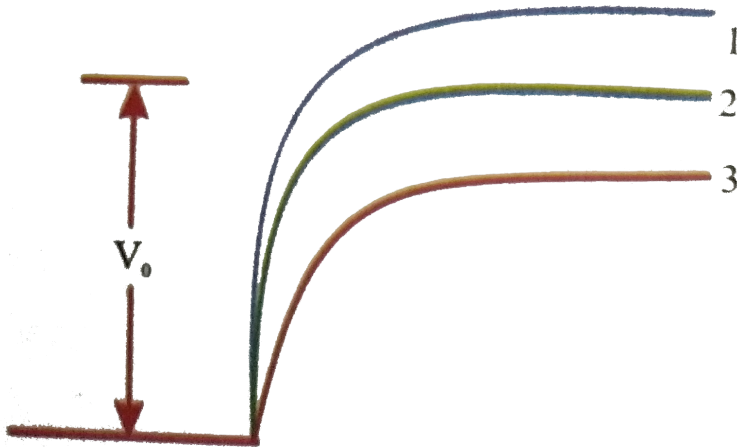8. In Fig.  $V_0$  is the potential barrier across a  $p - n$  junction, when no battery is connected across the junction :



A. 1 and 3 both correspond is forward bias of junction

B. 3 corresponds to forward bias of junction and 1 corresponds to reverse bias junction


C. 1 corresponds to forward bias and 3 corresponds to reverse bias junction

D. 3 and 1 both correspond to reverse bias and 3 corresponds to reverse bias of junction

**Answer: B**

 [Watch Video Solution](#)

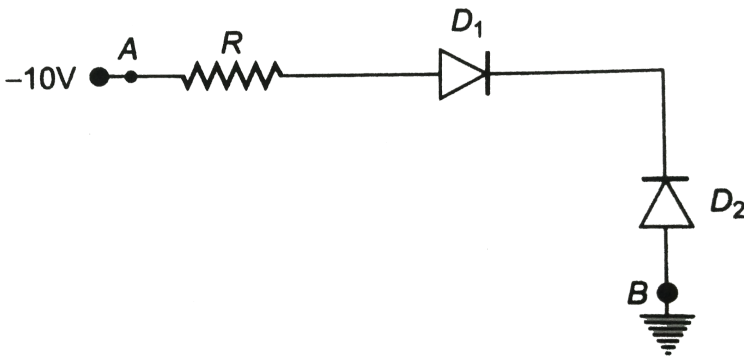9. In figure , assuming the diodes to be ideal ,



A.  $D_1$  is forward biased and  $D_2$  is reverse biased and hence current flows from  $A$  to  $B$


- B.  $D_2$  is forward biased and  $D_1$  is reverse biased and hence no current flows from  $B$  to  $A$  and vice versa
- C.  $D_1$  and  $D_2$  are both forward biased and hence current flows from  $A$  to  $B$
- D.  $D_1$  and  $D_2$  are both reverse biased and hence no current flows from  $A$  and  $B$  and vice-versa.

**Answer: B**




[Watch Video Solution](#)

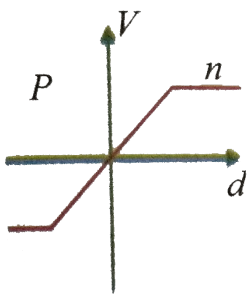
**10.** The correct curve between potential ( $V$ ) and distance ( $d$ ) near  $p - n$  junction is.




A.

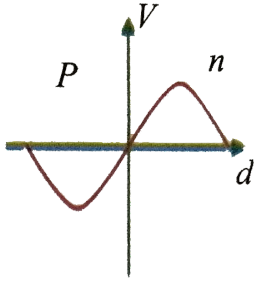

B.

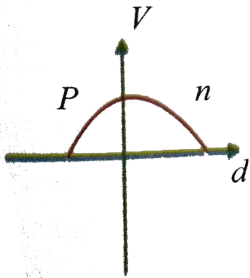

C.

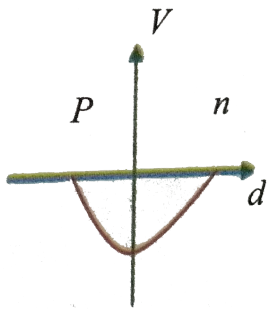


D.

**Answer: A**



Watch Video Solution

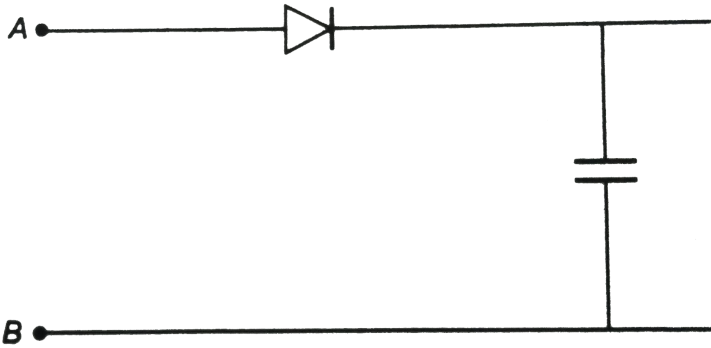
11. A 220 V AC supply is connected between points A and B .  
What will be the potential difference  $V$  across the capacitor ?



- A. 220 V
- B. 110 V
- C. 0 V
- D. 220 V

**Answer: D**

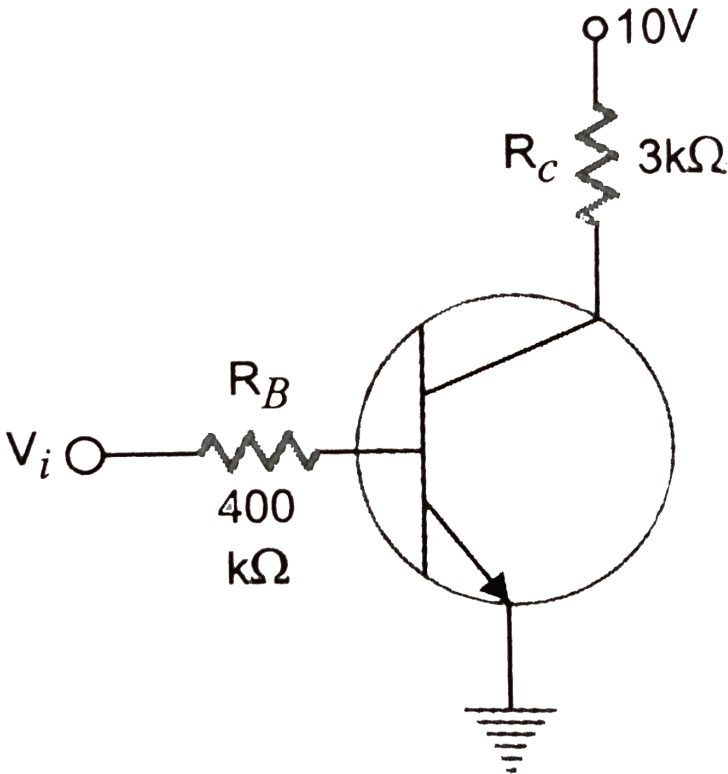12. In the circuit shown in Fig. when the input voltage of the base resistance is  $10V$ ,  $V_{be}$  is zero and  $V_{ce}$  is also zero. Find the values of  $I_B$ ,  $I_C$  and  $\beta$ .



A.  $25\mu A$ ,  $3.33mA$

B.  $20\mu A$ ,  $3.33mA$

C.  $20\mu A$ ,  $1.33mA$

D.  $25\mu A$ , *zero*

**Answer: A**



**Watch Video Solution**

**13.** In the above problem the current amplification factor  $\beta$  is

A. 83

B. 100

C. 133

D. 203

**Answer: C**





Watch Video Solution

Level I H W

1. The electrical conductivity of a semiconductor increases when electromagnetic radiation of wavelength shorter than  $1240nm$  is incident on it. The forbidden band energy for the semi conductor is (in eV).

A. 0.5

B. 0.97

C. 0.7

D. 1.1

**Answer: B**

 [Watch Video Solution](#)

2. A semiconductor is known to have an electron concentration of  $5 \times 10^{13} / \text{cm}^3$  and hole concentration of  $8 \times 10^{12} / \text{cm}^3$ .

The semiconductor is

- A. n-type
- B. p-type
- C. intrinsic
- D. insulator

**Answer: A**

 [Watch Video Solution](#)

3. A potential barrier of  $0.50V$  exists a  $p - n$  junction. If the width of depletion layer is  $10^6m$ , then intensity of electric field in this region will be

A.  $1 \times 10^6V / m$

B.  $5 \times 10^5V / m$

C.  $4 \times 10^4V / m$

D.  $2 \times 10^6V / m$

**Answer: B**



[Watch Video Solution](#)

4. A  $p - n$  junction diode has breakdown voltage of  $28V$ . If applied external in reverse bias is  $40V$  the current through it is

- A. Zero
- B. infinite
- C. 10A
- D. 15A

**Answer: B**

 [Watch Video Solution](#)

5. The value of current in the following diagram is (diode assumed to be ideal one)



- A. 0.1amp
- B. 0.01amp

C.  $1\text{amp}$

D. zero

**Answer: D**



**Watch Video Solution**

6. A half-wave rectifier is used to convert  $50\text{Hz}$  A.C. to D.C voltage. The number of pulses per second in the rectified voltage are

A. 50

B. 25

C. 100

D. 75

**Answer: A**



**Watch Video Solution**

7. If a full wave rectifier circuit is operating from  $50Hz$  mains, the fundamental frequency in the ripple will be

A.  $25Hz$

B.  $50Hz$

C.  $70.7Hz$

D.  $100Hz$

**Answer: D**



**Watch Video Solution**

8. In an  $npn$  transistor the base the collector currents are  $100\mu A$  and  $9\mu A$  respectively. Then the emitter current will be

- A.  $9.1mA$
- B.  $18.2mA$
- C.  $3.91mA$
- D.  $18.2\mu A$

**Answer: A**



[Watch Video Solution](#)

9. A change of  $8mA$  in the emitter current brings a change of  $7.9mA$  in the collector current. The change in base current required to have the same change in the collector is

A.  $0.01mA$

B.  $1A$

C.  $10mA$

D.  $0.1mA$

**Answer: D**



**Watch Video Solution**

**10.** For a  $p - n - p$  transistor in  $CB$  configuration, the emitter current  $I_E$  is  $1mA$  and  $\alpha = 0.95$ . The base current and collector current are

A.  $0.95, A, 0.05mA$

B.  $0.05mA, 0.95mA$



C.  $9.5, A, 0.5mA$

D.  $0.5mA, 9.5mA$

**Answer: B**



[Watch Video Solution](#)

11. If a change of  $100\mu A$  in the base current of an  $n - p - n$  transistor in  $CE$  causes a change of  $10mA$  in the collector current, the  $ac$  current gain of the transistor is

A. 10

B. 100

C. 1000

D. 10000

**Answer: B**



**Watch Video Solution**

12. For a common emitter amplifier, current gain is 70. If the emitter current is  $8.4\text{mA}$ , then the base current is

A.  $0.236\text{mA}$

B.  $0.118\text{mA}$

C.  $0.59\text{mA}$

D.  $8.3\text{mA}$

**Answer: B**



**Watch Video Solution**

13. The base current of a transistor is  $105\mu A$  and the collector current is  $2.05mA$ . Then  $\beta$  of the transistor is

- A. 1.952
- B. 19.52
- C. 195.2
- D. 1952

**Answer: A**



[Watch Video Solution](#)

14. For a transistor the value of  $\alpha$  is 0.9.  $\beta$  value is

- A. 9
- B. 0.9

C. 0.09

D. 90

**Answer: C**



**Watch Video Solution**

**15.** For a transistor the current amplification factor is 0.8 The transistor is connected in common emitter configuration, the change in collector current when the base current changes by  $6mA$  is

A.  $6mA$

B.  $4.8mA$

C.  $24mA$

D.  $8mA$

**Answer: C**



**Watch Video Solution**

**16.** A change of  $400mV$  in base-emitter voltage causes a change of  $200\mu A$  in the base current. The input resistance of the transistor is

A.  $1K\Omega$

B.  $6K\Omega$

C.  $2K\Omega$

D.  $8K\Omega$

**Answer: C**



**Watch Video Solution**

17. In a common base circuit, if the collector base voltage is changed by  $0.6V$ , collector current changes by  $0.02mA$ . The output resistance will be

A.  $10^4\Omega$

B.  $2 \times 10^4\Omega$

C.  $3 \times 10^4\Omega$

D.  $4 \times 10^4\Omega$

**Answer: C**



**Watch Video Solution**

18. A common emitter transistor amplifier has a current gain of 50. If the load resistance is  $4k\Omega$ , and input resistance is  $500\Omega$ ,

the voltage gain of amplifier is.

A. 100

B. 200

C. 300

D. 400

**Answer: D**



**Watch Video Solution**

**19.** Equivalent of decimal number 8 in the binary number is

A. 10

B. 101

C. 1000

D. 1011

**Answer: C**



**Watch Video Solution**

20. The equivalent of 110 in the decimal number is

A. 2

B. 4

C. 8

D. 6

**Answer: D**



**Watch Video Solution**



21. If  $A = 1, B = 0$  then the value of  $\bar{A} + B$  in terms of Boolean algebra is

A. A

B. B

C. B + A

D.  $A \cdot \bar{B}$

**Answer: B**



[Watch Video Solution](#)

22. In the Boolean algebra :  $A + B =$

A.  $\bar{A} + \bar{B}$

B.  $A \cdot B$

c.  $\overline{\overline{A}} + \overline{\overline{B}}$

d.  $\overline{\overline{A}} + \overline{\overline{B}}$

**Answer: C**



**Watch Video Solution**

**23.** The following one represents logic addition is

A.  $1 + 1 = 2$

B.  $1 + 1 = 10$

C.  $1 + 1 = 1$

D.  $1 + 1 = 11$

**Answer: C**



**Watch Video Solution**

24. In the Boolean algebra :  $\overline{A} \cdot \overline{B} = \dots$

A.  $\overline{A + B}$

B.  $A \cdot B$

C.  $\overline{\overline{A + B}}$

D.  $A + B$

**Answer: A**



[Watch Video Solution](#)

25. In the Boolean algebra, which gate is expressed as

$$Y = \overline{A + B}.$$

A. *OR*

B. *NAND*

C. *AND*

D. *NOR*

**Answer: D**



**Watch Video Solution**

**26.** The truth table for *NOT* gate is.

A.  $\begin{bmatrix} 1 & 1 \\ 0 & 0 \end{bmatrix}$

B.  $\begin{bmatrix} 1 & 0 \\ 0 & 0 \end{bmatrix}$

C.  $\begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}$

D.  $\begin{bmatrix} 0 & 1 \\ 1 & 1 \end{bmatrix}$


**Answer: C**



Watch Video Solution

Level II H W

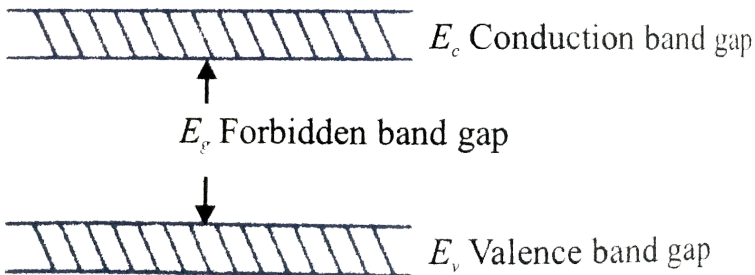1. If the lattice constant of this semiconductor is decreased, then which of the following is correct ?



- A. All  $E_c$ ,  $E_g$  &  $E_v$  decrease
- B. All  $E_c$ ,  $E_g$  &  $E_v$  increase
- C.  $E_c$  and  $E_v$  increase, but  $E_g$  decrease
- D.  $E_c$  and  $E_v$  decrease but  $E_g$  increase

**Answer: D**



**Watch Video Solution**

2. A *Ge* specimen is dopped with *Al*. The concentration of acceptor atoms is  $\sim 10^{21} \text{ atoms}/\text{m}^3$ . Given that the intrinsic concentration of electron hole pairs is  $\sim 10^{19}/\text{m}^3$ , the concentration of electron in the speciman is

A.  $10^{17}/\text{m}^3$

B.  $10^{15}/\text{m}^3$

C.  $10^4/\text{m}^3$

D.  $10^2/\text{m}^3$

**Answer: A**



**Watch Video Solution**

3. The following data are for intrinsic germanium at  $300K$ .  $n_i = 2.4 \times 10^{19} / m^3$ ,  $\mu_e = 0.39m^2 / Vs$ ,  $\mu_h = 0.19m^2 / Vs$ . Calculate the conductivity of intrinsic germanium.

A.  $4.3Sm^{-1}$

B.  $1.21Sm^{-1}$

C.  $2.22Sm^{-1}$





D.  $4.22Sm^{-1}$

**Answer: C**



**Watch Video Solution**

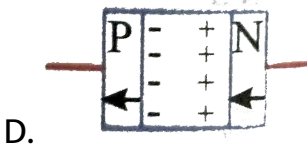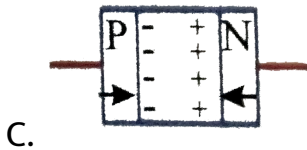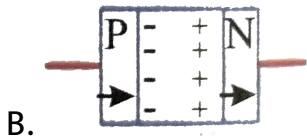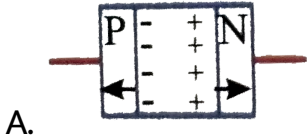4. The diagram correctly represents the direction of flow of charge carriers in the forward bias of  $p - n$  junction is.





Answer: C



Watch Video Solution



5. In the figure shown below

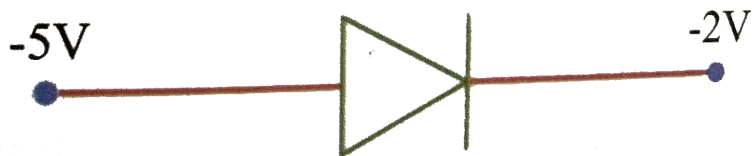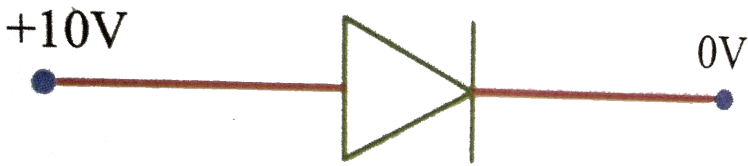

- A. In both Fig *a* and Fig *b* the diodes are forward biased
- B. In both Fig, *a* and Fig *b* the diodes are reverse biased
- C. In Fig *a* the diode is forward biased and in Fig *b*, the diode is reverse biased
- D. In Fig *a* the diode is reverse biased and in Fig *b*, it is forward biased

Answer: C



Watch Video Solution

6. A  $P - N$  junction diode can withstand currents up to  $10\text{mA}$ . Under forward bias, The diode has a potential drop of  $0.5\text{V}$  across it which is assumed to be independent of current. The maximum voltage of the battery used to forward bias the diode when a resistance of  $200\Omega$  is connected in series with it is

A.  $2.5\text{V}$

B.  $2.6\text{V}$

C.  $2.7\text{V}$

D.  $2.8\text{V}$

**Answer: A**



**Watch Video Solution**

7. A cell of emf.  $4.5V$  is connected to a junction diode whose barrier potential is  $0.7V$ . If the external resistance in the circuit is  $190\Omega$ . The current in the circuit is

A.  $20mA$

B.  $2mA$

C.  $23mA$


D.  $200mA$

**Answer: A**



**Watch Video Solution**

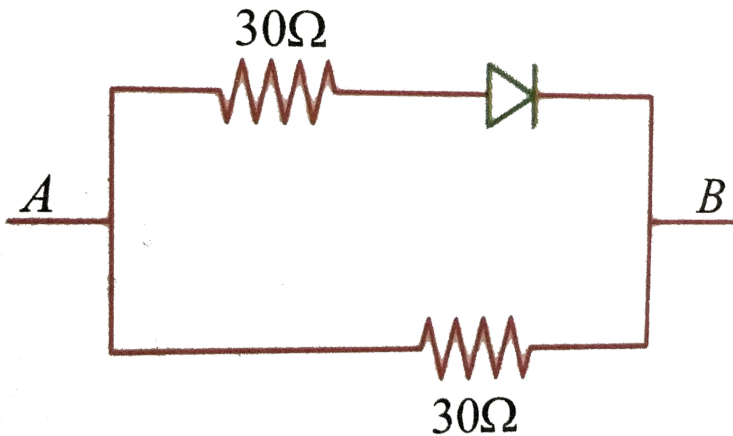8.  $V_A$  and  $V_B$  denote potential of  $A$  and  $B$ , then the equivalent resistance between  $A$  and  $B$  in the adjoining circuit is (ideal diode).




- A.  $15\Omega$  if  $V_A > V_B$
- B.  $30\Omega$  if  $V_A < V_B$
- C. both 1 and 2
- D. neither 1 nor 2

**Answer: C**



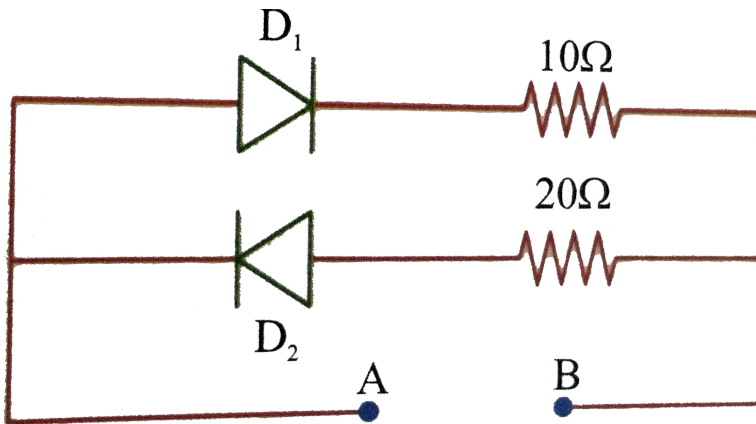9. Two ideal junction diodes  $D_1$ ,  $D_2$  are connected as shown in the figure. A  $3V$  battery is connected between  $A$  and  $B$ . The current supplied by the battery if its positive terminal is connected to  $A$  is



A.  $0.1A$

B.  $0.3A$


C.  $0.9A$

D.  $90A$

Answer: B

 Watch Video Solution

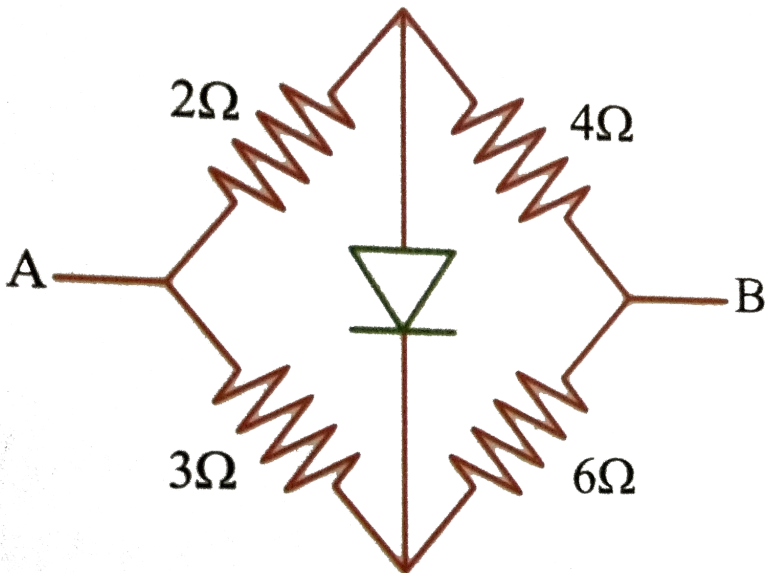10. Find the effective resistance between  $A$  and  $B$



A.  $5/18\Omega$

B.  $9/5\Omega$

C.  $18/5\Omega$

D.  $5/9\Omega$

**Answer: C**



[Watch Video Solution](#)

11. The peak voltage in the output of a half-wave diode rectifier fed with a sinusoidal signal without filter is  $10V$ . The *dc* component of the output voltage is

A.  $10/\sqrt{2}V$

B.  $10/\pi V$


C.  $10V$

D.  $20/\pi V$

**Answer: B**

 [Watch Video Solution](#)

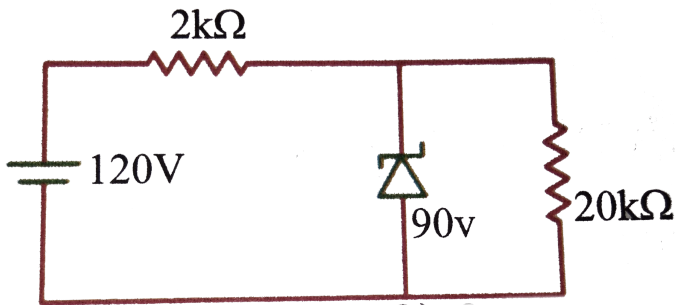12. In the figure shown the potential drop across the series resistor is



A. 30 V

B. 60 V

C. 90 V




D. 120 V

**Answer: A**

 [Watch Video Solution](#)

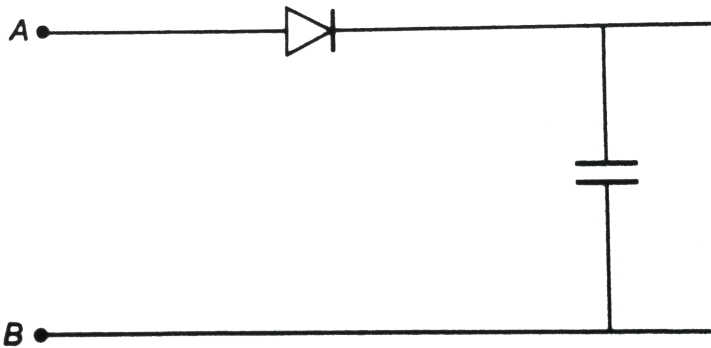13. A 220 V AC supply is connected between points A and B .

What will be the potential difference V across the capacitor ?



A. 200 V

B. 110 V

C. 0 V


D.  $220\sqrt{2}V$

**Answer: D**



**Watch Video Solution**

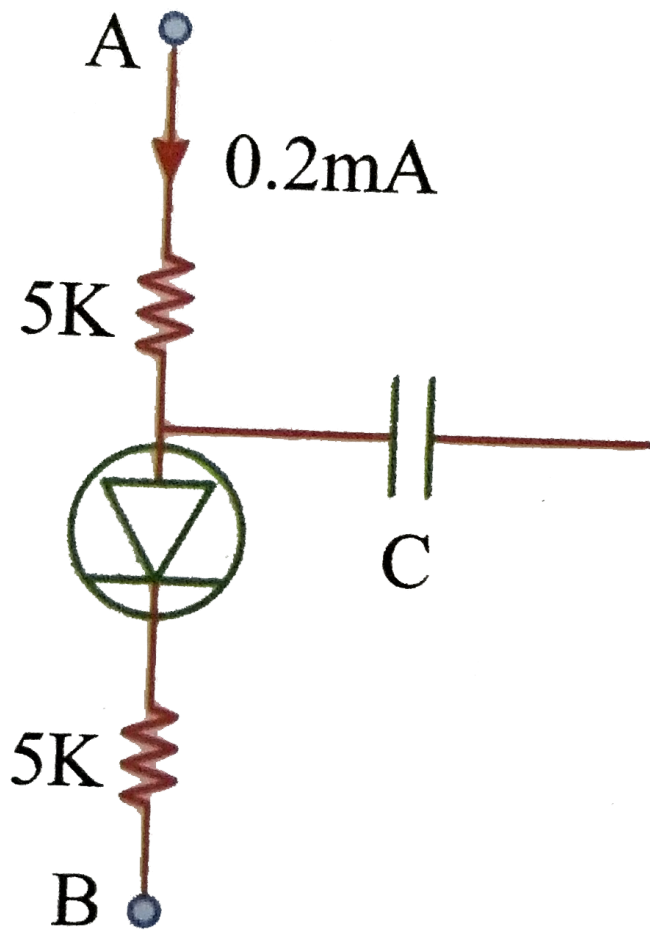**14.** In the circuit shown(Fig.) if the diode forward voltage drop is  $0.3V$ , the voltage difference between  $A$  and  $B$  is :



- A.  $1.3\text{V}$
- B.  $2.3\text{V}$
- C.  $0$
- D.  $0.5\text{V}$

**Answer: B**



[Watch Video Solution](#)

15. In an n-p-n transistor  $10^{10}$  electrons enter the emitter in  $10^{-6}$ s. If 2% of the electrons are lost in the base, find the current transfer ratio and the current amplification factor.

A. 0.98, 49

B. 0.49, 49

C. 0.98, 98

D. 0.49, 98

**Answer: A**



[Watch Video Solution](#)

16. In a common base mode of transistor, collector current is  $5.488\text{mA}$  for an emitter current of  $5.60\text{mA}$ . The value of the base current amplification factor ( $\beta$ ) will be :

A. 48

B. 49

C. 50

D. 51

**Answer: B**



[Watch Video Solution](#)

17. Current amplification factor of a common base configuration is 0.88. Find the value of base current when the

emitter current is  $1\text{mA}$ .

A.  $0.12\text{mA}$

B.  $0.1\text{mA}$

C.  $0.5\text{mA}$

D.  $0.2\text{mA}$

**Answer: A**



[Watch Video Solution](#)

**18.** For a transistor  $\beta = 40$  and  $I_B = 25\mu\text{A}$ . Find the value of  $I_E$ .

A.  $1\text{mA}$

B.  $1.025\text{mA}$

C. 2 mA

D.  $1.2\text{mA}$

**Answer: B**



**Watch Video Solution**

**19.** In a transistor if  $\frac{I_C}{I_E} = \alpha$  and  $\frac{I_C}{I_B} = \beta$ , if  $\alpha$  varies between  $\frac{20}{21}$  and  $\frac{100}{101}$ , then the value of  $\beta$  lies between.

A. 1 – 10

B. 0.95 – 0.99

C. 20 – 100

D. 200 – 300

**Answer: C**



Watch Video Solution

20. For a transistor  $x = \frac{1}{\alpha}$  &  $y = \frac{1}{\beta}$  where  $\alpha$  &  $\beta$  are current gains in common base and common emitter configuration.

Then

A.  $x + y = 1$

B.  $x - y = 1$

C.  $2x = 1 - y$

D.  $x + y = 0$

**Answer: B**



Watch Video Solution



21. A voltage amplifier operated from a 12 volt battery has a collector load  $6k\Omega$ . Calculate the maximum collector current in the circuit.

A.  $0.5mA$

B.  $1mA$

C.  $3mA$

D.  $2mA$

**Answer: D**



[Watch Video Solution](#)

22. A  $CE$  amplifier is designed with a transistor having  $\alpha = 0.99$ . Input impedance is  $1k\Omega$  and load is  $10k\Omega$ . Voltage

gain will be :

A. 9900

B. 99000

C. 99

D. 990

**Answer: D**



[Watch Video Solution](#)

**23.** In a common emitter amplifier the load resistance of the output circuit is 792 times the resistance of the input circuit. If  $\alpha = 0.99$ . The voltage gain is.

A. 79200

B. 39600

C. 7920

D. 3960

**Answer: A**



**Watch Video Solution**

**24.** In a transistor amplifier  $\beta = 62$ ,  $R_L = 5000\Omega$  and internal resistance of the transistor is  $500\Omega$ . Its power amplification will be.

A. 25580

B. 33760

C. 38440

D. 55760

**Answer: C**



**Watch Video Solution**

**25.** The tuned collector oscillator circuit used in the local oscillator of a ratio receiver makes use of a tuned circuit with  $L = 60\mu H$  and  $C = 400pE$ . Calculate the frequency of oscillations.

A.  $1.03KHz$

B.  $1.03Hz$

C.  $1.03GHz$

D.  $1.03MHz$

**Answer: D**



[Watch Video Solution](#)

**26.** When we add binary number 111 and 111 we get the binary number :

- A. 222
- B. 1000
- C. 1110
- D. 000

**Answer: C**



[Watch Video Solution](#)

27. If  $A = B = C = 1$  and  $X = \overline{ABC} + \overline{BBC} + \overline{CAB}$ , then

$X =$

A. 0

B. 1

C. 100

D. 110

**Answer: A**



[Watch Video Solution](#)

28. The input of  $A$  and  $B$  for the Boolean expression

$$(\overline{A + B}) \cdot (\overline{A \cdot B}) = 1 \text{ is.}$$

A. 0, 0

B. 0, 1

C. 1, 0


D. 1, 1

**Answer: A**



**Watch Video Solution**

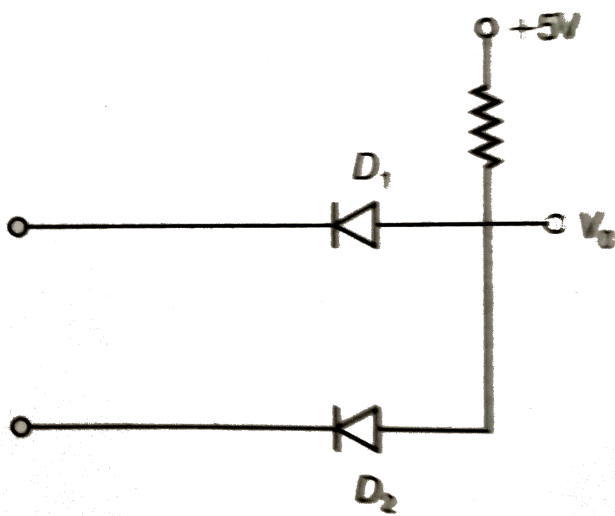**29.** Write the truth table for the circuit shown in figure given below. Name the gate that the circuit resembles.



A. *AND* gate

B. *OR* gate

C. *NOR* gate

D. *XOR* gate


**Answer: A**



**Watch Video Solution**



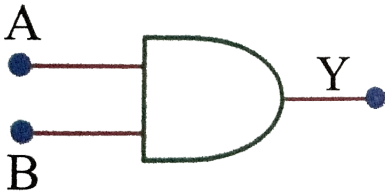30. Consider a two-input *AND* gate of figure below. Out of the four entries for the Truth Table given here, the correct ones are.



	Input		Output
	A	B	Y
1	0	1	0
2	1	0	0
3	1	1	1
4	0	0	1

- A. All
- B. 1 and 2 only
- C. 1, 2 and 3 only
- D. 1, 3 and 4 only

**Answer: C**

 [Watch Video Solution](#)

31. A Truth table is given below. The below. The logic gate having following truth table is.

$A$	$B$	$Y$
0	0	1
1	0	0
0	1	0
1	1	0

A. *NAND* gate

B. *NOR* gate

C. *AND* gate


D. *OR* gate

**Answer: B**



**Watch Video Solution**

32. For a logic 0101 the waveform is.

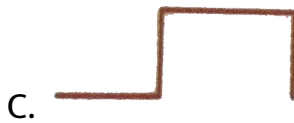


Answer: A



Watch Video Solution

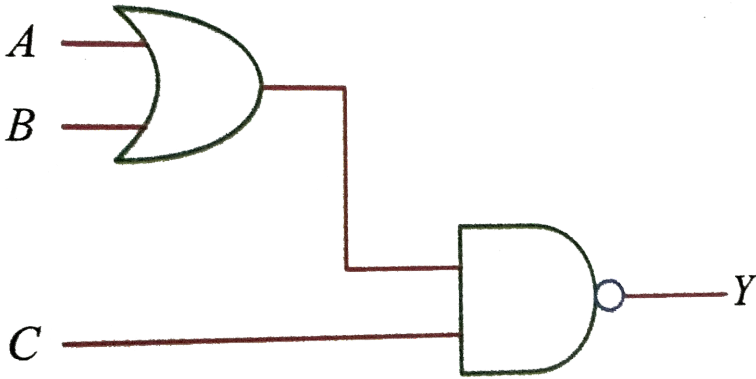33. For the given combination of gates, if the logic states of inputs  $A, B, C$  are as follows  $A = B = C = 0$  and

$A = B = 1, C = 0$  then the logic states of output  $D$  are



A. 0, 0

B. 0, 1

C. 1, 0


D. 1, 1

**Answer: D**



**Watch Video Solution**

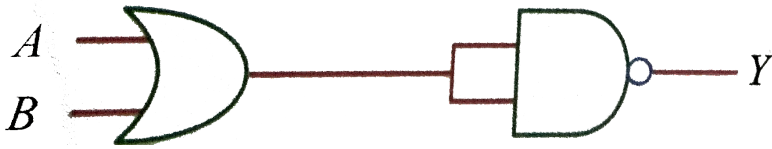34. Identify the gate represented by the block diagram as shown in fig.




- A. *AND* gate
- B. *NOT* gate
- C. *NAND* gate
- D. *NOR* gate

**Answer: D**



**Watch Video Solution**

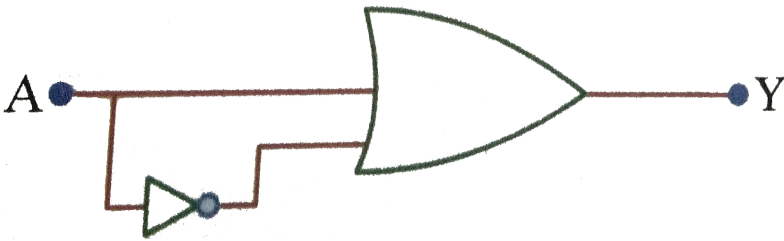35. The Boolean expression for the gate circuit shown below is



A.  $A + \bar{A} = 1$

B.  $A + 1 = 1$

C.  $A + A = A$


D.  $A + 0 = A$

**Answer: A**



**Watch Video Solution**

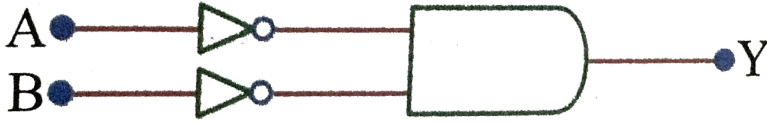36. The output  $Y$  of the gate circuit shown in the figure below is



A.  $\overline{A} \cdot \overline{B}$

B.  $\overline{A} \cdot B$

C.  $\overline{\overline{A} \cdot \overline{B}}$

D.  $\overline{A} + \overline{B}$

**Answer: B**



**Watch Video Solution**