



PHYSICS

BOOKS - ZEN PHYSICS (KANNADA ENGLISH)

ELECTRICITY

Questions Section In Text Questions

1. What does an electric circuit mean?



Watch Video Solution

2. Define the unit of current.



[Watch Video Solution](#)

3. Calculate the number of electrons constituting one coulomb of c.harge. (charge on 1 electron = 1.6×10^{-19} C)



[Watch Video Solution](#)

4. Name a device that helps to maintain a potential difference across a conductor.



Watch Video Solution

5. What is meant by saying that the potential difference between two points is 1 V?



Watch Video Solution

6. How much energy is given to each coulomb of charge passing through a 6 V battery?



Watch Video Solution

7. On what factors does the resistance of a conductor depend?



Watch Video Solution

8. Will current flow more easily through a thick wire or a thin wire of the same material, when connected to the same source? Why?



Watch Video Solution

9. Let the resistance of an electrical component remain constant while the potential difference across the two ends of the component decreases to half of its former

value. What change will occur in the current through it?



Watch Video Solution

10. Why are coils of electric toasters and electric irons made of an alloy rather than a pure metal?



Watch Video Solution

11. Use the data in table 12.2 to answer the following

a] Which among iron and mercury is better conductor?

b] Which material is the best conductor?



View Text Solution

12. Draw a schematic diagram of a circuit consisting of a battery of three cells of 2 V

each, a 5Ω , 8Ω and 12Ω and a plug key, all connected in series.



[Watch Video Solution](#)

13. Redraw the circuit of question 1, putting in an ammeter to measure the current through the resistors and a voltmeter to measure potential difference across the 12Ω resistor. What would be the readings in the ammeter and the voltmeter?



[Watch Video Solution](#)

14. Judge the equivalent resistance when the following are connected in parallel

→ a. 1Ω and $10^6\Omega$. b. 1Ω and $10^3\Omega$ and $10^6\Omega$

.



Watch Video Solution

15. An electric lamp of 100Ω , a toaster of resistance 50Ω , and a water filter of resistance 500Ω are connected in parallel to a 220 V source. What is the resistance of an electric

iron connected to the same source that takes as much current as all three appliances and what is the current through it?



[Watch Video Solution](#)

16. What are the advantages of connecting electrical devices in parallel with the battery instead of connecting them in series?



[Watch Video Solution](#)

17. How can three resistors of resistances 2Ω , 3Ω and 6Ω be connected to give a total resistance of a] 4Ω . b] 1Ω ?



[Watch Video Solution](#)

18. What are [i] the highest and [ii] the lowest total resistances which can be secured by combinations of four coils of resistances 4Ω , 8Ω , 12Ω and 24Ω ?



[Watch Video Solution](#)

19. Why does the cord of an electric heater not glow while the heating element does?



Watch Video Solution

20. Compute the heat generated while transferring 96000 coulomb of charge in one hour through a potential difference of 50 V.



Watch Video Solution

21. An electric iron of resistance 20Ω takes a current of 5 A. Calculate the heat developed in 30 sec.



Watch Video Solution

22. What determines the rate at which energy is delivered by a current?



Watch Video Solution

23. An electric motor takes 5 A from a 220 V line. Determine the power of the motor and the energy consumed in 2 h.



Watch Video Solution

24. What does an electric circuit mean?



Watch Video Solution

25. Define the unit of current.



[Watch Video Solution](#)

26. Calculate the number of electrons constituting one coulomb of charge.



[Watch Video Solution](#)

27. Name a device that helps to maintain a potential difference across a conductor.



[Watch Video Solution](#)

28. What is meant by saying that the potential difference between two points is 1 V?



Watch Video Solution

29. How much energy is given to each coulomb of charge passing through a 6 V battery?



Watch Video Solution

30. On what factors does the resistance of a conductor depend?



Watch Video Solution

31. Will current flow more easily through a thick wire or a thin wire of the same material, when connected to the same source? Why?



Watch Video Solution

32. Let the resistance of an electrical component remain constant while the potential difference across the two ends of the component decreases to half of its former value. What change will occur in the current through it?



Watch Video Solution

33. Why are coils of electric toasters and electric irons made of an alloy rather than a

pure metal?



Watch Video Solution

34. Use the data in table 12.2 to answer the following

a] Which among iron and mercury is better conductor?

b] Which material is the best conductor?



View Text Solution

35. Draw a schematic diagram of a circuit consisting of a battery of three cells of 2 V each, a 5Ω , 8Ω and 12Ω and a plug key, all connected in series.



Watch Video Solution

36. Redraw the circuit of question 1, putting in an ammeter to measure the current through the resistors and a voltmeter to measure potential difference across the 12Ω resistor.

What would be the readings in the ammeter and the voltmeter?



[Watch Video Solution](#)

37. Judge the equivalent resistance when the following are connected in parallel

→ a. 1Ω and $10^6\Omega$. b. 1Ω and $10^3\Omega$ and $10^6\Omega$

.



[View Text Solution](#)

38. An electric lamp of 100Ω , a toaster of resistance 50Ω , and a water filter of resistance 500Ω are connected in parallel to a 220 V source. What is the resistance of an electric iron connected to the same source that takes as much current as all three appliances and what is the current through it?



Watch Video Solution

39. What are the advantages of connecting electrical devices in parallel with the battery instead of connecting them in series?



[View Text Solution](#)

40. How can three resistors of resistances 2Ω , 3Ω and 6Ω be connected to give a total resistance of a) 4Ω . b) 1Ω ?



[View Text Solution](#)

41. What are [i] the highest and [ii] the lowest total resistances which can be secured by combinations of four coils of resistances 4Ω , 8Ω , 12Ω and 24Ω ?



Watch Video Solution

42. Why does the cord of an electric heater not glow while the heating element does?



Watch Video Solution

43. Compute the heat generated while transferring 96000 coulomb of charge in one hour through a potential difference of 50 V.



Watch Video Solution

44. An electric iron of resistance 20Ω takes a current of 5 A. Calculate the heat developed in 30 sec.



Watch Video Solution

45. What determines the rate at which energy is delivered by a current?



Watch Video Solution

46. An electric motor takes 5 A from a 220 V line. Determine the power of the motor and the energy consumed in 2 h.



Watch Video Solution

1. A piece of wire resistance R is cut into five equal parts. These parts are then connected in parallel. If the equivalent resistance of this combination is R' then the ratio R/R' is

A. $1/25$

B. $1/5$

C. 5

D. 25

Answer: D



Watch Video Solution

2. Which of the following terms does not represent electrical power in a circuit?

A. $I^2 R$

B. IR^2

C. VI

D. V^2/R

Answer: B



Watch Video Solution

3. An electric bulb is rated 220 V and 100 W. When it is operated on 110 V, the power consumed will be-

A. 100 W

B. 75 W

C. 50 W

D. 25 W

Answer: D



Watch Video Solution

4. Two conducting wires of the same material and of equal lengths and equal diameters are first connected in series and then parallel in a circuit across the same potential difference. The ratio of heat produced in series and parallel combinations would be -

A. 1 : 2

B. 2 : 1

C. 1 : 4

D. 4: 1

Answer: C



Watch Video Solution

5. How is a voltmeter connected in the circuit to measure the potential difference between two points?



Watch Video Solution

6. A copper wire has diameter 0.5mm and resistivity of $1.6 \times 10^{-8} \Omega\text{m}$. what will be the length of this wire to make its resistance 10Ω ?
How much does the resistance change if the diameter is doubled ?



[Watch Video Solution](#)

7. The values of current I flowing in a given resistor for the corresponding values or potential difference V across the resistor are

given below

I (amperes)	0.5	1.0	2.0	3.0	4.0
V (volts)	1.6	3.4	6.7	10.2	13.2

Plot a graph between V and I and calculate the resistance of that resistor.



[Watch Video Solution](#)

8. When a 12 V battery is connected across an unknown resistor there is a current of 2.5 mA in the circuit. Find the value of the resistance of the resistor.



[Watch Video Solution](#)

9. A battery of 9V is connected in series with resistors of 0.2Ω , 3Ω , 0.4Ω and 12Ω respectively. How much current would flow through the 12Ω resistors ?



[Watch Video Solution](#)

10. How many 176Ω resistors (in parallel) are required to carry 5A on a 220 V line ?



[Watch Video Solution](#)

11. Show how you would connect three resistors, each of resistance 6Ω so that combination has a resistance of

(i) 9Ω (ii) 4Ω



[Watch Video Solution](#)

12. Several electric bulbs designed to be used on a 220 V electric supply line, are rated 10 W. How many lamps can be connected in parallel

with each other across the two wires of 220V line of the maximum allowable current is 5A ?



[Watch Video Solution](#)

13. A hot plate of an electric oven connected to a 220 V line has two resistance coils A and B, each of 24Ω resistance, which may be used separately, in series or in parallel. What are the currents in the three cases?



[Watch Video Solution](#)

14. Compare the power used in the 2Ω resistors in each of the following circuits :

(i) a 6V battery in series with 1Ω and 2Ω resistor, and

(ii) a 4 V battery in parallel with 12Ω and 2Ω resistors.



Watch Video Solution

15. Two lamps, one rated 100 W at 220 V, and the other 60 W at 220 V, are connected in parallel to electric mains supply. What current

is drawn from the line if the supply voltage is 220 V?



[Watch Video Solution](#)

16. Which uses more energy, a 250 W TV set in 1 hr, or a 1200 W toaster in 10 minutes?



[Watch Video Solution](#)

17. An electric heater of resistance 8Ω draws 15 A from the service mains 2 hours. Calculate the

rate at which heat is developed in the heater.



Watch Video Solution

18. Explain the following.

a] Why is tungsten used almost exclusively for filament of electric lamps?

b] Why are the conductors of electric heating devices, such as bread-toasters and electric irons made of an alloy rather than a pure metal?

c] Why is the series arrangement not used for

domestic circuits?

d] How does the resistance of a wire vary with its area of cross-section?

e] Why are copper and aluminum wires usually employed for electricity transmission?



[Watch Video Solution](#)

19. A piece of wire resistance R is cut into five equal parts. These parts are then connected in parallel. If the equivalent resistance of this combination is R' then the ratio R/R' is

A. $1/25$

B. $1/5$

C. 5

D. 25

Answer: D



Watch Video Solution

20. Which of the following terms does not represent electrical power in a circuit?

A. $I^2 R$

B. IR^2

C. VI

D. V^2/R

Answer: B



Watch Video Solution

21. An electric bulb is rated 220 V and 100 W.

When it is operated on 110 V, the power consumed will be-

A. 100 W

B. 75 W

C. 50 W

D. 25 W

Answer: D



Watch Video Solution

22. Two conducting wires of the same material and of equal lengths and equal diameters are first connected in series and then parallel in a

circuit across the same potential difference.

The ratio of heat produced in series and parallel combinations would be -

A. 1 : 2

B. 2 : 1

C. 1 : 4

D. 4 : 1

Answer: C



Watch Video Solution

23. How is a voltmeter connected in the circuit to measure the potential difference between two points?



[Watch Video Solution](#)

24. A copper wire has diameter 0.5mm and resistivity of $1.6 \times 10^{-8} \Omega\text{m}$. what will be the length of this wire to make its resistance 10Ω ?
How much does the resistance change if the diameter is doubled ?



[Watch Video Solution](#)

25. The values of current I flowing in a given resistor for the corresponding values of potential difference V across the resistor are given below

I (amperes)	0.5	1.0	2.0	3.0	4.0
V (volts)	1.6	3.4	6.7	10.2	13.2

Plot a graph between V and I and calculate the resistance of that resistor.



Watch Video Solution

26. When a 12 V battery is connected across an unknown resistor there is a current of 2.5 mA in the circuit. Find the value of the resistance of the resistor.



Watch Video Solution

27. A battery of 9V is connected in series with resistors of 0.2Ω , 3Ω , 0.4Ω and 12Ω respectively. How much current would flow through the 12Ω resistors ?





[Watch Video Solution](#)

28. How many 176Ω resistors (in parallel) are required to carry 5A on a 220 V line ?



[Watch Video Solution](#)

29. Show how you would connect three resistors, each of resistance 6Ω so that combination has a resistance of

(i) 9Ω (ii) 4Ω



[Watch Video Solution](#)

30. Several electric bulbs designed to be used on a 220 V electric supply line, are rated 10 W. How many lamps can be connected in parallel with each other across the two wires of 220V line if the maximum allowable current is 5A ?



Watch Video Solution

31. A hot plate of an electric oven connected to a 220 V line has two resistance coils A and B,

each of 24Ω resistance, which may be used separately, in series or in parallel. What are the currents in the three cases?



[Watch Video Solution](#)

32. Compare the power used in the 2Ω resistor in each of the following circuits:

i] a 6 V battery in series with 1Ω and 2Ω resistors, and

ii] a 4 V battery in parallel with 12Ω and 2Ω resistors.



[Watch Video Solution](#)

33. Two lamps, one rated 100 W at 220 V, and the other 60 W at 220 V, are connected in parallel to electric mains supply. What current is drawn from the line if the supply voltage is 220 V?



[Watch Video Solution](#)

34. Which uses more energy, a 250 W TV set in 1 hr, or a 1200 W toaster in 10 minutes?



[Watch Video Solution](#)

35. An electric heater of resistance 8Ω draws 15 A from the service mains 2 hours. Calculate the rate at which heat is developed in the heater.



[Watch Video Solution](#)

36. Explain the following.

a] Why is tungsten used almost exclusively for

filament of electric lamps?

b] Why are the conductors of electric heating devices, such as bread-toasters and electric irons made of an alloy rather than a pure metal?

c] Why is the series arrangement not used for domestic circuits?

d] How does the resistance of a wire vary with its area of cross-section?


e] Why are copper and aluminum wires usually employed for electricity transmission?



[Watch Video Solution](#)

Zen Additional Questions Section Multiple Choice Questions

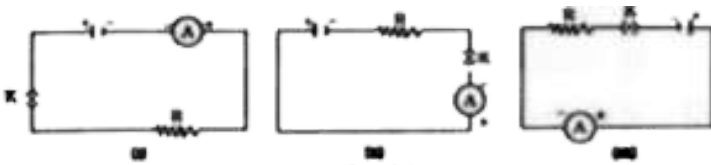1. A cell, a resistor, a key and ammeter are arranged as shown in the circuit diagrams. The current recorded in the ammeter will be



- A. maximum in [i]
- B. maximum in [ii]
- C. maximum in [iii]

D. the same in all the cases

Answer: B



Watch Video Solution

2. Electrical resistivity of a given metallic wire depends upon

A. its length

B. its thickness

C. its shaps

D. nature of the material

Answer: D



Watch Video Solution

3. What is the maximum resistance which can be made using five resistors each of $1/5\Omega$?

A. $1/5\Omega$

B. 10Ω

C. 5Ω

D. 1Ω

Answer: D



Watch Video Solution

4. What is the minimum resistance which can be made using five resistors each of $1/5\Omega$?

A. $1/5\Omega$

B. $1/25\Omega$

C. $1/10\Omega$

D. 25Ω

Answer: B



Watch Video Solution

5. Which of the following represents voltage?

A. Work done/Current \times Time

B. Work done/Charge

C. Work done \times Time/Current

D. Work done Charge Time

Answer: A



Watch Video Solution

6. Unit of electric power may also be expressed
as

- A. volt ampere
- B. kilowatt hour
- C. watt second
- D. joule second

Answer: A



Watch Video Solution

7. Which of the following statements does not represent Ohm's law?

A. current/potential difference = constant

B. potential difference/current = constant

C. potential difference = current \times
resistance

D. current = resistance \times potential

difference.

Answer: D



Watch Video Solution

8. Two resistances of $100\ \Omega$ and zero ohm are connected in parallel. The overall resistance will be

A. $100\ \Omega$

B. 50Ω

C. 25Ω

D. zero ohm

Answer: A



Watch Video Solution

9. Three resistors 2Ω , 3Ω and 4Ω are connected so that the equivalent resistance is 9Ω . The resistors are connected

A. all in series

B. all in parallel

C. 2Ω and 3Ω in parallel and the combination in series with 4Ω

D. 2Ω and 3Ω in series and the combination in parallel to 4Ω

Answer: A



Watch Video Solution

10. When a current 'I' flows through a resistance 'R' for time 't' the electrical energy spent is given by

A. IRt

B. I^2Rt

C. IR^2t

D. I^2R/t

Answer: B



Watch Video Solution

11. When a fuse is rated 8 A, it means

- A. it will not work if current is less than 8 A
- B. it has a resistance of 8Ω
- C. it will work only if current is 8 A
- D. it will melt if current exceeds 8 A

Answer: D



Watch Video Solution

12. The work done in moving a unit positive charge across two points in an electric circuit is a measure of

- A. Current
- B. potential difference
- C. resistance
- D. power

Answer: B



Watch Video Solution

13. The potential at a point is 20 V. The work done to bring a charge of 0.5 C from infinity to this point will be

A. 20 J

B. 10 J

C. 5 J

D. 40 J

Answer: B



Watch Video Solution

14. The free electrons of a metal

A. do not collide with each other

B. are free to escape through the surface

C. are free to fall into the nuclei

D. are free to move anywhere in the metal

Answer: D



Watch Video Solution

15. The path of a free electron in a metal is

A. Parabolic

B. Circular

C. a straight line

D. zig zag

Answer: D



Watch Video Solution

16. When there is an electric current passing through a wire, the particles moving are

A. Electrons

B. Protons

C. Atoms

D. Ions

Answer: A



Watch Video Solution

17. A positive charge released from rest

A. moves towards the regions of lower potential

B. moves towards the regions of higher potential

C. moves towards the regions of equal potential

D. does not move

Answer: A



Watch Video Solution

18. Three equal resistances when combined in series are equivalent to 90Ω . Their equivalent resistance when combined in parallel will be

A. $270\ \Omega$

B. $30\ \Omega$

C. $810\ \Omega$

D. $10\ \Omega$

Answer: D



Watch Video Solution

19. For which of the following substances, resistance decreases with increase in temperature?

A. Copper

B. Platinum

C. Mercury

D. Carbon

Answer: D



Watch Video Solution

20. Two electric bulbs have resistances in the ratio 1 : 2. If they are joined in series, the energy consumed in them are in the ratio

A. 1 : 2

B. 2 : 1

C. 4 : 1

D. 1 : 1

Answer: B



Watch Video Solution

21. Among the following statements.

1. A discharge lamp uses a discharge tube which is filled with a gas at a very low pressure.

2. Always white light is emitted independent of gas taken in the lamp.

A. Only 1 is true

B. Only 2 is true

C. Both 1 and 2 are true

D. Both 1 and 2 are false.

Answer: A



Watch Video Solution

22. Among identical spheres A and B having charges as -5 and -16 C

A. -16 C is at higher potential

B. Both are at equal potential

C. It cannot be said

D. $-5C$ is at higher potential

Answer: A



Watch Video Solution

23. Keeping the potential difference constant, the resistance of a circuit is doubled. The current will become

A. Double

B. Half

C. One-fourth

D. Four times

Answer: B



Watch Video Solution

24. The resistance of a conductor is 27Ω . If it is cut into three equal parts and connected in parallel, then its total resistance is

A. 6Ω

B. 3Ω

C. 9Ω

D. 27Ω

Answer: B



Watch Video Solution

25. A piece of metallic wire of resistance R is cut into 3 equal parts. These parts are then connected in parallel. If the total resistance of

this combination is R' , then the value of $R : R'$ is

A. 1 : 3

B. 9 : 1

C. 1 : 9

D. 3 : 1

Answer: B



Watch Video Solution

26. An electric kettle for use on a 230 V supply is rated at 3000 W. For safe working, the cable connected to it should be able to carry at least:

A. 2A

B. 5A

C. 10A

D. 15A

Answer: D



Watch Video Solution

27. At a given time, a house is supplied with 100 A at 220 V. How many 75 W, 220 V light bulbs could be switched on in the house at the same time [if they are all connected in parallel]?

A. 93

B. 193

C. 293

D. 393

Answer: C



Watch Video Solution

28. If the potential difference between the ends of a fixed resistor is halved, the electric power will become:

A. Double

B. Half

C. Four times

D. One-fourth

Answer: D



Watch Video Solution

29. The heat produced in a wire of resistance 'X' when a current 'Y' flows through it in time 'Z' is given by

A. $X^2 \times Y \times Z$

B. $X \times Z \times Y^2$

C. $Y \times Z \times X$

D. $Y \times X \times X$

Answer: B



Watch Video Solution

30. If the current flowing through a fixed resistor is halved, the heat produced in it will become:


- A. Double
- B. One-half
- C. One-fourth
- D. Four times

Answer: C



Watch Video Solution

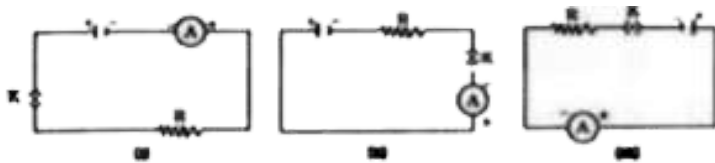31. A cell, a resistor, a key and ammeter are arranged as shown in the circuit diagrams. The current recorded in the ammeter will be



A. maximum in [i]

B. maximum in [ii]

C. maximum in [iii]

D. the same in all the cases

Answer: B



View Text Solution

32. Electrical resistivity of a given metallic wire depends upon

A. its length

B. its thickness

C. its shaps

D. nature of the material

Answer: D



Watch Video Solution

33. What is the maximum resistance which can be made using five resistors each of $1/5\Omega$?

A. $1/5\Omega$

B. 10Ω

C. 5Ω

D. 1Ω

Answer: D



Watch Video Solution

34. What is the minimum resistance which can be made using five resistors each of $1/5\Omega$?

A. $1/5\Omega$

B. $1/25\Omega$

C. $1/10\Omega$

D. 25Ω

Answer: B



Watch Video Solution

35. Which of the following represents voltage?

A. Work done/Current \times Time

B. Work done/Charge

C. Work done \times Time/Current

D. Work done Charge Time

Answer: A



Watch Video Solution

36. Unit of electric power may also be expressed as

- A. volt ampere
- B. kilowatt hour
- C. watt second

D. joule second

Answer: A



Watch Video Solution

37. Which of the following statements does not represent Ohm's law?

A. current/potential difference = constant

B. potential difference/current = constant

C. potential difference = current \times
resistance

D. current = resistance \times potential
difference.

Answer: D



Watch Video Solution

38. Two resistances of $100\ \Omega$ and zero ohm are connected in parallel. The overall resistance will be

A. 100 W

B. 50 W

C. 25 W

D. zero ohm

Answer: A



Watch Video Solution

39. Three resistors $2\ \Omega$, $3\ \Omega$ and $4\ \Omega$ are connected so that the equivalent resistance is $9\ \Omega$. The resistors are connected

A. all in series

B. all in parallel

C. 2 W and 3 W in parallel and the combination in series with 4 W

D. 2 W and 3 W in series and the combination in parallel to 4W

Answer: A



Watch Video Solution

40. When a current 'I' flows through a resistance 'R' for time 't' the electrical energy spent is given by

A. IRt

B. $I^2 R t$

C. $I R^2 t$

D. $I^2 R / t$

Answer: B



Watch Video Solution

41. When a fuse is rated 8 A, it means

- A. it will not work if current is less than 8 A
- B. it has a resistance of 8 W
- C. it will work only if current is 8 A
- D. it will melt if current exceeds 8 A

Answer: D



Watch Video Solution

42. The work done in moving a unit positive charge across two points in an electric circuit is a measure of

- A. Current
- B. potential difference
- C. resistance
- D. power

Answer: B



Watch Video Solution

43. The potential at a point is 20 V. The work done to bring a charge of 0.5 C from infinity to this point will be

A. 20 J

B. 10 J

C. 5 J

D. 40 J

Answer: B



Watch Video Solution

44. The free electrons of a metal

A. do not collide with each other

B. are free to escape through the surface

C. are free to fall into the nuclei

D. are free to move anywhere in the metal

Answer: D



Watch Video Solution

45. The path of a free electron in a metal is

A. Parabolic

B. Circular

C. a straight line

D. zig zag

Answer: D



Watch Video Solution

46. When there is an electric current passing through a wire, the particles moving are

A. Electrons

B. Protons

C. Atoms

D. Ions

Answer: A



Watch Video Solution

47. A positive charge released from rest

A. moves towards the regions of lower potential

B. moves towards the regions of higher potential

C. moves towards the regions of equal potential

D. does not move

Answer: A



Watch Video Solution

48. Three equal resistances when combined in series are equivalent to 90Ω . Their equivalent resistance when combined in parallel will be

A. 270 W

B. 30 W

C. 810 W

D. 10 W

Answer: D



Watch Video Solution

49. For which of the following substances, resistance decreases with increase in temperature?

A. Copper

B. Platinum

C. Mercury

D. Carbon

Answer: D



Watch Video Solution

50. Two electric bulbs have resistances in the ratio 1 : 2. If they are joined in series, the energy consumed in them are in the ratio

A. 1 : 2

B. 2 : 1

C. 4 : 1

D. 1 : 1

Answer: B



Watch Video Solution

51. Among the following statements.

1. A discharge lamp uses a discharge tube which is filled with a gas at a very low pressure.

2. Always white light is emitted independent of gas taken in the lamp.

A. Only 1 is true

B. Only 2 is true

C. Both 1 and 2 are true

D. Both 1 and 2 are false.

Answer: A



Watch Video Solution

52. Among identical spheres A and B having charges as -5 and -16 C

A. -16 C is at higher potential

B. Both are at equal potential

C. It cannot be said

D. $-5C$ is at higher potential

Answer: A



Watch Video Solution

53. Keeping the potential difference constant, the resistance of a circuit is doubled. The current will become

A. Double

B. Half

C. One-fourth

D. Four times

Answer: B



Watch Video Solution

54. The resistance of a conductor is 27Ω . If it is cut into three equal parts and connected in parallel, then its total resistance is

A. 6

B. 3Ω

C. 9Ω

D. 27Ω

Answer: B



Watch Video Solution

55. A piece of metallic wire of resistance R is cut into 3 equal parts. These parts are then connected in parallel. If the total resistance of

this combination is R' , then the value of $R : R'$ is

A. 1 : 3

B. 9 : 1

C. 1 : 9

D. 3 : 1

Answer: B



Watch Video Solution

56. An electric kettle for use on a 230 V supply is rated at 3000 W. For safe working, the cable connected to it should be able to carry at least:

A. 2A

B. 5A

C. 10A

D. 15A

Answer: D



Watch Video Solution

57. At a given time, a house is supplied with 100 A at 220 V. How many 75 W, 220 V light bulbs could be switched on in the house at the same time [if they are all connected in parallel]?

A. 93

B. 193

C. 293

D. 393

Answer: C



Watch Video Solution

58. If the potential difference between the ends of a fixed resistor is halved, the electric power will become:

A. Double

B. Half

C. Four times

D. One-fourth

Answer: D



Watch Video Solution

59. The heat produced in a wire of resistance 'X' when a current 'Y' flows through it in time 'Z' is given by

A. $X^2 \times Y \times Z$

B. $X \times Z \times Y^2$

C. $Y \times Z \times X$

D. $Y \times X \times X$

Answer: B



Watch Video Solution

60. If the current flowing through a fixed resistor is halved, the heat produced in it will become:

- A. Double
- B. One-half
- C. One-fourth
- D. Four times

Answer: C



Watch Video Solution

Zen Additional Questions Section Very Short Answer Type Questions

1. What is meant by saying that the electric potential at a point is 1 volt?



Watch Video Solution

2. How much work is done when one coulomb charge moves against a potential difference is 1 volt?



[Watch Video Solution](#)

3. What is the SI unit of electric current?



[Watch Video Solution](#)

4. Compare how an ammeter and a voltmeter are connected in a circuit.



[Watch Video Solution](#)

5. What is the current in a circuit if the charge passing through each point is 20 C in 40 s?



[Watch Video Solution](#)

6. Name the unit of electrical resistance and give its symbol.



[Watch Video Solution](#)

7. A resistance of 20 ohms has a current of 2 amperes flowing in it. What potential difference is there between its ends?



[Watch Video Solution](#)

8. A current of 5 amperes flows through a wire whose ends are at a potential difference of 3 volts. Calculate the resistance of wire.



Watch Video Solution

9. Give the law of combination of resistances in series.



Watch Video Solution

10. State the law of combination of resistances in parallel.



Watch Video Solution

11. Two resistances x and y are connected

i] in parallel and,

ii] in series. In which case the resultant resistance will be the less than either of the individual resistance?



Watch Video Solution

12. What is the SI unit of [i] electric energy, and [ii] electric power?



Watch Video Solution

13. Explain why, filament type electric bulbs are not power efficient.



Watch Video Solution

14. Resistance of an incandescent filament of a bulb is comparatively much more than that when it is at room temperature. Why?



Watch Video Solution

15. What happens to the other bulbs in series circuit, if one bulb blows off?



Watch Video Solution

16. Calculate the number of electrons constituting one coulomb of charge.



Watch Video Solution

17. State the relationship between 1 ampere and 1 coulomb.



Watch Video Solution

18. State the relationship between 1 volt and 1 joule.



Watch Video Solution

19. Would electrons move from higher potentials to lower potentials or vice-versa?



Watch Video Solution

20. Why is a voltmeter connected in parallel across a circuit element?



Watch Video Solution

21. What is the SI unit of potential difference ?

Name the device used to measure the potential difference.



Watch Video Solution

22. What is meant by saying that the electric potential at a point is 1 volt?



Watch Video Solution

23. How much work is done when one coulomb charge moves against a potential difference is 1 volt?



Watch Video Solution

24. What is the SI unit of electric current?



Watch Video Solution

25. Compare how an ammeter and a voltmeter are connected in a circuit.



Watch Video Solution

26. What is the current in a circuit if the charge passing through each point is 20 C in

40 s?



[Watch Video Solution](#)

27. Name the unit of electrical resistance and give its symbol.



[Watch Video Solution](#)

28. A resistance of 20 ohms has a current of 2 amperes flowing in it. What potential difference is there between its ends?



[Watch Video Solution](#)

29. A current of 5 amperes flows through a wire whose ends are at a potential difference of 3 volts. Calculate the resistance of wire.



[Watch Video Solution](#)

30. Give the law of combination of resistances in series.



[Watch Video Solution](#)

31. State the law of combination of resistances in parallel.



Watch Video Solution

32. Two resistances x and y are connected

i] in parallel and,

ii] in series. In which case the resultant resistance will be the less than either of the individual resistance?



Watch Video Solution

33. What is the SI unit of [i] electric energy, and [ii] electric power?



Watch Video Solution

34. Explain why, filament type electric bulbs are not power efficient.



Watch Video Solution

35. Resistance of an incandescent filament of a bulb is comparatively much more than that when it is at room temperature. Why?



Watch Video Solution

36. What happens to the other bulbs in series circuit, if one bulb blows off?



Watch Video Solution

37. Calculate the number of electrons constituting one coulomb of charge.



Watch Video Solution

38. State the relationship between 1 ampere and 1 coulomb.



Watch Video Solution

39. State the relationship between 1 volt and 1 joule.



Watch Video Solution

40. Would electrons move from higher potentials to lower potentials or vice-versa?



Watch Video Solution

41. Why is a voltmeter connected in parallel across a circuit element?



Watch Video Solution

42. What is the SI unit of potential difference ?

Name the device used to measure the potential difference.



Watch Video Solution

Zen Additional Questions Section Short Answer

Type 1 Questions

1. What is nichrome? State its one use.



[Watch Video Solution](#)

2. Which has more resistance:

a] A long piece of nichrome wire or a short one?

b] A thick piece of nichrome wire or a thin piece?



[Watch Video Solution](#)

3. What is the meaning of the symbol kWh?

Which quantity does it represent?



[Watch Video Solution](#)

4. Calculate the amount of charge flowing in a

wire if it draws a current of 2 A in 10 minutes.



[Watch Video Solution](#)

5. What happens to resistance of a conductor if area of cross section is doubled?



[Watch Video Solution](#)

6. Why closed path is required for the flow of current?



[Watch Video Solution](#)

7. Draw the V-I graph for ohmic and non-ohmic conductors.



[Watch Video Solution](#)

8. A wire of resistivity ρ is pulled to double its length. What will be its new resistivity?



[Watch Video Solution](#)

9. List in a tabular form two differences between a voltmeter and an ammeter.



[Watch Video Solution](#)

10. A given length of a wire is doubled on itself and this process is repeated once again. By what factor does the resistance of the wire change?



[Watch Video Solution](#)

11. What is the need of using combination of resistance in electrical circuits? Define equivalent resistance.



Watch Video Solution

12. What is heating effect of current? Mention any two of its applications.



Watch Video Solution

13. Define the term electric power. Write an expression for it.



Watch Video Solution

14. Draw the diagram of an electric circuit in which the resistors R_1 , R_2 and R_3 are connected in parallel including an ammeter and a voltmeter and mark the direction of the current.



Watch Video Solution

15. An electric refrigerator rated 400 W is used for 8 hours a day. An electric iron box rated 750 W is used for 2 hours a day. Calculate the cost of using these appliances for 30 days, if the cost of 1 kWh is Rs 3/-.



Watch Video Solution

16. A bulb is marked 220 V and 40 W. Calculate the current flowing through the bulb and its resistance.



[Watch Video Solution](#)

17. What are the advantages of connecting electrical devices in parallel with the battery instead of connecting them in series?



[Watch Video Solution](#)

18. According to Joule's law of heating, mention the factors on which heat produced in a resistor depends.

According to this law write the formula used to calculate the heat produced.




[Watch Video Solution](#)

19. The resistivity of manganese wire of length 1 m is $1.84 \times 10^{-6} \Omega m$ at $20^\circ C$. If the diameter of the wire is $3 \times 10^{-4} m$, what will be the resistance of the wire at that temperature?



[Watch Video Solution](#)

20. Observe the given circuit:

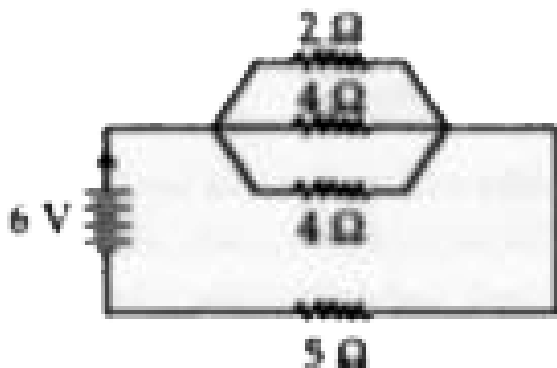

Calculate the total resistance in the circuit and the total current flowing in the circuit.

[Watch Video Solution](#)

21. What is nichrome? State its one use.

[Watch Video Solution](#)

22. Which has more resistance:

a] A long piece of nichrome wire or a short one?

b] A thick piece of nichrome wire or a thin piece?



Watch Video Solution

23. What is the meaning of the symbol kWh?

Which quantity does it represent?





[Watch Video Solution](#)

24. Calculate the amount of charge flowing in a wire if it draws a current of 2 A in 10 minutes.



[Watch Video Solution](#)

25. What happens to resistance of a conductor if area of cross section is doubled?



[Watch Video Solution](#)

26. Why closed path is required for the flow of current?



Watch Video Solution

27. Draw the V-I graph for ohmic and non-ohmic conductors.



Watch Video Solution

28. A wire of resistivity ρ is pulled to double its length. What will be its new resistivity?



[Watch Video Solution](#)

29. List in a tabular form two differences between a voltmeter and an ammeter.



[Watch Video Solution](#)

30. A given length of a wire is doubled on itself and this process is repeated once again. By what factor does the resistance of the wire change?



[Watch Video Solution](#)

31. What is the need of using combination of resistance in electrical circuits? Define equivalent resistance.



[Watch Video Solution](#)

32. What is heating effect of current? Mention any two of its applications.



[Watch Video Solution](#)

33. Define the term electric power. Write an expression for it.



Watch Video Solution

34. Draw the diagram of an electric circuit in which the resistors R_1 , R_2 and R_3 are connected in parallel including an ammeter and a voltmeter and mark the direction of the current.



Watch Video Solution

35. An electric refrigerator rated 400 W is used for 8 hours a day. An electric iron box rated 750 W is used for 2 hours a day. Calculate the cost of using these appliances for 30 days, if the cost of 1 kWh is Rs 3/-.



Watch Video Solution

36. A bulb is marked 220 V and 40 W. Calculate the current flowing through the bulb and its resistance.



[Watch Video Solution](#)

37. What are the advantages of connecting electrical devices in parallel with the battery instead of connecting them in series?



[Watch Video Solution](#)

38. According to Joule's law of heating, mention the factors on which heat produced in a resistor depends.

According to this law write the formula used
to calculate the heat produced.




[Watch Video Solution](#)

39. The resistivity of manganese wire of length 1 m is $1.84 \times 10^{-6} \Omega m$ at $20^\circ C$. If the diameter of the wire is $3 \times 10^{-4} m$, what will be the resistance of the wire at that temperature?



[Watch Video Solution](#)

40. Observe the given circuit:

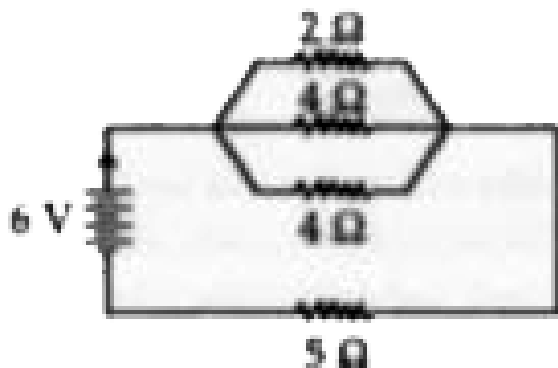


Calculate the total resistance in the circuit and the total current flowing in the circuit.



[Watch Video Solution](#)

Zen Additional Questions Section Short Answer
Type 2 Questions

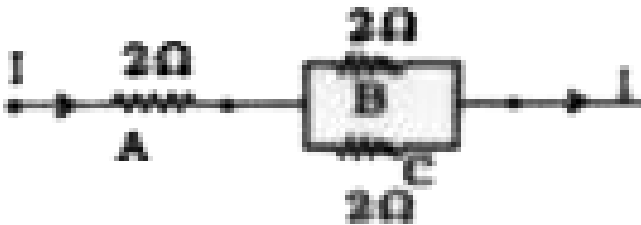1. Three 2Ω resistors, A, B and C, are connected as shown in figure. Each of them dissipates energy and can withstand a maximum power of 18 W without melting. Find the maximum current that can flow through the three resistors?



[Watch Video Solution](#)

2. Draw a circuit diagram of an electric circuit containing a cell, a key, an ammeter, a resistor of 2Ω in series with a combination of two resistors [4Ω each] in parallel and a voltmeter across the parallel combination. Will the potential difference across the 2Ω resistor be the same as that across the parallel combination of 4Ω resistors? Give reason.



[Watch Video Solution](#)

3. A current of 1 ampere flows in a series circuit containing an electric lamp and a conductor of 5Ω when connected to a 10 V battery. Calculate the resistance of the electric lamp. Now if a resistance of 10Ω is connected in parallel with this series combination, what change [if any] in current flowing through 5Ω conductor and potential difference across the lamp will take place? Give reason.



[Watch Video Solution](#)

4. Draw a schematic circuit diagram consisting a battery, a plug key, an ammeter and a bulb all connected in series with the bulb. Also show a voltmeter across the bulb.




[Watch Video Solution](#)

5. Why is an ammeter always connected in series in a circuit? What change do you observe in the reading of an ammeter if it is connected in parallel in a circuit?



[Watch Video Solution](#)

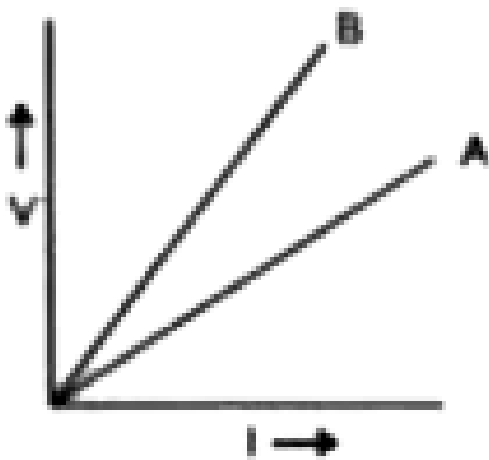6. Two V-I graphs are drawn individually for two resistors and their combination. Out of A and B which one represents the graph for parallel combination? Give reason for your answer.



[Watch Video Solution](#)

7. Show four different ways in which three resistors of Rohm each may be connected in a circuit. In which case is the equivalent resistance of the combination.

i] Maximum

ii] Minimum



[Watch Video Solution](#)

8. Two wires of equal length, one of copper and the other of manganin [an alloy] have the

same thickness. Which one can be used for

i] electrical transmission lines

ii] electrical heating devices? Why?



[Watch Video Solution](#)

9. If Three resistors of 6Ω , 9Ω and 21Ω are connected in series to a 12 V battery, find

a] The total resistance of the circuit.

b] The current flowing through the circuit.

c] The potential difference across the 21Ω resistor.



[Watch Video Solution](#)

10. Two resistances when connected in parallel give resultant value of 2Ω , when connected in series the value becomes 9Ω . Calculate the value of each resistance.



[Watch Video Solution](#)

11. i] Define electric potential difference. How is ammeter connected in an electric circuit ?

ii] Explain the application of heating effect of

electric current E in an electric bulb and the fuse used in an electric circuit.



[Watch Video Solution](#)


12. i] State Ohm's law

ii] Explain the factors on which the resistance of a conductor depends.



[Watch Video Solution](#)

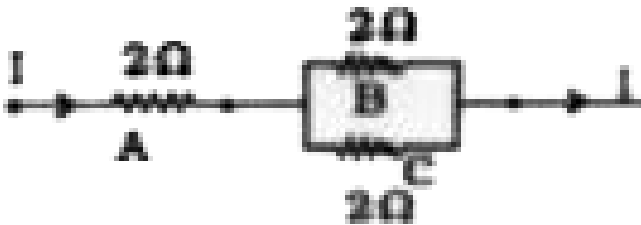13. Three 2Ω resistors, A, B and C, are connected as shown in figure. Each of them dissipates energy and can withstand a maximum power of 18 W without melting. Find the maximum current that can flow through the three resistors?



[Watch Video Solution](#)

14. Draw a circuit diagram of an electric circuit containing a cell, a key, an ammeter, a resistor of 2Ω in series with a combination of two resistors [4Ω each] in parallel and a voltmeter across the parallel combination. Will the potential difference across the 2Ω resistor be the same as that across the parallel combination of 4Ω resistors? Give reason.



Watch Video Solution

15. A current of 1 ampere flows in a series circuit containing an electric lamp and a conductor of 5Ω when connected to a 10 V battery. Calculate the resistance of the electric lamp. Now if a resistance of 10Ω is connected in parallel with this series combination, what change [if any] in current flowing through 5Ω conductor and potential difference across the lamp will take place? Give reason.



Watch Video Solution

16. Draw a schematic circuit diagram consisting a battery, a plug key, an ammeter and a bulb all connected in series with the bulb. Also show a voltmeter across the bulb.




Watch Video Solution

17. Why is an ammeter always connected in series in a circuit? What change do you observe in the reading of an ammeter if it is connected in parallel in a circuit?



Watch Video Solution

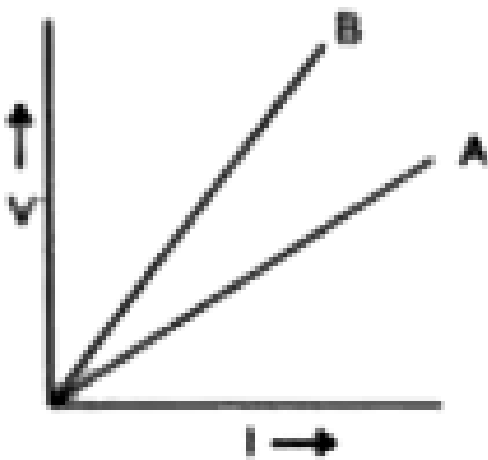18. Two V-I graphs are drawn individually for two resistors and their combination. Out of A and B which one represents the graph for parallel combination? Give reason for your answer.



[Watch Video Solution](#)

19. Show four different ways in which three resistors of Rohm each may be connected in a circuit. In which case is the equivalent resistance of the combination.

i] Maximum

ii] Minimum



Watch Video Solution

20. Two wires of equal length, one of copper and the other of manganin [an alloy] have the

same thickness. Which one can be used for

i] electrical transmission lines

ii] electrical heating devices? Why?



[Watch Video Solution](#)

21. If Three resistors of 6Ω , 9Ω and 21Ω are connected in series to a 12 V battery, find

a] The total resistance of the circuit.

b] The current flowing through the circuit.

c] The potential difference across the 21Ω resistor.



[Watch Video Solution](#)

22. Two resistances when connected in parallel give resultant value of 2Ω , when connected in series the value becomes 9Ω . Calculate the value of each resistance.



[Watch Video Solution](#)

23. i] Define electric potential difference. How is ammeter connected in an electric circuit ?

ii] Explain the application of heating effect of

electric current E in an electric bulb and the fuse used in an electric circuit.



[Watch Video Solution](#)

24. i] State Ohm's law

ii] Explain the factors on which the resistance of a conductor depends.



[Watch Video Solution](#)

1. State Ohm's law? How can it be verified experimentally? Does it hold good under all conditions? Comment.



[Watch Video Solution](#)

2. What is electrical resistivity of a material? What is its unit? Describe an experiment to study the factors on which the resistance of conducting wire depends.



[Watch Video Solution](#)

3. How will you infer with the help of an experiment that the same current flows through every part of the circuit containing three resistances in series connected to a battery?



[Watch Video Solution](#)

4. How will you conclude that the same potential difference [voltage] exists across

three resistors connected in a parallel arrangement to a battery?



[Watch Video Solution](#)

5. a] Obtain an expression for the equivalent resistance of three resistors connected in series. Also write the expressions for current and voltage in the circuit.

b] Mention any two advantages of connecting resistors in series.



[Watch Video Solution](#)

6. a] Derive an expression for the equivalent resistance of three resistors R_1 , R_2 and R_3 connected in a parallel.

b] Fuse of 3 A, 5 A and 10 A are available, calculate and select the fuse for operating electric iron of 1 kW power at 220 V line.



[Watch Video Solution](#)

7. a] What is the function of fuse in an electric circuit?

b] What would be the rating of the fuse for an electric kettle which is operated at 220V and consumes 500W power?

c] How is the SI unit of electric energy related to its commercial unit?



[Watch Video Solution](#)

8. a] State Ohm's law. Write it in the form of equation and give graphical representation for it.

b] An electric oven rated at 500W is connected

to a 220V line and used for 2 hours daily. Calculate the cost of electric energy per month at the rate of Rs. 5 per kWh.



[Watch Video Solution](#)

9. What is meant by resistance of conductor?

Name and define its SI unit. List the factors by which the resistance of a wire is affected.

What happens if

i] its length is doubled

ii] its radius is doubled?



[Watch Video Solution](#)

10. A household uses the following electrical appliances:

i] Refrigerator of rating 400 W for 10 h each day.

ii] Two electric fans of rating 80 W each for 6 h daily.

iii] Six tube lights of 18 W each for 6 h daily.

Calculate the energy consumed per day by each of these appliances in kWh.



[Watch Video Solution](#)

11. i] List the differences between electrical resistance and resistivity of conductor.

ii] A copper wire of resistivity $1.63 \times 10^{-8} \Omega - m$ has cross section area of $10.3 \times 10^{-4} cm^2$. Calculate the length of the wire required to make a 20Ω coil.



[Watch Video Solution](#)

12. i] Heating elements of electrical heating devices is made up of an alloy rather than a

pure metal. Give two reasons.

ii] Four resistors of 2Ω each are joined end to end to form a square. Calculate the equivalent resistance of the combination between two adjacent corners?



[Watch Video Solution](#)

13. Obtain an expression for the heat produced in a conductor when a voltage V is applied across it. Heating effect of electric

current is desirable as well as undesirable.

Explain this statement.



[Watch Video Solution](#)

14. Compare the power used in the 2Ω resistor in each of the following circuits:

i] a 6 V battery in series with 1Ω and 2Ω resistors, and

ii] a 4 V battery in parallel with 12Ω and 2Ω resistors.



[Watch Video Solution](#)

15. a] Define electric resistance of a conductor.
- b] List the factors on which resistance of a conductor depends.
- c] Resistance of a metal wire of length 1 m is 104Ω at $20^\circ C$. If the diameter of the wire is 0.15 mm, find the resistivity of the metal at this temperature.



[Watch Video Solution](#)

16. State Ohm's law? How can it be verified experimentally? Does it hold good under all conditions? Comment.



Watch Video Solution

17. What is electrical resistivity of a material? What is its unit? Describe an experiment to study the factors on which the resistance of conducting wire depends.



Watch Video Solution

18. How will you infer with the help of an experiment that the same current flows through every part of the circuit containing three resistances in series connected to a battery?



Watch Video Solution

19. How will you conclude that the same potential difference [voltage] exists across

three resistors connected in a parallel arrangement to a battery?



[Watch Video Solution](#)

20. a] Obtain an expression for the equivalent resistance of three resistors connected in series. Also write the expressions for current and voltage in the circuit.

b] Mention any two advantages of connecting resistors in series.



[Watch Video Solution](#)

21. a] Derive an expression for the equivalent resistance of three resistors R_1 , R_2 and R_3 connected in a parallel.

b] Fuse of 3 A, 5 A and 10 A are available, calculate and select the fuse for operating electric iron of 1 kW power at 220 V line.



[Watch Video Solution](#)

22. a] What is the function of fuse in an electric circuit?

b] What would be the rating of the fuse for an electric kettle which is operated at 220V and consumes 500W power?

c] How is the SI unit of electric energy related to its commercial unit?



[Watch Video Solution](#)

23. a] State Ohm's law. Write it in the form of equation and give graphical representation for it.

b] An electric oven rated at 500W is connected

to a 220V line and used for 2 hours daily. Calculate the cost of electric energy per month at the rate of Rs. 5 per kWh.



[Watch Video Solution](#)

24. What is meant by resistance of conductor?

Name and define its SI unit. List the factors by which the resistance of a wire is affected.

What happens if

i] its length is doubled

ii] its radius is doubled?



Watch Video Solution

25. A household uses the following electrical appliances:

i] Refrigerator of rating 400 W for 10 h each day.

ii] Two electric fans of rating 80 W each for 6 h daily.

iii] Six tube lights of 18 W each for 6 h daily.

Calculate the energy consumed per day by each of these appliances in kWh.



Watch Video Solution

26. i] List the differences between electrical resistance and resistivity of conductor.

ii] A copper wire of resistivity $1.63 \times 10^{-8} \Omega - m$ has cross section area of $10.3 \times 10^{-4} cm^2$. Calculate the length of the wire required to make a 20Ω coil.



[Watch Video Solution](#)

27. i] Heating elements of electrical heating devices is made up of an alloy rather than a

pure metal. Give two reasons.

ii] Four resistors of 2Ω each are joined end to end to form a square. Calculate the equivalent resistance of the combination between two adjacent corners?



[Watch Video Solution](#)

28. Obtain an expression for the heat produced in a conductor when a voltage V is applied across it. Heating effect of electric

current is desirable as well as undesirable.

Explain this statement.



[Watch Video Solution](#)

29. Compare the power used in the 2Ω resistor in each of the following circuits:

i] a 6 V battery in series with 1Ω and 2Ω resistors, and

ii] a 4 V battery in parallel with 12Ω and 2Ω resistors.



[Watch Video Solution](#)

30. a] Define electric resistance of a conductor.

b] List the factors on which resistance of a conductor depends.

c] Resistance of a metal wire of length 1 m is 104Ω at $20^\circ C$. If the diameter of the wire is 0.15 mm, find the resistivity of the metal at this temperature.



[Watch Video Solution](#)