



# PHYSICS

## BOOKS - ARIHANT PHYSICS (HINGLISH)

### ALTERNATING CURRENT

Level 1

1. An electric appliance draws 3 A current from a 200 V, 50 Hz power supply.


(a) Find the average of square of the current.

(b) Find the amplitude of the supply voltage.




**Watch Video Solution**

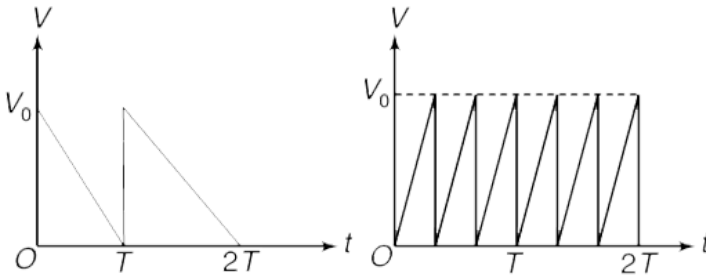2. Which of the two waveforms shown in Figure has a higher average value?



**Watch Video Solution**

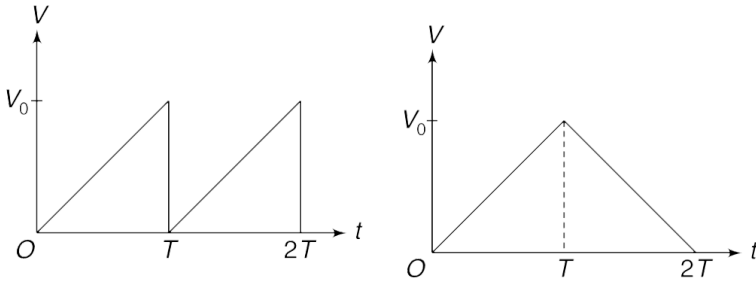
3. Which of the two waveforms shown in Figure has a higher rms value?



[Watch Video Solution](#)

4. A voltage waveform is as shown in the Figure calculate the ratio of rms value and

average value of the voltage.

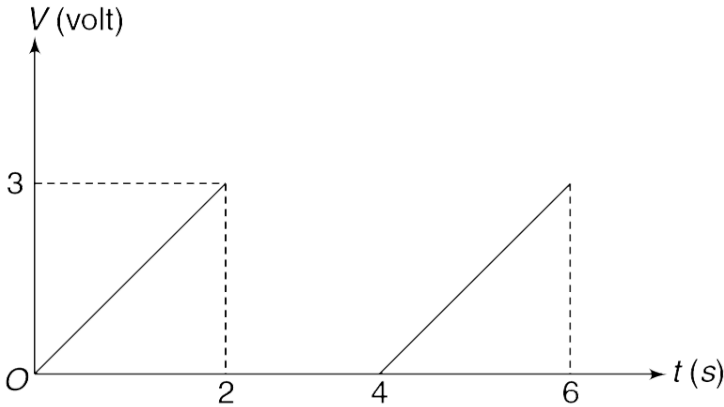

[Watch Video Solution](#)

5. The graph given here represents an idealized sinusoidal current flow between a cloud at a height of 1 km and the earth, during a lightning discharge. Value of  $I_0$  is 157 kA and


$T = 0.2$  ms. Assume that discharge happens when the electric field in the air between the cloud and the earth becomes equal to the breakdown field of air i.e.,  $E_0 = 3 \times 10^6 \text{ V/m}$

(a) Calculate the total charge flow due to lightning.

(b) Calculate the average current between the cloud and the earth during the lightning.

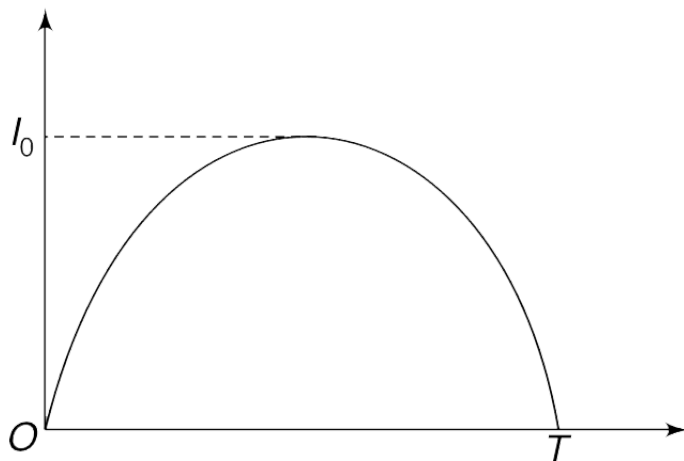(c) Assume that the entire charge on the cloud is released during the lightning and estimate


the capacitance of the cloud – Earth system.



[Watch Video Solution](#)

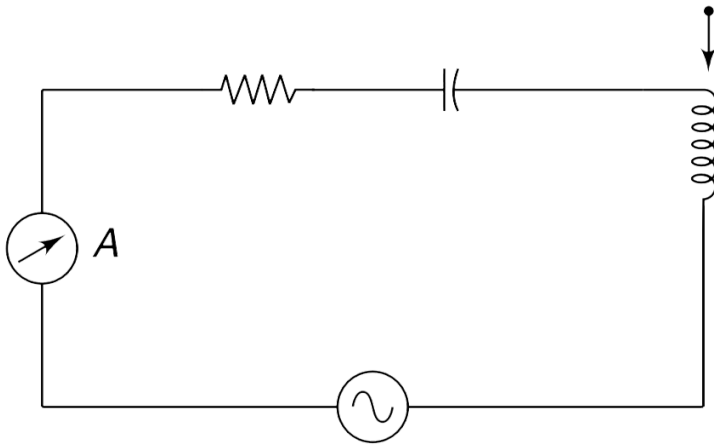**6.** In the circuit shown, the frequency of the source is adjusted so that the reading of the ac ammeter is maximum. The inductor shown is a short coil in vertical orientation. A steel


ball is dropped through the coil. How is the reading of ammeter affected when the ball enters the coil?



[Watch Video Solution](#)

7. A lamp L is connected to an ac source along with an air core inductor as shown in the

Figure. How is the brilliance of the lamp affected if core made of following material is inserted inside the inductor? (a) Iron (b) Copper (c) Iron sheets pasted together with insulation in between [laminated Iron core] In which case the lamp will be least bright?

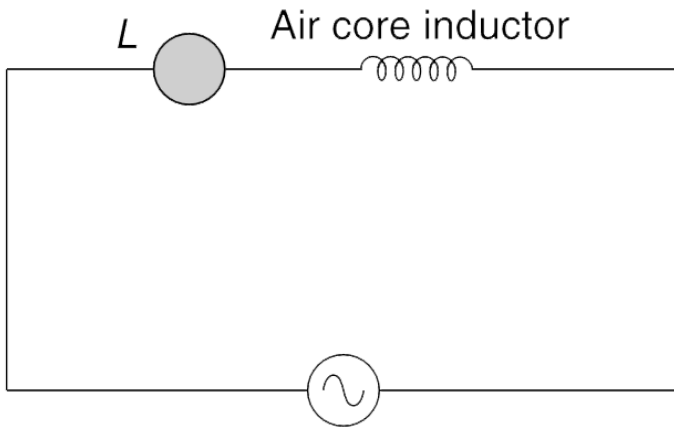

[Watch Video Solution](#)




8. In the circuit shown in the Figure, the voltage across resistance R, box A and box B are represented as

$$v_R = v \sin(\omega t), v_A = \sqrt{2}V \sin\left(\omega t + \frac{\pi}{4}\right) \text{ and}$$

$$v_B = v \sin\left(\omega t + \frac{\pi}{2}\right) \text{ Find the phase}$$

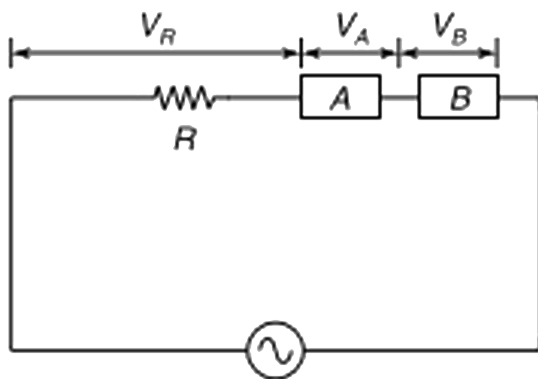difference between current and the applied voltage.



Watch Video Solution

## Level 2

1. A series LCR circuit containing a resistance of  $120\Omega$  has angular resonance frequency  $4 \times 10^5 \text{ rads}^{-1}$ . At resonance the voltage across resistance and inductance are 60V and 40 V, respectively,

At what frequency, the current in the circuit lags the voltage by  $45^\circ$  ?



[Watch Video Solution](#)

2. A resistance ( $R$ ), inductance ( $L$ ) and capacitance ( $C$ ) are connected in series to an ac source of voltage  $V$  having variable frequency. Calculate the energy delivered by the source to the circuit during one period if the operating frequency is twice the resonance frequency.




[Watch Video Solution](#)

3. A FM radio receiver has a series LCR circuit with  $L = 1 \mu H$ , and  $R = 100 \Omega$ . The antenna receives radio waves and induces a sinusoidally alternating emf of amplitude  $10 \mu V$ . The induced voltage is fed to the series LCR circuit. The capacitance in the circuit is adjusted to a value of  $C = 2 \text{ pF}$ .

(a) Find the frequency of radio wave to which the radio will tune to.

(b) Find the rms current in the circuit.

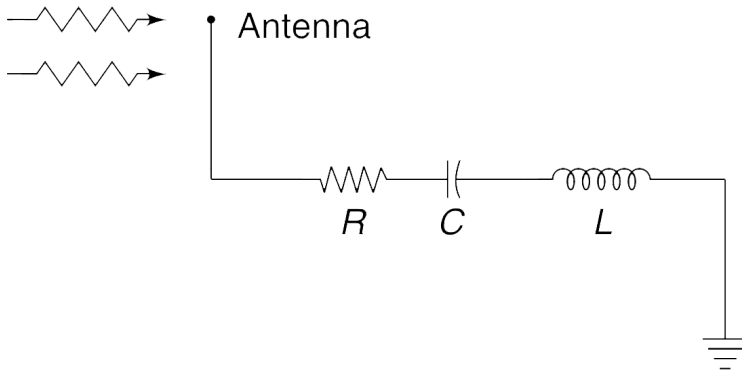
(c) Find quality factor of the resonance.



[Watch Video Solution](#)

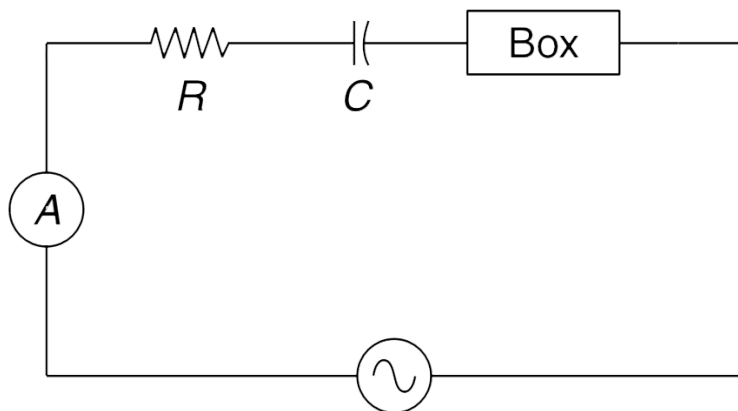4. In the circuit shown in Figure, the source has a rating of 15 V, 100 Hz. The resistance  $R$  is  $3 \Omega$  and the reactance of the capacitor is  $4 \Omega$ . It is known that the box certainly contains one or more element (resistance, capacitance or

inductance). Which element/s are present inside the box?




[Watch Video Solution](#)

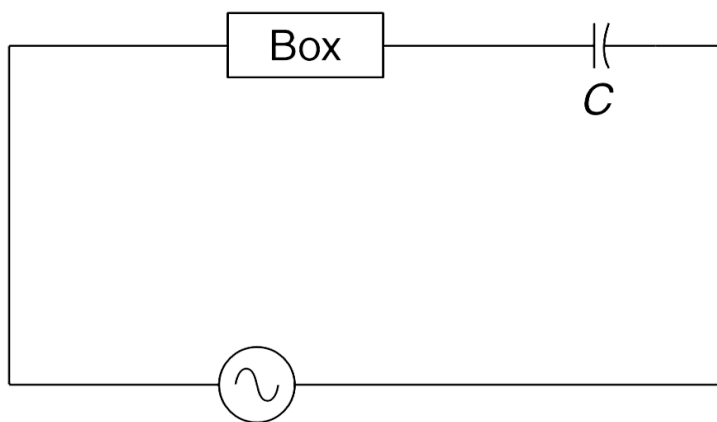5. A box has a large electric circuit inside it. When it was connected to an ac generator it was found that it was putting a lot of load on


the generator and the power factor of the box was  $\frac{1}{\sqrt{2}}$ . A capacitor of capacitance  $C$  was connected in series with the box and the power factor of the circuit became equal to the ideal value. Find the impedance of the box.

The generator has an angular frequency of  $\omega$ .



[Watch Video Solution](#)

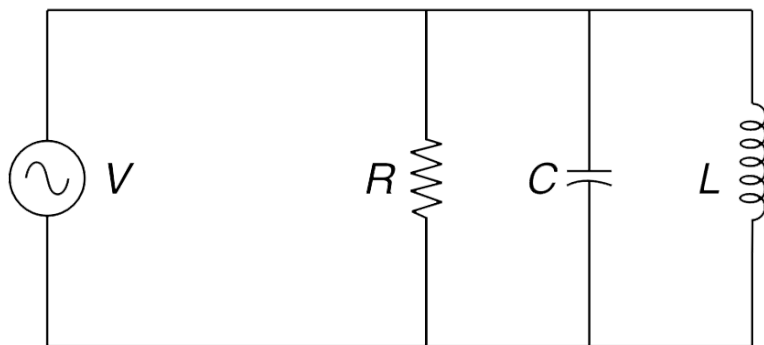6. In the circuit shown the source voltage is given as  $v = V_0 \sin \omega t$ . Find the current through the source as a function of time.




[Watch Video Solution](#)

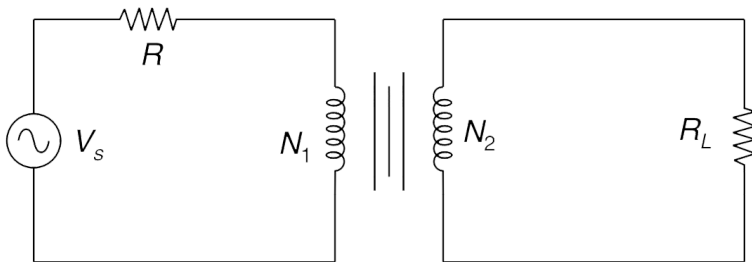7. In the circuit shown the transformer is ideal with turn ratio  $\frac{N_1}{N_2} = \frac{5}{1}$ . The voltage of the




source is  $V_s = 300$  Volt. The voltage measured across the load resistance  $R_L = 100\Omega$  is 50 Volt. Find the value of resistance  $R$  in the primary circuit.



[View Text Solution](#)

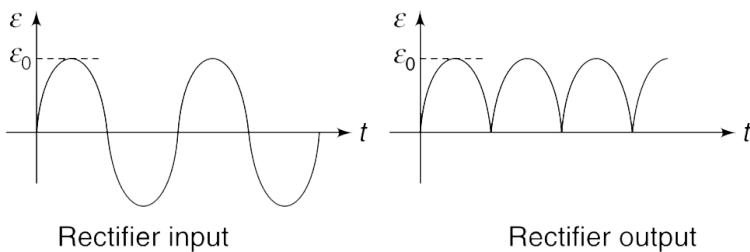**8.** A transformer with 20 turns in its secondary coil is used to step down the input 220 V ac

emf. The output of the transformer is fed to a rectifier circuit which converts the ac input into dc output. The input and output of rectifier are as shown in Figure (there is no change in peak voltage). The rectifier output has an average emf of 8.98 volt. Calculate the number of turns in the primary coil of the transformer.



[Watch Video Solution](#)

9. Two boys are holding a wire, standing 4 m apart. The wire sags in the shape of a circular arc with a sag of 1.0 m. The students rotate the wire about the horizontal line connecting their hands, as if they were playing jump rope. The boys rotate the wire at a speed of 4 revolutions per second. The earth's magnetic field at the location is  $4 \times 10^{-5}$  T. Calculate the rms value of emf developed between the ends of the wire. Assume that the shape of the wire is maintained as it is rotated.



**Watch Video Solution**

**10.** In a series LCR circuit the phasors corresponding to voltage across resistance, capacitor and inductor at an instant are as shown in the Figure and have amplitudes of  $V_{RO} = 4\text{volt}$ ,  $V_{CO} = 3\text{volt}$ , and  $V_{LO} = 6\text{volt}$


(a) Is the source frequency larger than or lesser than the resonance frequency? Does the current (I) lead or lag the source voltage?

(b) Find the voltage amplitude of the source.

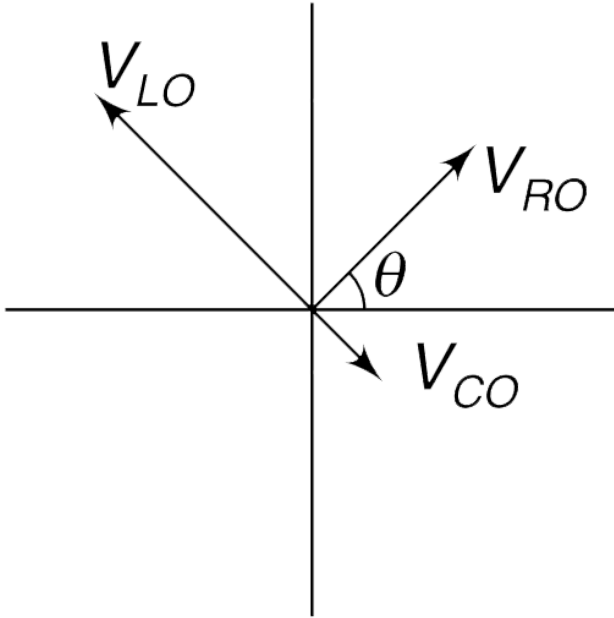(c) If VR phasor makes  $\theta = 53^\circ$  at time  $t = 0$ , write the source voltage as function of time.

Take angular frequency of the source to be

$$\omega \left[ \sin 53^\circ = \frac{4}{5} \right]$$



**Watch Video Solution**

**11.** A series LCR circuit having resistance  $R$ , capacitance  $C$  and inductance  $L$  has a voltage source of angular frequency  $\omega$  and voltage  $V_{\in}$ . Output voltage ( $V_{out}$ ) is taken as voltage across the resistor and inductor combined.


(a) Find  $\eta = \frac{V_{out}}{V_{in}}$

(b) Find  $\eta$  in the limit of large

$$\omega \left( \omega \gg \frac{1}{RC}, \frac{1}{\sqrt{LC}}, \frac{R}{L} \right)$$

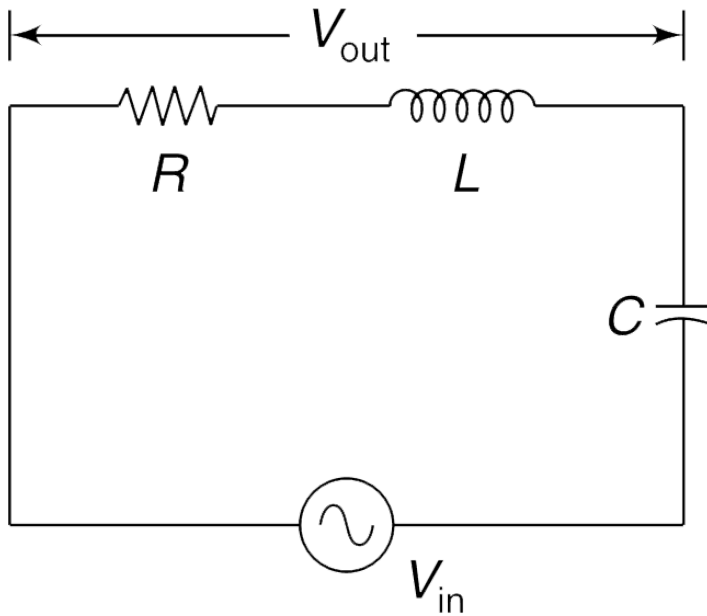(c) Find  $\eta$  in the limit of small

$$\omega \left( \omega > \frac{1}{RC}, \frac{1}{\sqrt{LC}}, \frac{R}{L} \right)$$



[Watch Video Solution](#)

**12.** In a series LCR circuit, the frequencies at which the current amplitude is  $\frac{1}{\sqrt{2}}$  mes the

current amplitude at resonance are  $f_1$  and  $f_2$  ( $> f_1$ ). Find the frequency bandwidth of resonance which is defined as  $\Delta f = f_2 - f_1$ . Express your answer in terms of R and L. Assume that resonance frequency  $f_0 \gg \Delta f$



[Watch Video Solution](#)

**13.** A series RLC circuit is in resonance with a source of frequency  $\omega_0 = 10$  MHz. The current amplitude in the circuit is  $I_0$ . It was found that



when a different source of frequency  $\omega = \omega_0 + \Delta\omega$  [ $\Delta\omega = 10\text{KHz}$ ] was used the current amplitude in the circuit was only 1% of  $I_0$ . Find the inductance in the circuit if it is known that resistance in the circuit is  $R = 0.314 \Omega$ .




[Watch Video Solution](#)

**14.** In the circuit shown in the figure, one of the three switches is kept closed and other two are open. The value of resistance is  $R = 20$

$\Omega$ . When the angular frequency( $\omega$ ) of the 100 V source is adjusted to 500 rad/s, 1000 rad/s and 2000 rad/s it was found that the current  $I$  was 4A, 5A and 4A respectively.

(a) Which switch is closed ? ( $S_1$ ,  $S_2$  or  $S_3$ )

(b) Find the value of  $L$  and  $C$ .

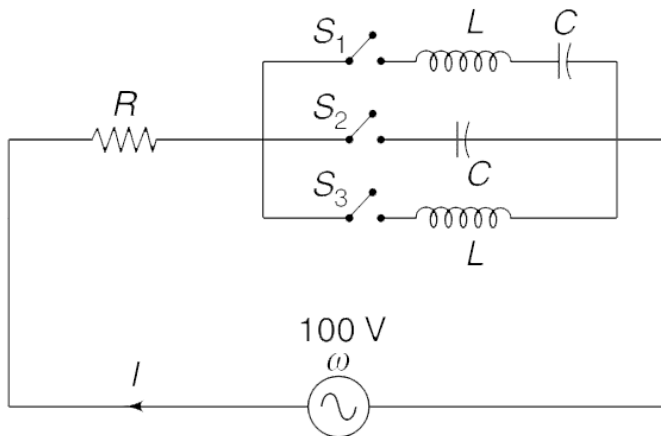

 **Watch Video Solution**

**15.** A village with a demand of 800 kW electric power at 220 V is located 30 km from an electric plant generating power at 440 V. The resistance of the two wire line carrying power is  $0.25 \Omega/\text{km}$ . The village gets power from the line through a 4000 V – 220 V step down transformer at a sub-station in the village. Assume negligible power loss in the transformers

(a) Estimate the power loss in form of heat in the transmission line.

(b) How much power must the plant supply?

(c) What is the input and output voltage of step-up transformer at the plant ?

(d) What difference will it make if the village receives power through a 40,000 V – 220 V step down transformer



[Watch Video Solution](#)

**Level 3**

1. A resistance  $R$  and a capacitor having capacitance  $C$  are connected to an alternating

source

having

emf


$v = V_0 \sin(\omega t)$ . It is given that  $\omega = \frac{1}{\sqrt{3}RC}$

(a) Plot the variation of power supplied by the source as a function of time. Mark the maximum and minimum values of power in the graph.

(b) How does the plot change if capacitor is removed and only R remains connected to the source?

(c) Plot the graph when only C remains

connected to source and R is removed.

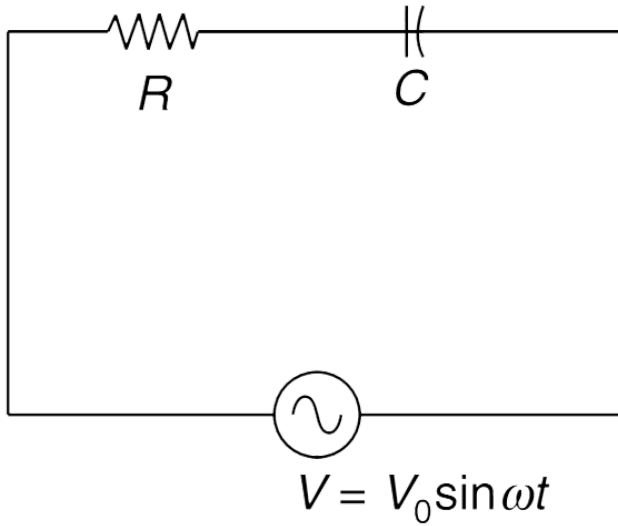

**Watch Video Solution**