




PHYSICS

BOOKS - CAREER POINT

UNIT TEST 7

Physics

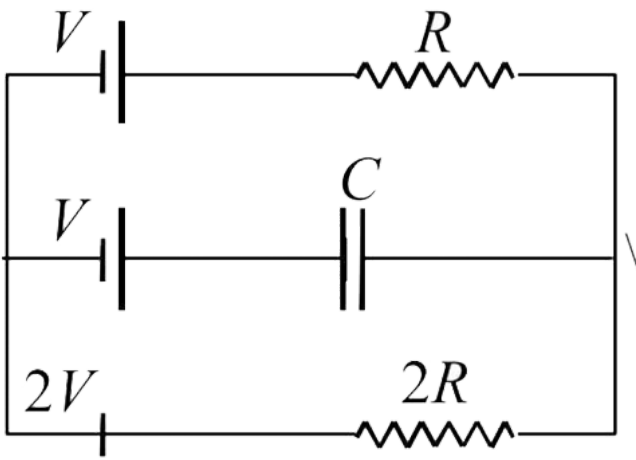1. In the given circuit, with steady current, the potential drop across the capacitor must be



A. V

B. $V/2$

C. $V/3$


D. $2V/3$

Answer: C



Watch Video Solution

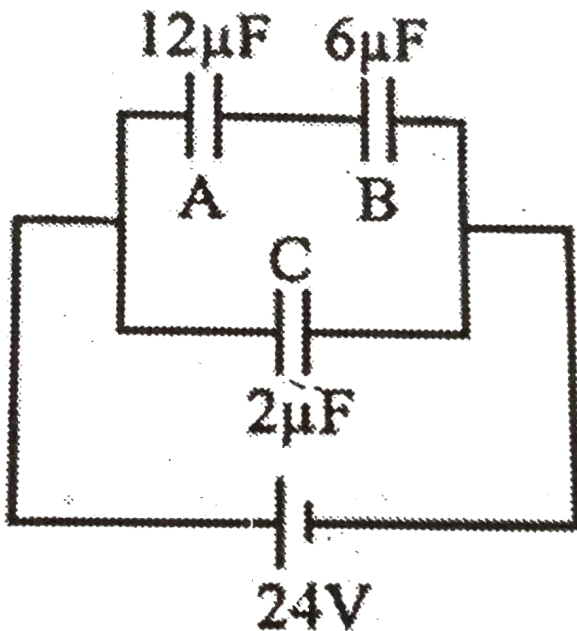2. For the circuit shown in figure the charges on three capacitors, A, B and C are respectively



A. $96\mu\text{C}$, $96\mu\text{C}$, and $48\mu\text{C}$

B. $32\mu\text{C}$, $64\mu\text{C}$, and $48\mu\text{C}$

C. $64\mu C$, $32\mu C$, and $48\mu C$

D. $32\mu C$, $32\mu C$, and $48\mu C$

Answer: A



Watch Video Solution

3. A capacitor of $2\mu F$ is charged to a potential of 4V using a battery, and then the battery is disconnected and the charged capacitor is connected to an uncharged capacitor of $4\mu F$ capacitance. When the equilibrium is

established the total energy stored in the capacitors is

A. $16\mu J$

B. $\frac{16}{3}\mu J$

C. $\frac{32}{3}\mu J$


D. $\frac{32}{9}\mu J$

Answer: B



View Text Solution

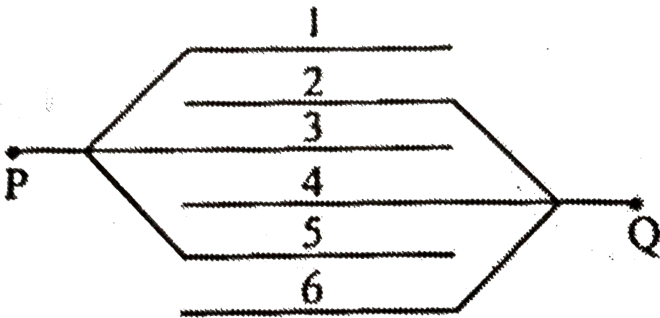4. Six metallic plates each with a surface area of one side A , are placed at a distance d from each other. The alternate plates are connected to points P and Q as shown in figure :



The capacitance of the system is :

A. $\epsilon_0 A / d$

B. $5\epsilon_0 A / d$

C. $6\epsilon_0 A / d$

D. $\epsilon_0 A / 5d$


Answer: B



Watch Video Solution

5. In the given circuit when S_1 & S_2 are closed,


The potential of point A will be

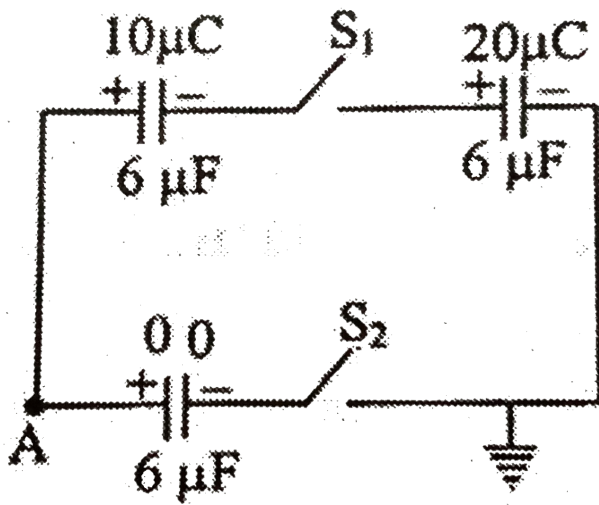

- A. $\frac{5}{3}V$
- B. $-\frac{5}{3}V$
- C. $\frac{10}{3}V$
- D. $-\frac{10}{3}V$

Answer: A

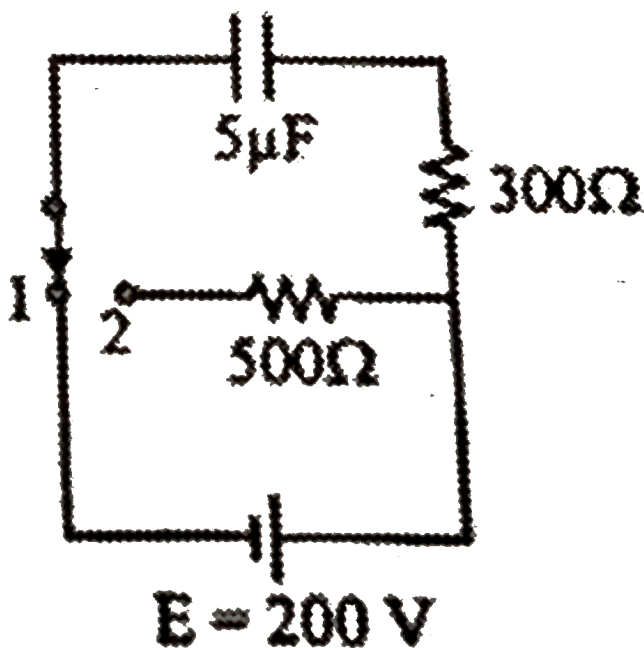6. The amount of heat generated in $500\ \Omega$ resistance, when the key is thrown over from contact 1 to 2, as shown in figure, is



A. $6.25 \times 10^{-2}\text{ J}$

B. $6.25 \times 10^{-3} J$

C. $3.75 \times 10^{-3} J$

D. $3.75 \times 10^{-2} J$

Answer: A



View Text Solution

7. The capacity of an isolated sphere is increased n times when it is enclosed by an earthed concentric sphere. The ratio of their radii is

A. $\frac{n^2}{n-1}$

B. $\frac{n}{n-1}$

C. $\frac{2n}{n+1}$

D. $\frac{2n+1}{n+1}$


Answer: B



Watch Video Solution

8. Initially K_1 is closed, now if K_2 is also closed, find heat dissipated in the resistances

of connecting wires

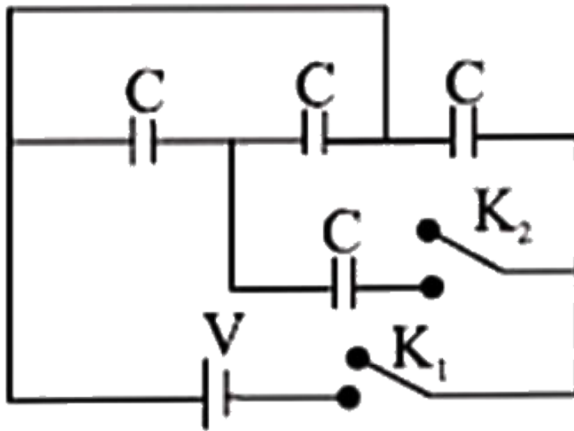

A. $\frac{1}{2}CV^2$

B. $\frac{2}{3}CV^2$

C. $\frac{1}{3}CV^2$

D. $\frac{1}{4}CV^2$

Answer: C



Watch Video Solution

9. The capacitance of a parallel plate condenser is C_0 . If a dielectric of relative permittivity ϵ_r and thickness equal to one fourth the plate separation is placed between the plates, then its capacity becomes C . The value of $\frac{C}{C_0}$ will be -

A. $\frac{5\epsilon_r}{4\epsilon_r + 1}$

B. $\frac{4\epsilon_r}{3\epsilon_r + 1}$

C. $\frac{3\epsilon_r}{2\epsilon_r + 1}$

D. $\frac{2\varepsilon_r}{2\varepsilon_r + 1}$

Answer: B



Watch Video Solution

10. A fully charged capacitor has a capacitance 'C'. It is discharged through a small coil of resistance wire embedded in a thermally insulated block of specific heat capacity 's' and mass 'm'. If the temperature of the block is

raised by 'DeltaT', the potential difference 'V' across the capacitance is

A. $\sqrt{\frac{2mC\Delta T}{s}}$

B. $\frac{mC\Delta T}{s}$

C. $\frac{ms\Delta T}{C}$


D. $\sqrt{\frac{2ms\Delta T}{C}}$

Answer: D



Watch Video Solution

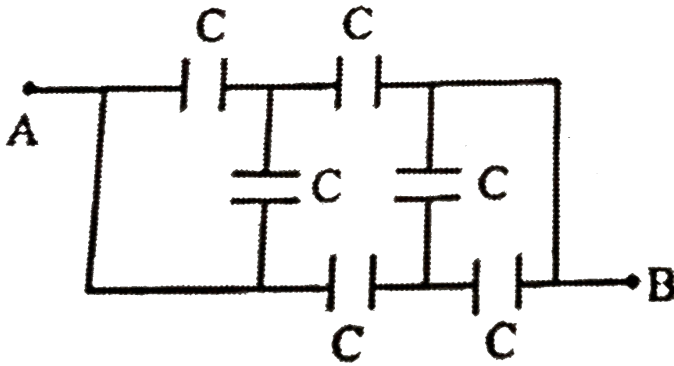11. Find equivalent capacitance between A & B




- A. $\frac{C}{4}$
- B. $\frac{3G}{4}$
- C. $\frac{3G}{2}$
- D. $\frac{4G}{3}$

Answer: D



View Text Solution

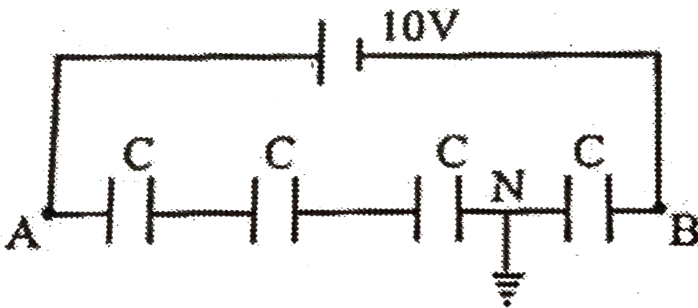12. The potential at point A in the circuit is - (N point is grounded. Grounding means that potential of that point is zero.)



A. 10 V

B. 7.5 V

C. 5 V


D. 2.5 V

Answer: B



View Text Solution

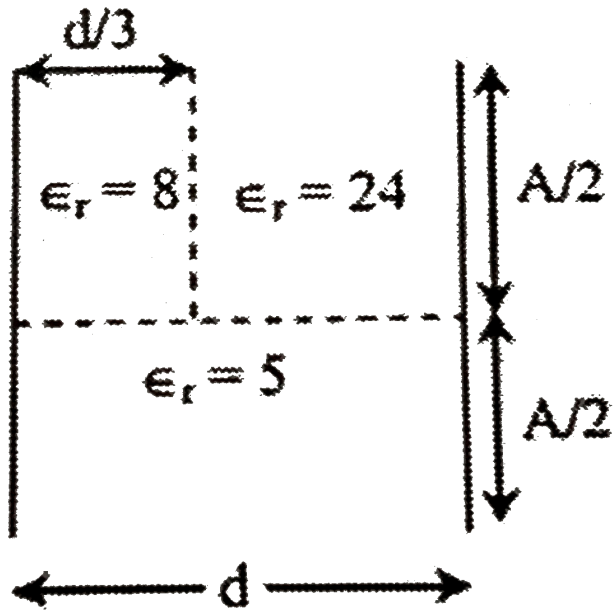13. Equivalent dielectric constant of given arrangement is



A. 7.2

B. 9.7

C. 2.5

D. None of these

Answer: B



[View Text Solution](#)

14. A parallel plate capacitor having capacitance C Farad is connected with a battery of emf V volts. Keeping the capacitor connected with the battery, a dielectric slab of dielectric constant K is inserted between the plates. The dimensions of the slab are such that it fills the space between the capacitor plates, consider the following statements

(i) Potential difference between the capacitor plates remains the same

(ii) The capacitance increases by a factor K

(iii) The energy stored increases by a factor K

Then the correct statements are

A. (i),(ii)

B. (ii),(iii)

C. (i),(ii),(iii)


D. None of these

Answer: C







View Text Solution

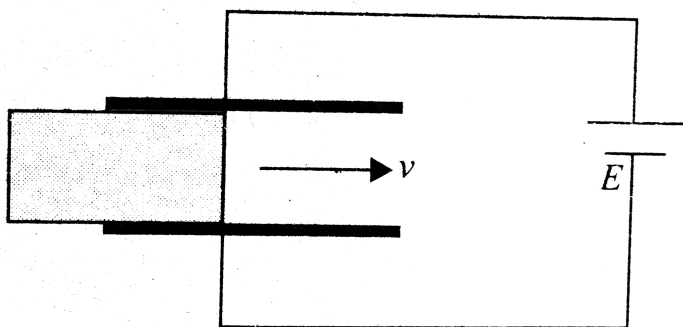15. A dielectric slab of area A and thickness d is inserted between the plates of a capacitor of area $2A$ with constant speed v as shown in. Distance between the plates is (d) .



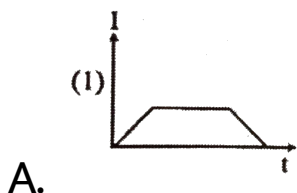The capacitor is connected to a battery of emf E . The current in the circuit varies with time as.



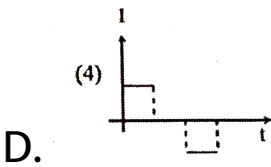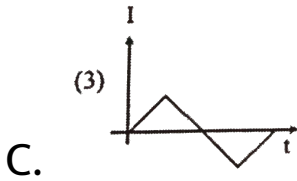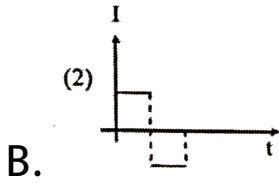

Answer: D



Watch Video Solution

16. n identical cells, each of emf ε and internal resistance r , are joined in series to form a

closed circuit. One cell a is joined with reversed polarity. The potential difference across each cell, except A, is

A. $\frac{2\varepsilon}{n}$

B. $\frac{n-1}{n}\varepsilon$

C. $\frac{n-2}{n}\varepsilon$


D. $\frac{2n}{n-2}\varepsilon$

Answer: A



Watch Video Solution

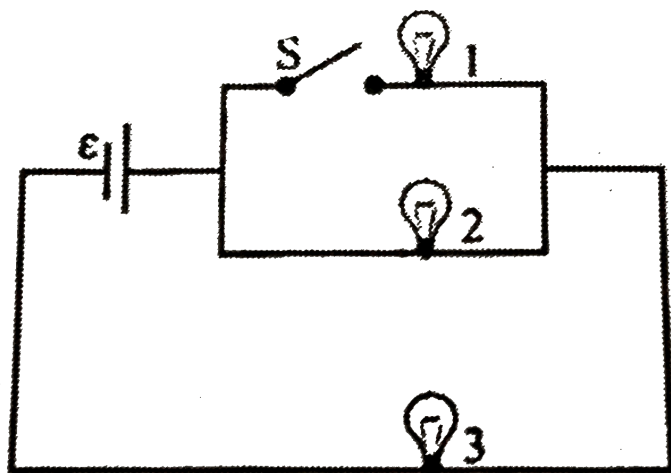17. The three light bulbs in the circuit below are identical, and the battery has zero internal resistance. When switch S is closed to cause bulb 1 to light, which of the other two bulbs increase(s) in brightness?



A. Neither bulb

B. Bulb 2 only

C. Bulb 3 only

D. Both bulbs


Answer: C



[View Text Solution](#)

18. Twelve wires each of resistance 6Ω are connected to form a cube as shown in the adjoining figure. The current enters at a corner A and leaves at the diagonally opposite corner G. The equivalent resistance

across the corners A and G is

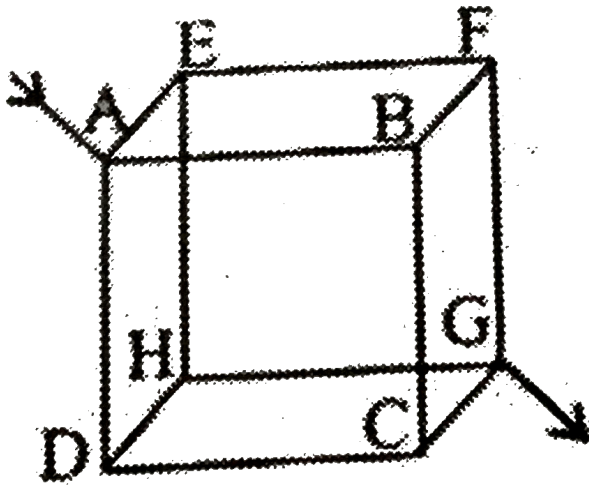

A. 12Ω

B. 6Ω

C. 3Ω


D. 5Ω

Answer: D



View Text Solution

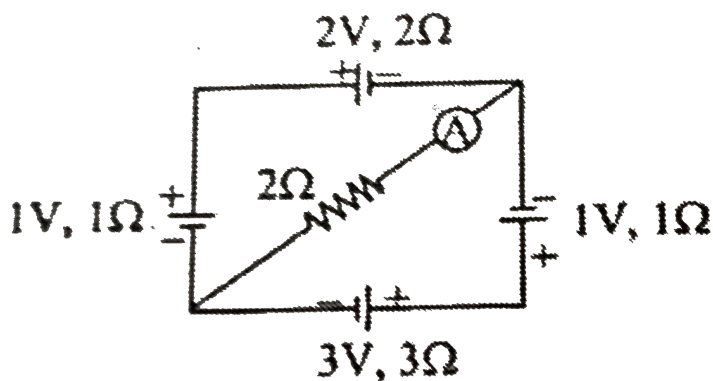19. The reading of ammeter in the adjoining diagram will be



A. $\frac{2}{17} A$

B. $\frac{3}{11} A$

C. $\frac{1}{13} A$

D. $\frac{4}{15} A$

Answer: C

 [View Text Solution](#)

20. If a given volume of water in a 220V heater is boiled in 5 min , then how much time will it take for the same volume of water in a 110V heater to be boiled?

A. 20 min

B. 30 min

C. 25 min

D. 40 min

Answer: A



Watch Video Solution

21. The temperature co-efficient of resistance of a wire is $0.00125^{\circ}C$. At 500 K, its resistance is 1Ω . The resistance of the wire will be 2Ω at

A. 1154 K

B. 1100 K

C. 1400 K

D. 1300K


Answer: D



Watch Video Solution

22. In figure, the e.m.f. of the cell is 120V and internal resistance is negligible. The resistance of the voltmeter is 80 ohm. The % error in

reading of voltmeter will be

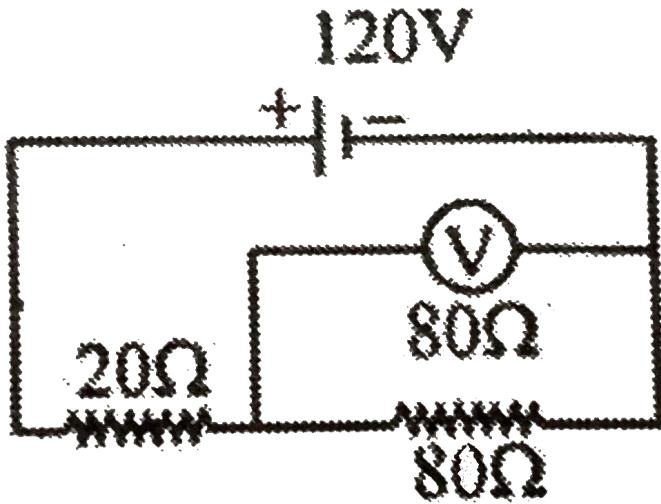

- A. 20 %
- B. 16.7 %
- C. 21.2 %
- D. 12.8 %

Answer: B



[View Text Solution](#)

23. The charge flowing through a resistance R varies with time $tasQ = at - bt^2$. The total heat produced in R is

A. $\frac{a^3 R}{6b}$

B. $\frac{a^2 R}{27b}$

C. $\frac{a^3 R}{3b}$

D. None of these


Answer: A



Watch Video Solution

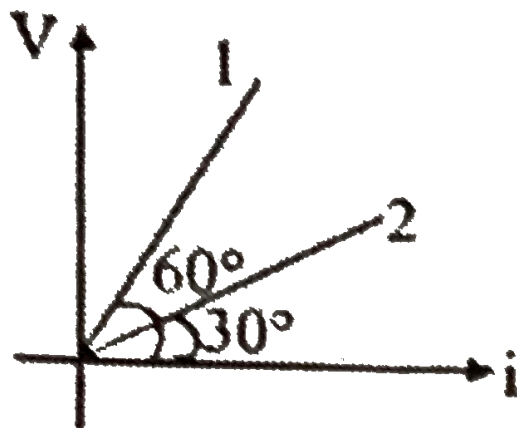24. The V-I graph is given for two conductors of same area and length. If σ_1 and σ_2 are the conductivities of the conductors 1 and 2

respectively, $\frac{\sigma_1}{\sigma_2} =$



A. 2:1

B. 3 : 1

C. 1 : $\sqrt{2}$


D. 1 : 3

Answer: D



View Text Solution

25. The potential of C is :

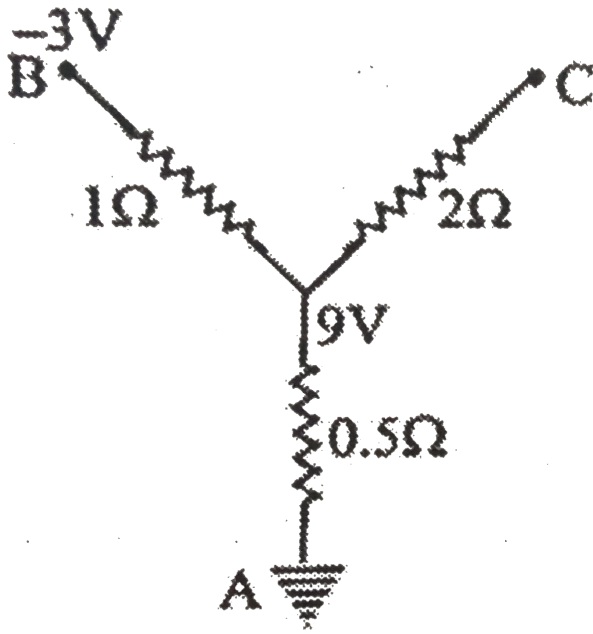

A. $51V$

B. 0

C. $+3V$

D. 69V

Answer: D



Watch Video Solution

26. If a copper wire is stretched so that its length increases by 20 % then what is the percentage increase in its resistance (assuming its volume remaining constant) ?

A. 10 %

B. 21 %

C. 44 %


D. 120 %

Answer: C



Watch Video Solution

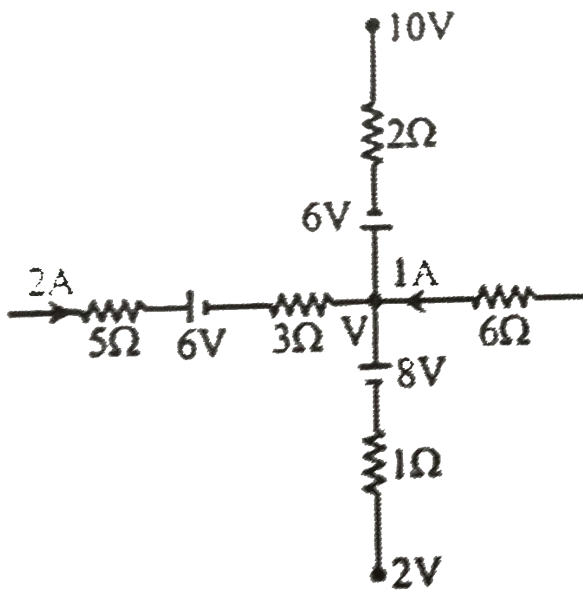27. For the part of the circuit gives in figure, find the current following through 2Ω resistor:



A. 1A

B. 3A

C. 4A

D. information insufficient

Answer: A



Watch Video Solution

28. Twelve cells each having the same e.m.f are connected in series and are kept to a closed box. Some of the cell are connected in reverse order .The battery is connected in series with an ammeter an external resistance R and two cells of the same type as an in the battery .The current when they and support each other is 3 ampere and current is 2 ampere when the two oppose each other. How many cells are connected in servese order ?

A. 4

B. 3

C. 2

D. 1

Answer: D



Watch Video Solution

29. The current density varies radical distance r as $J = ar^2$, in a cylindrical wire of radius R .

The current passing through the wire between radial distance $R/3$ and $R/2$ is,

A. $\frac{65\pi a R^4}{2592}$

B. $\frac{25\pi a R^4}{72}$

C. $\frac{65\pi a^2 R^3}{2938}$


D. None of these

Answer: A



Watch Video Solution

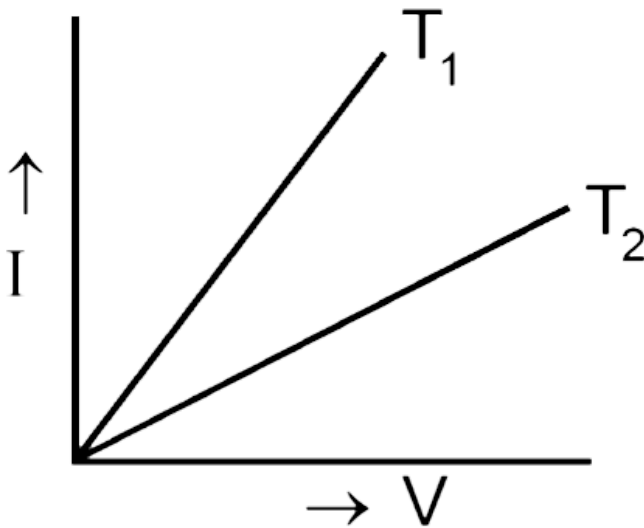30. The current (I) and voltage (V) graphs for a given metallic wire at two different temperature (T_1) and (T_2) are shown in fig. It is concluded that



A. $T_1 = T_2$

B. $T_1 > T_2$

C. $T_1 < T_2$

D. None of these

Answer: C



Watch Video Solution