

India's Number 1 Education App

# **PHYSICS**

# BOOKS - NEET PREVIOUS YEAR (YEARWISE + CHAPTERWISE)

# **CURRENT ELECTRICITY**



**1.** The resistance of a wire is 'R' ohm. If it is melted and stretched to n times its origianl

length, its new resistance will be

A. nR B.  $\frac{R}{n}$ C.  $n^2 R$ D.  $\frac{R}{n^2}$ 

## Answer: C



**2.** A potentiometer is an accurate and versatile device to make electrical measurements of E. M. F. because the method involves

A. cells

- B. potential gradients
- C. a condition of no current flow through

the galvanometer

D. a combination of cells, galvanometer

# Answer: C



**3.** The diagram below show regions of equipotential:

A positive chrages is moved from A to B in each diagram.



A. Maximum work is required to move q in

figure (ii)

B. In all the four cases, the work done is the

same

- C. Minimum work is required to move q in figure (i)
- D. Maximum work is required to move q in

figure (ii)

Answer: B

Watch Video Solution

**4.** A potentiometer wire is 100cm long and a constant potential difference is maintained across it. Two cells are connected in series first to support one another and then in opposite direction. The balance points are obtained at 50cm and 10cm from the positive end of the wire in the two cases. The ratio of emfs is:

A. 5:4

B. 3:4

C. 3:2

D. 5:1

#### Answer: C



# 5. The potential difference $(V_A - V_B)$ between the point A and B in the given figure

is



### A. -3V

 $\mathsf{B.} + 3V$ 

# $\mathsf{C.}+6V$

 $\mathsf{D.}+9V$ 

# Answer: D

Watch Video Solution

**6.** A potentiometer wire has length 4m and resistance  $8\Omega$ . The resistance that must be connected in series with the wire and an

accumulator of e.m.f. 2V, so as the get a

potential gradient 1mV per cm` on the wire is

A.  $32\Omega$ 

 $\mathrm{B.}\,40\Omega$ 

 $\mathsf{C.}\,44\Omega$ 

D.  $48\Omega$ 

Answer: A



7. A, B and C are voltmeters of resistances R, 1.5R and 3R respectively. When some potential difference is applied between x and y the voltmeter readings are  $V_A, V_B$  and V C, then



A. 
$$V_A = V_B = V_C$$

 $\mathsf{B}.\,V_A\neq V_B=V_C$ 

$$\mathsf{C}.\,V_A=V_B\neq V_C$$

# D. $V_A \neq V_B \neq V_C$

# Answer: A

Watch Video Solution

**8.** Across a metallic conductor of non-uniform cross-section a constant potential difference is applied. The quantity

A. current density

B. current

C. drift velocity

D. electric field

#### Answer: B



**9.** Two metal wires of identical dimesnios are connected in series. If  $\sigma_1$  and  $\sigma_2$  are the conducties of the metal wires respectively, the effective conductivity of the combination is

A. 
$$\frac{2\sigma_1\sigma_2}{\sigma_1 + \sigma_2}$$
  
B. 
$$\frac{\sigma_1 + \sigma_2}{2\sigma_1\sigma_2}$$
  
C. 
$$\frac{\sigma_1 + \sigma_2}{\sigma_1\sigma_2}$$
  
D. 
$$\frac{\sigma_1\sigma_2}{\sigma_1 + \sigma_2}$$

## Answer: A



**10.** A circuit contains an ammeter, a battery of 30V and a resistance 40.8ohm all connected in series. If the ammeter has a coil of

resistance 480 ohm and a shunt of 20 ohm, the

# reading in the ammeter will be

A. 0.5A

B. 0.25A

C. 2A

D. 1A

Answer: A



**11.** A potentiometer wire of Length L and a resistance r are connected in series with a battery of e.m.f.  $E_0$  and a resistance  $r_1$ . An unknown e.m.f. E is balanced at a length l of the potentiometer wire. The e.m.f. E will be given by :

A. 
$$rac{LE_0r}{lir_1}$$
  
B.  $rac{E_0r}{(r+r_1)}$ .  $rac{l}{L}$   
C.  $rac{E_0l}{L}$   
D.  $rac{LE_0r}{(r+r_1)l}$ 

# Answer: B



12. The resistance in the two arms of the meter bridge are  $5\Omega$  and  $R\Omega$ , respectively. When the resistance R is shunted with an equal resistance, the new balance point is  $1.6l_1$ .

# The resistance R is



A.  $10\Omega$ 

 $\mathsf{B}.\,15\Omega$ 

# $\mathsf{C.}\,20\Omega$

# D. $25\Omega$

# Answer: B



**13.** A potentiometer circuit has been setup for finding. The internal resistance of a given cell. The main battery used a negligible internal resistance. The potentiometer wire itseff is 4mlong. When the resistance, R, connected across the given cell, has value of (i) Infinity  $9.5\Omega$ , (ii) the 'balancing length' , on the

potentiometer wire are found to be 3m and

2.85m, respectively.

The value of internal resistance of the cell is

A.  $0.25\Omega$ 

 $\mathsf{B}.\,0.95\Omega$ 

 $\mathrm{C.}\,0.5\Omega$ 

D.  $0.75\Omega$ 

Answer: C

Watch Video Solution

14. In a ammeter 0.2% of main current passes through the galvanometer. If resistance of galvanometer is G, the resistance of ammeter will be



# Answer: C



15. A wire of resistance  $4\Omega$  is stretched to twice its original length. The resistance of stretched wire would be

A.  $2\Omega$ 

 $\mathsf{B.}\,4\Omega$ 

 $\mathsf{C}.\,8\Omega$ 

D.  $16\Omega$ 

### Answer: D

Watch Video Solution

16. The internal resistance of a 2.1V cell which gives a current 0.2A through a resistance of  $10\Omega$ 

A.  $0.2\Omega$ 

 $\mathsf{B}.\,0.5\Omega$ 

 ${\rm C.}\,0.8\Omega$ 

D.  $1.0\Omega$ 

#### Answer: B



17. The resistance of the four arms P, Q, Rand S in a Wheatstone's bridge are 10ohm30ohm and 90ohm rerspectively. The e.m.f. and internal resistance of the cell are 7vo < and 5ohm respectively. If the galvanometer resistance is 50ohm, the current drawn for the cell will be

A. 1.0A

#### B. 0.2A

C. 0.1A

D. 2.0A

### Answer: B



**18.** A milli voltmeter of 25 milli volt range is to be converted into an ammeter of 25 ampere range. The value (in ohm) of necessary shunt will be A. 0.001

B. 0.01

C. 1

D. 0.05

Answer: A

# Watch Video Solution

**19.** In the circuit shown the cells A and B have

negligible resistance. For  $V_A=12V, R_1=500\Omega$  and  $R=100\Omega$ , the

galvanometer (G) shows no deflection. The

value of  $V_B$  is



### A. 4V

B. 2V

# C. 12V

## D. 6V

Answer: B

**20.** A current of 2A flows through a  $2\Omega$  resistor when connected across a battery. The same battery supplies a current of 0.5A when connected across a  $9\Omega$  resistor. The internal resistance of the battery is

A.  $1/3\Omega$ 

B.  $1/4\Omega$ 

# $\mathsf{C}.\,1\Omega$

# D. $0.5\Omega$

#### Answer: A

# Watch Video Solution

**21.** A potentiometer circuit is setup as shown. The potential gradient across the potentiometer wire is kvolt/cm and the ammeter present in the circuit reads. 1.0AWhen two-way key is switched off. The balance point, when the key between the terminals (i) 1 and 2 (ii) 1 and 3, is plugged in, are found to be at lengths  $l_2cm$  and  $l_2cm$  respectively. The magnitudes, of the resistors R and X, in ohm, are then, equal, respectively, to



A.  $k(l_2 - l_1)$  and  $kl_2$ 

B.  $kl_1$  and  $k(l_2 - l_1)$ 

 $\mathsf{C}.\,k(l_2-l_1)$  and  $kl_1$ 

 $D. kl_1$  and  $kl_2$ 

Answer: C



22. A galvanometer has a coil of resistance  $100\Omega$  and gives a full-scale deflection for 30mA current. If it is to work as a voltmeter of

30V range, the resistance required to be

added will be

A.  $900\Omega$ 

 $\mathsf{B}.\,1800\Omega$ 

 $\mathsf{C}.\,500\Omega$ 

D.  $1000\Omega$ 

Answer: A



**23.** Consider the following two statements: (A)Kirchhoff's junction law follows from conservation of charge. (B)Kirchhoff's loop law follows from conservative nature of electirc field. A. Both I and II are wrong B. I is correct and II is wrong C. I is wrong and II is correct D. Both I and II are correct

Answer: D

24. The mean free path of electrons in a metal is  $4 \times 10^{-8}m$  The electric field which can give on an average 2eV energy to an electron in the metal will be in the units V/m

A.  $8 imes 10^7$ 

- $\text{B.5}\times10^{-11}$
- ${\sf C.8} imes 10^{-11}$

D.  $5 imes 10^7$ 

# Answer: D



**25.** See the electrical circuit shown in this figure. Which of the following equations is the correct equation for it ?



A. 
$$arepsilon_1(i_1+i_2)R-i_1r_1=0$$

B. 
$$arepsilon_2-i_2r_2-arepsilon_1-i_1r_1=0$$

C. 
$$arepsilon_2(i_1+i_2)R+i_2r_2=0$$

D. 
$$arepsilon_1(i_1+i_2)R-i_1r_1=0$$

#### Answer: A

# Watch Video Solution

# **26.** A student measures the terminal potential difference (V) of a cell (of emf $\varepsilon$ and internal resistance r) as a function of the current (I)

flowing through it. The slope and intercept of the graph between V and I, then respectively, equal

- A.  $\varepsilon$  and -r
- $\mathsf{B}.-r$  and  $\varepsilon$
- C. r and  $-\varepsilon$
- $\mathsf{D}. \varepsilon$  and r

# Answer: B

Watch Video Solution
**27.** A wire of resistance  $12\Omega m^{-1}$  is bent to from a complete circle of radius 10cm. The resistance between its two diametrically opposite points, A and B as shown in the figure, is



# A. $0.6\pi\Omega$

B.  $3\Omega$ 

C.  $6\pi\Omega$ 

D.  $6\Omega$ 

Answer: A

Watch Video Solution

**28.** In the circuit shown, the current through the  $4\Omega$  resistors is 1amp when the points Pand M are connected to a dc voltage source. The potential difference between the points

# M and N is.



# A. 1.5V

B. 1.0V

# C. 0.5V

#### D. 3.2V

## Answer: D



**29.** A cell can be balanced against 110cm and 100cm of potentiometer wire, respectively with and without being short circuited through a resistance of  $10\Omega$ . Its internal resistance is

A.  $1.0\Omega$ 

 $\mathsf{B}.\,0.5\Omega$ 

 $\mathsf{C}.\,2.0\Omega$ 

D. zero

#### **Answer: A**



**30.** A wire of a certain material is stretched slowly by ten percent. Its new resistance and specific resistance become respectively.

A. 1.2 times,1.1 times

# B. 1.21times, same

C. Both remain the same

D. 1.1times,1.1times

Answer: B

Watch Video Solution

**31.** Three resistance P, Q, R each of  $2\Omega$  and an unknown resistance S from the four amrs of a Wheatstone's bridge circuit. When a resistance of  $6\Omega$  is connected in parallel to S the bridge gets balanced. What is the value of

S ?

A.  $2\Omega$ 

 $\mathsf{B.}\,3\Omega$ 

 $\mathsf{C.}\, 6\Omega$ 

D.  $1\Omega$ 

Answer: B



**32.** The resistance of an ammeter is  $13\Omega$  and its scale is graduated for a current upto 100A. After an additional shunt has been connected to this ammeter it becomes possible to measure currents upto 750A by this meter. The value of shunt resistance is

A.  $20\Omega$ 

 $\mathsf{B.}\,2\Omega$ 

 $\mathsf{C}.\,0.2\Omega$ 

#### D. $2k\Omega$

## Answer: B



**33.** Two cells, having the same emf, are connected in series through an external resistance R. Cells have internal resistance  $r_1$ and  $r_2(r_1 > r_2)$  respectively. When the circuit is closed, the potentail difference across the first cell is zero the value of R is

A. 
$$r_1 - r_2$$

B. 
$$rac{r_1 + r_2}{2}$$
  
C.  $rac{r_1 - r_2}{2}$ 

$$\mathsf{D.}\,r_1+r_2$$

## Answer: A

Watch Video Solution

# **34.** In the circuit of a condacting wire is connected between point A and B the current

#### is this wire will



# A. flow from A to B

B. flow in the direction which will be

decided by the value of V

C. be zero

D. flow from B to A

#### Answer: D

Watch Video Solution

**35.** When a wire of uniform cross-section a, length I and resistance R is bent into a complete circle, resistance between two of diametrically opposite points will be

A. 
$$\frac{R}{4}$$

B.  $\frac{R}{8}$ C. 4R

D. 
$$\frac{R}{2}$$

# Answer: A

Watch Video Solution

**36.** Two batteries, one of emf 18V and internal resistance  $2\Omega$  and the other of emf 12 and internal resistance  $1\Omega$ , are connected as shown. The voltmeter V will record a reading

of



A. 15V

B. 30V

# C. 14V

# D. 18V

# Answer: C



**37.** A battery of 6 volts is connected of the termainals of a three meter long wire of uniform thickness and resistance of the order of  $100\Omega$ . The difference of potential between two points separated by 50cm on the wire will

A. 2V

C. 1V

D. 1.5V

#### Answer: C



**38.** Five equal resistances each of resistance R

are connected as shown in the figure. A

battery of V volts is connected between A

# and B. The current flowing in AFCEB will be



A. 
$$\frac{3V}{R}$$
  
B.  $\frac{V}{R}$   
C.  $\frac{V}{2R}$   
D.  $\frac{2V}{R}$ 

# Answer: C



**39.** Resistance *n*, each of *rohm*, when connected in parallel give an equivalent resistance of *Rohm*. If these resistances were connected series, the combination would have a resistance in ohm, equal to

A. 
$$n^2 R$$

$$\mathsf{B.}\,\frac{R}{n^2}$$

C.  $\frac{R}{n}$ 

D. nR

#### Answer: A



**40.** The electric resistance of a certain wire of iron is R. If its length and radius are both doubled, then

A the resistance will be doubled and the specific resistance will be halved B. the resistance will be halved and the specific resistance will remain unchanged C. the resistance will be halved and the specific resistance will be doubled D. the resistance and the specific resistance will both remain unchanged

Answer: B

**41.** A battery is charged at a potential fo 15 V for 8 h when the current folwing is 10A. The battery on discharge supplies a current of 5A fo 15h . The mean terminal voltage during discharge is 14V. The watt-hour efficiency of the battery is

A. 0.825

B. 0.8

#### D. 0.875

#### Answer: D

# Watch Video Solution

**42.** In a Wheatstone's bridge all the four arms have equal resistance R. If the resistance of the galvanometer arm is also R, the equivalent resistance of the combination as seen by the battery is

B. 2R

C. 
$$\frac{R}{4}$$
  
D.  $\frac{R}{2}$ 

## Answer: A

Watch Video Solution

**43.** For a cell, the terminal potential difference is 2.2V, when circuit is open and reduces to 1.8V. When cell is connected to a resistance  $R = 5\Omega$ , the internal resistance of cell (R) is



# Answer: A



**44.** The specific resistance of a conductor increases with:

- A. increase in temperature
- B. increase in cross-sectional area
- C. decrease in length
- D. decrease in cross-sectional area

Answer: A

Watch Video Solution

**45.** Resistivity of potentiometer wire is  $10^{-7}$  ohm metre and its area of cross-section is

 $10^{-6}m^2$ . When a current l=0.1A flows

through the wire, its potential gradient is:

A. 
$$10^{-2}V/m$$

B. 
$$10^{-4}V/m$$

C. 0.1V/m

# D. 10V/m

#### Answer: A



**46.** In a wheatstone bridge resistance of each of the four sides is  $10\Omega$ . If the resistance of the galvanometer is also  $10\Omega$ , then effective resistance of the bridge will be

A.  $10\Omega$ 

 $\mathsf{B.}\,5\Omega$ 

 $\mathrm{C.}\,20\Omega$ 

D.  $40\Omega$ 

Answer: A



**47.** A cell has an emf 1.5V. When connected across an external resistance of  $2\Omega$ , the terminal potential difference falls to 1.0V. The internal resistance of the cell is:

- A.  $2\Omega$
- $\mathsf{B}.\,1.5\Omega$
- $\mathsf{C}.\,1.0\Omega$
- D.  $0.5\Omega$

# Answer: C



**48.** Potentiometer measures the potential difference more accurately than a voltmeter, because

- A. it has a wire of high resistance
- B. it has a wire of low resistance
- C. it does not draw current from external

circuit

D. it draws a heavy current from external

circuit

Answer: C

Watch Video Solution

**49.** A bridge circuit is shown in figure. The equivalent resistance between A and B will be



# A. $21\Omega$

 $\mathsf{B.}\,7\Omega$ 

C. 
$$rac{252}{85}\Omega$$
  
D.  $rac{14}{3}\Omega$ 

# Answer: D



**50.** A potentiometer consists of a wire of length 4 m and resistance  $10\Omega$ . It is connected to a cell of emf 2V.The potential gradient of the wire is

A. 0.5 V/m

B. 2 V/m

C. 5V/m

D. 10V/m

#### Answer: A





**51.** In meter bridge , the balancing length from left is found to be 20 cm when standard connected of  $1\Omega$  is in right gap . The value of unknown resistance is

A.  $0.25\Omega$ 

 $\mathrm{B.}\,0.4\Omega$ 

 $\mathrm{C.}\,0.5\Omega$ 

# D. $4\Omega$





# **52.** The resistance of a discharge tube is

A. zero

B. ohmic

C. non-ohmic

D. infinity

Answer: C



A. 1.6 A

 $\mathsf{B.}\,2A$ 

#### C. 0.32A

# D. 3.2 A

## Answer: B



**54.** From the given between current I and voltage V shown in figure , indentify the portion corresponding to negative resistance


A. DE

B. CD

C. BC

D. AB

Answer: B



**55.** There are three copper wires of length and cross-sectional area (L,A),(2L,A/2)(L/2,2A). In which case in the resistance minimum?



B. Wire of cross-sectional are 2A

C. Wire of cross-sectional area A

D. Wire of cross-sectional are  $\frac{1}{2}$ A

Answer: B

Watch Video Solution

56. The current in the following circuit is



A. 1A

B. 
$$\frac{2}{3}A$$
  
C.  $\frac{2}{9}A$   
D.  $\frac{1}{8}A$ 

#### Answer: A



57. Kirchhoff's first law i.e.,  $\sum I=0$  at a

junction is based on the law of conservation of

A. angular momentum

B. linear momentum

C. energy

D. charge

Answer: D

Watch Video Solution

**58.** What will be the equivalent resistance fo circuit shown in figure between two points A and D?



A.  $10\Omega$ 

# $\mathrm{B.}\,20\Omega$

# D. $40\Omega$

### Answer: C

# Watch Video Solution

**59.** A negligibly small current is passed through a wire of length 15 m and uniform cross-section  $6.0 \times 10^{-7} \Omega m^2$ , and its resistance is measured to be  $5.0\Omega$ . What is the resistivity of the material at the temperature of the experiment ?

A. 
$$1 imes 10^{-7}\Omega-m$$
  
B.  $2 imes 10^{-7}\Omega-m$   
C.  $3 imes 10^{-7}\Omega-m$   
D.  $4 imes 10^{-7}\Omega-m$ 

#### Answer: B



60. If the resistance of a conductor is  $5\Omega$  at  $50^{\circ}C$  and  $7\Omega$  at  $100^{\circ}C$  then the mean

temperature coefficient of resistance of the

### material is

A. 
$$0.01/^\circ~{
m C}$$

- B.  $0.04/^{\circ}$  C
- $\mathrm{C.}\,0.06\,/^{\,\circ}\,\mathrm{C}$
- D.  $0.08 / ^{\circ}$  C

### Answer: A



**61.** If a wire of resistance R is melted and recasted in to half of its length, then the new resistance of the wire will be

A. 
$$\frac{R}{4}$$
  
B.  $\frac{R}{2}$ 

C. R

D. 2R

### Answer: A



**62.** Two wire of the same meta have same length, but their cross-sections are in the rati 3:1. They are joined in series. The resistance of thicker wire is  $10\Omega$ . The total resistance of the combination will be

A.  $10\Omega$ 

 $\mathsf{B.}\,20\Omega$ 

 $\mathsf{C.}\,40\Omega$ 

D.  $100\Omega$ 

Answer: C



**63.** In the circuit of figure, the current in  $4\Omega$  resistance is 1.2A , what is the potential difference between B and C?



### A. 3.6V

B. 6.3V

C. 1.8V

D. 2.4V

Answer: A

Watch Video Solution

**64.** Current through  $3\Omega$  resistor is 0.8A, then

potential drop through  $4\Omega$  resistor is



#### A. 9.6V

- B. 2.6V
- C. 4.8V
- D. 1.2V

### Answer: C





**65.** Three resistance each of  $4\Omega$  are connected to form a triangle. The resistance between any two terminals is

- A.  $12\Omega$
- $\mathsf{B.}\,2\Omega$
- $\mathsf{C.}\, 6\Omega$

D. 
$$rac{8}{3}\Omega$$

# Answer: D





**66.** Kirchhoff's first law of electricity follows.

- A. only law of conservation of energy
- B. only law of conservation of charge
- C. law of conservation of both energy and

charge

D. sometimes law of conservation of energy

and some other times law of

conservation of charge

# Answer: B



**67.** The velocity of charge carries of current (about 1 A) in a metal under normal conditions is of the order of

A. a fraction of mm/s

B. velocity of light

C. several thousands m/s

D. a few hundred m/s

## Answer: A



68. You are given several identical resistors each of value  $10\Omega$  and each capable of carrying a maximum current of 1 A. It is required to make a suitable combination of these to resistances to produce a resistance of  $5\Omega$  which can carry a current of 4 A. The minimum number of resistors required for this job is

A. 4

B. 10

C. 8

D. 20

Answer: C



**69.** In the network shown in figure each resistance is  $1\Omega$  . The effective resistance

between A and B is



A. 
$$\frac{4}{3}\Omega$$
  
B.  $\frac{3}{2}\Omega$   
C.  $7\Omega$ 

D. 
$$\frac{8}{7}\Omega$$

### Answer: D

Watch Video Solution

**70.** n equal resistors are first connected in series and then connected in parallel. What is the ratio of the maximum to the minimum resistance ?

A. n

B.  $1/n^2$ 

 $\mathsf{C.}\,n^2$ 

 $\mathsf{D}.1/n$ 

#### Answer: C





**71.** The masses of the three wires of copper are in the ratio 1 : 3 : 5. And their lengths are in th ratio 5 : 3 : 1. the ratio of their electrical resistance is

A. 1:3:5

B. 5: 3: 1

C. 1: 25: 125

D. 125:15:1

# Answer: D



72. Two batteries of e.m.f. 4V and 8V with internal resistances  $1\Omega$  and  $2\Omega$  are connected in a circuit with a resistance of  $9\Omega$  as shown in figure. The current and potential difference between the points P and Q



A. 
$$\frac{1}{3}A$$
 and  $3V$   
B.  $\frac{1}{6}A$  and  $4V$   
C.  $\frac{1}{9}A$  and  $9V$   
D.  $\frac{1}{12}A$  and  $12V$ 

# Answer: A

