



## PHYSICS

# **BOOKS - CENGAGE PHYSICS (HINGLISH)**

# **HEATING EFFECT OF CURRENT**

#### Illustration

**1.** Two wires of same mass , having ratio of lengths 1:2, *density*1:3, and respectively2:1, are connected one by one to the same volltage supply. The rate of

heat dissipation in the wire is found to be 10W. Find

the rate of heat dissipation in the second wire.



**2.** A 100W bulb is designed to operate on a potential difference of 230V.

(i) Find the resistance of the bulb.

(ii) Find the current drawn by the bulb if it is operated

at a potential difference for which it is designed.

(iii) Find the current drawn and power consumed by

the bulb if it is connected to a 200V supply.



**3.** A 500W heating unit is designed to operate from a 200V line . By what percentage will its heat output drop if the line voltage drops to 160V? Find the heat produced by it in 10 min .

Watch Video Solution

**4.** Two bulbs are marked 220V - 100W and 220V - 50W.

(i) Which bulb will produce more illumination if they are connected in parallel to a 220V supply? (iii) Also find the total power consumed by both the bulbs in each of the two parts above.



5. Two bulbs are rated 30W - 200V and 60W - 200V. They are connected with a 400V power supply. Find which bulb will get fused if they are connected in (i) series and (ii) parallel.



**6.** An electric tea kettle has two heating coils. When one of the coils is switched on , boiling begins in  $6 \min$ . When the other coil is switched on , boiling begins in 8 min . In what time will the boiling begin if both coils are switched on simultaneously (i) in series and (ii) in parallel.



7. How will you connect ( series and parallel ) 24cells

each of internal resistance  $1\Omega$  to get maximum power

output across a load of  $10\Omega$ ?



**8.** A dry cell of emf 1.5V and internal resistance  $0.10\Omega$ 

is connected across a resistor in series with a very low

resistance ammeter. When the circuit is switched on , the ammeter reading settles to a steady value of 2.0A

(i) What is the steady rate of chemical energy consumption of the cell ?

What is the steady rate of energy dissipation inside the cell ?

(ii) What is the steady rate of energy dissipation inside the cell ?

(ii) What is the steady rate of energy dissipation

inside the resistor ?

•

(iv) What is the steady power out put of the source?

Watch Video Solution

**9.** Two wires made of tinned copper having identical cross section  $(=10^{-6}m^2)$  and lengths 10 and 15*cm* are to be used as fuses. Show that the fuses will melt at the same value of current in each case.



# 10. An electric kettle taking 3Aat210V brings 1L of water from $20^\circ C o 80^\circ Cin10$ min . Find its efficiency.



**11.** A line having a total resistance of  $0.2\omega$  delivers 10KWat220V to a small factory . Calculate the efficiency of transmission .

Watch Video Solution

#### Solved Examples

**1.** A series battery of six cells each of emf2V and internal resistance  $0.5\Omega$  is charged by a 100Vdcsupply. What resistance should be used in the charging circuit in order to limit the charging current to 8A. Using this relation , obtain (a) the powwer supplied by the dc source, (b) the power dissipated as heat , and (c) the chemical energy stored in the

battery in  $15 \min$ .



**2.** Dertermine the current through the battery of internal resistance  $0.5\Omega$  for the circuit shown in fig. 7.14. How much power is dissipated in  $6\omega$  resistance ?



**3.** Two uniform wires of same material , each weighing 1g but one having double the length of the other, are connected in series , carrying a current of 10A. The length of the longer wire is 20cm. Calculate the rate of consumption of energy in each of the two wires. which wire gets hotter ? The density of the material of the wire is  $20 \times 10^{-5} \Omega cm$ .

Watch Video Solution

**4.** In a house having 220V line , the following appliances are operating :

(i) a 60W bulb, (ii) a 1000W heater , and (iii) a40W radio.

Calculate (a) the current drawn by the heater and (b)

the current passing through the fuse in the main line.

Watch Video Solution

**5.** A heater is designed to operate with a power of 1000 walts in a 100 volt line. It is connected in a combinations with a resistance of 10 ohms and a resistance R to a 100 volts mains as shown in figure. What should be the value of R so that the heater operates with a power of 62.5 watts.



**6.** (i). Find the time taken by a filament of 200W to heat 500ml of water from  $25^{\circ}C \rightarrow 75^{\circ}C$ . Specific heat of water is  $1calg^{-1} \circ C^{-1}$ . Take 1cal = 4.2J. (ii) Find the power produced by each resistor shown in Fig. 7.17. If  $R_1$  is dipped in 1000ml of water at  $30\,^\circ\,C$  , find the time taken by it to boil the water.



7. A heating coil of 2000W is immersed in water . How much time will it take in raising the temperature of 1L of water from  $4^{\circ}C$ to $100^{\circ}C$ ? Only 80% of the thermal energy produced is used in raising the temperature of water. **8.** Consider the following circuit (*Fig.* 7.18) where some resistances have been arranged in a definite order . With the given condition that heat produced by  $6\Omega$  resistance is  $60cals^{-1}$  due to the current flowing throught it , find out the heat produced across  $2\Omega$  resistance in calorie per second.





**9.** Consider a wheatstone bridge PQRS as shown in

Fig.7.19wherecurrentI

 $is \in the \circ uitoffour resis an ces$ 10 ,20 ,30, and 40

Omega

 $. \ F \in dtheratio of the heat \geq \ 
eq rated \in the four arms$ 

PQ,QR, PS, and SR`.

View Text Solution

**10.** A person with body resistance between his hands of  $10K\Omega$  accidentally grasps the terminals of a 18kVpower supply.

(i) If the internal resistance of the power supply is  $2000\Omega$ , what is the power dissipated in his body?

(ii) What is the power dissipated in his body?

(iii) If the power supply is to be made safe by increasing its internal resistance, what should the internal resistance be for the maximum current in the above situation to be 1.00mA or less?



Watch Video Solution

**11.** An electric kettle has two coils of same power . When one coil is switched on , it takes 15 min to boil water , and when the second coil is switched on , it takes 30 min . How long will it take to boil water when both the coils are used in *i*. Series and *ii*. parallel?



12. What amount of heat will be generated in a coil of resistance R due to a charge q passing through it if the current in the coil a. decreases down to zero uniformly during a time

interval  $t_0$ ?

b. decrases down to zero having its value every  $t_0$  seconds?



13. A variable capacitor is adjusted to its lowest capacitance  $C_0$  and is connected with a source of constant voltage V for a long time. The resistance of connecting wires is R. At t = 0, its capacitance starts to increase so that a constant current I starts to flow through the circuit. Calculate at time t, (i) Power supplied by the source

(ii) thermal power generated in the connecting wire

(iii) rate of increase of electrostatic energy stored in capacitor

(iv) What do you infer from the above three results?

Watch Video Solution

1. (a) what is the rate at which energy being delivered to a light bulb higher : just after it is turned on , the glow of the filament is increasing, or after it has been on for a few seconds and the glow is steady? (b) IF a piece of wire is used to connect points b and c in Fig. 7.9, does the brightness of bulb  $R_1$ increase, decrease or stay constant? What happens to the brightness of bulb  $R_2$  ? (  $I_1 = I_2 = I$  ) (c) Compare the brightness of four identical light bulbs in Fig. 7.10. What happens if the bulb A fails so that it cannot conduct ? What if C fails ? What if D fails?

(d) If electric power is transmitted over long distances, the resistance of the wires becomes significant. Why? Which mode of transmission would result in less energy losss: high current and low voltage or low current and high voltage? Discuss. (e) In Fig. 7.11, describe wha happens to the light bulb after the switch is closed . Assume the capacitor has a large capacitance and is initially uncharged. (f) Astuident claims that a second light bulb in series is less bright than the first, because the first bulb uses up some of the current. How would you respond to this statement?

(g) If you were to design an electeric heater using nichrome wire as the heating element , what parameters of the wire would you vary to meet a specific power output, sch as 1000W?







**2.** A heater joined in series with a 50W bulb is connected to the mains . If the 50W bulb is replaced by a 100W bulb , then will the heater now give more heat , less heat, or same heat ? Why ?

Watch Video Solution

**3.** Each of three resistors in fig. 7.12 has a resistance of  $2\Omega$  and can dissipate a maximum of 18W without becoming excessively heated. Find the maximum



**4.** An electric bulb rated 220V and 60W is connected in series with another electric bulb rated 220V and 40W. The combination is connected across a source of emf220V. Which bulb will glow more?



5. We have a 30W, 6V bulb , which we want to glow

by a supply of 120V . What can be done for this ?

Watch Video Solution

**6.** Two heater coils made of the same material are connected in parallel across the mains : the length and the diameter of one coil is double that of the other . Which of them will produce more heat?



7. A series circuit consists of three identical lamps connected to a battery as shown in Fig. 7.13. when the switch S is closed, what happens (a) to the intensities of lamps A and B, (b) to the intensity of lamp C, (c) to the current in the circuit, and (d) to the voltage drop across the three lamps? Does the power dissipated in the circuit increase, decrease, or remain the same?



Watch Video Solution



8. Two wires of the same material and having the same uniform area of cross section are connected in an electric circuit. The masses of the wires are m and 2m, respectively. When a current I flows through both of them connected in series, then find the ratio of heat produced in them in a given time .

### Watch Video Solution

**9.** Water boils in an electric kettle in  $15 \min$  after being switched on . Using the same main supply , should the length of the heating element be

increased or decreased if the water is to be boiled in

 $10 \min$ ? Why?



10. An electric motor operating on a 50Vdc supply draws a current of 12A. If the efficiency of the motor is 30%, estimate the resistance of the windings of the motor.



11. A fuse with a circular cross - sectional radius of

0.15mm blows at 15A. What should be the radius of

the cross section of a fuse made of the same material

that blows at 30A?



Watch Video Solution

**13.** The walls of a closed cubical box of edge40cm are made of a material of thickness 1mm and thermal conductivity  $4 \times 10^{-4} cals^{-1} C^{-1}$ . The interior of the box is maintained at  $100^{\circ}C$  above the outside temperature by a heater placed inside the box and connected across 400Vdc. Calculate the resistance of the heater.



#### Watch Video Solution

14. Two tungsten lamps with resistances  $R_1$  and  $R_2$ , respectively, are connected first in parallel and then in series in a lighting circuit of negligible internal resistance. Given  $R_1 > R_2$ .

(a) Which lamp will glow more brightly when they are connected in parallel ?

(b) If the lamps of resistance  $R_1$  now burns out, how

will the net illumination produced change ?

(c ) Which lamp will glow more brightly when they are

connected in series ?

(d) If the lamp of resistance  $R_2$  now burns out and

lamp  $R_1$  alone is plugged in , will the net illumination

increase or decrease ?

Watch Video Solution

**15.** n identical bulbs are connected in series and illuminated by a power supply. One of the bulbs gets fused. The fused bulb is removed , and the remaining bulbs are again illuminated by the same power

supply. Find the fractional change in the illuminated

of (a) all the bulbs and (b) one bulb.



**16.** An electric motor is designed to work at 100V and draws a current of 6A. The output power supplied by the motor is 150W, and the remaining of the motor and its percentage efficiency?



**17.** A house is fitted with certain numbers of 100W, 230V incandescent lamps. The power to the

house is fed by a generator producing the power at 240V. The resistance of the wires from the generator to the house is  $2\Omega$ . Find the maximum number of lamps that can be illuminated so that the voltage across none of the lampsdrops below 230V.



## Watch Video Solution

**18.** A house is fitted with seven tubelights of rating 220V, 40W each , two bulbs of rating 220V, 60W each, five fans each drawing a current of 0.4at220V, and a heater of resistance  $48.4\Omega$ . The main line power supplied to the house is at 220V. Calculate the bill for the month of january if tubelights and bulbs are used

for 6h daily, fans for 1h daily , and heater for 10h

daily. The electricity is to cost  $Rs. \ 2per$  unit.

Watch Video Solution

**19.** Two bulbs are marked 200V, 300W and 200V, 600W, respectively. The bulbs are connected in series and the combination is connected to a 200V supply.

(a) Which bulb will produce more illumination ?

(b) Find the total power consumed by both the bulbs.

(c) Find the total power consumed if both the bulbs

were connected in parallel.



**20.** A servo voltage stabiliser restricts the voltage output to  $220V \pm 1 \%$ . If an electric bulb rated at 220V, 100W is connected to it, what will be the minimum and maximum power consumed by it?

Watch Video Solution

**21.** The efficiency of a cell when connected to a resistance R is 60 %. What will be its efficiency if the external resistance is increased by six times?



**22.** A 25W, 220V bulb and a 100W, 220V bulb are connected in series across a 220V line , which electric bulb will glow brightly?

0	Watch Video Solution	
---	----------------------	--

## Subjective

**1.** A circuit shown in the figure has resistances  $20\Omega$ and  $30\Omega$ . At what value of resistance  $R_x$  will the thermal power generated in it be practically independent of small variations of that resistance? The voltage between points A and B is supposed to
be constant in this case.





- **2.** A 1kW heater is meant to operate at 200V.
- (a) What is the resistance?
- (b) How much power will it consume if the line voltage drops to 100V?
- ( c ) How many units of electrical energy will it

consume in a month (of 30 days) if it operates 10h

daily at the specified voltage (200V)?



# Watch Video Solution

**3.** A resistor  $R_1$  consumes electrical power  $P_1$  when connected to an  $emf\varepsilon$ . When resistor  $R_2$  is connected to the same emf, it consumes electrical power  $P_2$ . In terms of  $P_1$  and  $P_2$ , what is the total electrical power consumed when they are both connected to this emf source

(a) in parallel

(b) in series

4. In a experiment, N identical electrical bulbs, each having resistance R, are connecteed in parallel to a dc source of emf E and internalresistance r. What is the power consumed by each bulb. Also find the percentage change in power by each bulb if one bulb turns out.



**5.** In the circuit shown in fig. 7.24, all the resistors are rated at a maximum power of 1.00W. What is the maximum  $emf\varepsilon$  that the battery can have without

burning up any of the resistors?



**6.** In the circuit shown in Fig 7.25,

(a) what must the emfarepsilon of the battery be in order for

a current of 2.00A to flow through the 5.00V battery

, as shown ? In the polarity of the battery correct as

shown?

b. How long does it take for 60.0J of thermal energy

to be produced in the  $10.0\Omega$  resistor?



7. If two bulbs of 25W and 100W rated at 220V are connected in series across a 440V supply, will both the bulbs fuse ? If not which one ?



**8.** Three 60W, 120V light bulbs are connected across a 120V power lines as shown in Fig. 7.26. Find (a) the voltage across each bulb and (b) the total power dissipated in the three bulbs.





**1.** The operating temperature of the filament of lamp is  $2000^{\circ}C$ . The temperature coefficient of the material of the filament is  $0.005^{\circ}C^{-1}$ . If the atmospheric temperature is  $0^{\circ}C$ , then the current in the 100W - 200V lamp when it is switched on is nearest to

 $\mathsf{A.}\,2.5A$ 

 ${\rm B.}\,3.5A$ 

C.4.5A

 $\mathsf{D.}\,5.5A$ 

## Answer: D



**2.** In the circuit in Fig. 7.27, bulb B does not glow although ammeter A indicates that the current is flowing . Why does the bulb not glow?



A. The bulb is fused .

B. tThere is a break in the circuit between bulb

and ammeter.

C. The variable resistor has too large resistance.

D. There is a break in the circuit between the bulb

and the variable resistance.

Answer: C



**3.** Three bulbs  $B_1$ ,  $B_2$  and  $B_3$  are connected to the mains as shown in Fig. 7.28. How will the brightness of bulb  $B_1$  be affected  $B_2$  or  $B_3$  are disconnected

# from the circuit?



A. Bulb  $B_1$  becomes brighter

- B. Bulb  $B_1$  becomes dimmer.
- C. No change occurs in the brightness.
- D. Bulb  $B_1$  becomes brighter if bulb  $B_2$  is disconnected and dimmer if bulb  $B_3$  is disconnected.

## Answer: A



**4.** Three identical cells , each having an emf1.5V and a constant internal resistance  $2.0\omega$ , are connected in series with a  $4.0\omega resis \rightarrow rR$ , first as in circuit (i) , and second as in circuit (ii) . Then

( power in R in circuit (i))/( Power in R in circuit (ii)) =



A. 9.0

 $\mathsf{B.}\,7.2$ 

 $C.\,1.8$ 

D. 3.0

Answer: A

Watch Video Solution

5. All bulbs in the circuit shown in figure are identical.

Which bulb glows most brightly?



# A. 1

- $\mathsf{B.}\,2$
- C. 3
- $\mathsf{D.}\,4$

## Answer: A



**6.** Which of two switches  $S_1$  and  $S_2$  shown in Fig.

7.31 will produce short - circuiting?



## A. $S_1$

 $\mathsf{B.}\,S_2$ 

- C. Both  $S_1$  and  $S_2$
- D. Neither  $S_1 n$  or  $S_2$

#### Answer: B



7. Three similar light bulbs are connected to a constant to a constant voltage dc supply as shown in Fig. 7.32. Each bulb operates at normal brightness and the ammeter ( of negligible resistance) registers a steady current. The filament of one of the bulbs breaks. What happens to the ammeter reading and to the brightness of the remaining bulbs?



A. Ammeter reading - increases, Bulb brightness -

increases

B. Ammeter reading - increases, Bulb brightness -

unchanged

C. Ammeter reading - unchanged , Bulb brightness

- unchanged

D. Ammeter reading - decreases, Bulb brightness -

unchanged

Answer: D

Watch Video Solution

**8.** The circuit shownin Fig. 7.33 contains a battery , a rheostat , and two identical lamps. What will happen to the brightness of the lamps if the resistance of the rheostat is increased?



A. Lamp P - Less bright , Lamp Q - Brighter

B. Lamp P - Less brighter , Lamp Q - Less brighter

C. Lamp P - Brighter , Lamp Q - Less brighter

D. Lamp P - No change , Lamp Q - Brighter

### Answer: A

# Watch Video Solution

**9.** A cell of internal resistances r is connected to a load of resistance R. Energy is dissipated in the load, but some thermal energy is also wasted in the cell. The efficiency of such an arrangement is found from the expression (Energy dissipated in the load )/(Energy dissipated in

the complete circuit)

Which of the following gives the efficiency in this case?

A. 
$$\frac{r}{R}$$
  
B.  $\frac{R}{r}$   
C.  $\frac{r}{R+r}$   
D.  $\frac{R}{R+r}$ 

#### Answer: D



10. Two identical batteries each of emf E=2volt and internal resistance r=1 ohm are available t. produce

heat in an external resistance by passing a current through it. What is the maximum power that can be developed across an external resistance R using these batteries?

A. 1W

 $\mathsf{B.}\,2W$ 

 $\mathsf{C.}\,4W$ 

D. 8W

Answer: B

**Watch Video Solution** 

**11.** Two similar headlight lamps are connected in parallel to each other. Together , they consume 48W from a 6V battery . What is the resistance of each filament ?

A.  $6\Omega$ 

 $\mathrm{B.}\,4\Omega$ 

 $\mathsf{C}.\,3.0\Omega$ 

D.  $1.5\Omega$ 

Answer: D



12. Two electric bulbs , rated for the same voltage , have powers of 200W and 100W, respectively. If their resistances are  $r_1$  and  $r_2$ , respectively, then

A. 
$$r_1=2r_2$$

B. 
$$r_2=2r_1$$

C. 
$$r_2=4r_1$$

D. 
$$r_1=4r_2$$

#### Answer: B



13. If the current in an electric bulb decreases by 0.5~%, the power in the bulb decreases by approximately

A. 1~%

 $\mathsf{B.}\,2\,\%$ 

 $\mathsf{C}.\,0.5\,\%$ 

D. 0.25~%

Answer: A

Watch Video Solution

**14.** An electric bulb rated for 500W at 100V is used in a circuit having a 200V supply. The reistance R that must be put in series with bulb, so that the bulb delivers 500W is ......Ω.

A.  $18\Omega$ 

 $\mathsf{B.}\,20\Omega$ 

 $\mathsf{C.}\,40\Omega$ 

D.  $700\Omega$ 

Answer: B



**15.** A  $1^{\circ}C$  rise in temperature is observed in a conductor by passing a certain current. If the current is doubled , then the rise in temperature is approximately

A.  $2.5^{\,\circ}\,C$ 

 $\mathsf{B.4}^\circ C$ 

C.  $2^\circ C$ 

D.  $1^\circ C$ 

#### Answer: B



16. Two electric bulbs have tungsten filament of same length. If one of them gives 60W and the other 100W, then

A. 100W bulb has thicker filament

B. 60W bulb has thicker filament

C. both filaments are of same thickness

D. it is not possible to get different wattages

unless the lengths are different

**Answer: A** 

Watch Video Solution

17. n identical light bulbs, each designed to draw P power from a certain voltage supply, are joined in series across that supply. The total power which they will draw is

A. nP

 $\mathsf{B}.\,P$ 

 $\mathsf{C}.P/n$ 

D.  $P/n^2$ 

### Answer: C



**18.** How many calories of heat will be approximately developed in a 210W electric bulb in 5 min ?

A. 15,000

**B**. 1050

C. 63, 000

D. 80, 000

Answer: A



**19.** A constant voltage is applied between the two ends of a metallic wire . If both the length and the radius of the wire are doubled , the rate of heat developed in the wire will

A. be halved

B. be doubled

C. remain the same

D. be quadrupled

**Answer: B** 



20. The power rating of an electric motor that draws a

current of 3.75A, when operated at 200V, is nearly

A. 54W

B.1hp

 $\mathsf{C.}\,500W$ 

D. 750hp

Answer: B



**21.** A cable of resistance  $10\Omega$  carries electric power from a generator producing 250kWat10,000V. The current in the cable is

A. 1000A

 $\mathsf{B.}\,250A$ 

 $\mathsf{C.}\,100A$ 

 $\mathsf{D.}\,25A$ 

Answer: D

Watch Video Solution

22. In the previous problem , the power lost in the

cable during transmission is

A. 3.15kW

 $\mathsf{B}.\,12.5kW$ 

 $\mathsf{C.}\, 6.25 kW$ 

D. 25kW

Answer: C



23. The heat generated through  $4\Omega$  and  $9\Omega$  resistances separately, when a capacitor pf 100myF capacity charged to 200V is discharged one by one, will be

- A. `2 J and 8 J, respectively
- B. `8 J and 2 J, respectively
- C. `2 J and 4 J, respectively
- D. `2 J and 2 J, respectively

#### Answer: D



24. If the length of the filament of a heater is reduced

by 10~% , the power of the heater will

A. increases by about 9~%

B. increases by about  $11\,\%$ 

C. increases by about 19~%

D. decreases by about 10~%

Answer: B



**25.** A 2kW heater used for 1h every day consumes the

following electrical energy in 30 days

A. 60units

 ${\tt B.}\,120 units$ 

 ${\sf C}.\,15 units$ 

D. none of the above

Answer: A



**26.** Two cells , each of emfE and internal resistance r, are connected in parallel across a resistor R. The power delivered to the resistor is maximum if R is equal to

A. r/2

 $\mathsf{B.}\,r$ 

 $\mathsf{C.}\,2r$ 

D. 0

Answer: A


**27.** A constant voltage is applied between the two ends of a uniform metallic wire. Some heat is developed in it. The heat developed is doubled if

A. both the lengths and radius of the wire are halved

B. both the length and radius of the wire are doubled

C. the radius of the wire is doubled

D. the length of the wire is doubled

Answer: B



**28.** A given resistor cannot carry currents exceeding 20*A*, without exceeding its maximum power dissipaation ratings . By forced air cooling suppose that we increase the rate at which heat can be carried by a factor of 2. Now the maximum current that the resistor can carry is

A. 10A

B.  $20\sqrt{2}A$ 

C.  $30\sqrt{2}A$ 

D. 40A

Answer: B



**29.** A wire when connected to 220 V mains supply has power dissipation  $P_1$ . Now the wire is cut into two equal pieces which are connected in parallel to the same supply. Power dissipation in this case is  $P_2$ . Then  $P_2: P_1$  is

**A.** 1

B.4

 $\mathsf{C.}\,2$ 

D. 3



**30.** A 220 volt, 1000 watt bulb is connected across a 110 volt mains supply. The power consumed will be

A. 1000W

 $\mathsf{B.}\,750W$ 

 $\mathsf{C.}\,500W$ 

 $\mathsf{D.}\,250W$ 

AAVELEN AND DE MELLER DE

Answer: D



**31.** A heater coil is cut into two equal parts and only one part is now used in the heater. The heat generated will now be

A. `halved

B. one - fourth

C. four times

D. doubled

Answer: D



**32.** Three  $10\Omega$ , 2W resistors are connected as in Fig. 7.34. The maximum possible voltage between points A and B without exceeding the power dissipation limits of any of the resistors is



A.  $5\sqrt{3}V$ 

B.  $3\sqrt{5}V$ 

 $\mathsf{C}.\,15V$ 

D. 
$$\frac{5}{3}V$$

Answer: B



**33.** A torch bulb rated 4.5W, 1.5V is connected as shown in Fig. 7.35. The emf of the cell needed to make the bulb glow at full intensity is



A. 4.5V

 $\mathsf{B}.\,1.5V$ 

 $\mathsf{C.}\,2.67V$ 

 $\mathsf{D}.\,13.5V$ 

Answer: D

Watch Video Solution

**34.** A heater is designed to operate with a power of 1000W in a 100V line. It is connected in combination with a resistance of  $10\Omega$  and a resistance R, to a 100V mains as shown in figure. What will be the value

of R so that the heater operates with a power of 62.5W?



A.  $5\Omega$ 

- $\mathsf{B.}\,10\Omega$
- $\mathsf{C}.\,15\Omega$
- D.  $20\Omega$

Answer: C



**35.** The supply voltage to room is 120 V. The resistance of the lead wires is  $6\Omega$ . A 60 W bulb is already switched on. What is the decrease of voltage across the bulb, when a 240 W heater is switched on in parallel to the bulb?

A. no change

 $\mathsf{B.}\,10V$ 

 $\mathsf{C.}\,20V$ 

D. more than 10V

Answer: D



**36.** Figure 7.37 shows a network of three resistances. When some potential difference is applied across the network , thermal powers dissipated by A, B and Care in the ratio



A. 2:3:4

B. 2:4:3

C.4:2:3

D. 3:2:4

## Answer: C



**37.** Resistors P, Q, and R in the circuit have equal resistances. If the battery is supplying a total power of 12W, what is the power dissipated as heat in resistors R?



 $\mathsf{A.}\ 2W$ 

 $\mathsf{B.}\, 6W$ 

 $\mathsf{C.}\, 3W$ 

 $\mathsf{D.}\,8W$ 

Answer: A

Watch Video Solution

**38.** Three bulbs of 40W, 60W and 100W are connected in series with a 240V source.

A. The potential difference will be maximum across

the 40W bulb .

B. The current difference will be maximum in

 $100W {\rm \ bulb}.$ 

C. The resistance of the 40W bulb is minimum.

D. The current through the 60W bulb will be 0.1A.

Answer: A

**Watch Video Solution** 

**39.** In the circuit shown in fig the heat produced in the 5 ohm resistor due to the current flowing

through it is 10 calories per second.



The heat generated in the 4 ohms resistor is

- A.  $1Cals^{-1}$
- B.  $2Cals^{-1}$
- C.  $3Cals^{-1}$
- D.  $4Cals^{-1}$

#### Answer: B



**40.** A battery of internal resistance  $4\Omega$  is connected to the network of resistance as shown . In order that the maximum power can be delivered to the network, the value of R in  $\Omega$  should be



A.  $\frac{4}{9}$ 

C. 
$$\frac{8}{3}$$

D. 18

#### Answer: B

Watch Video Solution

**41.** Four resistances carrying a current shown in Fig. 7.41 are immersed in a box containing ice at  $0^{\circ}C$ . How much ice must be put in the box every 10 min to keep the average quantity of ice in the box

constant? Latent heat of ice is  $80 calg^{-1}$ .



A. 1.190 kg

 $\mathsf{B}.\,3.20kg$ 

C. 4.2kg

D.0.25kg

**Answer: A** 



**42.** The three resistance of equal value are arranged in the different combination shown below. Arrange them in increasing order of power dissipation.





# A. III < II < IV < I

 ${\rm B.}\,II < III < IV < I$ 

 ${\rm C.}\,I < IV < III < II$ 

 $\mathsf{D}.\, I < III < II < IV$ 

### Answer: A



**43.** An ideal gas is filled in a closed rigid and thermally insulated container. A coil of  $100\Omega$  resistor carrying current 1 A for 5 minutes supplies heat to the gas. The change in internal energy of the gas is

A. 10kJ

 $\mathsf{B.}\, 30kJ$ 

C. 20kJ

D. 0kJ

## Answer: B



44. The resistance in which the maximum heat is

produced is given by (Fig. 7.43)



A.  $2\omega$ 

 $\mathsf{B.}\,6\Omega$ 

 $\mathsf{C.}\,4\Omega$ 

D.  $12\Omega$ 

Answer: A

Watch Video Solution

**45.** The resistance of hot tungsten filament is about 10 times the cold resistance. What will be the resistance of 100 W and 200 V lamp when not in use?

A. 14,  $000\Omega$ 

 $\mathrm{B.}\,400\Omega$ 

 ${\rm C.}~40\Omega$ 

D.  $4\Omega$ 

Answer: C

**Watch Video Solution** 

46. The resistance of the filament of a lamp increases with the increase in temperature. A lamp rated 100W and 220V is connected across 220V power supply. If the voltage drops by 10%, then the power of the lamp will be

A. 90W

 $\mathsf{B.}\,81W$ 

C. between 90W and 100W

D. between 81W and 90W

Answer: D

Watch Video Solution

**47.** A wire of length L and 3 identical cells of negligible internal resistance are connected in series. Due to the current, the temperature of the wire is raised by  $\Delta T$  in a time t. A number N of similar cells is now

connected in series with a wire of the same material and cross-section but of length 2L. The temperature of the wire is raised by the same amount  $\Delta T$  in the same time t. the value of N is

**A.** 4

**B**. 6

**C**. 8

D. 9

Answer: B

**48.** An electric immersion heater of 1.08kW is immersed in water . After it has reaches a temperature of  $100^{\circ}C$  , how much time will be required to produce 100g of steam?

A. 50*s* 

 $\mathsf{B.}\,420s$ 

 $\mathsf{C}.\ 105s$ 

 $\mathsf{D.}\ 210s$ 

**Answer: D** 



**49.** Two electric bulbs A and B are rated 60 and 100W, respectively. If they are connected in parallel to the same source , then

A. both the bulbs draw the same current

B. bulb A draws more current than bulb B

C. bulb B draws more current than bulb A

D. currents drawn in the bulbs are in the ratio of

their resistances

Answer: C

**50.** A 25W, 220V bulb and a 100W, 220V bulb are connected in series across a 220V line , which electric bulb will glow brightly?

A. 25W bulb

B. 100W bulb

C. Both will have equal incandescence.

D. Neither will give light.

Answer: A

**51.** Two identical heaters rated 220V, 1000W are paced in series with each other across 220V line , then the combined power is

A. 1000W

 $\mathsf{B.}\,2000W$ 

 $\mathsf{C.}\ 500W$ 

 $\mathsf{D.}\,4000W$ 

Answer: C

**52.** Figure 7.44 shows three similar lamps  $L_1, L_2$ , and  $L_3$  connectged across a power supply. If the lamp  $L_3$  fuses, how will the light emitted by  $L_1$  and  $L_2$  change?



A. no change

B. brillance of  $L_1$  decreases and that of  $L_2$  increases

C. brilliance of both  $L_1$  and  $L_2$  increases

D. brillance of both  $L_1$  and  $L_2$  decreases

# Answer: B

**Watch Video Solution** 

53. If a wire of resistance  $20\Omega$  is covered with ice and a voltage of 210V is applied across the wire , then the

rate of melting of ice is

A.  $8.85 gs^{-1}$ 

B.  $1.92 g s^{-1}$ 

C.  $6.56 gs^{-1}$ 

D. none of these



 $\mathsf{B.}\,22$ 

C. 33

D. 66

### Answer: B

AATLE LATEL CLEEP



**55.** It takes 16 min to boil some water in an electric kettle. Due to some defect it becomes necessary to remove 10 % turns of the heating coil of the kettle . After repairs , how much time will it take to boil the same mass of water ?

A. 17.7 min

**B**. 14.4 min

C. 20.9 min

D. 13.7 min

Answer: B

**56.** A electric kettle (rated accurately at 2.5kW) is used to heat 3kg of water from  $15^{\circ}C$  to boiling point . It takes  $9.5 \min$  . Then the amount of heat that has been lost is

A.  $3.5 imes 10^5 J$ 

B.  $7 imes 10^8 J$ 

C.  $3.5 imes 10^4 J$ 

D.  $7 imes 10^8 J$ 

## Answer: A





**57.** How many 60W lamps may be safely run on a 230V circuit fitted with a 5A fuse?

 $\mathsf{A.}\ 2$ 

B.19

 $\mathsf{C.}\,20$ 

**D.** 4

#### Answer: B
**58.** If a given volume of water in a 220V heater is boiled in 5 min , then how much time will it take for the same volume of water in a 110V heater to be boiled?

A. 20 min

B. 30 min

C. 25 min

D. 40 min

Answer: A



**59.** The charge flowing through a resistance R varies with time t as  $Q = at - bt^2$ . The total heat produced in R is

A. 
$$\frac{a^{3}R}{6b}$$
  
B. 
$$\frac{a^{3}R}{3b}$$
  
C. 
$$\frac{a^{3}R}{2b}$$
  
D. 
$$\frac{a^{3}R}{b}$$

**Answer: A** 

# Watch Video Solution

**60.** A 100W bulb designed to operate on 100V is to be connected across a 500V source . Find the resistance to be put in series so that bulb consumes 100W only.

A.  $100\Omega$ 

 $\mathrm{B.}\,500\Omega$ 

 $\mathsf{C.}\,400\Omega$ 

D.  $300\Omega$ 

Answer: C



**1.** Two electric bulbs rated 25W, 220V and 100W, 220V are connected in series across a 220V voltage source . The 25W and 100W bulbs now draw  $P_1$  and  $P_2$  powers , respectively.

A. 
$$P_1=16W$$

B. 
$$P_1 = 4W$$

C. 
$$P_2 = 16W$$

D. 
$$P_2 = 4W$$

Answer: A::D

Watch Video Solution

2. A voltmeter and an ammeter are connected in series to an ideal cell of emfE. The voltmeter reading is V, and the ammeter readings is I. Then (i) V < E (ii) the voltmeter resistance is V/I(iii) the potential difference across the ammeter is E - V

(iv) Voltmeter resistance + ammeter resistance = E//I`Correct statements are

A. I and ii

B. ii and iii

C.iii and iv

D. all

Answer: A::B::C::D



A. Power supplied by the battery is 200W

B. current flowing in the circuit is 5A

C. Potential difference across the  $4\Omega$  resistance is

equal to the potential difference across the  $6\Omega$ 

resistance

D. current in wire AB is zero

Answer: A::C

**Watch Video Solution** 

4. Two bulbs consume same energy when operated at

200V and 300V, respectively. When these bulbs are

connected in series across a dc source of 500V, then

A. ratio of potential difference across them is  $3\,/\,2$ 

B. ratio of potential difference across them is 4/9

C. ratio of power produced in them is 2/3

D. ratio of power produced in them is 2/3

**Answer: B** 

**Watch Video Solution** 

5. An element with  $emf\varepsilon$  and interval resistance r is connected across an external resistance R. The maximum power in external circuit is 9W. The current flowing through the circuit in these conditions is 3A. Then which of the following is // are correct ?

A. 
$$arepsilon=6V$$

$$\mathsf{B.}\,r=R$$

C. 
$$r=1\Omega$$

D. 
$$r=3\Omega$$

## Answer: A::B::C



**Assertion Reasoning** 

**1.** Statement I : The wires supplying current to an electric heater are not heated appreciably. Statement II: Resistance of connecting wires is very small and  $H \propto R$ .

A. Statement I is True , Statement II is True , Statement II is a correct explanation for Statement I.

B. Statement I is True, Statement II is True, Statement II is NOT a correct explanation for statement I.

C. Statement I is True, Statement is False.

D. Statement I is False, Statement II is True.

### Answer: A

Watch Video Solution

2. Statement I : If the current of a lamp increases by 20%, the percentage increases in the illumination of the lamp is 40%. Statement II : Illumination of the lamp is directly

proportional to the square of the current through the lamp.

A. Statement I is True, Statement II is True,

Statement II is a correct explanation for Statement I.

B. Statement I is True, Statement II is True,

Statement II is NOT a correct explanation for

statement I.

C. Statement I is True, Statement is False.

D. Statement I is False, Statement II is True.

#### Answer: D

Watch Video Solution

3. Statement I: Heater wire must have high resistance than connecting wires and high netallic point.
Statement II : If resistance is high , the electrical conductivity will be less.

A. Statement I is True , Statement II is True , Statement II is a correct explanation for Statement I.
B. Statement I is True, Statement II is True , Statement II is NOT a correct explanation for statement I.

C. Statement I is True, Statement is False.

D. Statement I is False, Statement II is True.

## Answer: B



**4.** Statement I : In the circuit in Fig. 7.46, both cells are ideal and of fixed emf, the resistor  $R_1$  has fixed resistance and the resistance of resistor  $R_2$  can be varied ( but  $R_2$  is always non zero). Then the electric power delivered to the resistor of resistance  $R_1$  is independent of the value of resistance  $R_2$ . Statement II: If potential difference across a fixed

resistance is unchanged , the poweer delivered to the

resistor remains constant.



A. Statement I is True , Statement II is True , Statement II is a correct explanation for Statement I.
B. Statement I is True, Statement II is True , Statement II is NOT a correct explanation for statement I.

C. Statement I is True, Statement is False.

D. Statement I is False, Statement II is True.

## Answer: A



**5.** Statement I: Since all the current coming to our house returns to powerhouse (as current travels in a closed loop), there is no need to pay the electricity bill.

Statement II: The electricity bill is paid for the power used , not for the current used.

A. Statement I is True, Statement II is True,

Statement II is a correct explanation for Statement I.

B. Statement I is True, Statement II is True,

Statement II is NOT a correct explanation for

statement I.

C. Statement I is True, Statement is False.

D. Statement I is False, Statement II is True.

#### Answer: D

Watch Video Solution

6. Statement I: Internal resistance of a battery is drawn parallel to a battery in electical circuit.
Statement II: Heat generated in a battery is due to internal resistance.

A. Statement I is True , Statement II is True ,
Statement II is a correct explanation for
Statement I.
B. Statement I is True, Statement II is True ,
Statement II is NOT a correct explanation for

statement I.

C. Statement I is True, Statement is False.

D. Statement I is False, Statement II is True.



## Comprehension

**1.** In figure circuit section AB absorbs energy at the rate of 5.0W when a currenti = 1.0A passes through it in the indicated direction.

(a) What is the potential difference between points  ${\boldsymbol{A}}$ 

and B?

(b) Emf device X does not have internal resistance. What is its emf?

(c) What is its polarity (the orientation of its positive

and negative terminals)?



A. 10V

 ${\rm B.}\,50V$ 

 $\mathsf{C.}\,20V$ 

 $\mathsf{D.}\,30V$ 

Answer: B



2. In figure circuit section AB absorbs energy at the rate of 5.0W when a currenti = 1.0A passes through it in the indicated direction.

(a) What is the potential difference between points A and B?

(b) Emf device X does not have internal resistance. What is its emf?

(c) What is its polarity (the orientation of its positive and negative terminals)?



## A. 24V

C. 48 V`

 $\mathsf{D}.\,12V$ 

#### Answer: C

Watch Video Solution

**3.** A three - way light bulb has three brightness settings (low, medium, and high) but only two filaments. The two filaments are arranged in three settings, when connected across a 120V line and can dissipate 60, 120 and 180W. Answer the following questions:

(i) Higher resistance filament only works for 60W

ii. Low resistance filament works for 120W

iii.Low resistance filament works for 60W

iv. High resistance filament works for 120W

v. Low and high resistance filaments in parallel for 180W

vi. Low and high resistance filament in series for 180W

A. I, ii, and v are correct

B. I, ii, and vi are correct

C. iii, iv, and v are correct

D. iii, iv, and vi are correct

#### Answer: A

**4.** A three - way light bulb has three brightness settings (low, medium, and high) but only two filaments. The two filaments are arranged in three settings, when connected across a 120V line and can dissipate 60, 120 and 180W. Answer the following questions:

A. all three settings is 120W

B. all three settings is 60W

C. two settings is 60W

D. two settings is 120W

## Answer: D



5. In Fig. 7.48, each of the segments (e. g., AE, GM, etc.) has resistance r. A battery of emf V is connected between A and C. Internal resistance of the battery is negligible.



What is the equivalent resistance of the system about A and C?

A. *r* 

B. 
$$\frac{r}{2}$$
  
C.  $\frac{3r}{2}$ 

 $\mathsf{D.}\,2r$ 

## Answer: C



**6.** In Fig. 7.48, each of the segments (e. g., AE, GM, etc.) has resistance r. A battery of emf V is connected between A and C. Internal resistance of the battery is negligible.



Find the ratio of the power developed in segment AE

to that in segment HM.

A. 1 B. 2

C. 3

**D**. 4

## Answer: D



7. In Fig. 7.48, each of the segments (e. g., AE, GM, etc.) has resistance r. A battery of

emf V is connected between A and C. Internal resistance of the battery is negligible.



If a potentiometer circuit having gradient k is connected across the points H and C, the balancing length shown by the potentiometer is

A. 
$$\frac{v}{k}$$
  
B.  $\frac{2v}{k}$ 

3vC.  $\overline{2k}$ 

D. none of these

### Answer: B

**O** Watch Video Solution

8. Refer to Fig. 7.49.



At t=0 , the switch is closed . Just after closing the switch, find the current through the  $5\Omega$  resistor.

A. 
$$\frac{4}{5}A$$
  
B.  $\frac{2}{5}A$   
C.  $\frac{6}{5}A$ 

 $\mathsf{D.}\,2A$ 

### Answer: D



**9.** Refer to Fig. 7.49.



Long time after closing the switch , find the current through the  $5\Omega$  resistor.

A. 
$$\frac{4}{5}A$$
  
B.  $\frac{2}{5}A$   
C.  $\frac{6}{5}A$   
D.  $\frac{8}{5}A$ 

## Answer: C



**10.** Refer to Fig. 7.49.



Now the switch is opened after closing it for a long time. Find the total energy dissipated in the system.

A.  $40.8 \mu J$ 

B.  $50.8 \mu J$ 

C.  $40\mu J$ 

D. None of these

Answer: A

Watch Video Solution

11. All bulbs consume same power. The resistance of

bulb 1 is  $36\Omega$  . Answer the following questions:



What is the resistance of bulb 3?

A.  $4\Omega$ 

 $\mathsf{B}.\,9\Omega$ 

 $\mathsf{C}.\,12\Omega$ 

D.  $18\Omega$ 

Answer: B



12. All bulbs consume same power. The resistance of bulb 1 is  $36\Omega$  . Answer the following questions:



What is the resistance of bulb 4?

A.  $4\Omega$ 

 $\mathsf{B.}\,9\Omega$ 

 $\mathsf{C}.\,12\Omega$
D.  $18\Omega$ 

### Answer: A



13. All bulbs consume same power. The resistance of

bulb 1 is  $36\Omega$  . Answer the following questions:



What is the voltage output of the battery if the power

of ecach bulb is 4W?

A. 12V

 ${\rm B.}\,16V$ 

 $\mathsf{C.}\,24V$ 

D. none of these

#### Answer: B





**1.** Two circular rings of identical radii and resistance of  $36\Omega$  each are placed in such a way that they cross each others centre  $C_1$  and  $C_2$  as shown in figure. Conducting joints are made at intersection point A and B of the rings. An ideal cell of emf 20 volts is connected across AB. The power delivered by cell is:





2. Three identical resistors are connected in series . When a certain potential difference is applied across the combination , the total power would be dissipated is 27W. How many times the power would be dissipated if the three resistors were connected in parallel across the same potential difference ?

Watch Video Solution

**3.** A heating coil is rated 100W, 200V. The coil is cut in half and two pieces are joined in parallel to the

same source . Now what is the energy  $({
m in} imes 10^2 J)$ 

liberated per second?

Watch Video Solution

4. A dynamo developos 0.5Aat6V. Find the energy it

generated in 1s.

Watch Video Solution

5. If in the circuit shown in Fig.7.55, power dissipation

is 150W, then find the value of  $R(\mathrm{in}\Omega)$ .



# Calculating Thermal Power In Resistance

**1.** Which of the following plots may represent the thermal energy produced in a resistor for a given

## current as a function of time?



A. a

B.b

C. c

D. d

### Answer: D



**2.** Two heating coils, one of fine wire and the other of thick wire of the same material and of the same length are connected in series and in parallel. Which of the following statement is correct ?

A. In series fine wire liberates more energy while in

parallel thich wire will liberate more energy.

B. In series fine wire liberates less energy while in

parallel thick wire will liberate more energy

C. Both will liberate quickly

D. In series the thick wire will liberate more while

in paralel it will liberate less energy

Answer: A



**3.** A resistor  $R_1$  dissipates the power P when connected to a certain generator. If the resistor  $R_2$  is put in series with  $R_1$ , the power dissipated by  $R_1$ 

A. decreases

B. increases

C. remains the same

D. any of the above depending upon the relative

values of  $R_1$  and  $R_2$ 

Answer: A



**4.** If two bulbs of wattage 25 and 100 respectively each rated at 220 volt are connected in series with the supply of 440 volt , then which bulbs will fuse

A. 100 W bulb

B. 25 W bulb

C. none of them

D. Both of them

Answer: B

**Watch Video Solution** 

**5.** A 100 watt bulb working on 200 volt and a 200 watt bulb working on 100 volt have

A. resistance in the ratio of 4:1

B. maximum current ratings in the ratio of 1:4

C. resistance in the ratio of 2:1

D. maximum current ratings in the ratio of 1:2

#### Answer: B

# Watch Video Solution

**6.** There are two electric bulbs of 40W and 100W. Which one will be brighter when first connected in series and then in parallel ?

A. 40 W in series and 100 W in parallel.

B. 100 W in series and 40 W in parallel

C. 40 W both in series and parallel will be uniform

D. 100W both in series and parallel will be uniform



**7.** Two bulbs of 500 watt and 200 watt are manufactured to operate on 220 volt line. The ratio of heat produced in 500W and 200W, in two cases, when firstly they are joined in parallel and secondly in series, will be

A. 
$$\frac{5}{2}$$
,  $\frac{2}{5}$   
B.  $\frac{5}{2}$ ,  $\frac{5}{2}$   
C.  $\frac{2}{5}$ ,  $\frac{5}{2}$ 

D. 
$$\frac{2}{5}, \frac{2}{5}$$

### Answer: A

# Watch Video Solution

8. Two wires 'A' and 'B' of the same material have their lengths in the ratio 1:2 and radii in the ratio 2:1 The two wires are connected in parallel across a battery. The ratio of the heat produced in 'A' to the heat produced in 'B' for the same time is

A. 1:2

### B. 2:1

C. 1:8

D.8:1

#### Answer: D

**Watch Video Solution** 

**9.** Two wires A and B of same material and mass have their lengths in the ratio 1:2. On connecting them to the same source, the rate of heat dissipation in B is found to be 5 W. The rate of heat dissipation in A is

A. 10W

B. 5W

C. 20W

D. None of these

#### Answer: C

Watch Video Solution

**10.** An electric kettle has two heating coils. When one coil is used, water in the kettle boils in 5 minutes, while when second coil is used, same water boils in 10 minutes. If the two coils, connected in parallel are used simultaneously, the same water will boil in time

A. 3 min 20 sec

B. 5 min

C. 7 min 30sec

D. 2 min 30sec

**Answer: A** 



**11.** An electric kettle has two coils. When one of these is switched on, the water in the kettle boils in 6 minutes. When the other coil is switched on, the water boils in 3 minutes. If the two coils are connected in series, find the time taken to boil the water in the kettle. A. 3 minutes

B. 6 minutes

C. 2 minutes

D. 9 minutes

#### Answer: D

> Watch Video Solution

12. If resistance of the filament increases with temperature, what will be power dissipated in a 220V - 100W lamp when connected to 110V power supply

A. 25W

B. lt25W

C. gt25W

D. None of these

#### Answer: C

Watch Video Solution

**13.** Two bulbs consume same energy when operated at 200V and 300V, respectively. When these bulbs are connected in series across a dc source of 500V,

then

```
A. ratio of potential difference across them is \frac{3}{2}
B. ratio of potential difference across them is \frac{9}{4}
C. ratio of power concumed across them is \frac{4}{9}
D. ratio of power consumed across them is \frac{2}{3}
```

## Answer: C

Watch Video Solution

**14.** A steel wire has a resistance twice that of an aluminium wire. Both of them are connected with a constant voltage supply. More heat will be dissipated

A. steel wire when both are connected in series

- B. steel wire when both are connected in parallel
- C. aluminium wire when both are connected in

series

D. aluminium wire when both are connected in parallel.

Answer: A::D

Watch Video Solution

Thermal Power In Resistance Connected In Circuit

1. A room AC run for 5 hour at a voltage of 220V The wiring of the room constant of Cu of 1mm ratio and a length of 10m consumption per day is 10 commercial unit What fraction of it goes in the joule heated in wire? What would happen if the wiring is made of aluminum of the same distances?  $[\rho_{cu} = 1.7 \times 10^{-8}\Omega, \rho_{A1} = 2.7 \times 10^{-8}\Omega m]$ 

# Watch Video Solution

**2.** Power P is to be delivered to a device via transmission cables having resistance  $R_c$ . If V is the

voltage across R and I the current through it , find

the power wasted and how can it be reduced.



**3.** When an electric heater is switched on, the current flowing through it ( i ) is plotted against time ( t ). Taking into account the variation of resistance with temperature, which of the following best represents the resulting curve





#### Answer: B



**4.** A constant current i is passed through a resistor. Taking the temperature coefficient of resistance into account, indicate which of the plots shown in Figure best represents the rate of production of thermal

energy in the resistor



### A. a

B.b

С. с

D. d

#### Answer: D



**5.** Electric bulb 50W - 100V glowing at full power are to be used in parallel with battery 120V,  $10\Omega$ . Maximum number of bulbs that can be connected so that they glow in full power is

A. 2

B. 8

C. 4

D. 6

Answer: C

**6.** What will happen when a 40 watt 220 volt lamp and 100 watt-220 volt lamp are connected in series across 40 volt supply?

A. 100 watt lamp will fuse

B. 40 watt lamp will fuse

C. Both lamps will fuse

D. Neither lamp will fuse

#### Answer: D



**7.** Some electric bulbs are connected in series across a 220 V supply in a room. If one bulb is fused then remaining bulbs are connected again in series across the same supply. The illumination in the room will

A. increase

B. decrease

C. remains the same

D. not continous

Answer: A

8. Two bulbs X and Y having same voltage rating and of power 40 watt and 60 watt respectively are connected in series across a potential difference of 300 volt, then



A. X will glow brigher

B. Resistance of Y is greater than X

C. Hear produced in Y will be greater than Y

D. Voltage drop in X will be greater than Y





The heat generated in the 4 ohms resistor is

A. 1cal/sec

B. 2cal/sec

C. 3cal/sec

D. 4cal/sec

#### Answer: B

> Watch Video Solution

10. Water boils in an electric kettle in 15 minutes after switching on. If the length of the heating wire is decreased to 2/3 of its initial value, then the same amount of water will with the supply voltage in A. 15 minutes

B. 12 minutes

C. 10 minutes

D. 8 minutes

#### Answer: C

Watch Video Solution

**11.** In the circuit as shown in the figure, the heat produced by 6 ohm resistance due to current flowing in it is 60 calorie per second. The heat generated

across 3 ohm resistance per second will be



- A. 30 calorie/sec
- B. 60 calorie/sec
- C. 100 calorie/sec
- D. 120 calorie/sec

#### **Answer: D**



12. The resistance of a heater coil is 110ohm. A resistance R is connected in parallel with it and the combination is joined in series with a resistance of 11ohm to a 220 volt main line. The heatter operates with a power of 110 watt. The value of R in ohm is

A. 12.22

B. 24.42

C. negative

D. that the given values are not correct

Answer: A



**13.** Four identical electrical lamps are labelled 1.5V0.5A which describes the condition necessary for them to operate at normal brightness. A 12V battery of negligible internal resistance is connected to lamps as shon, then



A. The value of R for normal brightness of each

lamp is 
$$\left(rac{3}{4}
ight)\Omega$$

B. The value of R for normal brightness of each

lamp is 
$$\left(\frac{21}{4}\right)\Omega$$

C. Total power dissipated in circuit when all lamps

are normally bright is 24W.

D. Power dissipated in R is 21 W when all lamps are

normally bright

Answer: B
14. If the cell of emf 5 volt shown in the figure gives a power of 10W. Q, find the powers consumed by the resistors  $2\Omega$  and  $1\Omega$ 



A. 2W, 18W

B. 8W, 49W

C. 8W, 18W

 $\mathsf{D.}\,2W,\,49W$ 





(A) Consider circuit in figure. How much energy is absorbed by electrons from the initial state of no current (Ignore thermal motion) to the state of drift velocity?

(b) electrons give up energy at the rate of  $RI^2$  per second tot he thermal energy. What time scale would

number associate with energy in problem (a)? n =number of electron/volume  $= \frac{10^{29}}{m^3}$  length of circuit = 10cm, cross-section  $A = (1mm)^2$ 

# Watch Video Solution

**16.** Battery shown in figure has e.m.f. E and internal resistance r. Current in the circuit can be varied by sliding the contact J. If at any instant current flowing through the circuit is I, potential difference between terminals of the cells is V, thermal power generated in the cell is equal to  $\eta$  fraction of total electrical power generated in it, then which of the following

# graphs is correct ?









D. Both a and b are correct

# Answer: D



**17.** Two identical electric lamps marked 500W, 220V are connected in series and then joined to a 110V line. The power consumed by each lamp is

A. 
$$\left(\frac{125}{4}\right)W$$
  
B.  $\frac{25}{4}W$   
C.  $\frac{225}{4}W$ 

 $\mathsf{D}.\,125W$ 

**Answer: A** 



**18.** Figure 7.37 shows a network of three resistances. When some potential difference is applied across the network , thermal powers dissipated by A, B and C are in the ratio



- A. 2:3:4
- B. 2:4:3

### C.4:2:3

#### D. 3:2:4

# Answer: C

Watch Video Solution

**19.** If the length of the filament of a heater is reduced

by 10~% , the power of the heater will

A. increase by about 9%

B. increase by about 11%

C. increase by about 19%

D. decrease by about 10%

# Answer: B



**20.** The resistance of the filament of a lamp increases with the increase in temperature. A lamp rated 100W and 220V is connected across 220V power supply. If the voltage drops by 10%, then the power of the lamp will be

A. 90 W

B. 81 W

C. Between 90 W and 100 W

D. Between 81 W and 90 W

### Answer: D



**21.** In the following circuit,  $18\Omega$  resistor develops 2J/sec due to current flowing through it. The power developed across  $10\Omega$  resistance is



A. 125 W

B. 10 W

C. 4/5 W

D. 25 W

Answer: B

Watch Video Solution

22. For ensuring dissipation of same energy in all three resistors  $(R_1, R_2, R_3)$  connected as shown in

figure, their values must be related s



A. 
$$R_1=R_2-R_3$$

B.  $R_2 = R_3$  and  $R_1 = 4R_2$ 

C. 
$$R_2 = R_3$$
 and  $R_1 = \frac{1}{4}R_2$ 

D.  $R_1 = R_2 + R_3$ 

#### Answer: C



23. The resistance of the filament of an electric bulb changes with temperature. If an electric bulb rated 220 volt and 100 watt is connected  $(220 \times 8)$  volt sources, then the actual power would be

A.  $100 imes 0.8 \mathrm{W}$ 

 $\mathsf{B.100}\times\left(0.8\right)^2\mathsf{W}$ 

C. Between  $100 \times 0.8 \, \text{W}$  and  $100 \times 0.8 \, \text{W}$ 

D. Between  $100 imes \left( 0.8 
ight)^2$  W and 100 imes 0.8W

#### Answer: D



**24.** An electric bulb rated for 500W at 100V is used in a circuit having a 200V supply. The reistance R that must be put in series with bulb, so that the bulb delivers 500W is ......Ω.

A.  $10\Omega$ 

 $\mathsf{B.}\,20\Omega$ 

 $\mathsf{C}.\,50\Omega$ 

D.  $100\Omega$ 



**25.** The wiring of a house has resistance  $6\Omega A100W$  bulb is glowing. If a geyser of 1000W is switched on, the changee in potential drop across the bulb is nearly

A. Nil

B. 23V

C. 32V

D. 12V





In the following circuit,  $5\Omega$  resistor develops 45 J/s due to current flowing through it. The power developed across  $12\Omega$  resistor is

A. 16 W

B. 192 W

C. 36 W

D. 64 W



**27.** Consider a resistor of uniform cross-sectional area connected to a battery of internal resistance zero. If the length of the resistor is doubled by stretching it, then

- A. Current will become four times.
- B. the electric field in the wire will become half.
- C. the thermal power produced by the resistor will

become one-fourth.

D. the product of the current density and conductance will become half.



**28.** A variable current flows through a  $1\Omega$  resistor for 2 s. Time dependence of the current is shown in the graph.



A. Total charge flows through the resistor is  $10^{\,\circ}$  C.

B. Average current through the resistor is 5A.

C. Total heat produced in the resistor is 50 J.

D. Maximum power during the flow of current is

100 W.

Answer: A::B::D

**Watch Video Solution**