



PHYSICS

BOOKS - A2Z PHYSICS (HINGLISH)

ALTERNATING CURRENT

Properties Of Alternating Current

1. Alternating current can not be measured by D.C.

Ammeter because

A. AC voltage pass through DC ammeter

B. Average value of complete cycle is zero

C. AC is virtual

D. AC change its direction

Answer: B



Watch Video Solution

2. An AC generator produced an output voltage $E = 170 \sin 377t$ volts, where t is in seconds. The frequency of AC voltage is

A. $50Hz$

B. $110Hz$

C. $60Hz$

D. $230Hz$

Answer: C



Watch Video Solution

3. An electron lamp is connected to $220V, 50Hz$ supply. Then the peak value of voltage is

A. $210V$

B. $211V$

C. $310V$

D. $320V$

Answer: C



Watch Video Solution

4. The r.m.s. voltage of domestic electricity supply is 220 volt. Electrical appliances should be designed to withstand an instantaneous voltage of

A. $220V$

B. $311V$

C. $330V$

D. $440V$

Answer: B



Watch Video Solution

5. The frequency of an alternating voltage is 50 cycles/sec and its amplitude is $120V$. Then the r.m.s value of voltage is

A. $101.3V$

B. $84.8V$

C. $70.7V$

D. $56.5V$

Answer: B



Watch Video Solution

6. A resistance of 20ohms is connected to a source of an alternating potential $V = 220 \sin(100\pi t)$. The time taken by the current to change from its peak value to r.m.s. value is

A. 0.2 sec

B. 0.25 sec

C. 25×10^{-3} sec

D. 2.5×10^{-3} sec

Answer: D



Watch Video Solution

7. Voltage and current in an AC circuit are given by

$$V = \sin\left(100\pi t - \frac{\pi}{6}\right) \quad \text{and}$$

$$I = 4 \sin\left(100\pi t + \frac{\pi}{6}\right)$$

A. Voltage leads the current by 30°

B. Current leads the voltage by 30°

C. Current leads the voltage by 60°

D. Voltage leads the current by 60°

Answer: C



Watch Video Solution

8. If an AC main supply is given to be $220V$. What would be the average e.m.f during a positive half cycle?

A. $198V$

B. $386V$

C. $256V$

D. None of these

Answer: A



Watch Video Solution

9. In an AC circuit $I = 100 \sin 200\pi t$. The time required for the current to achieve its peak value of will be

A. $\frac{1}{100}\text{sec}$

B. $\frac{1}{200}\text{sec}$

C. $\frac{1}{300}\text{sec}$

D. $\frac{1}{400}\text{sec}$

Answer: D



Watch Video Solution

10. The peak value of Alternating current is 6amp, then r.m.s. value of current will be

A. $3A$

B. $3\sqrt{3}A$

C. $3\sqrt{2}A$

D. $2\sqrt{3}A$

Answer: C



Watch Video Solution

11. A generator produces a time varying voltage given by $V = 240 \sin 120t$, where t is in second.

The rms voltage and frequency are

A. $60Hz$ and $240V$

B. $19Hz$ and $120V$

C. $19Hz$ and $170V$

D. $754Hz$ and $70V$

Answer: C



Watch Video Solution

12. The peak voltage in a $220V AC$ source is

A. $155.6volts$

B. $220.0volts$

C. $311.0volts$

D. 440volts

Answer: C



Watch Video Solution

13. A 40Ω electric heater is connected to a 200V , 50Hz main supply. The peak value of electric current flowing in the circuit is approx.

A. 2.5A

B. 5A

C. 7A

D. 10A

Answer: C



Watch Video Solution

14. The rms value of an ac of 50Hz is 10A. The time taken by an alternating current in reaching from zero to maximum value and the peak value will be

A. 2×10^{-2} sec and 14.14amp

B. 1×10^{-2} sec and 7.07amp

C. 5×10^{-3} sec and 7.07amp

D. 5×10^{-3} sec and 14.14 amp

Answer: D



Watch Video Solution

15. The peak value of an alternating emf E given by

$$E = (E_0) \cos \omega t$$

is 10V and frequency is 50 Hz . At time

$t = (1/600)\text{s}$ the instantaneous value of emf is

A. 10V

B. $5\sqrt{3}\text{V}$

C. $5V$

D. $1V$

Answer: B



Watch Video Solution

16. An alternating current is given by

$$I = i_1 \cos \omega t + i_2 \sin \omega t.$$

The rms current is given by

A. $\frac{1}{\sqrt{2}}(i_1 + i_2)$

B. $\frac{1}{\sqrt{2}}(i_1 + i_2)^2$

C. $\frac{1}{\sqrt{2}} (i_1^2 + i_2^2)^{1/2}$

D. $\frac{1}{2} (i_1^2 + i_2^2)^{1/2}$

Answer: C



Watch Video Solution

17. An AC is given by the equation $I = I_1 \cos \omega t + I_2 \sin \omega t$. The r.m.s. current is given by

A. $\frac{I_1 + I_2}{2}$

B. $\frac{(I_1 + I_2)^2}{\sqrt{2}}$

C. $\frac{1}{\sqrt{2}} \sqrt{I_1^2 + I_2^2}$

D. $\frac{I_1^2 + I_2^2}{2}$

Answer: C



Watch Video Solution

18. Two alternating voltage generators produce emfs of the same amplitude(E_0) but with a phase difference of $(\pi) / 3$. The resultant emf is

A. $E_0 \sin(\omega t + \pi / 3)$

B. $E_0 \sin(\omega t + \pi / 6)$

C. $\sqrt{3}E_0 \sin(\omega t + \pi / 6)$

D. $\sqrt{3}E_0 \sin(\omega t + \pi / 2)$

Answer: C



Watch Video Solution

19. The phase difference between the voltage and the current in an AC circuit is $\pi/4$. If the frequency is $50Hz$ then this phase difference will be equivalent to a time of

A. $0.02s$

B. $0.25s$

C. $2.5ms$

D. $25ms$

Answer: C



Watch Video Solution

20. Instantaneous values of current and e.m.f in an AC circuit are $I = I/\sqrt{2} \sin 314t$ amp and $E = \sqrt{2} \sin(314t - \pi/6)V$ respectively. The phase difference between E and I will be

A. $-\pi/6rad$

B. $-\pi/3rad$

C. $\pi/6rad$

D. $\pi/3rad$

Answer: A



Watch Video Solution

21. An alternating voltage $E = 200\sqrt{2}\sin(100t)$ is connected to a 1 microfarad capacitor through an AC ammeter. The reading of the ammeter shall be

A. $10mA$

B. $20mA$

C. $40mA$


D. $80mA$

Answer: B



Watch Video Solution

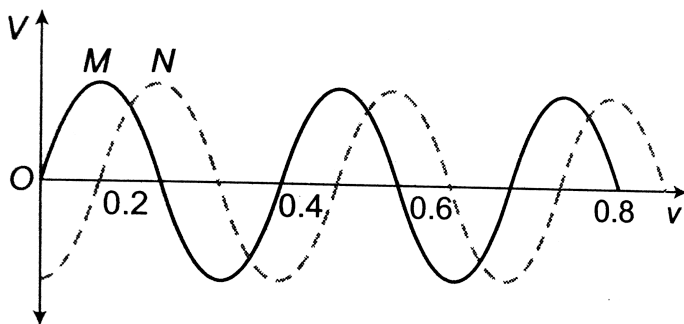22. Two sinusoidal voltage of the same frequency are shown in the diagram. What is the frequency, and the phase relationship between the voltage?



Frequency in Hz phase lead of N over M in
radians

A. $0.4 = -\pi/4$

B. $2.5 = -\pi/2$

C. $2.5 = +\pi/2$


D. $2.5 = -\pi/2$

Answer: B



Watch Video Solution

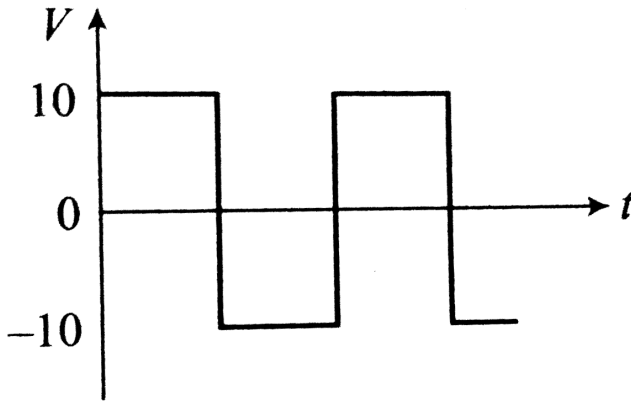23. The r.m.s. voltage of the wave form shown is




- A. $10V$
- B. $7V$
- C. $6.63V$
- D. None of these

Answer: A



Watch Video Solution

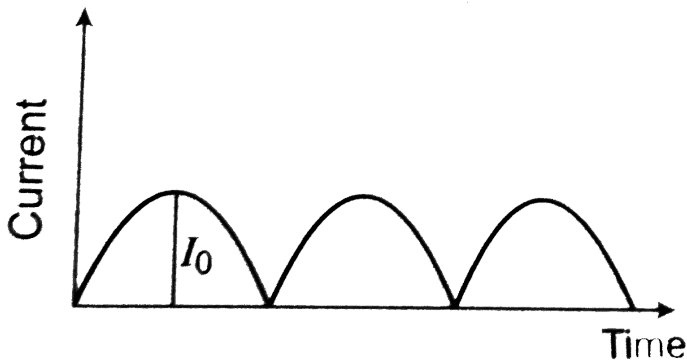24. The output current versus time curve of a rectifier is shown in the figure. The voltage value of output current in this case is



A. 0

B. $\frac{I_0}{2}$

C. $\frac{2I_0}{\pi}$

D. I_0


Answer: C



Watch Video Solution

25. The variation of the instantaneous current (I) and the instantaneous e.m.f (E) in a circuit is as shown in figure. Which of the following statement

is correct?

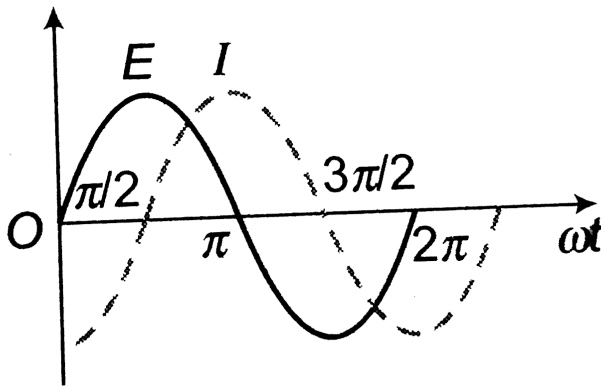

- A. The voltage lags behind the current by $\pi/2$
- B. The voltage leads the current by $\pi/2$
- C. The voltage and the current are in phase
- D. The voltage leads the current by π

Answer: B



Watch Video Solution

26. If $i = t^2$, $0 < t < T$ then *r.m.s.* value of current is

A. $\frac{T^2}{\sqrt{2}}$

B. $\frac{T^2}{2}$

C. $\frac{T^2}{\sqrt{5}}$

D. None of these

Answer: C



Watch Video Solution

27. In a certain circuit current changes with time according to $i = 2\sqrt{t}$. r.m.s. value of current between $t = 2$ to $t = 4s$ will be

A. $3A$

B. $3\sqrt{3}A$

C. $2\sqrt{3}A$

D. $(2 - \sqrt{2})A$

Answer: C



Watch Video Solution

28. The voltage of an AC source varies with time according to the equation $V = 100 \sin 100\pi t \cos 100\pi t$ where t is in seconds and V is in volts. Then

- A. The peak voltage of the source is 100 volts
- B. The peak voltage of the source is 50volts
- C. The peak voltage of the source is $100\sqrt{2}$ volts
- D. The frequency of the source is $50Hz$

Answer: B



Watch Video Solution

29. The capacitance of a pure capacitance is 1 farad. In DC circuits, its effective resistance will be

A. Zero

B. Infinite

C. 1ohm

D. $1/2\text{ohm}$

Answer: B



Watch Video Solution

1. A capacitor becomes a perfect insulator for

A. Alternating currents

B. Direct current

C. Both AC and DC

D. None of these

Answer: B



Watch Video Solution

2. An alternating e.m.f. is applied to purely capacitive circuit. The phase relation between e.m.f. and current flowing in the circuit is or in a circuit containing capacitance only

A. e.m.f. is ahead of current by $\pi / 2$

B. Current ahead of e.m.f by $\pi / 2$

C. Current lags behind e.m.f. by π

D. Current is ahead of e.m.f. by π

Answer: B



Watch Video Solution

3. In a circuit containing an inductance of zero resistances, the e.m.f of the applied AC voltage leads the current by

A. 90°

B. 45°

C. 30°

D. 0°

Answer: A



Watch Video Solution

4. The instantaneous values of current and voltage in an AC circuit are $i = 100 \sin 314t$ amp and $e = 200 \sin(314t + \pi/3)V$ respectively. If the resistance is 1Ω then the reactance of the circuit will be

A. $-200\sqrt{3}\Omega$

B. $\sqrt{3}\Omega$

C. $-200/\sqrt{3}\Omega$

D. $100\sqrt{3}\Omega$

Answer: B



Watch Video Solution

5. A 120 volt AC source is connected across a pure inductor of inductance 0.70 henry. If the frequency of the source is $60Hz$, the current passing through the inductor is

A. $4.55amps$

B. $0.355amps$

C. $0.455amps$

D. $3.55amps$

Answer: C



Watch Video Solution

6. The reactance of a coil when used in the domestic AC power supply ($220V$, $50cycles$) is $100ohm$. The self inductance of the coil is nearly

A. 3.2 henry

B. $0.32henry$

C. $2.2henry$

D. $0.22henry$

Answer: B



Watch Video Solution

7. The reactance of a $25\mu F$ capacitor at the AC frequency of $4000Hz$ is

A. $\frac{5}{\pi} ohm$

B. $\sqrt{\frac{5}{\pi}} ohm$

C. $10 ohm$

D. $\sqrt{10} ohm$

Answer: A



Watch Video Solution

8. The frequency for which a $5\mu F$ capacitor has a reactance of $\frac{1}{100}$ ohm is given by

A. $\frac{100}{\pi} MHz$

B. $\frac{1000}{\pi} Hz$

C. $\frac{1}{1000} Hz$

D. $1000 Hz$

Answer: A



Watch Video Solution

9. The value of the current through an inductance of $1H$ and of negligible resistance, when connected through an AC source of $200V$ and $50Hz$ is

A. $0.637A$

B. $1.637A$

C. $2.637A$

D. $3.637A$

Answer: A



Watch Video Solution

10. The reactance of a coil when used in the domestic AC power supply ($220V$, $50cycles$) is $50ohm$. The inductance of the coil is nearly



- A. 2.2 henry
- B. 0.22 henry
- C. 1.6 henry
- D. 0.16 henry

Answer: D






Watch Video Solution

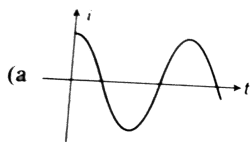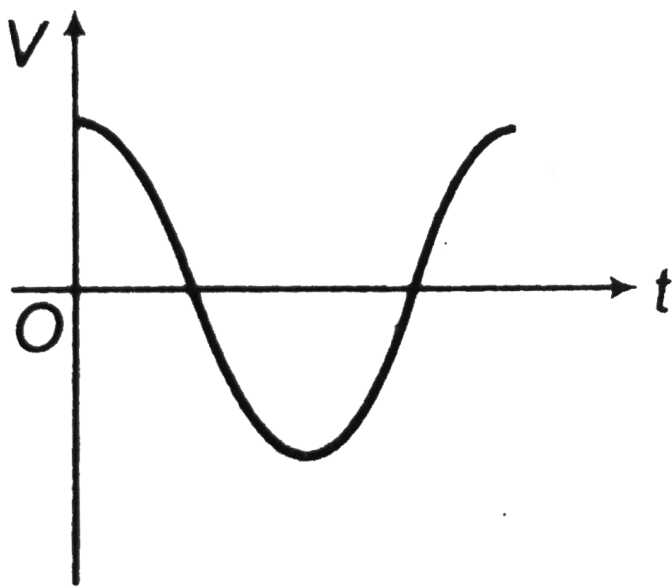11. The figure represents the voltage applied across a pure inductor. The diagram which correctly represents the variation of current i with time t is given by



A.

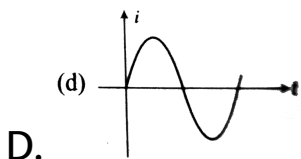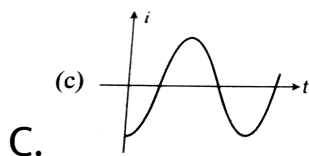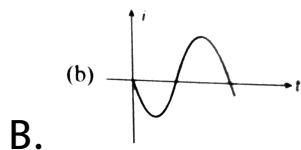


Answer: D



Watch Video Solution

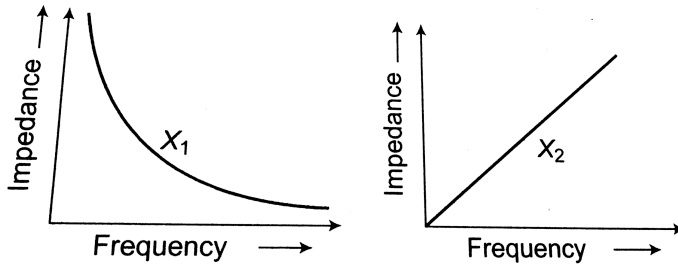12. The graphs given below depict the dependence of two reactive impedances X_1 and X_2 on the frequency of the alternating e.m.f. applied

individually to them. We can then say that







- A. X_1 is an inductor and X_2 is a capacitor
- B. X_1 is an resistor and X_2 is a capacitor
- C. X_1 is an capacitor and X_2 is a inductor
- D. X_1 is an inductor and X_2 is a resistor

Answer: C



Watch Video Solution

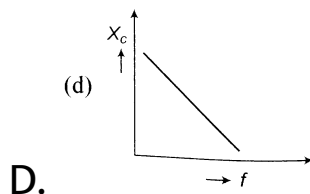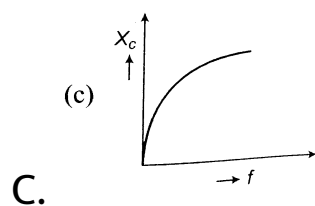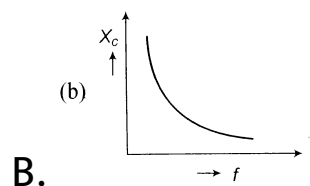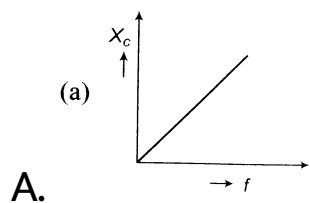13. Identify the graph which correctly represents the variation of capacitive reactance X_C with frequency



Answer: B



Watch Video Solution

14. A resistance of 40 ohms and an inductance of 95.5 millihenry are connected in series in a 50 cycle/sec AC circuit. The impedance of this combination is very nearly

A. 30ohm

B. 40ohm

C. 50ohm

D. 60Ω

Answer: C



Watch Video Solution

15. For high frequency, a capacitor offers

A. More reactance

B. Less reactance

C. Zero reactance

D. Infinite reactance

Answer: B



Watch Video Solution

16. Reactance of an inductor of $\frac{1}{\pi}$ henry at $50Hz$ frequency is

A. $\frac{50}{\pi} ohm$

B. $\frac{\pi}{50} ohm$

C. $100 ohm$

D. $50 ohm$

Answer: C



[Watch Video Solution](#)

17. The resistance of a coil for DC is in ohms. In AC, the resistance

- A. Will remain same
- B. Will increases
- C. Will decrease
- D. Will be zero

Answer: B



[Watch Video Solution](#)

18. An alternating current of frequency ' f ' is flowing in a circuit containing a resistance R and a choke L in series. The impedance of this circuit is

A. $R + 2\pi fL$

B. $\sqrt{R^2 + 4\pi^2 f^2 L^2}$

C. $\sqrt{R^2 + L^2}$

D. $\sqrt{R^2 + 2\pi fL}$

Answer: B



Watch Video Solution

19. An inductance of $1mH$ a condenser of 0.5 henry and capacitance of $10 \times 10^{-6}F$ are connected in series through $50Hz$ AC supply, then impedance is

A. 100Ω

B. 30Ω

C. 3.2Ω

D. 10Ω

Answer: D



20. If resistance of 100Ω , inductance of 0.5 henry and capacitor of $10 \times 10^{-6}F$ are connected in series through $50Hz$ AC supply, then impedance is

A. 1.876

B. 18.76

C. 189.72

D. 101.3

Answer: C



Watch Video Solution

21. An inductive circuit a resistance of 10Ω and an inductance of 2.0 henry. If an AC voltage of 120 volt and frequency of 60Hz is applied to this circuit, the current in the circuit would be nearly

A. 0.32amp

B. 0.16amp

C. 0.48amp

D. 0.80amp

Answer: B



Watch Video Solution

22. An inductive circuit a resistance of 10Ω and an inductance of 2.0 henry. If an AC voltage of 120 volt and frequency of 60Hz is applied to this circuit, the current in the circuit would be nearly

A. 0.32amp

B. 0.16amp

C. 0.48amp

D. 0.80amp

Answer: B



Watch Video Solution

23. Same current is flowing in two alternating circuits. The first circuit contains only inductances and the other contains only a capacitor, if the frequency of the e.m.f of AC is increased, the effect on the value of the current will be

- A. Increases in the first circuit and decreases in the other
- B. Increases in both the circuits
- C. Decreases in both the circuits
- D. Decreases in the first circuit and increases in the other

Answer: D



Watch Video Solution

24. In a series circuit

$R = 300\Omega$, $L = 0.9H$, $C = 2.0\mu F$ and

$\omega = 1000\text{rad/sec}$. The impedance of the circuit is

A. 1300Ω

B. 900Ω

C. 500Ω

D. 400Ω

Answer: C



Watch Video Solution

25. In a $L - R$ circuit, the value of L is $\left(\frac{0.4}{\pi}\right)$ henry and the value of R is 30 ohm. If in the circuit, an alternating e.m.f of 200 vol at 50 cycles per sec is connected, the impedance of the circuit will be

A. 11.4Ω , $17.5A$

B. 30.7Ω , $6.5A$

C. 40.7Ω , $5A$

D. 50Ω , $4A$

Answer: D



[Watch Video Solution](#)

26. An e.m.f. $E = 4 \cos(1000t)$ volt is applied to an LR circuit of inductance $3mH$ and resistance $4ohm$. The amplitude of current in the circuit is

A. $\frac{4}{\sqrt{7}} A$

B. $1.0A$

C. $\frac{4}{7} A$

D. $0.8A$

Answer: D

[Watch Video Solution](#)

27. In an AC circuit, a resistance of $R\ \Omega$ is connected in series with an inductance L . If phase angle between voltage and current be 45° , the value of inductive reactance will be

A. $\frac{R}{4}$

B. $\frac{R}{2}$

C. R

D. Cannot be found with the given data

Answer: C



[Watch Video Solution](#)

28. If an 8Ω resistance and 6Ω reactance are present in an AC series circuit then the impedance of the circuit will be

A. 20ohm

B. 5ohm

C. 10ohm

D. $14\sqrt{2}\text{ohm}$

Answer: C

[Watch Video Solution](#)

29. A $220V$, $50Hz$ Ac source is connected to an inductance of $0.2H$ and a resistance of 20Ω in series. What is the current in the circuit?

A. $10A$

B. $5A$

C. $33.3A$

D. $3.33A$

Answer: D



Watch Video Solution

30. When 100volts DC is applied across a coil, a current of $1amp$ flows through it. When 100 volt AC at $50\text{ cycles } s^{-1}$ is applied to the same coil, only 0.5 ampere current follows.

A. 100Ω

B. 200Ω

C. 300Ω

D. 400Ω

Answer: B



Watch Video Solution

31. A circuit has a resistance of 11Ω , an inductive reactance of 25Ω , and a capacitive resistance of 18Ω . It is connected to an AC source of $260V$ and $50Hz$. The current through the circuit (in amperes) is

A. 11

B. 15

C. 18

D. 20

Answer: D



Watch Video Solution

32. A 0.7 henry inductor is connected across a $120V - 60HzAC$ source. The current in the inductor will be very nearly

A. $4.55amp$

B. $0.355amp$

C. $0.455amp$

D. $3.55amp$

Answer: C



Watch Video Solution

33. There is a 5Ω resistance in an AC , circuit. Impedence of $0.1H$ is connected with it in series. If equation of AC emf is $5 \sin 50t$ then the phase difference between current and e.m.f. is

A. $\frac{\pi}{2}$

B. $\frac{\pi}{6}$

C. $\frac{\pi}{4}$

D. 0

Answer: C



Watch Video Solution

34. The coefficient of induction of a choke coil is $0.1H$ and resistance is 12Ω . If it is connected to an alternating current source of frequency $60Hz$, then power factor will be

A. 0.32

B. 0.30

C. 0.28

D. 0.24

Answer: B



Watch Video Solution

35. In a series LCR circuit, resistance $R = 10\Omega$ and the impedance $Z = 20\Omega$ the phase difference between the current and the voltage is

A. 30°

B. 45°

C. 60°

D. 90°

Answer: C



Watch Video Solution

36. A 12Ω resistor and a 0.21 henry inductor are connected in series to an AC source operating at 20volts , 50 cycle/second. The phase angle between the current and the source voltage is

A. 30°

B. 40°

C. 80°

D. 40°

Answer: C



Watch Video Solution

37. A coil of inductance L has an inductive reactance of X_L in an AC circuit in which the effective current is I . The coil is made from a

super-conducting material and has no resistance.

The rate at which power is dissipated in the coil is

A. 0

B. IX_L

C. $I^2 X_L$

D. IX_L^2

Answer: A



Watch Video Solution

38. The impedance of a consists of 3Ω resistance and 4Ω reactance. The power factor of the circuit is across the coil to the current through the coil will be

A. 0.4

B. 0.6

C. 0.8

D. 1.0

Answer: B



Watch Video Solution

39. In an AC circuit the reactance of a coil is $\sqrt{3}$ times its resistance, the phase difference between the voltage across the current through the coil will be

A. $\pi / 3$

B. $\pi / 2$

C. $\pi / 4$


D. $\pi / 6$

Answer: A



Watch Video Solution

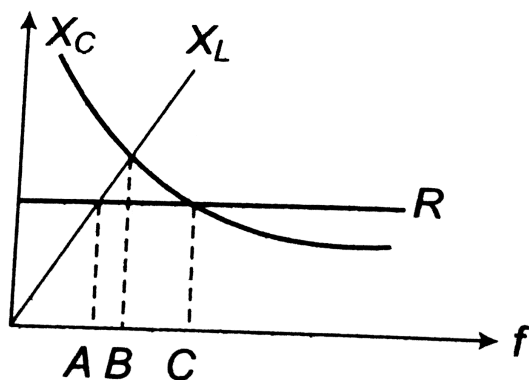40. The figure shows variation of R , X_L and X_C with frequency f in a series L, C, R circuit. Then for what frequency point, the circuit is inductive ?



A. A

B. B

C. C


D. All points

Answer: C







Watch Video Solution

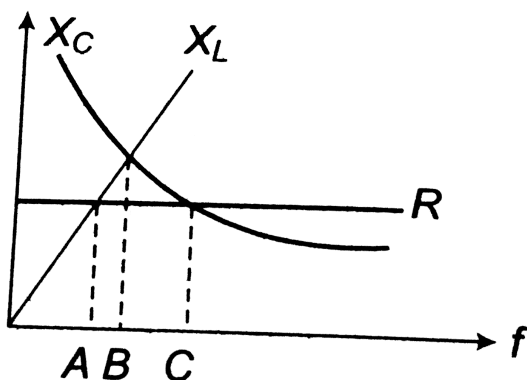41. A constant voltage at different frequencies is applied across a capacitance C as shown in the figure.



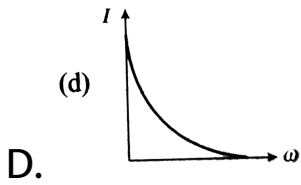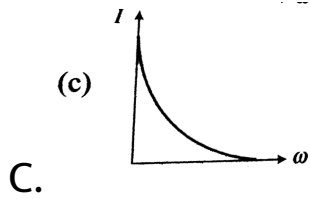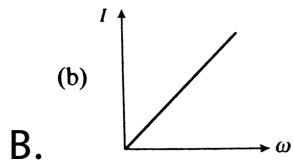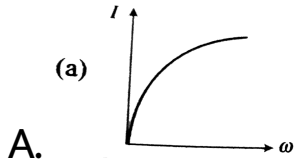Which of the following graphs correctly depicts the variation of current with frequency?




Answer: B




Watch Video Solution

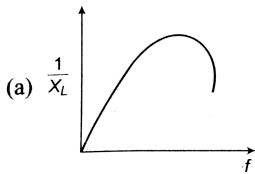
42. In pure inductive circuit, the curves between frequency f and reciprocal of inductive reactance $1/X_L$ is




A.

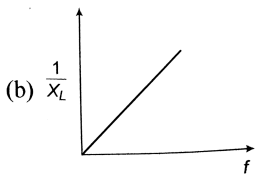

B.

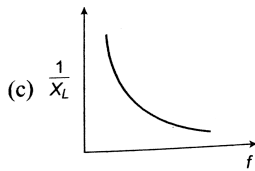

C.

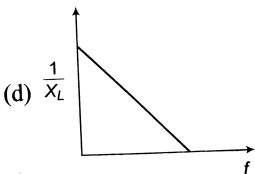

D.

Answer: C



Watch Video Solution

Different Ac Circuits

1. A bulb and a capacitor are connected in series to a source of alternating current. If its frequency is increased, while keeping the voltage of the source constant, then

A. Bulb will give more intense light

B. Bulb will give less intense light

C. Bulb will give light of same intensity as before

D. Bulb will stop radiating light

Answer: A



Watch Video Solution

2. Choke coil is used to control

A. AC

B. DC

C. Both AC and DC

D. Neither AC nor DC

Answer: A



Watch Video Solution

3. A choke coil is preferred to a rheostate in AC circuit as


- A. It consumes almost zero power
- B. It increases current
- C. It increases power
- D. It increases voltage

Answer: A



Watch Video Solution

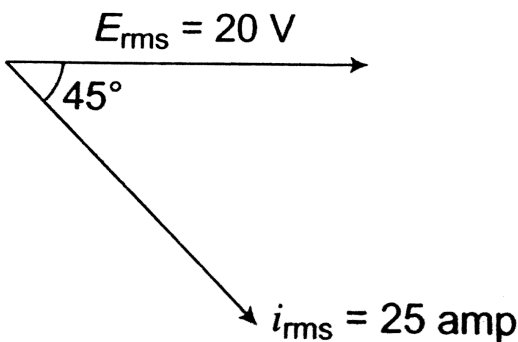4. The vector diagram of current and voltage for a circuit as shown. The components of the circuit will be



A. LCR

B. LR

C. LCR or LR

D. None of these

Answer: C



Watch Video Solution

5. A resonant AC circuit contains a capacitor of capacitance $10^{-6}F$ and an inductor of $10^{-4}H$.

The frequency of electrical oscillation will be

A. $105Hz$

B. $10Hz$

C. $\frac{10^5}{2\pi} Hz$


D. $\frac{10}{2\pi} Hz$

Answer: C



Watch Video Solution

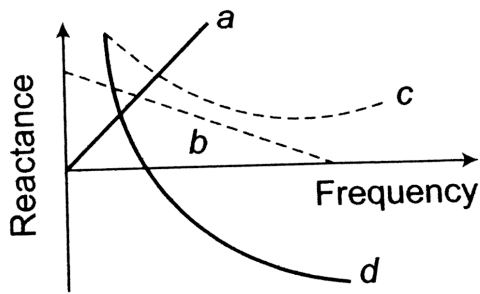6. Which of the following plots may represent the reactance of a series LC combination?



A. *a*

B. *b*

C. *c*

D. *d*

Answer: D



Watch Video Solution

7. An alternating voltage is connected in series with a resistance R and inductance L if the potential drop across the resistance is $200V$ and across the inductance is $150V$, then the applied voltage is

A. $350V$

B. $250V$

C. $500V$

D. $300V$

Answer: B



Watch Video Solution

8. A 20volts AC is applied to a circuit consisting of a resistance and a coil with negligible resistance. If the voltage across the resistance is $12V$, the voltage across the coil is

A. 16 volts

B. 10 volts

C. 8 volts

D. 6 volts

Answer: A



Watch Video Solution

9. A resistance of 300Ω and an inductance of $\frac{1}{\pi}$ henry are connected in series to an AC voltage of 20volts and $200Hz$ frequency. The phase angle between the voltage and current is

A. $\tan^{-1}\left(\frac{4}{3}\right)$



B. $\tan^{-1}\left(\frac{3}{4}\right)$



C. $\tan^{-1}\left(\frac{3}{2}\right)$

D. $\tan^{-1}\left(\frac{2}{5}\right)$

Answer: A

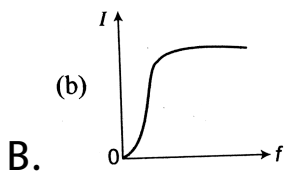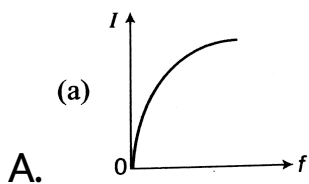10. An AC source of variable frequency f is connected to an LCR series circuit. Which one of the graphs in figure represents the variation of current I in the circuit with frequency f ?





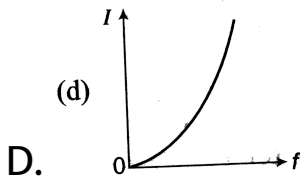
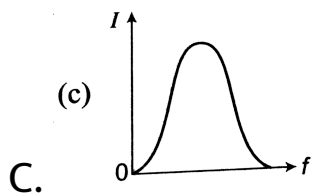


Answer: C



Watch Video Solution

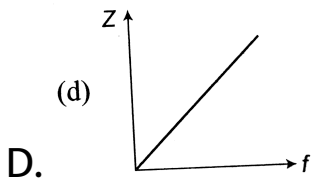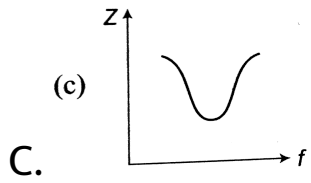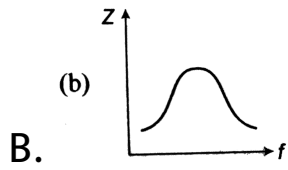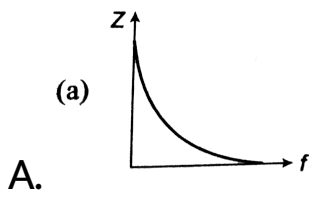11. Which of the following curves represents the variation of impedance (Z) with frequency f in series LCR circuit?



Answer: C



Watch Video Solution

12. An AC circuit consists of an inductor of inductance $0.5H$ and a capacitor of capacitance $8\mu F$ in series. The current in the circuit is maximum when the angular frequency of AC source is

A. $500rad/sec$

B. $2 \times 10^5 rad/sec$

C. $4000rad/sec$

D. $5000rad/sec$

Answer: A



Watch Video Solution

13. L, C and R represent the physical quantities, inductance, capacitance and resistance respectively. The combination(s) which have the dimensions of frequency are

A. LC

B. $(LC)^{-1/2}$

C. $\left(\frac{L}{C}\right)^{-1/2}$

D. $\frac{C}{L}$

Answer: B

14. The phase difference between the current and voltage of LCR circuit in series combination at resonance is

A. 0

B. $\pi / 2$

C. π

D. $-\pi$

Answer: A

15. In a series resonant circuit, the AC voltage across resistance R , inductance L , and capacitance C are $5V$, $10V$ and $10V$ respectively. The AC voltage applied to the circuit will be

A. $20V$

B. $10V$

C. $5V$

D. $25V$

Answer: C

16. The resonant frequency of a circuit is f . If the capacitance is made 4 times the initial values, then the resonant frequency will become

A. $f/2$

B. $2f$

C. f

D. $f/4$

Answer: A

17. In the non-resonant circuit, what will be the nature of the circuit for frequencies heigher than the resonant frequency?

- A. Resistive
- B. Capacitive
- C. Inductance
- D. None of the above

Answer: B



18. In an ac circuit the potential differences across an inductance and resistance joined in series are, respectively, 16 V and 20 V. The total potential difference across the circuit is

A. $20.0V$

B. $25.6V$

C. $31.9V$

D. $53.5V$

Answer: B



19. An LCR circuit contains $R = 50\Omega$, $L = 1mH$ and $C = 0.1\mu F$. The impedance of the circuit will be minimum for a frequency of

A. $\frac{10^5}{2\pi} s^{-1}$

B. $\frac{10^6}{2\pi} s^{-1}$

C. $2\pi \times 10^5 s^{-1}$

D. $2\pi \times 10^6 s^{-1}$

Answer: A



20. A series AC circuit consists of an inductor and a capacitor. The inductance and capacitance is respectively 1henry and $25\mu F$ if the current is maximum in circuit then angular frequency will be

A. 200 rad/s

B. 100 rad/s


C. 50 rad/s

D. $200 / 2\pi\text{ rad/s}$

Answer: A



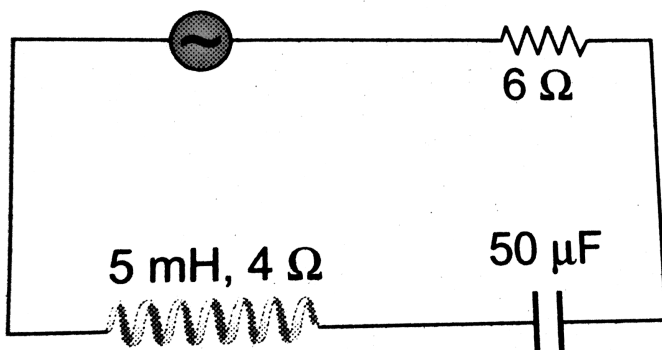21. In the circuit below, the AC source the voltage $V = 20 \cos(\omega t)$ volts with $\omega = 2000 \text{ rad/sec}$. The amplitude of the current will be nearest to



A. $2A$

B. $3.3A$

C. $2/\sqrt{5}A$

D. $\sqrt{5}A$

Answer: A



Watch Video Solution

22. An oscillator circuit consists of an inductance of $0.5mH$ and a capacitor of $20\mu F$. The resonant frequency of the circuit is nearly

A. $15.92Hz$

B. $159.2Hz$

C. $1592Hz$

D. $15910Hz$

Answer: C



Watch Video Solution

23. A coil of 200Ω resistance and $1.0H$ inductance is conneted to an AC source of frequency $200/2\pi Hz$. Phase angle between potential and current will be

A. 30°

B. 90°

C. 45°

D. 0°

Answer: C



Watch Video Solution

24. In a LCR circuit the $P.D$ between the terminals of the inductance is $60V$, between the terminals of the capacitor is $30V$ and that between the terminals of resistance is $40V$. The supply voltage will be equal to.....

A. $50V$

B. $70V$

C. $130V$

D. $10V$

Answer: A



Watch Video Solution

25. A coil has $L = 0.04H$ and $R = 12\Omega$. When it is connected to $220V, 50Hz$ supply the current flowing through the coil, in ampere is

A. 10.7

B. 11.7

C. 14.7

D. 12.7

Answer: D



Watch Video Solution

26. A virtual current of $4A$ and $50Hz$ flows in an AC circuit containing a coil. The power consumed in the coil is $100W$ its inductance will be

A. $\frac{1}{3\pi}H$

B. $\frac{1}{5\pi}H$

C. $\frac{1}{7\pi}H$

D. $\frac{1}{9\pi}H$

Answer: B



Watch Video Solution

27. For a series RLC circuit $R = X_L = 2X_C$. The impedance of the circuit and phase difference (between) V and i will be

A. $\frac{\sqrt{5}R}{2}, \tan^{-1}(2)$

B. $\frac{\sqrt{5}R}{2}, \tan^{-1}\left(\frac{1}{2}\right)$

C. $\sqrt{5}X_C, \tan^{-1}(2)$

D. $\sqrt{5}R, \tan^{-1}\left(\frac{1}{2}\right)$

Answer: B



Watch Video Solution

28. The current in series LCR circuit will be the maximum when ω is

A. As large as possible

B. Equal o natural frequency of LCR system

C. \sqrt{LC}

D. $\sqrt{1/LC}$

Answer: D



Watch Video Solution

29. One $10V, 60W$ bulb is to be connected to $100V$ line. The required inductance coil has self-inductance of value ($f = 50Hz$)

A. $0.052H$

B. $2.42H$

C. $16.2mH$

D. $1.62mH$


Answer: A



Watch Video Solution

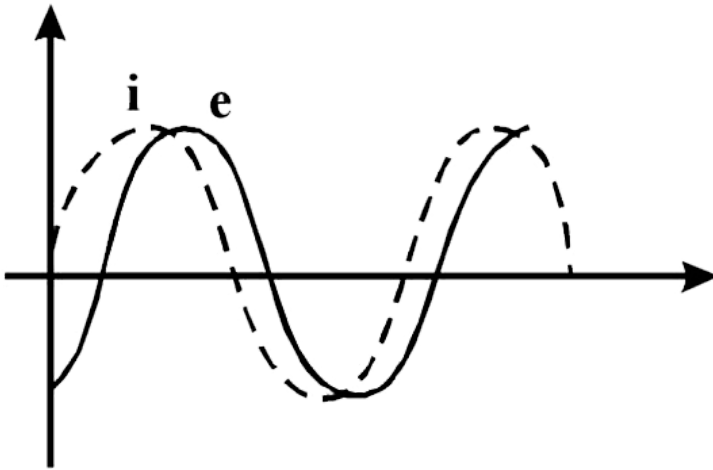30. When an AC source of emf $e = E_0 \sin(100t)$ is connected across a circuit i in the circuit, the phase difference between the emf e and the current i in the circuit is observed to be $(\pi/4)$, as shown in the diagram. If the circuit consists

possibly only of R-C or R-L or L-C in series, find the relationship between the two elements



A. $R = 1k\Omega, C = 10\mu F$

B. $R = 1k\Omega, C = 1\mu F$

C. $R = 1k\Omega, L = 10H$

D. $R = 1k\Omega, L = 1H$

Answer: A



Watch Video Solution

Power In Ac Circuits

1. The power is transmitted from a power house on a voltage AC because

- A. Electric current travels faster at higher volts
- B. It is more economical due to less power wastage
- C. It is difficult to less power voltage

D. Chance of stealing transmission lines are minimize

Answer: B



Watch Video Solution

2. Current in the circuit is wattless, if

A. Inductance in the circuit is zero

B. Resistance in the current is zero

C. Current is alternating

D. Resistance and inductance both are zero

Answer: B



Watch Video Solution

3. In an AC circuit, V and I are given by

$$V = 100 \sin(100t) \text{ volts}, I = 100 \sin\left(100t + \frac{\pi}{3}\right) \text{ mA}$$

. The power dissipated in circuit is

A. 10^4 watt

B. 10 watt

C. 2.5 watt

D. 5 watt

Answer: C



Watch Video Solution

4. A sinusoidal alternating current of peak value (I_0) passes through a heater of resistance R .

What is the mean power output of the heater?

A. $I_0^2 R \cos \theta$

B. $\frac{1}{2} I_0^2 R$

C. $\frac{4}{\pi} I_0^2 R$

D. $\frac{1}{\pi} I_0^2 R$

Answer: B



Watch Video Solution

5. In an a.c. Circuit the voltage applied is $E = E_0 \sin(\omega)t$. The resulting current in the circuit is $I = I_0 \sin\left((\omega)t - \left(\frac{\pi}{2}\right)\right)$. The power consumption in the circuit is given by

A. $P = \frac{E_0 I_0}{\sqrt{2}}$

B. $P = \sqrt{2} E_0 I_0$

C. $P = \frac{E_0 I_0}{2}$

D. $P = 0$

Answer: D



Watch Video Solution

6. In an AC circuit, the instantaneous values of e.m.f and current are $e = 200 \sin 314t$ volt and $i = \sin\left(314t + \frac{\pi}{3}\right)$ ampere. The average power consumed in watt is

A. 200

B. 100

C. 50

D. 25

Answer: C



Watch Video Solution

7. In an AC circuit, the current is given by

$$i = 5 \sin\left(100t - \frac{\pi}{2}\right) \text{ and the } AC \text{ potential is}$$

$$V = 200 \sin(100t) \text{ volt. Then the power}$$

consumption is

A. 20 watt

B. 40 watt

C. 1000 watt

D. 0 watt

Answer: D



Watch Video Solution

8. What is the r.m.s. value of an alternating current which when passed through a resistor produces heat which is thrice of that produced by a direct current of 2 amperes in the same resistor?

A. 6 amp

B. 2 amp

C. 3.46 amp

D. 0.66 amp

Answer: C



Watch Video Solution

9. In an AC circuit with voltage V and current I , the power dissipated is

A. VI

B. $\frac{1}{2}VI$

C. $\frac{1}{\sqrt{2}}VI$

D. Depended on the phase between V and I

Answer: D



Watch Video Solution

10. For an AC circuit $V = 15 \sin \omega t$ and $I = 20 \cos \omega t$ the average power consumed in this circuit is

A. 300 watt

B. 150 watt

C. 75 watt

D. zero

Answer: D



Watch Video Solution

11. An alternating e.m.f. of angular frequency ω is applied across an inductance. The instantaneous power developed in the circuit has an angular frequency

A. $\frac{\omega}{4}$

B. $\frac{\omega}{2}$

C. ω

D. 2ω

Answer: D



Watch Video Solution

12. The power factor of a good choke coil is

A. Nearly zero

B. Exectly zero

C. Nearly one

D. Exactly one

Answer: A



Watch Video Solution

13. For wattless power is an AC circuit, the phase angle between the current and voltage is

A. 90°

B. 45°

C. 180°

D. 60°

Answer: A



Watch Video Solution

14. The r.m.s current in an AC circuit is $2A$. If the wattless current be $\sqrt{3}A$, what is the power factor?

A. $\frac{1}{\sqrt{3}}$

B. $\frac{1}{\sqrt{2}}$

C. $\frac{1}{2}$

D. $\frac{1}{3}$

Answer: C



Watch Video Solution

15. In an LR -circuit, the inductive reactance is equal to the resistance R of the circuit. An e.m.f $E = E_0 \cos(\omega t)$ applied to the circuit. The power consumed in the circuit is

A. $\frac{E_0^2}{R}$

B. $\frac{E_0^2}{2R}$

C. $\frac{E_0^2}{4R}$

D. $\frac{E_0^2}{8R}$

Answer: C



Watch Video Solution

16. An $L - C - R$ series circuit with 100Ω resistance is connected to an AC source of $200V$ and angular frequency $300rad/s$. When only the capacitance is removed, the current lags behind the voltage by 60° . When only the inductance is removed the current leads the voltage by 60° .

Calculate the power dissipated in the $L - C - R$ circuit

- A. $50W$
- B. $100W$
- C. $200W$
- D. $400W$

Answer: D



Watch Video Solution

17. An rms voltage of 110 V is applied across a series circuit having a resistance 11Ω and an impedance 22Ω . The power consumed is

A. $275W$

B. $366W$

C. $550W$

D. $1100W$

Answer: A



Watch Video Solution

18. $\frac{2.5}{\pi} \mu F$ capacitor and $3000 \text{ } \Omega$ resistance are joined in series to an AC source of 200 volts and 50 sec^{-1} frequency. The power factor of the circuit and the power dissipated in it will respectively

A. $0.6, 0.06 W$

B. $0.06, 0.6 W$

C. $0.6, 4.8 W$

D. $4.8, 0.6 W$

Answer: C



Watch Video Solution

19. The self-inductance of a choke coil is 10mH .

When it is connected with a 10VDC source, then the loss of power is 20watt . When it is connected with 10voltAC source loss of power is 10watt .

The frequency of AC source will be

A. 50Hz

B. 60Hz

C. 80Hz

D. 100Hz

Answer: C



Watch Video Solution

20. A group of electric lamps having a total power rating of 1000 watt is supplied by an AC voltage $E = 200 \sin(310t + 60^\circ)$. Then the r.m.s value of the circuit current is

A. $10A$

B. $10\sqrt{2}A$

C. $20A$


D. $20\sqrt{2}A$

Answer: B



Watch Video Solution

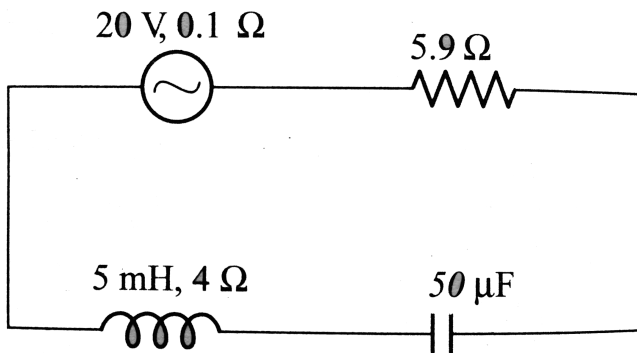21. In the circuit of fig, the source frequency is $\omega = 2000 \text{ rad s}^{-1}$. The current in the circuit will be



A. 2A

B. $3.3A$

C. $2/\sqrt{5}A$

D. $\sqrt{5}A$

Answer: A




Watch Video Solution

Problems Based On Mixed Concepts

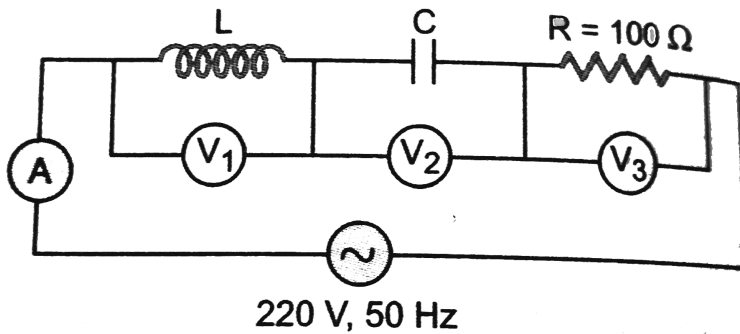1. In the given circuit, Fig., the reading of voltmeter V_1 and V_2 300 volts each. The reading

of the voltmeter V_3 and ammeter A are respectively



A. 800V, 2A

B. 300V, 2A

C. 220V, 2.2A


D. 100V, 2A

Answer: C



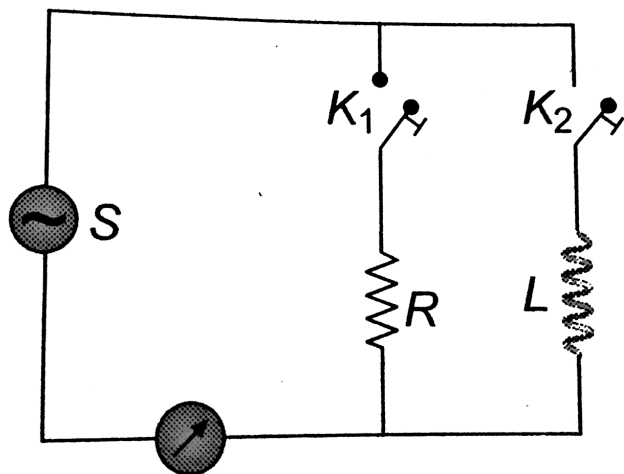2. In the circuit shown here, R is pure resistor, L is an inductor of negligible resistance (as compared to R), S is a $100V, 50Hz AC$ source of negligible resistance. With either key K_1 alone or K_2 alone closed, the current is I_0 . if the source is changed to $100V, 150Hz$ the current with K_1 , alone closed

and with K_2 alone closed will be respectively.



A. $I_0, \frac{I_0}{3}$

B. $I_0, 3I_0$

C. $3I_0, I_0$

D. $3I_0, \frac{I_0}{3}$

Answer: A



3. A transmitter transmits at a wavelength of 30 meter. A condenser or capacitance $2.4\mu F$ is being used. The value of the inductance for the resonant circuit is approximately.

A. $10^{-4} H$

B. $10^{-6} H$

C. $10^{-8} H$

D. $10^{-10} H$

Answer: D



Watch Video Solution

4. A resistor and an inductor are connected in series to a 220 volt AC supply. When measured with an AC is 123 volts. Then the potential difference across the terminals of the inductor is

A. 88 volt

B. 352 volt

C. 176 volt

D. $\sqrt{220 \times 132}$ volt

Answer: C



Watch Video Solution

5. In a step-up transformer the turn ratio is $1:10$. A resistance of $200\ \text{ohm}$ connected across the secondary is drawing a current of 0.5A . What is the primary voltage and current?

A. 50V , 1A

B. 10V , 5A

C. 25V , 4A

D. $20V$, $2A$

Answer: B



Watch Video Solution

6. A 50 Hz a.c. current of crest value $1A$ flows through the primary of a transformer. If the mutual inductance between the primary and secondary be $1.5H$, the crest voltage induced in secondary is-

A. $75V$

B. $150V$

C. $225V$

D. $300V$



Answer: D



Watch Video Solution

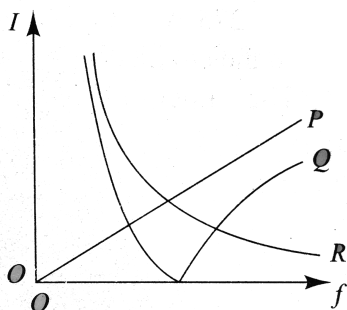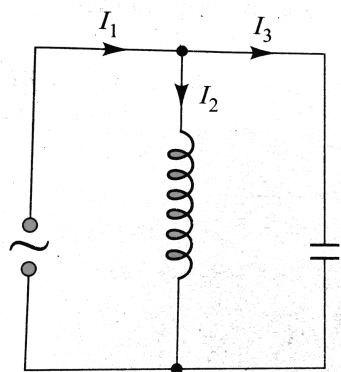7. In the circuit shown in fig, the rms currents (I_1) , (I_2) and (I_3) are altered by varying the frequency f of the oscillator. The output voltage of the oscillator remains sinusoidal and has a fixed amplitude.

When curves in figure correctly indicate the variation with frequency of the currents (I_1), (I_2), and (I_3).




- A. I_1 I_2 I_3
 q q q
- B. I_1 I_2 I_3
 r q q
- C. I_1 I_2 I_3
 q p r
- D. I_1 I_2 I_3
 q r p

Answer: D



Watch Video Solution

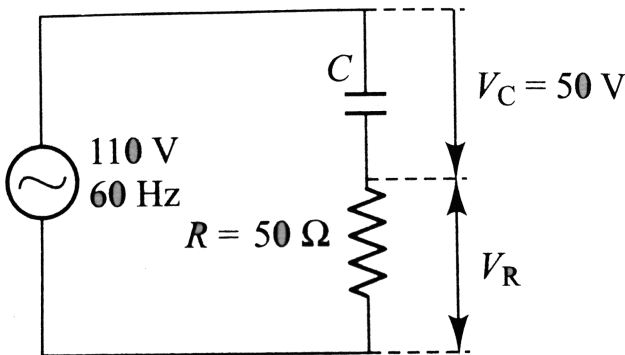8. In the circuit given in fig. $(V_C) = 50V$ and $R = 50\Omega$. The values of C and (V_R) are



A. $3.3\mu F$, $60V$

B. $3.3\mu F, 98V$

C. $1.6\mu F, 30V$

D. $2\mu F, 60V$

Answer: B



Watch Video Solution

9. A power transformer is used to set up an alternating e.m.f of $220V$ to $4.4kV$ to transmits $6.6kW$ of power. The primary coil has 1000 turns. What is current rating of secondary? (Assume efficiency is 100 %)

A. $2.5A$

B. $1.5A$

C. $1.0A$

D. $0.75A$

Answer: B



Watch Video Solution

10. A 220-V, 50 Hz, ac generator is connected to an inductor and a 50Ω resistance in series. The

current in the circuit is $1.0A$. What is the PD across inductor?

A. $102.2V$

B. $186.4V$

C. $213.6V$

D. $302V$

Answer: C



Watch Video Solution

11. An $8\mu F$ capacitor is connected across a 220 V, 50 Hz line. What is the peak value of charge through the capacitor?

A. $2.5 \times 10^{-3} C$

B. $2.5 \times 10^{-4} C$

C. $5 \times 10^{-5} C$

D. $7.5 \times 10^{-2} C$

Answer: A



Watch Video Solution

12. A coil of inductance $0.1H$ is connected to $50V$, $100Hz$ generator and current is found to be $0.5A$. The potential difference across resistance of coil is:

A. $15V$

B. $20V$

C. $25V$

D. $39V$

Answer: D



Watch Video Solution

13. A dc ammeter and a hot wire ammeter are connected to a circuit in series. When a direct current is passed through circuit, the dc ammeter shows 6 A. When ac current flows through circuit, the ac ammeter shows 8A. What will be reading of each ammeter if dc and ac current flow simulataneously through the circuit?

A. $DC = 6A, AC = 10A$

B. $DC = 3A, AC = 5A$

C. $DC = 5A, AC = 8A$

D. $DC = 2A, AC = 3A$


Answer: A



Watch Video Solution

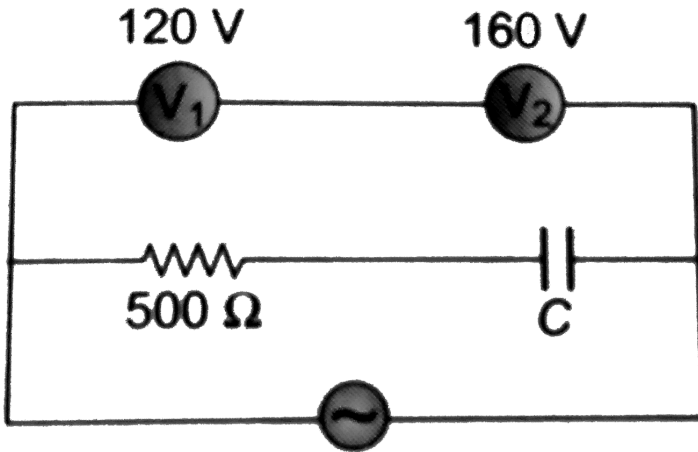14. A 500Ω resistor and a capacitor C are connected in series across $50HzAC$ supply mains. The r.m.s potential difference recorded on voltmeter V_1 and V_2 are $V_1 = 120V$ and

$V_2 = 160V$. The power taken for the mains is:




- A. $480W$
- B. $240W$
- C. $28.8W$
- D. $14.4W$

Answer: C



Watch Video Solution

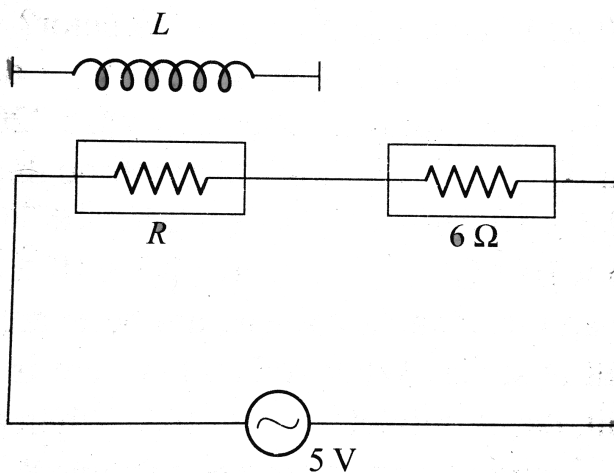15. Two resistor are connected in series across a $5V$ rms source of alternating potential. The potential difference across 6Ω resistor is $3V$. If R is replaced by a pure inductor L of such magnitude that current remains same. Then the potential difference across L is



A. $1V$

B. $2V$

C. $3V$

D. $4V$

Answer: D



Watch Video Solution

16. A coil has an inductance of 0.7 H and is joined in series with a resistance of 220 ohm . Find the wattless component of current in the circuit,

when an alternating e.m.f. of 220 V at a frequency of 50 Hz is supplied to it.

A. $0.2A$

B. $0.4A$

C. $0.5A$


D. $0.7A$

Answer: C



Watch Video Solution

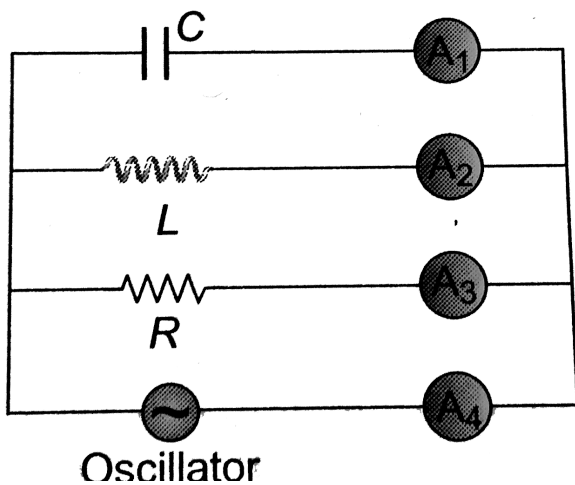17. In the circuit shown in figure when the frequency of oscillator is increased, the reading of ammeter A_4 is same as that of ammeter.



A. A_1

B. A_2

C. A_3


D. A_1 and A_2

Answer: C



Watch Video Solution

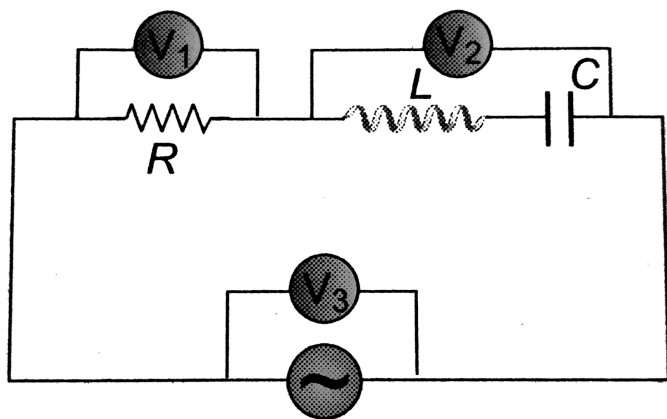18. In the figure shown, three AC voltmeters have been connected. At resonance, the reading of



A. V_1 is zero

B. V_2 is zero

C. V_3 is zero

D. $V_1 = V_2 = V_3 = \text{zero}$


Answer: B



Watch Video Solution

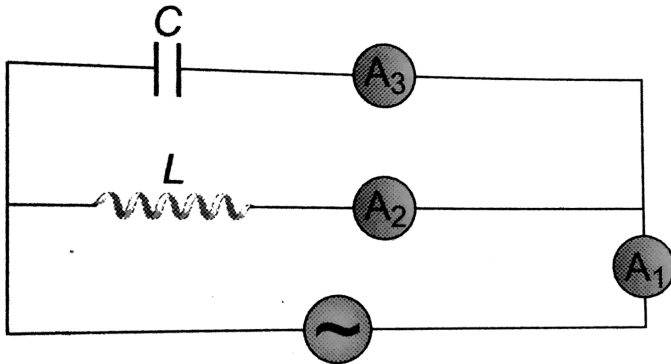19. An inductor L , a capacitor C and AC ammeters A_1 , A_2 and A_3 are connected in the circuit as shown. When the frequency of the

oscillators is increased, then at resonant frequency, the reading of ammeter ?



- A. A_1 zero
- B. A_2 zero
- C. A_3 zero
- D. is same in A_1 , A_2 and A_3


Answer: A



Watch Video Solution

20. In the circuit shown, R is a pure resistor, L is an inductor of negligible resistance (as compared to R) and S is a $100V, 50Hz AC$ source of negligible resistance. With either key k_1 alone or k_2 alone closed, the current is I_0 . If the source is changed to $100V, 100Hz$, the current with k_1 alone closed and with k_2 alone closed will be

respectively

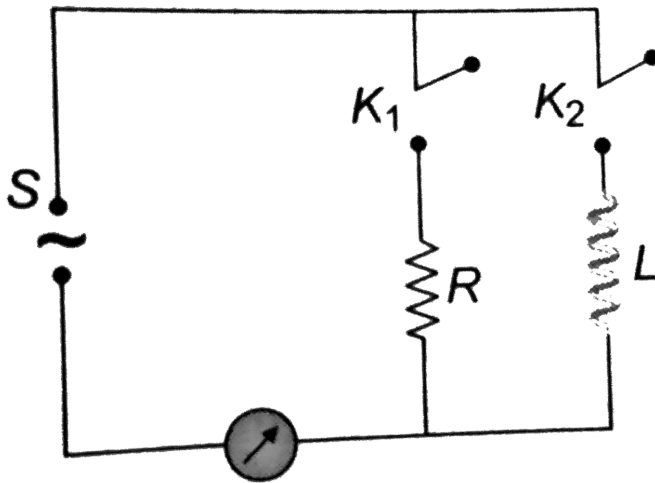

- A. $I_0, \frac{1}{2}I_0$
- B. $2I_0, \frac{1}{2}I_0$
- C. $2I_0, I_0$
- D. $2I_0, \frac{1}{2}I_0$


Answer: A



Watch Video Solution

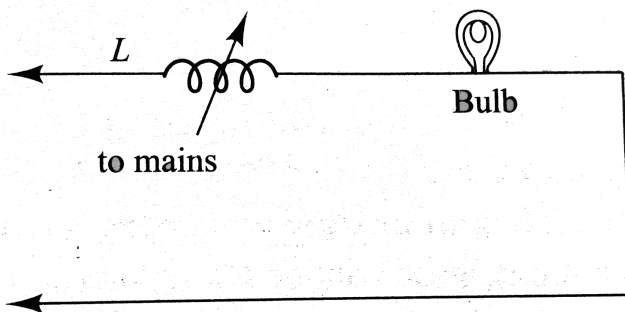21. A typical light dimmer used to dim the stage lights in a theater consists of a variable induction for L (where inductance is adjustable between zero and L_{\max}) connected in series with a light bulb B as shown in fig. the mains electrical supply is 220 V at 50 Hz, the light bulb is rated at 220 V, 1100 W. What (L_{\max}) is required if the rate of energy dissipated in the light bulb is to be varied

by a factor of 5 from its upper limits of 1100 W?



A. $0.69H$

B. $0.28H$

C. $0.38H$

D. $0.56H$

Answer: B



Watch Video Solution

22. If the instantaneous current in a circuit is given by $i = 2 \cos(\omega t - \phi)$ ampere, the r.m.s. value of the current is

- A. 2 ampere
- B. $\sqrt{2}$ ampere
- C. $2\sqrt{2}$ ampere
- D. zero ampere

Answer: B



Watch Video Solution

23. A coil has an inductance of 0.7 H and is joined in series with a resistance of 220 ohm . Find the wattless component of current in the circuit, when an alternating e.m.f. of 220 V at a frequency of 50 Hz is supplied to it.

- A. 5 ampere
- B. 0.5 ampere
- C. 0.7 ampere
- D. 7 ampere

Answer: B



Watch Video Solution

24. In a region of uniform magnetic inductance $B = 10^{-2}$ tesla. A circular coil of radius 30cm and resistance $\pi^2\text{ohm}$ is rotated about an axis which is perpendicular to the direction of B and which forms a diameter of the coil. If the coil rotates at 200 r.p.m the amplitude of the alternating current induced in the coil is

A. $4\pi^2\text{mA}$

B. 30mA

C. $6mA$


D. $200mA$

Answer: C



Watch Video Solution

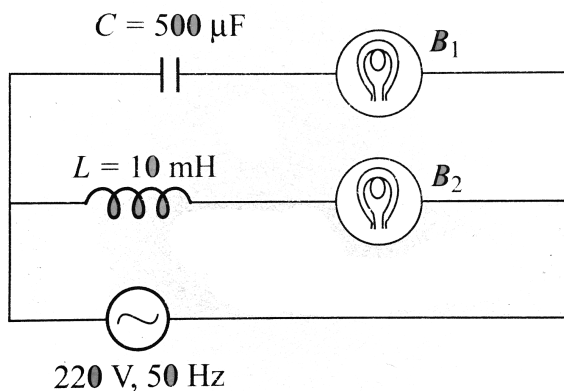25. In the circuit shown in fig. if both the bulbs (B_1) and (B_2) are identical



- A. their brightness will be the same
- B. B_2 will be brighter than B_1
- C. As frequency and that of B_2 will decreases
- D. Only B_2 will glow because the capacitor has infinite impedance

Answer: B



Watch Video Solution

26. In a region of uniform magnetic inductance $B = 10^{-2}$ tesla. A circular coil of radius $30cm$ and resistance $\pi^2 ohm$ is rotated about an axis which is perpendicular to the direction of B and which forms a diameter of the coil. If the coil rotates at 200 r.p.m the amplitude of the alternatic current induced in the coil is

A. $4\pi^2 mA$

B. $30mA$

C. $6mA$


D. 200mA

Answer: C



Watch Video Solution

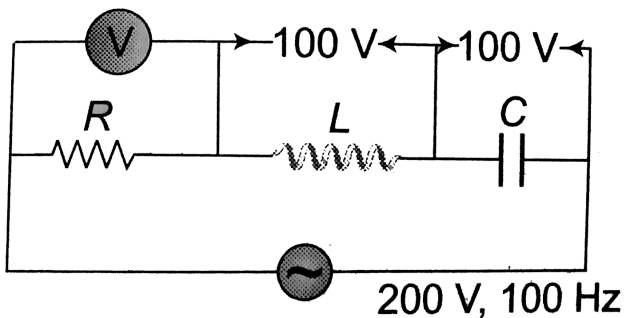27. In the circuit given below, what will be the reading of the voltmeter?



A. 300V

B. $900V$

C. $200V$


D. $400V$

Answer: C



Watch Video Solution

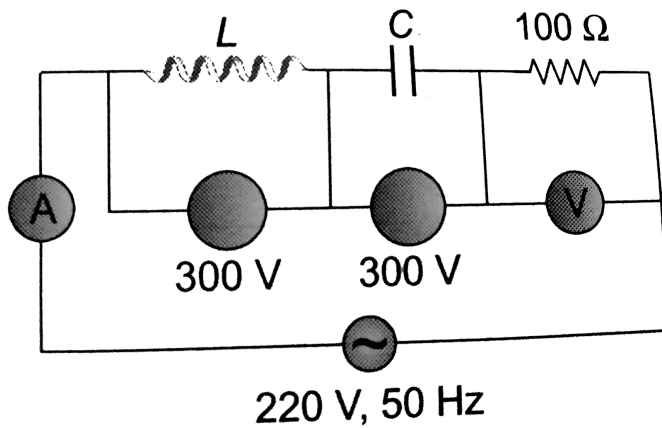28. In the circuit shown below, what will be the reading of the voltmeter and ammeter?



- A. $800\text{V}, 2\text{A}$
- B. $300\text{V}, 2\text{A}$
- C. $220\text{V}, 2.2\text{A}$
- D. $100\text{V}, 2\text{A}$


Answer: C



Watch Video Solution

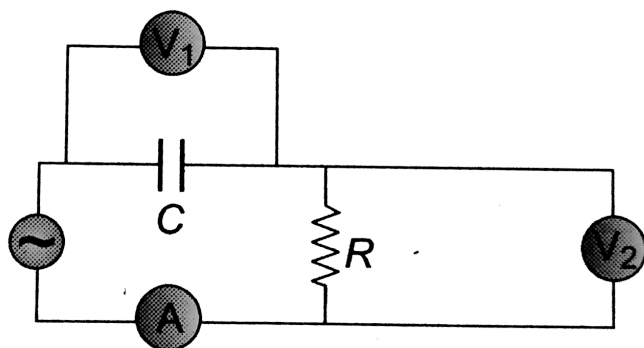29. The diagram shows a capacitor C and a resistor R connected in series to an AC source.

V_1 and V_2 are voltmeters and A is ammeter



Now, consider the following statements :

(I) Reading in A and V_2 are always in phase.

(II) Reading in V_1 is ahead in phase with reading in V_2 ,

(III) Reading in A and V_1 are always in phase.

Which of these statements are/is correct

A. I only

B. II only

C. I and II only

D. II and III only


Answer: A



Watch Video Solution

30. In the circuit shown in figure neglecting source resistance the voltmeter and ammeter

reading will respectively, will be

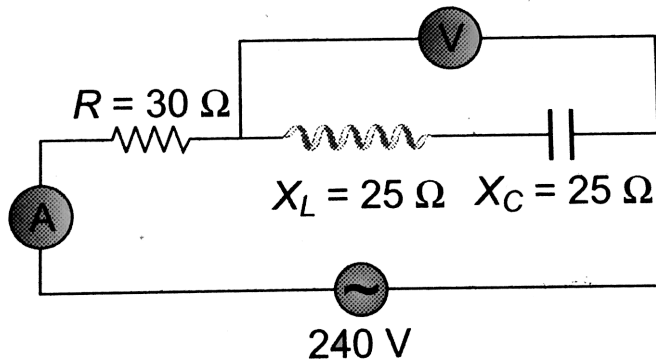


- A. $0V, 3A$
- B. $150V, 3A$
- C. $150V, 6A$
- D. $0V, 8A$

Answer: D



Watch Video Solution

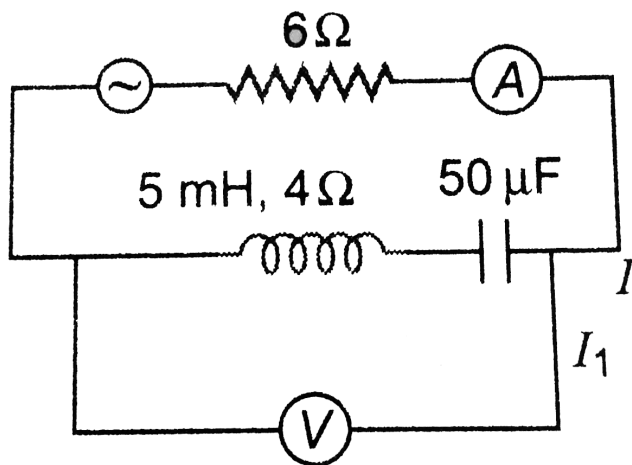31. In the circuit shown in figure the AC source gives a voltage $V = 20 \cos(2000t)$. Neglecting source resistance, the voltmeter and ammeter readings will be



A. $0V$, $0.47A$

B. $1.68V$, $0.47A$

C. $0V$, $1.4A$

D. $5.6V$, $1.4A$

Answer: D



Watch Video Solution

32. A telephone wire of length $200km$ has a capacitance of $0.014\frac{\mu F}{km}$. If it carries an AC of frequency $5kHz$ what should be the value of an inductor required to be connected in series so that impedance of the circuit is minimum ?

A. $0.35mH$

B. $35mH$

C. $3.5mH$


D. Zero

Answer: A



Watch Video Solution

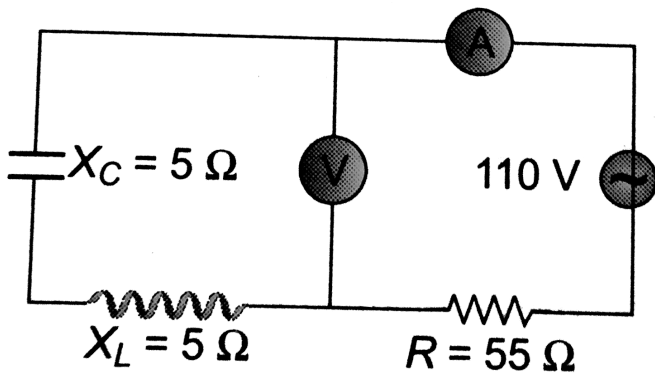33. The reading of ammeter in the circuit shown will be




- A. $2A$
- B. $2.4A$
- C. zero
- D. $1.7A$

Answer: A



Watch Video Solution

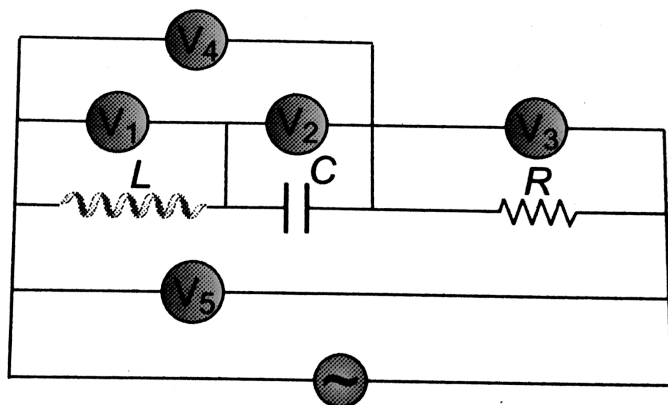34. In the adjoining AC circuit the voltmeter whose reading will be zero at resonance is



A. V_1

B. V_2

C. V_3


D. V_4

Answer: D



Watch Video Solution

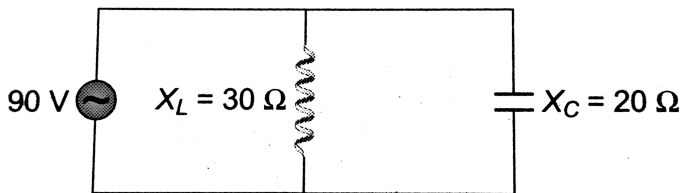35. In the adjoining figure the impedance of the circuit will be



A. 120 ohm

B. 50 ohm

C. 60 ohm

D. 90 ohm

Answer: C



Watch Video Solution

36. In a series circuit $C = 2\mu F$, $L = 1mH$ and $R = 10\Omega$, when the current in the circuit is maximum, at that time the ratio of the energies stored in the capacitor and the inductor will be

A. 1 : 1

B. 1 : 2

C. 2:1

D. 1:5





Answer: D




Watch Video Solution

37. An alternating current I in an inductance coil varies with time t according to the graph as shown: Which one of the following graph gives

the variation of voltage with time?

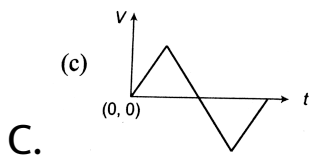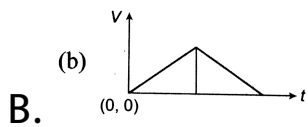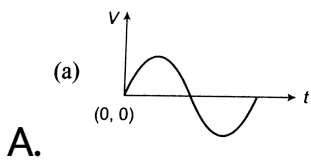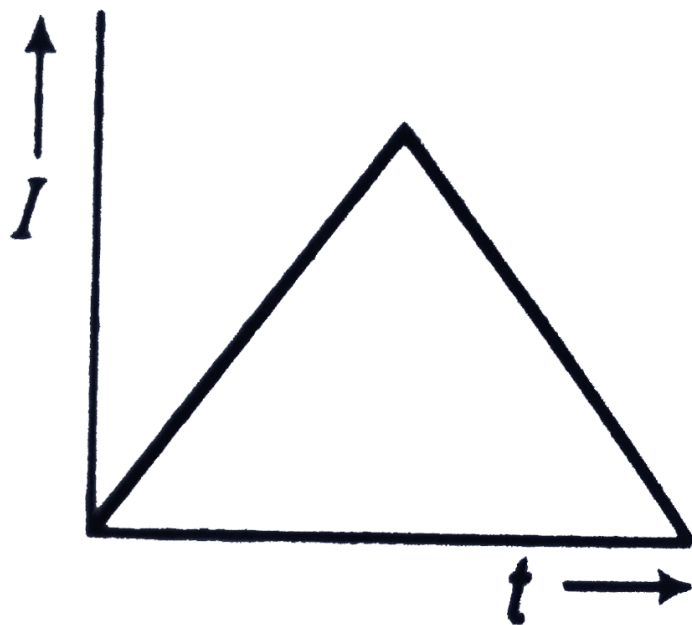


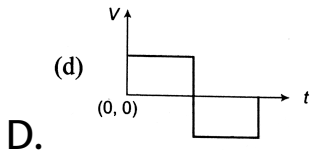

Answer: B

 **Watch Video Solution**

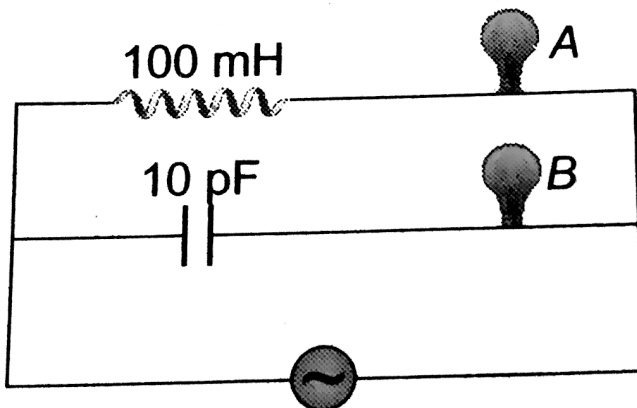38. If A and B are identical bulbs, which bulb glows brighter?



A. A

B. B

C. Both equally bright

D. Cannot say

Answer: A



Watch Video Solution

39. In an LCR circuit $R = 100\Omega$. When capacitance C is removed, the current lags behind the voltage by $\pi/3$. When inductance L is

removed, the current leads the voltage by $\pi/3$.

The impedance of the circuit is

A. 50Ω

B. 100Ω

C. 200Ω


D. 400Ω

Answer: B



Watch Video Solution

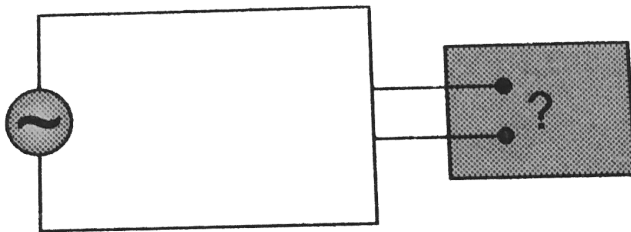40. Following figure shows an AC generator connected to a "block box" through a pair of terminals. The box contains possible R , L , C or their combination, whose elements and arrangements are not known to us.



Measurements, outside the box reveals that $e = 75 \sin(\omega t)$ volts, $i = 1.5 \sin(\omega t + 45^\circ)$ ampere. Then the wrong statement is

A. There must be a capacitor in the box.

- B. There must be an inductor in the box.
- C. There must be a resistance in the box.
- D. The power factor is 0.70.

Answer: B



Watch Video Solution

Section B - Assertion Reasoning

1. STATEMENT-1: By only knowing the power factor for a given LCR circuit it is not possible to tell

whether the applied alternating emf leads or lags the current.

STATEMENT-2: $\cos \theta = \cos(-\theta)$

A. If both the assertion and reason are true and reason is a true explanation of the assertion.

B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.

C. If the assertion is true but reason false

D. If both the assertion and reason are false.

Answer: A



Watch Video Solution

2. Statement 1: In the purely resistive element of a series LCR, ac circuit the maximum value of rms current increase with increase in the angular frequency of the applied emf.

Statement

2:

$$I_{\max} = \frac{\varepsilon_{\max}}{Z}, Z = \sqrt{R^2 + \left(\omega L - \frac{1}{(\omega C)^2} \right)^2},$$

where (I_{\max}) is the peak current in a cycle.

A. If both the assertion and reason are true and reason is a true explanation of the assertion.

B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.

C. If the assertion is true but reason false

D. If both the assertion and reason are false.

Answer: D



Watch Video Solution

3. Statement 1: In a series LCR circuit at resonance condition power consumed by circuit is maximum.

Statement 2 : At resonance condition, the effective resistance of circuit is maximum.

A. If both the assertion and reason are true and reason is a true explanation of the assertion.

B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.

C. If the assertion is true but reason false

D. If both the assertion and reason are false.

Answer: C



Watch Video Solution

4. Assertion: In series $L - R$ circuit voltage leads the current.

Reason: In series $L - C$ circuit leads the voltage.

A. If both the assertion and reason are true
and reason is a true explanation of the
assertion.

- B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.
- C. If the assertion is true but reason false
- D. If both the assertion and reason are false.

Answer: B



Watch Video Solution

5. Assertion: Average value of AC over a complete cycle is always zero.

Reason: Average value of AC is always defined over half cycle.

A. If both the assertion and reason are true and reason is a true explanation of the assertion.

B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.

C. If the assertion is true but reason false


D. If both the assertion and reason are false.

Answer: B



Watch Video Solution

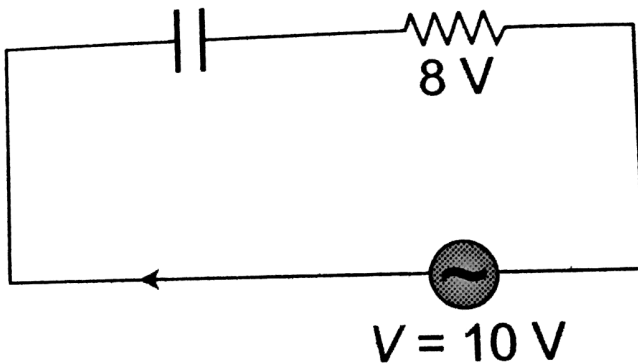6. Assertion: *KVL* rule is also being applied in *AC* circuit shown below.



V_C in the circuit $= 2V$.

A. If both the assertion and reason are true and reason is a true explanation of the assertion.

B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.

C. If the assertion is true but reason false

D. If both the assertion and reason are false.

Answer: C



Watch Video Solution

7.Assertion: AC generators are based upon EMI principle.

Reason: Resistance offered by capacitor for alternating current is zero.

A. If both the assertion and reason are true and reason is a true explanation of the assertion.

B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.

C. If the assertion is true but reason false

D. If both the assertion and reason are false.

Answer: C



Watch Video Solution

8. Assertion: Rate of heat generated when resistance is connected with AC source depends on time.

Reason : $R.M.S.$ voltage may be greater than maximum AC voltage.

A. If both the assertion and reason are true and reason is a true explanation of the assertion.

B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.

C. If the assertion is true but reason false

D. If both the assertion and reason are false.

Answer: C



Watch Video Solution

9. An inductor, a capacitor, and a resistor are connected in series. The combination is connected across an ac source.

Statement 1: Peak current through each remains same.

Statement 2: Average power delivered by source is equal to average power developed across resistance.

A. If both the assertion and reason are true and reason is a true explanation of the assertion.

B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.

C. If the assertion is true but reason false

D. If both the assertion and reason are false.

Answer: B



Watch Video Solution

10. Assertion: In alternating current direction of motion free electron changes periodically.

Reason: Alternating current changes its direction after certain time interval.

A. If both the assertion and reason are true and reason is a true explanation of the assertion.

B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.

C. If the assertion is true but reason false

D. If both the assertion and reason are false.

Answer: B



Watch Video Solution

11. Assertion: When frequency is greater than resonance frequency in a series LCR circuit, it will be an inductive circuit.

Reason : Resultant voltage will lead the current.

A. If both the assertion and reason are true and reason is a true explanation of the assertion.

B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.

C. If the assertion is true but reason false

D. If both the assertion and reason are false.

Answer: A



Watch Video Solution

12. Assertion: When capacitive reactance is smaller than the inductive reactance in an LCR circuit, e.m.f.

leads the current.

Reason : The phase angle is the angle between the alternating e.m.f. and alternating current of the circuit.

A. If both the assertion and reason are true and reason is a true explanation of the assertion.

B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.

C. If the assertion is true but reason false

D. If both the assertion and reason are false.

Answer: C



Watch Video Solution

13. Statement 1: An alternating current shown magnetic effect.

Statement 2: Alternating current varies with time .

A. If both the assertion and reason are true
and reason is a true explanation of the
assertion.

- B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.
- C. If the assertion is true but reason false
- D. If both the assertion and reason are false.

Answer: B



Watch Video Solution

14. Assertion: The alternating current lags behind the e.m.f. by a phase angle of $\pi/2$, when

AC flows through an inductor.

Reason: The inductive reactance increases as the frequency of AC source decreases.

A. If both the assertion and reason are true and reason is a true explanation of the assertion.

B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.

C. If the assertion is true but reason false

D. If both the assertion and reason are false.

Answer: C



Watch Video Solution

15. Assertion: Capacitance serves as a block for DC and offers an easy path to AC .

Reason: Capacitance reactance is inversely proportional to frequency.

A. If both the assertion and reason are true and reason is a true explanation of the assertion.

B. If both the assertion and reason are true but the reason is not the correct explanation of the assertion.

C. If the assertion is true but reason is false

D. If both the assertion and reason are false.

Answer: A



Watch Video Solution

16. Assertion: When capacitive reactance is smaller than the inductive reactance in an LCR circuit, e.m.f.

leads the current.

Reason : The phase angle is the angle between the alternating e.m.f. and alternating current of the circuit.

A. If both the assertion and reason are true and reason is a true explanation of the assertion.

B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.

C. If the assertion is true but reason false

D. If both the assertion and reason are false.

Answer: B



Watch Video Solution

17. Assertion: Chock coil is the preferred over a resistor to adjust current in an AC circuit.

Reason: Power factor for inductance is zero.

A. If both the assertion and reason are true
and reason is a true explanation of the
assertion.

- B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.
- C. If the assertion is true but reason false
- D. If both the assertion and reason are false.

Answer: A



Watch Video Solution

18. Statement 1: An alternating current shown magnetic effect.

Statement 2: Alternating current varies with time .

A. If both the assertion and reason are true and reason is a true explanation of the assertion.

B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.

C. If the assertion is true but reason false

D. If both the assertion and reason are false.

Answer: B





19. Statement 1: Both dc and ac can be measured by a hot wire instrument.

Statement 2: the hot wire instrument is based on the principle of magnetic effect of current.

A. If both the assertion and reason are true and reason is a true explanation of the assertion.

B. If both the assertion and reason are true but the reason is not true the correct

explanation of the assertion.

C. If the assertion is true but reason false

D. If both the assertion and reason are false.

Answer: C



Watch Video Solution

20. Assertion: AC is more dangerous than DC

Reason: Frequency of AC is dangerous for human body.

A. If both the assertion and reason are true and reason is a true explanation of the assertion.

B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.

C. If the assertion is true but reason false

D. If both the assertion and reason are false.

Answer: A



Watch Video Solution

21. Assertion: Average value of AC over a complete cycle is always zero.

Reason: Average value of AC is always defined over half cycle.

A. If both the assertion and reason are true and reason is a true explanation of the assertion.

B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.

C. If the assertion is true but reason false

D. If both the assertion and reason are false.

Answer: B



Watch Video Solution

22. Assertion: The division are equally marked on the scale of AC ammeter.

Reason: Heat produced is directly proportional to the current

A. If both the assertion and reason are true
and reason is a true explanation of the

assertion.

B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.

C. If the assertion is true but reason false

D. If both the assertion and reason are false.

Answer: D



Watch Video Solution

23. Assertion: When AC circuit contain resistor only, its power is minimum.

Reason: Power of a circuit is independent of phase angle.

A. If both the assertion and reason are true and reason is a true explanation of the assertion.

B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.

C. If the assertion is true but reason false

D. If both the assertion and reason are false.

Answer: D



Watch Video Solution

24. Assertion: An electric lamp connected in series with a variable capacitor and AC source, its brightness increases with increases in capacitance.

Reason: Capacitive reactance decrease with increases in capacitance of capacitor.

A. If both the assertion and reason are true and reason is a true explanation of the assertion.

B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.

C. If the assertion is true but reason false

D. If both the assertion and reason are false.

Answer: A



Watch Video Solution

25. Assertion: An inductance and a resistance are connected in series with an AC circuit. In this circuit the current and the potential difference across the resistance lag behind potential difference across the inductance by an angle $\pi/2$.

Reason: In LR circuit voltage leads the current by phase angle which depends on the value of inductance and resistance both.

A. If both the assertion and reason are true and reason is a true explanation of the assertion.

- B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.
- C. If the assertion is true but reason false
- D. If both the assertion and reason are false.

Answer: B



Watch Video Solution

26. Assertion: A capacitor of suitable capacitance can be used in an AC circuit in place of the choke

coil.

Reason: A capacitor blocks DC and allows AC

- A. If both the assertion and reason are true and reason is a true explanation of the assertion.
- B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.
- C. If the assertion is true but reason false
- D. If both the assertion and reason are false.

Answer: B



Watch Video Solution

AIPMT/NEET Questions

1. In an AC circuit, the current is given by $i = 5 \sin\left(100t - \frac{\pi}{2}\right)$ and the AC potential is $V = 200 \sin(100t)$ volt. Then the power consumption is

A. 20 watts

B. 40 watt

C. 1000 watt

D. 0 watt

Answer: D



Watch Video Solution

2. In a circuit, the value of the alternating current is measured by hot wire ammeter as 10 ammeter. Its peak value will be

A. $10A$

B. $20A$

C. $14.14A$

D. $7.07A$

Answer: C



Watch Video Solution

3. If the value of potential in an *ac*, circuit is $10V$, then the peak value of potential is

A. $\frac{10}{\sqrt{2}}$

B. $10\sqrt{2}$

C. $20\sqrt{2}$

D. $\frac{20}{\sqrt{2}}$

Answer: B



Watch Video Solution

4. A coil of $40H$ inductance is connected in series with a resistance of 8 ohm and the combination is joined to the terminals of a $2V$ battery. The time constant of the circuit

A. $5s$

B. $1/5s$

C. $40s$

D. $20s$

Answer: A



Watch Video Solution

5. In a circuit L , C and R are connected in series with an alternating voltage source of frequency f .

The current lead the voltages by 45° . The value of

C is :

A.
$$\frac{1}{2\pi f(2\pi fL + R)}$$

$$\text{B. } \frac{1}{\pi f(2\pi fL + R)}$$

$$\text{C. } \frac{1}{2\pi f(2\pi fL - R)}$$

$$\text{D. } \frac{1}{\pi f(2\pi fL - R)}$$

Answer: C



Watch Video Solution

6. A coil of inductive reactance 31Ω has a resistance of 8ω . It is placed in series with a condenser of capacitive reactance 25Ω . The combination is connected to an *ac* source of $110V$. The power factor of the circuit is

A. 0.56

B. 0.64

C. 0.80

D. 0.33

Answer: C



Watch Video Solution

7. The core of any transformer is laminated so as to

- A. energy losses due to Eddy currents may be minimised
- B. the weight of the transformer may be reduced
- C. rusting of the core may be prevented
- D. ratio of voltage in primary and secondary may be increased

Answer: A



Watch Video Solution

8. A transistor -oscillator using a resonant circuit with an inductor L (of negligible resistance) and a capacitor C in series produce oscillations of frequency f . If L is doubled and C is changed to $4C$, the frequency will be

A. $f/4$

B. $8f$

C. $f/2\sqrt{2}$

D. $f/2$

Answer: C



Watch Video Solution

9. The primary and secondary coils of a transformer have 50 and 1500 turns respectively. If the magnetic flux ϕ linked with the primary coil is given by $\phi = \phi_0 + 4t$, where ϕ is in weber, t is time in second and ϕ_0 is a constant, the output voltage across the secondary coil is

A. $90V$

B. $120V$

C. $220V$

D. $30V$

Answer: B



Watch Video Solution

10. A transformer is used to light a $100W$ and $110V$ lamp from a $220V$ mains. If the main current is $0.5A$, the efficiency of the transformer is approximately:

A. 30 %

B. 50 %

C. 90 %

D. 10 %

Answer: C



Watch Video Solution

11. What is the value of inductance L for which the current is a maximum in series LCR circuit with $C = 10\mu F$ and $\omega = 1000s^{-1}$?

A. $100mH$

B. $1mH$

C. Cannot be calculated unless R is known

D. $10mH$

Answer: A



Watch Video Solution

12. In any AC circuit the emf (e) and the current (i) at any instant are given respectively by

$$e = E_0 \sin \omega t$$

$$i = I_0 \sin(\omega t - \phi)$$

The average power in the circuit over one cycle of AC is

A. $\frac{E_0 I_0}{2}$

B. $\frac{E_0 I_0}{2} \sin \phi$

C. $\frac{E_0 I_0}{2} \cos \phi$

D. $E_0 I_0$

Answer: C



Watch Video Solution

13. Power dissipated in an $L - C - R$ series circuit connected to an AC source of emf ε is

A.
$$\frac{\varepsilon^2 R}{\left[R^2 + \left(L\omega - \frac{1}{C\omega} \right)^2 \right]}$$

$$\text{B. } \frac{\varepsilon^2 \sqrt{R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2}}{R}$$

$$\text{C. } \frac{\varepsilon^2 \left[R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2 \right]}{R}$$

$$\text{D. } \frac{\varepsilon^2 R}{\sqrt{R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2}}$$


Answer: A



Watch Video Solution

14. In the given circuit, Fig., the reading of voltmeter V_1 and V_2 300 volts each. The reading of the voltmeter V_3 and ammeter A are

respectively

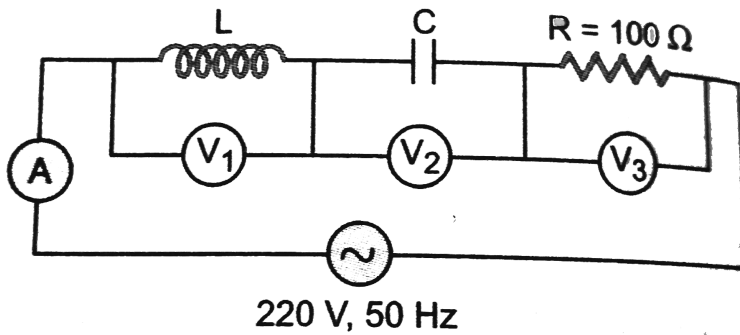

A. 150V, 2.2A

B. 220V, 2.2A

C. 220V, 2.0A

D. 100V, 2.0A

Answer: B



Watch Video Solution

15. A $220V$ input is supplied to a transformer. The output circuit draws a current of $2.0A$ at $440V$. If the efficiency of the transformer is 80% , the current drawn by the primary winding of the transformer is

A. $3.6A$

B. $2.8A$

C. $2.5A$

D. $5.0A$

Answer: D



Watch Video Solution

16. An AC voltage is applied to a resistance R and an inductance L in series. If R and the inductive reactance are both equal to 3Ω , the phase difference between the applied voltage and the current in the circuit is

A. $\pi / 4$

B. $\pi / 2$

C. zero

D. $\pi / 6$

Answer: A



Watch Video Solution

17. In an ac circuit , an alternating voltage $e = 200\sqrt{2}\sin 100t$ volts is connected to a capacitor of capacitance $1\mu F$. The rms value of the current in the circuit is :

A. $100mA$

B. $200mA$

C. $20mA$


D. $10mA$

Answer: C



Watch Video Solution

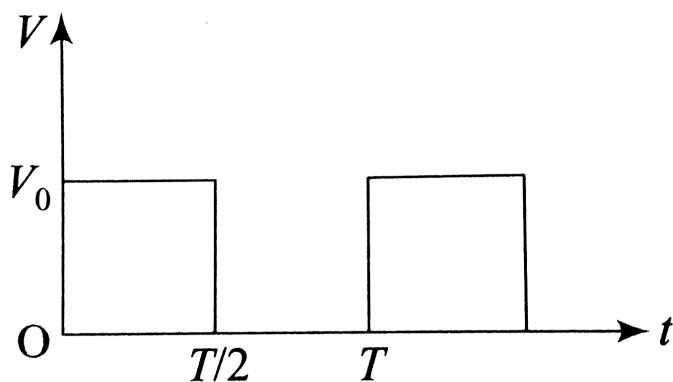18. The rms value of potential difference V shown in the figure is



A. V_0

B. $\frac{V_0}{\sqrt{2}}$

C. $\frac{V_0}{2}$

D. $\frac{V_0}{\sqrt{3}}$

Answer: B



Watch Video Solution

19. A coil has resistance 30Ω and inductive reactance 20Ω at 50Hz frequency. If an ac

source of 200 volts. $100H\Omega$, is connected across the coil, the current in the coil will be

A. $4.0A$

B. $8.0A$

C. $\frac{20}{\sqrt{13}}A$

D. $2.0A$

Answer: A



Watch Video Solution

20. In an electrical circuit R , L , C and an AC voltage source are all connected in series. When L is removed from the circuit, the phase difference between the voltage and the current in the circuit is $\pi/3$. If instead, C is removed from the circuit, difference the phase difference is again $\pi/3$. The factor of the circuit is

A. $\frac{1}{2}$

B. $\frac{1}{\sqrt{2}}$

C. 1

D. $\frac{\sqrt{3}}{2}$


Answer: C




Watch Video Solution

21. An alternating current I in an inductance coil varies with time t according to the graph as shown: Which one of the following graph gives


the variation of voltage with time?

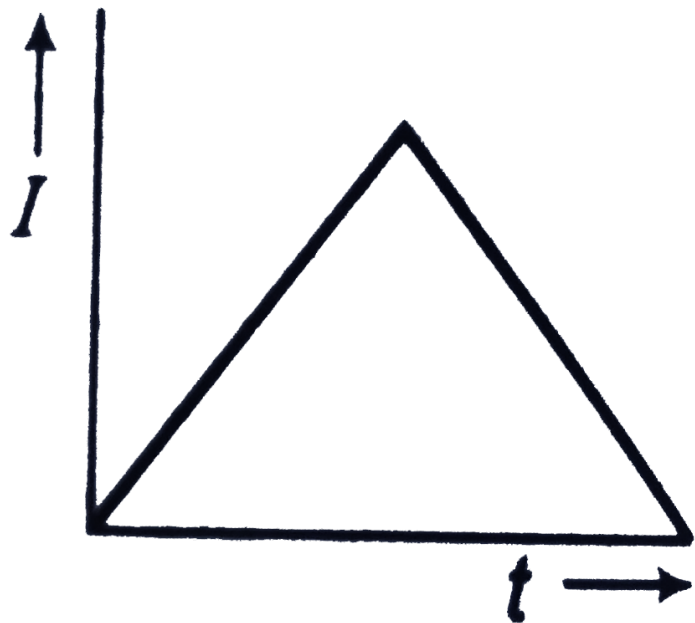


A.

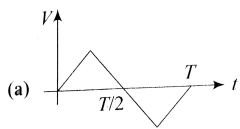


B.

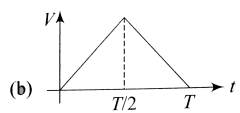

C.

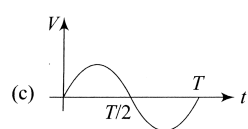

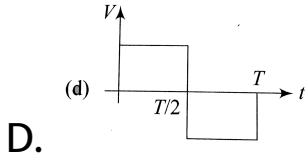

Answer: D



Watch Video Solution

22. The instantaneous value of alternating current and voltages in a circuit are given as

$$i = \frac{1}{\sqrt{2}} \sin(100\pi t) \text{ ampere}$$

$$e = \frac{1}{\sqrt{2}} \sin(100\pi t + \pi/3) \text{ volt}$$

The average power in watts consumed in the circuit is

A. $\frac{1}{4}$

B. $\frac{\sqrt{3}}{4}$

C. $\frac{1}{2}$

D. $\frac{1}{8}$

Answer: D



Watch Video Solution

23. A coil of self-inductance L is connected in series with a bulb B and an AC source. Brightness of the bulb decreases when

- A. Frequency of the AC source is decreased
- B. Number of turns in the coil is reduced
- C. A capacitance of reactance $X_C = X_L$ is included in the same circuit
- D. An iron rod is inserted in the coil

Answer: D



Watch Video Solution

24. A transformer having efficiency of 90% is working on $200V$ and $3kW$ power supply. If the

current in the secondary coil is $6A$, the voltage across the secondary coil and current in the primary coil respectively are

A. $300V$, $15A$

B. $450V$, $15A$

C. $450V$, $13.5A$

D. $600V$, $15A$

Answer: B



Watch Video Solution

25. A resistance R draws power P when connected to an AC source. If an inductance is now placed in series with the resistance, such that the impedance of the circuit becomes Z , the power drawn will be

A. $P\left(\frac{R}{Z}\right)^2$

B. $P\sqrt{\frac{R}{Z}}$

C. $P\left(\frac{R}{Z}\right)$

D. P

Answer: A



Watch Video Solution

26. A series $R - C$ circuit is connected to an alternating voltage source. Consider two situations

(a) When capacitor is air filled.

(b) When capacitor is mica filled.

current through resistor is i and voltage across capacitor is V then

A. $V_a = V_b$

B. $V_a < V_b$

C. $V_a > V_b$

D. $i_a = i_b$

Answer: C



Watch Video Solution

27. The input signal given to a CE amplifier having a voltage gain of 150 is $V_i = 2 \cos\left(15t + \frac{\pi}{3}\right)$. The corresponding output signal will be

A. $300 \cos\left(15t + \frac{4\pi}{3}\right)$

B. $300 \cos\left(15t + \frac{\pi}{3}\right)$

C. $75 \cos\left(15t + \frac{2\pi}{3}\right)$

D. $2 \cos\left(15t + \frac{5\pi}{3}\right)$

Answer: A



Watch Video Solution

28. An inductor $20mH$, a capacitor $50\mu F$ and a resistor 40Ω are connected in series across of emf $V = 10 \sin 340t$. The power loss in *A.C.* circuit is

A. $0.89W$

B. $0.51W$

C. $0.67W$

D. $0.76W$

Answer: B



Watch Video Solution

29. A small signal voltage $V(t) = V_0 \sin \omega t$ is applied across an ideal capacitor C :

A. Current $I(t)$, lags voltage $V(t)$ by 90°

B. Over a full cycle the capacitor C does not consume any energy from the voltage source.

C. Current $I(t)$ is in phase with voltage $V(t)$

D. Current $I(t)$ leads voltage $V(t)$ by 180°

Answer: B



Watch Video Solution

30. Which of the following combinations should be selected for better turning of an LCR circuit

used for communication ?

A. $R = 15\Omega, L = 3.5H, C = 30\mu F$

B. $R = 25\Omega, L = 1.5H, C = 45\mu F$

C. $R = 20\Omega, L = 1.5H, C = 35\mu F$

D. $R = 25\Omega, L = 2.5H, C = 45\mu F$

Answer: A



Watch Video Solution

31. The potential differences across the resistance, capacitance and inductance are $80V$, $40V$ and

100V respectively in an $L - C - R$ circuit. The power factor of this circuit is

A. 0.8

B. 1.0

C. 0.4

D. 0.5

Answer: A



Watch Video Solution

1. In a circuit, the current lags behind the voltage by a phase difference of $\pi/2$, the circuit will contain which of the following ?

A. Only R

B. Only L

C. R and C

D. only C

Answer: B



Watch Video Solution

2. A lamp consumes only 50 % of peak power in an *a. c.* circuit. What is the phase difference between the applied voltage and the circuit current

A. $\frac{\pi}{6}$

B. $\frac{\pi}{3}$

C. $\frac{\pi}{4}$

D. $\frac{\pi}{2}$

Answer: B



Watch Video Solution

3. An an ideal parallel LC circuit, the capacitor is charged by connecting it to a DC source which is then disconnected. The current in the circuit

- A. becomes zero instantaneously
- B. oscillates instantaneously
- C. grows monotonically
- D. decays monotonically

Answer: B



Watch Video Solution

4. A capacitor of capacitance $2\mu F$ is connected in the tank circuit of an oscillator oscillating with a frequency of 1 kHz. If the current flowing in the circuit is $2mA$, the voltage across the capacitor will be

A. $0.32V$

B. $0.16V$

C. $79.5V$

D. $159V$

Answer: B



Watch Video Solution

5. A short-circuited coil is placed in a time-varying magnetic field. Electrical power is dissipated due to the current induced in the coil. If the number of turns were to be quadrupled and the wire radius halved, the electrical power dissipated would be

A. halved

B. the same

C. doubled

D. quadrupled

Answer: B



Watch Video Solution

6. Power factor is maximum in an LCR circuit when

A. $X_L = X_C$

B. $R = 0$

C. $X_L = 0$



D. $X_C = 0$



Answer: A



Watch Video Solution

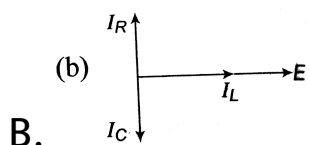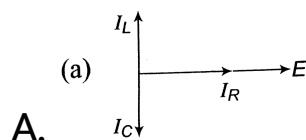7. An alternating emf is applied across a parallel combination of a resistance R , capacitance C and an inductance L . If I_R, I_L, I_C are the currents through R, L and C respectively. Then the diagram which correctly represents, the phase relationship among I_R, I_L, I_C and source emf E is given by



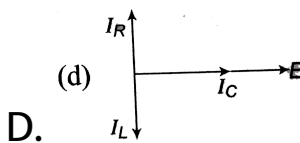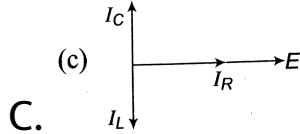

Answer: C



Watch Video Solution

8. An ac source of angular frequency ω is fed across a resistor R and a capacitor C in series. The current registered is I . If now the frequency of source is changed to $\omega/3$ (but maintaining the same voltage), the current in the circuit is found

to be halved. Calculate the ratio of the reactance to resistance at the original frequency ω .

A. $\sqrt{\frac{2}{5}}$

B. $\sqrt{\frac{3}{5}}$

C. $\sqrt{\frac{1}{5}}$

D. $\sqrt{\frac{4}{5}}$

Answer: B



Watch Video Solution

9. A circuit has a resistance of 11Ω , an inductive reactance of 25Ω , and a capacitive resistance of 18Ω . It is connected to an AC source of $260V$ and $50Hz$. The current through the circuit (in amperes) is

A. 11

B. 15

C. 18

D. 20

Answer: D



Watch Video Solution

10. A coil of 200Ω resistance and $1.0H$ inductance is connected to an AC source of frequency $200/2\pi Hz$. Phase angle between potential and current will be

A. 30°


B. 90°

C. 45°

D. 0°

Answer: C

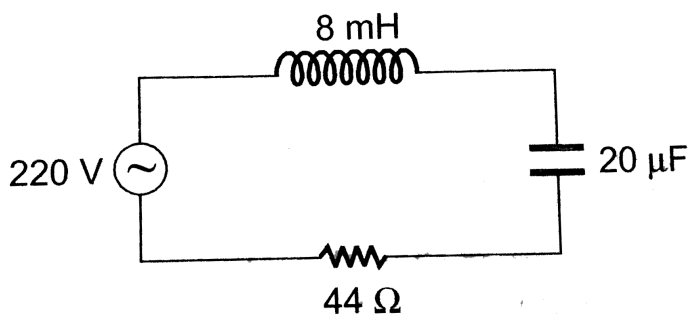11. For the series LCR circuit shown in the figure, what is the resonance frequency and the amplitude of the current at the resonating frequency



A. 2500rad s^{-1} and $5\sqrt{2}\text{A}$

B. 2500rad s^{-1} and 5A

C. 2500rads^{-1} and $\frac{5}{\sqrt{2}}A$

D. 25rads^{-1} and $5\sqrt{2}A$

Answer: B



Watch Video Solution

12. A coil of inductance 8.4 mH and resistance $6(\Omega)$ is connected to a 12 V battery. The current in the coil is 1.0 A at approximately the time

A. 500 sec

B. 20sec

C. 35 milli sec

D. 1milli sec


Answer: D



Watch Video Solution

13. In an LCR circuit as shown below both switches are open initially. Now switch S_1 kept open. (q is charge on the capacitor and $\tau = RC$ is Capacitive time constant). Which of the following statement

is correct?

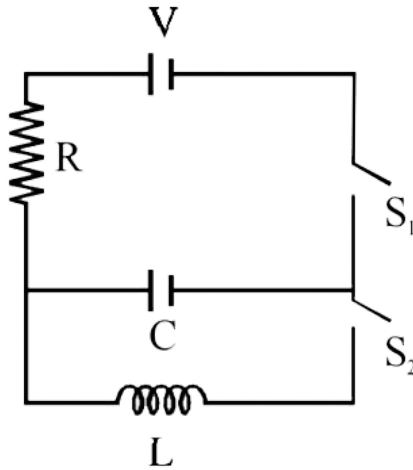

A. At $t = \tau/2$, $q = CV(1 - e^{-1})$

B. Work done by the battery is half of the energy dissipated in the resistor

C. At $t = 2\tau$, $q = CV(1 - e^{-2})$

D. At $t = \tau$, $q = CV/2$

Answer: C



Watch Video Solution

14. A step-down transformer is used on a $1000V$ line to deliver $20A$ at $120V$ at the secondary coil. If the efficiency of the transformer is 80% the current drawn from the line is.

A. $3A$

B. $30A$

C. $0.3A$

D. $2.4A$

Answer: A



Watch Video Solution

15. In a LCR series resonating circuit. Give the value of average power loss.

A. VI

B. $\frac{VI}{2}$

C. $\frac{VI}{\sqrt{2}}$

D. $\frac{VI}{\sqrt{3}}$

Answer: B



Watch Video Solution

16. Assertion: If the frequency of alternating current in an AC circuit consisting of an inductance coil is increased then current gets decreased.

Reason: The current is inversely proportional to frequency of alternating current.

A. If both the assertion and reason are true
and reason is a true explanation of the

assertion.

B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.

C. If the assertion is true but reason false

D. If both the assertion and reason are false.

Answer: A



Watch Video Solution

17. Assertion: The quantity L/R possesses dimensions of time.

Reason: To reduce the rate of increases of current through a solenoid should increase the time constant (L/R).

A. If both the assertion and reason are true and reason is a true explanation of the assertion.

B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.

C. If the assertion is true but reason false

D. If both the assertion and reason are false.

Answer: B



Watch Video Solution

18. Assertion: Faraday's laws are consequences of conservation of energy.

Reason: In a purely resistive AC circuit, the current lags behind the e.m.f. in phase

A. If both the assertion and reason are true and reason is a true explanation of the assertion.

B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.

C. If the assertion is true but reason false

D. If both the assertion and reason are false.

Answer: C



Watch Video Solution

19. Assertion: An electric lamp connected in series with a variable capacitor and AC source, its brightness increases with increases in capacitance.

Reason: Capacitive reactance decrease with increases in capacitance of capacitor.

A. If both the assertion and reason are true and reason is a true explanation of the assertion.

B. If both the assertion and reason are true but the reason is not true the correct

explanation of the assertion.

C. If the assertion is true but reason false

D. If both the assertion and reason are false.

Answer: A



Watch Video Solution

20. Assertion: The probability of an electric bulb fusing is higher at the time of switching *ON* and *OFF*.

Reason: Inductive effects produce a surge at the time of switch *OFF* and switch *ON*.

A. If both the assertion and reason are true and reason is a true explanation of the assertion.

B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.

C. If the assertion is true but reason false

D. If both the assertion and reason are false.

Answer: A



Watch Video Solution

21. Assertion : An electric motor will have maximum efficiency when back emf becomes equal to half of applied emf.

Reason : Efficiency of electric motor depends only on magnitude of back emf.

A. If both the assertion and reason are true and reason is a true explanation of the assertion.

B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.

C. If the assertion is true but reason false

D. If both the assertion and reason are false.

Answer: C



Watch Video Solution

22. Assertion: In electric circuits, wires carrying currents in opposite directions are often twisted together.

Reason: If the wires are not twisted together, the combination of the wires forms a current loop,

the magnetic field generated by the loop might affect adjacent circuits of components.

A. If both the assertion and reason are true and reason is a true explanation of the assertion.

B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.

C. If the assertion is true but reason false

D. If both the assertion and reason are false.

Answer: A



Watch Video Solution

23. Assertion: Eddy current is produced in any metallic conductor when magnetic flux is changed around it.

Reason: Electric potential determines the flow of charges

A. If both the assertion and reason are true and reason is a true explanation of the assertion.

B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.

C. If the assertion is true but reason false

D. If both the assertion and reason are false.

Answer: B



Watch Video Solution

24. Assertion: Only a change in magnetic flux will maintain an induced current in the coil.

Reason: The presence of large magnetic flux through a coil maintains a current in the coil if the circuit is continuous.

A. If both the assertion and reason are true and reason is a true explanation of the assertion.

B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.

C. If the assertion is true but reason false

D. If both the assertion and reason are false.

Answer: C



Watch Video Solution

25. Assertion: In series LCR circuit resonance can take place.

Reason: Resonance takes place if inductance and capacitive reactance are equal and opposite.

A. If both the assertion and reason are true and reason is a true explanation of the assertion.

- B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.
- C. If the assertion is true but reason false
- D. If both the assertion and reason are false.

Answer: A



Watch Video Solution

26. Assertion: The alternating current lags behind the e.m.f. by a phase angle of $\pi/2$, when

AC flows through an inductor.

Reason: The inductive reactance increases as the frequency of AC source decreases.

A. If both the assertion and reason are true and reason is a true explanation of the assertion.

B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.

C. If the assertion is true but reason false

D. If both the assertion and reason are false.

Answer: C



Watch Video Solution

Section D - Chapter End Test

1. A 280 ohm electric bulb is connected to 200V electric line. The peak value of current in the bulb will be

A. About one ampere

B. Zero

C. About two ampere

D. About four ampere

Answer: A



Watch Video Solution

2. An AC source is rated at $220V, 50Hz$. The time taken for voltage to change from its peak value to zero is

A. 50 sec

B. 0.02 sec

C. 5 sec

D. 5×10^{-3} sec

Answer: D



Watch Video Solution

3. If the value of potential in an *ac*, circuit is $10V$, then the peak value of potential is

A. $\frac{10}{\sqrt{2}}$

B. $10\sqrt{2}$

C. $20\sqrt{2}$

D. $\frac{20}{\sqrt{2}}$

Answer: B



Watch Video Solution

4. The maximum value of AC voltage in a circuit is $70V$. Its $r. m. s.$ value is

A. $70.7V$

B. $100V$

C. $500V$

D. $707V$

Answer: C



Watch Video Solution

5. If instantaneous current is given by $i = 4 \cos(\omega t + \varphi)$ amperes, then the *r.m.s.* value of current is

A. 4 ampere

B. $2\sqrt{2}$ ampere

C. $4\sqrt{2}$ ampere

D. Zero ampere

Answer: B



Watch Video Solution

6. In an AC circuit, peak value of voltage is 423 volts. Its effective voltage is

- A. 400 volts
- B. 323 volts
- C. 300 volts
- D. 340 volts

Answer: C



Watch Video Solution

7. The power factor of an AC circuit having resistance (R) and inductance (L) connected in series and an angular velocity ω is

A. $R / \omega L$

B. $R / (R^2 + \omega^2 L^2)^{1/2}$

C. $\omega L / R$

D. $R / (R^2 - \omega^2 L^2)^{1/2}$

Answer: B

8. An inductor of inductance L and resistor of resistance R are joined in series and connected by a source of frequency ω . Power dissipated in the circuit is

A. $\frac{(R^2 + \omega^2 L^2)}{V}$

B. $\frac{V^2 R}{(R^2 + \omega^2 L^2)}$

C. $\frac{V}{(R^2 + \omega^2 L^2)}$

D. $\frac{\sqrt{R^2 + \omega^2 L^2}}{V^2}$

Answer: B



Watch Video Solution

9. Alternating current can not be measured by D.C.

Ammeter because

A. AC voltage pass through DC ammeter

B. Average value of complete cycle is zero

C. AC is virtual

D. AC change its direction

Answer: B



Watch Video Solution

10. In a LCR circuit capacitance is changed from C to $2C$. For the resonant frequency to remain unchanged, the inductance should be changed from L to

A. $4L$

B. $2L$

C. $L/2$

D. $L/4$

Answer: C



Watch Video Solution

11. In an LCR series a.c. Circuit the voltage across each of the components L, C and R is 50V. The voltage across the LC combination will be

A. $50V$

B. $50\sqrt{2}V$

C. $100V$


D. $0V$ (Zero)

Answer: D



Watch Video Solution

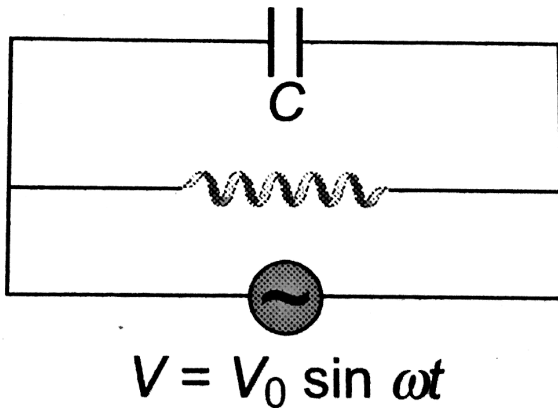12. For the circuit shown in the figure, the current through the inductor is $0.9A$ while the current through the condenser is $0.4A$. hence the current drawn from the generator is



A. $I = 1.13 \text{ amp}$

B. $I = 0.9 \text{ amp}$

C. $I = 0.5$ amp

D. $I = 0.6$ amp

Answer: C



Watch Video Solution

13. In a series LCR circuit, the voltage across the resistance, capacitance and inductance is 10 V each. If the capacitance is short circuited, the voltage across the inductance will be

A. 10V

B. $10 / \sqrt{2}V$

C. $10\sqrt{2}V$

D. $20V$

Answer: B



Watch Video Solution

14. An ideal choke takes a current of 10 A when connected to an ac supply of 125 V and 50 Hz. A pure resistor under the same conditions takes a current of 12.5 A. If the two are connected to an ac supply of 100 V and 40 Hz, then the current in

series combination of above resistor and inductor
is

- A. 10 amp
- B. 12.5 amp
- C. 20 amp
- D. 25 amp

Answer: A



Watch Video Solution

15. A direct current of 5 amp is superimposed on an alternating current $I = 10\sin\omega t$ flowing through a wire. The effective value of the resulting current will be:

A. $(15/2)$ amp

B. $5\sqrt{3}$ amp

C. $5\sqrt{5}$ amp

D. 15amp

Answer: B



Watch Video Solution

16. A group of electric lamps having a total power rating of 1000 watt is supplied by an AC voltage $E = 200 \sin(310t + 60^\circ)$. Then the r.m.s value of the circuit current is

A. 10 amp

B. $10\sqrt{2}$

C. 20 amp

D. $20\sqrt{2}$ amp

Answer: B



Watch Video Solution

17. In a LCR circuit having $L = 8.0\text{Henry}$, $C = 0.5\mu F$ and $R = 100\text{ohm}$ in series. The resonance frequency in per second is

A. 600radians

B. 600Hz

C. 500radians

D. 500Hz

Answer: C



Watch Video Solution

18. An alternating current source of frequency 100Hz is joined to a combination of a resistance, a capacitance and a coil in series. The potential difference across the coil, the resistance and the capacitor is 46, 8 and 40 volt respectively. The electromotive force of alternating current source in volt is

A. 94

B. 14

C. 10

D. 76

Answer: C



Watch Video Solution

19. A 10 ohm resistance, $5mH$ coil and $10\mu F$ capacitor are joined in series. When a suitable frequency alternating current source is joined to this combination, the circuit resonates. If the resistance is halved, the resonance frequency

A. Is halved

B. Is doubled

C. Remain unchanged

D. In quadrupled

Answer: C



Watch Video Solution

20. A resistor R , an inductor L and a capacitor C are connected in series to an oscillator of frequency n . If the resonant frequency is n_r , then the current lags behind voltage, when

A. $n = 0$

B. $n < n_r$

C. $n = n_r$

D. $n > n_r$

Answer: D



Watch Video Solution

21. If power factor is $1/2$ in a series RL circuit,

$R = 100\Omega$. AC mains is used then L is

A. $\frac{\sqrt{3}}{\pi} \text{Henry}$

B. πHenry

C. $\frac{\pi}{\sqrt{3}} \text{Henry}$

D. None of these

Answer: A



Watch Video Solution

22. A bulb is connected first with DC and the then AC of same voltage then it will shine brightly with

A. AC

B. DC

C. Brightness will be in ratio $1/1.4$

D. Equally with both

Answer: D



Watch Video Solution

23. An AC supply gives $30V_rms$ which passes through a 10Ω resistance. The power dissipated in it is

A. $90\sqrt{2}W$

B. $90W$

C. $45\sqrt{2}W$

D. $45W$

Answer: B



Watch Video Solution

24. The average power dissipation in a pure capacitance in AC circuit is

A. $\frac{1}{2}CV^2$

B. CV^2

C. $\frac{1}{4}CV^2$

D. Zero

Answer: D



Watch Video Solution

25. In a series LCR circuit, at resonance, power factor is

A. 0.707

B. 1

C. Zero

D. 0.5

Answer: B



Watch Video Solution

26. A bulb and a capacitor are in series with an AC source. On increasing frequency how will glow of the bulb change

- A. The glow decreases
- B. The glow increases
- C. The glow remain the same
- D. The bulb quench

Answer: B





27. What will be the self-inductance of a coil, to be connected in a series with a resistance of $\pi\sqrt{3}\Omega$ such that the phase difference between the e.m.f. and the current at $50Hz$ frequency is 30° ?

- A. 0.5 Henry
- B. 0.03 Henry
- C. 0.05 Henry
- D. 0.01 Henry

Answer: C



Watch Video Solution

28. The potential differences V and the current i flowing through an instrument in an AC circuit of frequency f are given by $V = 5 \cos \omega t$ and $I = 2 \sin \omega t$ amperes (where $\omega = 2\pi f$). The power dissipated in the instrument is

A. zero

B. $10W$

C. $5W$

D. $2.5W$

Answer: A



Watch Video Solution

29. Assertion: A bulb connected in series with a solenoid is connected to AC source. If a soft iron core is introduced in the solenoid, the bulb will glow brighter.

Reason: On introducing soft iron core in the solenoid, the inductance increases.

A. If both the assertion and reason are true
and reason is a true explanation of the

assertion.

- B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.
- C. If the assertion is true but reason false
- D. If assertion false but reason is true.

Answer: D



Watch Video Solution

30. Assertion: In series LCR circuit resonance can take place.

Reason: Resonance takes place if inductance and capacitive reactance are equal and opposite.

A. If both the assertion and reason are true and reason is a true explanation of the assertion.

B. If both the assertion and reason are true but the reason is not true the correct explanation of the assertion.

C. If the assertion is true but reason false

D. If assertion false but reason is true.

Answer: A



Watch Video Solution