



PHYSICS

BOOKS - IE IRODOV PHYSICS (HINGLISH)

ELECTRICITY AND MAGNETISM

Others

1. Find the electric field potential and strength at the centre of a hemisphere of radius R

ahcged uniformly with the the surface density

σ .



Watch Video Solution

2. A winch is driven by an electric motor with a separate excitation and fed from a battery of emf $E = 300V$. The rope and the hook of the winch rise at a velocity $v_1 = 4m/s$ without a load and at a velocity $v_2 = 1m/s$ with a load of mass $m = 10kg$.



Determine the velocity v' of the load and its mass m' for which the winch has the maximum power, neglecting the mass of the rope and the hook.



[Watch Video Solution](#)

3. A capacitor of unknown capacitance, a coil of inductance L , and a resistor of re-



sistance R are connected to a source of a.c. voltage $E = e_0 \cos \omega t$ (Fig. 112). The current in

the circuit is $I = (E_0 / R)\cos \omega t$.

Determine the amplitude U_0 of the voltage across the capacitor plates.



[Watch Video Solution](#)

4. Under the action of a constant voltage U , a capacitor of capacitance $C = 10^{-11} F$



included in the circuit shown in Fig. 113 is charged to $q_1 = 10^{-9} C$. The inductance of the coil, is $L = 10^{-5} H$, and the resistance of

the resistor is $R = 100\Omega$.

Determine the amplitude q_0 of steady-state oscillations of the charge on the capacitor at resonance if the amplitude of the external sinusoidal voltage is $U_0 = U$.



[Watch Video Solution](#)

5. A bank of two series-connected capacitors of capacitance C each is charged to a voltage U and is connected to a coil of inductance L so that an oscillatory circuit (Fig. 114) is formed at

the initial moment. After a time τ , a breakdown occurs in one of the capacitors, and the resistance between its plates becomes zero.

Determine the amplitude q_0 of charge oscillations on the undamaged capacitor.



[Watch Video Solution](#)

6. How can the damage due to overheating the coil of a superconducting solenoid be avoided?



Watch Video Solution