



# PHYSICS

## BOOKS - DISHA PHYSICS (HINGLISH)

### CURRENT ELECTRICITY

#### Physics

1. When 5 V potential difference is applied across a wire of length 0.1 m, the drift speed of electrons is  $2.5 \times 10^{-4} \text{ ms}^{-1}$ . If the electron

density in the wire is  $8 \times 10^{28} m^{-3}$ , the resistivity of the material is close to :

A.  $1.6 \times 10^{-6} \Omega m$

B.  $1.6 \times 10^{-5} \Omega m$

C.  $1.6 \times 10^{-8} \Omega m$


D.  $1.6 \times 10^{-7} \Omega m$

**Answer:**



**Watch Video Solution**

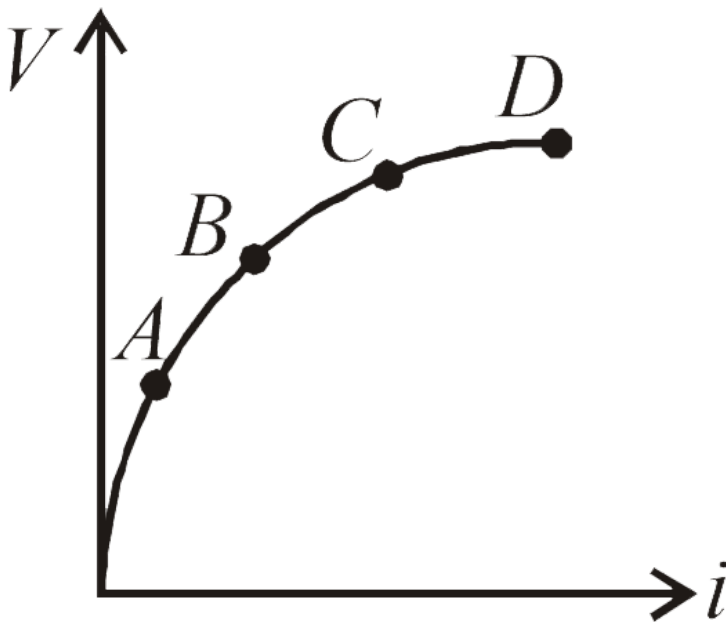2. Variation of current passing through a conductor as the voltage applied across its ends is varied as shown in the adjoining diagram. If the resistance ( $R$ ) is determined at the points A, B, C and D, we will find that



A.  $R_C = R_D$

B.  $R_B > R_A$

C.  $R_C > R_B$

D.  $R_A > R_B$

**Answer:**



**Watch Video Solution**

3. The length of a wire of a potentiometer is 100 cm, and the e.m.f. of its standard cell is E volt. It is employed to measure the e.m.f. of a



battery whose internal resistance is  $0.5\Omega$ . If the balance point is obtained at  $l = 30$  cm from the positive end, the e.m.f. of the battery is .

where  $i$  is the current in the potentiometer wire.

A.  $\frac{30E}{100.5}$

B.  $\frac{30E}{(100 - 0.5)}$

C.  $\frac{30(E - 0.5i)}{100}$

D.  $\frac{30E}{100}$

**Answer:**



4. The masses of the three wires of copper are in the ratio  $1 : 3 : 5$ . And their lengths are in the ratio  $5 : 3 : 1$ . the ratio of their electrical resistance is

A.  $1 : 3 : 5$

B.  $5 : 3 : 1$

C.  $1 : 25 : 125$

D.  $125 : 15 : 1$

**Answer:**



**Watch Video Solution**

5.  $n$  equal resistors are first connected in series and then connected in parallel. What is the ratio of the maximum to the minimum resistance ?

A.  $n$

B.  $1/n^2$

C.  $n^2$

D.  $1/n$

**Answer:**



**Watch Video Solution**

6. A battery is charged at a potential of  $15V$  for 8 hours when the current flowing is  $10A$ . The battery on discharge supplies a current of  $5A$  for 15 hours. The terminal voltage during discharge is  $14V$ . The 'Watt-hour' efficiency of the battery is.

A. 80.5 %

B. 82.5 %

C. 80 %


D. 90 %

**Answer:**



**Watch Video Solution**

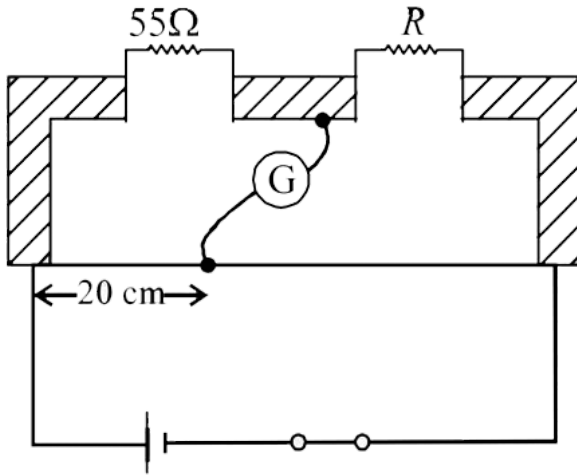7. Shown in the figure below is a meter- bridge set up will null deflection in the galvanometer.



The value of the unknown resistor  $R$  is

- A.  $13.75\Omega$
- B.  $220\Omega$
- C.  $110\Omega$
- D.  $55\Omega$

**Answer:**



Watch Video Solution

8. In the equation  $AB = C$ , A is the current density, C is the electric field, Then B is

A. resistivity

B. conductivity

C. potential difference

D. resistance

**Answer:**



Watch Video Solution

9. The Kirchhoff's first law ( $\sum i = 0$ ) and second law ( $\sum iR = \sum E$ ), where the symbols have their usual meanings, are respectively based on

A. conservation of charge, conservation of momentum

B. conservation of energy, conservation of charge



C. conservation of momentum,

conservation of charge

D. conservation of charge, conservation of

energy

**Answer:**



**Watch Video Solution**

**10.** You are given a resistance coil and a battery. In which of the following cases is largest amount of heat generated?

A. When the coil is connected to the battery directly

B. When the coil is divided into two equal parts and both the parts are connected to the battery in parallel

C. When the coil is divided into four equal parts and all the four parts are connected to the battery in parallel

D. When only half the coil is connected to the battery

**Answer:**



**Watch Video Solution**

**11.** The resistance of the coil of an ammeter is  $R$ . The shunt required to increase its range  $n - fold$  should have a resistance.

A.  $\frac{R}{n}$

B.  $\frac{R}{n - 1}$

C.  $\frac{R}{n + 1}$

D.  $nR$

**Answer:**



**Watch Video Solution**

**12.** On increasing the temperature of a conductor, its resistance increases because

- A. relaxation time increases
- B. mass of electron increases
- C. electron density decreases
- D. relaxation time decreases

**Answer:**



**Watch Video Solution**

**13.** An electric current is passed through a circuit containing two wires of the same material, connected in parallel. If the lengths and radii are in the ratio of  $4/3$  and  $2/3$ , then the ratio of the current passing through the wires will be

A.  $8/9$

B.  $1/3$

C. 3

D. 2

**Answer:**



**Watch Video Solution**

**14.** In a meter bridge experiment, null point is obtained at  $20\text{cm}$  from one end of the wire when resistance  $X$  is balanced against another resistance  $Y$ . If  $X < Y$ , then the new

position of the null point from the same end,  
if one decides to balance a resistance of  $4X$   
against  $Y$  will be at.

A. 40 cm

B. 80cm

C. 50 cm

D. 70 cm


**Answer:**



**Watch Video Solution**

15. In the circuit shown, the current through 8 ohm is same before and after connecting E.

The value of E is

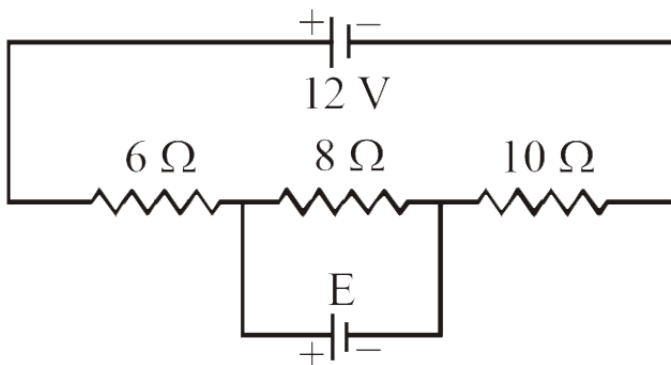

A. 12V

B. 6V

C. 4V

D. 2V




**Answer:**



**Watch Video Solution**

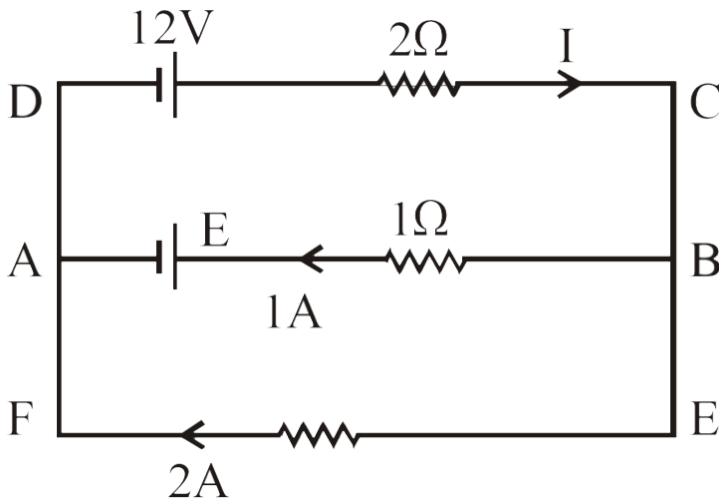**16.** Find emf  $E$  of the cell as shown in figure.



**A.  $15\text{ V}$**

B. 10 V

C. 12 V

D. 5 V


**Answer:**



**Watch Video Solution**

17. A torch bulb rated  $4.5W, 1.5V$  is connected as shown in Fig. 7.35. The emf of the cell needed to make the bulb glow at full

intensity is

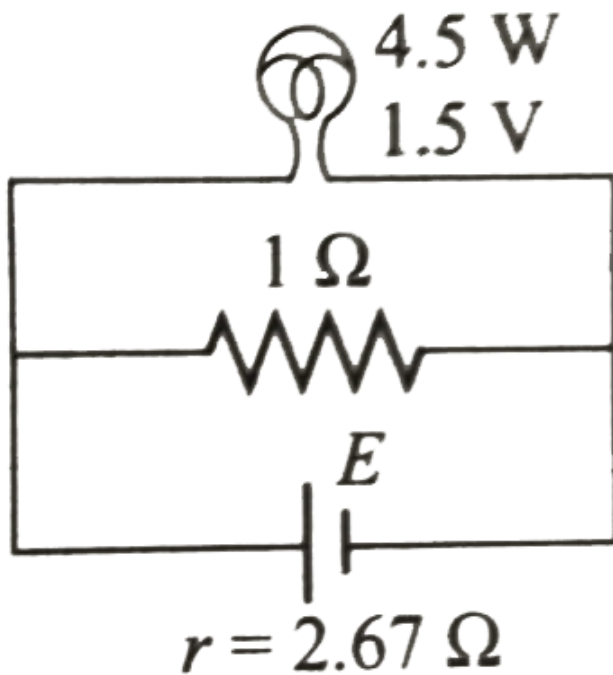


- A.  $4.5\text{ V}$
- B.  $1.5\text{ V}$
- C.  $2.67\text{ V}$
- D.  $13.5\text{ V}$

**Answer:**



**Watch Video Solution**

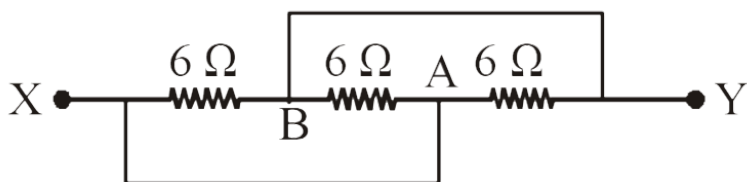**18.** In a given network, each resistance has value of  $6\Omega$ . The point X is connected to point A by a copper wire of negligible resistance and point Y is connected to point B by the same wire. The effective resistance between X and Y will be



A.  $18\Omega$

B.  $6\Omega$

C.  $3\Omega$

D.  $2\Omega$

**Answer:**



**Watch Video Solution**

**19.** If  $n$ ,  $e$ ,  $\tau$ ,  $m$ , are representing electron density charge, relaxation time and mass of an electron respectively then the resistance of

wire of length  $l$  and cross sectional area  $A$  is given by

A.  $\frac{2ml}{Ne^2 A \tau}$

B.  $\frac{2m\tau A}{Ne^2 l}$

C.  $\frac{Ne^2 \tau A}{2ml}$




D.  $\frac{Ne^2 A}{2m\tau l}$

**Answer:**




**Watch Video Solution**

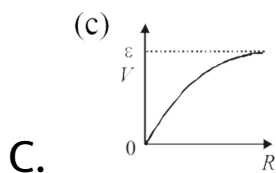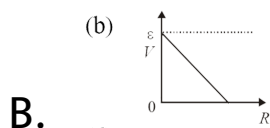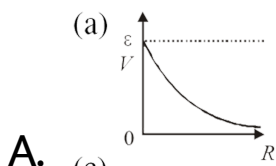20. A cell having an emf  $\varepsilon$  and internal resistance  $r$  is connected across a variable external resistance  $R$ . As the resistance  $R$  is increased, the plot of potential difference  $V$  across  $R$  is given by



(d)

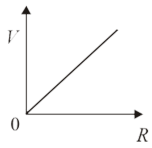

D.

**Answer:**



**Watch Video Solution**

21. If voltage across a bulb rated 220 volt-100 watt drops by 2.5 % of its value, the percentage of the rated value by which the power would decrease is

A. 20 %



B. 2.5 %

C. 5 %

D. 10 %

**Answer:**



**Watch Video Solution**

22. If specific resistance of a potentiometer wire is  $10^{-7} \Omega m$ , the current flow through it is  $0.1A$  and the cross-sectional area of wire is  $10^{-6} m^2$  then potential gradient will be

A.  $10^{-2} \text{ volt} / m$

B.  $10^{-4} \text{ volt} / m$

C.  $10^{-6} \text{ volt} / m$

D.  $10^{-8} \text{ volt} / m$

**Answer:**



**Watch Video Solution**

**23.** Two resistance  $R_1$  and  $R_2$  are made of different material. The temperature coefficient of the material of  $R_1$  is  $\alpha$  and of the material

of  $R_2$  is  $-\beta$ . Then resistance of the series combination of  $R_1$  and  $R_2$  will not change with temperature, if  $R_1 / R_2$  will not change with temperature if  $R_1 / R_2$  equals

A.  $\frac{\alpha}{\beta}$

B.  $\frac{\alpha + \beta}{\alpha - \beta}$

C.  $\frac{\alpha^2 + \beta^2}{2\alpha\beta}$

D.  $\frac{\beta}{\alpha}$

**Answer:**



**Watch Video Solution**

**24.** Five cells each of emf  $E$  and internal resistance  $r$  send the same amount of current through an external resistance  $R$  whether the cells are connected in parallel or in series.

Then the ratio  $\left(\frac{R}{r}\right)$  is

A. 2

B.  $\frac{1}{2}$

C.  $\frac{1}{5}$

D. 1

**Answer:**



**Watch Video Solution**

**25.** The length of a given cylindrical wire is increased by  $100\%$ . Due to the consequent decrease in diameter the change in the resistance of the wire will be

A.  $200\%$

B.  $100\%$

C.  $50\%$

D. 300 %

**Answer:**



**Watch Video Solution**

**26.** Potentiometer wire of length  $1m$  is connected in series with  $490\Omega$  resistance and  $2V$  battery. If  $0.2m\frac{V}{c}m$  is the potential gradient, then resistance of the potentiometer wire is approximately

A.  $4.9\Omega$

B.  $7.9\Omega$

C.  $5.9\Omega$

D.  $6.9\Omega$


**Answer:**



**Watch Video Solution**

**27.** See the electrical circuit shown in this figure. Which of the following equations is the

correct equation for it ?

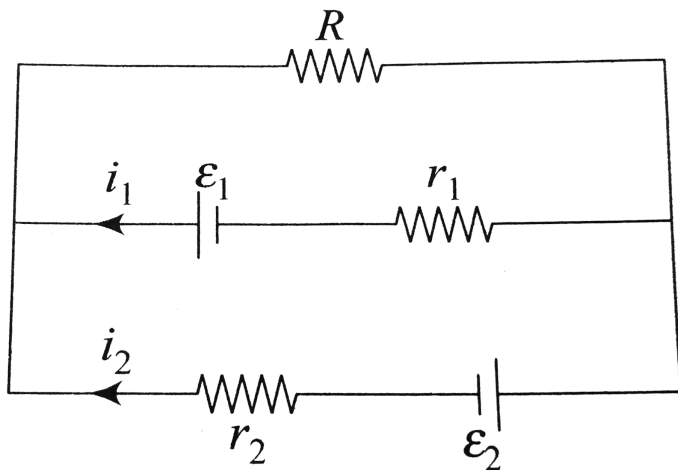

A.  $\epsilon_2 - i_2 r_2 - \epsilon_1 - i_1 r_1 = 0$

B.  $-\epsilon_2 - (i_1 + i_2)R + i_2 r_2 = 0$

C.  $\epsilon_1 - (i_1 + i_2)R + i_i r_2 = 0$

D.  $\epsilon_1 - (i_1 + i_2)R - i_i r_2 = 0$

**Answer:**





Watch Video Solution

**28.** In a large building, there are 15 bulbs of 40 W, 5 bulbs of 100 W, 5 fans of 80 W and 1 heater of 1 kW. The voltage of electric mains is 220 V. The minimum capacity for the main fuse of the building will be :

A. 8A

B. 10A

C. 12A

D. 14A

**Answer:**



**Watch Video Solution**

**29.** Two sources of equal emf are connected to an external resistance  $R$ . The internal resistance of the two sources are  $R_1$  and  $R_2$  ( $R_1 > R_2$ ). If the potential difference across the source having internal resistance  $R_2$  is zero, then

A.  $R = R_2 - R_1$

B.  $R = R_2 \times (R_1 + R_2) / (R_2 - R_1)$

C.  $R = R_1 R_2 / (R_2 - R_1)$

D.  $R = R_1 R_2 / (R_1 - R_2)$

**Answer:**



**Watch Video Solution**

**30.** The resistance of the series combination of two resistances is  $S$ . When they are joined in

parallel the total resistance is  $P$ . If  $S = nP$  then the minimum possible value of  $n$  is

A. 2

B. 3

C. 4

D. 1

**Answer:**



**Watch Video Solution**

**31.** If an ammeter is to be used in place of a voltmeter, then we must connect with the ammeter a

- A. low resistance in parallel
- B. high resistance in parallel
- C. high resistance in series
- D. low resistance in series.

**Answer:**



**Watch Video Solution**

**32.** A d.c. main supply of e.m.f.  $220V$  is connected across a storage battery of e.m.f.  $200V$  through a resistance of  $1\Omega$ . The battery terminals are connected to an external resistance 'R'. The minimum value of 'R', so that a current passes through the battery to charge it is:

A.  $7\Omega$

B.  $9\Omega$

C.  $11\Omega$

D. zero


**Answer:**



**Watch Video Solution**

**33.** In the given circuit diagram when the current reaches steady state in the circuit, the charge on the capacitor of capacitance  $C$  will

be

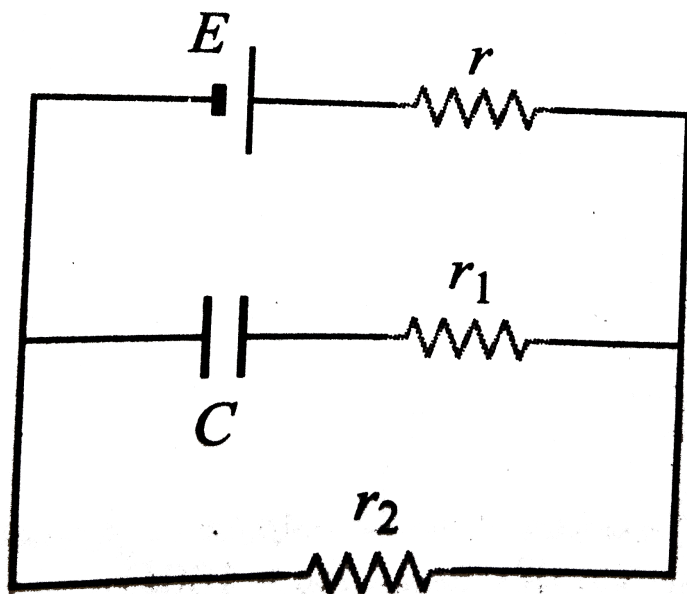

A.  $CE \frac{r_2}{(r + r_2)}$

B.  $CE \frac{r_1}{(r_1 + r)}$

C.  $CE \frac{r_2}{(r + r_1)}$

D.  $CE \frac{r_1}{(r_2 + r)}$







**Answer:**



**Watch Video Solution**

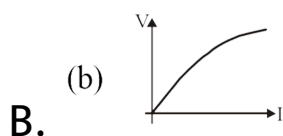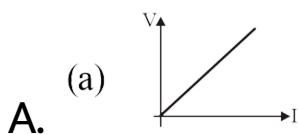**34.** Suppose the drift velocity  $v_d$  in a material varied with the applied electric field  $E$  as  $v_d \propto \sqrt{E}$ . Then  $V - I$  graph for a wire made of such a material is best given by :



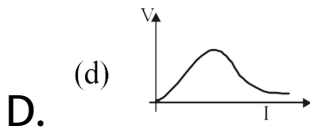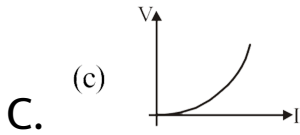

**Answer:**



**Watch Video Solution**

**35.** In a neon discharge tube  $2.9 \times 10^{18} Ne^+$  ions move to the right each second while  $1.2 \times 10^{18}$  electrons move to the left per

second. Electron charge is  $1.6 \times 10^{-19} C$ . The current in the discharge tube

A. 0.27 A to the right

B. 0.66 A to the right

C. 0.66 A to the left


D. zero

**Answer:**



**Watch Video Solution**

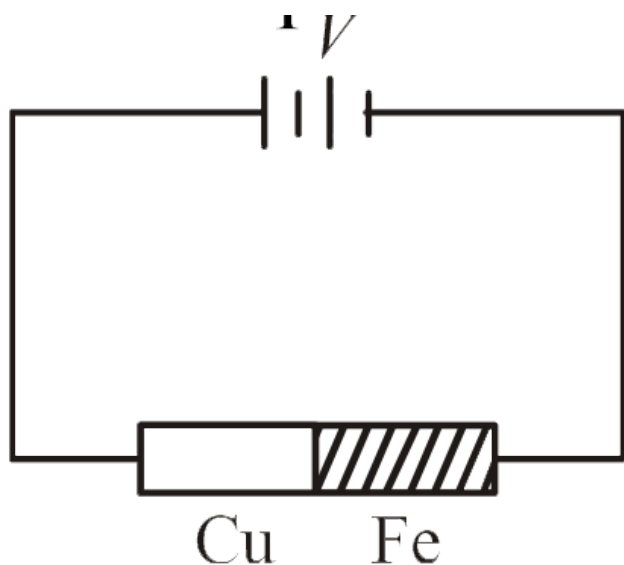**36.** Two rods are joined end to end, as shown. Both have a cross-sectional area of  $0.01\text{cm}^2$ . Each is 1 meter long. One rod is of copper with a resistivity of  $1.7 \times 10^{-6}$  ohm-centimeter, the other is of iron with a resistivity of  $10^{-5}$  ohm-centimeter. How much voltage is required to produce a current of 1 ampere in the rods?



A.  $0.117V$

B.  $0.00145V$

C.  $0.0145V$

D.  $1.7 \times 10^{-6}V$

**Answer:**



**Watch Video Solution**

**37.** An energy source will supply a constant current into the load if its internal resistance is

- A. very large as compared to the load resistance
- B. equal to the resistance of the load
- C. non-zero but less than the resistance of the load
- D. zero

**Answer:**



**Watch Video Solution**

**38.** The resistance of a wire at room temperature  $30^{\circ}C$  is found to be  $10\Omega$ . Now to increase the resistance by  $10\%$ , the temperature of the wire must be [ The temperature coefficient of resistance of the material of the wire is  $0.002 \text{ per } ^{\circ}C$ ]

A.  $36^{\circ}C$

B.  $83^{\circ}C$

C.  $63^{\circ}C$

D.  $33^{\circ}C$

**Answer:**



**Watch Video Solution**

**39.** If the current in the electric bulb changes by 1%, then by what percentage will the power change?

A. 10 %

B. 2 %

C. 1 %

D. 100 %




**Answer:**



**Watch Video Solution**

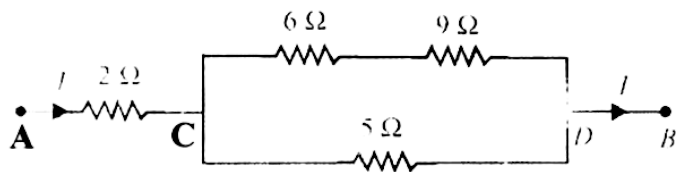**40.** In the circuit shown in figure, the  $5\Omega$  resistance develops  $20.00\text{ cal/s}$  due to the current flowing through it. The heat developed in  $2\Omega$  resistance (in  $\text{cal/s}$ ) is



**A. 23.8**

B. 14.2

C. 11.9

D. 7.1

**Answer:**



**Watch Video Solution**

**41.** In a Wheatstone's bridge, three resistances P, Q and R connected in the three arms and the fourth arm is formed by two resistances

$S_1$  and  $S_2$  connected in parallel. The condition for the bridge to be balanced will be

A.  $\frac{P}{Q} = \frac{2R}{S_1 + S_2}$

B.  $\frac{P}{Q} = \frac{R(S_1 + S_2)}{S_1 S_2}$

C.  $\frac{P}{Q} = \frac{R(S_1 + S_2)}{2S_1 S_2}$

D.  $\frac{P}{Q} = \frac{R}{S_1 + S_2}$

**Answer:**



**Watch Video Solution**

**42.** The electric resistance of a certain wire of iron is  $R$ . If its length and radius are both doubled, then

A. the resistance and the specific resistance, will both remain unchanged

B. the resistance will be doubled and the specific resistance will be halved

C. the resistance will be halved and the specific resistance will remain unchanged

D. the resistance will be halved and the specific resistance will be doubled

**Answer:**



**Watch Video Solution**

**43.** A car has a fresh storage battery of emf 12 V and internal resistance  $5.0 \times 10^{-2} \Omega$ . If the starter motor draws a current of 90A, what is the terminal voltage of the battery when the starter is on?

A. 15 volt

B. 3 volt

C. 5 volt

D. 9 volt

**Answer:**



**Watch Video Solution**

**44.** A conducting wire of cross-sectional area  $1\text{cm}^2$  has  $3 \times 10^{23}$  charge carriers per  $\text{m}^3$ . If

wire carries a current of  $24mA$ , then drift velocity of carriers is

A.  $5 \times 10^{-2} m/s$

B.  $0.5 m/s$

C.  $5 \times 10^{-3} m/s$

D.  $5 \times 10^{-6} m/s$

**Answer:**



**Watch Video Solution**

**45.** In the series combination of  $n$  cells each cell having emf  $\varepsilon$  and internal resistance  $r$ . If three cells are wrongly connected, then total emf and internal resistance of this combination will be

A.  $n\varepsilon, (nr - 3r)$

B.  $(n\varepsilon - 2\varepsilon)nr$

C.  $(n\varepsilon - 4\varepsilon), nr$

D.  $(n\varepsilon - 6\varepsilon), nr$

**Answer:**





**Watch Video Solution**