



PHYSICS

BOOKS - UNIVERSAL BOOK DEPOT 1960

PHYSICS (HINGLISH)

ALTERNATING CURRENT

Exercise

1. The power is transmitted from a power house on a voltage AC because

A. Electric current travels faster at higher volts

B. It is more economical due to less power wastage

C. It is difficult to generate power at low voltage

D. Chances of stealing transmission lines are minimized

Answer: B



[Watch Video Solution](#)

2. The potential differences V and the current i flowing through an instrument in an AC circuit of frequency f are given by $V = 5 \cos \omega t$ and $I = 2 \sin \omega t$ amperes (where $\omega = 2\pi f$). The power dissipated in the instrument is

A. Zero

B. 10 W

C. 5 W

D. 2.5 W

Answer: A



Watch Video Solution

3. In an AC circuit, V and I are given by

$$V = 100 \sin(100t) \text{ volts}, I = 100 \sin\left(100t + \frac{\pi}{3}\right) \text{ mA}.$$

The power dissipated in circuit is

A. 10^4 watt

B. 10 watt

C. 2.5 watt

D. 5 watt

Answer: C



Watch Video Solution

4. Alternating current can not be measured by D.C.

Ammeter because

A. ac cannot pass through dc ammeter

B. Average value of complete cycle is zero

C. ac is virtual

D. ac changes its direction

Answer: B



Watch Video Solution

5. The resistance of a coil for DC is in ohms. In AC, the resistance

A. Will remain same

B. Will increase

C. Will decrease

D. Will be zero

Answer: b



Watch Video Solution

6. If instantaneous current is given by $i = 4 \cos(\omega t + \varphi)$

amperes, then the *r. m. s.* value of current is

A. 4 amperes

B. $2\sqrt{2}$ amperes

C. $4\sqrt{2}$ amperes

D. Zero amperes

Answer: B



Watch Video Solution

7. In an AC circuit, peak value of voltage is 423 volts. Its effective voltage is

A. 400 volts

B. 323 volts

C. 300 volts

D. 340 volts

Answer: c



Watch Video Solution

8. In an ac circuit $I = 100 \sin 200\pi t$. The time required for the current to achieve its peak value will be

A. $\frac{1}{100}$ sec

B. $\frac{1}{200}$ sec

C. $\frac{1}{300}$ sec

D. $\frac{1}{400}$ sec

Answer: D



Watch Video Solution

9. The peak value of Alternating current is 6amp, then r.m.s. value of current will be

A. $3A$

B. $3\sqrt{3}A$

C. $3\sqrt{2}A$

D. $2\sqrt{3}A$

Answer: C



Watch Video Solution

10. A generator produces a time varying voltage given by

$V = 240 \sin 120t$, where t is in second. The rms voltage

and frequency are

A. 60 Hz and 240 V

B. 19 Hz and 120 V

C. 19 Hz and 170 V

D. 754 Hz and 70 V

Answer: C



Watch Video Solution

11. If E_0 represents the peak value of the voltage in an ac circuit, the r.m.s. value of the voltage will be

A. $\frac{E_0}{\pi}$

B. $\frac{E_0}{2}$

C. $\frac{E_0}{\sqrt{\pi}}$

D. $\frac{E_0}{\sqrt{2}}$

Answer: D



[Watch Video Solution](#)

12. The peak value of AC mains (in volt) is

- A. 155.6 volts
- B. 220.0 volts
- C. 311.0 volts
- D. 440 volts

Answer: c



[Watch Video Solution](#)

13. A sinusoidal ac current flows through a resistor of resistance R . If the peak current is I_p , then the power dissipated is

A. $I_p^2 R \cos \theta$

B. $\frac{1}{2} I_p^2 R$

C. $\frac{4}{\pi} I_p^2 R$

D. $\frac{1}{\pi} I_p^2 R$

Answer: B



Watch Video Solution

14. A 40Ω electric heater is connected to a 200 V , 50 Hz mains supply. The peak value of electric current flowing in the circuit is approximately

A. 2.5 A

B. 5.0 A

C. 7A

D. 10A

Answer: c



Watch Video Solution

15. The frequency of ac mains in India is

A. 30 c/s or Hz

B. 50 c/s or Hz

C. 60 c/s or Hz

D. 120 c/s or Hz

Answer: b



Watch Video Solution

16. The r.m.s value of an a.c of 59Hz is 10A . The time taken by the alternating current in reaching from zero to maximum value and the peak value of current will be

A. 2×10^{-2} sec and 14.14 amp

B. 1×10^{-2} sec and 7.07 amp

C. 5×10^{-3} sec and 7.07 amp

D. 5×10^{-3} sec and 14.14 amp

Answer: D



Watch Video Solution

17. The root mean square value of the alternating current is equal to

A. Twice the peak value

B. Half the peak value

C. $\frac{1}{\sqrt{2}}$ times the peak value

D. Equal to the peak value

Answer: C



Watch Video Solution

18. The peak value of an alternating emf E given by

$$E = (E_0)\cos \omega t$$

is 10V and frequency is 50 Hz. At time $t = (1/600)s$ the instantaneous value of emf is

A. 10 V

B. $5\sqrt{3}V$

C. 5 V

D. 1 V

Answer: B



Watch Video Solution

19. In an AC circuit the voltage applied is $E = E_0 \sin \omega t$.

The resulting current in the circuit is

$I = I_0 \sin\left(\omega t - \frac{\pi}{2}\right)$. The power consumption in the

circuit is given by

A. $P = \frac{E_0 I_0}{\sqrt{2}}$

B. $P = \sqrt{2} E_0 I_0$

C. $P = \frac{E_0 I_0}{2}$

D. $P = 0$

Answer: D



Watch Video Solution

20. In an AC circuit, the instantaneous values of e.m.f and current are $e = 200 \sin 314t$ volt and $i = \sin\left(314t + \frac{\pi}{3}\right)$ ampere. The average power consumed in watt is

A. 200

B. 100

C. 50

D. 25

Answer: C



Watch Video Solution

21. An AC generator produced an output voltage $E = 170 \sin 377t$ volts , where t is in seconds. The frequency of AC voltage is

A. 50 Hz

B. 110 Hz

C. 60 Hz

D. 230 Hz

Answer: C



Watch Video Solution

22. In general in an alternating current circuit

- A. The average value of current is zero
- B. The average value of square of the current is zero
- C. Average power dissipation is zero
- D. The phase difference between voltage and current
is zero

Answer: A



Watch Video Solution

23. An AC is given by the equation

$i = i_1 \cos \omega t + i_2 \sin \omega t$. The r.m.s. current is given by

A. $\frac{1}{\sqrt{2}}(i_1 + i_2)$

B. $\frac{1}{\sqrt{2}}(i_1 + i_2)^2$

C. $\frac{1}{\sqrt{2}}(i_1^2 + i_2^2)^{1/2}$

D. $\frac{1}{2}(i_1^2 + i_2^2)^{1/2}$

Answer: C



Watch Video Solution

24. In an AC circuit, the current is given by $i = 5 \sin\left(100t - \frac{\pi}{2}\right)$ and the AC potential is $V = 200 \sin(100t)$ volt. Then the power consumption is

- A. 20 watt
- B. 40 watt
- C. 1000 watt
- D. 0 watt

Answer: D



Watch Video Solution

25. An electron lamp is connected to $220V, 50Hz$ supply.

Then the peak value of voltage is

A. 210 V

B. 211 V

C. 311 V

D. 320 V

Answer: C



Watch Video Solution

26. In a circuit, the value of the alternating current is measured by hot wire ammeter as 10 ammeter. Its peak

value will be

A. $10A$

B. $20 A$

C. $14.14 A$

D. $7.07 A$

Answer: c



Watch Video Solution

27. The voltage of domestic ac is 220 volt . What does this represent

A. Mean voltage

B. Peak voltage

C. Root mean voltage

D. Root mean square voltage

Answer: d



Watch Video Solution

28. The r.m.s. voltage of domestic electricity supply is 220 volt. Electrical appliances should be designed to withstand an instantaneous voltage of

A. 220 V

B. 310 V

C. 330 V

D. 440 V

Answer: b



Watch Video Solution

29. The process of converting alternating current into direct current is known as

A. Purification

B. Amplification

C. Rectification

D. Current amplification

Answer: c



Watch Video Solution

30. In an AC circuit with voltage V and current I , the power dissipated is

A. VI

B. $\frac{1}{2}VI$

C. $\frac{1}{\sqrt{2}}VI$

D. Depends on the phase between V and I

Answer: d



Watch Video Solution

31. For an ac circuit $V = 15 \sin \omega t$ and $I = 20 \cos \omega t$ the average power consumed in this circuit is

A. 300 watt

B. 150 watt

C. 75 watt

D. zero

Answer: D



[Watch Video Solution](#)

32. A bulb is connected first with DC and then AC of same voltage then it will shine brightly with

A. AC

B. DC

C. Brightness will be in ratio 1/1.4

D. Equally with both

Answer: D



[Watch Video Solution](#)

33. An AC supply gives $30V_{rms}$ which passes through a 10Ω resistance. The power dissipated in it is

A. $90\sqrt{2}W$

B. $90W$

C. $45\sqrt{2}W$

D. $45W$

Answer: B



Watch Video Solution

34. The frequency of an alternating voltage is 50 cycles/sec and its amplitude is $120V$. Then the r.m.s value of voltage is

A. $101.3 V$

B. 84.8 V

C. 70.7 V

D. 56.5 V

Answer: b



Watch Video Solution

35. A resistance of 20Ω is connected to a source of an alternating potential $V = 220 \sin(100\pi t)$. The time taken by the current to change from the peak value to rms value is

A. 0.2 sec

B. 0.25 sec

C. 25×10^{-3} sec

D. 2.5×10^{-3} sec

Answer: d



Watch Video Solution

36. Voltage and current in an ac circuit are given by

$$V = 5 \sin\left(100\pi t - \frac{\pi}{6}\right) \text{ and } I = 4 \sin\left(100\pi t + \frac{\pi}{6}\right)$$

A. Voltage leads the current by 30°

B. Current leads the voltage by 30°

C. Current leads the voltage by 60°

D. Voltage leads the current by 60°

Answer: C



Watch Video Solution

37. If an AC main supply is given to be $220V$. What would be the average e.m.f during a positive half cycle?

A. 198 V

B. 386 V

C. 256 V

D. None of these

Answer: a



Watch Video Solution

38. In an AC circuit, the mass value of the current I_{rms} is related to the peak current I_0 as

A. $I_{\text{rms}} = \frac{1}{\pi} I_0$

B. $I_{\text{rms}} = \frac{1}{\sqrt{2}} I_0$

C. $I_{\text{rms}} = \sqrt{2} I_0$

D. $I_{\text{rms}} = \pi I_0$

Answer: b



Watch Video Solution

39. An alternating voltage is represented as $E = 20 \sin 300t$. The average value of voltage over one cycle will be

A. Zero

B. 10 volts

C. $20\sqrt{2}$ volt

D. $\frac{20}{\sqrt{2}}$ volt

Answer: a



Watch Video Solution

40. The ratio of peak value and r.m.s value of an alternating current is

A. 1

B. $\frac{1}{2}$

C. $\sqrt{2}$

D. $1/\sqrt{2}$

Answer: C



Watch Video Solution

41. A 280 ohm electric bulb is connected to 200V electric line. The peak value of current in the bulb will be

A. About one ampere

B. Zero

C. About two ampere

D. About four ampere

Answer: a



Watch Video Solution

42. An AC source is rated at $220V, 50Hz$. The time taken for voltage to change from its peak value to zero is

A. 50 sec

B. 0.02 sec

C. 5 sec

D. 5×10^{-3} sec

Answer: d



Watch Video Solution

43. If the value of potential in an *ac*, circuit is $10V$, then the peak value of potential is

A. $\frac{10}{\sqrt{2}}$

B. $10\sqrt{2}$

C. $20\sqrt{20}$

D. $\frac{20}{\sqrt{2}}$

Answer: b



Watch Video Solution

44. A lamp consumes only 50 % of peak power in an *a. c.* circuit. What is the phase difference between the applied voltage and the circuit current

A. $\frac{\pi}{6}$

B. $\frac{\pi}{3}$

C. $\frac{\pi}{4}$

D. $\frac{\pi}{2}$

Answer: b



Watch Video Solution

45. If an alternating voltage is represented as

$E = 141 \sin(628t)$, then the rms value of the voltage

and the frequency are respectively

A. 141V, 628 Hz

B. 100V, 50 Hz

C. 100 V, 100 Hz

D. 141 V, 100 Hz

Answer: C



[Watch Video Solution](#)

46. The maximum value of a.c. voltage in a circuit is 707 V . Its rms value is

A. 70.7 V

B. 100 V

C. 500 V

D. 707 V

Answer: C



[Watch Video Solution](#)

47. Choke coil works on the principle of

- A. Transient current
- B. Self induction
- C. Mutual induction
- D. Wattless current

Answer: B



[Watch Video Solution](#)

48. A choke coil has.

- A. High inductance and low resistance

B. Low inductance and high resistance

C. High inductance and high resistance

D. Low inductance and low resistance

Answer: a



Watch Video Solution

49. Choke coil is used to control

A. ac

B. dc

C. Both ac and dc

D. Neither ac nor dc

Answer: a



Watch Video Solution

50. Current in the circuit is wattless, if

- A. Inductance in the circuit is zero
- B. Resistance in the circuit is zero
- C. Current is alternating
- D. Resistance and inductance both are zero

Answer: B



Watch Video Solution

51. The phase angle between e.m.f. and current in LCR series ac circuit is

A. 0 to $\pi/2$

B. $\pi/4$

C. $\pi/2$

D. π

Answer: A



Watch Video Solution

52. A choke coil is preferred to a rheostate in AC circuit as

A. It consumes almost zero power

B. It increases current

C. It increases power

D. It increases voltage

Answer: a



Watch Video Solution

53. An alternating e.m.f. is applied to purely capacitive circuit. The phase relation between e.m.f. and current flowing in the circuit is or in a circuit containing capacitance only

A. e.m.f. is ahead of current by $\pi / 2$

B. Current is ahead of e.m.f. by $\pi / 2$

C. Current lags behind e.m.f. by π

D. Current is ahead of e.m.f. by π

Answer: B



Watch Video Solution

54. An ac source is connected to a resistive circuits.

Which of the following statements are false ?

A. Current leads the voltage and both are in same phase

B. Current lags behind the voltage and both are in same phase

C. Current and voltage are in same phase

D. Any of the above may be true depending upon the value of resistance

Answer: c



Watch Video Solution

55. Average energy stored in a pure inductance L when current i flows through it, is

A. $\frac{1}{2}LI^2$

B. $\frac{1}{4}LI^2$

C. $2Li^2$

D. Zero

Answer: d



Watch Video Solution

56. An alternating current of frequency ' f ' is flowing in a circuit containing a resistance R and a choke L in series. The impedance of this circuit is

A. $R + 2\pi fL$

B. $\sqrt{R^2 + 4\pi^2 f^2 L^2}$

C. $\sqrt{R^2 + L^2}$

D. $\frac{10}{2\pi} Hz$

Answer: b



Watch Video Solution

57. A resonant AC circuit contains a capacitor of capacitance $10^{-6}F$ and an inductor of $10^{-4}H$. The frequency of electrical oscillation will be

A. $10^5 Hz$

B. $10 Hz$

C. $\frac{10^5}{2\pi} Hz$

D. $\frac{10}{2\pi} Hz$

Answer: C



Watch Video Solution

58. Power delivered by an ac source of angular frequency ω_0 to an LCR series circuit is maximum when .

A. $\omega L = \omega C$

B. $\omega L = \frac{1}{\omega C}$

C. $\omega L = - \left(\frac{1}{\omega C} \right)^2$

D. $\omega L = \sqrt{\omega C}$

Answer: B



Watch Video Solution

59. An alternating voltage is connected in series with a resistance R and inductance L if the potential drop across the resistance is $200V$ and across the inductance is $150V$, then the applied voltage is

A. 350 V

B. 250 V

C. 500 V

D. 300 V

Answer: b



Watch Video Solution

60. An inductive circuit a resistance of 10ohm and an inductance of 2.0 henry. If an AC voltage of 120volt and frequency of 60Hz is applied to this circuit, the current in the circuit would be nearly

- A. 0.32 amp
- B. 0.016 amp
- C. 0.48 amp
- D. 0.80 amp

Answer: b



Watch Video Solution

61. Same current is flowing in two alternating circuits. The first circuit contains only inductances and the other contains only a capacitor, if the frequency of the e.m.f of AC is increased, the effect on the value of the current will be

- A. Increases in the first circuit and decreases in the other
- B. Increases in both the circuits
- C. Decreases in both the circuits
- D. Decreases in the first circuit and increases in the other

Answer: D



[Watch Video Solution](#)

62. A capacitor becomes a perfect insulator for

- A. Alternating currents
- B. Direct currents
- C. Both ac and dc
- D. None of these

Answer: b



[Watch Video Solution](#)

63. In a circuit containing an inductance of zero resistances, the e.m.f of the applied AC voltage leads the current by

A. 90°

B. 45°

C. 30°

D. 0°

Answer: a



Watch Video Solution

64. In a pure inductive circuit or In an ac circuit containing inductance only, the current

- A. Leads the e.m.f. by 90°
- B. Lags behind the e.m.f. by 90°
- C. Sometimes leads and sometime lags behind the e.m.f.
- D. Is in phase with the e.m.f.

Answer: B



Watch Video Solution

65. A 20volts AC is applied to a circuit consisting of a resistance and a coil with negligible resistance. If the voltage across the resistance is $12V$, the voltage across the coil is

A. 16 volts

B. 10 volts

C. 8 volts

D. 6 volts

Answer: a



Watch Video Solution

66. A resistance of 300Ω and an inductance of $\frac{1}{\pi}$ henry are connected in series to an AC voltage of 20volts and $200Hz$ frequency. The phase angle between the voltage and current is

A. $\tan^{-1} \frac{4}{3}$

B. $\tan^{-1} \frac{3}{4}$

C. $\tan^{-1} \frac{3}{2}$

D. $\tan^{-1} \frac{2}{5}$

Answer: a



Watch Video Solution

67. The power factor of LCR circuit at resonance is-

A. 0.707

B. 1

C. Zero

D. 0.5

Answer: B



[Watch Video Solution](#)

68. An inductance of 1 mH a condenser of $10\mu F$ and a resistance of 50Ω are connected in series. The

reactances of inductor and condensers are same. The reactance of either of them will be

A. 100Ω

B. 30Ω

C. 3.2Ω

D. 10Ω

Answer: d



Watch Video Solution

69. The natural frequency of a L - C circuit is equal to

A. $\frac{1}{2\pi} \sqrt{LC}$

B. $\frac{1}{2\pi\sqrt{LC}}$

C. $\frac{1}{2\pi}\sqrt{\frac{L}{C}}$

D. $\frac{1}{2\pi}\sqrt{\frac{C}{L}}$

Answer: b



Watch Video Solution

70. An alternating voltage $E = 200\sqrt{2}\sin(100t)$ is connected to a 1 microfarad capacitor through an AC ammeter. The reading of the ammeter shall be

A. 10 mA

B. 20 mA

C. 40 mA

D. 80 mA

Answer: b

 [Watch Video Solution](#)

71. An AC circuit consists of an inductor of inductance $0.5H$ and a capacitor of capacitance $8\mu F$ in series. The current in the circuit is maximum when the angular frequency of AC source is

A. 500 rad/sec

B. 2×10 rad/sec

C. 4000 rad/sec

D. 5000 rad/sec

Answer: a



Watch Video Solution

72. The average power dissipation in a pure capacitance in AC circuit is

A. $\frac{1}{2}CV^2$

B. CV^2

C. $\frac{1}{4}CV^2$

D. Zero

Answer: D



Watch Video Solution

73. In a region of uniform magnetic induction $B = 10^2$ tesla, a circular coil of radius 30cm and resistance π^2 ohm is rotated about an axis which is perpendicular to the direction of B and which forms a diameter of the coil. If the coil rotates at 200rpm the amplitude of the alternating current induced in the coil is

A. $4\pi\text{mA}$

B. 30mA

C. 6mA

D. 200mA

Answer: c



Watch Video Solution

74. An inductive circuit a resistance of 10ohm and an inductance of 2.0 henry. If an AC voltage of 120volt and frequency of 60Hz is applied to this circuit, the current in the circuit would be nearly

A. 0.32 amp

B. 0.16 amp

C. 0.48 amp

D. 0.80 amp

Answer: b



Watch Video Solution

75. In a LCR circuit having $L = 8.0$ henry, $C = 0.5\mu F$ and $R = 100$ ohm in series. The resonance frequency in per second is

A. 600 radian

B. 600 Hz

C. 500 radian

D. 500 Hz

Answer: c



Watch Video Solution

76. in a LCR circuit capacitance is chagned from C to $2C$.
For the resomat frequency to remain unchanged, the
inductance should be chagned from L to

A. $2L$

B. $L/2$

C. $L/4$

D. $4L$

Answer: c



Watch Video Solution

77. A 120 volt AC source is connected across a pure inductor of inductance 0.70 henry. If the frequency of the source is $60Hz$, the current passing through the inductor is

- A. 4.55 amps
- B. 0.355 amps
- C. 0.455 amps
- D. 3.55 amps

Answer: c



Watch Video Solution

78. The impedance of a circuit consists of 3ohm resistance and 4ohm reactance. The power factor of the circuit is

A. 0.4

B. 0.6

C. 0.8

D. 1

Answer: b



Watch Video Solution

79. L, C and R represent the physical quantities, inductance, capacitance and resistance respectively. The combination(s) which have the dimensions of frequency are

A. $\frac{1}{RC}$

B. $\frac{R}{L}$

C. $\frac{1}{\sqrt{LC}}$

D. $\frac{C}{L}$

Answer: d



Watch Video Solution

80. The power factor of a good choke coil is

- A. Nearly zero
- B. Exactly zero
- C. Nearly one
- D. Exactly one

Answer: a



[Watch Video Solution](#)

81. If resistance of 100Ω , inductance of 0.5 henry and capacitor of $10 \times 10^{-6}F$ are connected in series through $50Hz$ AC supply, then impedance is

A. 1.876

B. 18.76

C. 189.72

D. 101.3

Answer: c



Watch Video Solution

82. An alternating current source of frequency 100Hz is joined to a combination of a resistance, a capacitance and a coil in series. The potential difference across the coil, the resistance and the capacitor is 46, 8 and 40

volt respectively. The electromotive force of alternating current source in volt is

A. 94

B. 14

C. 10

D. 76

Answer: c



Watch Video Solution

83. A 10 ohm resistance, $5mH$ coil and $10\mu F$ capacitor are joined in series. When a suitable frequency alternating current source is joined to this combination,

the circuit resonates. If the resistance is halved, the resonance frequency

- A. Is halved
- B. Is doubled
- C. Remains unchanged
- D. In quadrupled

Answer: C



Watch Video Solution

84. L,C and R represent the physical quantities inductance, capacitance and resistance respectively.

Which of the following combinations have dimensions of frequency?

A. LC

B. $(LC)^{-1/2}$

C. $\left(\frac{L}{C}\right)^{-1/2}$

D. $\frac{C}{L}$

Answer: b



Watch Video Solution

85. In a series circuit $R = 300\Omega$, $L = 0.9H$, $C = 2.0\mu F$ and $\omega = 1000\text{rad/sec}$. The impedance of the circuit is

A. 1300Ω

B. 900Ω

C. 500Ω

D. 400Ω

Answer: C



Watch Video Solution

86. In a $L - R$ circuit, the value of L is $\left(\frac{0.4}{\pi}\right)$ henry and the value of R is 30 ohm. If in the circuit, an alternating e.m.f of 200 vol at 50 cycles per sec is connected, the impedance of the circuit will be

A. 11.4Ω , $17.5A$

B. 30.7Ω , $6.5A$

C. 40.4Ω , $5A$

D. 50Ω , $4A$

Answer: d



Watch Video Solution

87. The reactance of a coil when used in the domestic AC power supply ($220V$, $50cycles$) is $100ohm$. The selfinductance of the coil is nearly

A. 3.2 henry

B. 0.32 henery

C. 2.2 henry

D. 0.22 henry

Answer: b



Watch Video Solution

88. In a series LCR circuit, operated with an ac of angular frequency ω , the total impedance is

A. $\left[R^2 + (L\omega - C\omega)^2 \right]^{1/2}$

B. $\left[R^2 + \left(L\omega - \frac{1}{C\omega} \right)^2 \right]^{1/2}$

C. $\left[R^2 + \left(L\omega - \frac{1}{C\omega} \right)^2 \right]^{-1/2}$

$$D. \left[(R\omega)^2 + \left(L\omega - \frac{1}{C\omega} \right)^2 \right]^{1/2}$$

Answer: B



Watch Video Solution

89. The reactance of a $25\mu F$ capacitor at the AC frequency of $4000Hz$ is

A. $\frac{5}{\pi} ohm$

B. $\sqrt{\frac{5}{\pi}} ohm$

C. $10ohm$

D. $\sqrt{10}ohm$

Answer: A



Watch Video Solution

90. The frequency for which a $5\mu F$ capacitor has a reactance of $\frac{1}{100}$ ohm is given by

A. $\frac{100}{\pi} MHz$

B. $\frac{1000}{\pi} Hz$

C. $\frac{1}{1000} Hz$

D. $1000 Hz$

Answer: a



Watch Video Solution

91. An e.m.f. $E = 4 \cos(1000t)$ volt is applied to an LR circuit of inductance $3mH$ and resistance $4ohm$. The amplitude of current in the circuit is

A. $\frac{4}{\sqrt{7}} A$

B. $1.0A$

C. $\frac{4}{7} A$

D. $0.8A$

Answer: d



Watch Video Solution

92. In an AC circuit, a resistance of R ohm is connected in series with an inductance L . If phase angle between voltage and current be 45° , the value of inductive reactance will be

A. $\frac{R}{4}$

B. $\frac{R}{2}$

C. R

D. Cannot be found with the given data

Answer: c



Watch Video Solution

93. A coil of inductance L has an inductive reactance of X_L in an AC circuit in which the effective current is I . The coil is made from a super-conducting material and has no resistance. The rate at which power is dissipated in the coil is

A. 0

B. IX_L

C. $I^2 X_L$

D. IX_L^2

Answer: a



Watch Video Solution

94. The phase difference between the current and voltage of LCR circuit in series combination at resonance is

A. 0

B. $\pi/2$

C. π

D. $-\pi$

Answer: a



Watch Video Solution

95. In a series resonant circuit, the AC voltage across resistance R , inductance L , and capacitance C are $5V$, $10V$ and $10V$ respectively. The AC voltage applied to the circuit will be

A. 20 V

B. 10 V

C. 5 V

D. 25 V

Answer: c



Watch Video Solution

96. When 100volts *DC* is applied across a coil, a current of 1amp flows through it. When 100 volt *AC* at 50 cycles s^{-1} is applied to the same coil, only 0.5 ampere current follows.then the impedance of the coil is

A. 100Ω

B. 200Ω

C. 300Ω

D. 400Ω

Answer: b



Watch Video Solution

97. The coefficient of induction of a choke coil is $0.1H$ and resistance is 12Ω . If it is connected to an alternating current source of frequency $60Hz$, then power factor will be

A. 0.32

B. 0.30

C. 0.28

D. 0.24

Answer: b



Watch Video Solution

98. For series LCR circuit, correct statements are

A. Applied e.m.f. and potential difference across resistance are in same phase

B. Applied e.m.f. and potential difference at inductor coil have phase difference of $\pi / 2$

C. Potential difference at capacitor and inductor have phase difference of $\pi / 2$

D. Potential difference across resistance and capacitor have phase difference of $\pi / 2$

Answer: c



Watch Video Solution

99. In a purely resistive ac circuit, the current

A. Lags behind the e.m.f. in phase

B. Is in phase with the e.m.f.

C. Leads the e.m.f. in phase

D. Leads the e.m.f. in half the cycle and lags behind it
in the other half

Answer: B



Watch Video Solution

100. If an 8Ω resistance and 6Ω reactance are present in an AC series circuit then the impedance of the circuit will be

A. 20 ohm

B. 14 ohm

C. 10 ohm

D. $14\sqrt{2}$ ohm

Answer: C



Watch Video Solution

101. A 12ohm resistor and a 0.21 henry inductor are connected in series to an AC source operating at $20\text{volts}, 50$ cycle/second. The phase angle between the current and the source voltage is

A. 30°

B. 40°

C. 80°

D. 90°

Answer: c



Watch Video Solution

102. What will be the phase difference between virtual voltage and virtual current, when the current in the circuit is wattless

A. 90°

B. 45°

C. 180°

D. 60°

Answer: a



Watch Video Solution

103. The resonant frequency of a circuit is f . If the capacitance is made 4 times the initial values, then the resonant frequency will become

A. $f/2$

B. $2f$

C. f

D. $f/4$

Answer: a



Watch Video Solution

104. In the non-resonant circuit, what will be the nature of the circuit for frequencies heigher than the resonant frequency?

A. Resistive

B. Capacitive

C. Inductive

D. None of the above

Answer: b



Watch Video Solution

105. In an ac circuit the potential differences across an inductance and resistance joined in series are, respectively, 16 V and 20 V. The total potential difference across the circuit is

A. 20.0 V

B. 25.6 V

C. 31.9 V

D. 53.5 V

Answer: b



Watch Video Solution

106. A 220 V , 50 Hz ac source is connected to an inductance of 0.2 H and a resistance of 20 ohm in series.

What is the current in the circuit

A. 10A

B. 5A

C. 33.3 A

D. 3.33 A

Answer: d



Watch Video Solution

107. An LCR circuit contains $R = 50\Omega$, $L = 1mH$ and $C = 0.1\mu F$. The impedance of the circuit will be minimum for a frequency of

A. $\frac{10^5}{2\pi} s^{-1}$

B. $\frac{10^6}{2\pi} s^{-1}$

C. $2\pi \times 10^5 s^{-1}$

D. $2\pi \times 10^6 s^{-1}$

Answer: A



Watch Video Solution

108. In a series LCR circuit, resistance $R = 10\Omega$ and the impedance $Z = 20\Omega$ the phase difference between the current and the voltage is

A. 30°

B. 45°

C. 60°

D. 90°

Answer: C



Watch Video Solution

109. A series AC circuit consists of an inductor and a capacitor. The inductance and capacitance is respectively 1henry and $25\mu F$ if the current is maximum in circuit then angular frequency will be

A. 200

B. 100

C. 50

D. $200 / 2\pi$

Answer: a



Watch Video Solution

110. An alternating EMF of frequency $\frac{1}{2\pi\sqrt{LC}}$ is applied to a series LCR circuit. For this frequency of the applied EMF,

- A. The circuit is at resonance and its impedance is made up only of a reactive part
- B. The current in the circuit is in phase with the applied e.m.f. and the voltage across R equals this applied emf
- C. The sum of the p.d.'s across the inductance and capacitance equals the applied e.m.f. which is 180° ahead of phase of the current in the circuit

D. The quality factor of the circuit is $\omega L/R$ or $1/\omega CR$ and this is a measure of the voltage magnification (produced by the circuit at resonance) as well as the sharpness of resonance of the circuit


Answer: bd



Watch Video Solution

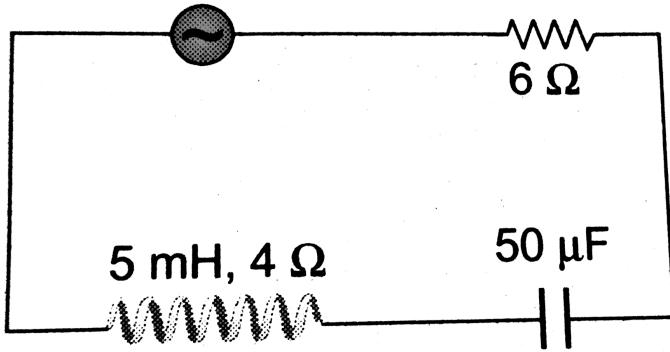111. In the circuit below, the AC source the voltage $V = 20 \cos(\omega t)$ volts with $\omega = 2000 \text{ rad/sec}$. The

amplitude of the current will be nearest to



- A. 2A
- B. 3.3A
- C. $2/\sqrt{5}\text{A}$
- D. $\sqrt{5}\text{A}$

Answer: a



Watch Video Solution

112. The value of the current through an inductance of 1 H and of negligible resistance, when connected through an ac source of 200 V and 50 Hz , is

A. 0.637 A

B. 1.637 A

C. 2.637 A

D. 3.637

Answer: a



Watch Video Solution

113. The quality factor of LCR circuit having resistance (R) and inductance (L) at resonance frequency (ω) is given by

A. $\frac{\omega L}{R}$

B. $\frac{R}{\omega L}$

C. $\left(\frac{\omega L}{R}\right)^{1/2}$

D. $\left(\frac{\omega L}{R}\right)^2$

Answer: a



Watch Video Solution

114. Power factor is maximum in an LCR circuit when

A. $X_L = X_C$

B. $R = 0$

C. $X_L = 0$

D. $X_C = 0$

Answer: a



Watch Video Solution

115. In an AC circuit the reactance of a coil is $\sqrt{3}$ times its resistance, the phase difference between the voltage across the current through the coil will be

A. $\pi/3$

B. $\pi / 2$

C. $\pi / 4$

D. $\pi / 6$

Answer: a



Watch Video Solution

116. The capacitance of a pure capacitance is 1 farad. In DC circuits, its effective resistance will be

A. Zero

B. Infinite

C. 1 ohm

D. $1/2$ ohm

Answer: b



Watch Video Solution

117. In an ac circuit, the current lags behind the voltage by $\pi/3$. The components in the circuit are

A. R and L

B. R and C

C. L and C

D. Only R

Answer: A



Watch Video Solution

118. The reactance of a coil when used in the domestic AC power supply ($220V, 50cycles$) is $50ohm$. The inductance of the coil is nearly

- A. 2.2 henry
- B. 0.22 henry
- C. 1.6 henry
- D. 0.16 henry

Answer: d



Watch Video Solution

119. In an AC circuit, the power factor

A. Is zero when the circuit contains an ideal resistance only

B. Is unity when the circuit contains an ideal resistance only

C. Is zero when the circuit contains an ideal inductance only

D. Is unity when the circuit contains an ideal inductance only

Answer: bc



Watch Video Solution

120. A resistance of 40 ohms and an inductance of 95.5 millihenry are connected in series in a 50 cycle/sec AC circuit. The impedance of this combination is very nearly

A. 30 ohm

B. 40 ohm

C. 50 ohm

D. 60 ohm

Answer: c



Watch Video Solution

121. For high frequency, a capacitor offers

- A. More reactance
- B. Less reactance
- C. Zero reactance
- D. Infinite reactance

Answer: b



Watch Video Solution

122. The coil of choke in a circuit

- A. Increases the current

- B. Decreases the current
- C. Does not change the current
- D. Has high resistance to dc circuit

Answer: b



Watch Video Solution

123. In a circuit, the current lags behind the voltage by a phase difference of $\pi/2$, the circuit will contain which of the following ?

- A. Only R
- B. Only L

C. Only C

D. R and C

Answer: b



Watch Video Solution

124. Reactance of an inductor of $\frac{1}{\pi}$ henry at $50Hz$ frequency is

A. $\frac{50}{\pi} ohm$

B. $\frac{\pi}{50} ohm$

C. $100ohm$

D. $50ohm$

Answer: c



Watch Video Solution

125. An oscillator circuit consists of an inductance of $0.5mH$ and a capacitor of $20\mu F$. The resonant frequency of the circuit is nearly

A. 15.92 Hz

B. 159.2 Hz

C. 1592 Hz

D. 15910 Hz

Answer: c



Watch Video Solution

126. Reactance of a capacitor of capacitance $C \mu F$ for ac frequency $\frac{400}{\pi} Hz$ is 25Ω . The value C is

A. $50 \mu F$

B. $25 \mu F$

C. $100 \mu F$

D. $75 \mu F$

Answer: a



Watch Video Solution

127. The power factor of an AC circuit having resistance (R) and inductance (L) connected in series and an angular velocity ω is

A. $R / \omega L$

B. $R / (R^2 + \omega^2 L^2)^{1/2}$

C. $\omega L / R$

D. $R / (R^2 - \omega^2 L^2)^{1/2}$

Answer: B



Watch Video Solution

128. A circuit has a resistance of 11Ω , an inductive reactance of 25Ω , and a capacitive resistance of 18Ω . It is connected to an *AC* source of $260V$ and $50Hz$. The current through the circuit (in amperes) is

A. 11

B. 15

C. 18

D. 20

Answer: d



Watch Video Solution

129. A 0.7 henry inductor is connected across a $120V - 60Hz AC$ source. The current in the inductor will be very nearly

A. 4.55 amp

B. 0.355 amp

C. 0.455 amp

D. 3.55 amp

Answer: C



Watch Video Solution

130. There is a 5Ω resistance in an AC , circuit. Inductance of $0.1H$ is connected with it in series. If equation of AC emf is $5\sin 50t$ then the phase difference between current and e.m.f. is

A. $\frac{\pi}{2}$

B. $\frac{\pi}{6}$

C. $\frac{\pi}{4}$

D. 0

Answer: c



Watch Video Solution

131. An inductor of inductance L and resistor of resistance R are joined in series and connected by a source of frequency ω . Power dissipated in the circuit is

A. $\frac{(R^2 + \omega^2 L^2)}{V}$

B. $\frac{V^2 R}{(R^2 + \omega^2 L^2)}$

C. $\frac{V}{(R^2 + \omega^2 L^2)}$

D. $\frac{\sqrt{R^2 + \omega^2 L^2}}{V^2}$

Answer: b



Watch Video Solution

132. In a ac circuit of capacitance the current from potential is

- A. Forward
- B. Backward
- C. Both are in the same phase
- D. None of these

Answer: a



[Watch Video Solution](#)

133. A coil of 200Ω resistance and $1.0H$ inductance is conneted to an AC source of frequency $200/2\pi Hz$.

Phase angle between potential and current will be

A. 30

B. 90

C. 45

D. 0

Answer: c



Watch Video Solution

134. In a LCR circuit the $P. D$ between the terminals of the inductance is $60V$, between the terminals of the capacitor is $30V$ and that between the terminals of resistance is $40V$. The supply voltage will be equal to.....

A. 50 V

B. 70 V

C. 130 V

D. 10 V

Answer: a



Watch Video Solution

135. Radio frequency choke uses core of

A. Air

B. Iron

C. Air and iron

D. None of these

Answer: a



Watch Video Solution

136. in a LCR circuit capacitance is chagned from C to $2C$.
For the resomat frequency to remain unchanged, the
inductance should be chagned from L to

A. $4L$

B. $2L$

C. $L/2$

D. $L/4$

Answer: c



Watch Video Solution

137. In an LCR series a.c. Circuit the voltage across each of the components L,C and R is 50V. The voltage across the LC combination will be

A. 50 V

B. $50\sqrt{2}V$

C. 100V

D. 0V (zero)

Answer: d



Watch Video Solution

138. A coil has $L = 0.04H$ and $R = 12\Omega$. When it is connected to $220V, 50Hz$ supply the current flowing through the coil, in ampere is

A. 10.7

B. 11.7

C. 14.7

D. 12.7

Answer: d



Watch Video Solution

139. The current in series LCR circuit will be the maximum when ω is

A. As large as possible

B. Equal o natural frequency of LCR system

C. \sqrt{LC}

D. $\sqrt{1/LC}$


Answer: d



Watch Video Solution

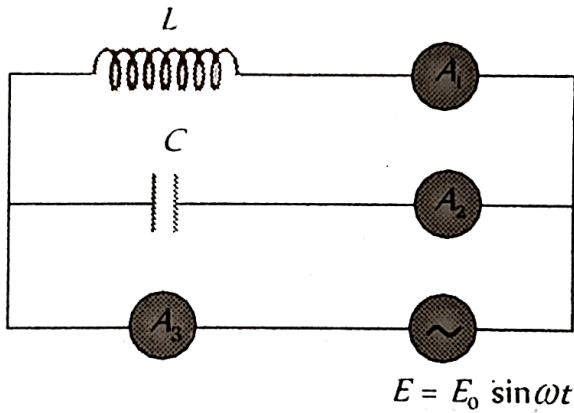140. An inductor L and a capacitor C are connected in the circuit as shown in the figure. The frequency of the

power supply is equal to the resonant frequency of the circuit. Which ammeter will read zero ampere



- A. A_1
- B. A_2
- C. A_3
- D. None of these

Answer: c



Watch Video Solution

141. Which of the following components of a LCR circuit, with ac supply, dissipates energy

A. LCR

B. R

C. C

D. All of these

Answer: b



Watch Video Solution

142. In a circuit L , C and R are connected in series with an alternating voltage source of frequency f . The current lead the voltages by 45° . The value of C is :

A. $\frac{1}{2\pi f(2\pi fL + R)}$

B. $\frac{1}{\pi f(2\pi fL + R)}$

C. $\frac{1}{2\pi f(2\pi fL - R)}$

D. $\frac{1}{\pi f(2\pi fL - R)}$

Answer: a



Watch Video Solution

143. In an A.C. circuit the current

- A. Always leads the voltage
- B. Always lags behind the voltage
- C. Is always in phase with the voltage
- D. May lead or lag behind or be in phase with the voltage


Answer: D



[Watch Video Solution](#)

144. For the series LCR circuit shown in the figure, what is the resonance frequency and the amplitude of

the current at the resonating frequency

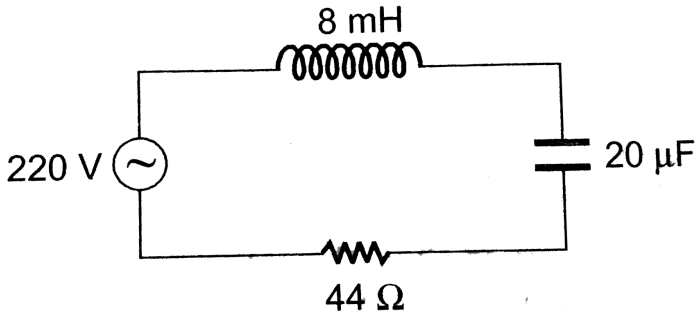

A. $2500\text{rad} - s^{-1}$ and $5\sqrt{2}A$

B. $2500\text{rad} - s^{-1}$ and $5A$

C. $2500\text{rad} - s^{-1}$ and $\frac{5}{\sqrt{2}}A$

D. $25\text{rad} - s^{-1}$ and $5\sqrt{2}A$

Answer: B



Watch Video Solution

145. When $100V$ DC is applied across a solenoid, a current of $1.0A$ flows in it. When $100V$ AC is applied across the same coil. The current drops to $0.5A$. If the frequency of the ac source is $50Hz$, the impedance and inductance of the solenoid are

A. 200Ω and 0.55 henry

B. 100Ω and 0.86 henry

C. 200Ω and 1.0 henry

D. 100Ω and 0.93 henry

Answer: a



Watch Video Solution

146. In an LR -circuit, the inductive reactance is equal to the resistance R of the circuit. An e.m.f $E = E_0 \cos(\omega t)$ applied to the circuit. The power consumed in the circuit is

A. $\frac{E_0^2}{R}$

B. $\frac{E_0^2}{2R}$

C. $\frac{E_0^2}{4R}$

D. $\frac{E_0^2}{8R}$

Answer: c



Watch Video Solution

147. One $10V$, $60W$ bulb is to be connected to $100V$ line. The required inductance coil has self-inductance of value ($f = 50Hz$)

A. 0.052 H

B. 2.42 H

C. 16.2 mH


D. 1.62 mH

Answer: a



Watch Video Solution

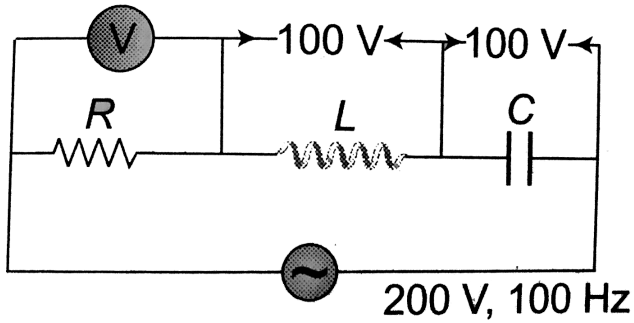148. In the circuit given below, what will be the reading of the voltmeter?




- A. 300 V
- B. 900 V
- C. 200 V
- D. 400 V

Answer: c

 Watch Video Solution

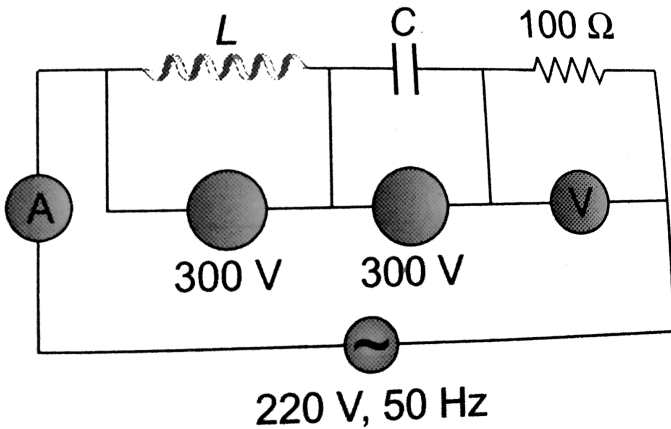149. In the circuit shown below, what will be the reading of the voltmeter and ammeter?



- A. 800 V, 2A
- B. 300 V, 2A
- C. 220 V, 2.2 A
- D. 100 V, 2A

Answer: c



Watch Video Solution

150. A bulb and a capacitor are connected in series to a source of alternating current. If its frequency is increased, while keeping the voltage of the source constant, then

- A. Bulb will give more intense light
- B. Bulb will give less intense light
- C. Bulb will give light of same intensity as before
- D. Bulb will stop radiating light

Answer: a



Watch Video Solution

151. An alternating e.m.f. of angular frequency ω is applied across an inductance. The instantaneous power developed in the circuit has an angular frequency

A. $\frac{\omega}{4}$

B. $\frac{\omega}{2}$

C. ω

D. 2ω

Answer: d



Watch Video Solution

152. The voltage of an ac source varies with time according to the equation $V = 100 \sin 100\pi t \cos 100\pi t$ where t is in seconds and V is in volt. Then


- A. The peak voltage of the source is 100 volts
- B. The peak voltage of the source is 50 volt
- C. The peak voltage of the source is $100 / \sqrt{2}$ volts
- D. The frequency of the source is 50 Hz

Answer: b



Watch Video Solution

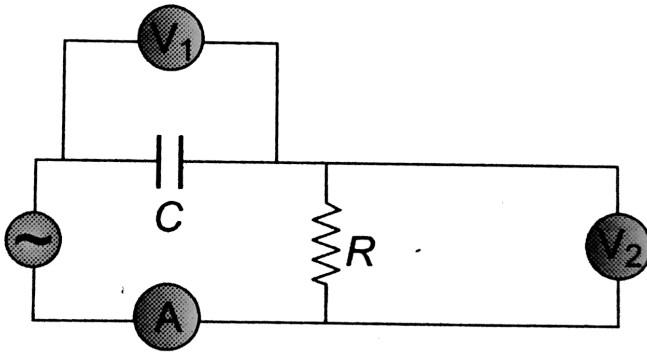153. The diagram shows a capacitor C and a resistor R connected in series to an AC source. V_1 and V_2 are voltmeters and A is ammeter



Now, consider the following statements :

- (I) Reading in A and V_2 are always in phase.
- (II) Reading in V_1 is ahead in phase with reading in V_2 ,
- (III) Reading in A and V_1 are always in phase. Which of these statements are/is correct

A. I only

B. II only

C. I and II only

D. II and III only


Answer: b



Watch Video Solution

154. In the circuit shown in figure neglecting source resistance the voltmeter and ammeter reading will

respectively, will be

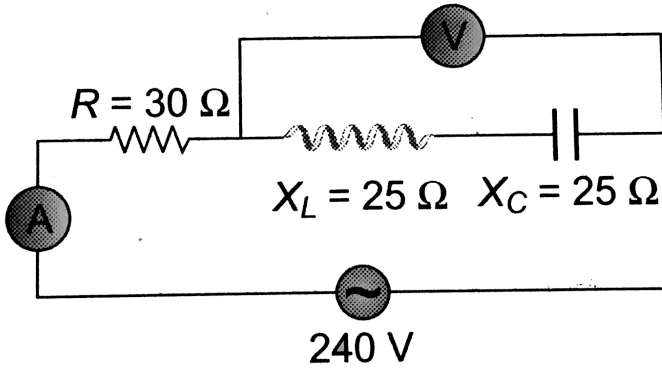

- A. 0 V, 3A
- B. 150 V, 3A
- C. 150 V, 6A
- D. 0 V, 8A

Answer: d



Watch Video Solution

155. The voltage of an AC source varies with time according to the relation: $E = 120 \sin 100\pi t \cos 100\pi t V$. What is the peak voltage of the source?

A. 120 volts, 100 Hz

B. $\frac{120}{\sqrt{2}}$ volts, 100 Hz

C. 60 volts, 200 Hz


D. 60 volts, 100 Hz

Answer: d



Watch Video Solution

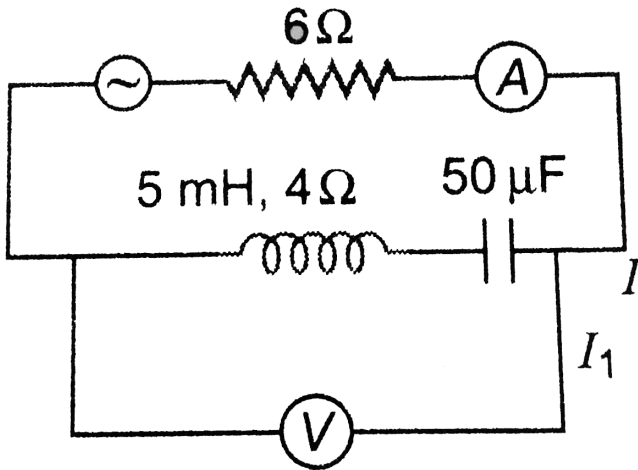156. In the circuit shown in figure the AC source gives a voltage $V = 20 \cos(2000t)$. Neglecting source resistance, the voltmeter and ammeter readings will be



- A. 0 V, 0.47 A
- B. 1.68 V, 0.47 A
- C. 0 V, 1.4 A
- D. 5.6 V, 1.4 A

Answer: d



Watch Video Solution

157. A telephone wire of length 200 km has a capacitance of $0.014\mu\text{F per km}$. If it carries an AC of frequency 5 kHz what should be the value of an inductor required to be connected in series so that impedance of the circuit is minimum ?

A. 0.35 mH

B. 35 mH

C. 3.5 mH

D. Zero

Answer: a



Watch Video Solution

158. In a certain circuit current changes with time according to $i = 2\sqrt{t}$. r.m.s. value of current between $t = 2$ to $t = 4s$ will be

A. $3A$

B. $3\sqrt{3}A$

C. $2\sqrt{3}A$

D. $(2 - \sqrt{2})A$

Answer: c



Watch Video Solution

159. Match the following

Currents

r.m.s. values

(1) $x_0 \sin \omega t$

(i) x

(2) $x_0 \sin \omega t \cos \omega t$

(ii) $\frac{x_0}{\sqrt{2}}$

(3) $x_0 \sin \omega t + x_0 \cos \omega t$

(iii) $\frac{x_0}{(2\sqrt{2})}$

A. 1. (i), 2. (ii), 3. (iii)

B. 1. (ii), 2. (iii), 3. (i)

C. 1. (i), 2. (iii), 3. (ii)


D. None of these

Answer: b



Watch Video Solution

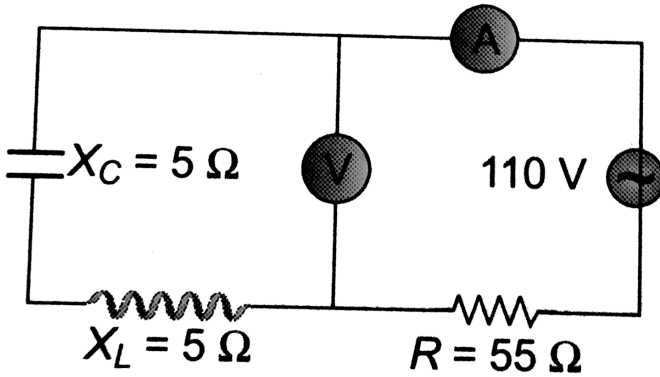160. The reading of ammeter in the circuit shown will be



- A. $2A$
- B. $2.4A$
- C. Zero
- D. $1.7A$

Answer: c



161. An AC source of angular frequency ω is fed across a resistor R and a capacitor C in series. The current registered is I . If now the frequency of source is changed to $\omega/3$ (but maintaining the same voltage), the current in the circuit is found to be halved. The ratio of reactance to resistance at the original frequency ω will be.

A. $\sqrt{\frac{3}{5}}$

B. $\sqrt{\frac{2}{5}}$

C. $\sqrt{\frac{1}{5}}$

D. $\sqrt{\frac{4}{5}}$

Answer: a



Watch Video Solution

162. An $L - C - R$ series circuit with 100Ω resistance is connected to an AC source of $200V$ and angular frequency $300\text{rad}/s$. When only the capacitance is removed, the current lags behind the voltage by 60° . When only the inductance is removed the current leads the voltage by 60° . Calculate the current and the power dissipated in the $L - C - R$ circuit

A. 50 W

B. 100 W

C. 200 W

D. 400 W

Answer: d



Watch Video Solution

163. A virtual current of $4A$ and $50Hz$ flows in an AC circuit containing a coil. The power consumed in the coil is $240W$. If the virtual voltage across the coil is $100v$ then its inductance will be

A. $\frac{1}{3\pi} H$

B. $\frac{1}{5\pi} H$

C. $\frac{1}{7\pi}H$

D. $\frac{1}{9\pi}H$

Answer: b



Watch Video Solution

164. For a series RLC circuit $R = X_L = 2X_C$. The impedance of the current and phase different (between) V and i will be

A. $\frac{\sqrt{5}R}{2}, \tan^{-1}(2)$

B. $\frac{\sqrt{5}R}{2}, \tan^{-1}\left(\frac{1}{2}\right)$


C. $\sqrt{5}X_C, \tan^{-1}(2)$

D. $\sqrt{5}R, \tan^{-1}\left(\frac{1}{2}\right)$

Answer: b

 Watch Video Solution

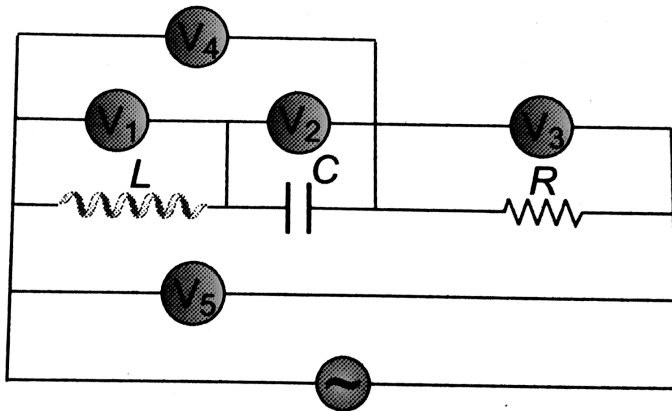165. In the adjoining AC circuit the voltmeter whose reading will be zero at resonance is



A. V_1

B. V_2


C. V_3

D. V_4

Answer: d

 Watch Video Solution

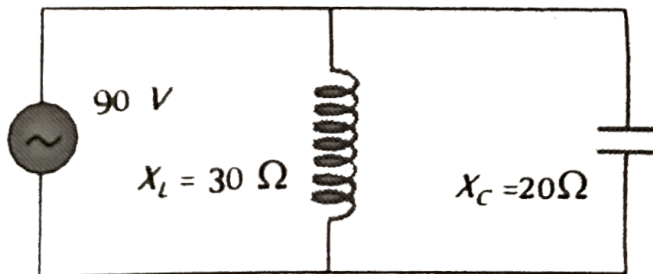166. In the adjoining figure the impedance of the circuit will be



A. 120 ohm

B. 50 ohm

C. 60 ohm

D. 90 ohm

Answer: c



Watch Video Solution

167. If $i = t^2$, $0 < t < T$ then *r. m. s.* value of current is

A. $\frac{T^2}{\sqrt{2}}$

B. $\frac{T^2}{2}$


C. $\frac{T^2}{\sqrt{5}}$

D. None of these

Answer: c

 Watch Video Solution

168. Is it possible

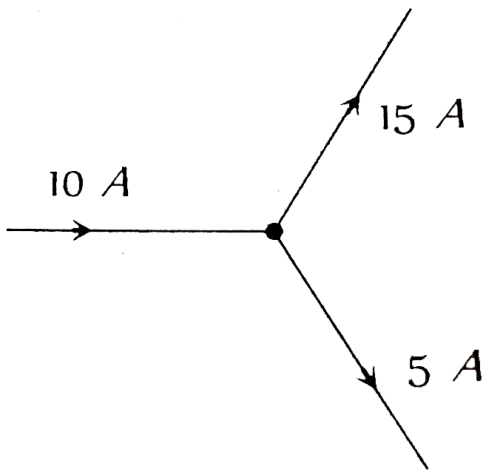

A. Yes

B. No

C. Cannot be predicted

D. Insufficient data to reply

Answer: a



Watch Video Solution

169. In a series circuit $C = 2\mu F$, $L = 1mH$ and $R = 10\Omega$, when the current in the circuit is maximum, at that time the ratio of the energies stored in the capacitor and the inductor will be

A. 1:1

B. 1:2

C. 2:1





D. 1:5

Answer: d



Watch Video Solution

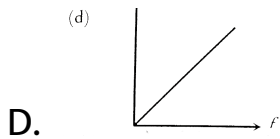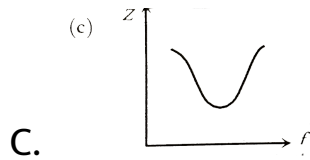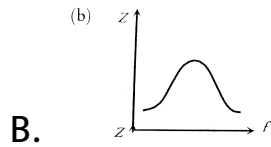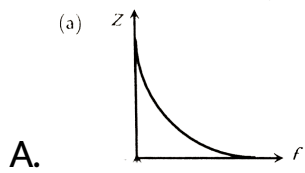170. Which of the following curves represents the variation of impedance (Z) with frequency f in series LCR circuit?




Answer: c



Watch Video Solution

171. The variation of the instantaneous current (I) and the instantaneous e.m.f (E) in a circuit is as shown in

figure. Which of the following statement is correct?

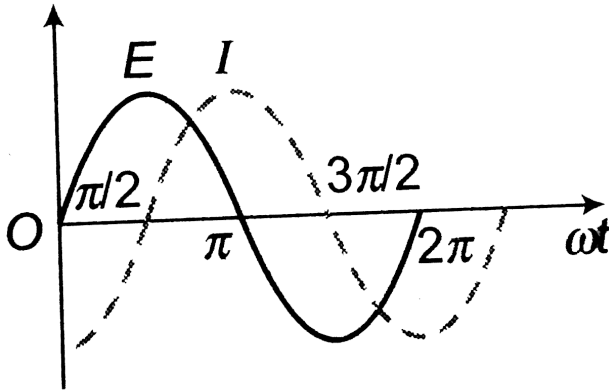


- A. The voltage lags behind the current by $\pi/2$
- B. The voltage leads the current by $\pi/2$
- C. The voltage and the current are in phase
- D. The voltage leads the current by π

Answer: b



Watch Video Solution

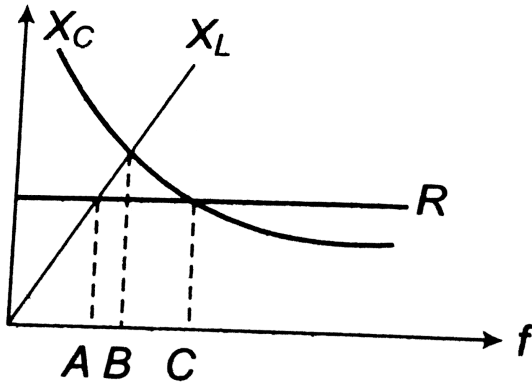172. The figure shows variation of R , X_L and X_C with frequency f in a series L, C, R circuit. Then for what frequency point, the circuit is inductive ?



A. A

B. B

C. C




D. All points


Answer: c



Watch Video Solution

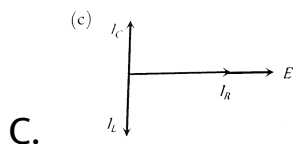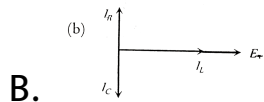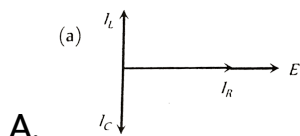173. An alternating emf is applied across a parallel combination of a resistance R , capacitance C and an inductance L . If I_R, I_L, I_C are the currents through R, L and C respectively. Then the diagram which correctly represents, the phase relationship among I_R, I_L, I_C and source emf E_m is given by



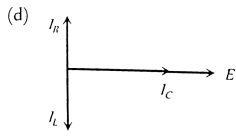


D.

Answer: c


 Watch Video Solution

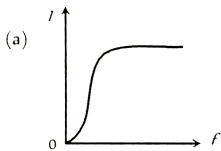174. An AC source of variable frequency f is connected to an LCR series circuit. Which one of the graphs in figure represents the variation of current of current I in the circuit with frequency f ?




A.


B.

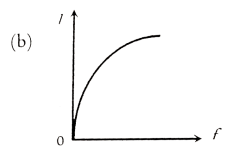

C.

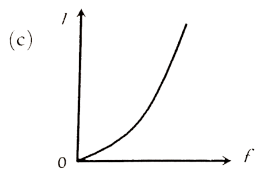


D.

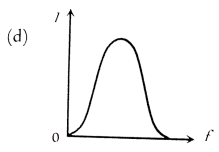

Answer: d

 **Watch Video Solution**

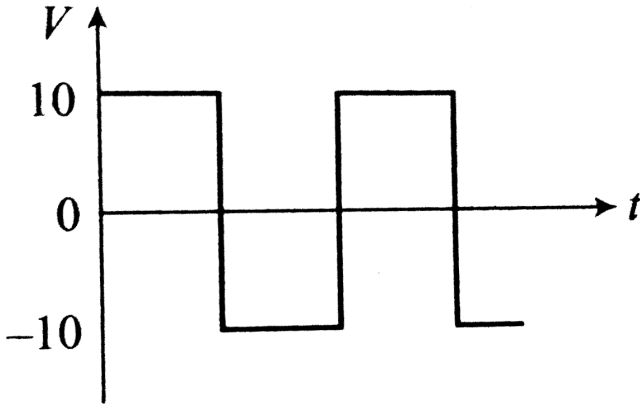
175. The r.m.s. voltage of the wave form shown is




- A. 10 V
- B. 7 V
- C. 6.37 V
- D. None of these


Answer: a

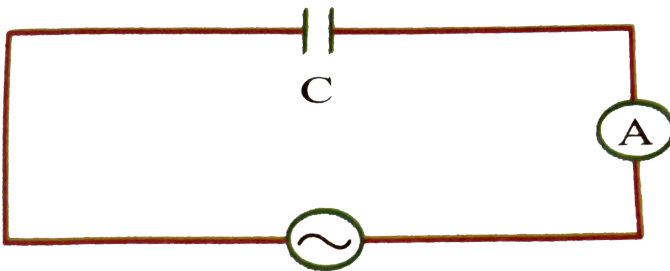176. A constant voltage at different frequencies is applied across a capacitance C as shown in the figure. Which of the following graphs correctly depicts the variation of current with frequency



A.C. generator

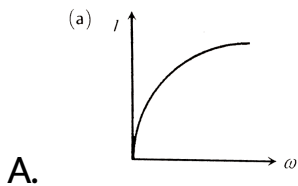


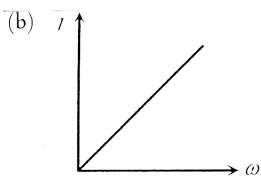

B.



C.

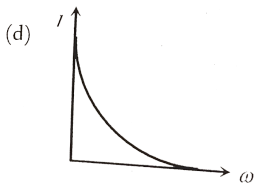

D.


Answer: b



Watch Video Solution

177. The output current versus time curve of a rectifier is shown in the figure. The voltage value of output current

in this case is

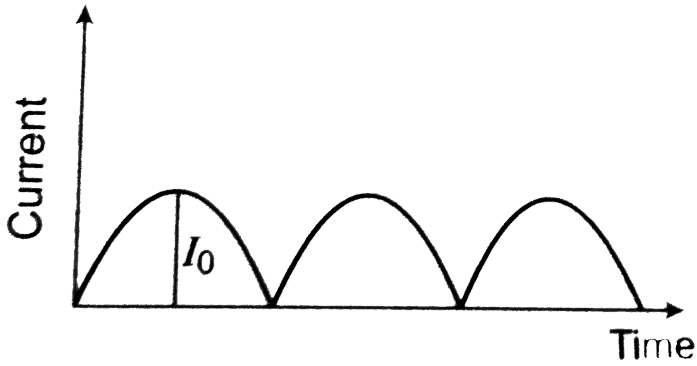

A. 0

B. $\frac{I_0}{2}$

C. $\frac{2I_0}{\pi}$



D. I_0


Answer: c




Watch Video Solution

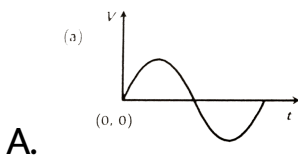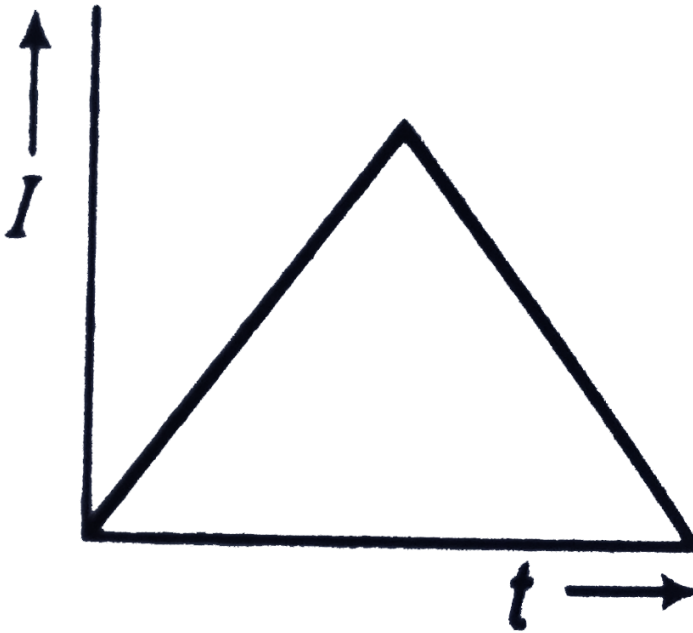178. An alternating current I in an inductance coil varies with time t according to the graph as shown: Which one of the following graph gives the variation of voltage with time?




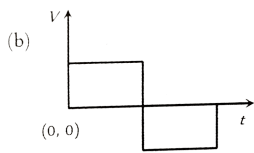

B.

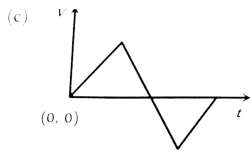

C.

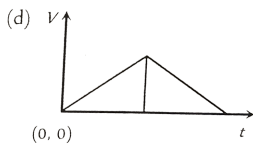

D.


Answer: b



Watch Video Solution

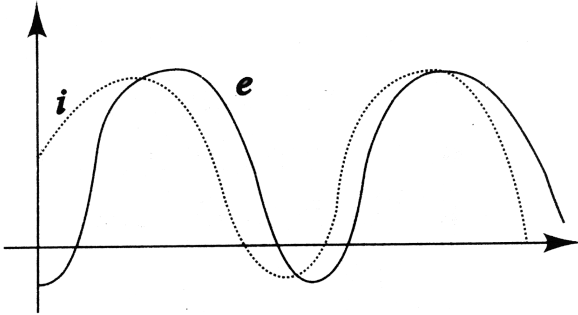179. When an ac source of emf $e = E_0 \sin(100t)$ is connected across a circuit, the phase difference between emf e and current I in the circuit is observed to be $(\pi)/(4)$ as shown in fig. If the circuit consists possibly

only of R-C or R-C of L-R series, find the relationship find the relationship between the two elements.




- A. $R = 1k\Omega, C = 10\mu F$
- B. $R = 1k\Omega, C = 1\mu F$
- C. $R = 1k\Omega, L = 10H$
- D. $R = 1k\Omega, L = 1H$

Answer: a



Watch Video Solution

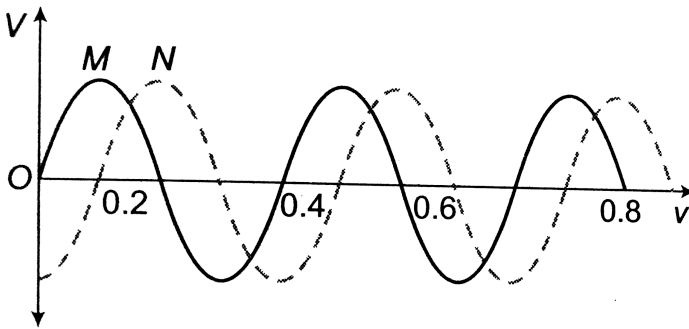180. Two sinusoidal voltage of the same frequency are shown in the diagram. What is the frequency, and the phase relationship between the voltage?



Frequency in Hz phase lead of N over M in radians

A.

Frequency in Hz Phase lead of N over M in radians
 0.4 $-\pi/4$

B.

Frequency in Hz Phase lead of N over M in radians
 2.5 $-\pi/2$

C.

Frequency m Hz	Phase lead of N over M in radians
2.5	$+\pi/2$

D.

Frequency m Hz	Phase lead of N over M in radians
2.5	$-\pi/4$






Answer: b



Watch Video Solution

181. The voltage across a pure inductor is represented by the following diagram. Which one of the following

diagrams will represent the current

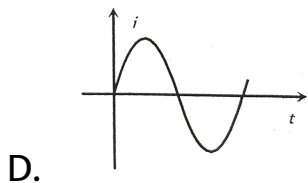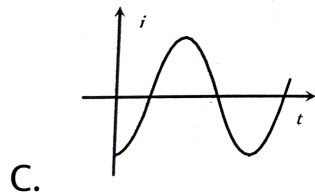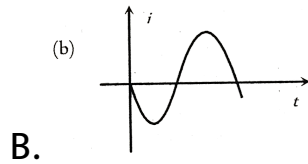
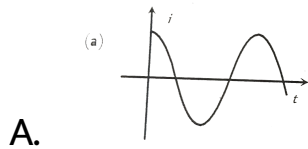
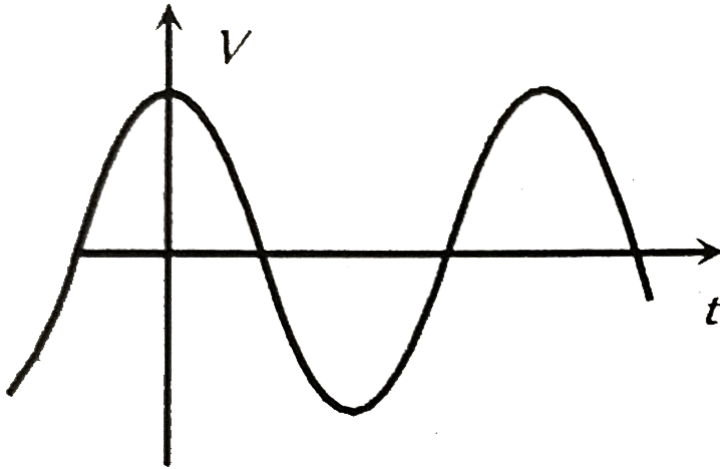



Answer: D



Watch Video Solution

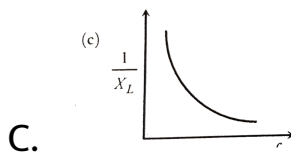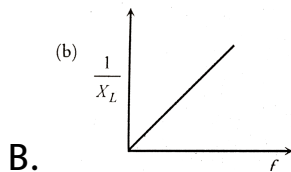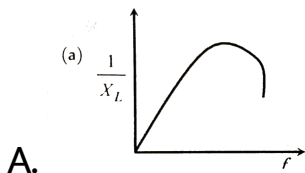182. In pure inductive circuit, the curves between frequency f and reciprocal of inductive reactance $1/X_L$ is



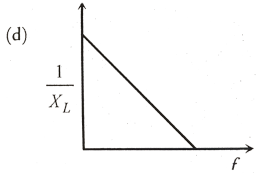


D.

Answer: c



Watch Video Solution

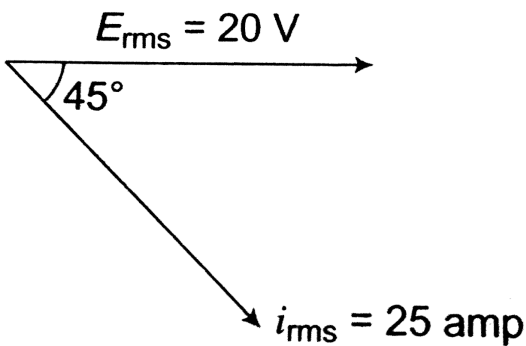183. The vector diagram of current and voltage for a circuit as shown. The components of the circuit will be



A. LCR

B. LR

C. LCR ot LR


D. None of these

Answer: c



Watch Video Solution

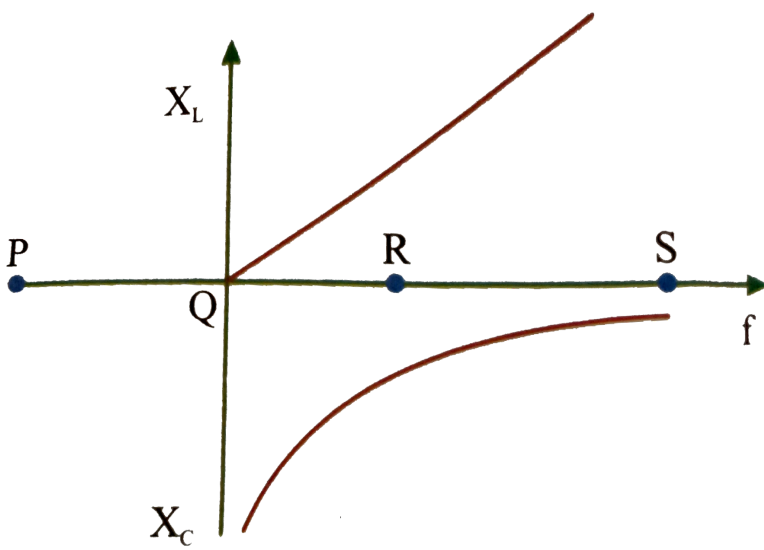184. The resonance point in $X_L - f$ and $X_C - f$ curves is
is



A. P

B. Q

C. R


D. S

Answer: c




Watch Video Solution

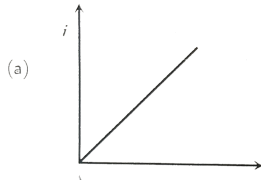
185. The $i - v$ curve for anti-resonant circuit is




A.

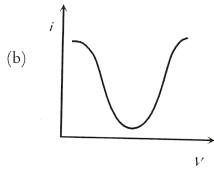

B.

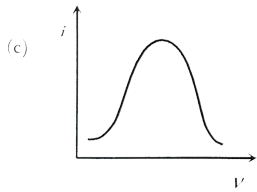

C.

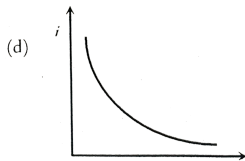


D.

Answer: b



Watch Video Solution

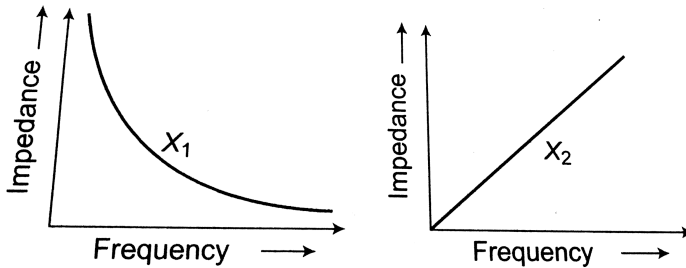186. The graphs given below depict the dependence of two reactive impedances X_1 and X_2 on the frequency of the alternating e.m.f. applied individually to them. We can then say that




- A. X_1 is an inductor and X_2 is a capacitor
- B. X_1 is a resistor and X_2 is a capacitor
- C. X_1 is a capacitor and X_2 is an inductor
- D. X_1 is an inductor and X_2 is a resistor

Answer: c



Watch Video Solution

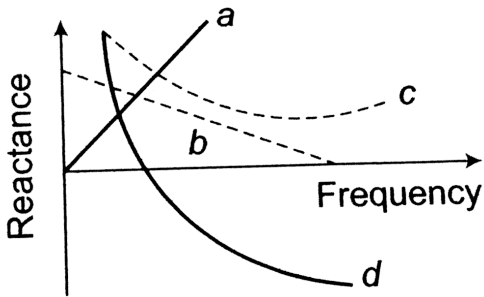187. Which of the following plots may represent the reactance of a series LC combination?






- A. a
- B. b
- C. c
- D. d


Answer: d



Watch Video Solution

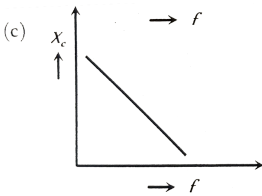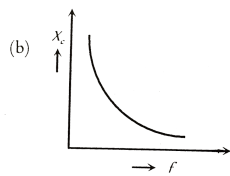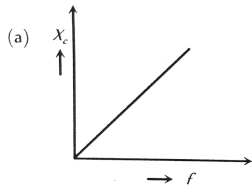188. Identify the graph which correctly represents the variation of capacitive reactance X_C with frequency



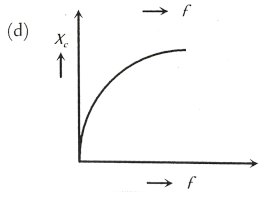

Answer: b

 [Watch Video Solution](#)

189. Assertion: In series LCR circuit resonance can take place.

Reason: Resonance takes place if inductance and capacitive reactance are equal and opposite.

A. If both assertion and reason are true and the reason is the correct explanation of the assertion.

B. If both assertion and reason are true but reason is not the correct explanation of the assertion.

C. If assertion is true but reason is false.

D. If the assertion and reason both are false.

Answer: a



[Watch Video Solution](#)

190. Assertion: The alternating current lags behind the e.m.f. by a phase angle of $\pi/2$, when AC flows through an inductor.

Reason: The inductive reactance increases as the frequency of AC source decreases.

- A. If both assertion and reason are true and the reason is the correct explanation of the assertion.
- B. If both assertion and reason are true but reason is not the correct explanation of the assertion.
- C. If assertion is true but reason is false.
- D. If the assertion and reason both are false.

Answer: c



Watch Video Solution

191. Assertion: Capacitance serves as a block for DC and offers an easy path to AC .

Reason: Capacitance reactance is inversely proportional to frequency.

A. If both assertion and reason are true and the reason is the correct explanation of the assertion.

B. If both assertion and reason are true but reason is not the correct explanation of the assertion.

C. If assertion is true but reason is false.

D. If the assertion and reason both are false.

Answer: a



Watch Video Solution

192. Assertion: When capacitive reactance is smaller than the inductive reactance in an LCR circuit, e.m.f. leads the current.

Reason : The phase angle is the angle between the alternating e.m.f. and alternating current of the circuit.

- A. If both assertion and reason are true and the reason is the correct explanation of the assertion.
- B. If both assertion and reason are true but reason is not the correct explanation of the assertion.
- C. If assertion is true but reason is false.
- D. If the assertion and reason both are false.

Answer: b



Watch Video Solution

193. Assertion: Chock coil is the preferred over a resistor to adjust current in an AC circuit.

Reason: Power factor for inductance is zero.

- A. If both assertion and reason are true and the reason is the correct explanation of the assertion.
- B. If both assertion and reason are true but reason is not the correct explanation of the assertion.
- C. If assertion is true but reason is false.
- D. If the assertion and reason both are false.

Answer: a

 [Watch Video Solution](#)

194. Assertion: If the frequency of alternating current in an AC circuit consisting of an inductance coil is increased then current gets decreased.

Reason: The current is inversely proportional to frequency of alternating current.

A. If both assertion and reason are true and the reason is the correct explanation of the assertion.

B. If both assertion and reason are true but reason is not the correct explanation of the assertion.

C. If assertion is true but reason is false.

D. If the assertion and reason both are false.

Answer: a



Watch Video Solution

195. Assertion: A bulb connected in series with a solenoid is connected to AC source. If a soft iron core is introduced in the solenoid, the bulb will glow brighter.

Reason: On introducing soft iron core in the solenoid, the inductance increases.

A. If both assertion and reason are true and the reason is the correct explanation of the assertion.

B. If both assertion and reason are true but reason is not the correct explanation of the assertion.

C. If assertion is true but reason is false.

D. If assertion is false but reason is true.

Answer: d



[Watch Video Solution](#)

196. Statement 1: An alternating current shown magnetic effect.

Statement 2: Alternating current varies with time .

- A. If both assertion and reason are true and the reason is the correct explanation of the assertion.
- B. If both assertion and reason are true but reason is not the correct explanation of the assertion.
- C. If assertion is true but reason is false.
- D. If the assertion and reason both are false.

Answer: b



Watch Video Solution

197. Statement 1: Both dc and ac can be measured by a hot wire instrument.

Statement 2: the hot wire instrument is based on the principle of magnetic effect of current.

A. If both assertion and reason are true and the reason is the correct explanation of the assertion.

B. If both assertion and reason are true but reason is not the correct explanation of the assertion.

C. If assertion is true but reason is false.

D. If the assertion and reason both are false.

Answer: c



Watch Video Solution

198. Assertion: AC is more dangerous than DC

Reason: Frequency of AC is dangerous for human body.

- A. If both assertion and reason are true and the reason is the correct explanation of the assertion.
- B. If both assertion and reason are true but reason is not the correct explanation of the assertion.
- C. If assertion is true but reason is false.
- D. If the assertion and reason both are false.

Answer: a



Watch Video Solution

199. Assertion: Average value of AC over a complete cycle is always zero.

Reason: Average value of AC is always defined over half cycle.

- A. If both assertion and reason are true and the reason is the correct explanation of the assertion.
- B. If both assertion and reason are true but reason is not the correct explanation of the a ssertion.
- C. If assertion is true but reason is false.
- D. If the assertion and reason both are false.

Answer: b



Watch Video Solution

200. Assertion: The division are equally marked on the scale of AC ammeter.

Reason: Heat produced is directly proportional to the current

- A. If both assertion and reason are true and the reason is the correct explanation of the assertion.
- B. If both assertion and reason are true but reason is not the correct explanation of the a ssertion.
- C. If assertion is true but reason is false.
- D. If the assertion and reason both are false.

Answer: d

 [Watch Video Solution](#)

201. Assertion: When AC circuit contain resistor only, its power is minimum.

Reason: Power of a circuit is independent of phase angle.

A. If both assertion and reason are true and the reason is the correct explanation of the assertion.

B. If both assertion and reason are true but reason is not the correct explanation of the a ssertion.

C. If assertion is true but reason is false.

D. If the assertion and reason both are false.

Answer: d

 [Watch Video Solution](#)

202. Assertion: An electric lamp connected in series with a variable capacitor and AC source, its brightness increases with increases in capacitance.

Reason: Capacitive reactance decrease with increases in capacitance of capacitor.

A. If both assertion and reason are true and the reason is the correct explanation of the assertion.

B. If both assertion and reason are true but reason is not the correct explanation of the assertion.

C. If assertion is true but reason is false.

D. If the assertion and reason both are false.

Answer: a



Watch Video Solution

203. Assertion: An inductance and a resistance are connected in series with an AC circuit. In this circuit the current and the potential difference across the resistance lag behind potential difference across the inductance by an angle $\pi / 2$.

Reason: In LR circuit voltage leads the current by phase angle which depends on the value of inductance and resistance both.

- A. If both assertion and reason are true and the reason is the correct explanation of the assertion.
- B. If both assertion and reason are true but reason is not the correct explanation of the assertion.
- C. If assertion is true but reason is false.
- D. If the assertion and reason both are false.

Answer: b



Watch Video Solution

204. Assertion: A capacitor of suitable capacitance can be used in an AC circuit in place of the choke coil.

Reason: A capacitor blocks DC and allows AC

- A. If both assertion and reason are true and the reason is the correct explanation of the assertion.
- B. If both assertion and reason are true but reason is not the correct explanation of the assertion.
- C. If assertion is true but reason is false.
- D. If the assertion and reason both are false.

Answer: b



Watch Video Solution

1. A bulb and a capacitor are in series with an AC source. On increasing frequency how will glow of the bulb change

- A. The glow decreases
- B. The glow increases
- C. The glow remain the same
- D. The bulb quenches

Answer: b



Watch Video Solution

2. The r.m.s current in an AC circuit is $2A$. If the wattless current be $\sqrt{3}A$, what is the power factor?

A. $\frac{1}{\sqrt{3}}$

B. $\frac{1}{\sqrt{2}}$

C. $\frac{1}{2}$

D. $\frac{1}{3}$

Answer: c



Watch Video Solution

3. $\frac{2.5}{\pi} \mu F$ capacitor and $3000 - \text{ohm}$ resistance are joined in series to an AC source of 200volts and

50 sec^{-1} frequency. The power factor of the circuit and the power dissipated in it will respectively

A. 0.6, 0.06W

B. 0.06, 0.6W

C. 0.6, 4.8W

D. 4.8, 0.6W

Answer: c



Watch Video Solution

4. The self-inductance of a choke coil is 10 mH . When it is connected with a 10 VDC source, then the loss of power is 20watt. When it is connected with 10 volt AC

source loss of power is 10watt. The frequency of AC source will be

- A. 50 Hz
- B. 60 Hz
- C. 80 Hz
- D. 100 Hz

Answer: c

 [Watch Video Solution](#)

5. In an LCR circuit $R = 100ohm$. When capacitance C is removed, the current lags behind the voltage by $\pi/3$.

When inductance L is removed, the current leads the voltage by $\pi / 3$. The impedance of the circuit is

- A. 50 ohm
- B. 100 ohm
- C. 200 ohm
- D. 400 ohm

Answer: B



Watch Video Solution

6. A group of electric lamps having a total power rating of 1000 watt is supplied by an AC voltage

$E = 200 \sin(310t + 60^\circ)$. Then the r.m.s value of the circuit current is

A. $10A$

B. $10\sqrt{2}A$

C. $20A$


D. $20\sqrt{2}A$

Answer: b

 [Watch Video Solution](#)

7. Following figure shows an AC generator to a "block box" through a pair of terminals. The box contains possible R , L , C or their combination, whose elements

and arrangements are not known to us.

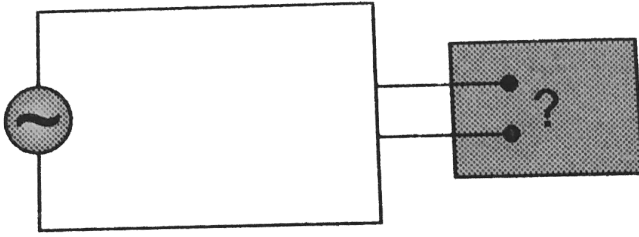

Measurements, outside the box reveals that $e = 75 \sin(\omega t)$ volts, $i = 1.5 \sin(\omega t + 45^\circ)$ amp then.

the wrong statements is

- A. There must be a capacitor in the box
- B. There must be an inductor in the box
- C. There must be a resistance in the box
- D. The power factor is 0.707

Answer: B



Watch Video Solution

8. A resistor R , an inductor L and a capacitor C are connected in series to a source of frequency n . If the resonant frequency is n_r , then the current lags behind voltage when

A. $n = 0$

B. $n < n_r$

C. $n = n_r$

D. $n > n_r$

Answer: d



Watch Video Solution

9. If power factor is $1/2$ in a series RL , circuit $R = 100\Omega$. AC mains is used then L is

A. $\frac{\sqrt{3}}{\pi}$ Henry

B. π Henry

C. $\frac{\pi}{\sqrt{3}}$ Henry

D. None of these

Answer: A



[Watch Video Solution](#)

10. What will be the self-inductance of a coil, to be connected in a series with a resistance of $\pi\sqrt{3}\Omega$ such

that the phase difference between the e.m.f. and the current at 50Hz frequency is 30° ?

- A. 0.5 Henry
- B. 0.03 Henry
- C. 0.05 Henry
- D. 0.01 Henry

Answer: D



[Watch Video Solution](#)

11. The phase difference between the voltage and the current in an AC circuit is $\pi/4$. If the frequency is 50Hz then this phase difference will be equivalent to a time of

A. 0.02 s

B. 0.25 s

C. 2.5 ms

D. 25 ms

Answer: C



Watch Video Solution

12. Instantaneous values of current and e.m.f in an AC circuit are $I = I/\sqrt{2} \sin 314$ amp and $E = \sqrt{2} \sin(314t - \pi/6)V$ respectively. The phase difference between E and I will be

A. $-\pi/6\text{rad}$

B. $-\pi/3\text{rad}$

C. $\pi/6\text{rad}$


D. $\pi/3\text{rad}$

Answer: a



Watch Video Solution

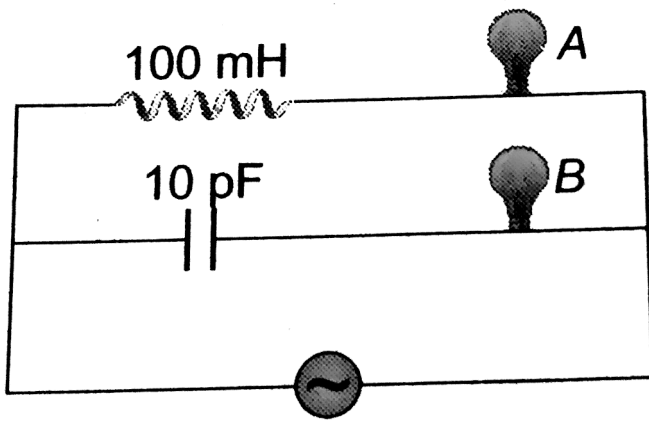13. If A and B are identical bulbs, which bulb glows brighter?



- A. A
- B. B
- C. Both equally bright
- D. Cannot say

Answer: a

 **Watch Video Solution**

14. The instantaneous values of current and voltage in an ac circuit are $i = 100 \sin 314t$ amp and $e = 200 \sin(314t + \pi/3)$ V respectively. If the resistance is 1Ω then the reactance of the circuit will be

A. $-200\sqrt{3}\Omega$

B. $\sqrt{3}\Omega$

C. $-200/\sqrt{3}\Omega$

D. $100\sqrt{3}\Omega$

Answer: b



Watch Video Solution

15. What is the r.m.s. value of an alternating current which when passed through a resistor produces heat which is thrice of that produced by a direct current of 2 amperes in the same resistor?

A. 6 amp

B. 2 amp

C. 3.46 amp

D. 0.66 amp

Answer: c



Watch Video Solution