



PHYSICS

BOOKS - D MUKHERJEE PHYSICS (HINGLISH)

ELECTRIC CURRENT IN CONDUCTORS

Others

1. The carrier density (number of free electrons per m^3) in metallic conductors is of the order

of

A. 10^{10}

B. 10^{-16}

C. 10^{22}

D. 10^{28}

Answer: D



Watch Video Solution

2. When a current flows in a conductor, the order of magnitude of drift velocity of electrons through it is :

A. $1\text{cm} / \text{s}$

B. $10\text{m} / \text{s}$

C. $10^4\text{m} / \text{s}$

D. $10^8\text{m} / \text{s}$

Answer: A



Watch Video Solution

3. The resistance of a metallic conductor increases with temperature due to.

A. change in carrier density

B. change in the dimensions of the conductor

C. increase in the number of collisions among the carriers

D. increase in the rate of collision between the carriers and the vibration atoms of

the conductor

Answer: D



Watch Video Solution

4. A piece of copper and another of germanium are cooled from room temperature to $80K$. The resistance of

A. each of them increases

B. each of them decreases

C. copper increases and that of germanium decreases

D. copper decreases and that of germanium increases

Answer: D



Watch Video Solution

5. A straight conductor of uniform cross-section carries a current I . Let $s =$ specific charge of an electron. The momentum of all

the free electrons per unit length of the conductor, due to their drift velocity only, is

A. $I s$

B. I / s

C. $\sqrt{I / s}$

D. $(I / s)^2$

Answer: B



Watch Video Solution

6. Current flows through a metallic conductor whose area of cross-section increases in the direction of the current. If we move in this direction.

- A. the current will change
- B. the carrier density will change
- C. the drift velocity will increase
- D. the drift velocity will decrease

Answer: D



Watch Video Solution

7. A conducting ring of radius R has charge Q distributed unevenly over it. If it rotates with an angular velocity ω , the equivalent current will be

A. zero

B. $Q\omega$

C. $Q \frac{\omega}{2\pi}$

D. $Q \frac{\omega}{2\pi R}$

Answer: C::D



Watch Video Solution

8. All the edges of a block with parallel faces are unequal. Its longest edge is twice its shortest edge. The ratio of the maximum to minimum resistance between parallel faces is.

A. 2

B. 4

C. 8

D. indeterminate unless the length of the third edge is specified


Answer: B



Watch Video Solution

9. In the network shown below, the equivalent resistance between A and B is

Physics MCQ

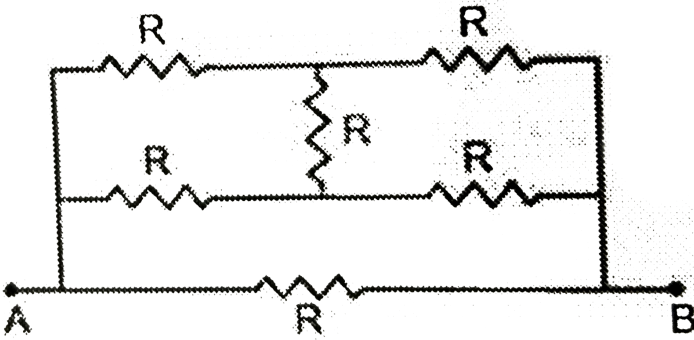

A. $R/2$

B. R

C. $2R$

D. $4R$

Answer: A



Watch Video Solution

10. A and B are two points on a uniform ring of resistance R the $\angle ASCB = \theta$, where C is the centre of the ring. The equivalent resistance between A and B

A. $\frac{R}{4\pi^2}(2\pi - \theta)\theta$

B. $R\left(1 - \frac{\theta}{2\pi}\right)$


C. $R\frac{\theta}{2\pi}$

D. $R\frac{2\pi - \theta}{4\pi}$

Answer: A



Watch Video Solution

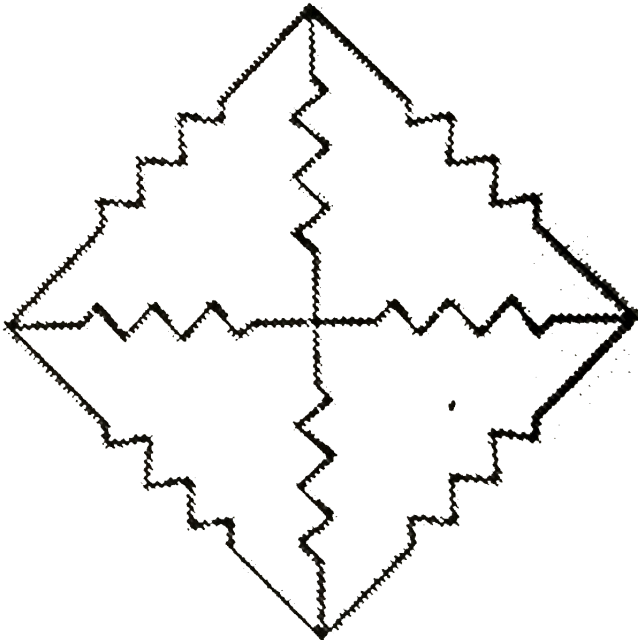

11.

In the network shown, each resistance is equal

to R . The equivalent resistance between diagonally opposite corners is

A. R

B. $R/3$

C. $2R/3$



D. $4R/3$

Answer: C::D



Watch Video Solution

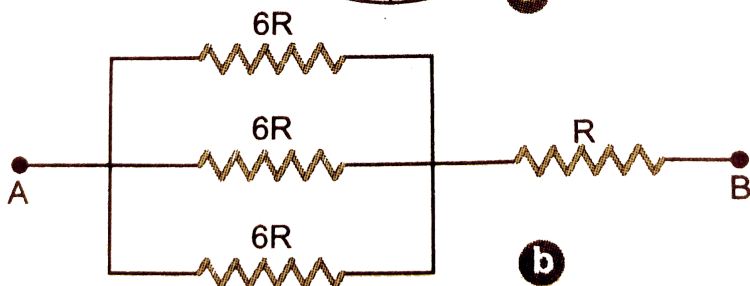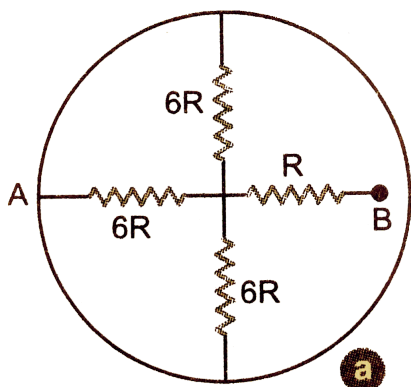12. In the network shown in figure, the ring has zero resistance. Find the resistance between A and B.



A. $2R$

B. $4R$

C. $7R$

D. $10R$





Answer: A



Watch Video Solution

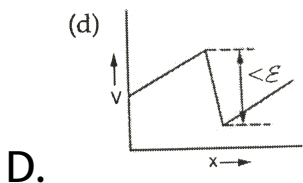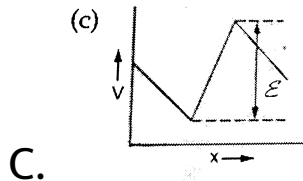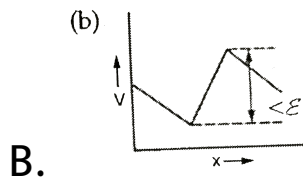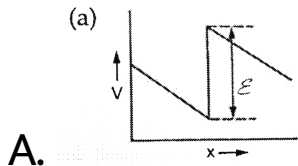13. The two ends of a uniform conductor are joined to a cell of e.m.f. E and some internal resistance. Starting from the midpoint P of the conductor, we move in the direction of current and return to P . The potential V at

every point on the path is plotted against the distance covered (x). which of the following graphs best represent the resulting curve ?



Answer: B



Watch Video Solution

14. The emf of a cell is ε and its internal resistance is r . Its terminals are connected to a resistance R . The potential difference between the terminals is $1.6V$ for $R = 4\Omega$, and $1.8V$ for $R = 9\Omega$. Then,

A. $\varepsilon = 1V, r = 1\Omega$

B. $\varepsilon = 2V, r = 1\Omega$

C. $\varepsilon = 2V, r = 2\Omega$

D. $\varepsilon = 2.5V, r = 0.5\Omega$

Answer: B



Watch Video Solution

15. N identical cells are connected to form a battery. When the terminals of the battery are joined directly (short - circuited), current I flows in the circuit. To obtain the maximum value of I ,

A. all the cells should be joined in series

B. all the cells should be joined in parallel

C. two rows of $N/2$ cells each should be
joined in parallel

D. \sqrt{N} rows of \sqrt{N} cells each should be
joined in parallel, given that \sqrt{N} is an
integer

Answer: B



Watch Video Solution

16. N identical cells, each emf E and internal resistance r are joined in series. Out of N cells, n cells are wrongly connected i.e., their terminals are connected in reverse of the required for series connection $\left(n < \frac{N}{2}\right)$. Let E_0 be the emf of resulting battery and r_0 be its internal resistance. Then

A. $\mathcal{E}_0 = (N - n)\mathcal{E}, r_0 = (N - n)r$

B. $\mathcal{E} = (N - 2n)\mathcal{E}, r_0 = (N - 2n)r$

C. $\mathcal{E}_0 = (N - 2n)\mathcal{E}, r_0 = Nr$

$$D. \mathcal{E} = (N - n)\mathcal{E}, r_0 = Nr$$

Answer: C::D



Watch Video Solution

17. n identical cells, each of emf E and internal resistance r , are joined in series to form a closed circuit. Find the potential difference across any one cell.

A. zero

B. ε

C. $\frac{\varepsilon}{n}$

D. $\frac{n-1}{n} \varepsilon$

Answer: A



Watch Video Solution

18. n identical cells, each of emf ε and internal resistance r , are joined in series to form a closed circuit. One cell is joined with

reversed polarity. The potential difference across each cell, except A, is

A. $\frac{2\varepsilon}{n}$

B. $\frac{n-1}{n}\varepsilon$


C. $\frac{n-2}{n}\varepsilon$

D. $\frac{2n}{n-2}\varepsilon$

Answer: A



Watch Video Solution

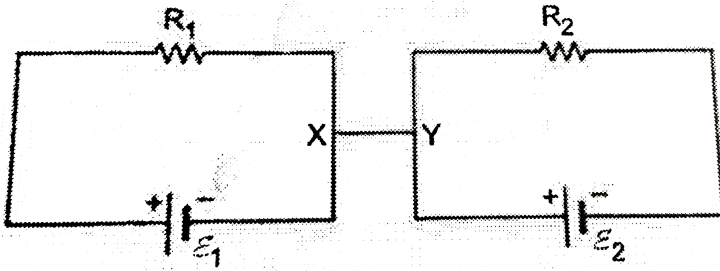

19.

In the circuit shown above, the conductor XY is of negligible resistance. Then

A. current will flow through XY if $\epsilon_1 \neq \epsilon_2$

B. current will flow through XY if

$$\frac{\epsilon_1}{R_1} \neq \frac{\epsilon_2}{R_2}$$


C. current will flow through XY if

$$\frac{\epsilon_1 + \epsilon_2}{R_1 + R_2} \neq \frac{|\epsilon_1 - \epsilon_2|}{R_1 - R_2}$$

D. no current will flow through XY

Answer: D

 Watch Video Solution

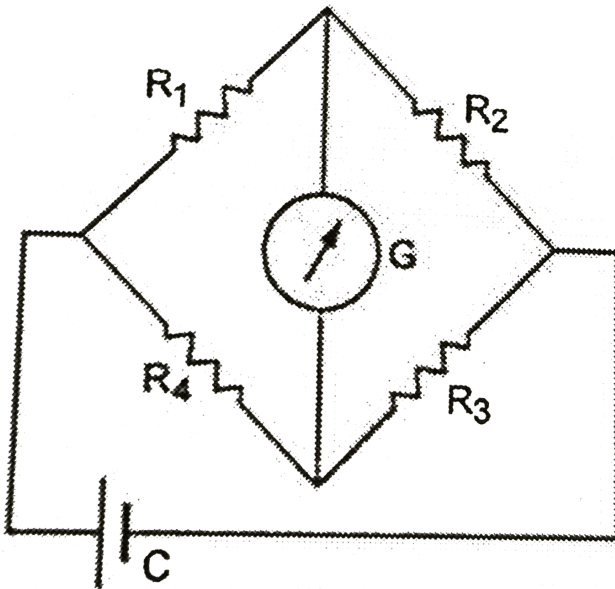

20.

The Wheatstone bridge shown in the above

figure is balanced. If the positions of the cell C and the galvanometer G are now interchanged, G will show zero deflection

A. in all cases

B. only if all the resistances are equal


C. only if $R_1 = R_3$ and $R_2 = R_4$

D. only if $R_1 / R_3 = R_2 / R_4$

Answer: A



Watch Video Solution

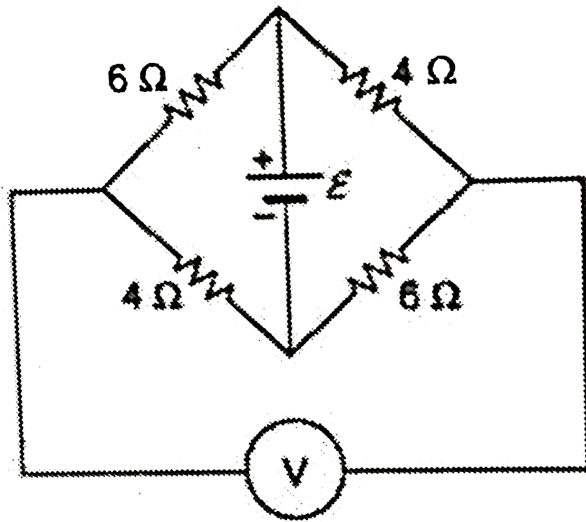

21.

In the circuit shown above the voltmeter is of large resistance. The emf of the cell is ϵ . The reading of the voltmeter is

A. zero

B. $\frac{\epsilon}{10}$

C. $\frac{\epsilon}{5}$

D. $\frac{\varepsilon}{2}$

Answer: C::D



Watch Video Solution

22. A Galvanometer of range $10mA$ has a coil of resistance 1Ω . To use it as an ammeter of range $1A$, the required shunt must have a resistance of

A. $\frac{1}{101}\Omega$

B. $\frac{1}{100}\Omega$

C. $\frac{1}{99}\Omega$

D. $\frac{1}{9}\Omega$

Answer: C::D



Watch Video Solution

23. A milliammeter of range of $10mA$ gives full-scale deflection for a current of $100mA$, when a shunt of 0.1Ω is connected in parallel

to it. The coil of the milliammeter has a resistance of.

A. 0.9Ω

B. 1Ω

C. 1.1Ω


D. 0.11Ω

Answer: A



Watch Video Solution

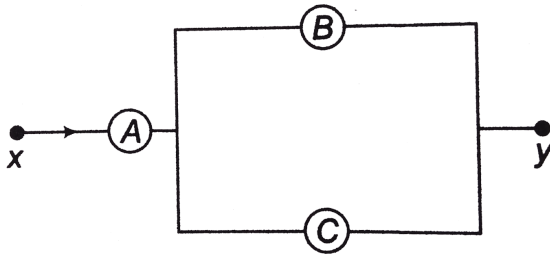24. A , B and C are voltmeters of resistances R , $1.5R$ and $3R$ respectively. When some potential difference is applied between x and y the voltmeter readings are V_A , V_B and V_C , then



A. $V_A = V_B = V_C$

B. $V_A \neq V_B = V_C$

C. $V_A = V_B \neq V_C$

$$D. V_B \neq V_A = V_C$$

Answer: A



Watch Video Solution

25. An ammeter and a voltmeter are joined in series to a cell. Their readings are A and V respectively. If a resistance is now joining parallel with the voltmeter. Then

A. both A and V will increase

B. both A and V will decrease

C. A will decrease, V will increase

D. A will increase, V will decrease

Answer: D



Watch Video Solution

26. In a moving -coil instrument, the coil is is suspended in a radial magnetilc field instead of a uniform magnetic field. This is done to

A. increase the sensitivity of the instrument

B. increase the accuracy of the instrument

C. make the instrument compact and portable

D. make its deflection proportional to the current through it

Answer: D



View Text Solution

27. A cell of internal resistance r drives a current through an external resistance R . The power delivered by the cell to the external resistance is maximum when

A. $R = r$

B. $R > r$

C. $R < r$



D. $R = 2r$

Answer: A




Watch Video Solution

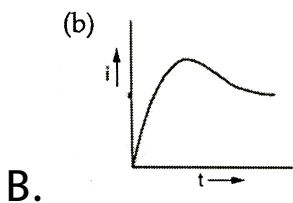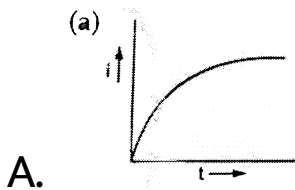
28. When an electric heater is switched on, the current flowing through it (i) is plotted against time (t). Taking into account the variation of resistance with temperature, which of the following best represents the resulting curve



C.

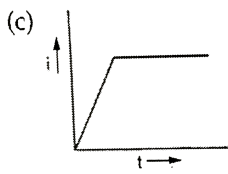

D.

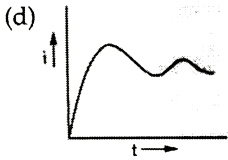


Answer: B



Watch Video Solution

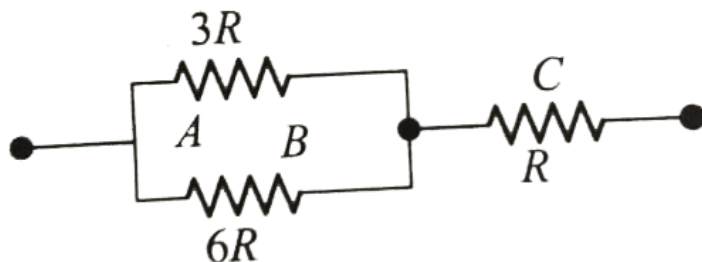29. Figure 7.37 shows a network of three resistances. When some potential difference is applied across the network, thermal powers

dissipated by A , B and C are in the ratio



A. 2 : 3 : 4

B. 2 : 4 : 3

C. 4 : 2 : 3

D. 3 : 2 : 4

Answer: C::D



Watch Video Solution

30. An electric bulb is designed to draw P_0 power at V_0 voltage. If the voltage is V , it draws power. Then

A. $P = \frac{V_0}{V} P_0$

B. $P = \frac{V}{V_0} P_0$

C. $P = \left(\frac{V}{V_0}\right)^2 P_0$

D. $P = \left(\frac{V_0}{V}\right)^2 P_0$

Answer: C::D



Watch Video Solution

31. An electric bulb rated for 500 watts at 100 volts is used in a circuit having a 200 volts supply. The resistance R that must be put in series with the bulb, so that the bulb delivers 500 watt isohm.

A. 10Ω

B. 20Ω

C. 50Ω

D. $100\Omega_s$

Answer: B



Watch Video Solution

32. Two electric bulbs A and B are designed for the same voltage. Their power ratings are P_A and P_B respectively with $P_A > P_B$. If they are joined in series across V voltage supply

A. A will draw more power than B

B. B will draw more power than A

C. the ratio of powers drawn by them will depend on V

D. A and B will draw the same power

Answer: B



Watch Video Solution

33. n identical light bulbs, each designed to draw P power from a certain voltage supply, are joined in series across that supply. The total power which they will draw is

A. nP

B. P

C. P/n

D. P/n^2

Answer: C::D



Watch Video Solution

34. When a $500 - W$ electric and a $500 - W$ heater operate at their rates voltages, the filament of the bulb reaches a much higher

temperature than the filament of the heater.

The most important reason for this that

A. their resistances are not equal

B. they are made of different materials

C. their dimensions are very different

D. they radiate different powers at
different temperatures

Answer: C::D



Watch Video Solution

35. A $100W$ bulb and a $25W$ bulb are designed for the same voltage. They have filaments of the same length and material. The ratio of the diameter of $100W$ bulb to that of the $25W$ bulb is

A. 4:1

B. 2:1

C. $\sqrt{2}:1$

D. 1:2

Answer: B



Watch Video Solution

36. If the length of the filament of a heater is reduced by 10 % , the power of the heater will




- A. increase by about 9 %
- B. increase by about 11 %
- C. increase by about 19 %
- D. decrease by about 10 %


Answer: B



Watch Video Solution

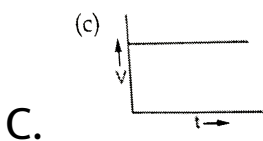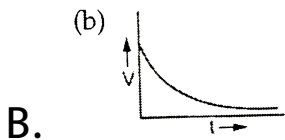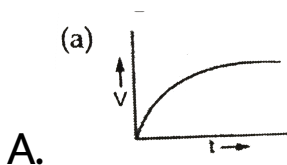37. An ideal cell is connected to a capacitor through a voltmeter. The reading V of the voltmeter is plotted against time. Which of the following best represents the resulting curve?



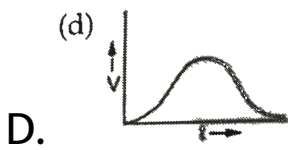


Answer: B



Watch Video Solution

38. In the circuit shown in fig. when the switch is closed, the capacitor charges with a time

constant

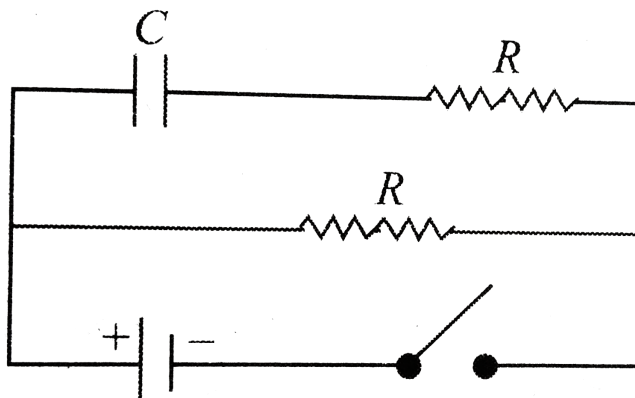

A. RC

B. $2RC$

C. $\frac{1}{2}RC$

D. $RC \ln 2$

Answer: A



Watch Video Solution

39. A capacitor is charged and then made to discharged through a resistance. The time constant is τ . In what time will the potential difference across the capacitor decreases by 10 % ?

A. $\tau \ln(0.1)$

B. $\tau \ln(0.9)$

C. $\tau \ln(10/9)$

D. $\tau \ln(11/10)$

Answer: C



Watch Video Solution

40. A capacitor charges from a cell through a resistance. The time constant is τ . In what time will the capacitor collect 10 % of the final charge?

A. $\tau \ln(0.1)$

B. $\tau \ln(0.9)$

C. $\tau \ln(10/9)$

$$D. \tau \ln(11/10)$$

Answer: C



Watch Video Solution

41. A capacitor of capacitance C has charge Q . it is connected to an identical capacitor through a resistance. The heat produced in the resistance is

A. $\frac{Q^2}{2C}$

B. $\frac{Q^2}{4C}$

C. $\frac{Q^2}{8C}$

D. dependent on the value of the resistance

Answer: B



Watch Video Solution

42. The charge on a capacitor decrease η time in time t , when it discharging through a circuit with a time constant τ

A. $t = \eta\tau$

B. $t = \tau \ln \eta$


C. $t = \tau(\ln \eta - 1)$

D. $t = \tau \ln \left(1 - \frac{1}{\eta}\right)$

Answer: B



Watch Video Solution

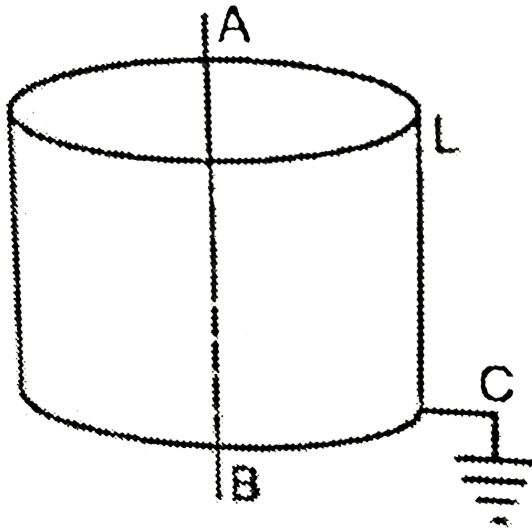

43.

A straight conductor AB lies along the axis of a hollow metal cylinder L , which is connected to earth through a conductor C . A quantity of charge will flow through C

A. if a current begins to flow through AB

B. if the current through AB is reversed


C. if AB is removed, and a beam of electrons flows in its place

D. if AB is removed, and a beam of protons flows in its place

Answer: C::D



Watch Video Solution

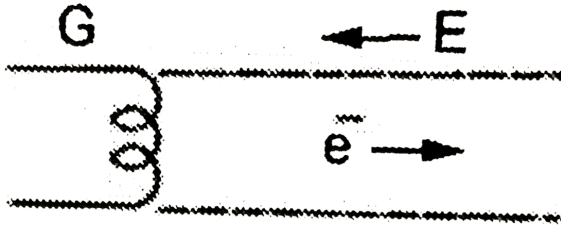

44.

A beam of electrons emitted from the electron gun G is accelerated by an electric field E . The area of cross-section of the beam remains constant. As the beam moves away from G

A. the speed of the electrons increases

B. the current constituted by the beam
increases

C. the number of electrons per unit volume
in the beam increases

D. the number of electrons per unit volume
in the beam decreases

Answer: A::D



Watch Video Solution

45. The charge flowing in a conductor varies with times as $Q = at - bt^2$. Then, the current

A. decreases linearly with time

B. reaches a maximum and then decreases

C. falls to zero after a time period $t = \frac{a}{2b}$

D. change at a rate $-2b$

Answer: A::C::D



Watch Video Solution

46. The charge flowing in a conductor varies time as,

$$q = at - \frac{1}{2}bt^2 + \frac{1}{6}ct^3$$

Where a, b, c are positive constants. Then, find
(i) the initial current (ii) the time after which
the value of current reaches a maximum value
(iii) the maximum or minimum value of
current.

A. has an initial value $i = a$

B. reaches a minimum value after a time
period $t = b/c$

C. reaches a maximum value after a time
period $t = b/c$

D. has either a maximum or a minimum

$$\text{value } i = a - \frac{b^2}{2c}$$


Answer: A::B::D



Watch Video Solution

47. When some potential difference is maintained between A and B, current I enters

the network at A and leaves at B

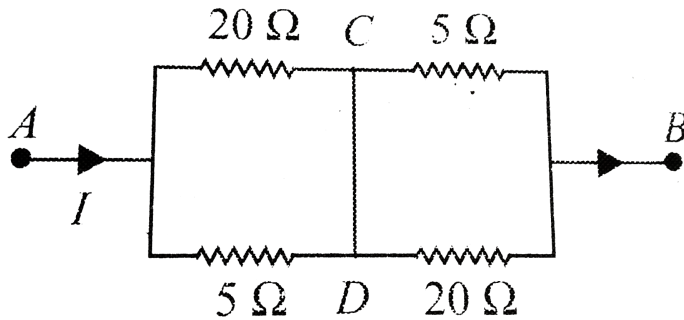


- A. The equivalent resistance between A and B is $8\ \Omega$
- B. C and D are at the same potential.
- C. No current flows between C and D
- D. Current $3I/5$ flows from D to C

Answer: A::B::D



Watch Video Solution

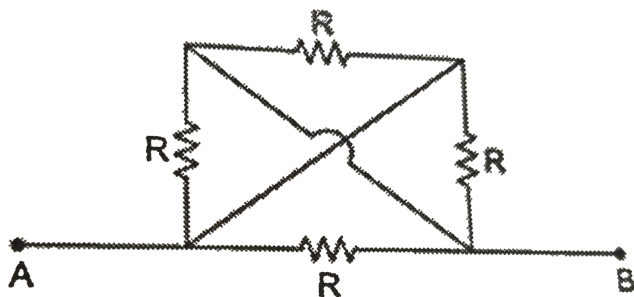

48.

In the circuit shown above, each of the four conductors is of resistance R . The potential difference between A and B is V . The current flowing between A and B is

A. $\frac{V}{R}$


B. $\frac{2V}{R}$

C. $\frac{3V}{R}$

D. $\frac{4V}{R}$

Answer: D

 **Watch Video Solution**

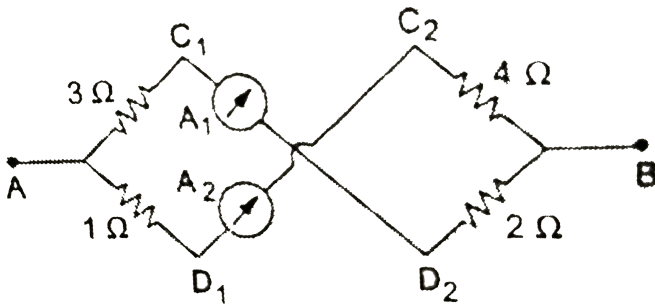

49.

In the circuit shown above, A_1 and A_2 are

ammeters of resistance 5Ω each. When an ideal cell of emf $10V$ is applied between A and B

A. the current drawn from the cell is $1A$

B. the reading of A_1 is $1A$

C. the reading of A_2 is $1A$


D. if C_1 is joined to C_2 and D_1 is joined to

D_2 , the ammeter readings will become equal

Answer: B::C::D



Watch Video Solution

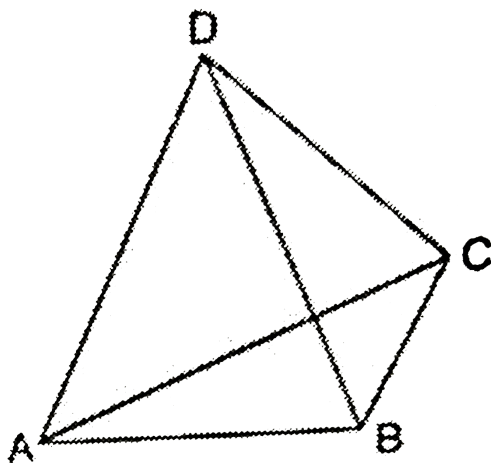

50.


Six identical wires of resistance R each are joined to form a pyramid, as shown in the figure above

- A. The equivalent resistance between any two corners will depend on the choice of corners
- B. The equivalent resistance between A and B is $R/2$
- C. The equivalent resistance between D and C is zero
- D. If an electric current enters at A and flows out at B , no current will pass through DC .

Answer: B::D



Watch Video Solution

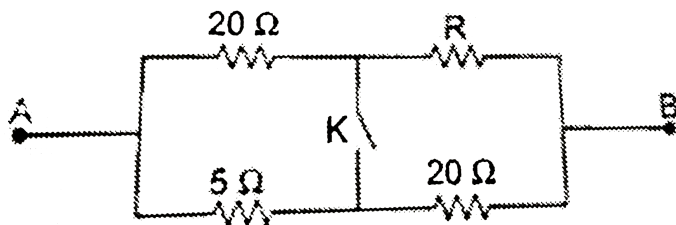

51.

When the switch K is open, the equivalent resistance between A and B is $20\ \Omega$. Then, which is the correct statement?

A. $R = 80\ \Omega$

B. No current flows through K when its closed.

C. The powers dissipated in R and in the $5 - \Omega$ resistor are always equal.


D. The power dissipated in the two $20 - \Omega$ resistors are unequal

Answer: A::B::C::D



Watch Video Solution

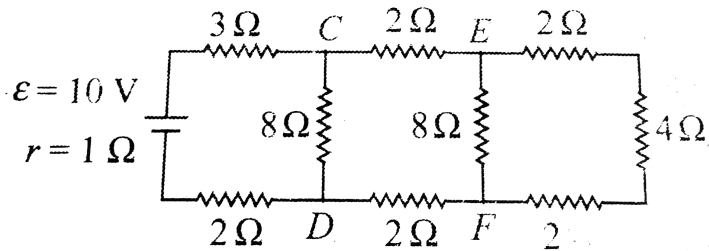52. In the circuit shown in fig. the cell has emf 10V and internal resistance 1Ω



A. The current through the $3 - \Omega_s$ resistor

is 1A .

B. The current though the $3 - Q$ resistor is

0.5A

C. The current through the $4 - \Omega$ resistor
is $0.5A$

D. The current through the $4 - \Omega$ resistor
is $0.25A$


Answer: A::D



Watch Video Solution

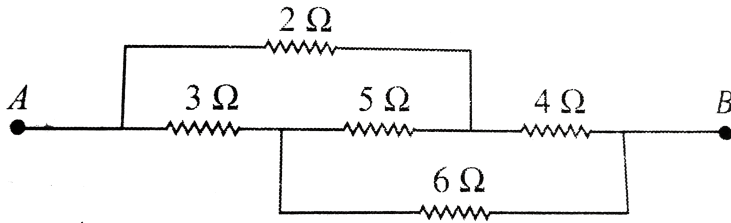53. In the circuit shown in fig. some potential difference is applied between A and B. The

equivalent resistance between A and B is R.



A. No current flows through the $5 - \Omega$ resistor

B. $R = 15\Omega$

C. $R = 12.5\Omega$

D. $R = \frac{18}{5}\Omega$

Answer: A::D



Watch Video Solution

54. A uniform wire of resistance R is shaped into a regular n – sided polygon (n is even), The equivalent resistance between any two corners can have.

(i) the maximum value $\frac{R}{4}$

(ii) the minimum value $\frac{R}{n}$

(iii) the minimum value $R\left(\frac{n-1}{n^2}\right)$

(iv) the minimum value $\frac{R}{n}$.

A. the maximum value $\frac{R}{4}$

B. the maximum value $\frac{R}{n}$

C. the minimum value $R \left(\frac{n-1}{n^2} \right)$

D. the minimum value $\frac{R}{n}$


Answer: A::C



Watch Video Solution

55. In the circuit shown in fig. the cell is ideal with emf 15V. Each resistance is of 3Ω . The potential difference across the capacitor in

steady state is

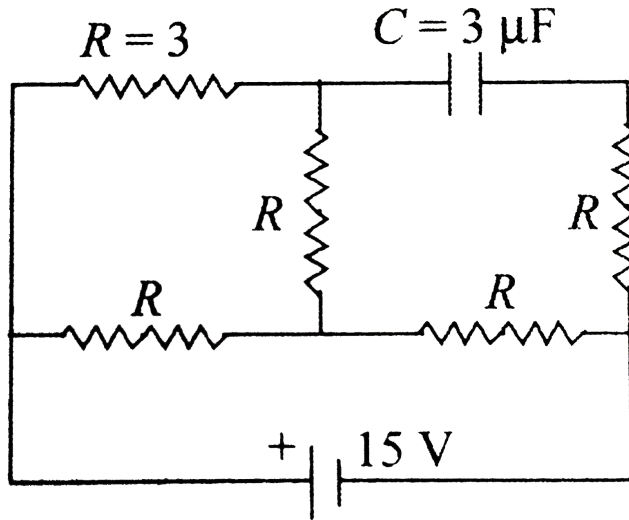

A. zero

B. $9V$

C. $12V$


D. $15V$

Answer: C



Watch Video Solution

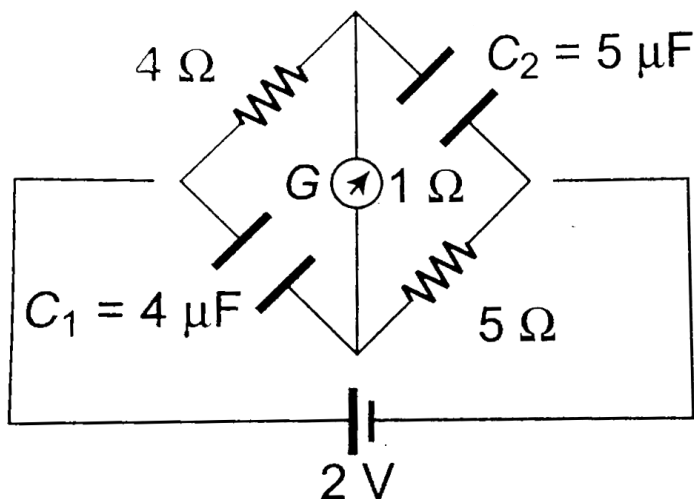56. In the circuit shown, the cell is ideal with $\text{emf} = 2V$. The resistance of the coil of the galvanometer G is 1Ω .



(i) No current flows in G

(ii) $0.2A$ current flows in G

(iii) potential difference across C_1 is $1V$

(iv) Potential difference across C_2 is $1.2V$

A. No current flows in G

B. $0.2 - A$ current flows in G


C. Potential difference across C_1 is $1V$

D. Potential difference across C_2 is $1.2V$.

Answer: B::C::D



Watch Video Solution

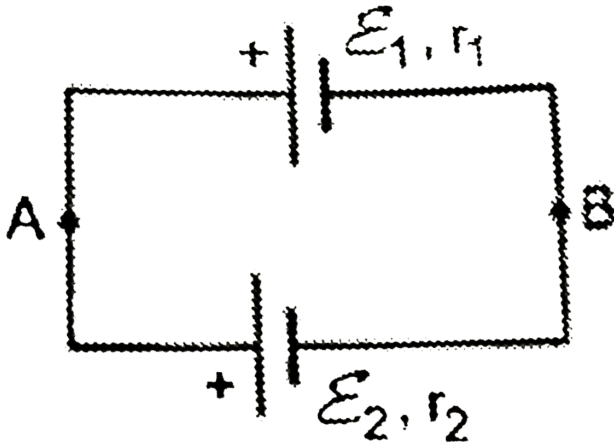

57.

Two cells of unequal emfs, \mathcal{E}_1 and \mathcal{E}_2 and internal resistances r_1 and r_2 are joined as shown. V_A and V_B are the potentials at A and B respectively.

A. Once cell wil continuously suply energy to the other.

B. The potential difference across both the cells will be equal.

C. The potential difference across one cell will be greater than its emf.


D.
$$V_A - V_B = \frac{(\mathcal{E}_1 r_2 + \mathcal{E}_2 r_1)}{(r_1 + r_2)}$$

Answer: A::B::C::D



Watch Video Solution

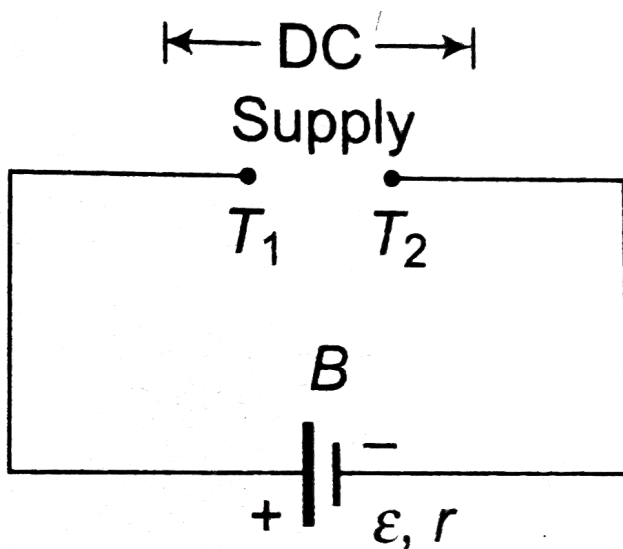58. An accumulator battery (storage cell) B of emf ε and internal resistance r is being charged from DC supply whose terminals are T_1 and T_2



A. Potential difference between T_1 and T_2

must be $> \varepsilon$

B. T_1 must be positive with respect to T_2

C. in the battery, current flows from the positive to the negative terminal.

D. All the above options are incorrect.

Answer: A::B::C



Watch Video Solution

59. A voltmeter and an ammeter are connected in series to an ideal cell of $emf E$. The voltmeter reading is V , and the ammeter

readings is I . Then

- (i) $V < E$
- (ii) the voltmeter resistance is V / I
- (iii) the potential difference across the ammeter is $E - V$
- (iv) Voltmeter resistance + ammeter resistance = E / I

Correct statements are

A. $V < \varepsilon$

B. The voltmeter resistance is V / I

C. The potential difference across the ammeter is $(\varepsilon - V)$

D. Voltmeter resistance plus ammeter

$$\text{resistanc} = \varepsilon / I$$


Answer: A::B::C::D



Watch Video Solution

60. A voltmeter of resistance 600Ω when connected in turn across resistances R_1 and R_2 gives readings of V_1 and V_2 , respectively. If

the battery is ideal, then

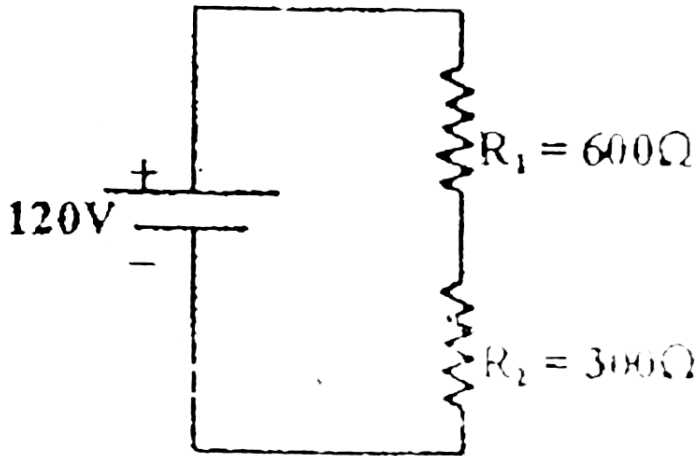

A. $V_1 = 80V$

B. $V_1 = 60V$

C. $V_2 = 30V$

D. $V_2 = 40V$

Answer: B::C



Watch Video Solution

61. A voltmeter and an ammeter are joined, in series to an ideal cell, giving reading V and A respectively. If a resistance equal to the resistance of the ammeter is now joined in parallel to the ammeter then :

- A. V will not change
- B. V will increase slightly

C. A will become exactly half to its initial value

D. A will become slightly more than half of its initial value


Answer: B::D



Watch Video Solution

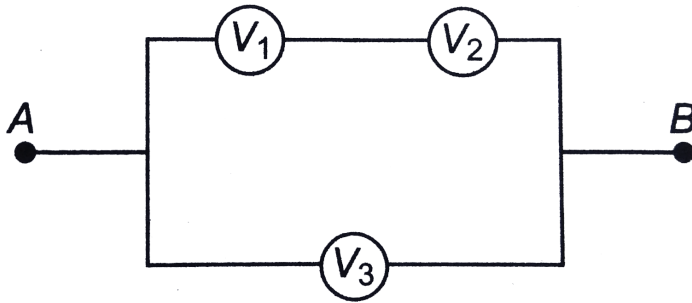62. Three voltmeters all having different resistance, are joined as shown. When some potential difference is applied across A and B ,

their readings are V_1 , V_2 and V_3 . Then



A. $V_1 = V_2$

B. $V_1 \neq V_2$

C. $V_1 + V_2 = V_3$


D. $V_1 + V_2 = V_3$

Answer: B::C



Watch Video Solution

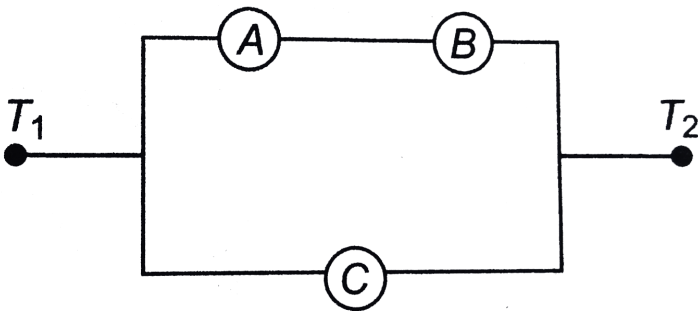63. Three ammeters A , B , and C of resistances R_A , R_b and R_C respectively are joined as shown. When some potential difference is applied across the terminals T_1 and T_2 their readings are I_A , I_B and I_C respectively Then,



A. $I_A = I_B$

$$\text{B. } I_A R_A + I_B R_B = I_C R_C$$

$$\text{C. } \frac{I_A}{I_C} = \frac{R_C}{R_A}$$

$$\text{D. } \frac{I_B}{I_C} = \frac{R_C}{R_A + R_B}$$

Answer: A::B::D



Watch Video Solution

64. A microammeter has a resistance of 100ω and a full scale range of $50\mu A$. It can be used as a voltmeter or as a higher range ammeter

provides a resistance is added to it . Pick the correct range and resistance combination(s)

A. Range $50V$, with a $10 - k\Omega$ resistance in series

B. Range $10V$, with a $(2 \times 10^5 - 100) - \Omega$ resistance in series

C. Range $5mA$, with $1.01 - \Omega$ resistance in parallel

D. Range $10mA$, with a $1 - \Omega$ resistance in parallel


Answer: B::C



Watch Video Solution

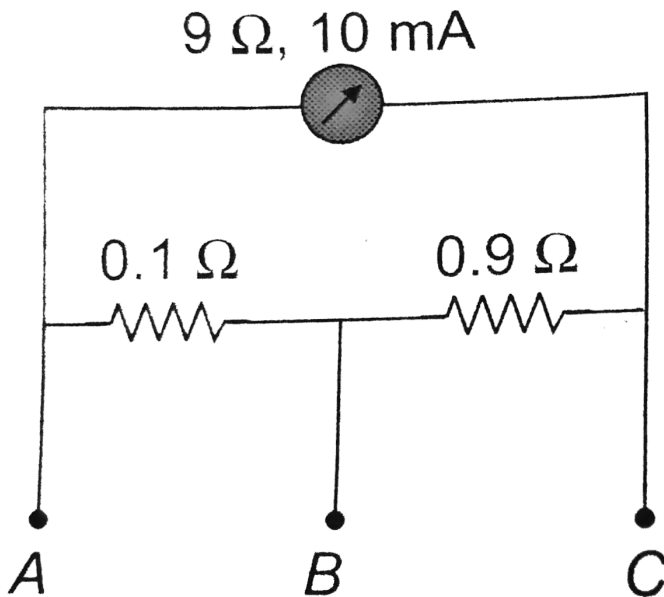65. A milliammeter of range $10mA$ and resistance 9Ω is joined in a circuit as shown. The metre gives full-scale deflection for current I when A and B are used as its terminals, i.e., current enters at A and leaves

at B (C is left isolated). The value if I is



A. $100\ \text{mA}$

B. $900\ \text{mA}$


C. $1\ \text{A}$

D. $1.1\ \text{A}$

Answer: C



Watch Video Solution

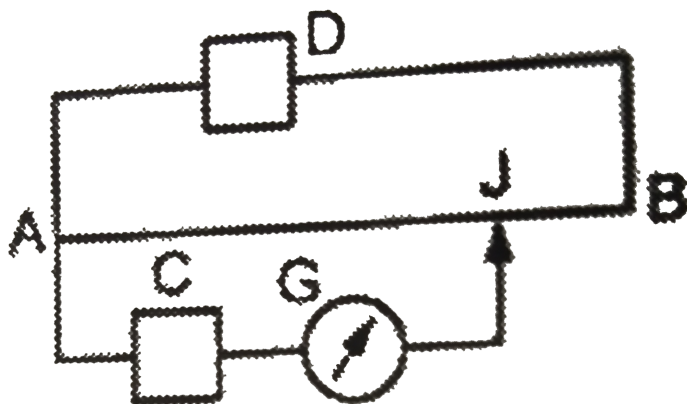

66.

The figure shows a potentiometer arrangement. D is the driving cell. C is the cell whose emf is to be determined. AB is the

potentiometer wire and G is a galvanometer.

J is a sliding contact which can touch any point on AB . Which of the following are essential conditions for obtaining balance?

A. The emf of D must be greater than the emf of C

B. Either the positive terminals of both D and C or the negative terminals of both D and C must be joined to A .

C. The positive terminals of D and C must be joined to A

D. The resistance of G must be less than the resistance of AB


Answer: A::B



View Text Solution

67. In the potentiometer arrangement shown, the driving cell A has emf ε and internal resistance r . The emf of the cell B is $\frac{\varepsilon}{2}$ and internal resistance $2r$. The potentiometer wire CD is 100cm long. If balance is obtained with

length $CJ = l$, then

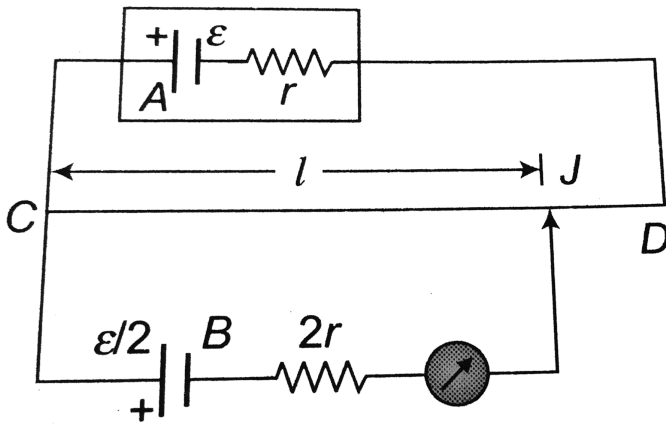

A. $l = 50\text{cm}$

B. $l > 50\text{cm}$

C. Balance will be obtained only if

resistance of AB is $> r$

D. Balance cannot be obtained.

Answer: B::C



Watch Video Solution

68. A cell drives a current through a circuit. The emf of the cell is equal to the work done in moving unit charge (Choose the incorrect option)

A. from the positive to the negative plate of the cell

B. from the positive plate, back to the positive plate

C. from the negative plate, back to the negative plate

D. from any point in the circuit back to the same point

Answer: B::C::D



Watch Video Solution

69. A cell of emf ε and internal resistance r drives a current i through an external resistance R

(i) The cell supplied εi power

(ii) Heat is produced in R at the rate εi

(iii) Heat is produced in R at the rate

$$\varepsilon I \left(\frac{R}{R + r} \right)$$

(iv) Heat is produced in the cell at the rate

$$\varepsilon i \left(\left(r \frac{?}{R + r} \right) \right)$$

A. The cell supplies εi power

B. Heat is produced in R at the rate ε

C. Heat is produced in R at the rate

$$\varepsilon i \left(\frac{R}{R + r} \right)$$

D. Heat is produced in the cell at the rate


$$\varepsilon i \left(\frac{r}{R + r} \right)$$

Answer: A::C::D



Watch Video Solution

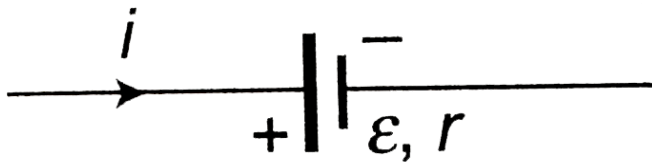70. Current i is being driven through a cell of emf ε and internal resistance r , as shown



(i) the cell absorbs energy at rate of ϵi

(ii) The cell stores chemical energy at the rate of $(\epsilon i - i^2 r)$

(iii) The potential difference across the cell is $\epsilon + ir$

(iv) some heat is produced in the cell

A. The cell absorbs energy at the rate of ϵi

B. The cell stores chemical energy at the rate of $(\epsilon i - i^2 r)$

C. The potential difference across the cell is

$$\mathcal{E} + ir$$

D. Some heat is produced in the cell.

Answer: A::B::C::D



Watch Video Solution

71. Two electric bulbs rated $25W, 220V$ and $100W, 220V$ are connected in series across a $220V$ voltage source . The

25W and 100W bulbs now draw P_1 and P_2 powers , respectively.

A. $P_1 = 16W$

B. $P_1 = 4W$

C. $P_2 = 16W$

D. $P_2 = 4W$

Answer: A::D



Watch Video Solution

72. Two heaters designed for the same voltage V have different power ratings. When connected individually across a source of voltage V , they produce H amount of heat each in time t_1 and t_2 respectively. When used together across the same source, they produce H amount of heat in time t

A. If they are in series $t = t_1 + t_2$

B. If they are in series $t = 2(t_1 + t_2)$

C. If they are in parallel $t = \frac{t_1 t_2}{(t_1 + t_2)}$

D. If they are in parallel $t = \frac{t_1 t_2}{2(t_1 + t_2)}$

Answer: A::C



Watch Video Solution

73. In a household electric circuit,

A. all electric appliances drawing power are

joined in parallel

B. a switch may be either in series or in

parallel with the appliance which it

controls

C. if a switch is in parallel with an appliance

it will draw power when the switch is in

the 'off' position (open)

D. if a switch is in parallel with an

appliance, the fuse will blow (burn out)

when the switch is put 'on' (closed)

Answer: A::C::D



View Text Solution

74. Two identical fuses are rated at $10A$. If they are joined

A. in parallel, the combination acts as a fuse of rating $20A$

B. in parallel the combination acts as a fuse of rating $5A$

C. in series, the combination acts as a fuse of rating $10A$

D. in series, the combination acts as a fuse of rating $20A$

Answer: A::C



Watch Video Solution

75. The charge flowing through a resistance R varies with time $tasQ = at - bt^2$. The total heat produced in R is

A. $\frac{a^3 R}{6b}$

B. $\frac{a^3 R}{3b}$

C. $\frac{a^3 R}{2b}$


D. $\frac{a^3 R}{b}$

Answer: A



Watch Video Solution

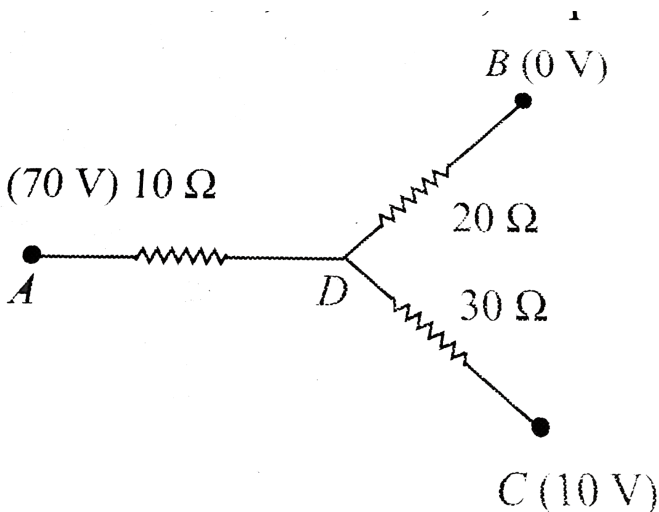76. In the network shown in fig. , points A, B, and C are at potentials of 70 V, 0, and 10V, respectively.



A. Point D is at a potential of $40V$.

B. The currents in the sections

AD, DB, DC are in the ratio $3:2:1$

C. The currents in the sections

AD, DB, DC are in the ratio $1:2:3$

D. The network draws a total power of

$200W$

Answer: A::B::D



Watch Video Solution

77. Two identical capacitors A and B are charged to the same potential and then made to discharge through resistance R_A and R_B respectively with $R_A > R_B$

A. A will require greater time than B to discharge completely

B. More heat will be produced in A than in B

C. More heat will be produced in B than in A

D. All the above options are incorrect.


Answer: D



Watch Video Solution

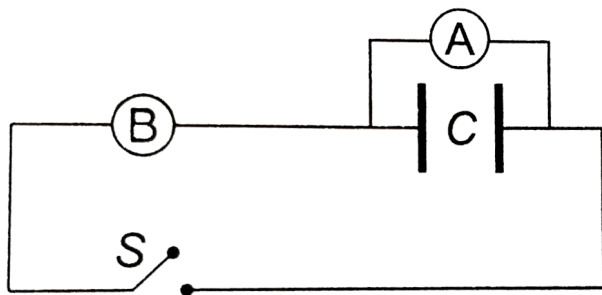78. a capacitor of capacitance C is connected to two voltmeter A and B . A is ideal , having infinite resistance, while B has resistance R . The capacitor is charged and then switch S is

closed. The reading of A and B will be equal



A. at all times

B. after time RC

C. after time $RC \ln 2$


D. only after a very long time

Answer: A



Watch Video Solution

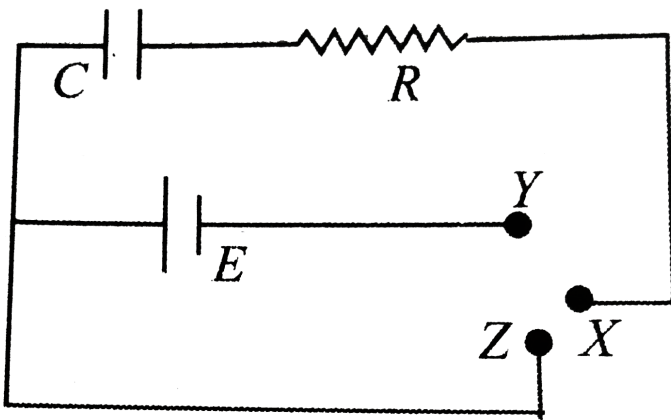79. The capacitor C is initially without charge. X is now joined to Y for a long time, during which H_1 heat is produced in the resistance R . X is now joined to Z for a long time, during which H_2 heat is produced in R



A. $H_1 = H_2$

B. $H_1 = \frac{1}{2}H_2$


C. $H_1 = 2H_2$

D. The maximum energy stored in C at any time is H_1

Answer: A::D



Watch Video Solution

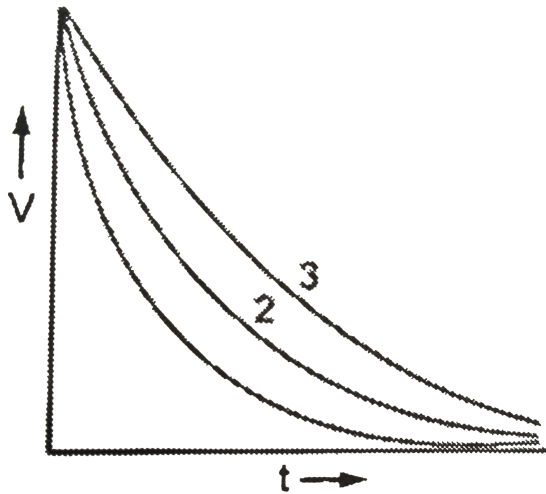

80.

Three identical capacitors A , B and C are charged to the same potential and then made to discharge through three resistances R_A , R_B and R_C , where $R_A > R_B > R_C$. Their potential differences (V) are plotted against time t giving the curves 1, 2, and 3. Find the correlations between A , B , C and 1, 2, 3

A. $1 \rightarrow A$

B. $2 \rightarrow B$

C. $1 \rightarrow C$

D. $3 \rightarrow A$





Answer: B::C::D



View Text Solution

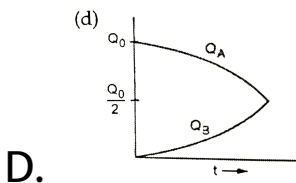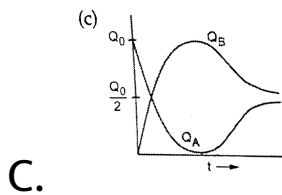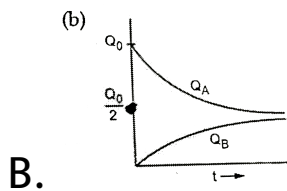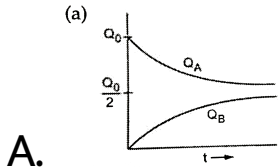81. A capacitor A with charge Q_0 is connected through a resistance to another identical capacitor B , which has no charge. The charges

on A and B after time t are Q_A and Q_B respectively, and they are plotted against time t . Find the correct curves



Answer: A



View Text Solution

82. A parallel- plate capacitor, filled with a dielectric of dielectric constant k , is charged to a potential V_0 . It is now disconnected from the cell and the slab is removed. If it now discharges, with time constant τ , through a resistance then find time after which the potential difference across it will be $V_0/2$?

A. $k\tau$

B. $\tau \ln k$

C. $\tau \ln \left(1 - \frac{1}{k} \right)$

D. $\tau \ln(k - 1)$

Answer: B



Watch Video Solution

83. When a capacitor discharges through a resistance R , the time constant is τ and the maximum current in the circuit is i_0

A. The initial charge on the capacitor was

$$i_0\tau$$

B. The initial charge on the capacitor was

$$\frac{1}{2}i_0\tau$$

C. The initial energy stored in the capacitor

was $i_0^2\tau$

D. The initial energy stored in the capacitor


was $\frac{1}{2}i_0^2R\tau$

Answer: A::D



View Text Solution

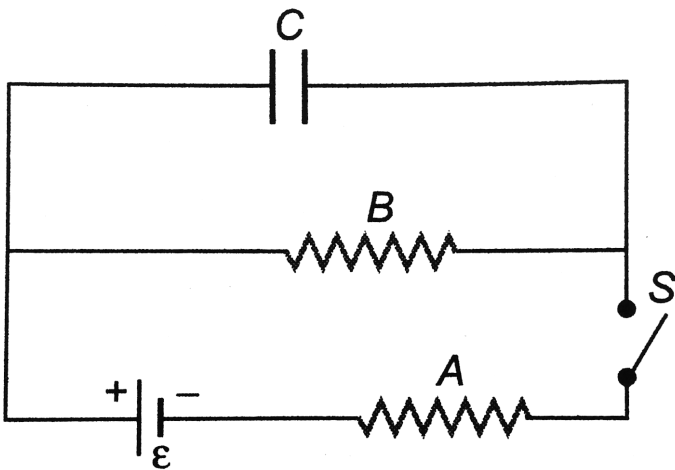84. In the circuit shown, A and B are equal resistances. When S is closed, the capacitor C charges from the cell of emf ϵ and reaches a steady state.



- A. During charging more heat is produced in A and B
- B. In the steady state, heat is produced at the same rate in A and B
- C. In the steady state, energy stored in C is
- $$\frac{1}{4} C \mathcal{E}^2$$
- D. In the steady state, energy stored in C is

$$\frac{1}{8} C \mathcal{E}^2$$

Answer: A::B::D



Watch Video Solution

85. Capacitors $C_1 = 1\mu F$ and $C_2 = 2\mu F$ are separately charged from the same battery. They are allowed to discharge separately through equal resistors

A. The currents in the two discharging circuits at $t = 0$ is zero

B. The currents in the two discharging circuits at $t = 0$ are equal but not zero.

C. The currents in the two discharging circuits at $t = 0$ are unequal.

D. C_1 loses 50% of its initial charge sooner than C_2 loses 50% of its initial charge.

Answer: C::D



Watch Video Solution