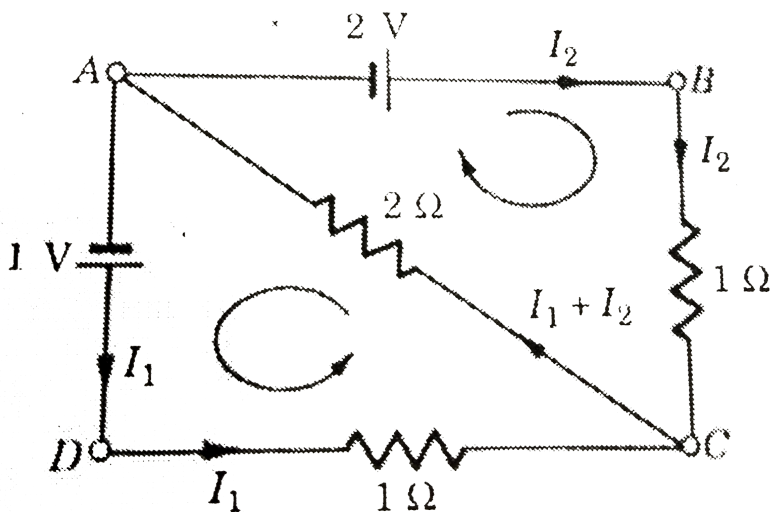


## PHYSICS

### BOOKS - DHANPAT RAI & CO PHYSICS (HINGLISH)

### ELECTRICAL INSTRUMENTS

#### Example




1.

In the circuit shown in figure. Calculate the current in each resistance. The internal resistances of the cells are negligible.

[Watch Video Solution](#)

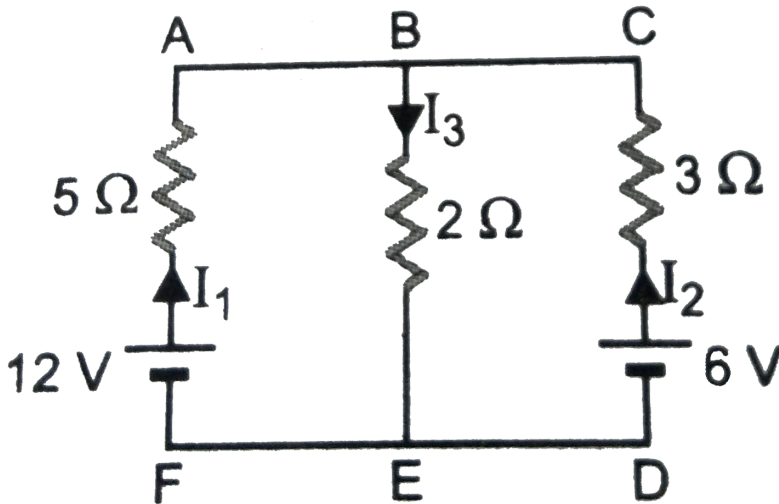2. Using Kirchoff's laws in the electrical net work shown in figure, calculate the values of  $I_1$ ,  $I_2$  and  $I_3$ .




[Watch Video Solution](#)

3. Two cells of emfs 1.5 V and 2.0V internal resistance  $1\Omega$  and  $2\Omega$  are connected in parallel so as to send current in the same direction through an external resistance of  $5\Omega$ .

(i) Draw the circuit diagram. (ii) Using Kirchoff's rules, calculate.

(a) current through each branch of the circuit (b) potential difference across the  $5\Omega$  resistance.

[▶ Watch Video Solution](#)

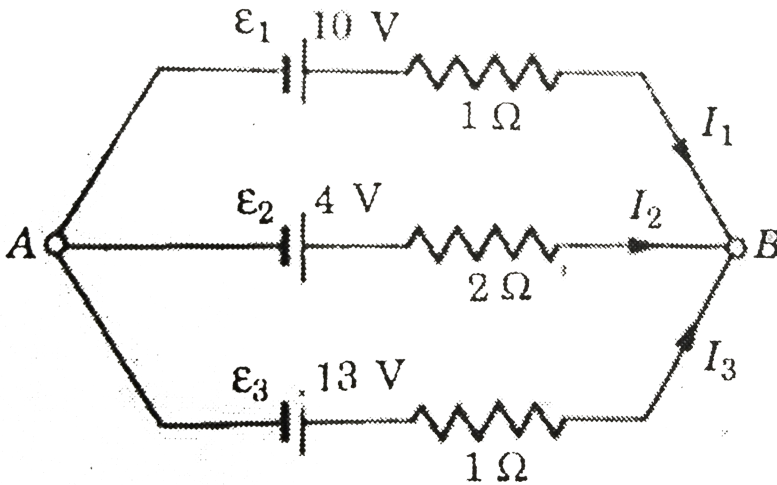


4.

Find the current flowing through each cell in the circuit shown in figure.


Also calculate the potential difference across the terminals of each cell.

[▶ Watch Video Solution](#)

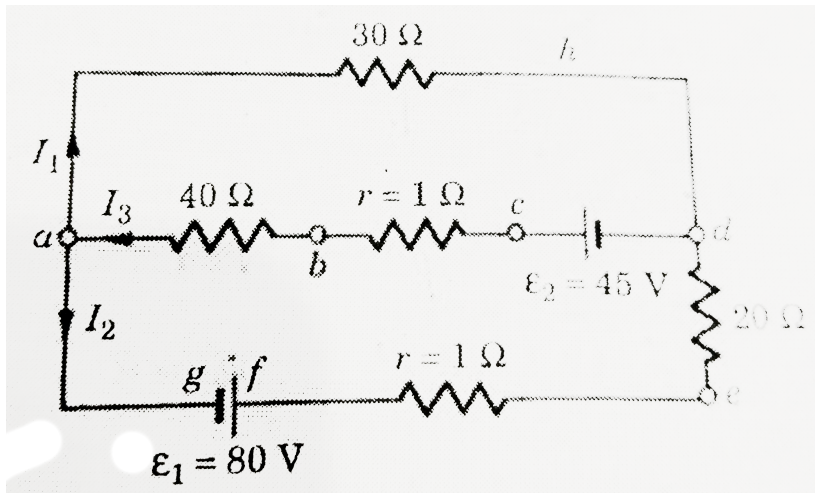


Determine the currents  $I_1$ ,  $I_2$  and  $I_3$  from the network shown in figure.

[▶ Watch Video Solution](#)


6. Determine current in each branch of the network shown in figure 

[▶ Watch Video Solution](#)

7. Determine current in each branch of the network shown in figure 

[▶ Watch Video Solution](#)

8.

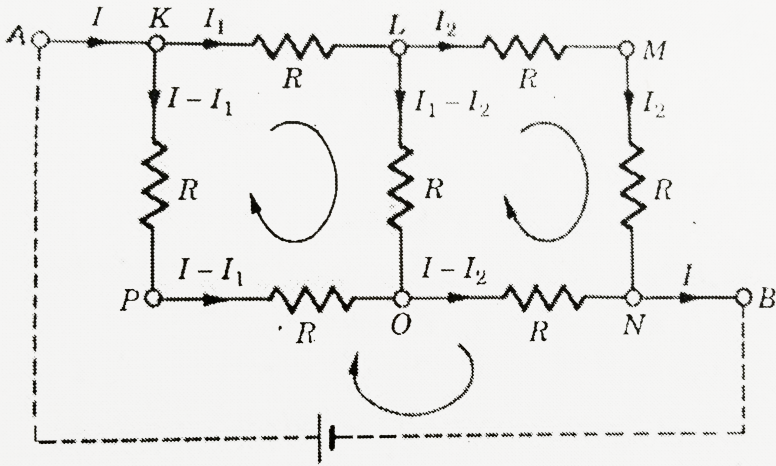

Find the equivalent resistance between the terminals A and B in the network shown figure. Given each resistor  $R$  of  $10\Omega$ .



[▶ Watch Video Solution](#)

9. Two squares ABCD and BEFC have the side BC in common. The sides are of conducting wires with resistances as follows: AB, BE, FC and CD each  $2\Omega$ ; AD, BC, EF each  $1\Omega$ . A cell of e.m.f.  $2V$  and internal resistance  $2\Omega$  is joined across AD. Find the currents in various branches of the circuit.

[▶ Watch Video Solution](#)

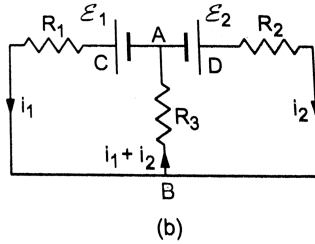
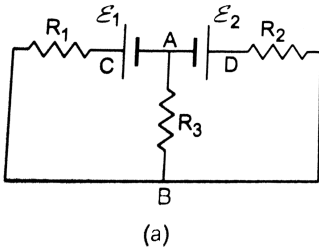
10. Find the currents going through the three resistors

$R_1, R_2$  and  $R_3$  in the circuit of figure.



[▶ Watch Video Solution](#)

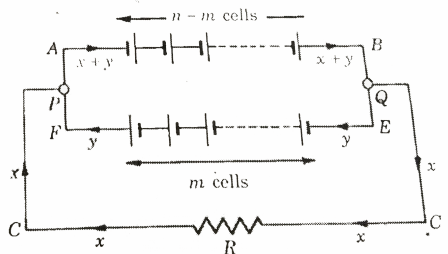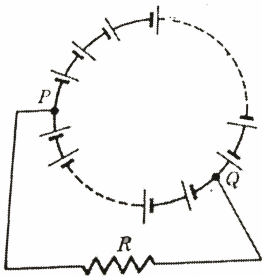11.  $n$  cells, each of emf ' $e$ ' and internal resistance ' $r$ ' are connected in a closed circuit so that the positive terminal of a cell is joined to the negative terminal of the next, as shown in figure. Any two points of the circuit are connected by an external resistance  $R$ . Find the current in  $R$ .



[▶ Watch Video Solution](#)

12. Eleven equal wires each of resistance  $r$  form the edges of a incomplete cube. Find the total resistance from one end of the vacant edge of the cube to the other.



[Watch Video Solution](#)

13. A galvanometer coil has resistance of  $30\Omega$  and the meter shows full scale deflection for the current of  $2.0\text{ mA}$ . Calculate the value of resistance required to convert it into an ammeter of range  $0$  to  $1\text{A}$ . Also calculate the resistance of the ammeter.



[Watch Video Solution](#)

14. A galvanometer with a coil of resistance  $12.0\Omega$  shows full scale deflection for a current of  $25\text{ mA}$ . How will you convert the meter into:


(i). An ammeter of range  $0$  to  $7.5\text{ A}$ .

(b). A voltmeter of range  $0$  to  $10.0\text{ V}$

Determine the net resistance of the meter in each case. when an ammeter is put in a circuit, does it read (slightly) less or more than the actual current in the original circuit? when a voltmeter is put across a part of the circuit, does it read (slightly) less or more than the original voltage drop? Explain.

 [Watch Video Solution](#)

15.

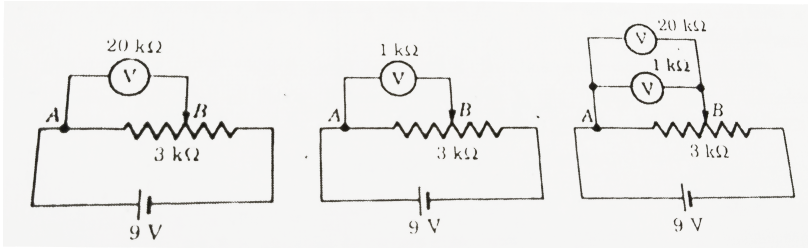


A battery of emf  $9\text{ V}$  and negligible internal resistance is connected to a  $3\text{ k}\Omega$  resistor. The potential drop across a part of the resistor (between points A and B in the figure) is measured by (i) a  $20\text{ k}\Omega$  voltmeter, (ii) a  $1\text{ k}\Omega$  voltmeter. in (iii). both the voltmeter are connected across AB. in which case would you get the (a) highest, (b) lowest reading?

 [Watch Video Solution](#)



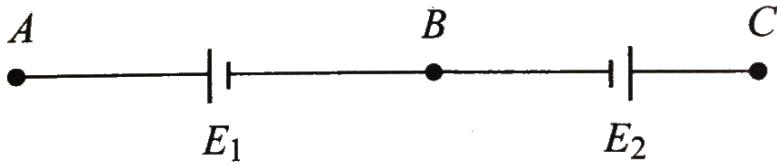16. Two cells of emfs  $E_1$  and  $(E_2(E_1 > E_2))$  are connected as shows in Fig. 6.45.




When a potentiometer is connected between  $A$  and  $B$ , the balancing length of the potentiometer wire is  $300\text{cm}$ . On connecting the same potentiometer between  $A$  and  $C$ , the balancing length is  $100\text{cm}$ . The ratio  $E_1 / E_2$  is

[▶ Watch Video Solution](#)

17. A potentiometer wire is  $100\text{ cm}$  long and a constant potential difference is maintained across it. Two cells of emfs  $\varepsilon_1$  and  $\varepsilon_2$  are connected in series first to support one another and then in opposition. The balance points were obtained at  $60\text{ cm}$  and  $12\text{ cm}$  from the same end of the wire in the two cases. find the ratio of the emfs.

[▶ Watch Video Solution](#)

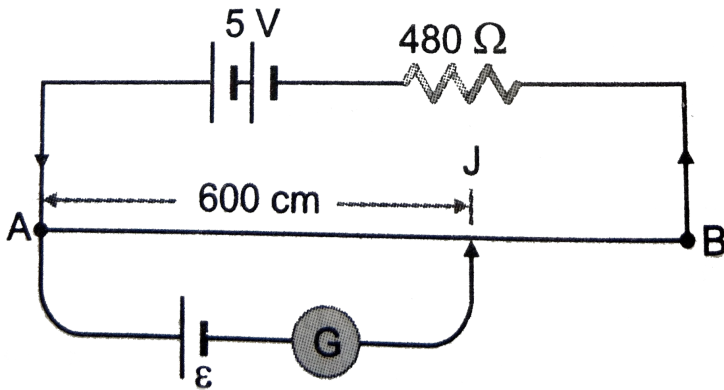
18. A 10 meter long wire of uniform cross section of  $20\Omega$  resistance is used as a potentiometer wire. This wire is connected in series with a battery of  $5V$  along with an external resistance of  $480\Omega$  if an unknown emf  $\varepsilon$  is balanced at  $600\text{cm}$  of this wire, calculate (i) the potential gradient of the potentiometer wire and (ii) the value of the unknown emf  $\varepsilon$ .



[Watch Video Solution](#)

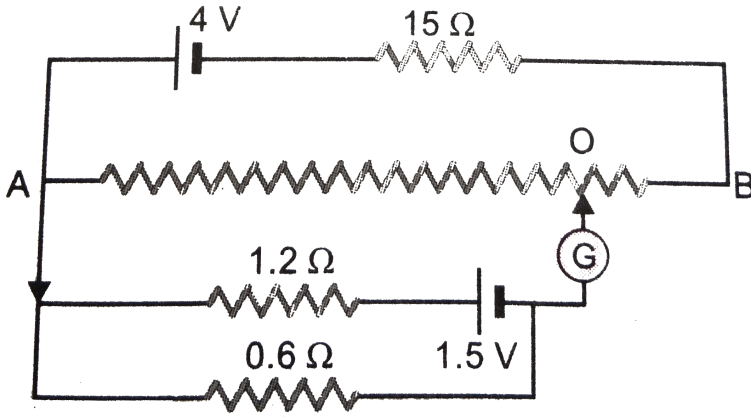19.  $AB$  is 1 meter long uniform wire of  $10\Omega$  resistance. Other data are shown in the diagram. Calculate (i) potential gradient along  $AB$  (ii)

length  $AO$  when galvanometer shown deflection




[Watch Video Solution](#)

20. In an experiment with a potentiometer, the null point is obtained at a distance of  $60\text{cm}$  along the wire from the common terminal with a leclanche cell. When a shunt resistance of  $1\ \Omega$  is connected across the cell, the null point shifts to a distance of  $30\text{cm}$  from the common terminal. what is the internal resistance of the cell?

[Watch Video Solution](#)

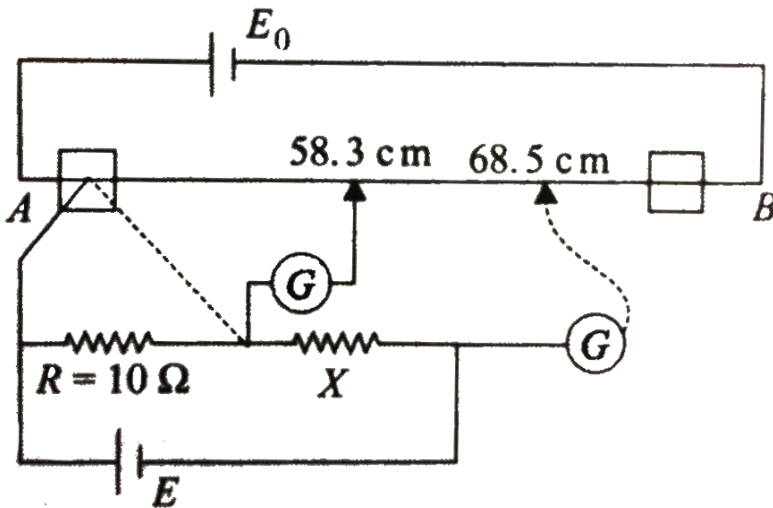21. Figure 6.12 shows a potentiometer circular for comparison of two resistances. The balance point with a standard resistor  $R = 10.0\Omega$  is found to be  $58.3\text{cm}$ , while that with the unknown resistance  $X$  is  $68.5\text{cm}$ . Determine the value of  $X$ . What would you do if you fail to find a balance point with the given cell  $E$ ?




[▶ Watch Video Solution](#)

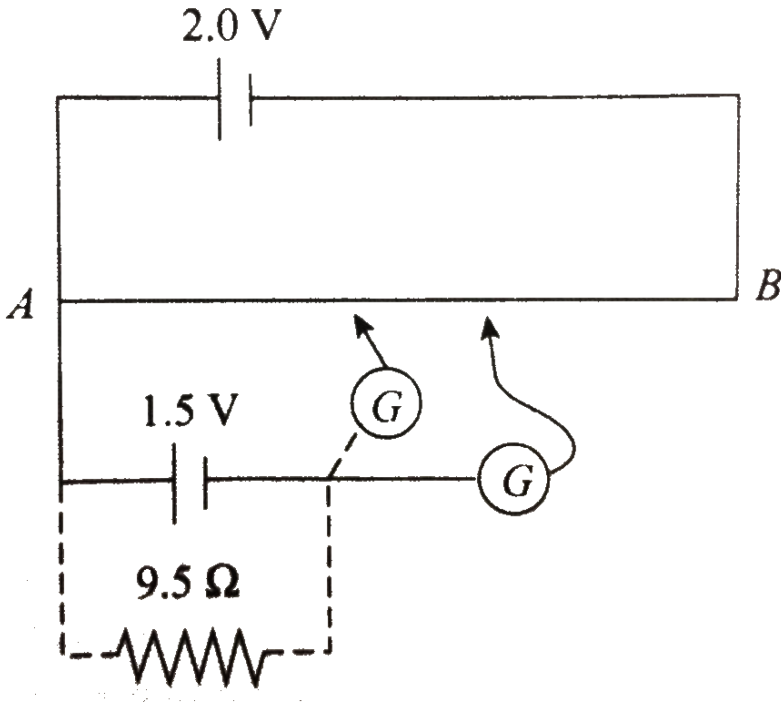22. Figure 6.13 shows a  $2.0\text{V}$  potentiometer used for the determination of internal resistance of a  $1.5\text{V}$  cell. The balance point of the cell in open circuit is  $76.3\text{cm}$ . When a resistor of  $9.5\Omega$  is used in the external circuit of

the cell, the balance point shifts to  $64.8\text{cm}$ , length of the potentiometer.

Determine the internal resistance of the cell.




[▶ Watch Video Solution](#)

23.  $P, Q, R$  and  $S$  are the resistances taken in cyclic order in a wheatstone bridge network.  $P$  and  $Q$  are the ratio coils,  $S$  is unknown resistance and  $R$  is a  $10\ \Omega$  coil. A balance is obtained when  $R$  is shunted with a resistance of  $190\ \Omega$ . When  $P$  and  $Q$  are interchanged, the balance is restored by altering the shunt across  $R$  to  $265\ \Omega$ . find the resistance of  $S$  and the ratio  $P:Q$ ?



Watch Video Solution


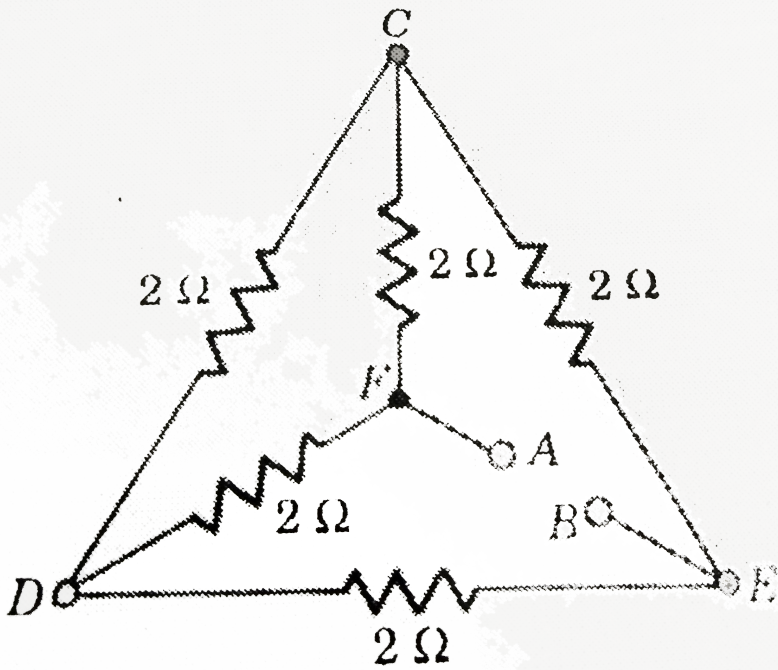


24.

In figure.  $P = 3\Omega$ ,  $Q = 2\Omega$ ,  $R = 6\Omega$ ,  $S = 4\Omega$  and  $X = 5\Omega$ . Calculate the current  $I$ .



Watch Video Solution

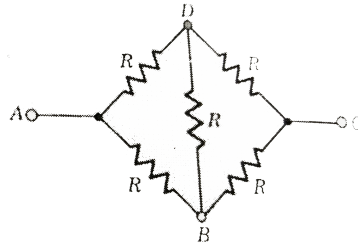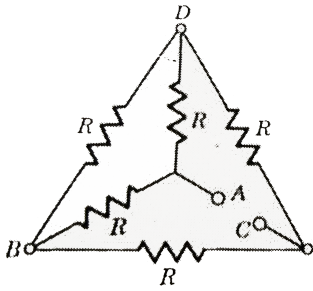

25.

Each of the resistances in the network shown in figure (a) equals  $R$ . find the resistance between two terminals A and C.

[▶ Watch Video Solution](#)

26. 

Each resistor  $r$  shown in figure. Has a resistance of  $10\Omega$  and the battery has an emf of  $6V$ . Find the current supplied by battery.

[▶ Watch Video Solution](#)

27. In the following circuit, a metre bridge is shown in its balanced state. The metre bridge wire has a resistance of  $1\text{ ohm/cm}$ . calculate the value of

the unknown resistance  $X$  and the current drawn from the battery of negligible internal resistance.

 [Watch Video Solution](#)

**28.** An unknown resistance ' $X$ ' is placed in the left gap and a known resistance of  $60\Omega$  is placed in the right gap of metre bridge. The null point is obtained at 40 cm from the left end of the bridge. Find the unknown resistance.

 [Watch Video Solution](#)

**29.** (i) In a metre bridge, the balance point is found to be at 39.5 cm from the end A, when the resistor Y is of  $12.5\Omega$ . Determine the resistance of X.

Made of thick copper strips?


(ii). Determine the balance point of the bridge above if X and Y are interchanged.

(iii). what happens if the galvanometer and cell are interchanged at the balance point of the bridge ? Would the galvanometer show any current?





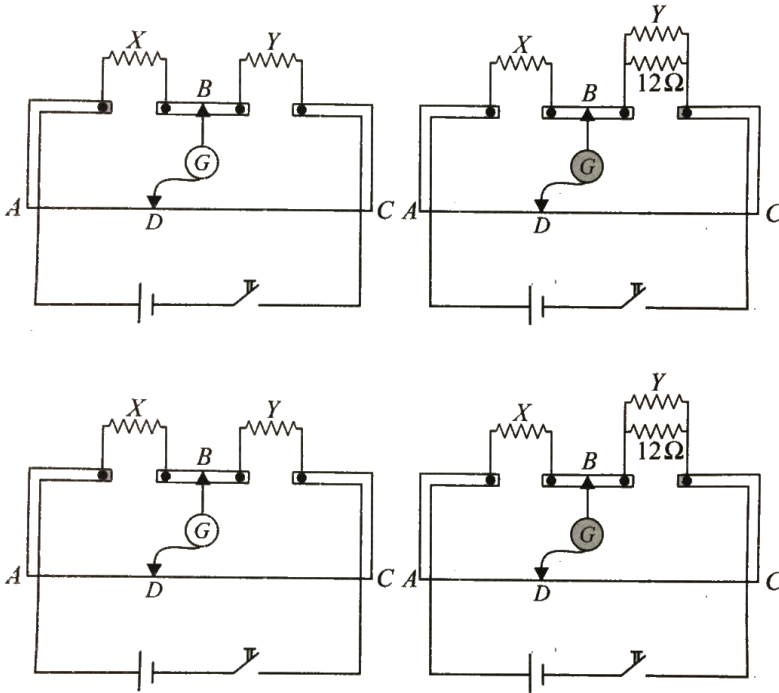30. Figure 6.32 shows a meter bridge in the (which is nothing but a particle wheastone bridge), consisting of two resistors  $X$  and  $Y$  together in pallel with a meter long constantan wire of uniform cross section.



with the help of a movable contact  $d$ , one can change the ratio of resistance of the two segments of the wire until a sensitive galvanometer  $G$  connected across  $b$  and  $D$  shows no deflection. The null point is found to be at a distance of  $33.7\text{cm}$ . The resistor  $Y$  is shunted by a resistance of

$12\Omega$ , and the null point is found to shift by a distance of  $18.2\text{cm}$ .


Determine the resistance of  $X$  and  $Y$ .

 [Watch Video Solution](#)

**31.** In the metre-bridge experiment with unknown resistance  $X$  in the left gap and a known resistance of  $60\Omega$  in the right gap, null point is obtained at  $l$  cm from left. If the unknown resistance  $X$  is shunted by an equal resistance, what should be the value of the known resistance in the right gap in order to get the null point at the same position?.

 [Watch Video Solution](#)

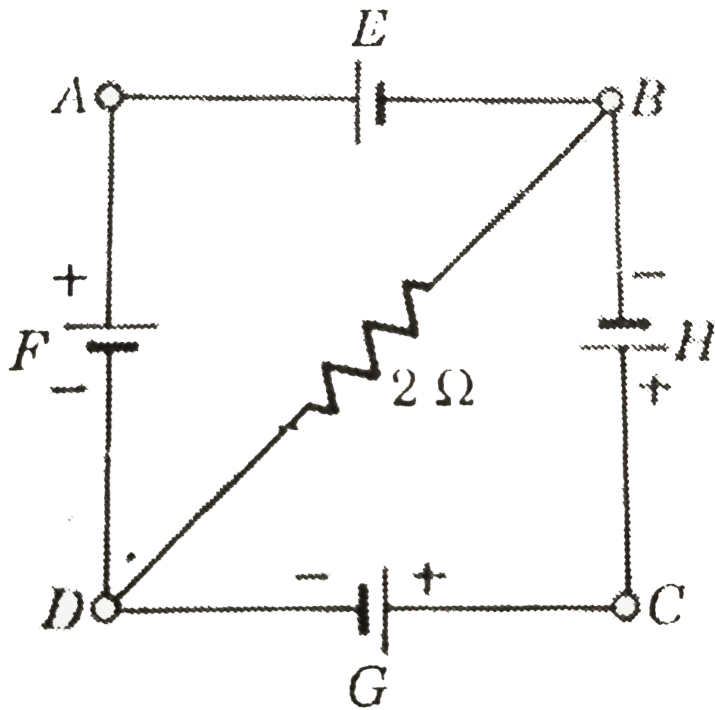
**Problem From Competitive Examinations**



1.

In the circuit shown in figure. The cells  $E, F, G$  and  $H$  have e.m.f's  $2, 1, 3$  and  $1$  V and internal resistance  $2, 1, 3$  and  $1\ \Omega$  respectively. Find the potential differences between points  $B$  and  $D$ , and across the terminals of the cells


G and H.

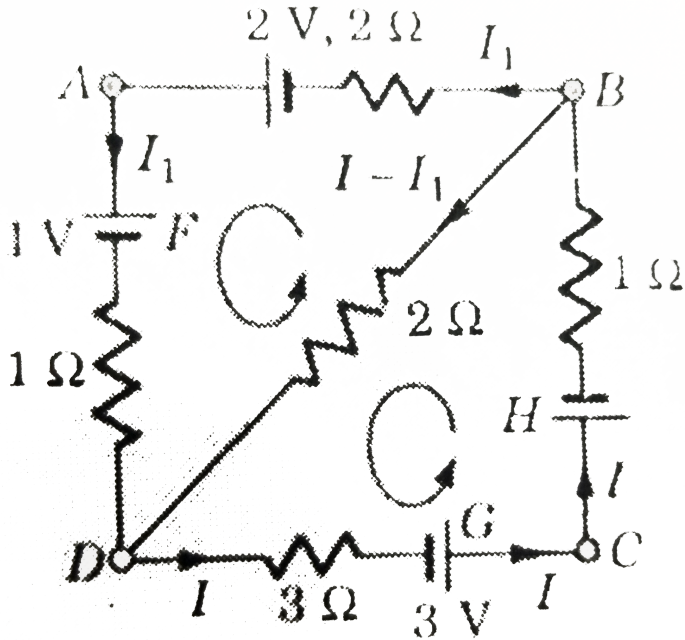

Watch Video Solution

2. In the circuit in figure  $E_1 = 3V$ ,  $E_2 = 2V$ ,  $E_3 = 1V$  and

$$R = r_1 - r_2 - r_3 = 1\Omega$$

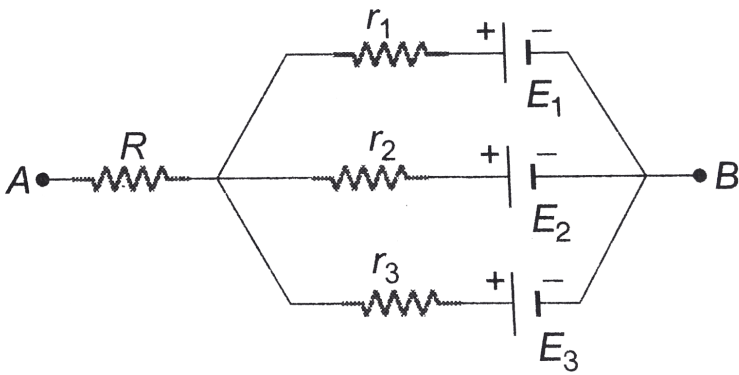

- Find the potential difference between the points  $A$  and  $B$  and the currents through each branch.
- If  $r_2$  is short circuited and the point  $A$  is connected to point  $B$ , find the currents through  $E_1$ ,  $E_2$ ,  $E_3$  and the resistor  $R$

[▶ Watch Video Solution](#)

3. 

A part of the circuit in a steady state along with the currents flowing in the branches, the values of resistance, etc. is shown in the figure. Calculate the energy stored in the capacitor.

[▶ Watch Video Solution](#)

4. 


In the circuit shown in figure.

$\varepsilon_1 = 3, \varepsilon_2 = 2, \varepsilon_3 = 6V, R_1 = 2, R_4 = 6\Omega, R_3 = 2, R_2 = 4\Omega$  and  $C = 5\mu$

. Find the current in the resistor  $R_3$  and the electrical energy stored in the capacitor C.

 **Watch Video Solution**

5.

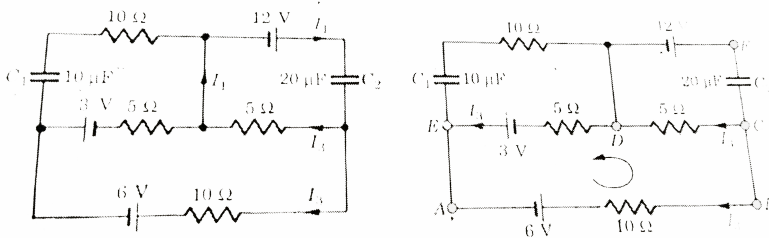


Find currents  $I_1, I_2$  and  $I_3$  and the energy stored in the capacitors  $C_1$  and  $C_2$  in the circuit shown in figure.

 **Watch Video Solution**

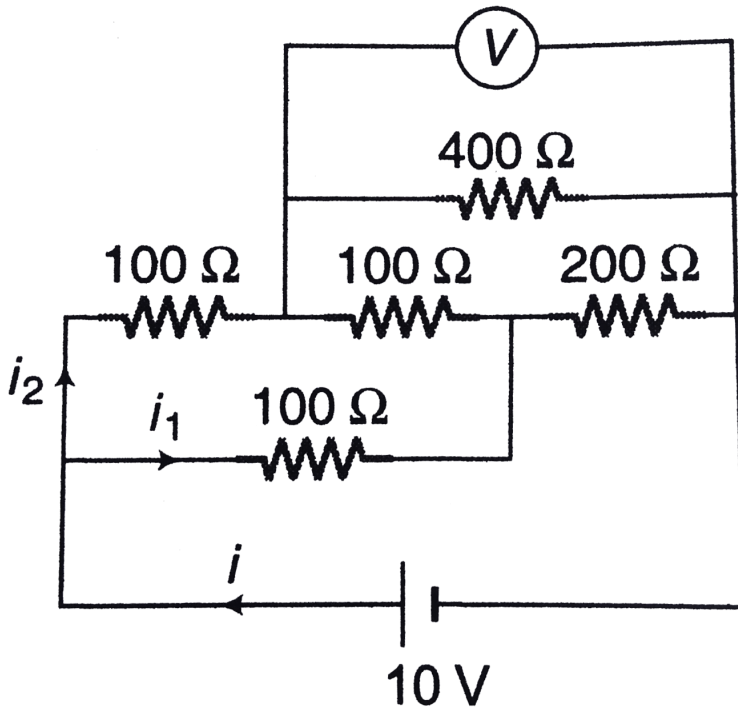6. An electrical circuit is shown in figure. Calculate the potential difference across the resistor of  $400\Omega$  as will be measured by the voltmeter  $V_{of}$

resistance  $400\Omega$  either by applying Kirchoff's rules or otherwise.



Watch Video Solution






9. A potentiometer wire of length 100 cm has a resistance of  $100\Omega$  it is connected in series with a resistance and a battery of emf 2 V and of negligible internal resistance. A source of emf 10 mV is balanced against a length of 40 cm of the potentiometer wire. what is the value of the external resistance?

 [Watch Video Solution](#)

10. In the arrangement of resistances shown in figure. Find the value of unknown resistance X if the potential difference between B and D is zero.

 [Watch Video Solution](#)

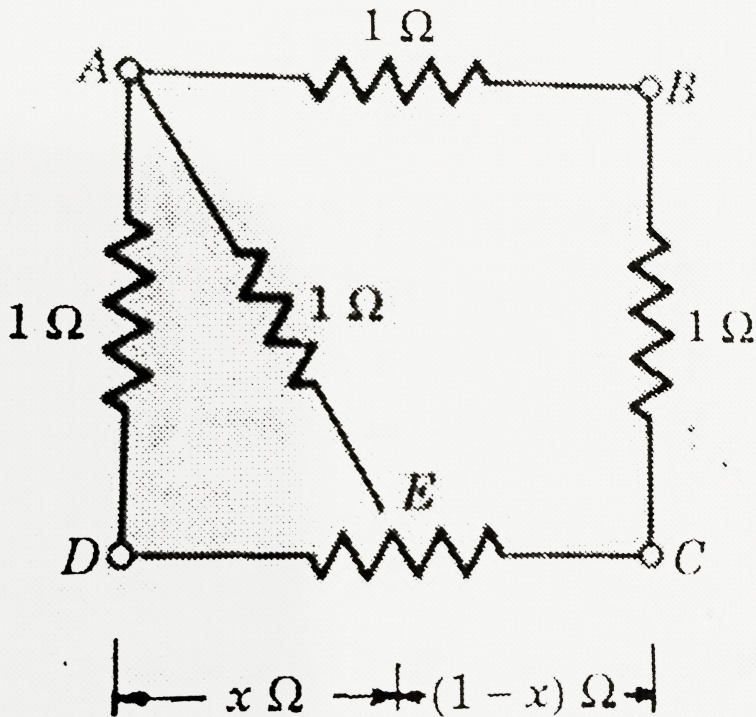

11.

In figure. ABCD is a square where side is a uniform wire of resistance  $1\ \Omega$ . Find the a point E on CD such that if a uniform wire of resistance  $1\ \Omega$  is connected across AE and a constant potential differene is applied across A and C the points B and E are equipotential.


[▶ Watch Video Solution](#)

Problem For Self Practice

1. A cell of emf  $2\text{ V}$  and internal resistance  $1\Omega$  has its terminals joined by resistances of  $5$  and  $10\Omega$  in parallel. Using kirchhoff's laws, find the current through the cell and the current drawn through each resistance.

[▶ Watch Video Solution](#)

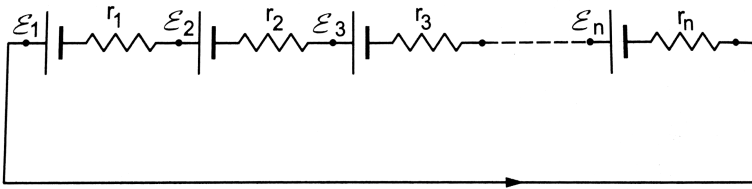2. Shown  $n$  batteries connected to form a circuit. The resistances denote the internal resistances of the batteries which are related to the emf's as  $r_i = k(\varepsilon)_i$  where  $K$  is a constant. The solid dots represent the terminals of the batteries. Find (a) the current through the circuit and (b) the potential difference between the terminals of the  $i$ th battery.




[▶ Watch Video Solution](#)

3. Two cells of emfs 1.5 V and 2.0V internal resistance  $1\Omega$  and  $2\Omega$  are connected in parallel so as to send current in the same direction through an external resistance of  $5\Omega$ .

(i) Draw the circuit diagram. (ii) Using Kirchoff's rules, calculate.


(a) current through each branch of the circuit (b) potential difference across the  $5\Omega$  resistance.

 [Watch Video Solution](#)

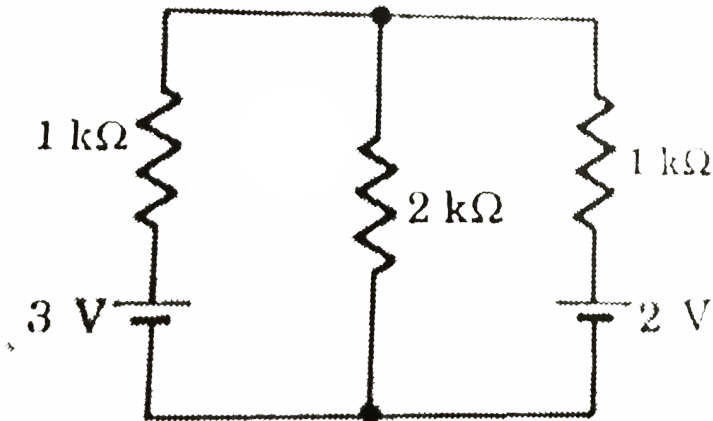

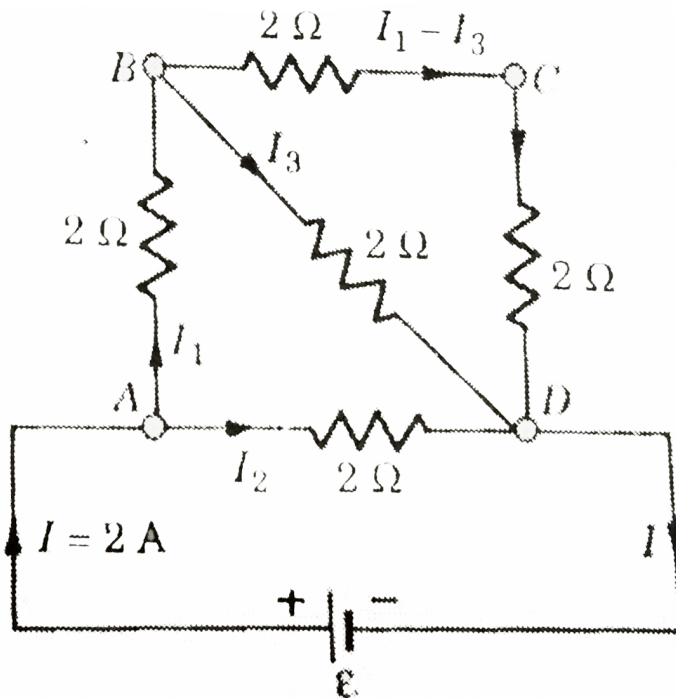
4.

Calculate the potential difference across the  $2k\Omega$  resistor in the circuit shown in figure. The internal resistance of the cells are negligible.



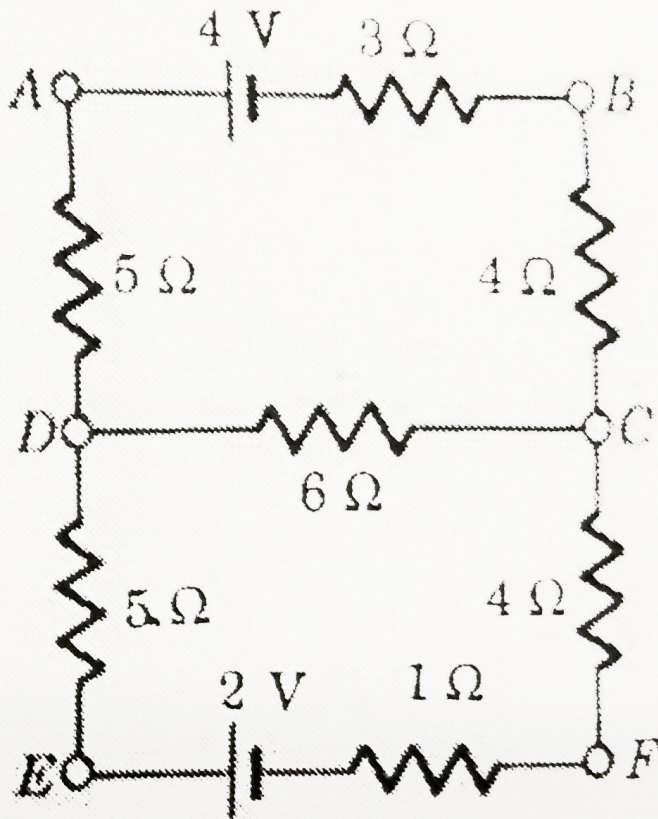5.

A network of resistors is connected to a battery of negligible internal resistance, as shown in figure. Calculate the equivalent resistance between the point A and D, and the value of the current  $I_3$ .



6.

Calculate (i) current in the  $6\Omega$  resistor, (ii) terminal voltage across the 4V cell in the circuit shown in figure.




[View Text Solution](#)

7. Three cells are connected in parallel with their like poles connected together with wires of negligible resistance. If the emfs of the cells are 2,

1 and 4 V respectively and their internal resistances are  $4\Omega$  and  $2\Omega$  respectively, find the current through each cell.


[▶ Watch Video Solution](#)

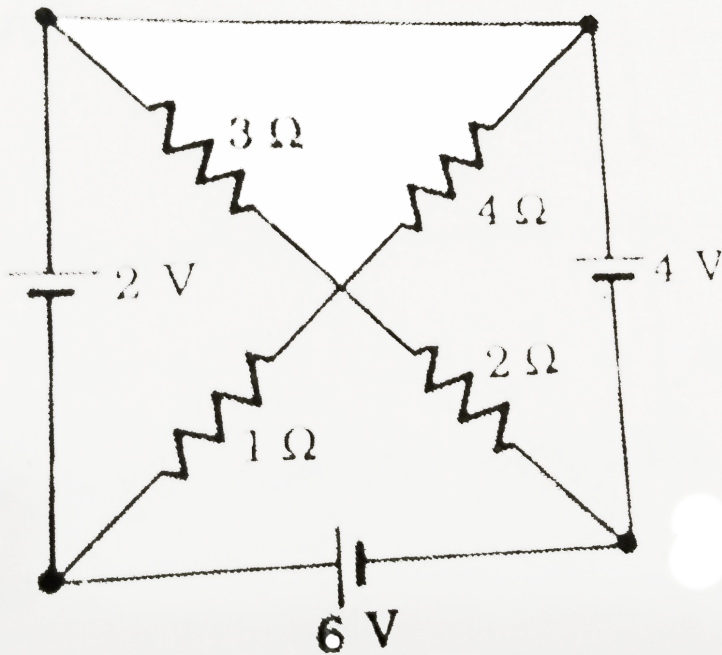

8.

In the network shown in figure. (i) calculate the current of the 6V battery and (ii) determine the potential difference between the points A and B.

[▶ View Text Solution](#)

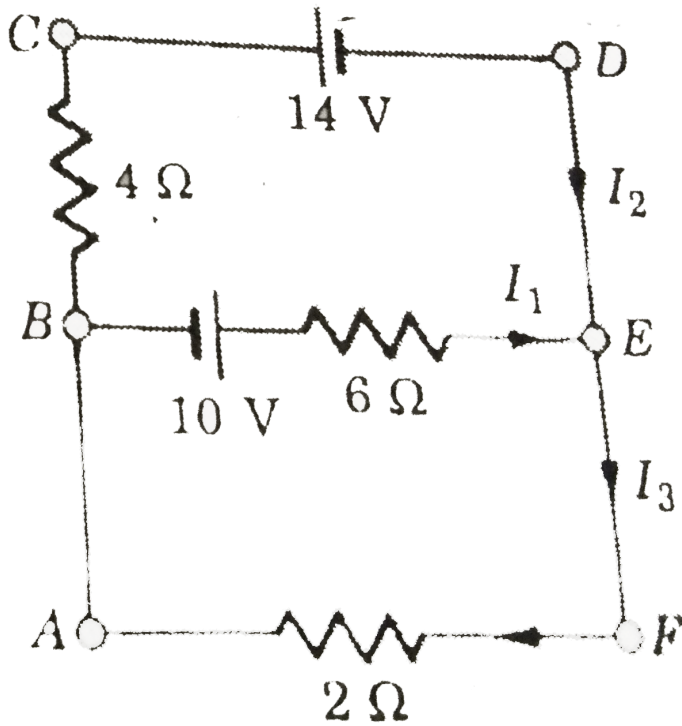


9.

In the network shown in figure. Find (i) the currents  $I_1$ ,  $I_2$  and  $I_3$  and (ii) the potential difference between the points B and F.

[▶ Watch Video Solution](#)



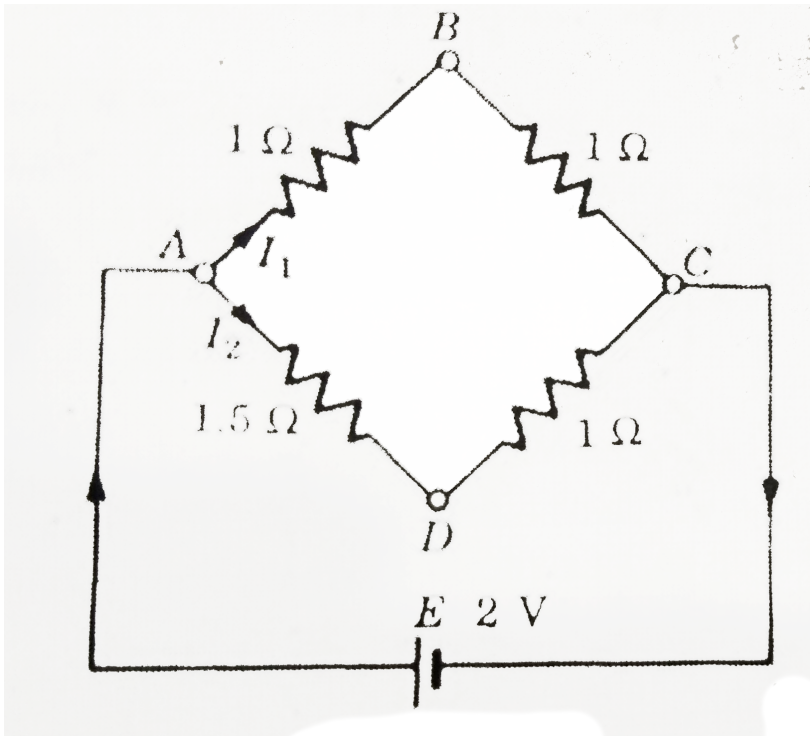


10.

Calculate the potential difference between the junctions B and D in the wheatstone's bridge shown in figure.


[▶ Watch Video Solution](#)

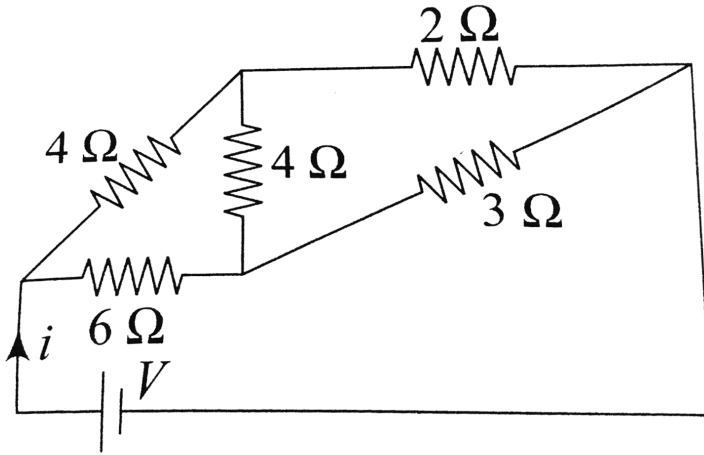11. For the network shown in the figure, the value of the current  $i$  is




[▶ Watch Video Solution](#)

12.

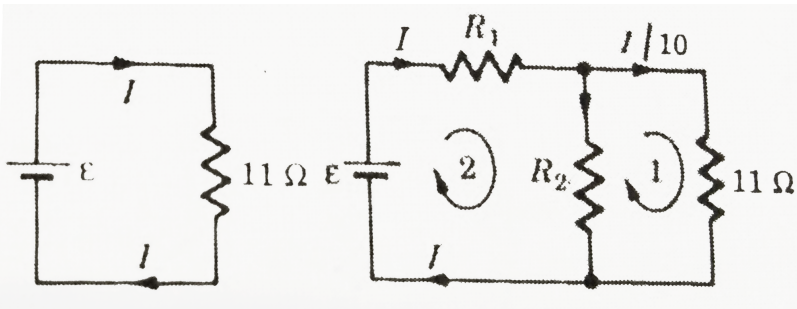

What does the ammeter A read in the circuit shown in figure? What if the positions of the cell and the ammeter are interchanged?

[▶ View Text Solution](#)

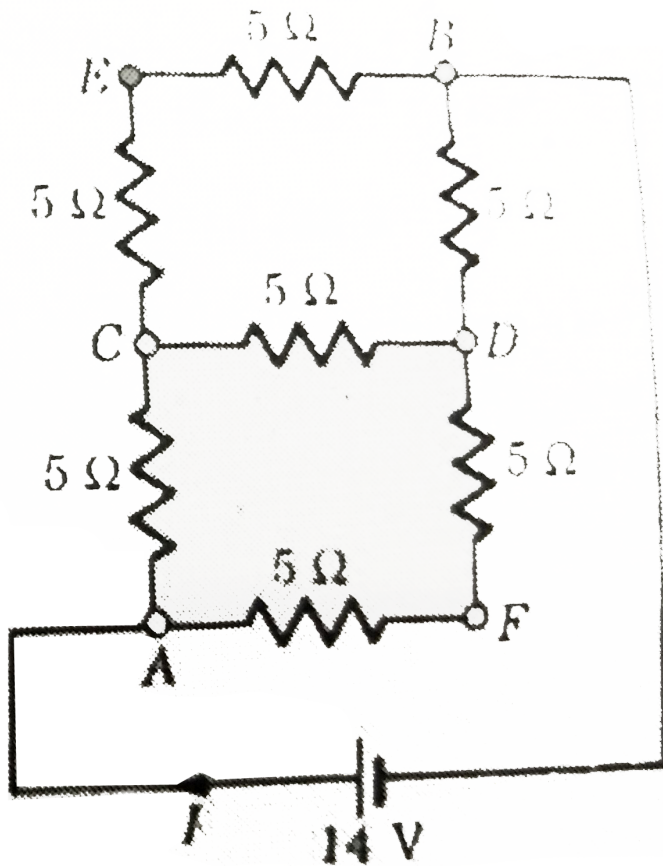


13.

In the circuit shown in figure. Determine the current in the resistance CD and equivalent resistance between the points A and B. the internal resistance of the cell is negligible.




Watch Video Solution

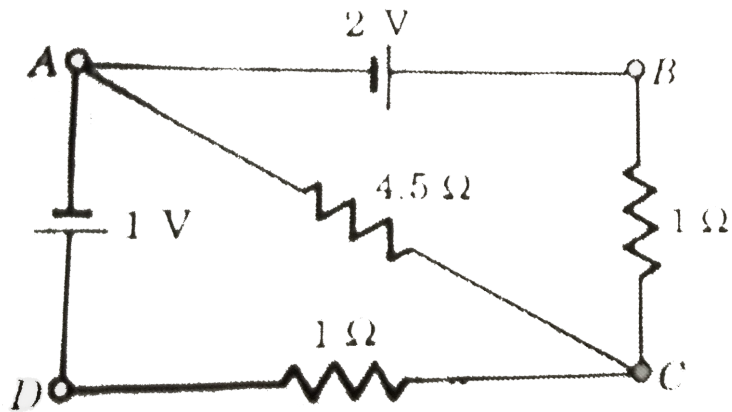

14.

calculate the current flowing in each of the resistances of the network shown in figure. The internal resistance of each cell is negligible.

[▶ Watch Video Solution](#)

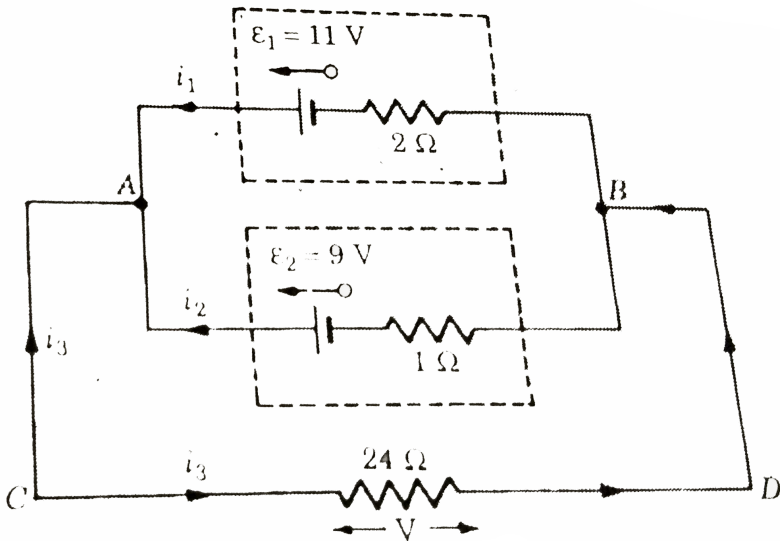

15.


Compute the values of  $i_1$ ,  $i_2$ ,  $i_3$  and  $V$  in the circuit, shown in figure. The emf and the internal resistance of the upper cell are 11V and  $2\Omega$ , and of the lower cell are 9 V and  $1\Omega$ .



[View Text Solution](#)

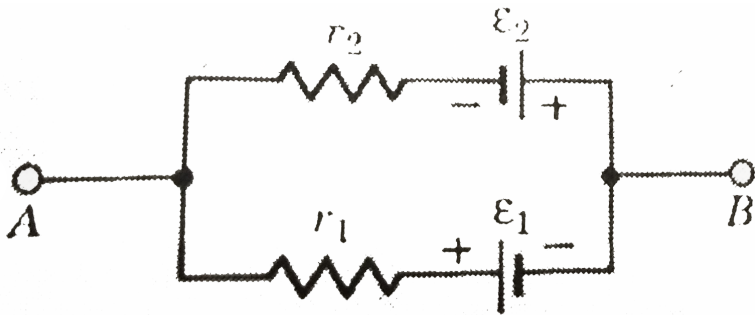
16. A certain length of a uniform wire of resistance  $12\Omega$  is bent into a circle and two points, a quarter of circumference apart, are connected to a battery of emf 4 V and internal resistance  $1\Omega$ . Find the current in the different parts of the circuit.





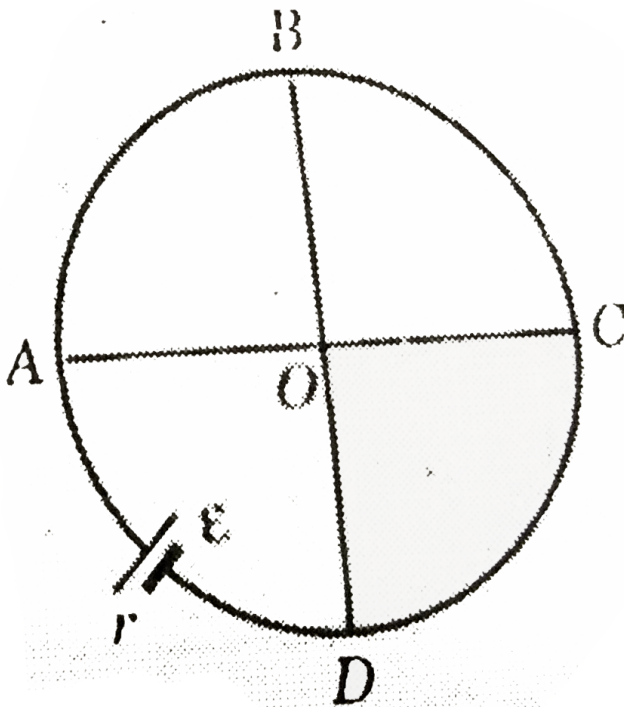17.

find the emf ( $\epsilon_0$ ) and internal resistance ( $r_0$ ) if a battery which is equivalent to a parallel combination of two batteries of emfs  $\epsilon_1$  and  $\epsilon_2$  and internal resistances  $r_1$  and  $r_2$  respectively, with polarities as shown in figure.



18.

In figure. ABCDA is a uniform circular wire of resistance  $2\Omega$ , AOC and BOD are two wires along two perpendicular diameters of the circle, each having same resistance  $1\Omega$ . A battery of emf  $\epsilon$  and internal resistance  $r$  is connected between the point A and D. Calculate the equivalent resistance of the network

[View Text Solution](#)

19. Three batteries of emf 4,5 and 6V and internal resistances  $1,2$  and  $3\Omega$  respectively are connected in parallel with each other and the combination sends a current through an external resistance of  $4\Omega$ . Find current drawn through each battery.




[View Text Solution](#)

20. One ampere of current enters the junction A of a wheatstone bridge ABCD with  $AB = 2\Omega$ ,  $BC = 2\Omega$ ,  $AC = 4\Omega$ ,  $CD = 2\Omega$  and  $R_g = 4\Omega$ . Find the current through the galvanometer.



[View Text Solution](#)



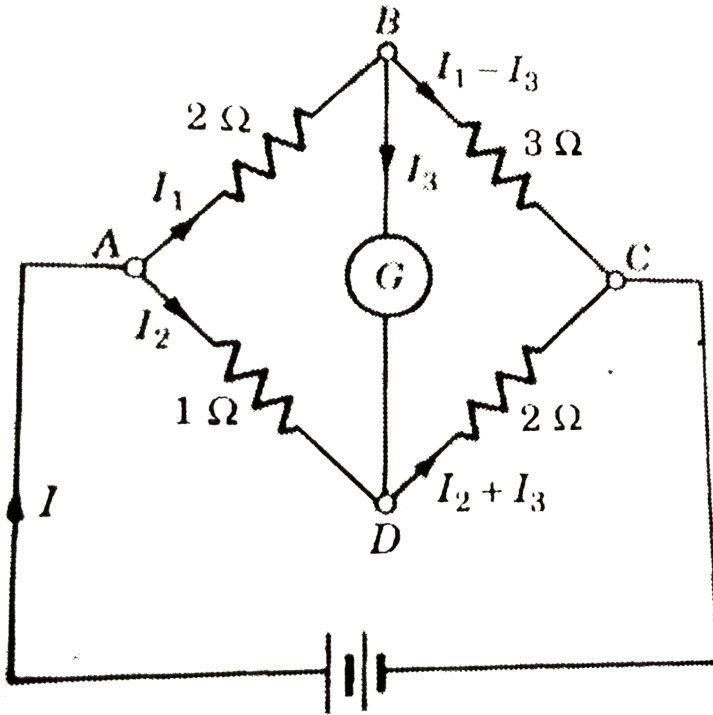


21.

In the circuit shown in figure. Find the currents  $I$ ,  $I_1$ ,  $I_2$  and  $I_3$  given that emf of the battery = 2V, internal resistance of the battery =  $2\Omega$  and resistance of the galvanometer =  $4\Omega$ .



[View Text Solution](#)

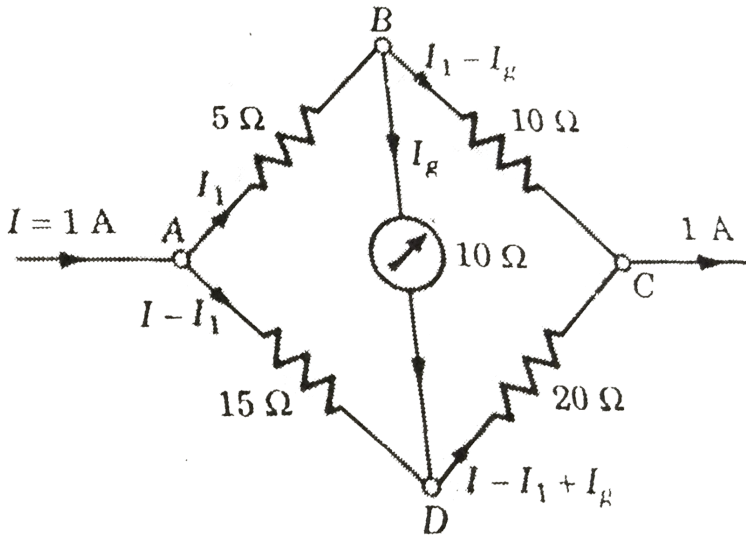22. Determine the current flowing through the galvanometer G of the Wheatstone bridge shown in figure.



[View Text Solution](#)

23. A current of 0.1 A enters a Wheatstone bridge consisting of three arms of  $10\Omega$  each and one of  $11\Omega$ . What is the current in galvanometer if its resistance is  $100\Omega$ ?

[Watch Video Solution](#)

24. The terminals of a battery of emf 3 V and internal resistance  $2.5\Omega$  are joined to the diagonally opposite corners of a cubical skeleton frame of

12 wires, each of resistance  $3\Omega$ . Find the current in the battery.



[Watch Video Solution](#)

25. Twelve identical wires each of resistance  $6\Omega$  are arranged to form a skeleton cube. A current of  $40\text{mA}$  is led into the cube at one corner and out at the diagonally opposite corner. Calculate the potential difference development across these current and the effective resistance of the network



[Watch Video Solution](#)

26. Twelve equal wires each of resistance  $r\Omega$  form a cube. The effective resistance between the corners of the same edge of the cube is



[Watch Video Solution](#)

27. A galvanometer has a resistance of  $49\Omega$ . If 2% of the main current is to be passed through the meter, The value of the shunt will be

 [Watch Video Solution](#)

28. how will you convert a 1mA full scale deflection meter of resistance  $100\Omega$  into an ammeter to read into 1.0A?

 [Watch Video Solution](#)

29. Calculate the value of resistance needed to convert a galvanometer of resistance  $200\Omega$ , which gives a full scale deflection for a current of 5 mA, into a voltmeter of 0-10V range.

 [Watch Video Solution](#)

**30.** A galvanometer with a coil of resistance  $10.0\Omega$  shows full scale deflection for a current of  $50\text{mA}$ . How will you convert the galvanometer into

(i). An ammeter of range 0 to  $0.5\text{ A}$  and

(ii). A voltmeter of range 0 to  $5\text{V}$ ?

 [View Text Solution](#)

**31.** A galvanometer has an internal resistance  $1.0\Omega$ . It given maximum deflection for a current of  $50\text{ mA}$ . Show how this instrument can be converted into (i) a voltmeter with a maximum reading of  $2.5\text{ V}$  and (ii) an ammeter with a maximum reading of  $2.5\text{ A}$

 [View Text Solution](#)

**32.** A galvanometer has a resistance of  $15.0\Omega$  and the meter shows full scale deflection for a current of  $2.0\text{ mA}$ . How will you convert this meter

into (i) an ammeter of range 0-5.0A and (ii) a voltmeter of range 0 to 15.0V? Also determine the resistance of the meter in each case.

 [View Text Solution](#)

**33.** In galvanometer of resistance  $20\Omega$  gives a deflection of one division when a potential difference of 4mV is applied across its terminals. Calculate the resistance of the shunt if the current of 10A is to be measured by it. The galvanometer has 25 divisions.

 [View Text Solution](#)

**34.** In a galvanometer there is a deflection of one divisions per mA. The internal resistance of the galvanometer is  $80\Omega$ . If a shunt of  $2.5\Omega$  is connected to the galvanometer and there are 50 divisions in all, one the scale of the galvanometer, what maximum current can this galvanometer read?

 [View Text Solution](#)

35. A galvanometer of resistance  $40\Omega$  gives a deflection of 5 divisions per mA. There are 50 divisions on the scale. Calculate the maximum current that can pass through it when a shunt resistance of  $2\Omega$  is connected.

 [View Text Solution](#)

36. It is intended to measure a maximum current of 25 A with an ammeter of range 2.5 A and resistance  $0.9\Omega$ . How will you do it? What will be the combined resistance?

 [View Text Solution](#)

37. A galvanometer has a resistance of  $30\Omega$  and a current of 2 mA is needed to give full scale deflection. What is the resistance needed and how is it to be connected to convert the galvanometer (i) into an ammeter of 0.3 A range and (ii) into a voltmeter of 0.2 V range?

 [View Text Solution](#)

**38.** A galvanometer has a resistance of  $100\Omega$ . A difference of potential of  $1.0\text{ V}$  between its terminals gives a full scale deflection. Calculate the shunt resistance which will enable the instrument to read upto  $2\text{A}$ .

 [View Text Solution](#)

**39.** When a galvanometer having 20 divisions scale and  $50\Omega$  resistance is connected in series to a cell of emf  $1.5\text{V}$  through a resistance of  $100\Omega$ , it shows full scale deflection. Find the figure of merit of the galvanometer.

 [View Text Solution](#)

**40.** A galvanometer has a sensitivity of  $60\text{ division/ampere}$ . When a shunt is used its sensitivity becomes  $10\text{ divisions/ampere}$ . What is the value of shunt used if the resistance of the galvanometer is  $20\Omega$ ?

 [Watch Video Solution](#)



41. A galvanometer of resistance  $3663\Omega$  gives full scale deflection for a certain current  $i_g$ . Calculate the resistance of the shunt which when joined to the galvanometer coil will result in  $1/34$  of the total current passing through the galvanometer. also find the total resistance of the galvanometer and the shunt.

 [View Text Solution](#)

42. A shunt of  $6\Omega$  is connected across a galvanometer of resistance  $294\Omega$ . Find the fraction of the total current passing through the galvanometer.

 [View Text Solution](#)

43. A galvanometer is shunted by  $1/n$  th of its resistance. Find the fraction of the total current passing through the galvanometer.

 [View Text Solution](#)

**44.** If a galvanometer is connected in series with a high resistance so that potential drop across the galvanometer is  $1/n$  th of the total applied voltage, then show that the combined resistance of the galvanometer and the series resistor is  $n$  times the resistance of the galvanometer i.e.,

 [Watch Video Solution](#)

**45.** A galvanometer has current sensitivity of 5 divisions/mA and a voltage sensitivity of 2 division/mV. If the instrument has 30 divisions, how will you use it to measure (i) a current of 3 A, and (ii) a voltage of 15V?

 [View Text Solution](#)

**46.** A  $250\mu A$  meter has 50 divisions and it needs 250 mV for full scale deflection. How will you convert it to read (i) 05 mA/division and (ii) 0.5 V/division?

 [View Text Solution](#)

47. It is required to pass only one-tenth of the main current through a galvanometer having a resistance of  $27\Omega$ . Calculate the length of the wire of specific resistance  $48 \times 10^{-6}\Omega\text{cm}$  and area of cross-section  $0.2\text{mm}^2$  required to make a shunt for this purpose.

 [View Text Solution](#)

48. With a potentiometer, null points were obtained at 140 cm and 180 cm with cells of emf 1.1 volt and one of unknown value respectively. Calculate the unknown emf.

 [View Text Solution](#)

49. In a method for comparing emfs by a potentiometer a balance point is found to be 50 cm with a Daniel cell of emf 1.1 volt. Where will you get the balance point with a Leclanche cell of emf 1.5 volt?

 [View Text Solution](#)

50. In a potentiometer with a cell of unknown emf the balance point was obtained at 60 cm and with a cell of emf 1.5 volt at 45 cm from the same end. Calculate the unknown e.m.f. of the cell.



[View Text Solution](#)

51. A potentiometer having a wire 10 m long stretched on it, is connected to accumulator having a steady voltage. A leclanche cell gives a null point at 750 cm. if the length of the potentiometer wire is increased by 100 cm, find the new position of the null point.



[View Text Solution](#)

52. With a certain cell, the balance point is obtained at 60 cm from the zero end of the potentiometer wire. With another cell whose emf differs from that of the first cell by 0.1 V, the balance point is obtained at 50 cm mark. Calculate the emf of the two cells.



[View Text Solution](#)

**53.** With a cell of emf 1.5 V, the balance point is obtained at a distance of 60 cm from one end of the potential wire. Calculate the potential difference between two ends of the potentiometer wire if its total length is 100 cm.

 [View Text Solution](#)


**54.** A 10 metre long potentiometer wire carries a steady current. A 1.018 volt standard cell is balanced at a length of 850 cm. find (i) the potential gradient along the wire and (ii) the maximum emf that can be measured.

 [View Text Solution](#)

**55.** A potentiometer wire has a potential gradient of 0.0025 volt/cm along its length. Calculate the length of the wire at which null-point is obtained

for a 1.025 volt standard cell. Also, find the emf of another cell for which the null-point is obtained at 860 cm length

[View Text Solution](#)

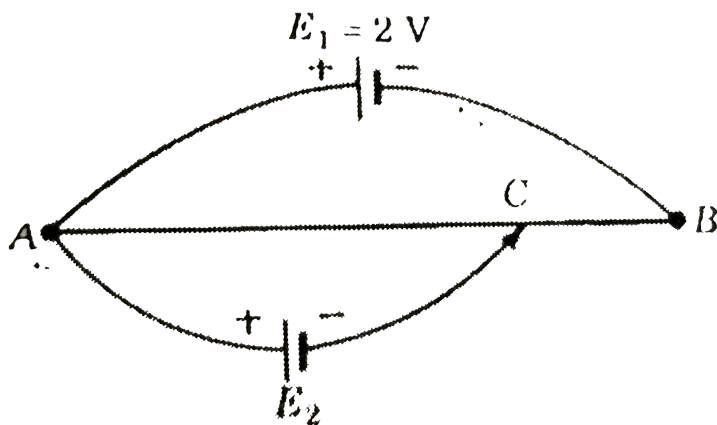

56.

AB is a potentiometer wire of length 100 cm. when a cell  $\varepsilon_2$  is connected across AC, where  $AC=75\text{cm}$ , no current flows from  $\varepsilon_2$ . Find (i) the potential gradient along AB and (ii) emf of the cell  $\varepsilon_2$ . the internal resistance of the cell  $\varepsilon_1$  is negligible.

[Watch Video Solution](#)

57. A potentiometer is being used to determine the internal resistance of a primary cell. The balance point for the cell in an open circuit is at 76.3 cm. when the cell sends a current in a resistor of  $9.5\Omega$ , the balance point shifts to 64.8cm. Find the internal resistance of the cell.



[View Text Solution](#)

58. A cell can be balanced against 110 cm and 100 cm of potentiometer wire respectively when in open circuit and shorted through a resistance of  $10\Omega$ . Find the internal resistance of the cell.



[View Text Solution](#)

59. A potentiometer wire of length 100 cm has a resistance of  $10\Omega$ . It is connected in series with a resistance and an accumulator of emf 2V and negligible internal resistance. A source of emf 10 mV is balanced against a length of 40 cm of the potentiometer wire. what is the value of the external resistance?



[View Text Solution](#)

**60.** The resistance of a potentiometer wire is  $18\Omega$ . A high resistance box and a 2 V accumulator are connected in series with it. What should be the value of the resistance in the box, if it is desired to have a potential drop of  $1\mu\text{V}/\text{mm}$ ?



[View Text Solution](#)

**61.** A standard cell of emf 1.08 V is balanced by the potential difference across 91 cm of a meter long wire supplied by a cell of emf 2 V through a series resistor of resistance  $2\Omega$ . The internal resistance of the cell is zero. Find the resistance per unit length of the potentiometer wire.



[View Text Solution](#)

**62.** In an experiment with a potentiometer to measure the internal resistance of a cell, when the secondary circuit is shunted by  $5\Omega$ , the null



point is at 220 cm. when the cell is shunted by  $20\Omega$ , the null point is at 300 cm. calculate the internal resistance of the cell.


 [View Text Solution](#)

**63.** Four resistances of  $15\Omega$ ,  $12\Omega$ ,  $4\Omega$  and  $10\Omega$  respectively are connected in cyclic order to form a wheatstone bridge. Is the network balanced? If not, calculate the resistance to be connected in parallel with the resistance of  $10\Omega$  to balance the network

 [View Text Solution](#)

**64.** Four coils resistances 3,6,9 and  $30\Omega$  respectively are arranged to form a wheatstone bridge. Determine the value of the resistance with which the coil of  $30\Omega$  should be shunted so as to balance the bridge.

 [View Text Solution](#)

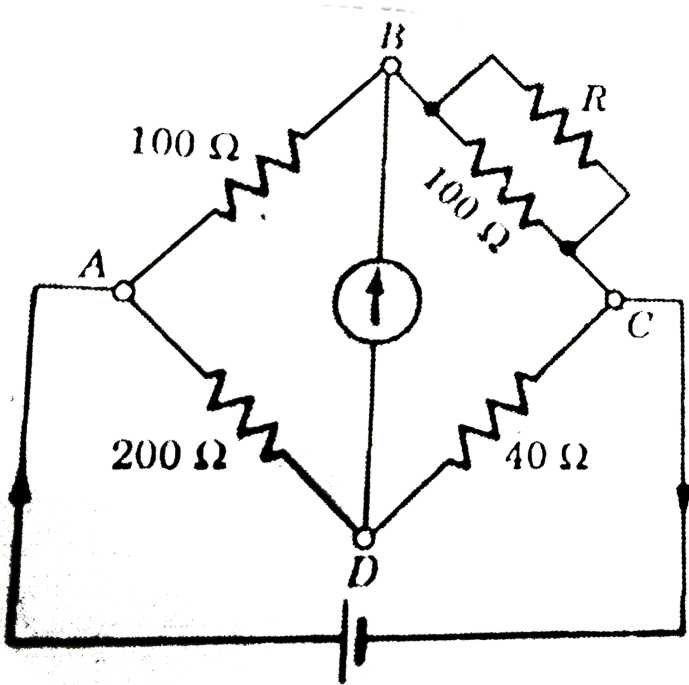


65.

The wheatstone's bridge of figure. Is showing no deflection in the galvanometer joined between the points B and D. compute the value of R.




[Watch Video Solution](#)

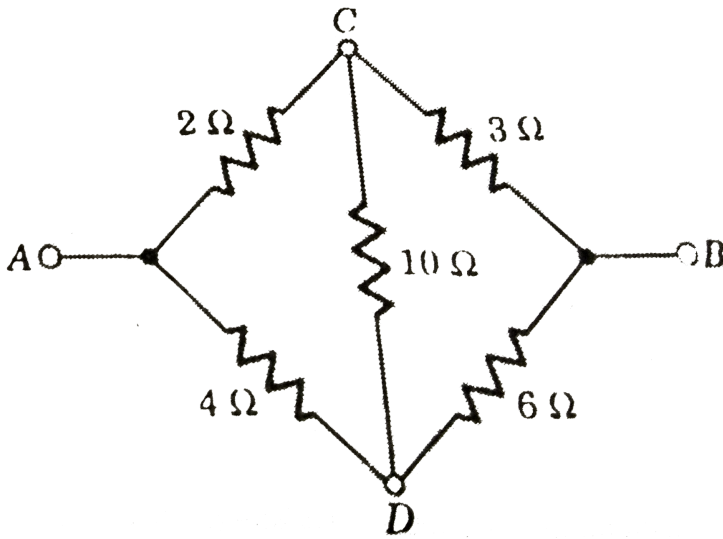

66.

Five resistances are connected as shown in figure. What is the effective resistance between points A and B?

[▶ Watch Video Solution](#)

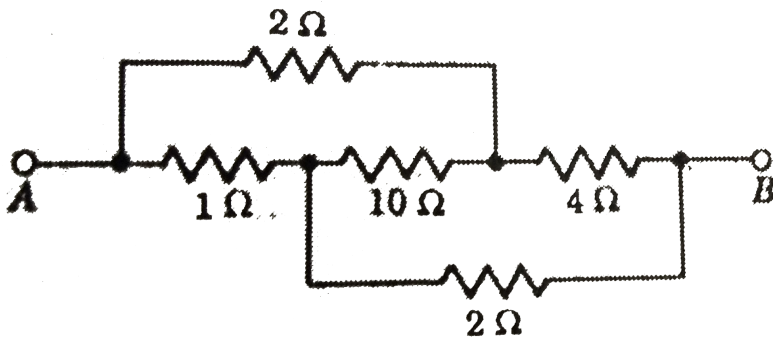


67.

Calculate the equivalent resistance between points A and B of the

network shown in figure.



[Watch Video Solution](#)

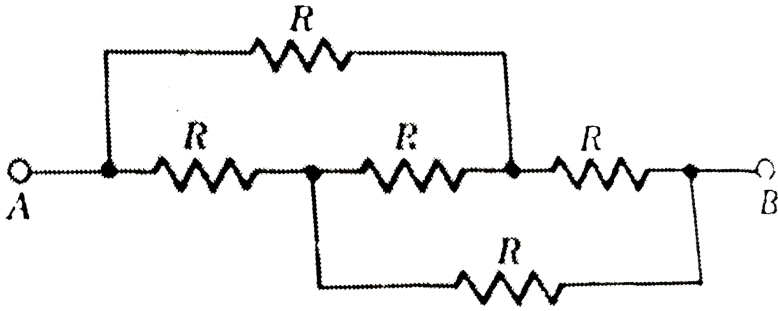


68.

Calculate the equivalent resistance between the points  $A$  and  $B$  of the network shown in figure.



[View Text Solution](#)

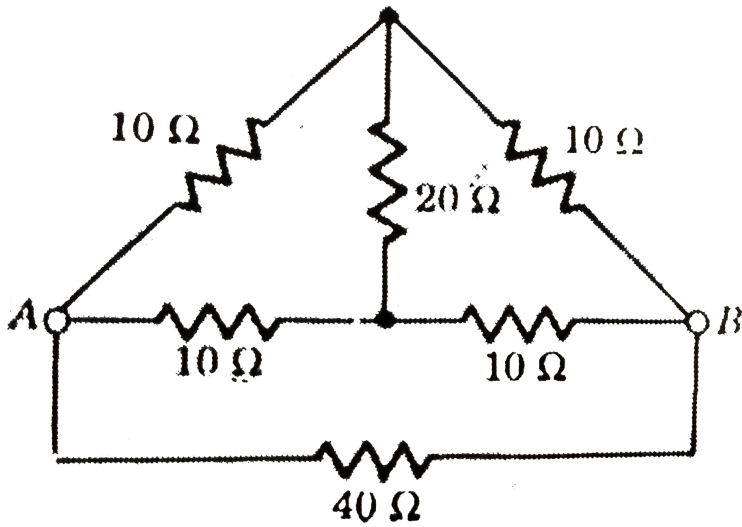


69.

Calculate the resistance between the points A and B of the network shown in figure.



[Watch Video Solution](#)

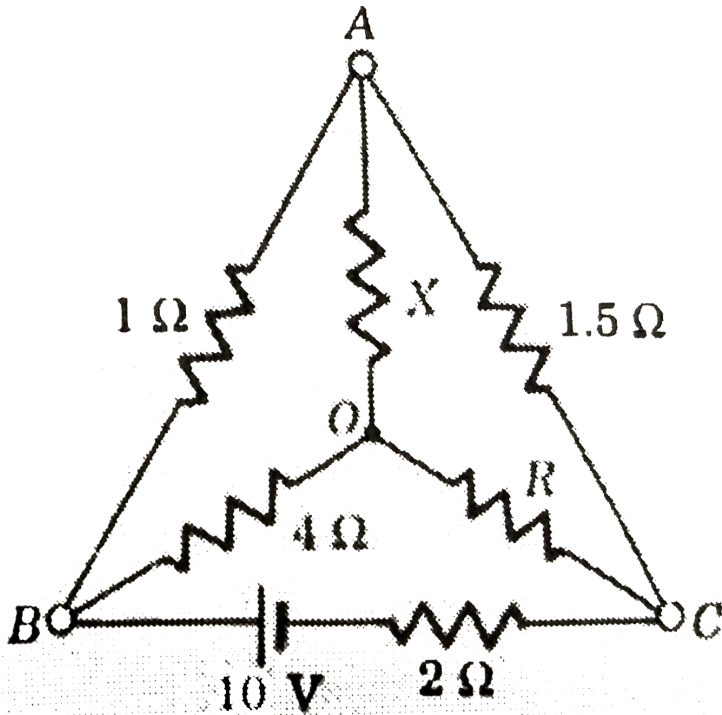


70.

for the network shown in figure, determine the value of  $R$  and the current through it, if the current through the branch  $AO$  is zero.




[View Text Solution](#)

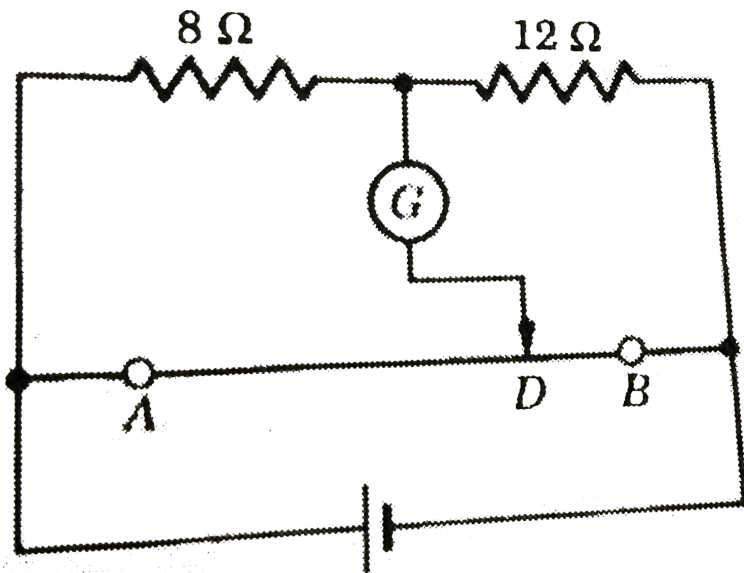

71.

The potentiometer wire AB shown in figure. Is 40 cm long. Where should the free end of the galvanometer be connected on AB so that the galvanometer may show zero deflection?

[View Text Solution](#)

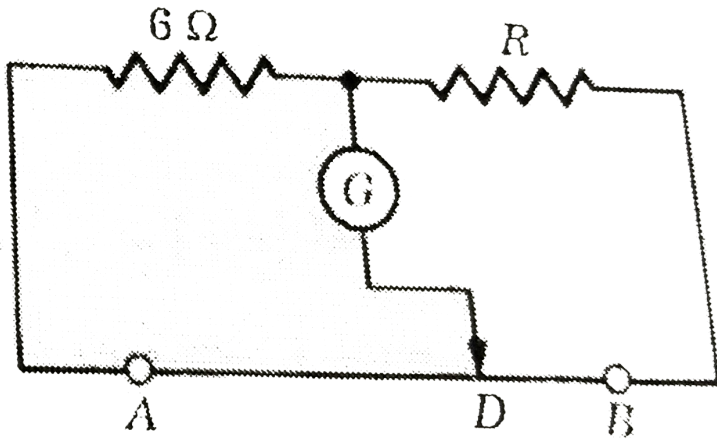

72.

The potentiometer wire  $AB$  shown in figure. Is 50 cm long. When  $AD = 30\text{ cm}$ , no deflection occurs in the galvanometer. Find  $R$

[View Text Solution](#)

73. In an experiment with post office box, the ratio arms are  $1000:10$ . If the value of third resistance is  $870\ \Omega$ , find the unknown resistance.

[View Text Solution](#)



74. P,Q,R and S are the resistances taken in the cyclic order in a wheatstone bridge network. P and Q are ratio coils, S is the unknown resistance and R is a  $20\Omega$  coil. A balance is obtained when R is shunted with a resistance of  $350\Omega$ . When P and Q are interchanged, the balance is restored by altering the shunt across R to  $498\Omega$ . find the resistance of S and the ratio P:Q.


 [Watch Video Solution](#)

75. A resistance of  $5\Omega$  is connected in one gap of a metre bridge and  $15\Omega$  in the other gap. Calculate the position of the balancing point.

 [View Text Solution](#)

76. In a metre bridge the length of the wire is 100 cm. At what point will the balance point be obtained if the two resistances are in the ratio of 4:5.

 [View Text Solution](#)

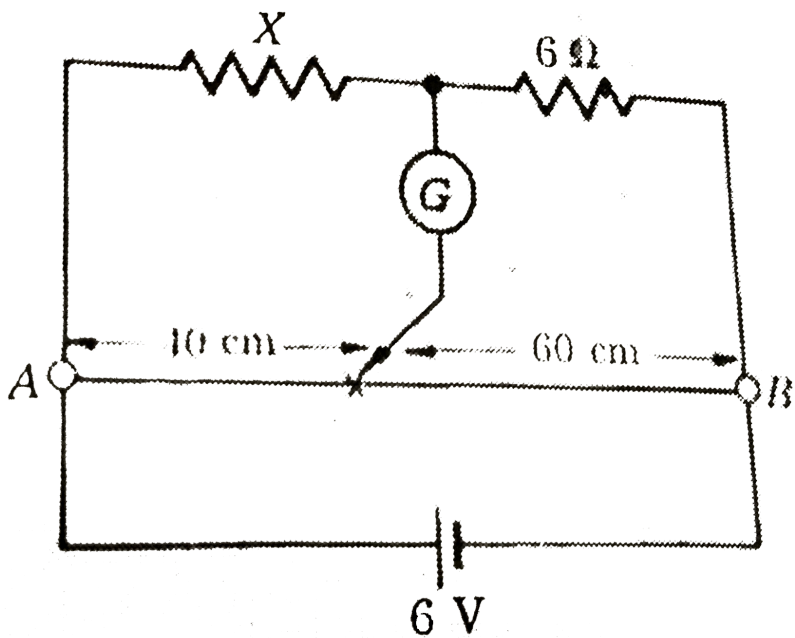

77.

In the circuit shown in figure. A metre bridge is shown in its balanced state. The metre bridge wire has a resistance of a 4 ohm/cm. calculate the value of the unknown resistance  $X$  and the current drawn from the battery of negligible resistance.

[▶ Watch Video Solution](#)

**78.** In a metre bridge when the resistance in the left gap is  $2\Omega$  and an unknown resistance in the right gap, the balance point is obtained at 40 cm from the zero end. On shunting the unknown resistance with  $2\Omega$ , find the shift of the balance point on the bridge wire.



[View Text Solution](#)

**79.** In comparing the resistance of two coils P and Q with the help of a metre-bridge arrangement, a balance point is obtained when the sliding contact is 50 cm from the zero end of the wire. The resistances P and Q are then interchanged and balance point is obtained at 120 cm from the zero end. Deduce the ratio of the resistances P and Q and the length of the wire.



[View Text Solution](#)

**80.** In a meter-bridge experiment, two resistances P and Q are connected in series in the left gap. When the resistance in the right gap is  $50\Omega$ , the

balance point is at the centre of the slide wire. If P and Q are connected in parallel in the left gap, the resistance in the right gap has to be changed to  $120\Omega$  so as to obtain the balance point at the same position. find P and Q.

 [Watch Video Solution](#)

**81.** In a meter-bridge experiment with a resistance  $R_1$  in left gap and a resistance  $X$  in a right gap. null point is obtained at  $40\text{cm}$  from the left emf. With a resistance  $R_2$  in the left gap, the null point is obtained at  $50\text{cm}$  from left hand. Find the position of the left gap is containing  $R_1$  and  $R_2$  (i) in series and (ii) in parallel.

 [Watch Video Solution](#)