



## PHYSICS

### BOOKS - DHANPAT RAI & CO PHYSICS (HINGLISH)

### SOLIDS AND SEMICONDUCTOR DEVICES

#### Illustration Type

1. In a pure semiconductor the number of conduction electrons is  $6 \times 10^{19}$  per cubic metre. How many holes are there in a sample of size  $1\text{cm} \times 1\text{cm} \times 1\text{mm}$ ?



Watch Video Solution

2. Find the maximum wavelength of electromagnetic radiation which can create a hole-electron pair in germanium. The band gap in germanium is  $0.65\text{eV}$ .



[Watch Video Solution](#)

3. A p-type semiconductor has acceptor levels  $57\text{meV}$  above the valence band. Find the maximum wavelength of light which can create a hole.



[Watch Video Solution](#)

4. A semiconductor has equal electron and hole concentration of  $2 \times 10^8 m^{-3}$ . On doping with a certain impurity, the hole concentration increases to  $4 \times 10^{10} m^{-3}$ . (i) What type of semiconductor is obtained on doping? (ii) Calculate the new electron hole concentration of the semiconductor. (iii) How does the energy gap vary with doping?



[Watch Video Solution](#)

5. A semiconductor has an electron concentration of  $0.45 \times 10^{12} m^{-3}$  and a hole concentration of  $5.0 \times 10^{20} m^{-3}$ . Calculate its conductivity. Given electron

mobility =  $0.135m^2V^{-1}s^{-1}$ , hole mobility  
=  $0.048m^2V^{-1}s^{-1}$ ,

 [Watch Video Solution](#)

6. A semiconductor is known to have an electron concentration of  $5 \times 10^{12}cm^{-3}$  and a hole concentration  $8 \times 10^{13}cm^{-3}$ . Is the semi-conductor n-type or p-type? What is the resistivity of the sample, if the electron mobility is  $23,000cm^2V^{-1}s^{-1}$ ? Take charge on electron,  $e = 1.6 \times 10^{-19}C$ .

 [Watch Video Solution](#)

7. Determine the number density of donor atoms which have to be added to an intrinsic germanium semiconductor to produce an n-type semiconductor of conductivity  $5\Omega^{-1}cm^{-1}$ , given that the mobility of electron in n-type germanium is  $3900cm^2V^{-1}s^{-1}$ . Neglect the contribution of holes to conductivity.



[Watch Video Solution](#)

8. A battery of emf  $2V$  is connected across a block of length  $0.1m$  and area of cross-section  $1 \times 10^{-4}m^2$ . If the block is of intrinsic silicon at  $300K$ , find the electron and hole currents. What will be the magnitude of the total current? What will be the magnitude of the total current

if germanium is used instead of silicon?

Given that for  $Si$  at  $300K$ :

$$\mu_e = 0.135m^2V^{-1}s^{-1}, \mu_h = 0.048m^2V^{-1}s^{-1} \quad \text{and}$$

intrinsic carrier concentration  $n_i = 1.5 \times 10^{16}m^{-3}$ . For

$Ge$  at

$$300K: \mu_e = 0.39m^2V^{-1}s^{-1}, \mu_h = 0.19m^2V^{-1}s^{-1} \quad \text{and}$$

$$n_i = 2.4 \times 10^{19}m^{-3}$$



[Watch Video Solution](#)

9. If resistivity of pure silicon is  $3000\Omega meter$ , and the electron and hole mobilities are  $0.12m^2V^{-1}s^{-1}$  and  $0.045m^2V^{-1}s^{-1}$  respectively, determine the resistivity of a specimen of the material when  $10^{19}$  atoms of

phosphorous are added per  $m^3$  are also added. Given charge on electron  $= 1.6 \times 10^{-19} C$ .

 [Watch Video Solution](#)

**10.** In an intrinsic semiconductor the energy gap  $E_g$  is  $1.2 eV$ . Its hole mobility is much smaller than electron mobility and independent of temperature. What is the ratio between conductivity at  $600K$  and  $300K$ ? Assume that temperature dependence intrinsic concentration  $n_i$  is given by

$$n_i = n_0 \exp\left(\frac{-E_g}{2k_T}\right), \text{ where } n_0 \text{ is a constant and } k = 8.62 \times 10^{-5} eV / K.$$

 [Watch Video Solution](#)

11. When the voltage drop across a  $p. n$  junction diode is increased from  $0.65V$  to  $0.70V$ , the change in the diode current is  $5mA$ . What is the dynamic resistance of the diode?


 [Watch Video Solution](#)

12. Figure shos the characteristic curve of a junction diode. Determie the d.c. and a.c. resistance of the diode, when it operates at  $0.3V$ .

 [View Text Solution](#)



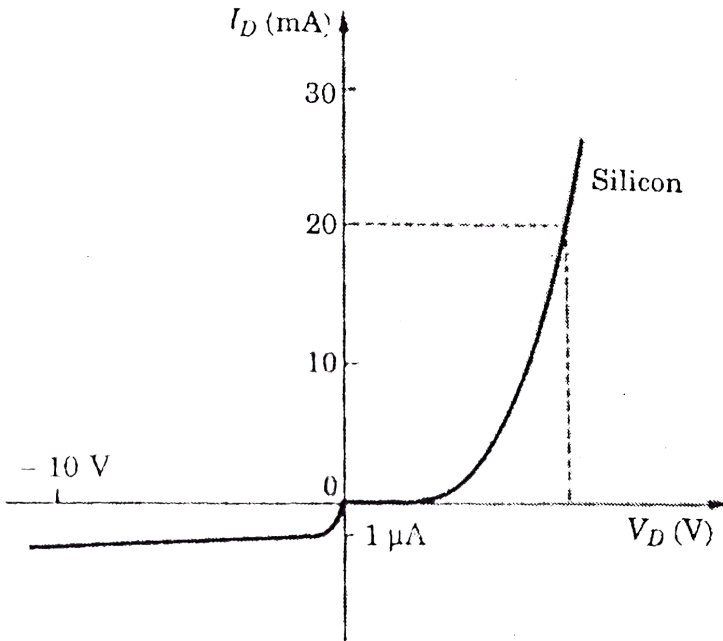13. The volt-ampere characteristic of a silicon diode is shown in fig. Determine the resistance of the diode at (i)  $I_D = 20\text{mA}$  and (ii)  $V_D = -10\text{V}$ .



[Watch Video Solution](#)


**14.** A  $p - n$  junction diode when forward biased has a drop of  $0.5V$  which is assumed to be independent of current. The current in excess of  $10mA$  through the diode produces a large Joule heating which damages (burns) the diode. If we want to use a  $1.5V$  battery to forward bias the diode, what should be the value of resistor used in series with the diode so that the maximum current does not exceed  $5mA$ ?



**Watch Video Solution**

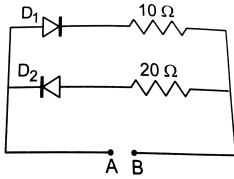**15.** A  $2V$  battery may be connected across the points A and B as shown in figure. Assume that the resistance of each diode is zero in forward bias and infinity in reverse

bias. Find the current supplied by the battery if the positive terminal of the battery is connected to (a) the point A (b) the point B.



 [Watch Video Solution](#)

**16.** Draw the circuit to forward bias a diode. (The supply is  $3V$  and  $100mA$  battery). If the diode is made of silicon and knee voltage is  $0.7V$ , and a current of  $20mA$  passes through the diode, find the wattage of the resistor and the diode.

 [Watch Video Solution](#)

17. In figure what is the voltage needed to maintain  $15V$  across the load resistance  $R_L$  of  $2K$ , assuming that the series resistance  $R$  is  $200\Omega$  and the zener requires a minimum current of  $10mA$  to work satisfactorily? What is the zener rating required?

 [View Text Solution](#)

18. A potential barrier of  $0.50V$  exists across a p-n junction.(a) If the depletion region is  $5.0 \times 10^{-7}m$  wide,what is the intensity of the electric field in this region?(b) An electron with speed  $5.0 \times 10^5ms^{-1}$  approaches the p-n junction from the n-side.With what speed will it enter the p-side?



[Watch Video Solution](#)

**19.** In half - wave rectification, what is the output frequency, if the input frequency is 50 Hz ? What is the output frequency of a full - wave rectifier for the same input frequency ?



[Watch Video Solution](#)

**20.** The turns ratio of a transformer used in a half wave rectifier is 12: 1. The primary is connected to the power mains 220V, 50Hz. Assuming the diode resistance in

forward bias to be zero, calculate the d.c. voltage across the load.

 [View Text Solution](#)

**21.** In a centre tap full wave rectifier, the load resistance  $R_L = 1k\Omega$ . Each diode has a forward bias dynamic resistance of  $10\Omega$ . The voltage across half the secondary winding is  $220 \sin 314t$ . Find (i) the peak value of current (ii) the dc value of current and (iii) the rms value of current.

 [Watch Video Solution](#)

**22.** Assume that the silicon diode in the circuit shown in fig. requires a minimum current of  $1\text{mA}$  to be above the knee point ( $0.7\text{V}$ ) of its  $I - V$  characteristics. Also assume that the voltage across the diode is independent of current above the knee point.

(a) If  $V_B = 5\text{V}$ , what should be the maximum value of  $R$  so that the voltage is above the knee point?

(b) If  $V_B = 5\text{V}$ , what should be the value of  $R$  to establish the current of  $5\text{mA}$  in the circuit?

(c) What is the power dissipated in the resistance  $R$  and in the diode, when a current of  $5\text{mA}$  flows in the circuit at  $V_B = 6\text{V}$ ?

(d) If  $R = 1\text{k}\Omega$ , what is the minimum voltage  $V_B$  required to keep the diode above the knee point?



**23.** In a  $p - n$  junction diode, the current  $I$  can be expressed as  $I = I_0 \exp\left(\frac{eV}{2k_B T} - 1\right)$  where  $I_0$  is called the reverse saturation current,  $V$  is the voltage across the diode and is positive for forward bias and negative for reverse bias, and  $I$  is the current through the diode,  $k_B$  is the Boltzmann constant ( $8.6 \times 10^{-5} \text{ eV/K}$ ) and  $T$  is the absolute temperature. If for a given diode  $I_0 = 5 \times 10^{-12} \text{ A}$  and  $T = 300 \text{ K}$ , then

(a) What will be the forward current at a forward voltage of  $0.6 \text{ V}$  ?

(b) What will be the increase in the current if the voltage across the diode is increased to  $0.7 \text{ V}$  ?

(c) What is the dynamic resistance ?



(d) What will be current if reverse bias voltage changes from  $1V$  to  $2V$  ?

 [Watch Video Solution](#)

**24.** In a common emitter transistor circuit, if the collector-emitter voltages changes by  $0.2V$ , the collector current changes by  $0.004mA$ . What is the output resistance of the circuit,

 [Watch Video Solution](#)

**25.** If a change of  $100\mu A$  in the base current of an  $n - p - n$  transistor in  $CE$  causes a change of  $10mA$  in

the collector current, the *ac* current gain of the transistor is

 [Watch Video Solution](#)

**26.** What is the change in the collector current, in a transistor of a.c. current gain 150 for a  $100\mu A$  change in its base current?

 [Watch Video Solution](#)

**27.** A transistor has a current gain of 30. If the collector resistance is  $6k\Omega$ , input resistance is  $1k\Omega$ , calculate its voltage gain?

 [Watch Video Solution](#)

 Watch Video Solution

**28.** For a transistor connected in common emitter mode, the voltage drop across the collector is  $2V$  and  $\beta$  is 50. Find the base current is  $R_C$  is  $2K$

 Watch Video Solution

**29.** In a transistor connected in a common emitter mode it has,  $R_c = 4k\Omega$ ,  $R_i = 1k\Omega$ ,  $I_c = 1mA$  and  $I_b = 20\mu A$ . Find the voltage gain.


 Watch Video Solution

30. In a silicon transistor, a change of  $80\text{mA}$  emitter current produces a change of  $7.9\text{mA}$  in the collector current. What change in the base current is necessary to produce an equivalent change in the collector current?

Find the values of  $\alpha$  and  $\beta$ .

 [Watch Video Solution](#)

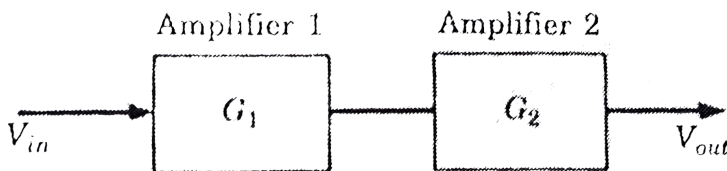31. Two amplifiers are connected as shown in fig. Find  $V_0$  if  $G_1 = 20$ ,  $G_2 = 10$  and  $V_{in} = 50, V$ .  $V_Z = 10V$  for each diode.



 [Watch Video Solution](#)

**32.** A transistor has  $\alpha = 0.95$ . If the emitter current is  $10\text{mA}$ , what is (a) the collector current, (b) the base current and (iii) gain  $\beta$ ?

 [Watch Video Solution](#)

**33.** The input resistance of a silicon transistor is  $665\Omega$ . Its base current is changed by  $15\mu\text{A}$  which results in the change in collector current by  $2\text{mA}$ . This transistor is used as a common emitter amplifier with a load resistance of  $5\text{k}\Omega$ . What is the voltage gain of the amplifier.

 [Watch Video Solution](#)

**34.** In a silicon transistor, base current is changed by  $20\mu A$ . This result in a change of  $0.02V$  in base-emitter voltage and a change of  $2mA$  in the collector current.

Find the input resistance,  $\beta_{a.c.}$  and transconductance of the transistor.

The transistor is used as an amplifier with the load resistance  $5k\Omega$ . What is the voltage gain of the amplifier?




[Watch Video Solution](#)

**35.** In a transistor amplifier  $\beta = 62$ ,  $R_L = 5000\Omega$  and internal resistance of the transistor  $= 500\Omega$ . Calculate the voltage amplification and power amplification.




[Watch Video Solution](#)

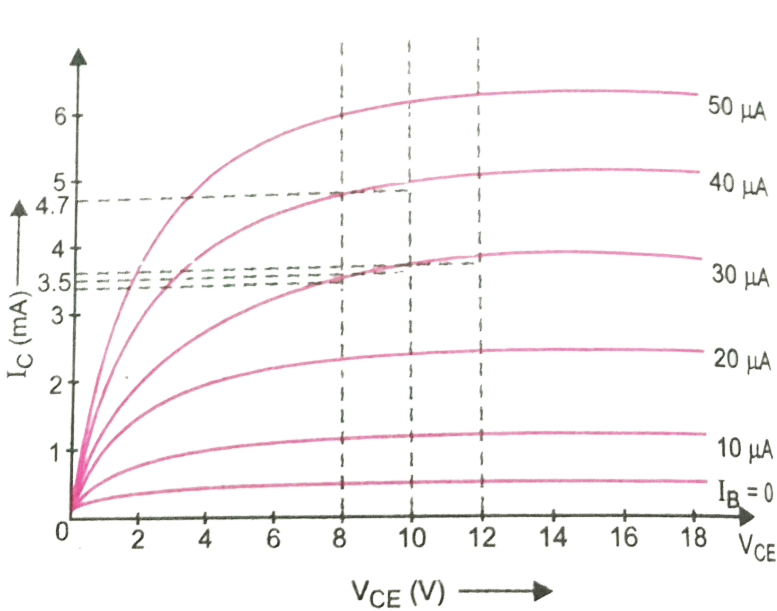36. Output characteristics of an n-p-n transistor in CE configuration is shown in the Fig. Determine



(i) dynamic output resistance (ii) dc current gain and (iii) ac current gain at an operating point  $V_{CE} = 10V$ , when  $I_B = 30 \mu A$ .

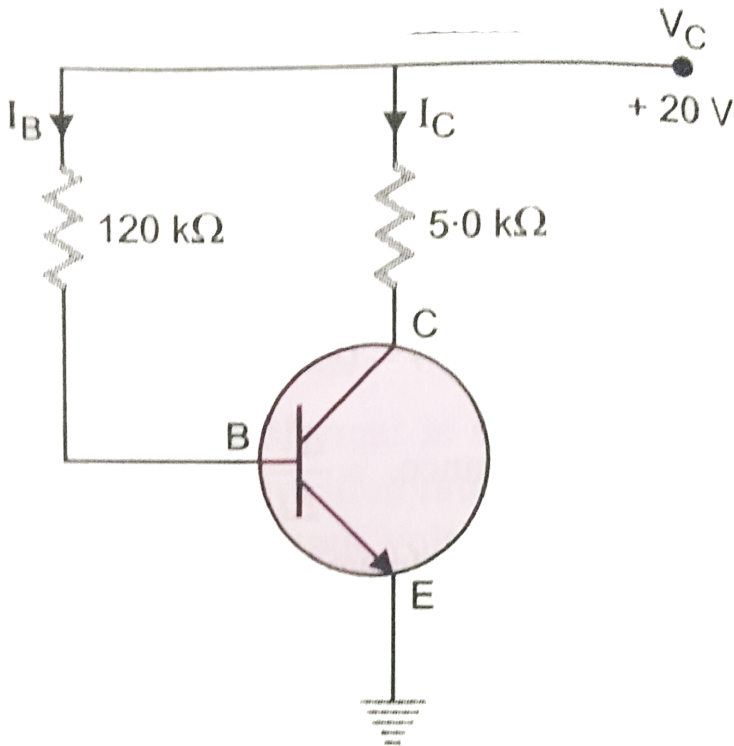37. In the circuit Fig. the value of beta is 200. Find  $I_B$ ,  $V_{CE}$ ,  $V_{BE}$  and  $V_{BC}$ , when  $I_C = 2.5\text{mA}$ . The transistor is in active, cut off or saturation state.



Watch Video Solution



**38.** In the circuit shown in fig., the base current  $I_B$  is  $10\mu A$  and the collector current is  $5.2mA$ . (a) Can this transistor circuit be used as an amplifier? (b) What happen if the resistance  $R_C$  is  $500\Omega$  and  $I_B$ ,  $I_C$  and  $R_B$  remain same as above?



[View Text Solution](#)

**39.** In the circuit shown in Fig.

if we assume that when the input voltage at the base resistance is  $5V$ ,  $V_{BE}$  is zero and  $V_{CE}$  is also zero. What is  $I_B$ ,  $I_C$  and beta?

When the input is zero, then  $I_B$  is zero. What would be

the output wave form if the input wave form is as shown in Fig.

 [Watch Video Solution](#)

**40.** An amplifier is represented by the adjoining circuit.  $r_i$  is the input resistance of the amplifier and the voltage  $v_i$  is appearing across it. This voltage is amplified by a factor of  $A_v$  and appears across the load as voltage  $v_o$ .

 [View Text Solution](#)


**41.** Fig represents an amplifier circuit with an input internal resistance  $r_i = 50k\Omega$ . It is connected to an ac voltage source through a series resistor of  $100k\Omega$ . The no

load voltage gain of the transistor is 100. What is the apparent gain of the amplifier?

[View Text Solution](#)

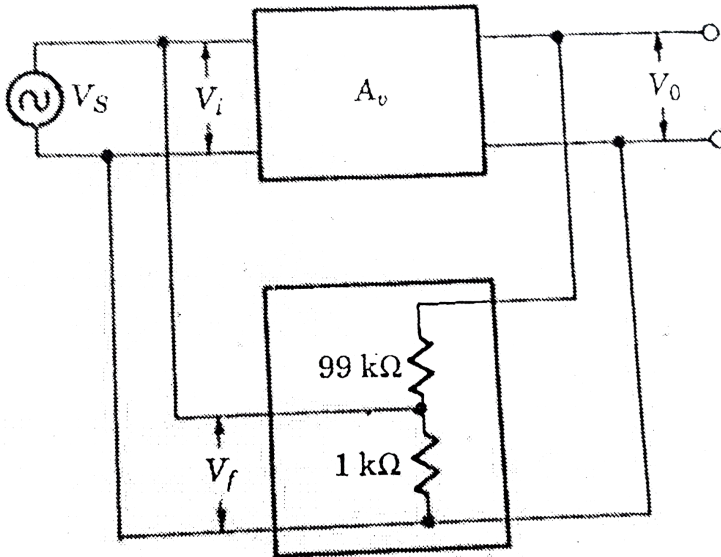42. In the circuit, shown in fig  $v_s = 0.2V$ ,  $v_0 = -10V$ .

Find  $v_i$  and gain  $A_v = v_0/v_i$  and  $A'_v = \frac{v_0}{v_s}$ ?



[View Text Solution](#)

**43.** Perform binary addition on the following sets numbers.

(a) 110010 and 111101 (b) 101010 and 010101 (c) 111111 and 000001

 [Watch Video Solution](#)

**44.** Complement (1's) the following binary numbers.

(a) 110010 (b) 111101 (c) 101010 (d) 11111

 [Watch Video Solution](#)

**45.** Find the 2's complement of the following numbers?

(a) 111111 (b) 000000 (c) 101010 (d) 001001



[Watch Video Solution](#)

**46.** Perform subtraction on the following sets of numbers.

(a) 110010 and 111101 (b) 010101 and 101010 (c) 1000001  
and 1111111



[Watch Video Solution](#)


**47.** Write the output waveform of the OR gate for the

inputs




[Watch Video Solution](#)

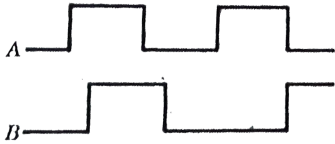48. Two input waveforms  $A$  and  $B$  shown in fig (a) are applied to an AND gate. Write the output waveform.



(a)

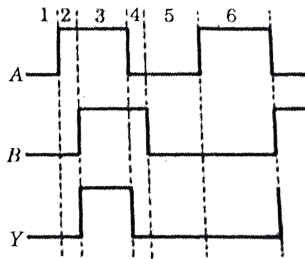

(b)



Watch Video Solution

49. Write the output waveform for the gates




View Text Solution

50. Write the Boolean equation and the truth table for the circuit shown in fig. What will be the output if both inputs are high?

[View Text Solution](#)

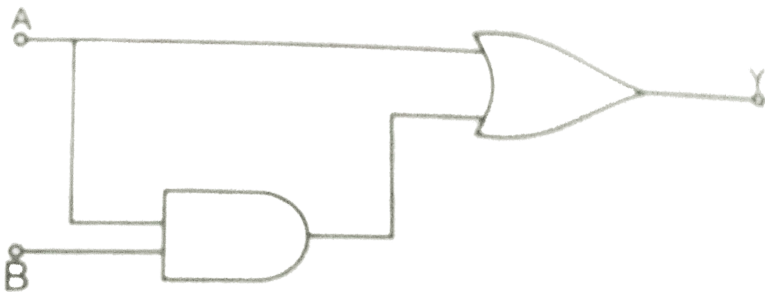51. Express by a truth table, the output Y for all possible input A and B in the following circuit Fig.



[Watch Video Solution](#)

**52.** The output of an OR gate is connected to both the input of a NOR gate. Draw the logic circuit of the combination and write the truth table.



**Watch Video Solution**

**53.** The output of an AND gate is connected to both the inputs of a NAND gate. Draw the logic circuit of this combination of gates and write its truth table.




**Watch Video Solution**

**54.** Identify which basic gate, OR, AND and NOT is represented by the circuits in the dotted line boxes 1, 2




and 3 Fig.

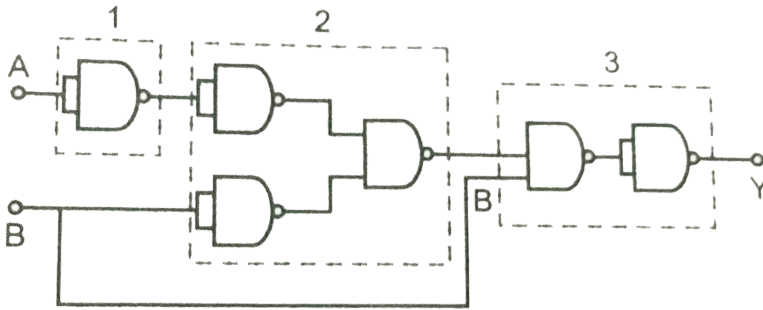


[▶ Watch Video Solution](#)

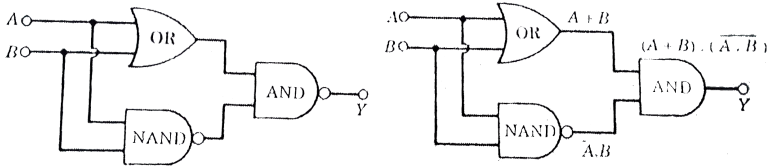55. Write the truth table for the circuit shown in fig. Show that it represents a XOR gate.



[▶ Watch Video Solution](#)

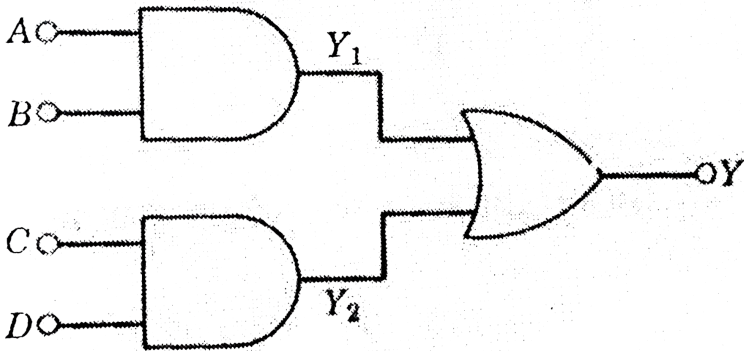56. Write the Boolean equation and the truth table for the circuit shown in fig. Which input words does the circuit recognise?



[▶ Watch Video Solution](#)

## Problem Type

1. Mobilities of electrons and holes in a sample of intrinsic germanium at room temperature are  $0.54m^2V^{-1}s^{-1}$

and  $0.18m^2V^{-1}s^{-1}$  respectively.

If the electron and hole densities are equal to  $3.6 \times 10^{19}m^{-3}$  calculate the germanium conductivity.



[Watch Video Solution](#)

2. An  $n$ -type silicon sample of width  $4 \times 10^{-3}m$ , thickness  $25 \times 10^{-5}m$  and length  $6 \times 10^{-2}m$  carries a current of  $4.8mA$  when the voltage is applied across the length of the sample. What is the current density? If the free electron density is  $10^{22}m^{-3}$  then find how much time does it take for the electrons to travel the full length of the sample?



[View Text Solution](#)

3. In n-p-n transistor circuit, the collector current is  $10\text{mA}$ . If 90% of the holes reach the collector, find emitter and base currents.

 [Watch Video Solution](#)

4. In an n-p-n transistor  $10^{10}$  electrons enter the emitter in  $10^{-6}\text{s}$ . If 2% of the electrons are lost in the base, find the current transfer ratio and the current amplification factor.

 [Watch Video Solution](#)

5. For a semiconductor of band energy gap  $1.5eV$ , calculate the wave-length of the emitted radiation when a conduction band electron combines with a valence band hole. Given Planck's constant  $6.6 \times 10^{-34} Js$



[Watch Video Solution](#)

6. A  $10V$  Zener diode along with a series resistance  $R$  is connected across a  $40V$  supply. Calculate the minimum value of the resistance, as required, if the maximum Zener current is  $50mA$ .



[Watch Video Solution](#)

7. A transistor is connected in common emitter configuration. The collector supply is 8V and the voltage drop across a resistor of  $800\Omega$  in the collector circuit is 0.5 V. If the current gain factor ( $\alpha$ ) is 0.96, find the base current.



[Watch Video Solution](#)

8. An n - p - n transistor is connected in common - emitter configuration in which collector supply is 8 V and the voltage drop across the load resistance of  $800\Omega$  connected in the collector circuit is 0.8 V . If current amplification factor is 25 , determine collector - emitter voltage and base current . If the internal resistance of the


transistor is  $200\Omega$  , calculate the voltage gain and the power gain.



[Watch Video Solution](#)

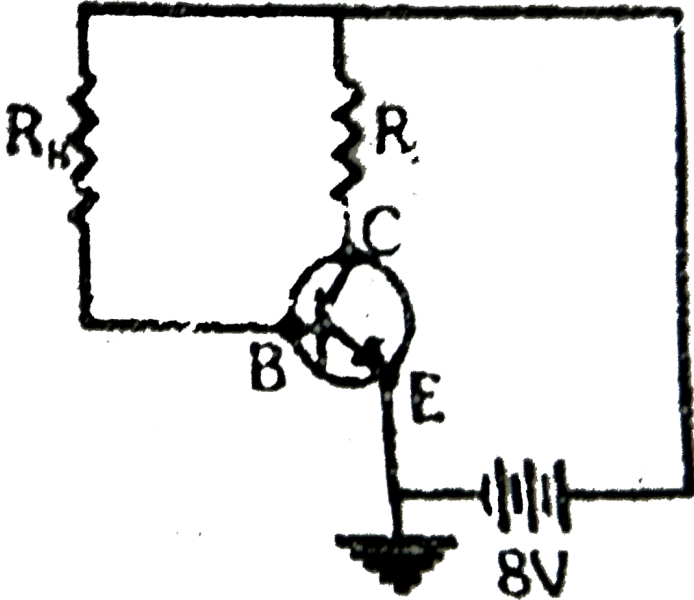9. An n-p-n transistor in a common emitter mode is used as a simple voltage amplifier with a collector connected to load resistance  $R_L$  and to the base through a resistance  $R_B$ . The collector-emmitter voltage  $V_{CE} = 4V$ , the base-emitter voltage  $V_{BE} = 0.6V$ , current through collector is  $4mA$  and the current amplification factor

$\beta = 100$  Calculate the value of  $R_L$  and  $R_B$ .



[▶ Watch Video Solution](#)

Others



1. The energy of a photon of sodium light ( $\lambda = 589nm$ ) equal the band gap of a semiconducting material.(a)Find the minimum energy  $E$  required to create a hole-electron pair.(b)Find the value of  $E/kT$  at a temperature of 300K.



[Watch Video Solution](#)

2. A doped semiconductor has impurity levels  $30meV$  below the conduction band. Is the material  $n$ -type or  $p$ -type? Find the maximum wavelength of ight so that an electron of impurity level is just able to jump to into conduction band.



[View Text Solution](#)

3. The band gap of an alloy semiconductor galliumarsenide phosphide is  $1.98\text{eV}$ . Calculate the wavelength of radiation that is emitted when electrons and holes in this material combine directly. What is the colour of the emitted radiation? Take  $h = 6.6 \times 10^{-34}\text{Js}$



[Watch Video Solution](#)

4. The number density of electrons and holes in intrinsic silicon at a given temperature is  $4.94 \times 10^{10}\text{cm}^{-3}$ . Calculate the resistivity and conductivity of the silicon. Given electron mobility  $= 100\text{cm}^2\text{V}^{-1}\text{s}^{-1}$  and hole mobility  $= 1000\text{cm}^2\text{V}^{-1}\text{s}^{-1}$



[View Text Solution](#)

5. Determine the number density of donor atoms which have to be added to an intrinsic germanium to produce an  $n$ -type semiconductor of conductivity  $0.06 \text{ Sm}^{-1}$ . Given the mobility of electrons  $= 0.39 \text{ m}^2 \text{ V}^{-1} \text{ s}^{-1}$ . Neglect the contribution of holes to the conductivity.



[Watch Video Solution](#)

6. Germanium is doped one part million with indium at room temperature. Calculate the conductivity of doped germanium. Given: concentration of Ge atoms  $= 4.4 \times 10^{28} \text{ m}^{-3}$ , intrinsic carrier concentration

$$(n_i) = 2.4 \times 10^{19} m^{-3}, \mu_e = 0.39 m^2 V^{-1} s^{-1} \quad \text{and}$$

$$\mu_k = 0.19 m^2 V^{-1} s^{-1}$$

 [View Text Solution](#)

7. Determine the conductivity and resistivity of pure germanium at  $300K$  assuming that at this temperature the concentration of germanium is  $2.5 \times 10^{13} cm^{-3}$ . The electron and hole mobilities are  $3600 cm^2 V^{-1} s^{-1}$  and  $1700 cm^2 V^{-1} s^{-1}$  respectively.

 [View Text Solution](#)

8. The resistivity of pure germanium at a particular temperature is  $0.52 \Omega m$ . If the material is doped with  $10^{20}$

atoms  $m^{-3}$  of a trivalent impurity material, determine the new resistivity. The electron and hole mobilities are given to be  $0.2$  and  $0.4m^2V^{-1}s^{-1}$  respectively.

 [Watch Video Solution](#)

9. A sample of germanium is doped to the extent of  $10^{14}$  donor atoms per  $cm^3$  and  $7 \times 10^{13}$  acceptor atoms per  $cm^3$ . The resistivity of pure germanium at the temperature of the sample is  $60\Omega cm$ . Find the total conduction current density due to an applied electric field of  $2Vcm^{-1}$ . The electron and hole mobilities are given to be  $3800cm^2V^{-1}s^{-1}$  and  $1800cm^2V^{-1}s^{-1}$ , respectively.

 [View Text Solution](#)

**10.** The energy gap in germanium is  $0.75\text{eV}$ . Compare the intrinsic conductivities of germanium at  $300\text{K}$  and  $330\text{K}$ .

Take  $k_B = 8.6 \times 10^{-5}\text{eVK}^{-1}$

 [View Text Solution](#)

**11.** In a photodiode the conductivity increases when the material is exposed to light. It is found that conductivity change only if the wavelength is less than  $600\text{nm}$ . What is the band gap?

 [Watch Video Solution](#)



**12.** When the voltage drop across a  $p - n$  junction diode is increased from  $0.70V$  to  $0.71V$  the change in the diode current is  $10mA$ . What is the dynamic resistance of the diode?

 [View Text Solution](#)

**13.** A  $P - N$  junction diode can withstand currents up to  $10mA$ . Under forward bias, The diode has a potential drop of  $0.5V$  across it which is assumed to be independent of current. The maximum voltage of the battery used to forward bias the diode when a resistance of  $200\Omega$  is connected in series with it is

 [Watch Video Solution](#)

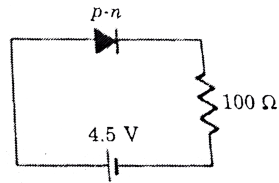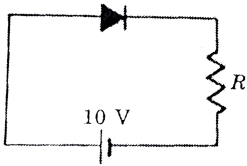14. The silicon diode shown in fig. is rated for a maximum current of  $10\text{mA}$ . Calculate the minimum value of resistor  $R$ . Assume the forward voltage drop across the diode to be  $0.7\text{V}$ .




 [Watch Video Solution](#)

15. Figure Shows a diode connected to an external resistance and an e.m.f. Assuming that the barrier potential developed in diode is  $0.5\text{V}$ , obtain the value of




current in the circuit in milliamperes.

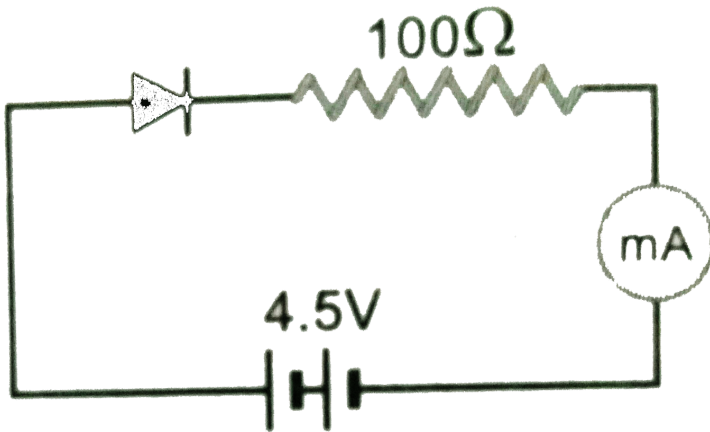

[▶ Watch Video Solution](#)


**16.** Find the current through the circuit and the potential difference across the diode shown in fig. The drift current

for the diode is  $20\mu A$

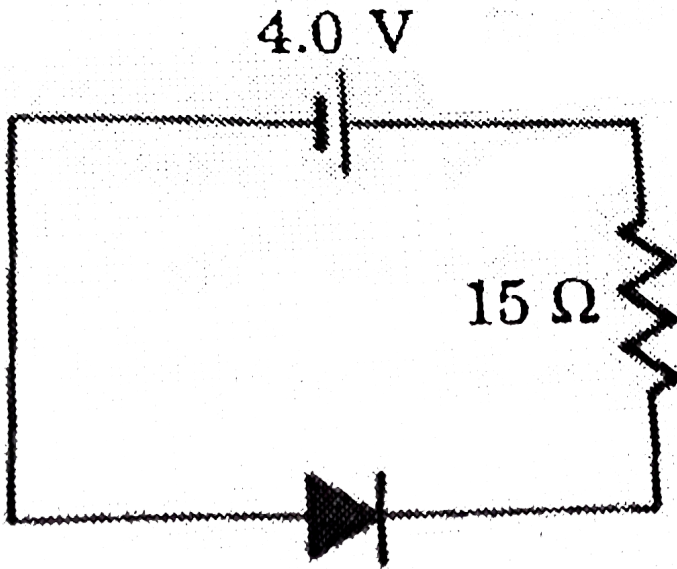


[Watch Video Solution](#)

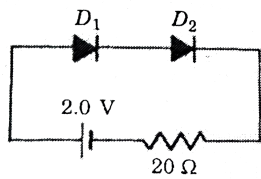
17. Determine the currents through the resistance of the circuits shown in fig.




(a)

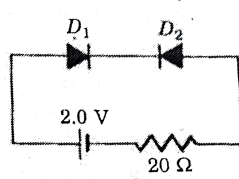

(b)

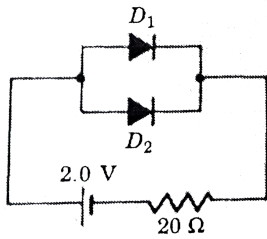



(c)

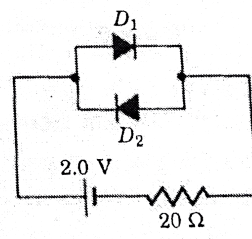

(d)


 [Watch Video Solution](#)

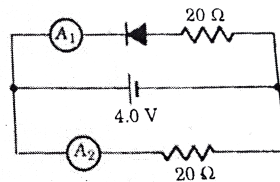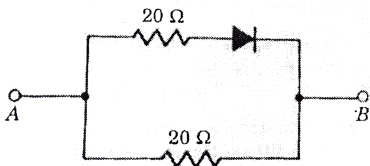**18.** Find the equivalent resistance of the circuit shown in fig between the points *A* and *B*



 [Watch Video Solution](#)

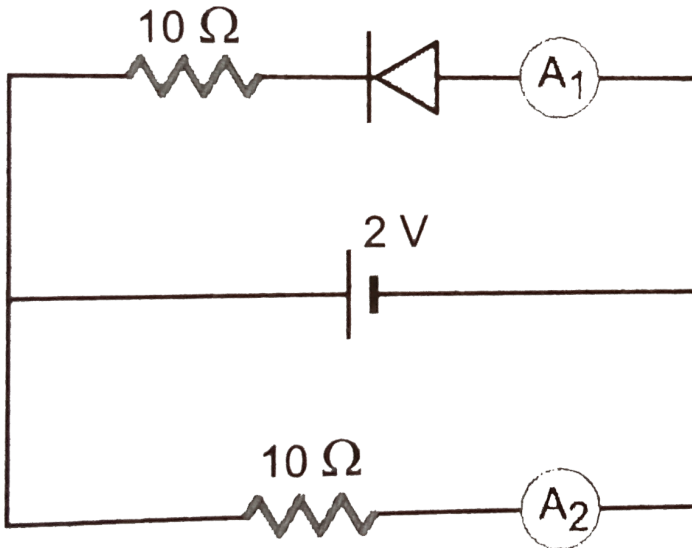19. Assuming that the resistance of the meters are negligible, what will be the readings of the ammeters  $A_1$  and  $A_2$  in the circuit shown in Fig.



[▶ Watch Video Solution](#)

20. A potential barrier of  $0.60V$  exists across a p-n junction. If the depletion region is  $6.0 \times 10^{-7}m$  wide, what


is the intensity of the electric field in this region. An electron with speed  $5.0 \times 10^5 \text{ m s}^{-1}$  approaches the p-n junction from the n-side, with what speed will it enter p-side.



[Watch Video Solution](#)

**21.** A sinusoidal voltage of rms value  $220\text{V}$  is applied to a diode and a resistor  $R$  in the circuit shown in fig. Show that half wave rectification occurs. If the diode is ideal,

what is the rms voltage across?

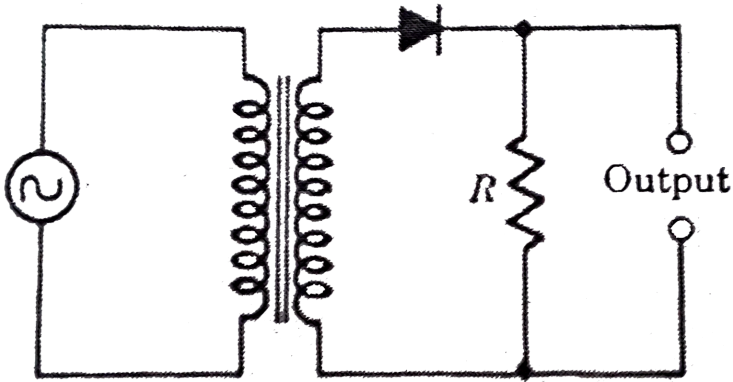

[View Text Solution](#)

22. In a full wave junction diode rectifier, the input a.c. has an rms value of  $10V$ . The transformer used is a step up transformer having transformation ratio  $1:2$ . Calculate the d.c. and a.c. voltages in the rectified output.

[Watch Video Solution](#)

**23.** The applied input a.c. power to a half wave rectifier is 100 watt. The d.c. output power obtained is 40 watt. (i) What is the rectification efficiency and (ii) What is the power efficiency?



[Watch Video Solution](#)

**24.** A crystal diode having internal resistance  $200\Omega$  is used as a half rectifier. If the applied voltage is  $V = 50 \sin \omega t$  volt and load resistance is  $800\Omega$ , find (i) maximum output current (ii) d.c. output current (iii) d.c. output power and (iv) d.c. output voltage.



[View Text Solution](#)

25. A transistor has a current gain of 50. If the collector resistance is  $5k\Omega$  and the input resistance is  $1k\Omega$  (approx), find the voltage gain of the amplifier.



Watch Video Solution

26. When the emitter current of a transistor is changed by  $1mA$ , its collector current changes by  $0.995mA$ . Calculate its CB current gain  $\alpha$  and CE current gain  $\beta$



Watch Video Solution

27. A transistor has a base current of  $0.08mA$  and the emitter current is  $10mA$ , . Determine (a) the collector



current (b)  $\alpha$  and (c)  $\beta$



Watch Video Solution

**28.** A transistor has  $\alpha = 0.95$ . If the emitter current is  $10\text{mA}$ , what is (a) the collector current, (b) the base current and (iii) gain  $\beta$ ?



Watch Video Solution

**29.** The collector current for a transistor is  $6.6\text{mA}$ , and its current gains  $\alpha$  is  $0.95$ . Determine  $I_B$  and  $\beta$



Watch Video Solution

**30.** The current gain of a transistor in common base arrangement is 0.95. Find the voltage gain and power gain if load resistance is  $200\Omega$



**Watch Video Solution**

**31.** For a *CB* amplifier the input resistance is  $800\Omega$  and the output resistance is  $600k\Omega$  (a) Determine the voltage gain if the emitter current is  $12mA$  and  $\alpha = 0.97$  (b) What is the power gain?



**Watch Video Solution**

**32.** The power gain for common base amplifier is 800 and the voltage amplification factor is 840. The collector current when base current is 1.2 mA is

 [Watch Video Solution](#)

**33.** The current gain of a transistor in CB configuration is 0.98. Find the change in collector current corresponding to a change of  $5.0\text{mA}$  in the emitter current. What would be the change in base current?

 [Watch Video Solution](#)

**34.** In common-emitter transistor amplifier the load resistance of the output circuit is 1000 times the load resistance of the input circuit. If  $\alpha = 0.98$ , then calculate the voltage gain.



[Watch Video Solution](#)

**35.** In a common -emitter transistor amplifier, an increase of  $50\mu A$  in the base current causes an increase of  $1.0mA$  in the collector current . Calculat gain  $\beta$ . What will be the change in emitter current? Also calculate current gain  $\alpha$



[Watch Video Solution](#)

**36.** The base current of a transistor is  $0.105 \text{ mA}$  and collector current is  $2.05 \text{ mA}$ .

Determine the value of  $\beta$ ,  $I_e$  and  $\alpha$

A change of  $27 \mu\text{A}$  in the base current produces a change of  $0.65 \text{ mA}$  in the collector current. Find  $\beta_{a.c.}$ .





**Watch Video Solution**

**37.** A transistor is used in common-emitter mode in an amplifier circuit. When a signal of  $30 \text{ mV}$  is added to the base-emitter voltage, the base current changes by  $30 \mu\text{A}$  and collector current by  $3 \text{ mA}$ . The load resistance is  $5 \text{ k}\Omega$ . Calculate (i) the current gain  $\beta_{ac}$  (ii) the input

resistance  $R_{BE}$  (iii) trans-conductance and (iv) voltage gain.

 Watch Video Solution

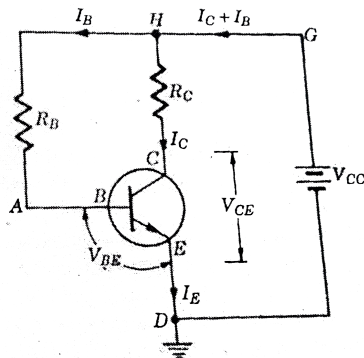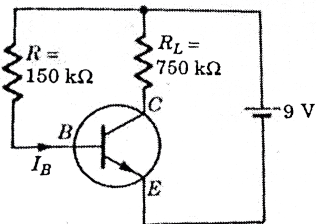**38.** In a transistor circuit shown in fig,  $R$  has a resistance of  $150\text{ k}\Omega$ ,  $R_L$  has a resistance of  $750\Omega$ , and the direct current gain of the transistor is 80. Assuming there is negligible potential difference between  $B$  and  $E$ , calculate (a) the base current  $I_B$  and (b) the potential difference between the collector and emitter.





[Watch Video Solution](#)

**39.** In the circuit shown in fig the base current  $I_B = 5.0\mu A$ , base resistor  $R_B = 1.0M\Omega$  collector resistor  $R_c = 1.0k\Omega$  the collector current  $I_C = 5.0mA$  and the d.c. voltage in the collect circuit  $V_{CC} = 6.0V$ . (i) Can this circuit be used as an ampifier? (ii) What happens if the resistance  $R_C$  is  $400\Omega$  and  $I_B$ ,  $I_C$  and  $i_C$  and  $R_B$  remain same as above?



[View Text Solution](#)

**40.** As shown in fig an amplifier of no load gain 400 and input resistance  $100\Omega$  is connected to external signal via

a series resistance of  $300\Omega$ . What is the apparent voltage gain?

 [View Text Solution](#)

**41.** How 2-input NAND gate can be converted into a NOT gate?


 [Watch Video Solution](#)

**42.** Write the truth table of a two input NOR gate. Explain, using a logic circuit, how a NOR gate can be converted into an AND gate.

 [Watch Video Solution](#)




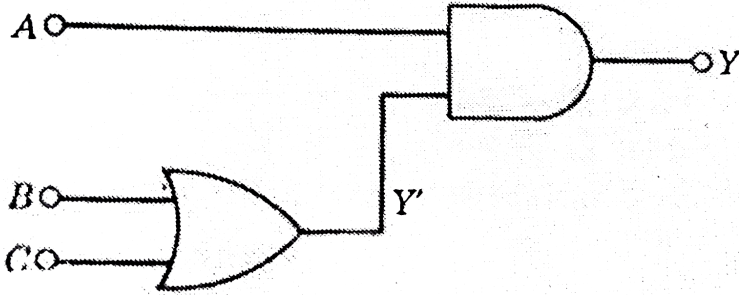43. Write the Boolean equation and the truth table for the following circuit?




[▶ Watch Video Solution](#)

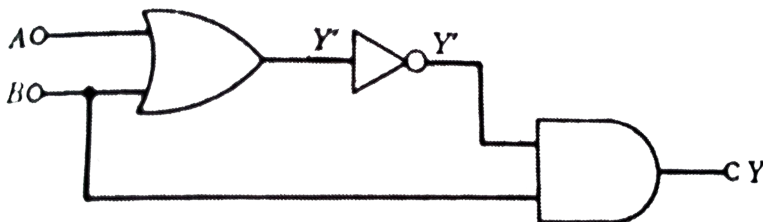44. Write the truth table for the following circuit:




[▶ Watch Video Solution](#)

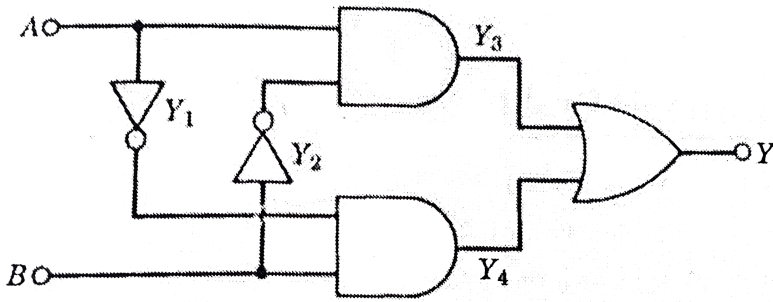45. Write the logic table for the following circuit:



 Watch Video Solution

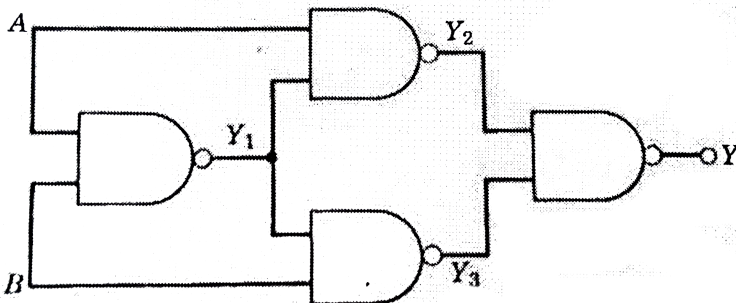46. Write the truth table for the following circuit? Give the name of the resulting gate.




Watch Video Solution

 Watch Video Solution

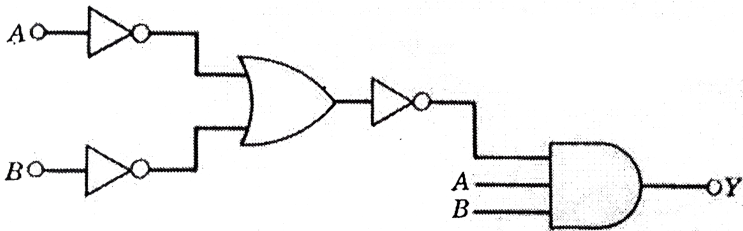47. Find the output  $Y$  of the following circuit if the inputs are:

$A = 0, B = 0, A = 0, B = 1, A = 1, B = 0, A = 1, B = 1$



 Watch Video Solution