



PHYSICS

BOOKS - BITSAT GUIDE

ALTERNATING CURRENT AND EM WAVE

Practice Exercise

1. An Ac source of volatage $V=100 \sin 100\pi t$ is connected to a resistor of ressistance 20Ω The

rms value of current through resistor is

A. $10A$

B. $\frac{10}{\sqrt{2}}A$

C. $\frac{5}{\sqrt{2}}A$

D. non of these

Answer:



Watch Video Solution

2. An AC source of voltage $V=100 \sin 100\pi t$ is connected to a resistor of resistance 20Ω . The rms value of current through resistor is average value of current for half cycle is

A. zero

B. $\frac{5}{\sqrt{2}} A$

C. $10A$

D. non of these

Answer:



Watch Video Solution

3. An Ac source of volatage $V=100 \sin 100\pi t$ is connected to a resistor of ressistance 20Ω The rsm value of current through resistor is the averge value for half cycle is

A. $\frac{10}{\pi} A$

B. $\frac{5}{\pi} A$

C. zero

D. non of these

Answer:



Watch Video Solution

4. An Ac source of volatage $V=100 \sin 100\pi t$ is connected to a resistor of ressistance 20Ω The rsm value of current through resistor is total charge transferred through resistor in long time is

A. zero

B. $\frac{2l_0}{\pi}$

C. $\frac{l_0}{25\pi}$

D. non of these

Answer:



Watch Video Solution

5. An Ac source of volatage $V=100 \sin 100\pi t$ is connected to a resistor of ressistance 20Ω The rsm value of current through resistor is ,total charge transferred in $1/100$ second is

A. $\frac{1}{10\pi}C$

B. $\frac{1}{5\pi}C$

C. zero

D. non of these

Answer:



Watch Video Solution

6. An Ac source of volatage $V=100 \sin 100\pi t$ is connected to a resistor of ressistance 20Ω The

rms value of current through resistor is ,total
heat generated in one cycle is

A. $\sqrt{2}J$

B. 5 J

C. $4\sqrt{2}J$

D. zero

Answer:



Watch Video Solution

7. An Ac source of volatage $V=100 \sin 100\pi t$ is connected to a resistor of ressistance 20Ω The rsm value of current through resistor is , power factor is

A. 1

B. 0

C. $\frac{1}{2}$


D. non of these

Answer:



Watch Video Solution

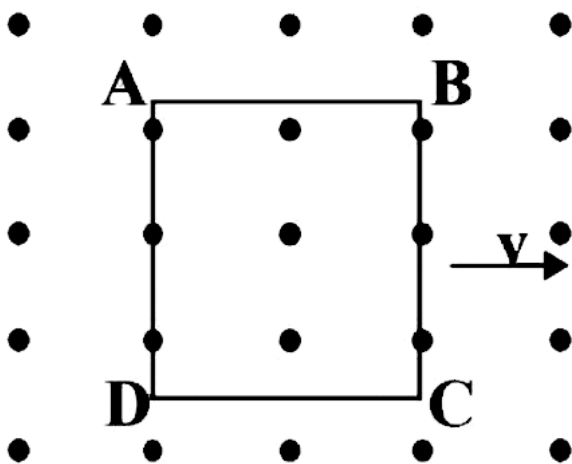8. A metallic square loop ABCD is moving in its own plane with velocity v in a uniform magnetic field perpendicular to its plane as shown in the figure. An electric field is induced



A. in AD, but not in BC

B. in BC, but not in AD

C. neither in AD nor in BC

D. in both AD and BC





Answer:




Watch Video Solution

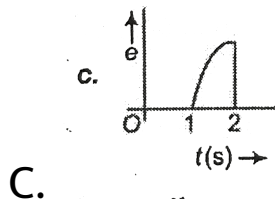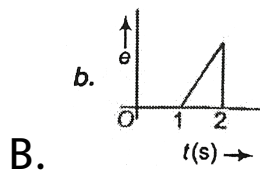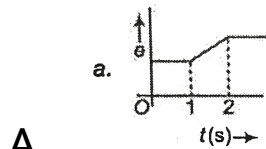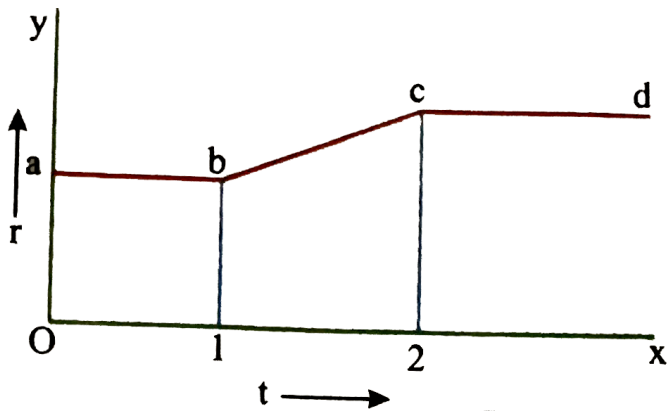9. A flexible wire bent in the form of a circle is placed in a uniform magnetic field perpendicular to the plane of the coil. The radius of the coil changes as shown in Figure.

The graph of magnetude of induced emf in the coil is represented by



D.

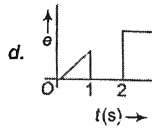


Answer:



[Watch Video Solution](#)

10. A uniform but time-varying magnetic field $B(t)$ exists in a circular region of radius a and is directed into the plane of the paper, as shown. The magnitude of the induced electric field at point P at a distance r from the centre

of the circular region

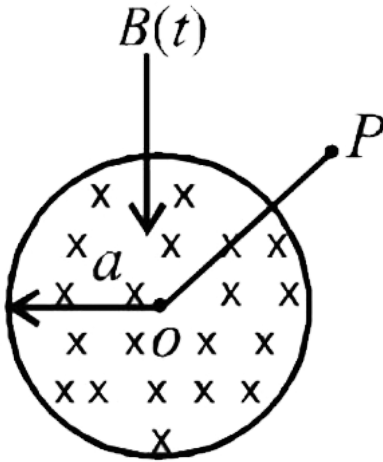

A. is zero

B. decreases as $1/r$

C. increases as r

D. decreases as $\frac{1}{r^2}$

Answer:



Watch Video Solution

11. Calculate the peak and rms value of current in AC circuit. The current is represented by the equation $i = 5 \sin(300t - \pi/4)$, where t is in second and I in ampere.

A. 5 A, 3.535 A

B. 5 A, 5.53 A

C. 3 A, 3.53 A

D. 6.25 A, 5.33 A

Answer:



Watch Video Solution

12. The average value for half cycle in a 200 V AC source is

A. 180 V

B. 200 V

C. 220 V

D. none

Answer:



Watch Video Solution

13. Two alternating current are given by

$$l_1 = l_0 \sin \omega t \text{ and } l_2 = l_0 \cos (\omega t + \phi)$$

The ratio of rms value is

A. 0.0423611111111111

B. $1 : \phi$

C. 0.0430555555555556

D. non of these

Answer:



Watch Video Solution

14. A current $I=3+8 \sin 100t$ is passing through a resistor of resistance 10Ω . The effective value of current is

A. $5A$

B. $10A$

C. $4\sqrt{2}A$

D. $3\sqrt{2}A$

Answer:



Watch Video Solution

15. An alternative voltage

$V=30 \sin 50t+40\cos 50t$ is applied to a resistor of resistance 10Ω . The rms value of current through resistor is

A. $\frac{5}{\sqrt{2}}$

B. $\frac{10}{\sqrt{2}}$

C. $\frac{7}{\sqrt{2}}$

D. $7A$

Answer:



[Watch Video Solution](#)

16. An alternating voltage $V=140 \sin 50 t$ is applied to a resistor of resistance 10Ω . This voltage produces ΔH heat in the resistor in

time Δt . To produce the same heat in the same time, required DC current is

- A. 14 A
- B. about 20 A
- C. about 10 A
- D. None of these

Answer:



Watch Video Solution

17. An Ac voltage is represented by $e=220 \sin (100\pi) t$ volt and is applied over a resistance of 110 ohm. Calculate the heat produced in 7 min.

A. 11×10^3 cal

B. 22×10^3 cal

C. 33×10^3 cal

D. 25×10^3 cal

Answer:



Watch Video Solution

18. What is the reactance of a capacitor connected to a constant DC source?

A. zero

B. ∞

C. 1Ω

D. None of these

Answer:



Watch Video Solution

19. The reactance of an inductor connected with DC voltage is

A. zero

B. ∞

C. 1Ω

D. None of these

Answer:



Watch Video Solution

20. An AC voltage

$e = e_0 \sin 50t - e_0 \cos 100\pi t$ is connected in series with a resistor and capacitor. The steady state current through circuit is found to be

$$I = I_0 \sin(50\pi t + \phi) + I_0' \cos(100\pi t + \phi_2)$$

Then, the ratio of $\frac{I_0}{I_0'}$ is

A. greater than 1

B. equal to 1

C. less than 1

D. None of these

Answer:



Watch Video Solution

21. An alternating voltage $V = V_0 \sin \omega t$ is connected to a capacitor of capacity C_0 through an AC ammeter of zero resistance.

The reading of ammeter is

A. $\frac{V_0}{\sqrt{2}}$

B. $\frac{V_0}{\omega C (\sqrt{2})}$

C. $\frac{V_0 \omega C}{\sqrt{2}}$

D. None of these

Answer:



Watch Video Solution

22. Calculate the maximum current in the circuit, if a capacitor of capacitance $1\mu F$ is charged to a potential of 2 V and is connected in parallel to an inductor of inductance $10^{-3} H$.

A. $\sqrt{4000} \text{ mA}$

B. $\sqrt{2000} \text{ mA}$

C. $\sqrt{1000} \text{ mA}$

D. $\sqrt{5000} \text{ mA}$

Answer:



Watch Video Solution

23. In a circuit consisting of inductor (L), capacitor (C) and resistor (R) are in series, if $\omega L < \frac{1}{\omega C}$, then the emf

- A. leads the current
- B. lags behind the current
- C. is in phase with current
- D. is zero

Answer:



Watch Video Solution

24. Find the resonant frequency of a series circuit consist of an inductance $200 \mu H$, a

capacitance of $0.0005\mu F$ and a resistance of $10\ \Omega$.

A. 480 kHz

B. 503 kHz

C. 406 kHz

D. 607 kHz

Answer:



Watch Video Solution

25. Find the frequency of voltage for an AC circuit. The equation of alternating voltage is

$$V = 200 \sin 314t.$$

A. 50 Hz

B. 60 Hz

C. 55 Hz

D. 65 Hz

Answer:



Watch Video Solution

26. An Ac circuit with $f=1000$ Hz consists of a coil of 200 mH and negligible resistance. Calculate the voltage across the coil, if the effective current of 5 mA is flowing.

- A. 7.64 V (rms)
- B. 7.452 V (rms)
- C. 6.28 V (rms)
- D. 74.62 V (rms)

Answer:



Watch Video Solution

27. Find the average power per unit area at distance of 2 m from a small bulb, if the bulb emits 20 W of electromagnetic radiation uniformly in all directions.

A. 0.69 W/m^2

B. 0.56 W/m^2

C. 0.78 W/m^2

D. 0.39 W/m^2

Answer:



Watch Video Solution

28. If a circuit made up of a resistance 1Ω and inductance 0.01 H , an alternating emf of 200 volt at 50 Hz is connected, then find the phase difference between the current and the emf in the circuit.

A. $\tan^{-1}(\pi)$

B. $\tan^{-1}\left(\frac{\pi}{2}\right)$

C. $\tan^{-1}\left(\frac{\pi}{4}\right)$

D. $\tan^{-1}\left(\frac{\pi}{3}\right)$

Answer:



Watch Video Solution

29. choose the correct option. If speed of gamma rays, X-rays and microwaves are V_g , V_x and V_m .

A. $V_g < V_x < V_m$

B. $V_g > V_x > V_m$

C. $V_g > V_x < V_m$

D. $V_g = V_x = V_m$

Answer:



Watch Video Solution

30. A condenser of capacitance of $2.4\mu F$, is used in a transmitter to transmit a λ wavelength. If the inductor of $10^{-8}H$ is used for resonant circuit, then value of λ is

A. 292 m

B. 400 m

C. 334 m

D. 446 m

Answer:



Watch Video Solution

31. If a dry cell of $\text{emf}=1.5\text{ V}$ is connected across the primary of a step-up transformer of turn

ratio 3:5, then calculate the voltage developed across the secondary.

A. 30 V

B. 5 V

C. zero

D. None of these

Answer:



Watch Video Solution

32. If at a certain instant, the magnetic induction of the electromagnetic wave in vacuum is $6.7 \times 10^{-12} \text{T}$, then the magnitude of electric field intensity will be

A. $2 \times 10^{-3} \text{ N/C}$

B. $3 \times 10^{-3} \text{ N/C}$

C. $4 \times 10^{-3} \text{ N/C}$

D. $1 \times 10^{-3} \text{ N/C}$

Answer:



Watch Video Solution

33. Find the energy of photon of electromagnetic radiation of wavelength 200 Å.

A. $1.76 \times 10^{-18} J$

B. $0.99 \times 10^{-18} J$

C. $0.54 \times 10^{-18} J$

D. $0.63 \times 10^{-18} J$

Answer:





34. Find the speed of light in air, if an electromagnetic wave is travelling in air whose dielectric constant is $K = 1006$.

A. $3 \times 10^8 \text{ m/s}$

B. $3.88 \times 10^8 \text{ m/s}$

C. $2.5 \times 10^8 \text{ m/s}$

D. $4.6 \times 10^8 \text{ m/s}$

Answer:



Watch Video Solution

35. An object is placed at some distance from a radio station. If the interval between transmission and reception of pulses is $2.66 \times 10^{-2} \text{S}$, then find the distance.

A. 4000 km

B. 2000 km

C. 3000 km

D. 2500 km

Answer:



Watch Video Solution

36. Calculate the wavelength of a radio wave of frequency of 1 MHz.

A. 400 m

B. 300 m

C. 350 m

D. 200 m

Answer:



Watch Video Solution

37. The electric in an electromagnetic wave is given by $E = (100 \text{ N/C}) \sin \omega \left(t - \frac{X}{C} \right)$.

If the energy contained in a cylinder of cross-section 10 cm^2 and length 50 cm along the X-axis is $4.4 \times 10^{-8} \text{ J/m}^3$, then find intensity of the wave.

A. 12.4 W/m^3

B. $13.2W / m^3$

C. $15.7W / m^3$

D. $11.9W / m^3$

Answer:



Watch Video Solution

Bitsat Archives

1. A radio wave of intensity I is reflected by a surface. Find intensity (I), if pressure exerted

on the surface is $2 \times 10^{-8} \text{ N/m}^2$.

A. 3 N/m^2

B. 4 N/m^2

C. 6 N/m^2

D. 7 N/m^2

Answer:



Watch Video Solution

2. A TV tower has a height of 100 m. Find the area covered by the TV broadcast, if radius of the earth is 6400 km.

A. $380 \times 10^7 m^2$

B. $402 \times 10^7 m^2$

C. $595 \times 10^7 m^2$

D. $440 \times 10^7 m^2$

Answer:



Watch Video Solution

3. An electromagnetic wave with pointing vector $5 \text{ W} / \text{m}^2$ is absorbed by a surface of same area. If the force on the surface is 10^{-7} N, then area is

A. 6m^2

B. 3m^2

C. 60m^2

D. 4m^2

Answer:



Watch Video Solution

4. Voltage V and current I in AC circuit are given by $V = 50\sin(50t)$ volt, $I = 50 \sin(50t + \frac{\pi}{3})$ mA

The power dissipated in the circuit is

A. 5.0 W

B. 2.5 W

C. 1.25 W

D. zero

Answer:



Watch Video Solution

5. The produced rays in sonography are

- A. microwaves
- B. infrared waves
- C. sound waves
- D. ultrasound

Answer:



Watch Video Solution

6. The ratio of secondary and primary turns of step-up transformer is 4 : 1. If a current of 4A is applied to the primary, the induced current in secondary will be

A. 8A

B. 2A

C. 1A

D. 0.5A

Answer:



Watch Video Solution

7. The impedance of a circuit consist of 3Ω resistance and 4Ω reactance. The power factor of the circuit is

A. 0.4

B. 0.6

C. 0.8

D. 1

Answer:



Watch Video Solution

8. The time taken by the current to rise to 0.63 of its maximum value in a DC circuit containing inductance (L) and resistance [®] depends on

A. L only

B. R only

C. $\frac{L}{R}$

D. LR

Answer:




Watch Video Solution

9. Figure represents two bulbs B_1 and B_2 resistor R and inductor L. When the switch S in

turned

off, then

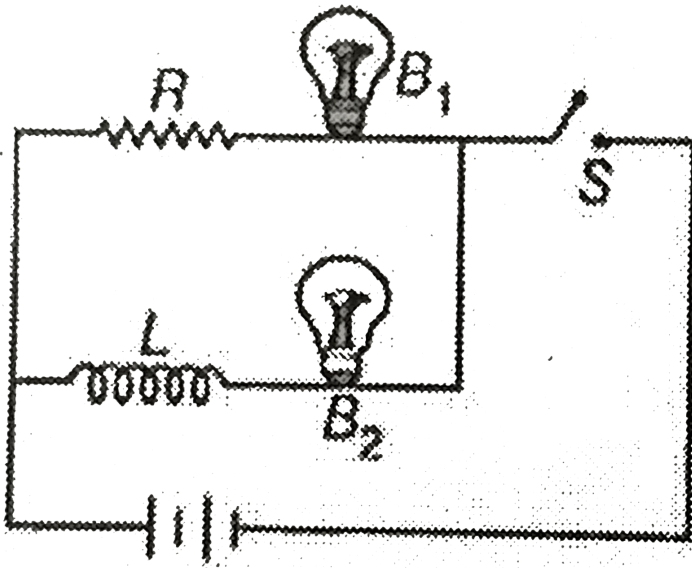

- A. both B_1 and B_2 die out promptly
- B. both B_1 and B_2 die out with some delay
- C. B_1 dies out promptly but B_2 with some delay

D. B_2 dies out promptly but B_1 with some delay


Answer:



[Watch Video Solution](#)

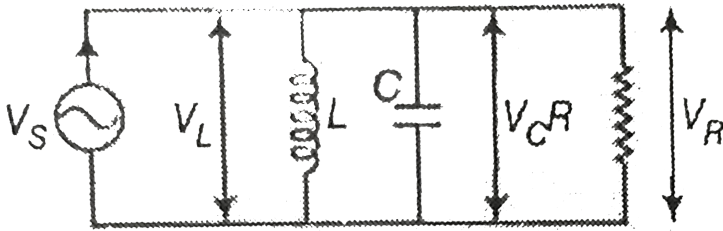10. An AC source is connected in parallel with an L-C-R circuit as shown. Let I_s, I_L, I_C and I_R denote the currents through and V_s, V_L, V_C and V_R the voltage

across the corresponding components. Then,



A. $l_S = l_L + l_C + l_R$

B. $V_S = V_L + V_C + V_R$

C. $(l_L, l_C, l_R) < l_S$

D. l_L, l_C may be greater than l_S

Answer:



Watch Video Solution

11. The number of turns in primary and secondary coils of a transformer is 50 and 200, respectively. If the current in the primary coil is 4 A, then current in the secondary coil is

A. 1A

B. 2A

C. 4A

D. 5A

Answer:



Watch Video Solution

12. An inductor of 2 H and a resistance of 10Ω are connected in series with a battery of 5 V. The initial rate of change of current is

A. 0.54A/s

B. 2.0 A/s

C. 2.5 A/s

D. 0.25 A/s

Answer:



Watch Video Solution

13. The transformation ratio in the step -up transformer is

A. 1

B. greater than one

C. less than one

D. the ratio greater or less than depends on the other factors

Answer:



Watch Video Solution

14. In a step-up transformer, if ratio of turns of primary to secondary is $1 : 10$ and primary voltage is 230 V . If the load current is 2 A , then current in primary is

A. 20 A

B. 10 A

C. 2 A

D. 1A

Answer:



Watch Video Solution

15. The square root of the product of inductance and capacitance has the dimension of

A. length

B. mass

C. time

D. no dimension

Answer:



Watch Video Solution