



# PHYSICS

## NCERT - NCERT PHYSICS(GUJRATI)

### ALTERNATING CURRENT

#### Example

1. A light bulb is rated at 100W for a 220 V supply. Find (a) the resistance of the bulb, (b)

the peak voltage of the source, and (c) the rms current through the bulb.



[Watch Video Solution](#)

2. A pure inductor of 25.0 mH is connected to a source of 220 V. Find the inductive reactance and rms current in the circuit if the frequency of the source is 50 Hz.



[Watch Video Solution](#)

3. A lamp is connected in series with a capacitor. Predict your observations for dc and ac connections. What happens in each case if the capacitance of the capacitor is reduced?



[Watch Video Solution](#)


4. A  $15.0 \mu F$  capacitor is connected to a 220 V, 50 Hz source. Find the capacitive reactance and the current (rms and peak) in the circuit. If

the frequency is doubled, what happens to the capacitive reactance and the current?



**Watch Video Solution**

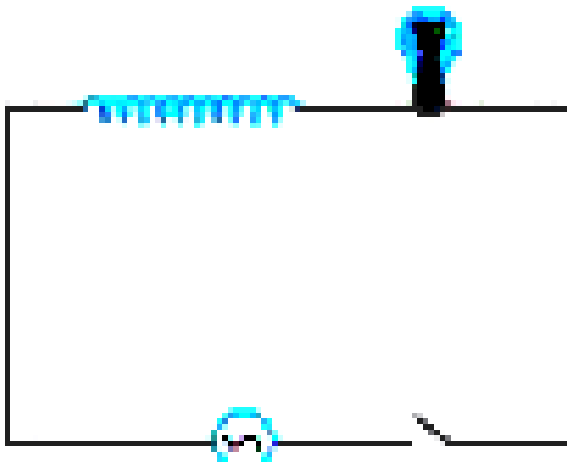5. A light bulb and an open coil inductor are connected to an ac source through a key as shown in Fig.



The switch is closed and after sometime, an iron rod is inserted into the interior of the inductor. The glow of the light bulb (a) increases, (b) decreases, (c) is unchanged, as the iron rod is inserted. Give your answer with reasons.



[Watch Video Solution](#)

**6.** A resistor of  $200 \Omega$  and a capacitor of  $15.0 \mu F$  are connected in series to a  $220 \text{ V}$ ,  $50 \text{ Hz}$  ac source. (a) Calculate the current in the circuit,

(b) Calculate the voltage (rms) across the resistor and the capacitor. Is the algebraic sum of these voltages more than the source voltage? If yes, resolve the paradox.



[Watch Video Solution](#)

7. (a) For circuits used for transporting electric power, a low power factor implies large power loss in transmission. Explain.

(b) Power factor can often be improved by the

use of a capacitor of appropriate capacitance in the circuit. Explain.



[Watch Video Solution](#)

8. A sinusoidal voltage of peak value 283 V and frequency 50 Hz is applied to a series LCR circuit in which

$$R = 3\Omega, L = 25.48mH, \text{ and } C = 796\mu F.$$

Find (a) the impedance of the circuit, (b) the phase difference between the voltage across the source and the current, (c) the power

dissipated in the circuit, and (d) the power factor.



[Watch Video Solution](#)

**9.** Suppose the frequency of the source in the previous example can be varied. (a) What is the frequency of the source at which resonance occurs? (b) Calculate the impedance, the current, and the power dissipated at the resonant condition.



[Watch Video Solution](#)



**10.** At an airport, a person is made to walk through the doorway of a metal detector, for security reasons. If she/he is carrying anything made of metal, the metal detector emits a sound. On what principle does this detector work?



**Watch Video Solution**

**11.** Show that in the free oscillations of an LC circuit, the sum of energies stored in the

capacitor and the inductor is constant in time.



[Watch Video Solution](#)

## Exercises

1. A  $100\ \Omega$  resistor is connected to a  $220\ \text{V}$ ,  $50\ \text{Hz}$  ac supply.

(a) What is the rms value of current in the circuit?

(b) What is the net power consumed over a full cycle?



[Watch Video Solution](#)

2. (a) The peak voltage of an ac supply is 300 V.

What is the rms voltage?

(b) The rms value of current in an ac circuit is 10 A. What is the peak current?



[Watch Video Solution](#)

3. A 44 mH inductor is connected to 220 V, 50 Hz ac supply. Determine the rms value of the current in the circuit.



[Watch Video Solution](#)

4. A  $60 \mu F$  capacitor is connected to a 110 V, 60 Hz ac supply. Determine the rms value of the current in the circuit.



[Watch Video Solution](#)

5. What is the net power absorbed by each circuit over a complete cycle. Explain your answer.



Watch Video Solution

6. Obtain the resonant frequency  $\omega_r$  of a series LCR circuit with  $L = 2.0H$ ,  $C = 32\mu F$  and  $R = 10\Omega$ . What is the Q-value of this circuit?



Watch Video Solution

7. A charged  $30 \mu F$  capacitor is connected to a 27 mH inductor. What is the angular frequency of free oscillations of the circuit?



Watch Video Solution

8. Suppose the initial charge on the capacitor in is 6 mC. What is the total energy stored in the circuit initially? What is the total energy at later time?



Watch Video Solution

9. A series LCR circuit with  $R = 20\Omega$ ,  $L = 1.5H$  and  $C = 35\mu F$  is

connected to a variable-frequency 200 V ac supply. When the frequency of the supply equals the natural frequency of the circuit, what is the average power transferred to the circuit in one complete cycle?



[Watch Video Solution](#)

**10.** A radio can tune over the frequency range of a portion of MW broadcast band: (800 kHz to 1200 kHz). If its LC circuit has an effective


inductance of  $200 \mu H$ , what must be the range of its variable capacitor?



[Watch Video Solution](#)

11. Figure shows a series LCR circuit connected to a variable frequency  $230 \text{ V}$  source.

$L = 5.0H, C = 80\mu F, R = 40\Omega$ .

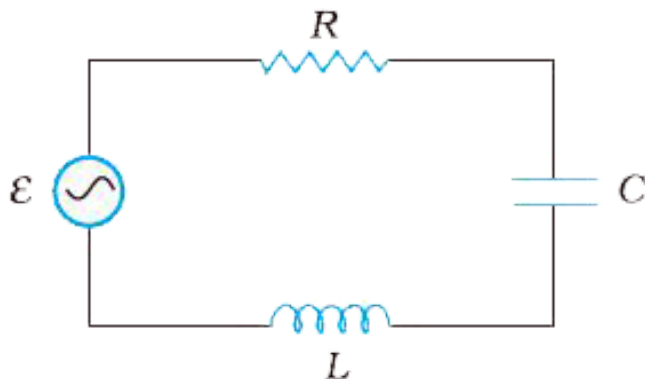

(a) Determine the source frequency which



drives the circuit in resonance.

(b) Obtain the impedance of the circuit and the amplitude of current at the resonating frequency.

(c) Determine the rms potential drops across the three elements of the circuit. Show that the potential drop across the LC combination is zero at the resonating frequency.



[Watch Video Solution](#)

**Additional Exercises**

1. An LC circuit contains a 20 mH inductor and a  $50 \mu\text{F}$  capacitor with an initial charge of 10 mC. The resistance of the circuit is negligible.

Let the instant the circuit is closed be  $t = 0$ .

(a) What is the total energy stored initially? Is it conserved during LC oscillations?

(b) What is the natural frequency of the circuit?

(c) At what time is the energy stored

(i) completely electrical (i.e., stored in the capacitor)? (ii) completely magnetic (i.e., stored in the inductor)?

(d) At what times is the total energy shared equally between the inductor and the capacitor?

(e) If a resistor is inserted in the circuit, how much energy is eventually dissipated as heat?



[Watch Video Solution](#)

2. A coil of inductance  $0.50 \text{ H}$  and resistance  $100\Omega$  is connected to a  $240 \text{ V}$ ,  $50 \text{ Hz}$  ac supply.

(a) What is the maximum current in the coil?

(b) What is the time lag between the voltage maximum and the current maximum?



**Watch Video Solution**

**3.** If the circuit is connected to a high frequency supply (240 V, 10 kHz). Hence, explain the statement that at very high frequency, an inductor in a circuit nearly amounts to an open circuit. How does an inductor behave in a dc circuit after the steady state?



[View Text Solution](#)

4. A  $100 \mu F$  capacitor in series with a  $40 \Omega$  resistance is connected to a 110 V, 60 Hz supply.

(a) What is the maximum current in the circuit?

(b) What is the time lag between the current maximum and the voltage maximum?



[Watch Video Solution](#)

5. If the circuit is connected to a 110 V, 12 kHz supply? Hence, explain the statement that a capacitor is a conductor at very high frequencies. Compare this behaviour with that of a capacitor in a dc circuit after the steady state.



[View Text Solution](#)

6. Keeping the source frequency equal to the resonating frequency of the series LCR circuit,

if the three elements, L, C and R are arranged in parallel, show that the total current in the parallel LCR circuit is minimum at this frequency. Obtain the current rms value in each branch of the circuit for the elements and source specified in Exercise for this frequency.



**Watch Video Solution**

7. A circuit containing a 80 mH inductor and a  $60 \mu F$  capacitor in series is connected to a

230 V, 50 Hz supply. The resistance of the circuit is negligible.

(a) Obtain the current amplitude and rms values.

(b) Obtain the rms values of potential drops across each element.

(c) What is the average power transferred to the inductor?

(d) What is the average power transferred to the capacitor?

(e) What is the total average power absorbed by the circuit? ['Average' implies 'averaged over one cycle'.]





Watch Video Solution

8. Suppose the circuit in has a resistance of 15 W. Obtain the average power transferred to each element of the circuit, and the total power absorbed.



Watch Video Solution

9. A series LCR circuit with  
 $L = 0.12H$ ,  $C = 480nF$ ,  $R = 23\Omega$  is

connected to a 230 V variable frequency supply.

(a) What is the source frequency for which current amplitude is maximum. Obtain this maximum value.

(b) What is the source frequency for which average power absorbed by the circuit is maximum. Obtain the value of this maximum power.

(c) For which frequencies of the source is the power transferred to the circuit half the power at resonant frequency? What is the current

amplitude at these frequencies?

(d) What is the Q-factor of the given circuit?



[Watch Video Solution](#)

**10.** Obtain the resonant frequency and Q-factor of a series LCR circuit with  $L = 3.0H$ ,  $C = 27\mu F$ , and  $R = 7.4\Omega$ . It is desired to improve the sharpness of the resonance of the circuit by reducing its 'full width at half maximum' by a factor of 2. Suggest a suitable way.



[Watch Video Solution](#)

**11.** In any ac circuit, is the applied instantaneous voltage equal to the algebraic sum of the instantaneous voltages across the series elements of the circuit? Is the same true for rms voltage?



[Watch Video Solution](#)

**12.** A capacitor is used in the primary circuit of an induction coil.



[Watch Video Solution](#)

**13.** An applied voltage signal consists of a superposition of a dc voltage and an ac voltage of high frequency. The circuit consists of an inductor and a capacitor in series. Show that the dc signal will appear across C and the ac signal across L.



[Watch Video Solution](#)

**14.** A choke coil in series with a lamp is connected to a dc line. The lamp is seen to shine brightly. Insertion of an iron core in the choke causes no change in the lamp's brightness. Predict the corresponding observations if the connection is to an ac line.



**Watch Video Solution**

**15.** Why is choke coil needed in the use of fluorescent tubes with ac mains? Why can we

not use an ordinary resistor instead of the choke coil?



[Watch Video Solution](#)

**16.** A power transmission line feeds input power at 2300 V to a stepdown transformer with its primary windings having 4000 turns. What should be the number of turns in the secondary in order to get output power at 230 V?



[Watch Video Solution](#)

**17.** At a hydroelectric power plant, the water pressure head is at a height of 300 m and the water flow available is  $100 \text{ m}^3 \text{ s}^{-1}$ . If the turbine generator efficiency is 60%, estimate the electric power available from the plant ( $g = 9.8 \text{ m s}^{-2}$ ).



**Watch Video Solution**

**18.** A small town with a demand of 800 kW of electric power at 220 V is situated 15 km away



from an electric plant generating power at 440 V. The resistance of the two wire line carrying power is  $0.5 \Omega$  per km. The town gets power from the line through a 4000-220 V step-down transformer at a sub-station in the town.

(a) Estimate the line power loss in the form of heat.

(b) How much power must the plant supply, assuming there is negligible power loss due to leakage?

(c) Characterise the step up transformer at the plant.



[Watch Video Solution](#)

**19.** Do the same exercise as above with the replacement of the earlier transformer by a 40,000-220 V step-down transformer (Neglect, as before, leakage losses though this may not be a good assumption any longer because of the very high voltage transmission involved). Hence, explain why high voltage transmission is preferred?



[Watch Video Solution](#)

