



## PHYSICS

### BOOKS - OSWAAL PUBLICATION PHYSICS

#### (KANNADA ENGLISH)

### CURRENT ELECTRICITY

#### Topic 1 Electric Current Resistance Calls Very Shory Answer Type Questions

1. a resistor is marked with colours red , red, orange and gold .

Write the value of its resistance .



Watch Video Solution

2. The colour code of a carbon resistor is Brown-Red-Brown-Gold. What is its resistance ?



[Watch Video Solution](#)

3. Name the charge carriers in metallic conductors.



[Watch Video Solution](#)

4. How does the resistance of a conductor vary with the increase of temperature ?



[Watch Video Solution](#)

5. Which combination of resistance gives maximum current ?



 [Watch Video Solution](#)

6. What is the color of the third band of a coded resistor of resistance  $2.3 \times 10^3 \Omega$ ?

 [Watch Video Solution](#)

7. Name the colors corresponding to the digits 4 and 7 in the color code scheme for carbon resistors.

 [Watch Video Solution](#)

8. How does the random motion of free electrons in a conductor get affected when a potential difference is applied across its ends ?

 [Watch Video Solution](#)

 [Watch Video Solution](#)

9. Write the expression for the drift velocity of charge carriers in a conductor of length  $l$  across which a potential difference  $V$  is applied.

 [Watch Video Solution](#)

10. Show variation of resistivity of copper as a function of temperature in a graph.

 [Watch Video Solution](#)

11. Why is that the terminal potential difference is always less than the e.m.f. of a cell?

 [Watch Video Solution](#)

 [Watch Video Solution](#)

12. Two wires of equal length, one of copper and the other of manganin have the same resistance. Which wire is thicker ?

 [Watch Video Solution](#)

13. A wire of resistance  $8R$  is bent in the form of a circle. What is the effective resistance between the ends of a diameter  $AB$  ?

 [Watch Video Solution](#)


## Topic 1 Electric Current Resistance Calls Shory Answer Type Questions I

1. Give any two practical limitations of Ohm's law.



[Watch Video Solution](#)

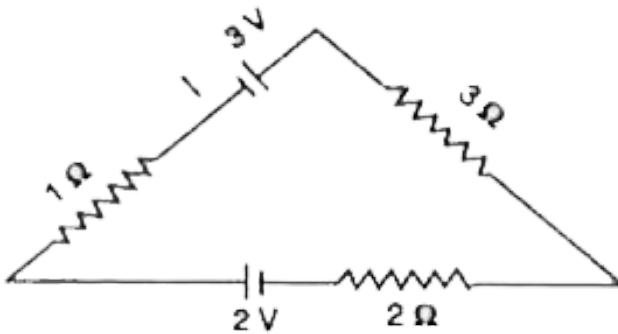2. Calculate the value of  $I$  in the circuit given below.



[Watch Video Solution](#)

3. An example of a non ohmic device is



[Watch Video Solution](#)

4. Draw a plot showing the variation of resistivity of a (i) conductor and (ii) semiconductor, with the increase in temperature.



[Watch Video Solution](#)

5. Distinguish between emf ( $E$ ) and terminal voltage ( $V$ ) of a cell having internal resistance ' $r$ '.



[Watch Video Solution](#)

6. Draw a plot showing the variation of terminal voltage ( $V$ ) v/s the current ( $I$ ) drawn from the cell.



[Watch Video Solution](#)

7. Draw a graph showing variation of resistivity with temperature of nichrome. Which property of nichrome is used to make standard resistance coils ?



[Watch Video Solution](#)

## Topic 1 Electric Current Resistance Calls Shory Answer Type Questions li

1. State and explain ohm's law



[Watch Video Solution](#)

2. Define the term current density.



[Watch Video Solution](#)



3. Define the terms (i) drift velocity, (ii) relaxation time. A conductor of length  $L$  is connected to a d.c. source of emf  $\varepsilon$ . If this conductor is replaced by another conductor of same material and same area of cross-section but of length  $3L$ , how will the drift velocity change ?



[Watch Video Solution](#)

4. Mention any two factors on which the internal resistance of the cell depends.



[Watch Video Solution](#)

1. Obtain an expression for the equivalent emf and internal resistance of two cells connected in parallel.



[Watch Video Solution](#)

2. Obtain an expression for equivalent resistance of two resistors connected in parallel.



[Watch Video Solution](#)

3. What is drift velocity of free electrons ? Deduce  $I = nAeV_d$  where the symbols have their usual meaning.



[Watch Video Solution](#)

4. Two resistors of  $5\Omega$  and  $10\Omega$  are connected in parallel with a cell of emf 3 V and internal resistance  $1\Omega$ . Calculate the current through each of the resistors.



[Watch Video Solution](#)

5. Derive an expression of effective resistance of four resistors connected in parallel.




[Watch Video Solution](#)

## Topic 1 Electric Current Resistance Calls Numerical Problems

1. In the given circuit , calculate the (i) effective resistance between A and B (ii) current through the circuit and (iii)

current through  $3\Omega$  resistor.

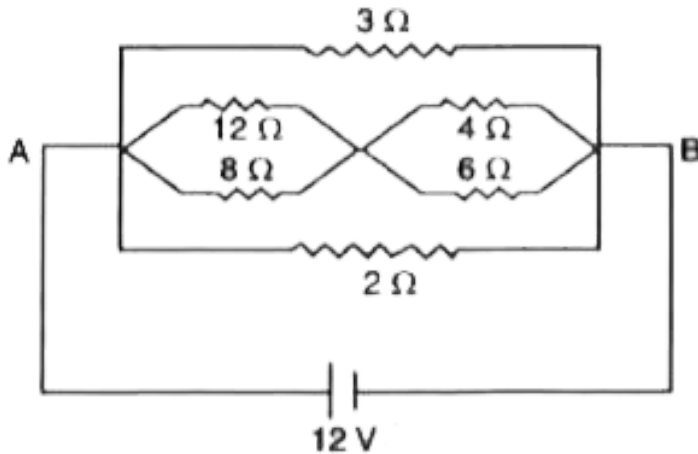

[▶ Watch Video Solution](#)

2. Calculate the internal resistance of the given cell using the following data. Balancing length for in open circuit

$$= l_1 = 0.60m$$

Trial No.	Resistance connected to the cell in $\Omega$	Balancing length in $m$	$r = R \left[ \frac{l_1}{l_2} - 1 \right]$ in $\Omega$
(i)	3	0.4	1.5
(ii)	4	0.44	1.45
(iii)	5	0.46	1.52



[Watch Video Solution](#)

3. Three resistors of  $3\Omega$ ,  $6\Omega$  and  $9\Omega$  are connected in parallel.

A potential difference of 18 V is maintained across the combination. Find the current in each resistor.



[Watch Video Solution](#)

4. A battery of internal resistance  $3\Omega$  is connected to  $20\Omega$  resistor and the potential difference across the resistor is 10V.

If another resistor  $30\Omega$  is connected in series with the first resistor and battery is again connected to the combination, then calculate the e.m.f and terminal potential difference across the combination..



[Watch Video Solution](#)

5. The resistance of the platinum wire of a platinum resistance thermometer at the ice point is  $5\Omega$  and at steam point is  $5.23\Omega$ . When the thermometer is inserted in a hot bath, the resistance of the platinum wire is  $5.795\Omega$ . Calculate the temperature of the bath.



[Watch Video Solution](#)

6. A copper wire of  $10^{-6}m^2$  area of cross section, carries a current of 2A. If the number of electrons per cubic meter is  $8 \times 10^{28}$ , calculate the current density and average drift velocity.

Given,  $e = 1.6 \times 10^{-19}C$



[Watch Video Solution](#)

7. The resistance of a copper wire of length 5 m is  $0.5\Omega$ . If the diameter of the wire is  $0.05\text{cm}$ , determine its specific resistance.



[Watch Video Solution](#)

8. Two wires of same material and length have resistance  $5\Omega$  and  $10\Omega$  respectively. Find the ratio of radii of the two wires.



[Watch Video Solution](#)

9. Find the current flowing across three resistors  $3\Omega$ ,  $5\Omega$  and  $2\Omega$ , connected in parallel to a 15 V supply. Also

find the effective resistance and total current drawn from the supply.



[Watch Video Solution](#)

## Topic 2 Kirchhoff's Laws Applications Short Answer Type Questions I

1. State Kirchhoff's laws of Electrical network.



[Watch Video Solution](#)

2. Draw Wheatstone bridge and write the condition for balance.



[Watch Video Solution](#)



## Topic 2 Kirchhoff's Laws Applications Short Answer Type Questions li

1. Why are the connections between the resistors in a meter bridge made of thick copper strips ?

 [Watch Video Solution](#)

2. Why is it generally preferred to obtain the balance point in the middle of the meter bridge wire ?

 [Watch Video Solution](#)

3. Which material is used for the meter bridge wire and why ?

 [Watch Video Solution](#)

## Topic 2 Kirchhoff's Laws Applications Long Answer Type Questions

1. Deduce the condition for balance of a wheatstone's bridge using Kirchoffs rules .

 [Watch Video Solution](#)

2. Describe an experiment to determine to determine the temperature co-efficient of a thermistor using a meter bridge.

 [Watch Video Solution](#)

3. Explain the experiment to determine the resistivity of the material of the wire using meter bridge.

 [Watch Video Solution](#)

## Topic 2 Kirchhoff S Laws Applications Numerical Problems


1. Two cells of emf 2V and 4V and internal resistance  $1\Omega$  and  $2\Omega$  respectively are connected in parallel so as to send the current in the same direction through an external resistance of  $10\Omega$ . Find the potential difference across  $10\Omega$  resistor.



Watch Video Solution

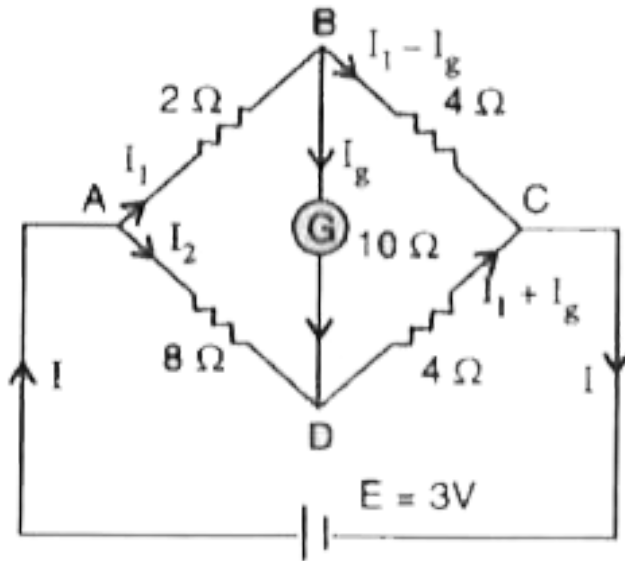2. Determine the current through the galvanometer in the circuit. Given

:  $P = 2\Omega$ ,  $Q = 4\Omega$ ,  $R = 8\Omega$ ,  $S = 4\Omega$ ,  $G = 10\Omega$ ,  $E = 5$  and  $r = 0$ .



[Watch Video Solution](#)

3. The following readings are obtained in a meter bridge experiment to find the resistivity of the material of a given wire. Calculate the resistivity of the material of the wire.


Diameter of the wire =  $d = 0.36mm$ , length of the wire

$$L = 60\text{cm}.$$

Tr. No.	Resistance in the right gap in $\Omega$	Balancing length in cm
1	3	59.0
2	6	43.0

 [Watch Video Solution](#)

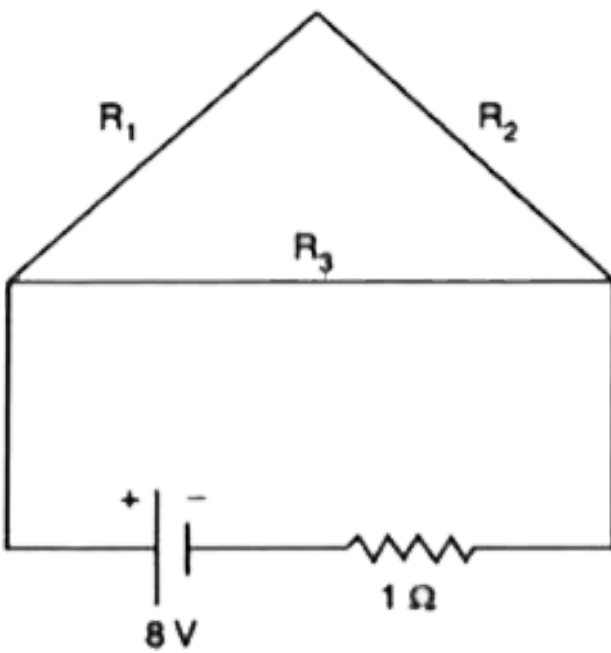4. A uniform wire of resistance  $12\Omega$  is cut into three pieces so that the ratio of the resistances  $R_1 : R_2 : R_3 = 1 : 2 : 3$  and the three pieces are connected to form a triangle across which a cell of emf  $8\text{V}$  and internal resistance  $1\Omega$  is connected as shown.




Calculate the current through each part of the circuit.

[Watch Video Solution](#)

5. Using Kirchhoffs rules in the given circuit, determine (i) the voltage drop across the unknown resistor  $R$  and (ii) current  $I$  in


the arm EF.

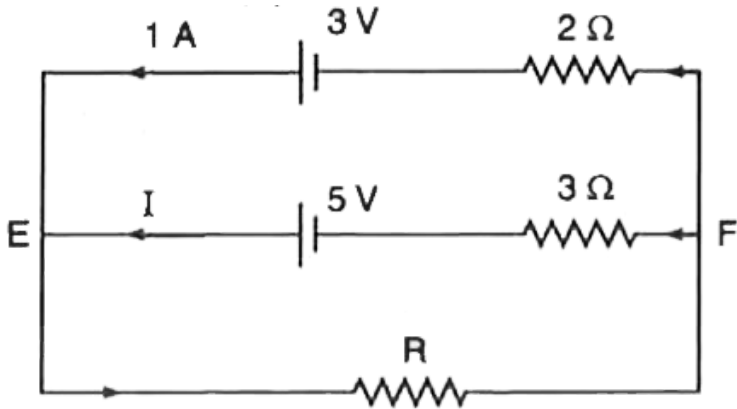

[Watch Video Solution](#)

6. In the electric network shown in the figure, use Kirchhoff's rules to calculate the power consumed by the resistance

$$R = 4\Omega.$$

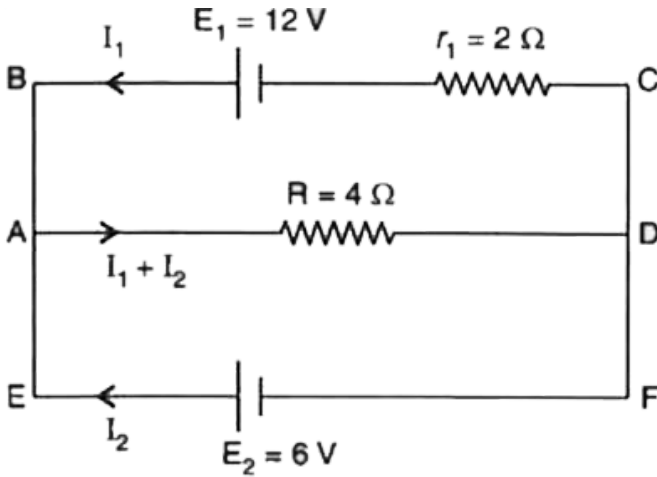


[Watch Video Solution](#)

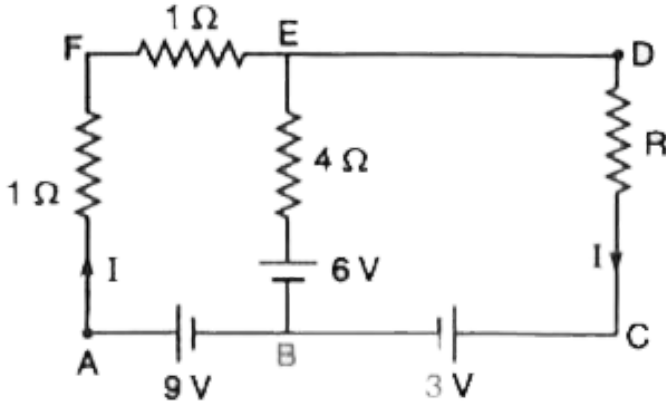7. Using Kirchhoff's rules determine the value of unknown resistance  $R$  in the circuit so that no current flows through  $4\Omega$



resistance. Also find the potential difference between A and D.



[▶ Watch Video Solution](#)

### Topic 3 Potentiometer Applications Vert Short Answer Type Questions

1. State the underlying principle of a potentiometer.

[▶ Watch Video Solution](#)

2. What is a potentiometer?




Watch Video Solution

### Topic 3 Potentiometer Applications Short Answer Type Questions

1

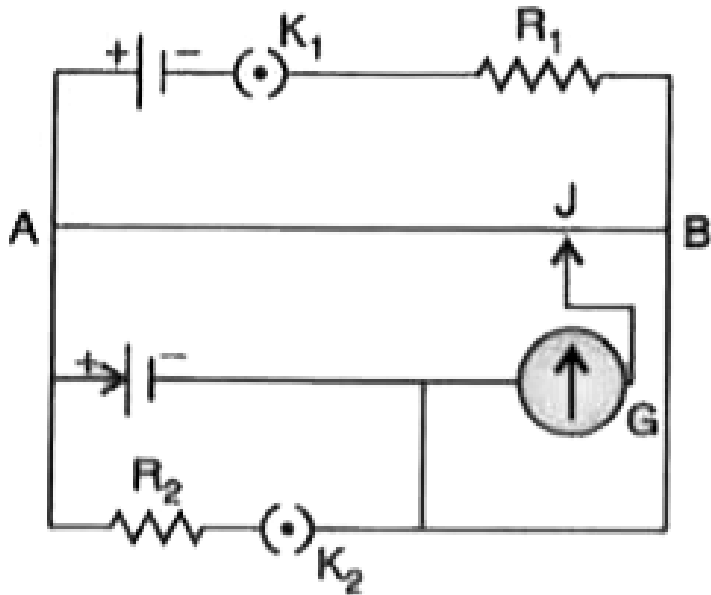1. For the circuit shown here, would the balancing length increase, decrease or remain the same, if



(i)  $R_1$  is decreased:

(ii)  $R_2$  is increased ,

without any other change, (in each case) in the rest of the circuit. Justify your answers in each case.



[Watch Video Solution](#)

2. Write two factors on which the sensitivity of a potentiometer depends.



[Watch Video Solution](#)

## Topic 3 Potentiometer Applications Short Answer Type Questions

### ii

1. State the underlying principle of a potentiometer. Why is it necessary to (i) use a long wire, (ii) have uniform area of cross-section of the wire ?



[Watch Video Solution](#)

## Topic 3 Potentiometer Applications Long Answer Type Question

1. Write the principle of working of a potentiometer. Describe briefly, with the help of circuit diagram, how a potentiometer is


used to determine the internal resistance of a given cell.



[Watch Video Solution](#)


### Topic 3 Potentiometer Applications Numerical Problems

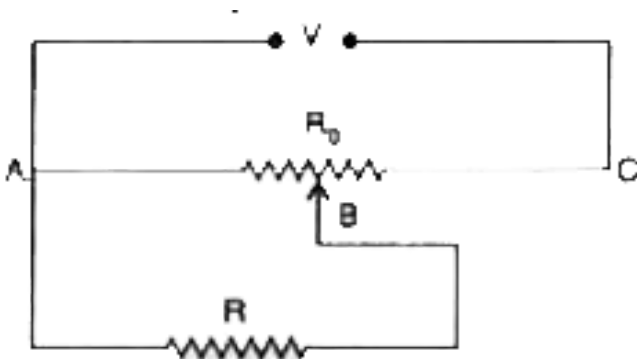1. A resistance of  $R\Omega$  draws current from a potentiometer. The potentiometer has a total resistance  $R_0\Omega$ . A voltage  $V$  is supplied to the potentiometer. Derive an expression for the voltage across  $R$  when the sliding contact is in the middle of the potentiometer.



[Watch Video Solution](#)

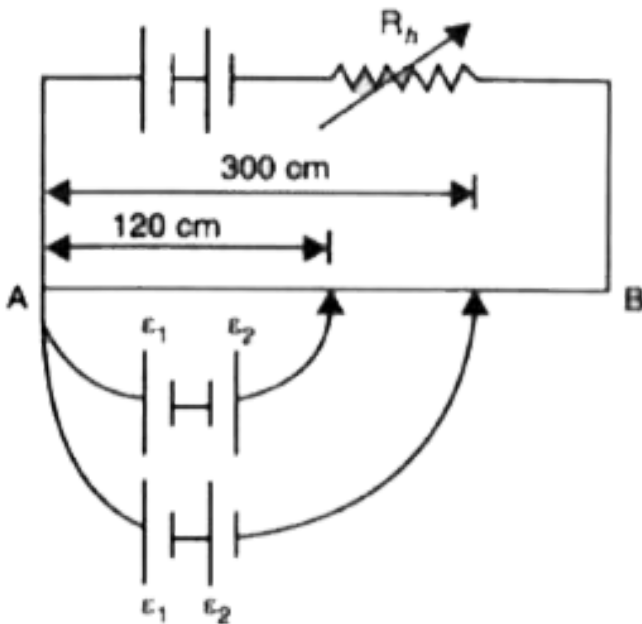2. Figure shows a long potentiometer wire AB having a constant potential gradient. The null points for the two primary cells of emfs  $\varepsilon_1$  and  $\varepsilon_2$  connected in the manner shown are obtained at a distance of  $l_1 = 120\text{cm}$  and  $l_2 = 300\text{cm}$  from the end A. Determine (i)  $\varepsilon_1/\varepsilon_2$  and (ii) position of null point for the cell  $\varepsilon_1$  only.



Watch Video Solution

