



PHYSICS

BOOKS - PUNJAB BOARD PREVIOUS YEAR PAPERS

Semiconductor Devices

Exercise

1. A transistor, connected in common-emitter configuration, has input resistance $R_{\epsilon} = 3k\Omega$

and load resistance of $6k\Omega$. If $\beta = 40$ and an input signal of $20mV$ is applied, calculate the voltage gain, output voltage and power gain.



[Watch Video Solution](#)

2. A transistor, is connected in common-emitter configuration, has input resistance $R_{\epsilon} = 1k\Omega$ and load resistance of $4k\Omega$. if $\beta = 50$ and an input signal of $10mV$ is applied, calculate the voltage gain, output voltage and power gain.



[Watch Video Solution](#)

3. A transistor, is connected in common-emitter configuration, has input resistance $R_{\epsilon} = 2k\Omega$ and load resistance of $5k\Omega$.if $\beta = 60$ and an input signal of $12mV$ is applied, calculate the voltage gain, output



[Watch Video Solution](#)

4. The base current is $100\mu A$ and collector-current is $3mA$. calculate the values of β, I_e

and α .



Watch Video Solution

5. A change of $20\mu A$ in the base current produces a change of $0.5mA$ in the collector current. Calculate β_{ac}



Watch Video Solution

6. The input resistance of a silicon transistor is 665Ω when base current is changed by $15\mu A$,

the collector current changes by 2mA. In a common emitter amplifier load resistance is $5k\Omega$. Calculate current gain β_{ac}



[Watch Video Solution](#)

7. The input resistance of a silicon transistor is 665Ω when base current is changed by $15\mu A$, the collector current changes by 2mA. In a common emitter amplifier load resistance is $5k\Omega$. Calculate transconductance (g_m) & voltage gain (A_v) of the amplifier.



[Watch Video Solution](#)

8. For a common emitter amplifier current gain = 50 if the emitter current is 6.6 mA. Calculate the collector and base current.



[Watch Video Solution](#)

9. For a common emitter amplifier current gain is 70 if the emitter current is 8.8 milliamperere (mA). Calculate the collector and base current.



[Watch Video Solution](#)

10. For a common emitter transistor as amplifier current gain is 72. Calculate the base current for which emitter current is 8.9 milliampere and also find collector current.



Watch Video Solution

11. A common emitter circuit has an input resistance of 570Ω and output resistance of

$59k\Omega$. If the current gain is 60, find the voltage gain and power gain.



[Watch Video Solution](#)

12. A transistor connected in common emitter configuration has input resistance $R_i = 2k\Omega$ (kilo ohm) and load resistance $6k\Omega$ (kilo ohm). If current gain $\beta = 60$ and input signal 10 mV (millivolt) is applied, calculate resistance gain



[Watch Video Solution](#)

13. A transistor connected in common emitter configuration has input resistance $R_i = 2k\Omega$ (kilo ohm) and load resistance $6k\Omega$ (kilo ohm). If current gain $\beta = 60$ and input signal 10 mV (millivolt) is applied, calculate voltage gain



Watch Video Solution

14. A transistor connected in common emitter configuration has input resistance $R_i = 2k\Omega$ (kilo ohm) and load resistance $6k\Omega$ (kilo ohm).

If current gain $\beta = 60$ and input signal 10 mV (millivolt) is applied, calculate power gain.



[Watch Video Solution](#)

15. A transistor is used in common emitter mode in an amplifier circuit. It is found that when a signal of 20 mV (millivolt) is added to base-emitter voltage the base current changes by $20\mu A$ (micro ampere) and collector current changes by 1.5 mA (milli ampere). Determine the current gain β , Input resistance R_i ,

transconductance and voltage gain. Give load resistance $R_l = 6k\Omega$ (kilo ohm).



[Watch Video Solution](#)

16. A transistor is used in common emitter mode in an amplifier circuit. When a signal of 24 mV (millivolt) is added to base emitter voltage, the base current changes by $32\mu A$ (micro ampere) and collector current by 3.6 mA (milli ampere) and the load resistance is $4.8k\Omega$ (kilo ohm). Calculate current gain



Watch Video Solution

17. A transistor is used in common emitter mode in an amplifier circuit. When a signal of 24 mV (millivolt) is added to base emitter voltage, the base current changes by $32\mu A$ (micro ampere) and collector current by 3.6 mA (milli ampere) and the load resistance is $4.8k\Omega$ (kilo ohm). Calculate the input resistance R_{be}



Watch Video Solution

18. A transistor is used in common emitter mode in an amplifier circuit. When a signal of 24 mV (millivolt) is added to base emitter voltage, the base current changes by $32\mu A$ (micro ampere) and collector current by 3.6 mA (milli ampere) and the load resistance is $4.8k\Omega$ (kilo ohm). Calculate trans conductance g_m



Watch Video Solution

19. A transistor is used in common emitter mode in an amplifier circuit. When a signal of 24 mV (millivolt) is added to base emitter voltage, the base current changes by $32\mu A$ (micro ampere) and collector current by 3.6 mA (milli ampere) and the load resistance is $4.8k\Omega$ (kilo ohm). Calculate voltage gain.



Watch Video Solution

20. For a common emitter amplifier, dc (direct current) current gain is 100. If the base current is $20\mu A$, calculate the collector and emitter current.



Watch Video Solution

21. For a common emitter amplifier, dc (direct current) current gain is 60. If the emitter current is $6.6mA$, calculate the collector and base current.





[Watch Video Solution](#)

22. For a common emitter amplifier, dc (direct current) current gain is 20. If the emitter current is 7mA, calculate the base and collector current.



[Watch Video Solution](#)

23. A common emitter (CE) transistor has a current gain of 100. If emitter current is 8.08 mA, find the base and collector current.



[Watch Video Solution](#)

24. A common emitter transistor has current gain of 96. If base current is $8\mu A$. Find the collector and emitter current.



[Watch Video Solution](#)

25. A semiconductor has electron mobility as $2.2 \times 10^4 \text{ cm}^2 \text{ V}^{-1} \text{ S}^{-1}$ and hole mobility as $1.5 \times 10^2 \text{ cm}^2 \text{ V}^{-1} \text{ S}^{-1}$. If the electron

concentration in this semiconductor is $40 \times 10^{12} \text{ cm}^{-3}$ and hole concentration as $7 \times 10^{14} \text{ cm}^{-3}$. Find the type of semiconductor and its conductivity.



[Watch Video Solution](#)

26. Draw a circuit diagram with a p-n junction in forward bias.



[Watch Video Solution](#)

27. Draw a circuit diagram with a p-n junction at reverse bias.



Watch Video Solution

28. State the factors, which controls intensity of light, emitted by a LED.



Watch Video Solution

29. Draw a circuit diagram to show how a photodiode is biased.



Watch Video Solution

30. State the factors, which controls wavelength of light, emitted by a LED.



Watch Video Solution

31. What do you mean by depletion region in a p-n junction ?



Watch Video Solution

32. Draw a PN-Junction with reverse bias.



Watch Video Solution

33. Write briefly, how a Zener diode acts as voltage regulator.



[Watch Video Solution](#)

34. Write in brief about Photo-diodes.



[Watch Video Solution](#)

35. Explain the terms depletion layer



[Watch Video Solution](#)

36. Explain the terms potential barrier for a junction diode.



Watch Video Solution

37. In a transistor, base is made very thin.Explain.



Watch Video Solution

38. Why a transistor cannot be used as a rectifier ?



Watch Video Solution

39. The resistance of a p-n junction is low, when forward biased and is high, when reverse is biased. Explain.



Watch Video Solution

40. What is photo cell ? State its three applications.



Watch Video Solution

41. Write briefly, how a Zener diode acts as voltage regulator.



Watch Video Solution

42. Why does the thickness of depletion layer of pn-junction increases in reverse biasing ?

Draw the circuit diagram of reverse biasing.



Watch Video Solution

43. What is a solar cell ? How does it work ?

Write its one use.



Watch Video Solution

44. Explain how the depletion layer and barrier potential are formed in pn junction diode ?



Watch Video Solution

45. Explain forward bias and reverse bias of the junction diode.



Watch Video Solution

46. With the help of circuit diagram explain working of junction diode as full wave rectifier.



Watch Video Solution

47. With the help of labelled circuit diagram, explain the working of transistor as a switch.



Watch Video Solution

48. With the help of circuit diagram, explain the working of transistor as a oscillator.



Watch Video Solution

49. With the help of circuit diagram, explain the working of transistor as a common emitter amplifier.



Watch Video Solution

50. With the help of suitable diagrams, explain the function of p-n junction diode as full wave rectifier.



Watch Video Solution

51. Define Rectification. With the help a circuit diagram explain the working of p-n junction diode as a half wave rectifier.



Watch Video Solution

52. What is junction diode ? How is depletion layer formed ? Draw its forward and reverse bias characteristics by showing biasing of diodes ?



Watch Video Solution

53. What is transistor ? Give the symbols of n-p-n and p-n-p transistor.



Watch Video Solution

54. Explain with diagram, the working of a transistor as a common-emitter amplifier.



Watch Video Solution

55. What is rectifier ? Explain the working of junction diode as a full wave rectifier, with diagram.



Watch Video Solution

56. Discuss the variation of current with voltage in a P-N Junction diode when it is forward biased.



Watch Video Solution

57. With the help of circuit diagram, explain the V-I characteristics of p-n junction diode in forward biasing.



Watch Video Solution

58. With the help of circuit diagram, explain the V-I characteristics of p-n junction diode in reverse biasing.



Watch Video Solution

59. With the help of circuit diagram explain working of junction diode as full wave rectifier.



Watch Video Solution

60. With the help of circuit diagram, explain the $V-I$ characteristics of p-n junction diode in forward biasing.



Watch Video Solution

61. With the help of circuit diagram, explain the working of transistor as a common emitter amplifier.



Watch Video Solution

62. What is rectifier ? Explain the working of junction diode as a full wave rectifier, with diagram.



Watch Video Solution

63. Discuss the working of n-p-n transistor as an amplifier in common base mode.



Watch Video Solution

64. Discuss the working of p-n-p transistor as an amplifier in common emitter mode.



Watch Video Solution

65. Discuss the construction and working of diode as full wave rectifier



Watch Video Solution

66. Why does the thickness of depletion layer of pn-junction increases in reverse biasing ?

Draw the circuit diagram of reverse biasing.



Watch Video Solution

67. With the help of circuit diagram explain working of junction diode as full wave rectifier.



Watch Video Solution

68. Why does the depletion layer of pn-junction diode decreases in forward biasing ?

Draw the circuit diagram of forward biasing.



Watch Video Solution

69. With the help of circuit diagram explain working of junction diode as full wave rectifier.



Watch Video Solution

70. Explain with the help of circuit diagram, how V-I characteristics of pn junction diode are obtained in forward biasing.



[Watch Video Solution](#)

71. What is an amplifier ? Draw a circuit diagram for an amplifier with PNP transistor in common emitter configuration. Also define current gain, voltage gain and power gain for it.





[Watch Video Solution](#)

72. What is an amplifier ? Draw a circuit diagram for an amplifier with PNP transistor in common emitter configuration. Also define current gain, voltage gain and power gain for it.



[Watch Video Solution](#)

73. What is an oscillator ? Draw a labelled circuit diagram for an oscillator using PNP

transistor. What is the function of feed back coil in it ? Write an expression for the frequency of waves produced by it. What is the use of waves produced by it ?



[Watch Video Solution](#)

74. With the help of circuit diagram explain working of junction diode as full wave rectifier.



[Watch Video Solution](#)

75. With the help of circuit diagram explain working of junction diode as full wave rectifier.



Watch Video Solution

76. With the help of circuit diagram, explain the working of transistor as a common emitter amplifier.



Watch Video Solution

77. With the help of labelled circuit diagram, discuss the working of transistor as a common emitter amplifier. Find the phase relationship between input and output signals. Also define its voltage gain.



Watch Video Solution

78. What is junction diode ? How is depletion layer formed ? Draw its forward and reverse

bias characteristics by showing biasing of diodes ?



[Watch Video Solution](#)

79. What is an electric oscillator ? With the help of labelled diagram, explain the use of junction transistor as an oscillator.



[Watch Video Solution](#)

80. With the help of circuit diagram, explain the working of transistor as a common emitter amplifier.



Watch Video Solution

81. What is p-n junction diode ? Explain the principle and of various components of full wave rectifier using circuit diagrams as well as input and output waveforms.



Watch Video Solution

82. What is an oscillator ? With the help of circuit diagram explain the principle and working of transistor as an oscillator in common emitter configuration, showing how feedback is accomplished by inductive



Watch Video Solution

83. What is transistor ? How is it formed ? Show with the help of diagram action of npn transistor



Watch Video Solution

84. What is transistor ? How is it formed ?
Show with the help of diagram action of pnp transistor.



Watch Video Solution