



# PHYSICS

**BOOKS - OSWAAL PUBLICATION**

**PHYSICS (KANNADA ENGLISH)**

**SEMI-CONDUCTORS ELECTRONICS**

**Topic 1 Energy Bands Short Answer Type  
Questions I**

1. Give three differences between intrinsic and extrinsic semiconductors



[Watch Video Solution](#)

2. How are p-type n-type semiconductors formed ?



[Watch Video Solution](#)

3. Draw energy band diagrams of n-type and p-type semiconductors at temperature  $T > 0$  K. Mark the donor and acceptor energy levels with their energies.



[Watch Video Solution](#)

## Topic 1 Energy Bands Short Answer Type Questions II

1. Classify metals, semiconductors and insulators on the basis of energy bands.



[Watch Video Solution](#)

2. Give three differences between intrinsic and extrinsic semiconductors



[Watch Video Solution](#)

3. Distinguish between conductors, insulators and semiconductors on the basis of band theory.



[Watch Video Solution](#)

## Topic 1 Energy Bands Long Answer Type Questions li

1. Classify metals, semiconductors and insulators on the basis of energy bands.



[Watch Video Solution](#)

2. Explain the working of a forward biased p-n junction diode.



[Watch Video Solution](#)

## Topic 2 Semiconductor Diodes And Their Applications Very Short Answer Type Questions

1. Why is photodiode used in reverse bias ?



[Watch Video Solution](#)

2. Give the expansion of LED.



[Watch Video Solution](#)

3. How biasing in diode, used in rectification ?



[Watch Video Solution](#)

4. The graph shown here represents the V-I characteristics of a device. Identify the region, if any, over which this device has a negative resistance.



[View Text Solution](#)

5. The graph shown in the figure represents a plot of current versus voltage for a given semiconductor. Identify the region, if any, over which the semiconductor has a negative resistance.



[View Text Solution](#)

6. What happens to the width of depletion layer of a p-n junction when it is (i) forward biased, (ii) reverse biased ?





[Watch Video Solution](#)

## Topic 2 Semiconductor Diodes And Their Applications Short Answer Type Questions I

1. What is Rectification? Describe with a circuit diagram the working of a p-n junction diode as half wave rectifier with input and output waveforms.



[Watch Video Solution](#)

2. Mention the important considerations required while fabricating a p-n junction diode to be used as a Light Emitting Diode (LED). What should be the order of band gap of an LED if it is required to emit light in the visible range ?



[Watch Video Solution](#)

3. Assuming that the two diodes  $D_1$ , and  $D_2$ , used in the electric circuit shown in the figure

are ideal, find out the value of the current flowing through  $2.5 \Omega$  resistor.



 [View Text Solution](#)

4. For the circuit shown here, find the current flowing through the  $1\Omega$  resistor. Assume that the two diodes  $D_1$  and  $D_2$  are ideal diodes.



 [View Text Solution](#)

5. The current in the forward bias is known to be more (mA) than the current in the reverse bias ( $\sim\mu\text{A}$ ). What is the reason, then why photo diodes is to operate in reverse bias.



[Watch Video Solution](#)

6. Name the semiconductor device that can be used to regulate an unregulated d.c. powersupply. With the help of I-V characteristics of this device, explain its working principle.



[Watch Video Solution](#)

7. Draw the circuit diagram of an illuminated photodiode in reverse bias. How is photodiode used to measure light intensity ?



[Watch Video Solution](#)

8. In the figure given below the input waveform is converted into the output waveform by a device 'X'. Name the device and

draw its circuit diagram.



[View Text Solution](#)

9. What is a light emitting diode? Write an advantage of using it over conventional low power lamps.



[Watch Video Solution](#)

1. Explain the use Zener diode as a voltage regulator.



[Watch Video Solution](#)

2. Explain the working of a zener diode as a voltage regulator.



[Watch Video Solution](#)

### 3. Give reasons

The Zener diode is fabricated by heavily doping both the p and n sides of the junction.



[Watch Video Solution](#)

### 4. Why is photodiode used in reverse bias ?



[Watch Video Solution](#)



## 5. Give reasons

The band gap of the semiconductor used for fabrication of visible LED's must at least be 1.8 eV.



[Watch Video Solution](#)

## 6. How is a photodiode Fabricated ?



[Watch Video Solution](#)

7. Briefly explain its working. Draw its V-I characteristics for two different intensities of illumination.



[View Text Solution](#)

8. Give reasons

The Zener diode is fabricated by heavily doping both the p and n sides of the junction.



[Watch Video Solution](#)

9. Explain the working of a zener diode as a voltage regulator.



[Watch Video Solution](#)

## Topic 2 Semiconductor Diodes And Their Applications Long Answer Type Questions

1. Explain with the help of a diagram, how a depletion layer and barrier potential are formed in a junction diode.



[Watch Video Solution](#)

2. What is a rectifier ? With suitable circuit describe the action of a full wave rectifier by drawing input and output waveforms.



[Watch Video Solution](#)

3. Draw the circuit arrangement for studying the V - I characteristics of a p-n junction diode in (i) forward and (ii) reverse bias. Briefly explain how the typical V - I characteristics of a

diode are obtained and draw these characteristics.



**Watch Video Solution**

4. With the help of necessary circuit diagram explain the working of a photo diode used for detecting optical signals.



**Watch Video Solution**

5. Describe briefly, with the help of a diagram, the role of the two important processes involved in the formation of a p-n junction.



[Watch Video Solution](#)

6. Name the semiconductor device that can be used to regulate an unregulated d.c. powersupply. With the help of I-V characteristics of this device, explain its working principle.





[Watch Video Solution](#)

## Topic 3 Transistors And Their Applications Very Short Answer Type Questions

1. Draw the circuit symbol of n-p-n transistor



[Watch Video Solution](#)

2. Draw the circuit symbol of p-n-p transistor.



[Watch Video Solution](#)

3. In a transistor, doping level in base is increased slightly. How will it affect (i) collector current and (ii) base current ?



[Watch Video Solution](#)

4. Draw the transfer characteristic curve of a base biased transistor in CE configuration. Explain clearly how the active region of the  $V_0$  versus  $V_F$  curve in a transistor is used as an amplifier.







[Watch Video Solution](#)

## Topic 3 Transistors And Their Applications Short Answer Type Questions I

1. Draw a neat labelled diagram of a transistor amplifier in a CE mode.



[Watch Video Solution](#)

2. In the given circuit diagram, a voltmeter 'V' is connected across a lamp 'L'. How would (i)

the brightness of the lamp and (ii) voltmeter reading 'V' be affected, if the value of resistance 'R' is decreased ? Justify your answer.



[View Text Solution](#)

3. Describe briefly with the help of a circuit diagram, how the flow of current carriers in a p-n-p transistor is regulated with emitter-base

junction forward biased and base-collector

junction reverse biased



[View Text Solution](#)

## Topic 3 Transistors And Their Applications Short Answer Type Questions li

1. Draw a neat labelled diagram of a transistor amplifier in a CE mode.



[Watch Video Solution](#)

2. Output characteristics of an n-p-n transistor in CE configuration is shown in the figure. Determine : (i) Dynamic output resistance (ii) d.c. current gain and (iii) a.c. current gain at an operating point  $V_{CE} = 10V$ , when  $I_B = 30\mu A$ .



[View Text Solution](#)

**Topic 3 Transistors And Their Applications Long Answer Type Questions**

1. What is amplification? With a circuit diagram, explain the working of npn transistor as an amplifier in CE configuration.



[Watch Video Solution](#)

2. What is a rectifier ? With suitable circuit describe the action of a full wave rectifier by drawing input and output waveforms.



[Watch Video Solution](#)

3. (a) Draw the circuit diagram of an 1-p-transistor with emitter-base junction forward biased and collector-base junction reverse biased. Describe briefly how the motion of charge carriers in the transistor constitutes the emitter current ( $I_E$ ), the base current ( $I_B$ ) and the collector current ( $I_C$ ). Hence deduce the relation  $I_E = I_B + I_C$



**View Text Solution**

4. What is amplification? With a circuit diagram, explain the working of npn transistor as an amplifier in CE configuration.



[Watch Video Solution](#)

5. What is amplification? With a circuit diagram, explain the working of npn transistor as an amplifier in CE configuration.



[Watch Video Solution](#)

6. Describe briefly the underlying principle of a transistor amplifier working as an oscillator. Hence, use the necessary circuit diagram to explain how self sustained oscillations are achieved in the oscillator.



[Watch Video Solution](#)

7. Differentiate between three segments of a transistor on the basis of their size and level of doping,



[Watch Video Solution](#)



8. How is a transistor biased to be in active state ?



[Watch Video Solution](#)

9. With the help of necessary circuit diagram, describe briefly how h-p-n transistor in CE configuration amplifies a small sinusoidal input voltage. Write the expression for the ac current gain.



[Watch Video Solution](#)

**10.** Draw a simple circuit of a CE transistor amplifier. Explain its working. Show that the voltage gain,  $A_V$  of the amplifier is given by  $A_v = - \frac{\beta_{ac} R_L}{I_i}$  where  $\beta_{Ac}$  is the current gain,  $R_L$  is the load resistance and  $r_1$  is the input resistance of the transistor. What is the significance of the negative sign in the expression for the voltage gain?



[View Text Solution](#)

# Topic 3 Transistors And Their Applications

## Numerical Problems

1. The current gain  $\beta$  of the silicon transistor used in the circuit as shown in figure is 50.

(Barrier potential for silicon is 0.69 V) Find (i)

$I_B$  (ii)  $I_E$ . (iii)  $I_C$  and (iv)  $V_{CE}$



Data :

$$V_{BB} = 2V, V_{CC} = 10V, \beta = 50$$

$$R_B = 10K\Omega, R_C = 1K\Omega$$

The barrier potential for silicon transistor

$$V_{BE} = 0.69V$$



[View Text Solution](#)

2. A transistor is connected in CE configuration. The voltage drop across the load resistance ( $R_C$ ) 3 ks is 6 V. Find the base current. The current gain  $\alpha$  of the transistor is 0.97 Data : Voltage across the collector load resistance ( $R_C$ ) = 6 V .

$$\alpha = 0.97: R_C = 3k\Omega$$



[Watch Video Solution](#)

3. When the negative feedback is applied to an amplifier of gain 50, the gain after feedback falls to 25. Calculate the feedback ratio. Data :

$$A = 50, A_f = 25$$



[Watch Video Solution](#)

4. Find the output of the ideal operational amplifier shown in the figure for each of the following input signals

$$V_{In} = 120mVdC$$



[View Text Solution](#)

5. Find the output of the ideal operational amplifier shown in the figure for each of the following input signals

$$V_{In} = 0.5 \sin \omega t$$



[View Text Solution](#)

6. Find the output of the ideal operational amplifier shown in the figure for each of the following input signals

$$V_{In} = -2.5V_{dc}$$



[View Text Solution](#)

7. Find the output of the ideal operational amplifier shown in the figure for each of the following input signals

$$V_{In} = 0.8 \sin(\omega t + 70^\circ) V$$

$$V_{In} = 0.8 \sin(\omega t + 75^\circ) V$$



[View Text Solution](#)

8. Find the output of the ideal operational amplifier shown in the figure for each of the following input signals

*data*:  $R_f = 39K\Omega$ ,  $R_1 = 15k\Omega$



[View Text Solution](#)



9. Find the output of the circuit given below



Data :

$$R_f = 740K\Omega, R_f = 650K\Omega, R_1 = 10k\Omega$$

$$R_1 = 100k\Omega$$



[View Text Solution](#)

Topic 4 Logic Gates Very Short Answer Type Questions

1. Give the logic symbol, Boolean expression and truth table of a NOR gate.



**Watch Video Solution**

2. write the symbol of NAND gate .



**Watch Video Solution**

3. Write the truth table for logic OR gate.



**Watch Video Solution**

## Topic 4 Logic Gates Short Answer Type Questions

1

1. Give the circuit symbol and truth table for OR gate



[Watch Video Solution](#)

2. Give the logic symbol, Boolean expression and truth table of a NAND gate?



[Watch Video Solution](#)

3. The outputs of two NOT gates are fed to a NOR gate. Draw the logic circuit of the combination of gates. Give its truth table. Identify the gate represented by this combination.



[Watch Video Solution](#)

4. The input waveforms 'A' and 'B' and the output waveform 'Y' of a gate are shown

below. Name the gate it represents, write its truth table and draw the logic symbol of this gate.



[View Text Solution](#)

5. Identify the logic gates marked 'P' and 'Q' in the given circuit. Write the truth table for the combination.



[View Text Solution](#)

6. Identity the equivalent gate represented by the circuit shown in the figure. Draw its logic symbol and write the truth table.



[View Text Solution](#)

7. Write the truth table for the combination of the gates shown. Name the gates used.



[View Text Solution](#)

8. In the circuit shown in the figure, identify the equivalent gate of the circuit and make its truth table.



[View Text Solution](#)

9. Show the output waveforms (Y) for the following inputs A and B of (i) OR gate, (ii)

NAND gate.



[View Text Solution](#)

**10.** In the circuit shown in the figure, identify the equivalent gate of the circuit and make its truth table.



[View Text Solution](#)



**11.** For the digital circuit given below, write the truth table showing outputs  $Y_1$  and  $Y_2$  for all possible inputs of A and B.



[View Text Solution](#)

**12.** Show output waveform for all possible inputs of A and B.



[View Text Solution](#)

**13.** Draw the output waveform at X, using the given inputs A and B for the logic circuit shown below. Also, identify the logic operation performed by this circuit.



**View Text Solution**

**14.** Identify the logic gate represented by the circuit as shown and write its truth table.



**View Text Solution**

## Topic 4 Logic Gates Short Answer Type Questions

ii

1. A student has to use an appropriate number of (i) NAND gates (only) to get the output  $Y_1$   
(ii) NOR gates (only) to get the output  $Y_2$

From two given inputs A and B as shown in the diagram.



Identify the 'equivalent gate' needed in each case. Show how one can connect an

appropriate number of (i) NAND (ii) NOR gates respectively in the two cases to get these 'equivalent gates'.



[View Text Solution](#)

2. You are given a circuit below. Write its truth table. Hence, identify the logic operation carried out by this circuit. Draw the logic symbol of the gate, it corresponds to.



[View Text Solution](#)

## Topic 4 Logic Gates Numerical Problems

1. Prove the Boolean identity :

$$(A + B)(A + C) = A + BC$$



[Watch Video Solution](#)

2. The outputs of two NOT gates are NORed, as shown in figure. What is this combination equivalent to?





[View Text Solution](#)

3. Construct a logic circuit using NAND gates only for  $Y = \overline{A} + \overline{BC}$ .



[Watch Video Solution](#)

4. Determine the output wave form for the circuit given below, if the input waveforms are as indicated by A and B.





[View Text Solution](#)