



PHYSICS

BOOKS - MBD NCERT SOLUTIONS

ELECTRICITY

Example

1. What is an electric circuit ?



[Watch Video Solution](#)

2. Define electric current. What is the unit of electric current? Define it?



[Watch Video Solution](#)

3. Name a device that helps to maintain a potential difference across a conductor.



[Watch Video Solution](#)

4. What is meant by saying that the potential difference between two points is $1V$?



Watch Video Solution

5. How much energy is given to each coulomb of charge passing through a $6V$ battery ?



Watch Video Solution

6. On what factors does the resistance of a conductor depend?



Watch Video Solution

7. What is the resistance of a conductor ? State the factors on which resistance of a conductor depends? How is it related to conductivity of the conductor?



Watch Video Solution

8. Will current flow more easily through a thick wire or a thin wire of the same material when connected to the same source ? Why ?



[Watch Video Solution](#)

9. Let the resistance of an electrical component remain constant while the potential difference across the two ends of the component decreases to half its former value. What change will occur in the current through it ?



[Watch Video Solution](#)

10. What are the factors on which resistance of a conductor depends? Why are coils of electric toasters and electric irons made of an alloy rather than that of a pure metal?



[Watch Video Solution](#)

11. Which material is best conductor?



[Watch Video Solution](#)

12. Draw a schematic diagram of a circuit consisting of a battery of three cells of $2V$ each, a $5\ \text{ohm}$ resistor, an $8\ \text{ohm}$ resistor, and a $12\ \text{ohm}$ resistor, and a plug key, all connected in series.



Watch Video Solution

13. Redraw the circuit of $Q.12$, putting in an ammeter to measure the current through the resistors and a voltmeter to measure the

voltage across the 12Ω resistor. What would be the readings in the ammeter and the voltmeter ?

A. pi

B.

C.

D.

Answer:



Watch Video Solution

14. Find the equivalent resistance when the following are connected in parallel: 1Ω and 100Ω



Watch Video Solution

15. Find the equivalent resistance when the following are connected in parallel: 1Ω and 100Ω and 1000Ω



Watch Video Solution

16. An electric lamp of 100Ω , a toaster of resistance 50Ω and a water filter of resistance 500Ω are connected in parallel to a $220V$ source. What is the resistance of an electric iron connected to the same source that takes as much current as all three appliances and what is the current through it ?



Watch Video Solution

17. What are the advantages of connecting electrical devices in parallel with the battery instead of connected them in series ?



Watch Video Solution

18. How can three resistors of resistances 2Ω , 3Ω , and 6Ω be connected to give a total resistance of

(a) 4Ω

(b) 1Ω ?





[Watch Video Solution](#)

19. What is the

(a) maximum

(b) minimum

total resistance that can be secured by combination of four resistors of resistances 2Ω , 4Ω , 6Ω , 12Ω ?



[Watch Video Solution](#)

20. Why does the cord of an electric heater not glow while the heating element does ?



Watch Video Solution

21. Compute the heat generated while transferring 96000 coulombs of charge in one hour through a potential difference of 50V.



Watch Video Solution

22. An electric iron of resistance 20Ω takes a current of $5A$. Calculate the heat developed in $30s$.



Watch Video Solution

23. What determines the rate at which energy is delivered by a current ?



Watch Video Solution

24. An electric motor takes $5A$ from a $220V$ line. Determine the power and energy consumed in $2h$.



[Watch Video Solution](#)

25. A piece of wire of resistance R is cut into five equal parts. These parts are then connected in parallel. If the equivalent resistance of this combination is R' , then the ratio R/R' is :





[Watch Video Solution](#)

26. Which of the following terms does not represent electrical power in a circuit :



[Watch Video Solution](#)

27. Two conducting wires of the same material and of equal length and equal diameters are first connected in series and then in parallel in an electric circuit. The ratio of the heat

produced in series and parallel combinations
would be :



[Watch Video Solution](#)

28. How is voltmeter connected in the circuit
to measure potential difference between two
points ?



[Watch Video Solution](#)

29. The value of current, I , flowing in a given resistor for the corresponding values of potential difference, V , across the resistor are given below :

I (ampere)	0.5	1.0	2.0	3.0	4.0
V (volt)	1.6	3.4	6.7	10.2	13.2

Plot a graph between V and I and calculate the resistance of the resistor.



Watch Video Solution

30. When a $12V$ battery is connected across an unknown resistor, there is a current of $2.5mA$ in the circuit. Find the value of the resistance of the resistor.



[Watch Video Solution](#)

31. A battery of $9V$ is connected in series with resistors of 0.2Ω , 0.3Ω , 0.4Ω , 0.5Ω and 12Ω . How much current would flow through the 12Ω resistor ?





[Watch Video Solution](#)

32. How many 176Ω resistors (in parallel) are required to carry 5 A in 220 V line ?



[Watch Video Solution](#)

33. Show how you would connect three resistors, each of resistance 6Ω , so that the combination has a resistance of

(i) 9Ω

(ii) 2Ω .



[Watch Video Solution](#)

34. Several electric bulbs designed to be used on a $220V$ electric supply line, are rated $10W$. How many lamps can be connected in parallel with each other across the two wires of $220V$ line if the maximum allowable current is $5A$?



[Watch Video Solution](#)

35. A hot plate of an electric oven connected to a $220V$ lines has two resistance coils A and B , each of 24Ω resistance, which may be used separately, in series or in parallel. What are the currents in the three cases ?



Watch Video Solution

36. Compare the power used in the 2Ω resistor in each of the following circuits :

(i) a $6V$ battery in series with 1Ω and 2Ω

resistors, and

(ii) a $4V$ battery in parallel with 12Ω and 2Ω resistors.



[Watch Video Solution](#)

37. Compare the power used in the 2Ω resistor in each of the following circuits :

(i) a $6V$ battery in series with 1Ω and 2Ω resistors, and

(ii) a $4V$ battery in parallel with 12Ω and 2Ω resistors.



[Watch Video Solution](#)

38. Two lamps, one rated $100W$ at $220V$, and the other $60W$ at $220V$, are connected in parallel to the electric mains supply. What current is drawn from the line if the supply voltage is $220V$?



[Watch Video Solution](#)

39. Which uses more energy: a $250 W$ TV set in 1 hour or a $1200 W$ toaster in 10 minutes?



Watch Video Solution

40. An electric heater of resistance 8Ω draws $15A$ from the service mains for 2 hours. Calculate the rate at which heat is developed in the heater.



Watch Video Solution

41. Explain why, tungsten is used for making the filaments of electric bulbs.



[Watch Video Solution](#)

42. Why are coils of electric toasters and electric irons made of an alloy rather than a pure metal ?



[Watch Video Solution](#)

43. Why is series arrangement not used for domestic circuits?



[Watch Video Solution](#)

44. How does the resistance of a wire vary with its:

(a) area of cross-section?

(b) diameter?



Watch Video Solution

45. Why are copper and aluminium wires usually used for electricity transmission?



Watch Video Solution

46. What is meant by Joule's heating effect due to flow of current through a conductor?



Watch Video Solution

47. Define electric power and give its unit.



Watch Video Solution

48. What do you mean by electric energy ? give the definition of its unit.





[Watch Video Solution](#)

49. Define resistance of a conductor. What is its cause? Explain the factors on which the resistance of a conductor depends.



[Watch Video Solution](#)

50. On what factors does the resistance of a conductor depend ?



[Watch Video Solution](#)

51. State Ohm's law ? How can it be verified experimentally ? Does it hold good under all conditions ? Comment.



Watch Video Solution

52. State Ohm's law. How can it be verified experimentally ? Explain with the help of a circuit diagram. Express the result graphically.



Watch Video Solution

53. What is the need of combining different resistors? What is the resultant resistance when number of resistances are connected in series?



Watch Video Solution

54. State Ohm's law. Derive the laws of resistances, when they are connected: (i) in series (ii) in parallel.



Watch Video Solution

55. With the help of a diagram derive the formula for the equivalent resistance of three resistances connected in parallel?



Watch Video Solution

56. Define electric power and give its unit.



Watch Video Solution

57. What is meant by power and energy ? Give their units.



Watch Video Solution

58. What is electric energy ? what is its si unit?



Watch Video Solution

59. What is the contribution of electricity in our daily life?



[Watch Video Solution](#)

60. What do you understand by static electricity?



[Watch Video Solution](#)

61. What are positive and negative charges?
how are these produced?



[Watch Video Solution](#)

62. What is an electric circuit ?



Watch Video Solution

63. Distinguish between good conductors, resistors and insulators. Name two good conductors, two resistors and two insulators.



Watch Video Solution

64. What is electromotive force of a cell?





[Watch Video Solution](#)

65. What is the potential difference between two points in the electric field? Name its SI unit.



[Watch Video Solution](#)

66. Define volt it is unit of which physical quantity?



[Watch Video Solution](#)

67. How can we say that electric current is due to flow of charge?



Watch Video Solution

68. What is meant by electric current?



Watch Video Solution

69. What is an electric current ? Give its *SI* unit.



[Watch Video Solution](#)

70. How does electric current produce heat?



[Watch Video Solution](#)

71. Define resistance of conductor.also give its units



[Watch Video Solution](#)

72. What is meant by resistance of conductor define its units.



Watch Video Solution

73. What is electrical resistivity? What is its S.I. unit?



Watch Video Solution

74. What is an electric current ? Give its *SI* unit.



Watch Video Solution

75. Name and define the SI unit of current.



Watch Video Solution

76. What is electric energy? what is its SI unit?
Also name another quantity with same unit.



[Watch Video Solution](#)

77. Which instrument is used to measure current in the circuit ? how is it connected in the circuit?



[Watch Video Solution](#)

78. Define unit of electric energy?



[Watch Video Solution](#)

79. How many joules are present in 1 kilowatt hour? Also derive numerically



Watch Video Solution

80. Why is it that very small amount of heat is produced in connecting wires whereas large amount of heat is produced in heating filament of electric bulb?



Watch Video Solution

81. Give reasons for the following:

If you connect ammeter in parallel it burns



Watch Video Solution

82. On what factors does resistance depend?

What is the effect on resistance, if the length of wire is increased?



Watch Video Solution

83. On what factors does resistance depend?

What is the effect on resistance, if: the area of cross section is increased.



[Watch Video Solution](#)

84. Current of 100 mA flows through the filament of an electric bulb for 30 minutes calculate the charge that flow through the circuit.



[Watch Video Solution](#)

85. 60 coulomb of charge flows through a circuit for 5 minutes. Calculate the current flowing in a circuit.



Watch Video Solution

86. Calculate the area of cross section of wire whose length is 10.0 m and resistance is 230Ω take specific resistance of the material of wire as $1.84 \times 10^{-6} \text{ ohm-m}$



Watch Video Solution

87. Resistance of a metal wire of length 1 m is 26Ω at 20°C . If the diameter of the wire is 0.3 mm, what will be the resistivity of the metal at that temperature? Using Table 12.2, predict the material of the wire.



Watch Video Solution

88. In an electric circuit, a battery of five cells each of 2 V, resistors of 5Ω 10Ω 15Ω and a key

plug are connected in series arrangement

Draw its schematic diagram



[Watch Video Solution](#)


89. An electric lamp, whose resistance is 20Ω and a conductor of 4Ω resistance are connected to a $6V$ battery as shown in (Fig. 3.18) Calculate.

(a) the total resistance of the circuit,

(b) the current through the circuit, and

(c) the potential difference across the electric

lamp and the conductor.

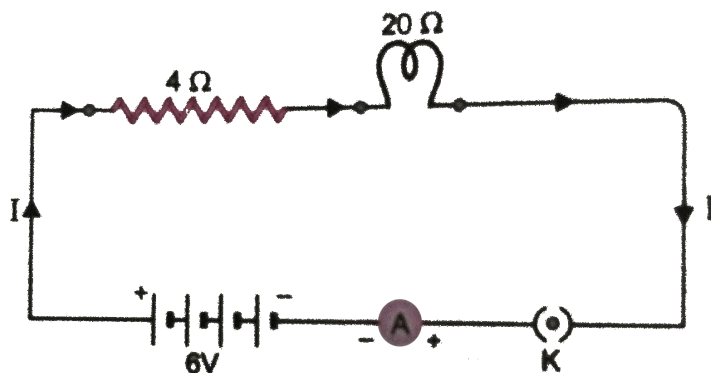

[Watch Video Solution](#)

90.98 J of heat is produced each second in $2\ \Omega$ resistor. Find the potential difference.

[Watch Video Solution](#)

91. The rating of an electric heater is 1100 W, 220V calculate the resistance when it operates at 220 V, also calculate the energy consumed in kWh in the month of November, if the heater is used daily for 4 hours at the rated voltage.



[Watch Video Solution](#)

92. What is the (a) highest : (b) lowest total resistance that can be secured by combination of four coils of resistances 4Ω 8Ω 10Ω 20Ω ?



[Watch Video Solution](#)

93. An electric bulb of power of power 40 W is lighted daily for 8 hours for 15 days how many units of electric energy will be consumed? also find the amount of electric bill if the rate of electricity consumption is rs.8.00 per unit



Watch Video Solution

94. A household uses the following electric appliance:

Refrigerator of rating 400 W for 10 hours each day, find the energy consumed.



[Watch Video Solution](#)

95. A household uses two electric fans of rating 80 W each for 12 hours each day, find energy consumed.



[Watch Video Solution](#)

96. A household uses six electric tubes of rating 18 W each for 6 hours each day. calculate the electricity bill of the household for the month of april if the cost per unit of electric energy is rs.4.00



Watch Video Solution

97. An electric motor takes 5 A from a 220 V line. Determine the power of the motor and the energy consumed in 4 hours





[Watch Video Solution](#)

98. Define energy.



[Watch Video Solution](#)

99. Define electrical energy and electrical power. Give their respective SI unit also.



[Watch Video Solution](#)

100. Define electric current. What is the unit of electric current? Define it?



Watch Video Solution

101. Define a volt, whose unit is this?



Watch Video Solution

102. Show the switch signs in circuit in (i) open(ii) closed circuit,



[Watch Video Solution](#)

103. Is electric potential a scalar or a vector quantity?



[Watch Video Solution](#)

104. What is practical unit of power and electric energy?



[Watch Video Solution](#)

105. Which one is having more resistance, 100 W bulb or a 50 W bulb?



Watch Video Solution

106. What constitutes current in a metal wire ?



Watch Video Solution

107. The SI unit of resistance .



Watch Video Solution

108. What is an electrical conductor ? Give some examples.



Watch Video Solution

109. The unit of electric energy is :

A. Joule

B. volt

C. ohm

D. watt

Answer:



Watch Video Solution

110. The resistance of a conductor depends on its

A. its length

B. its area of cross section

C. nature of its material

D. all of these

Answer:



Watch Video Solution

111. n resistors each of resistance R first combine to give maximum effective resistance and then combine to give minimum. The ratio of the maximum resistance is



Watch Video Solution

112. The unit of electric current is denoted by

A. coulomb

B. ampere

C. watt

D. kilowatt

Answer:



Watch Video Solution

113. Electric current in circuit is measured by:

A. ammeter

B. voltmeter

C. galvanometer

D. electric meter

Answer:



Watch Video Solution

114. How is ammeter always connected in circuits?

A. in series

B. in parallel

C. both in series and parallel

D. none of these

Answer:



Watch Video Solution

115. How is potential difference between two points expressed?

A. $V = \frac{W}{Q}$

B. $Q = VW$

C. $W = \frac{V}{Q}$

D. $V = \frac{Q}{W}$

Answer:



Watch Video Solution

116. How much work is done to carry 2 c of charge between two points having potential difference of 12V?

A. 2 j

B. 6 j

C. 24 j

D. $\frac{1}{6}$ j

Answer:



Watch Video Solution

117. According to ohm's law, which of these is correct?

A. $R = \frac{1}{V}$

B. $R = \frac{V}{1}$

C. $V = \frac{R}{T}$

D. $I = \frac{V}{R}$

Answer:



Watch Video Solution

118. A stream of moving through a conducto xonstitues,electric current



Watch Video Solution

119. The SI unit of electric current is



Watch Video Solution

120. In an electric circuit... is always connected inparallel



Watch Video Solution

121. The equivalent resistance of number of resistors will be lesser, if they are connected in..



Watch Video Solution

122. If the potential difference across the ends of a conductor is i volt and the current flowing through the conductor is 1 ampere, the resistance of the conductor?



Watch Video Solution

