



PHYSICS

BOOKS - HC VERMA

DISPERSION AND SCATTERING OF LIGHT

Question Bank

1. A 4-V battery is connected to a lamp of resistance 4Ω . Calculate the current through

the lamp.



[View Text Solution](#)

2. A 3-V battery is connected across a $5 - \Omega$ resistance. Calculate the heat produced in 5 seconds.



[View Text Solution](#)

3. An electric kettle is rated 500W, 220V. It is used to heat water for 30 seconds. Assuming

the voltage to be 220 V, calculate the heat produced.



[View Text Solution](#)

4. Calculate the current in a wire if 900 C of charge passes through it in 10 minutes.



[View Text Solution](#)

5. How much current will flow through a resistor of resistor of resistance 12Ω if a

battery of 18 V is connected across it ?



[View Text Solution](#)

6. Calculate the resistance of a copper wire of length 1 m and area of cross section 2mm^2 .

Resistivity of copper is $1.7 \times 10^{-5} \Omega\text{m}$.



[View Text Solution](#)

7. Calculate the wattage of an electric heater which draws 5A current when connected to a

220-V power supply.



[View Text Solution](#)

8. When a particle of charge $10\mu C$ is brought from infinity to a point P, 2.0 Mj of work is done by the external forces. What is the potential at P?



[View Text Solution](#)

9. Calculate the work done in taking a charge of 0.02 C from A to B if the potential at A is 20 V , and that at B is 30 V .



View Text Solution

10. How much charge flows through a wire in 10 minutes if the current through it is 2.5 A ?



View Text Solution

11. A 2-V cell is connected to a $1 - \Omega$ resistor .
How many electrons come out of the negative terminal of the cell in 2 minutes ?



View Text Solution

12. The amount of charge passing through a cell in 4 seconds is 12 C. What is the current supplied by the cell?



View Text Solution

13. A 6-V battery is connected across a $5 - \Omega$ resistor. Calculate the current passing through the resistor .



View Text Solution

14. When a 24V battery is connected to resistor, the current in it is 0.4 A. What is the resistance of the resistor ? What would be the current through it when it is connected to a battery of 6V?



View Text Solution

15. In an experiment, the current flowing through a resistor and the potential difference across it are measured. The values are given below. Show that these values confirm Ohm's law, and find the resistance of the resistor.

i (ampere)	1.0	1.5	2.0	2.5	3.0
V (volt)	4.0	6.0	8.0	10.0	12



[View Text Solution](#)

16. The resistivity of copper is $1.7 \times 10^{-8} \Omega m$.

What length of copper wire of diameter 0.1 mm will have a resistance of 34Ω ?



View Text Solution

17. The resistivity of copper is $1.7 \times 10^{-8} \Omega m$.

Another copper wire of the same length but of half the diameter as the first is taken. What is the ratio of its resistance to that of the first wire ?





[View Text Solution](#)

18. Three resistors, each of resistance 12Ω , are connected in parallel. What is the equivalent resistance ?



[View Text Solution](#)

19. A uniform wire of resistance R is cut into two equal pieces, and these pieces are joined in parallel. What is the resistance of the combination ?



[View Text Solution](#)

20. How will you join the resistors of resistances 3Ω , 6Ω and 8Ω to get an equivalent resistance of 10Ω ?



[View Text Solution](#)

21. Find the current supplied by the cell in the circuit shown in Figure 4.E3.

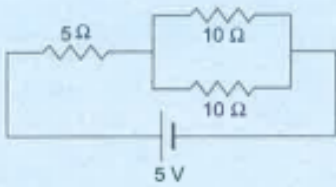



Fig. 4.E3



[View Text Solution](#)

22. In the circuit shown below, calculate the total resistance of the circuit and the current


flowing through it.

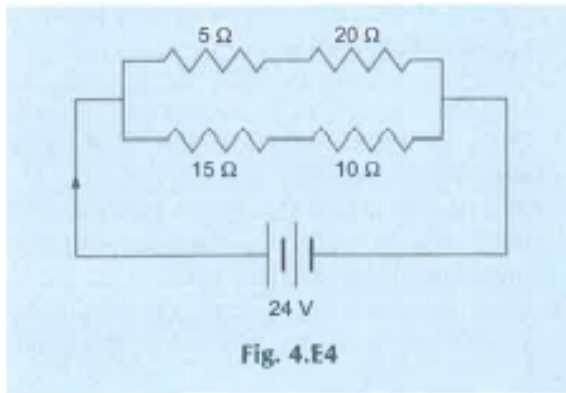

 [View Text Solution](#)

23. Figure 4.E5 shows a part of an electric circuit. The reading of the ammeter is 3.0 A. Find the currents through the 10Ω and

20 Ω resistors.

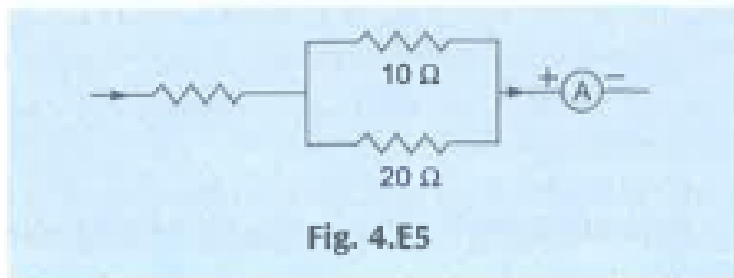

[View Text Solution](#)

24. A 12 -V battery connected to a bulb drives a current of 2.0 A through it. Find the energy supplied by the battery in 10 minutes.



[View Text Solution](#)

25. A current of 1.5 A flows through a wire of 8Ω Find the amount of heat produced in 10 seconds.



[View Text Solution](#)

26. A current of 2A produces 200J of heat in a wire in a given period of time. If the current is

increased to $4A$, how much heat will be produced in the same time ?



[View Text Solution](#)

27. A bulb is rated 5.0 V , 100 mA . Calculate its rated power and resistance.



[View Text Solution](#)

28. Calculate the resistance of a bulb rated 40 W , 230 V when in On condition.



[View Text Solution](#)

29. Calculate the current 10Ω and 20Ω are joined in series. A potential difference of 12 V is applied across the combination. Find the power consumed by each resistor.



[View Text Solution](#)

30. Two resistors of resistances 10Ω and 20Ω are joined in series. A potential difference of

12V is applied across the combination. Find the power consumed by each resistor.



[View Text Solution](#)

31. Two resistors of resistances 10Ω and 20Ω are joined in parallel. A potential difference of 12V is applied across the combination. Find the power consumed by each resistor.



[View Text Solution](#)

32. Calculate the energy consumed in kilowatt hours by a 60-W fan in 2 hours.



View Text Solution

33. A heater draws 1100 W at 220 V. Find the resistance of the heater when in On condition



View Text Solution

34. A heater draws 1100 W at 220 V. Calculate the kilowatt hours consumed in a week if the heater is used daily for four hours at the rated voltage .



View Text Solution

35. A bulb used in a car is rated 12 V, 48 W. Find the energy consumed in one minute when the bulb is connected to a 12 -V battery.



View Text Solution

36. A bulb used in a car is rated 12 V, 48 W. Find the energy consumed in one minute when the bulb is connected to a 6 -V battery.



View Text Solution

37. The potential at a point is 20 V. The work done in bringing a charge of 0.5 C. from infinity to this point will be

A. 20 J

B. 10 J

C. 5 J

D. 40 J

Answer: B



View Text Solution

38. A negative charge released from a point A moves along the line AB. The potential at A is 15 V, and it varies uniformly along AB. The potential at B.

A. may be 10 V

B. may be 15 V

C. may be 20 V

D. must be 15 V

Answer: C



View Text Solution

39. A charge is taken a point A to a point B.

The work done per unit charge in the process

is called

A. the potential at A

B. the potential at B

C. the potential difference between B and A

D. the current from A to B

Answer: C



View Text Solution

40. Joule/coulomb is the same as

A. watt

B. volt

C. ampere

D. ohm

Answer: B



View Text Solution

41. A voltmeter is used to measure

A. potential difference

B. electric current

C. electric power

D. resistance

Answer: A



View Text Solution

42. On which of the following no plus' or 'minus' sign is marked ?

A. a cell

B. an ammeter

C. a voltmeter

D. a resistor

Answer: D



View Text Solution

43. An ammeter is always connected in

And a voltmeter in The suitable words, in

order, for the blanks are

A. series, series

B. parallel , parallel

C. parallel , series

D. series , parallel

Answer: D



View Text Solution

44. In a metal,

A. all the electrons are free to move

B. all the electrons are bound to their parent atoms

C. there are no electrons

D. some electrons are free to move

Answer: D



View Text Solution

45. The free electrons of a metal are free to

A. move on the surface only

B. are free to escape through the surface

C. are free to fall into the nuclei

D. are free to move anywhere in the metal

Answer: D



View Text Solution

46. The current in a wire depends

A. only on the potential difference applied

B. only on the resistance of the wire

C. on both of them

D. on none of them

Answer: C



View Text Solution

47. Consider the following incomplete statement "Ohm's law relates potential difference with ... for a given resistance".The suitable choice of the missing word is

A. Power

B. energy

C. current

D. time

Answer: C



View Text Solution

48. Consider the following statements:(A) In series connection, the same current flows through each element.

B. In parallel connection, the same potential difference is applied across each element.

A. both A and B are correct

B. A is correct but B is wrong

C. A is wrong but B is correct

D. both A and B are wrong

Answer: A



View Text Solution

49. It is not possible to have a particle with charge 20×10^{-19} C.



View Text Solution

50. An electron released from rest at a point A moves towards a nearby point B. The potential at A is higher than the potential at B.



View Text Solution

51. A metal has a large number of electrons, but a nonmetal has only a small number of electrons.



View Text Solution

52. The Positive terminal of cell is connected to the end A, and the negative terminal is connected to the end B of a metallic wire AB. Electrons flow in the wire in the direction B to A.





[View Text Solution](#)

53. If two equal resistances are connected in parallel the equivalent resistance is halved.



[View Text Solution](#)

54. A thick wire has a larger resistance than a thin wire.



[View Text Solution](#)