



CHEMISTRY

BOOKS - VGS BRILLIANT CHEMISTRY (TELUGU ENGLISH)

ELECTRIC CURRENTT

Exercise

1. The net charge on a current carrying conductor is

A. Zero

B. Constant

C. varying

D. Negative

Answer:



Watch Video Solution

2. A steady current is passing through a conductor of non-uniform cross-section . The

net quantity of charge crossing any cross-section per second is

A. Independent of area of cross-section

B. Directly proportional to the length of conductor

C. Directly proportional to the area of cross – section

D. Inversely proportional to the length of conductor

Answer:



Watch Video Solution

3. If a current of 300 mA is following in a conductor, then the no.of electrons passed through the conductor in 4 min is (charge on an electron = $1.6 \times 10^{-19}C$)

A. 4.5×10^{20}

B. 9.0×10^{20}

C. 4.5×10^{18}

D. 9.0×10^{18}

Answer:



Watch Video Solution

4. At room temperature, copper has free electron density of $8.4 \times 10^{28} m^{-3}$. The electron drift velocity in a copper conductor of cross-sectional area of $10^{-6} m^2$ and carrying a current of 5.4 A , will be

A. $4m-s^{-1}$

B. $0.4m-s^{-1}$

C. 4 cm-s^{-1}

D. 0.4 mm-s^{-1}

Answer:



Watch Video Solution

5. The resistance of an incandescent lamp is

A. Greater when switched ON

B. Smaller when switched ON

C. Greater when switched OFF

D. same whether it is switched OFF or ON

Answer:



Watch Video Solution

6. Three copper wires have lengths and cross-sectional areas of $(l \text{ and } A)$, $(2l \text{ and } A / 2)$ and $(l/2 \text{ and } 2A)$. Resistance will be minimum in

A. Wire of cross – sectional area A

B. Wire of cross – sectional area $A / 2$

C. Wire of cross – sectional area $2A$

D. same in all three cases

Answer:



Watch Video Solution

7. If the length of a conductor is halved, then its conductance will be

A. halved

B. Doubled

C. Quadrupled

D. unchanged

Answer:



Watch Video Solution

8. What length of the wire (specific resistance $48 \times 10^{-8} \Omega - m$) is needed to make a resistance of 4.2Ω ?

A. $1 \cdot 1m$

B. $2 \cdot 1\text{m}$

C. $3 \cdot 1\text{m}$

D. $4 \cdot 1\text{m}$

Answer:



Watch Video Solution

9. A wire of length l is drawn such that its diameter is reduced to half of its original diameter. If the initial resistance of the wire were 10Ω , its new resistance would be

A. 40Ω

B. 80Ω

C. 120Ω

D. 160Ω

Answer:



Watch Video Solution

10. A uniform wire of resistance R is uniformly compressed along its length, until its radius

becomes n times the original radius. Now resistance of the wire becomes.

A. $\frac{R}{n^4}$

B. $\frac{R}{n^2}$

C. $\frac{R}{n}$

D. nR

Answer:



Watch Video Solution

11. A series combination of two resistors $1\ \Omega$ each is connected to a $12\ \text{V}$ battery of internal resistance $0.4\ \Omega$. The current flowing through it is

A. $10\ \text{A}$

B. $7.5\ \text{A}$

C. $5\ \text{A}$

D. $2.5\ \text{A}$

Answer:



Watch Video Solution

12. An electric current is passed through a circuit containing two wires of the same material, connected in parallel. If lengths and radii of the wires are in the ratio of 4 : 3 and 2 : 3 , then ratio of the currents passing through the wires will be

A. 0.125694444444444

B. 0.084027777777778

C. 0.04375

D. 0.0430555555555556

Answer:



Watch Video Solution

13. What will be the resistance between P and Q in the following circuit ?

A. 2Ω

B. 3Ω

C. 4Ω

D. 5Ω

Answer:



Watch Video Solution

14. A_3 volt battery with negligible internal resistance is connected in a circuit as shown in the figure. The current (1) in circuit will be

A. $\frac{1}{3}A$

B. $1A$

C. $1 \cdot 5A$

D. $2A$

Answer:



Watch Video Solution

15. A current of $2A$ flows in a system as shown in the figure. The potential difference between A and B ($V_A - V_B$) will be

A. $1v$

B. 2v

C. 3V

D. 4V

Answer:



Watch Video Solution

16. The current flowing through a lamp ,
marked as 60 W and 240 V is

A. 0.25A

B. 1A

C. $2 \cdot 5A$

D. 5A

Answer:



Watch Video Solution

17. The power of an electric bulb marked as 40 W and 200 V used in a circuit of supply voltage 100 V will be

A. 100 W

B. 40 W

C. 20 W

D. 10W

Answer:



Watch Video Solution

18. In India, electricity is supplied for domestic use at 220V. It is supplied at 110 V in USA. If the resistance of a 60 W bulb for use in India is R ,

then resistance of a 60 W bulb for use in USA
will be

A. R

B. $2R$

C. $\frac{R}{2}$

D. $\frac{R}{4}$

Answer:



Watch Video Solution

19. The net charge on a current carrying conductor is

A. Zero

B. Constant

C. varying

D. Negative

Answer:



Watch Video Solution

20. A steady current is passing through a conductor of non-uniform cross-section . The net quantity of charge crossing any cross-section per second is

A. Independent of area of cross-section

B. Directly proportional to the length of conductor

C. Directly proportional to the area of cross – section

D. Inversely proportional to the length of
conductor

Answer:



Watch Video Solution

21. If a current of 300 mA is following in a conductor, then the no.of electrons passed through the conductor in 4 min is (charge on an electron = $1.6 \times 10^{-19} C$)

A. 4.5×10^{20}

B. 9.0×10^{20}

C. 4.5×10^{18}

D. 9.0×10^{18}

Answer:



Watch Video Solution

22. At room temperature, copper has free electron density of $8.4 \times 10^{28} m^{-3}$. The electron drift velocity in a copper conductor of

cross-sectional area of $10^{-6}m^2$ and carrying a current of 5.4 A , will be

A. $4m\cdot s^{-1}$

B. $0.4m\cdot s^{-1}$

C. $4\text{ cm}\cdot s^{-1}$

D. $0.4\text{ mm}\cdot s^{-1}$

Answer:



Watch Video Solution

23. The resistance of an incandescent lamp is

A. Greater when switched ON

B. Smaller when switched ON

C. Greater when switched OFF

D. same whether it is switched OFF or ON

Answer:



Watch Video Solution

24. Three copper wires have lengths and cross-sectional areas of $(l \text{ and } A)$, $(2l \text{ and } A / 2)$ and $(l/2 \text{ and } 2A)$. Resistance will be minimum in

- A. Wire of cross – sectional area A
- B. Wire of cross – sectional area $A / 2$
- C. Wire of cross – sectional area $2A$
- D. same in all three cases

Answer:



Watch Video Solution

25. If the length of a conductor is halved, then its conductance will be

- A. halved
- B. Doubled
- C. Quadrupled
- D. unchanged

Answer:



Watch Video Solution

26. What length of the wire (specific resistance $48 \times 10^{-8} \Omega - m$) is needed to make a resistance of 4.2Ω ?

A. $1 \cdot 1m$

B. $2 \cdot 1m$

C. $3 \cdot 1m$

D. $4 \cdot 1m$

Answer:



Watch Video Solution

27. A wire of length l is drawn such that its diameter is reduced to half of its original diameter. If the initial resistance of the wire were 10Ω , its new resistance would be

A. 40Ω

B. 80Ω

C. 120Ω

D. 160Ω

Answer:



Watch Video Solution

28. A uniform wire of resistance R is uniformly compressed along its length, until its radius becomes n times the original radius. Now resistance of the wire becomes.

A. $\frac{R}{n^4}$

B. $\frac{R}{n^2}$

C. $\frac{R}{n}$

D. nR

Answer:



Watch Video Solution

29. A series combination of two resistors $1\ \Omega$ each is connected to a $12\ \text{V}$ battery of internal resistance $0.4\ \Omega$. The current flowing through it is

A. $10\ \text{A}$

B. $7.5\ \text{A}$

C. $5\ \text{A}$

D. $2.5\ \text{A}$

Answer:



Watch Video Solution

30. An electric current is passed through a circuit containing two wires of the same material, connected in parallel. If lengths and radii of the wires are in the ratio of 4 : 3 and 2 : 3 , then ratio of the currents passing through the wires will be

A. 0.125694444444444

B. 0.0840277777777778

C. 0.04375

D. 0.0430555555555556

Answer:



Watch Video Solution

31. What will be the resistance between P and Q in the following circuit ?

A. 2Ω

B. 3Ω

C. 4Ω

D. 5Ω

Answer:



Watch Video Solution

32. A 3 volt battery with negligible internal resistance is connected in a circuit as shown in the figure. The current (1) in circuit will be

A. $\frac{1}{3}A$

B. $1A$

C. $1 \cdot 5A$

D. $2A$

Answer:



Watch Video Solution

33. A current of $2A$ flows in a system as shown in the figure. The potential difference between A and B ($V_A - V_B$) will be

A. 1v

B. 2v

C. 3V

D. 4V

Answer:



Watch Video Solution

34. The current flowing through a lamp ,
marked as 60 W and 240 V is

A. $0 \cdot 25A$

B. $1A$

C. $2 \cdot 5A$

D. $5A$

Answer:



Watch Video Solution

35. The power of an electric bulb marked as 40 W and 200 V used in a circuit of supply voltage 100 V will be

A. 100 W

B. 40 W

C. 20 W

D. 10W

Answer:



Watch Video Solution

36. In India, electricity is supplied for domestic use at 220V. It is supplied at 110 V in USA. If the resistance of a 60 W bulb for use in India is R ,

then resistance of a 60 W bulb for use in USA
will be

A. R

B. $2R$

C. $\frac{R}{2}$

D. $\frac{R}{4}$

Answer:



Watch Video Solution