



# PHYSICS

## BOOKS - R G PUBLICATION

### ALTERNATING CURRENT

#### Exercise

1. The frequency of a.c. is doubled. How do  $X_L$  and  $X_C$  get affected?



Watch Video Solution

2. If  $L$  and  $R$  represent respectively the inductance and resistance the dimensions of  $L/R$  are



[Watch Video Solution](#)

3. What is eddy current? State two applications of eddy current.



[Watch Video Solution](#)

4. Show that the mean value of complete G.C. cycle is zero.



[Watch Video Solution](#)

5. In a series LCR circuit in which  $R = 3\Omega$ ,  $L=25\text{mH}$  and  $C = 800\mu\text{F}$  a sinusoidal a.c. voltage of peak value 250 V is applied. Find frequency at which resonance occurs



[Watch Video Solution](#)

6. In a series LCR circuit in which  $R = 3\Omega$ ,  $L=25\text{mH}$  and  $C = 800\mu\text{F}$  a sinusoidal a.c. voltage of peak value 250 V is applied. Find current in the circuit at resonant condition.



[Watch Video Solution](#)

7. What is step up and step down transformer?

To transfer electric energy from generating station initially step up transformer is used.

Why?




[Watch Video Solution](#)

8. Describe in brief the concept of displacement.

 [Watch Video Solution](#)

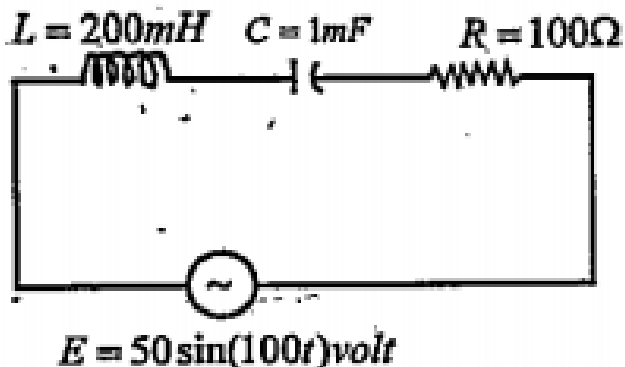9. Find the peak current in the circuit given below.





[Watch Video Solution](#)

**10.** what is power factor of an L-C-R circuit?

Explain on the basis of power factor than an ideal inductor is a Wattless component.



[Watch Video Solution](#)

**11.** Why is electrical energy transmitted at high voltage from a distance power generating station?



[Watch Video Solution](#)

**12.** An AC source of emf  $E = 200 \sin(100\pi t)$  is connected across an inductor having resistance  $100\Omega$  and self inductance  $2\text{H}$ . Calculate Frequency of AC.



[Watch Video Solution](#)

**13.** An AC source of emf  $E = 200 \sin(100\pi t)$  is connected across an inductor having

resistance  $100\Omega$  and self inductance  $2\text{H}$ .

Calculate- Total impedance of the circuit.



[Watch Video Solution](#)

**14.** An AC source of emf  $E = 200 \sin(100\pi t)$  is connected across an inductor having resistance  $100\Omega$  and self inductance  $2\text{H}$ . Calculate-Peak value of current flowing through the circuit.



[Watch Video Solution](#)



**15.** State the working principle of a transformer. What is hysteresis loss in transformer?



**Watch Video Solution**

**16.** Briefly explain the working of A.C. generator.



**Watch Video Solution**

17. An a.c. source of e.m.f.  $V_m \sin \omega t$  is connected with a circuit which contains an inductor  $L$ , a capacitor  $C$  and a resistor  $R$  in series. Establish the differential equation of e.m.f and find the total impedance of the series LCR circuit. What is quality factor of the circuit.



**Watch Video Solution**

**18.** A 40W-110V bulb is to be used in 220V-50Hz AC. Calculate the inductance required for this purpose.



**Watch Video Solution**

**19.** Explain the physical process on the basis of which the r.m.s value of AC is defined? Derive the expression for r.m.s value of an alternating voltage. How does the value of Capacitive voltage. How does the value of Capacitive

reactance of a capacitor change with the frequency of the applied alternating e.m.f across it.



[Watch Video Solution](#)

**20.** A charged capacitor is connected to an inductor at an instant of time  $t=0$ . If the capacitor and the inductor are taken to be pure, write down the equation of effective potential difference across the combination at any instant of time  $t$  and solve it for

instantaneous current through  $I$  the combination. Explain briefly the exchange of electric and magnetic energy between the capacitor and the inductor.



[Watch Video Solution](#)

21. Show that average power dissipated by a pure inductor and a pure capacitor are zero when they are connected to an AC voltage source.



[Watch Video Solution](#)

22. The amplitude of current in series LCR circuit connected to an AC frequency " $\omega$ " is given by

$$i_m = \frac{v_m}{\sqrt{R^2 + (X_L - X_C)^2}}$$

Where  $X_L$  and  $X_C$  are inductive and capacitive reactances respectively and  $v_m$  is amplitude of voltage. Starting from this equation show that sharpness of resonance in the circuit is equal to the quality factor of the circuit.



[Watch Video Solution](#)

### 23. Fill in the blanks

For an alternating current  $i = i_m \sin \omega t$ , passing through a resistor R, the average power loss p due to joule heating is\_\_\_\_\_.



[Watch Video Solution](#)

### 24. Fill in the blanks

The voltage of 220 v in an rms value with a peak value of \_\_\_\_\_



Watch Video Solution

25. Fill in the blanks

At resonant frequency the current amplitude

is \_\_ and  $i_m$  \_\_ \_



Watch Video Solution

26. Fill in the blanks

The ratio  $\left( W_o \frac{L}{R} \right)$  is called \_\_\_\_\_.



Watch Video Solution



**27. Fill in the blanks**

The average power supplied to an inductor over one complete cycle is \_\_\_\_\_.



**Watch Video Solution**

**28. Fill in the blanks**

Transformer use the principle of\_\_



**Watch Video Solution**

**29.** What is alternating current?



**Watch Video Solution**

**30.** What is root mean square value of current?



**Watch Video Solution**

**31.** What is quality factors?



**Watch Video Solution**

**32.** What is impedance?



**Watch Video Solution**

**33.** Deduce the expression for instantaneous power supplied to a capacitor when the capacitor is connected to an ac source.



**Watch Video Solution**

**34.** What is capacitive reactance?



[Watch Video Solution](#)

**35.** What is power factor?



[Watch Video Solution](#)

**36.** What is Iron in transformer?



[Watch Video Solution](#)

**37.** Can a transformer work on d.c.?



[Watch Video Solution](#)

**38.** What is meant by form factor?



[Watch Video Solution](#)

**39.** What is peak value of 220V a.c.?



[Watch Video Solution](#)

**40.** What is meant by wattless current?



[Watch Video Solution](#)

**41.** Does the steady state current in RL circuit depend upon L.



[Watch Video Solution](#)

**42.** What is the average value of a.c. over a complete cycle?



[Watch Video Solution](#)

**43.** What is the relation between mean value and peak value in a.c.



**Watch Video Solution**

**44.** What is the relation between r.m.s value and peak value?



**Watch Video Solution**

**45.** Can we use a capacitor instead of choke coil for reducing a.c.



**Watch Video Solution**

**46.** What is the minimum value of power factor?



**Watch Video Solution**



**47.** What is the phase difference between voltage and current in L-C-R circuit at resonance?



**Watch Video Solution**

**48.** What is meant by electric inertia?



**Watch Video Solution**

49. What is the impedance of a pure inductance?



[Watch Video Solution](#)

50. Show that an alternating voltage  $V = V_m \sin \omega t$  applied to a resistor  $R$  drives a current  $i = i \sin \omega t$  in the resistor.



[Watch Video Solution](#)

51. A light bulb is rated at 60w for a 230 v supply. Find the resistance of the bulb



**Watch Video Solution**

52. A light bulb is rated at 60w for a 230 v supply. Find the peak voltage of the source.




**Watch Video Solution**

53. A light bulb is rated at 60w for a 230 v supply. Find the rms current through the bulb



[Watch Video Solution](#)

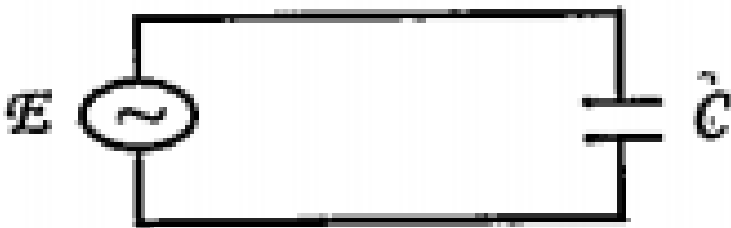54. Draw the phasor diagram and graph of  $v$  versus  $i$  for the circuit below:



[Watch Video Solution](#)

**55.** Draw the graphs of  $v$  and  $I$  versus  $\omega t$  for a series LCR circuit when  $X_C > X_L$ .



**Watch Video Solution**

**56.** Write a short note on resonance.



**Watch Video Solution**

**57.** Write the different applications of resonant circuit.



[Watch Video Solution](#)

**58.** Write a short note on sharpness of resonance.



[Watch Video Solution](#)

**59.** What are the two reasons for which LC Oscillations is not realistic?



[Watch Video Solution](#)

**60.** Differentiate between step up and step down transformer.



**Watch Video Solution**

**61.** Define the turn ratio, voltage ratio and current ratio of a transformer.



**Watch Video Solution**

**62.** An ideal inductor consumes no power in the circuit. Explain.



**Watch Video Solution**

**63.** Show that the average power dissipated depends not only on only on the voltage and current, but also on the cosine of the phase angle  $\phi$  between them.



**Watch Video Solution**



**64.** Discuss grow and decay of current in L-R ckt?



**Watch Video Solution**

**65.** What is meant by mean value of a.c. Derive an expression for mean value of a.c. over first half cycle.



**Watch Video Solution**

**66.** Discuss parallel resonance circuit. Where is it used?



**Watch Video Solution**

**67.** An ideal inductor consumes no power in the circuit. Explain.



**Watch Video Solution**

**68.** In what situation it is preferable to use an a.c. over dc.?



**Watch Video Solution**

**69.** A capacitor allows only a.c. to pass through. Why?



**Watch Video Solution**

**70.** Calculate the phase difference between voltage and current when circuit contains only capacitor.



**Watch Video Solution**

**71.** Calculate the energy stored in a capacitor.



**Watch Video Solution**

**72.** With a diagram show that in pure resistor, the voltage and current are in phase. The minima, zero and maxima occurred at the same respective times.



**Watch Video Solution**

**73.** An ac voltage is applied to a series of LCR circuit. Determine the instantaneous current  $i$  and its phase relationship to the applied alternating voltage  $v$ .





Watch Video Solution

74. "Larger the value of  $Q$ , the smaller of the value of  $2\Delta\omega$  or the bandwidth and sharper is the resonance". Describe.



Watch Video Solution

75. A resistor of  $100\Omega$  and a capacitor of  $\frac{20}{\pi}\mu F$  are connected in series to a 230V, 50Hz ac source. Calculate the current in the circuit.

Also calculate the voltage (rms) across the resistor and the capacitor.



[Watch Video Solution](#)

**76.** Show that the LC oscillation is similar to the mechanical oscillation of a block attached to a spring.



[Watch Video Solution](#)

77. What are the main two types of transformer.



[Watch Video Solution](#)

78. A transformer is used to illuminate a bulb (36 watt and 12v) with the help of 220V mains. If the efficiency of the transformer is 75%, then calculate the current in the primary coil.



[Watch Video Solution](#)



**79.** Calculate the total resistance in L-C-R circuit by mathematical method.



**Watch Video Solution**

**80.** Calculate the phase difference between voltage and current at resonance in L-C-R circuit



**Watch Video Solution**

**81.** The instantaneous current from an a.c. source is given by  $I = 5 \sin 314t$ . What is the r.m.s value of the current.



[Watch Video Solution](#)

**82.** The electric mains in house are marked 220V, 50 Hz. Write down the equation of instantaneous voltage.



[Watch Video Solution](#)

**83.** A sinusoidal voltage  $V = 200 \sin 314t$  is applied to a resistor of  $10\Omega$ . Calculate r.m.s value of voltage



**Watch Video Solution**

**84.** A sinusoidal voltage  $V = 200 \sin 314t$  is applied to a resistor of  $10\Omega$ . Calculate r.m.s value of current.



**Watch Video Solution**

**85.** What should be the frequency of alternating 200V so as to pass maximum current of 9A through an inductance of 1 henry.



**Watch Video Solution**

**86.** A  $3\mu F$  capacitor is connected to a 220V, 50 Hz a.c. source. Calculate the r.m.s value of current through the ckt.



**Watch Video Solution**

**87.** Obtain the resonance frequency of a series LCR circuit with  $L=2\text{H}$ ,  $C = 32\mu\text{F}$  and  $R = 10\Omega$ . What is the Q-value of this circuit.



[Watch Video Solution](#)

**88.** An inductor  $20\text{ mH}$ , a capacitor  $50\ \mu\text{F}$  and a resistor  $40\ \Omega$  are connected in series across a source of emf  $V=10\sin 340t$ . Calculate the power loss in A.C. circuit



[Watch Video Solution](#)

