



PHYSICS

BOOKS - R G PUBLICATION

CURRENT ELECTRICITY

Exercise

1. Give the dimensional representation of Resistance.



Watch Video Solution

2. State Ampere's circuital law.



[Watch Video Solution](#)

3. What is the missing term is Ampere's Circuital law?



[Watch Video Solution](#)

4. On a resistor, the four colour bands are green, violet, red and gold. Give the complete information about the resistor.



[Watch Video Solution](#)

5. Draw the circuit diagram of potentiometer to compare the emf of two cells and briefly describe the procedure.



[Watch Video Solution](#)

6. State Kirchoff's laws of current electricity.



[Watch Video Solution](#)

7. Establish the following relation for current flowing through a circuit containing an external resistance R , a battery of e.m.f E and internal resistance r .

$$I = \frac{E}{R + r}$$



[Watch Video Solution](#)

8. How do you define mobility of a charge carrier in a conductor? Establish the following relation for mobility.

$$\mu = q\tau / m$$




[Watch Video Solution](#)

9. State Ohm's law of current electricity. Define one Ohm resistance.



[Watch Video Solution](#)

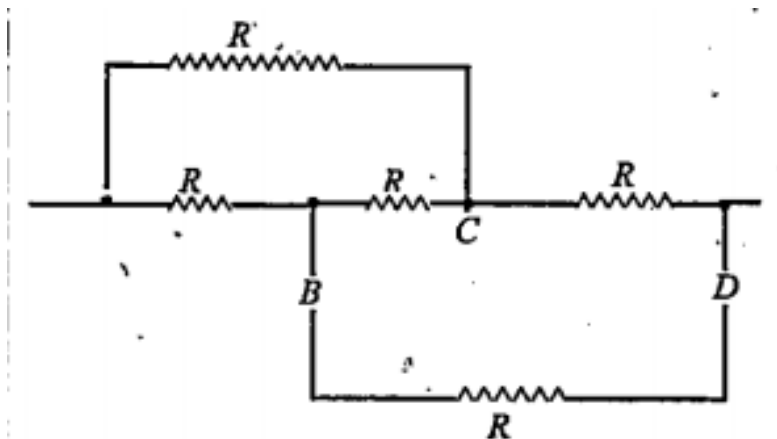10. Find the equivalent resistance between A and D.



 [Watch Video Solution](#)

11. What do you mean by specific resistance of a conductor? What is its S.I. unit?





[Watch Video Solution](#)

12. What is a potentiometer? Would you prefer a voltmeter or a potentiometer to measure the e.m.f. of a battery?




[Watch Video Solution](#)

13. Apply Kirchoff's laws of current electricity to establish the condition of a balanced Wheatstone's bridge.



[Watch Video Solution](#)

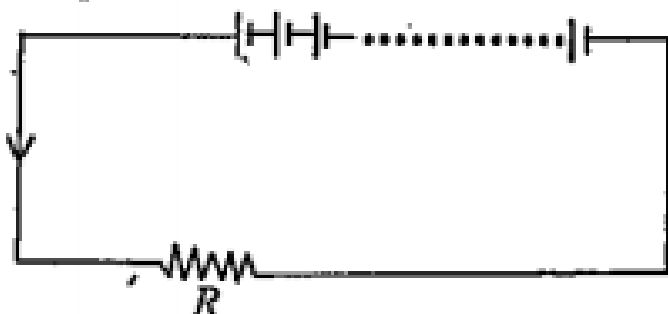14. n -identical cells each of emf E and internal resistance r are connected in series. Find the expression for current in the circuit given below.



[Watch Video Solution](#)

15. Establish the following relation for drift velocity.

$$V_d = \frac{eE}{m} \tau$$



Watch Video Solution

16. A copper wire is stretched so as to increase its length by 0.2% . Calculate the percentage change in the resistance of the wire.



Watch Video Solution

17. A 100W heater coil is rated 200V. Find the resistance of the coil.



[Watch Video Solution](#)

18. Draw the circuit diagram of a potentiometer to compare the emf of two cells and briefly describe the procedure.



[Watch Video Solution](#)

19. Draw the circuit diagram of the potentiometer to determine the internal resistance of a cell and briefly describe the procedure.



Watch Video Solution

20. You are given a potentiometer, a rheostat, one key, a driving cell for potentiometer, one galvanometer, two cells of unknown e.m.f., one two way key and some connecting wires. Using

all those given draw a circuit diagram for finding the ratio of the e.m.f. of the two cells.



[Watch Video Solution](#)

21. A battery of e.m.f. 2V and internal resistance 1Ω is used to send a current through a potentiometer wire of length 200cm and resistance 4Ω . What length of the wire will be required to balance a cell of e.m.f. 1.08V?




[Watch Video Solution](#)

22. Compare the amount of heat developed in three similar wires having length in the ratio 1:5:8 and radii 1:2:3 when joined in parallel.

 [Watch Video Solution](#)

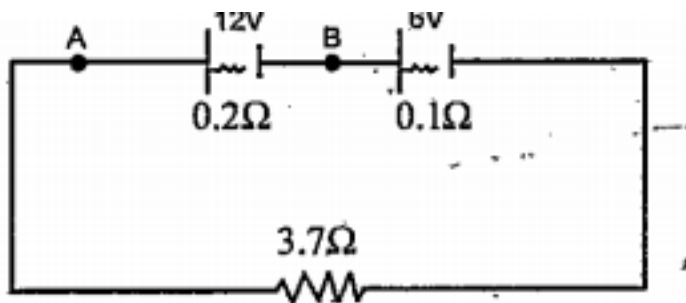23. In the circuit given below, find the potential difference between A and B




 [Watch Video Solution](#)

24. State Kirchoff's laws of current electricity.

 [Watch Video Solution](#)

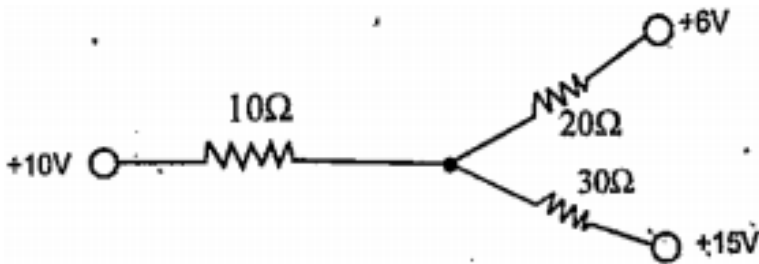25. In the circuit given below, find the current through 10Ω .



 [Watch Video Solution](#)


26. How is the changing electric field between the plates of a parallel plate capacitor during its charging, related to the idea of displacement current?



[Watch Video Solution](#)

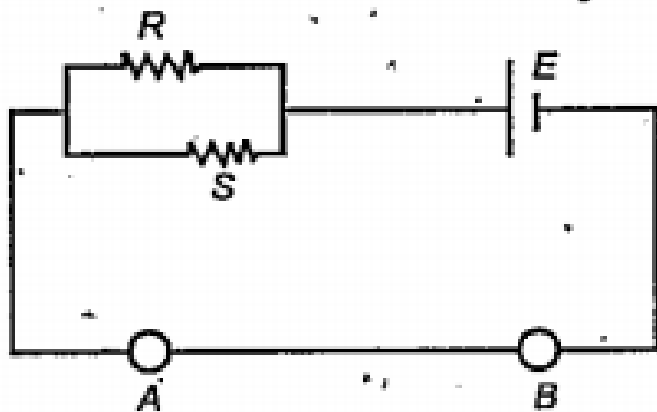27. A potentiometer wire AB has a length 0.5, and resistance 0.5Ω . As shown in the diagram, it is connected with a cell of e.m.f 3V and a combination of resistance $R = S = 5\Omega$. Fin


the potential dropt per unti length of the wire.



[Watch Video Solution](#)

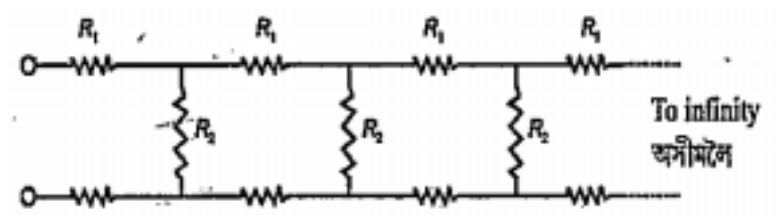28. As shown in the diagram, network of resistors R_1 and R_2 extends off to infinity of

the right. Find the equivalent resistance.



[Watch Video Solution](#)

29. Establish the following relation for drift velocity.

$$V_d = \frac{eE}{m} \tau$$



[Watch Video Solution](#)

30. With the help of graphs, how resistivity changes with temperature in the case of Copper



Watch Video Solution

31. With the help of graphs, how resistivity changes with temperature in the case of Nichrome



Watch Video Solution

32. With the help of graphs, how resistivity changes with temperature in the case of Semiconductor.



Watch Video Solution

33. Why is an insulator sometimes called a dielectric? What is the main difference between free and bound charge? Generally one of the two plates of a Capacitor System is earthed, why? Derive the expression for the energy stored in a charged capacitor.



[Watch Video Solution](#)


34. Define drift velocity of free electrons in a conductor across which a potential difference is applied. How is it related to mobility?



[Watch Video Solution](#)

35. Calculate the equivalent resistance between the points A and C of the following

circuit.

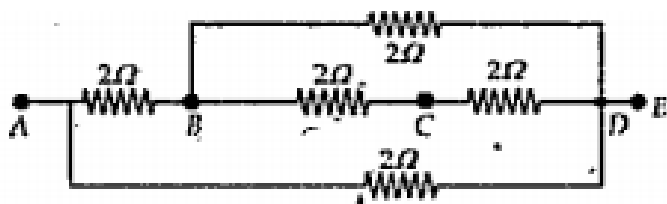

[Watch Video Solution](#)

36. Establish the following relation for current flowing through a circuit containing an external resistance R , a battery of e.m.f E and internal resistance r .


$$I = \frac{E}{R + r}$$

[Watch Video Solution](#)

37. State and explain Kirchhoff's rules used for analysis of an electric circuit.

 [Watch Video Solution](#)

38.

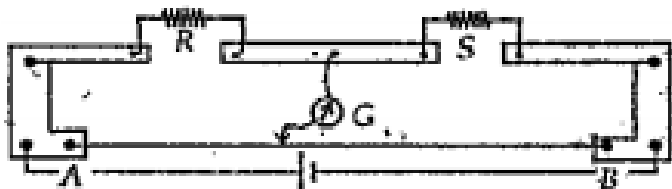


In the meter bridge shown in the above figure, the null point is found at a distance 33.7 cm from A and of the wire for particular values of R and S. If a resistance of 12Ω is connected

parallel with S, the null point is found to be at 48.1 cm from B end. Determine the value of R and S.



Watch Video Solution

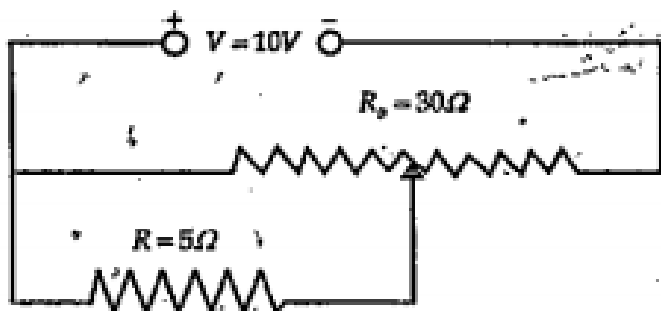

39.

As shown in the figure above, a resistance of $R = 5\Omega$ draws current from a potentiometer of total resistance $R_0 = 30\Omega$. A voltage $V = 10V$ is

supplied to the potentiometer. What is the voltage across R when the sliding contact is in the middle of the potentiometer?



[Watch Video Solution](#)

40. What is the SI unit of current?



[Watch Video Solution](#)

41. Who discovered the basic law regarding the flow of current?



[Watch Video Solution](#)

42. What is resistance of a conductor?



[Watch Video Solution](#)

43. Define the resistance of a conductor. What is its unit?



[Watch Video Solution](#)

44. What is the resistivity range of metals.



Watch Video Solution

45. Give the relation between emf and P.D.



Watch Video Solution

46. What is electromotive force(emf)?



Watch Video Solution

47. Give the relation between emf and P.D.



Watch Video Solution

48. Why a meter bridge is used?



Watch Video Solution

49. Give the unit of electromotive force.



Watch Video Solution

50. What is the unit of current density?



[Watch Video Solution](#)

51. In which principle Kirchhoff's junction rule is based on?



[Watch Video Solution](#)

52. Define conductivity.



[Watch Video Solution](#)

53. What are semiconductors? How electrical conductivity of semiconductors vary with temperature? Give one example of intrinsic semiconductor.



Watch Video Solution

54. What are the factors on which resistance of a conductor depends?



Watch Video Solution

55. What is super conductivity.



Watch Video Solution

56. State the principle of working of a potentiometer.



Watch Video Solution

57. What is the principle of a meter bridge.





[Watch Video Solution](#)

58. Kirchhoff's first law obeys laws of conservation of charge, how?



[Watch Video Solution](#)

59. When a Wheatstone Bridge will be balanced?



[Watch Video Solution](#)

60. What is ohmic and non ohmic conductor?



Watch Video Solution

61. How drift velocity related with random velocity?



Watch Video Solution

62. What is one ampere current?



Watch Video Solution

63. Write an expression for the ratio of resistance in balanced Wheatstone bridge.



Watch Video Solution

64. What is meant by free electron of a conductor?



Watch Video Solution

65. What is the difference between electric current and electric current density?



Watch Video Solution

66. What is a shunt? What is its use?



Watch Video Solution

67. What is electric current?



Watch Video Solution

68. Show that for a conductor $R = \rho \frac{l}{A}$ where l is the length and A is the cross sectional area of the conductor.



Watch Video Solution

69. What is the resistivity and current density?
Give their SI unit.



Watch Video Solution

70. Define conductivity.



Watch Video Solution

71. What is the drift velocity of electrons in a conductor? Establish the relation for drift velocity where the symbols have their usual meaning.



Watch Video Solution

72. What is mobility? Give its SI unit.



Watch Video Solution

73. Draw the characteristic curve of a diode of voltage V versus current I ?



Watch Video Solution

74. What is resistors? Why resistors are made mostly from carbon?



[Watch Video Solution](#)

75. Distinguish between conductors and insulators .Give examples.



[Watch Video Solution](#)

76. What is semiconductors? Give examples.



[Watch Video Solution](#)

77. "To reduce power dissipation in the connecting wires between different power stations of hundreds miles long, wires current at enormous value of V ". Explain.



[Watch Video Solution](#)

78. What is internal resistance of a cell?



[Watch Video Solution](#)

79. State and explain Kirchhoff's rules used for analysis of an electric circuit.



Watch Video Solution

80. State and explain Kirchhoff's rules used for analysis of an electric circuit.



Watch Video Solution

81. Give the experimental procedure to find out the internal resistance of a given cell using a potentiometer.



Watch Video Solution

82. What is the principle of a meter bridge.



Watch Video Solution

83. What is specific resistance of a conductor?

How it is related to electrical conductivity?



Watch Video Solution

84. The resistance of a Cu wire at $20^{\circ}C$ is 200Ω what is the resistance at $50^{\circ}C$?



Watch Video Solution

85. A current of 10 ampere passes through a wire having cross-sectional area 1mm^2 . The number of free electron per 1m^3 of the conductor is 10^{28} . Find the drift velocity of electron.



Watch Video Solution

86. Obtain an expression for equivalent resistance of three conductors when they are connected in series.






[Watch Video Solution](#)

87. State how resistance of a conductor depends upon length and cross-section.



[Watch Video Solution](#)

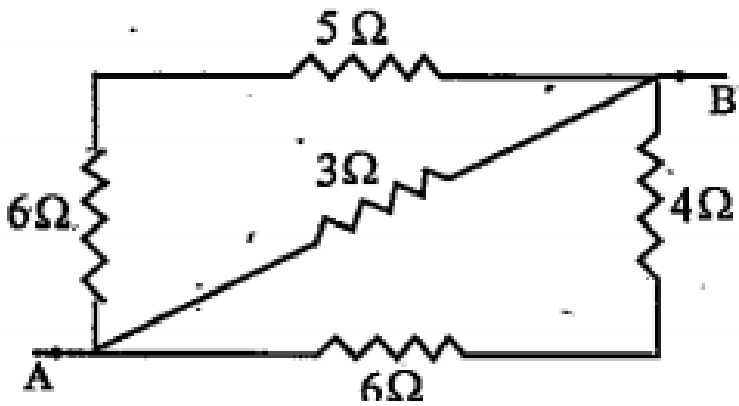
88. Find the equivalent resistance across A and B in the circuit.



[▶ Watch Video Solution](#)

89. From the circuit the reading of a volt meter is 18 volts. What is the resistance of the volt


meter?

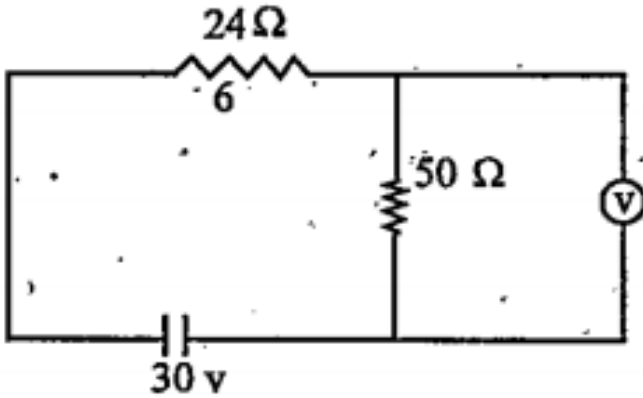

Watch Video Solution

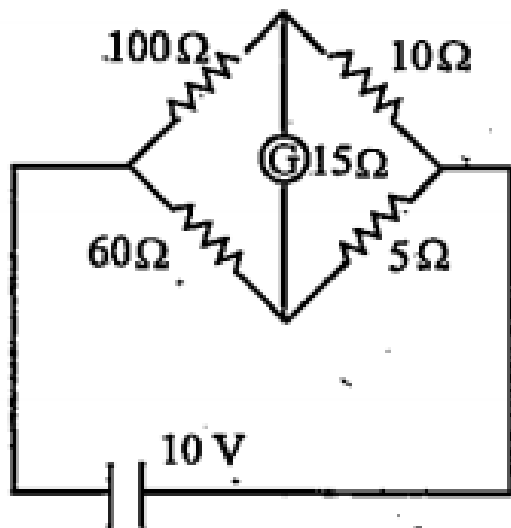90. The Wheatstone bridge circuit have the resistance in the various arms shown as figure

Calculate the current through galvanometer



[Watch Video Solution](#)

91. 12 identical wire each of resistance 6Ω are joined to form a cube. Find the resistance between the corner of edges of the cube.

A. `

B.

C.

D.

Answer:



Watch Video Solution

92. State Kirchhoff's voltage law and mention its significance.



 [Watch Video Solution](#)

93. What is Ohm's law? Describe.

 [Watch Video Solution](#)

94. Show that the current I through an area of cross section is given by the scalar product of two vectors $I = j \delta S$ where j and δs and vectors.

 [Watch Video Solution](#)

95. Write the limitation of Ohm's law.



[Watch Video Solution](#)

96. Find out the resistance value of the following resistors of four colour codes as

Brown	Black	Black	Gold
Blue	Orange	Yellow	Silver
Red	Orange	Brown	Gold
Brown	Black	Green	No colour.



[Watch Video Solution](#)

97. Deduce the relation of resistors when connected in parallel.



Watch Video Solution

98. N resistors are connected in series, and all resistors are same. Find out the equivalent resistance between the two ends.



Watch Video Solution

99. Give the equations for combination of n cells in series.



Watch Video Solution

100. Write an expression for the ratio of resistance in balanced Wheatstone bridge.



Watch Video Solution

101. Write the experimental procedure to find out an unknown resistance using a meter bridge.



Watch Video Solution

102. Give the experimental procedure to find out the internal resistance of a given cell using a potentiometer.



Watch Video Solution

103. Is Ohm's law universally applicable for all conducting elements? Write with examples.




Watch Video Solution

104. Apply Kirchoff's laws of current electricity to establish the condition of a balanced Wheatstone's bridge.



Watch Video Solution

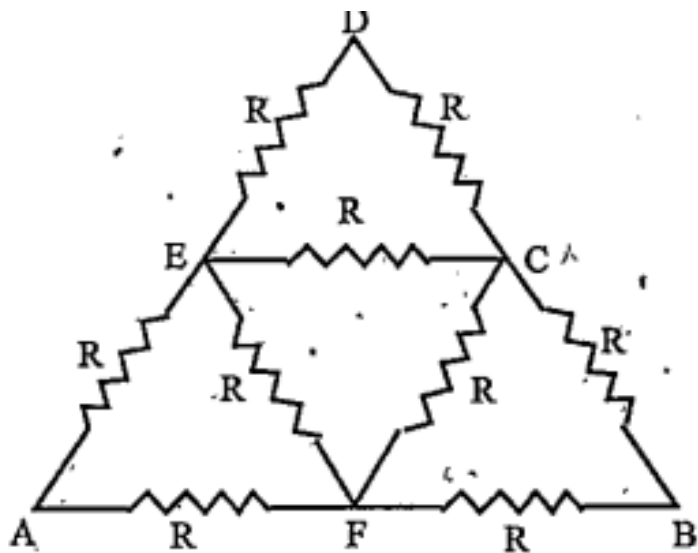105. From the circuit calculate the resistance between A and B.



Watch Video Solution


106. In a Wheatstone bridge the ratio arm P and Q are approximately equal. When $R = 500\Omega$ the bridge is balanced. On interchanging P and Q the value of R is 505Ω . Calculate the value of S.



Watch Video Solution

107. Calculate the potential difference between the junction B and D in the Wheatstone

bridge.

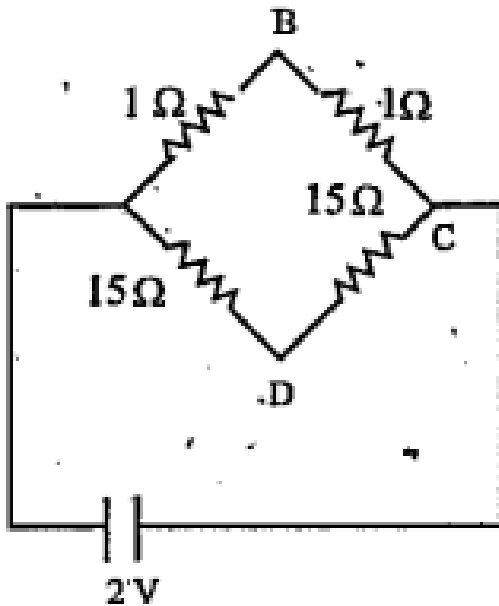

[Watch Video Solution](#)

108. In a meter bridge the resistance R and x , R being less than x . A balance point is obtained

40 cm from zero and on shunting the coil by 50Ω the balance point moves through 10cm.

Calculate the value of R and x.



[Watch Video Solution](#)

109. In a meterbridge length of the wire is 100cm. At what point balance point be obtained if the resistance are in the ratio 4:5.



[Watch Video Solution](#)

110. Two cells of emf. 1.5V and 2 V and internal resistance 2 Ω and 1 Ω respectively have their negative terminal joined by a wire of 6 Ω and positive terminal by another wire of 4 Ω . A third resistance of 8 Ω connected mid point of these wire. Find the potential difference at the end of the third wire.



Watch Video Solution

111. State the principle of working of a potentiometer.



Watch Video Solution