



PHYSICS

BOOKS - BINA LIBRARY PHYSICS

(ASSAMESE ENGLISH)

CURRENT ELECTRICITY

Example

1. A silver wire of 1 mm diameter has a charge of 90 coulombs flowing in 1 hours and 15

minutes. Silver contains 5.28×10^{28} free electrons per cm^3 . Find the current in the wire and drift velocity in the electron?



[Watch Video Solution](#)

2. A force of 1000 Newton is applied on a 25 kg mass for 5 seconds. What would be its velocity?



[Watch Video Solution](#)

3. Momentum of an object changes from 100 kg m/s to 200 kg m/s in 2 seconds. What is the force applied to it?



[Watch Video Solution](#)

4. A force of 200 N is applied to a body and its velocity changes from 5m/s to 10m/s in a second. What is the mass of the body?



[Watch Video Solution](#)

5. A copper wire has a diameter of 0.5 mm and a resistivity of 1.6×10^{-6} ohm-m. How much of this wire would be necessary to make a resistance of 10 ohm?



[Watch Video Solution](#)

6. If a copper wire is stretched to make 0.1% longer, what is the P.C. change in its resistance?



[Watch Video Solution](#)

7. A wire of one ohm resistance is stretched to three times its original length. Calculate the new resistance if the new radius is one-third the original radius.



[Watch Video Solution](#)

8. If the distance between 2 objects is doubled then how will the gravitational force between them change?



[Watch Video Solution](#)

9. Two resistances of 5 ohm and 10 ohm are connected in parallel and then a current is passed through them from a battery of 6 volt. Calculate the currents drawn from the battery and also the currents flowing through each of the resistances.



Watch Video Solution

10. Two resistances 99 ohms and 1 ohm are connected in parallel. Find the current in each

when the main current in the circuit is 10 ampere.



Watch Video Solution

11. Filament of an electric lamp draws a current of 0.4 A, which lights for 3 hours. What is the amount charge passed in coulomb ?



Watch Video Solution

12. A force of 1200 N acts on the surface of area 10 cm^2 normally. What would be the thrust and pressure on the surface?



Watch Video Solution

13. The elephant weighs 20,000 N stands on one foot of area 1000 cm^2 . How much pressure would it exert on the ground?



Watch Video Solution

14. Calculate the pressure produced by a force of 800 N acting on an area of 2.0 m²



Watch Video Solution

15. The pressure of a gas contained in a cylinder with a movable piston is 300 Pa. The area of the piston is 0.5 m². Calculate the force that is exerted on the piston.




Watch Video Solution

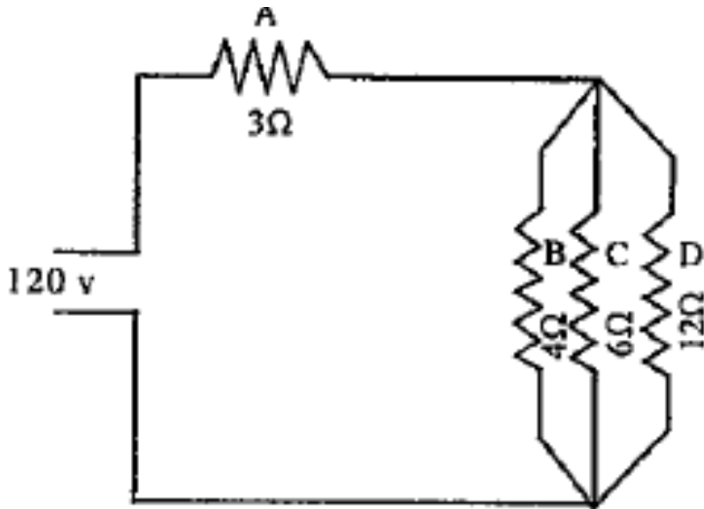16. With reference to the circuit shown in Fig.

find the following:

Potential difference across the parallel.



[Watch Video Solution](#)

17. Two resistances each of value 2 ohm and 4 ohm are connected in parallel and the total

current through the combination is 1 amp.

What are the values of current through each resistance?




[Watch Video Solution](#)

18. Calculate the resistivity of a wire having resistance .02 ohm, length = 10 m and area = 1mm^2



[Watch Video Solution](#)

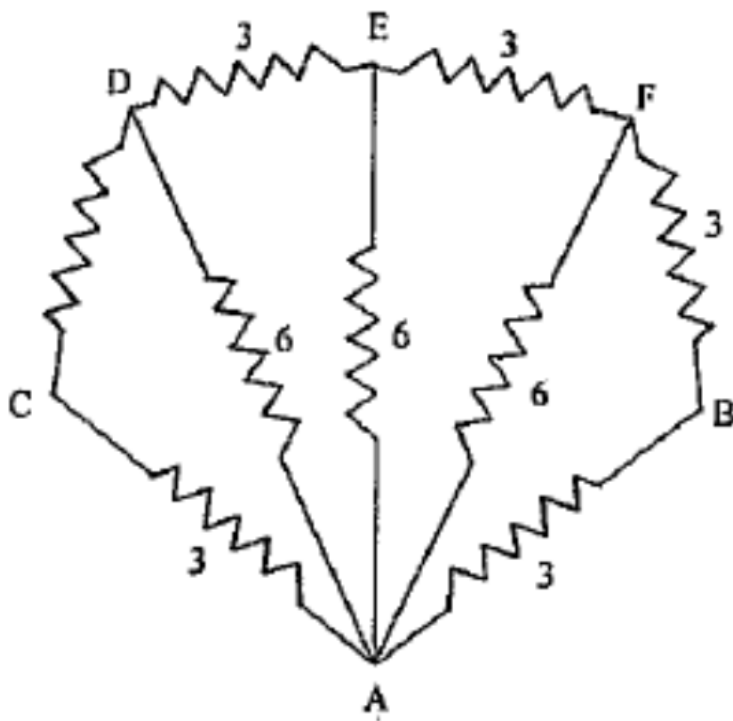19. All resistances in diagram are in ohm. Find the effective resistance between A and B.



Watch Video Solution

20. Calculate the value of the shunt resistance necessary to increase the measuring range of an ammeter of internal resistance 0.1 ohm from 1 ampere to 5 ampere .



Watch Video Solution

21. A milliammeter of resistance 5 ohms gives a full scale deflection for a current of 15 mA . If the milliammeter is to be used to measure

currents upto 1.5 A the size of the resistance that must be attached to the milliammeter is ?



[Watch Video Solution](#)

22. When a 12V battery is connected across an unknown resistor, there is a current of 2.5 mA in the circuit. Find the value of the resistance of the resistor.



[Watch Video Solution](#)

23. A 25 watt and a 100 watt bulbs are joined in series and connected to mains. Which will glow brighter? What will happen when the bulbs are connected in parallel?



Watch Video Solution

24. An electric kettle has two coils. When one of these is switched on, the water in the kettle boils in 15 minutes. When the other is switched on, the water boils in 30 minutes.

In how many minutes will water boil if the coils are connected in series and switched on?



[Watch Video Solution](#)

25. Two boys exert force of 40 N and 60 N in opposite direction on an object. What will be the resultant force ?



[Watch Video Solution](#)

26. The potential difference between the terminals of a cell in open circuit is 2.2V. When it is connected through a resistance of 5ohm , the P.D. falls to 1.8V. Find the internal resistance of the cell.



Watch Video Solution

27. A box weighing 2 kg exerts a force of 20 N on the ground. The box covers an area of 2 sq.

m on the ground. Find the pressure exerted by the box on the ground.



[Watch Video Solution](#)

28. Find the best arrangement for 36 cells, each of emf 1.5 volt and internal resistance 0.5 ohm when they are connected with 2 ohm resistance. Calculate the maximum current in the arrangement.



[Watch Video Solution](#)

29. What is contact force?



Watch Video Solution

30. What is the similarity between electrostatic and magnetic forces?



Watch Video Solution


31. How can we change the speed and the direction of a moving body?





Watch Video Solution

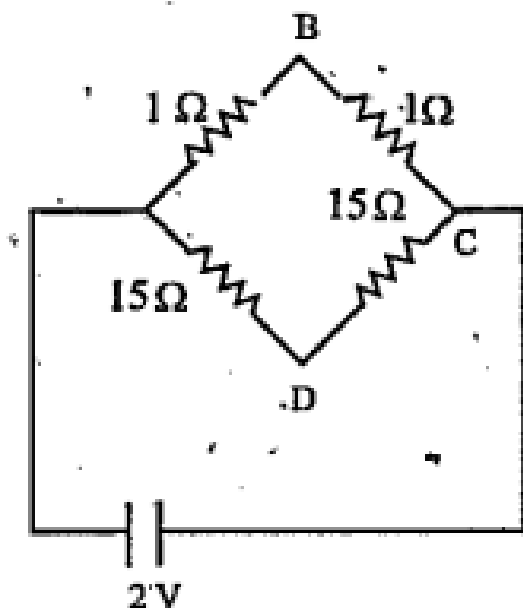32. Calculate the potential difference between the junction B and D in the Wheatstone bridge.



Watch Video Solution

33. Give two examples of contact force.



Watch Video Solution

34. The speed of a car weighing 1500 kg increases from 36 km/h to 72 km/h uniformly.

What will be the change in momentum of the car?



Watch Video Solution

35. What is the unit of measuring the momentum of a moving body ?



Watch Video Solution

36. Find force required in accelerating a 3 kg mass at 5 m/s^2 and a 4 kg mass at 4 m/s^2



Watch Video Solution

37. A bullet of mass 40gm is fired from a gun of mass 8kg with a velocity of 800 m/s,

calculate the recoil velocity of gun.



[Watch Video Solution](#)

38. A potentiometer wire is of length 10 m and has a total resistance of 18 ohm. It carries a current of 120 mA. What length of it will be necessary to balance a cell of emf 1.5 volt ?



[Watch Video Solution](#)

39. Using a potentiometer, balance points are obtained at 60 cm and 10 cm with two cells connected in series first to support one another and then in opposition respectively. Find the ratio of the emfs of the cells.



Watch Video Solution

40. In a potentiometer experiment, it is found that no current passes through the galvanometer, when the terminals of a cell are

connected across 50 cm of the potentiometer wire. If the cell is shunted by a resistance of 5 ohm, the balance point is found at 40 cm of the wire from the same end. Find the internal resistance of the cell.



[Watch Video Solution](#)

41. A potentiometer wire of length 100 cm has a resistance of 10 ohm. It is connected in series with a resistance and a battery of emf 2V and of negligible internal resistance. A

source of emf 10mV is balanced against a length of 40 cm of the potentiometer wire.

What is the value of the external resistance?



[Watch Video Solution](#)

Exercise

1. Define electric current. Is it scalar or vector?



[Watch Video Solution](#)

2. What is the direction of flow of current?



[Watch Video Solution](#)

3. What is needed to cause an electric current?



[Watch Video Solution](#)

4. Define emf of a cell. What is its unit?



[Watch Video Solution](#)

5. Is emf a scalar or a vector quantity?



[Watch Video Solution](#)

6. Define electrical conductivity.



[Watch Video Solution](#)

7. What quantity of a circuit affects the current?



[Watch Video Solution](#)

8. What is meant by drift velocity of electrons ?



[Watch Video Solution](#)

9. How does electric field vary with drift velocity?



[Watch Video Solution](#)

10. What is the order of the drift velocity of electrons?



Watch Video Solution

11. Why the drift of the positive ions is not considered?



Watch Video Solution

12. What is Ohm's law? Describe.



[Watch Video Solution](#)

13. Define the resistance of a conductor. What is its unit?



[Watch Video Solution](#)

14. Define the specific resistance of the material of a conductor. What is its unit?



[Watch Video Solution](#)

15. What is conductance? What is its unit?



Watch Video Solution

16. Define one ohm.



Watch Video Solution

17. How does resistance of a metal vary with temperature?



Watch Video Solution

18. What is super conductivity.



Watch Video Solution

19. Give the dimensional representation of Resistance.



Watch Video Solution

20. What is a shunt? What is its use?





[Watch Video Solution](#)

21. Will the bends in a wire effect its resistance?



[Watch Video Solution](#)

22. What type of charges are responsible for conduction of electricity in a metallic conductor?



[Watch Video Solution](#)

23. How is current density related to electric field?



Watch Video Solution

24. Is a current carrying conductor electrically charged?



Watch Video Solution

25. Is there any electric field inside a current carrying conductor?



Watch Video Solution

26. What is the basic concept of first law of Kirchhoff?



Watch Video Solution

27. State Kirchhoff's current law



[Watch Video Solution](#)

28. State Kirchhoff's voltage law and mention its significance.



[Watch Video Solution](#)

29. Name one substance whose resistance decreases with increase of temperature.



[Watch Video Solution](#)

30. What is potential gradient.



Watch Video Solution

31. What is the principle of a meter bridge.



Watch Video Solution

32. Is it necessary to keep the length of a metre bridge wire one metre?



Watch Video Solution

33. Why is a potentiometer named as potentiometer



Watch Video Solution

34. State two uses of a potentiometer.



Watch Video Solution

35. Discuss various situations, which describe the failure of Ohm's law,



Watch Video Solution

36. Define mobility of a charge carrier. What is its relation with relaxation time?



Watch Video Solution

37. What is meant by drift velocity of electrons ?



Watch Video Solution

38. State Kirchoff's laws of current electricity.



Watch Video Solution

39. Apply Kirchoff's laws to establish the principle of a balanced Wheatstone's bridge.



Watch Video Solution

40. Establish the following relation for current flowing through a circuit containing an external resistance R , a battery of e.m.f E and internal resistance r .

$$I = \frac{E}{R + r}$$



Watch Video Solution

41. Obtain an expression for the equivalent resistance when n identical resistors each having resistance R are connected in series.



Watch Video Solution

42. n identical resistors each having resistance R are connected in parallel. Find the value of equivalent resistance.



Watch Video Solution

43. One low resistance is connected in parallel to a high resistance. Show that their equivalent resistance is of the order of low resistance.



Watch Video Solution

44. What is a potentiometer? Why is it most accurate device in measuring emf of a cell?



Watch Video Solution

45. Define rest and motion



Watch Video Solution

46. What is Ohm's law? Describe.



Watch Video Solution

47. Give an example of circular motion.



Watch Video Solution

48. What is meant by rectilinear motion? Give two examples.



Watch Video Solution

49. Why heat energy is produced, when electric current passes through a resistance wire?



Watch Video Solution

50. Obtain an expression for the heat produced in a wire, when a current I passes through it against potential difference V .



[Watch Video Solution](#)

51. Write two differences between electromotive force and potential difference.



[Watch Video Solution](#)

52. Give two example of periodic motion.



Watch Video Solution

53. What is the principle of a meter bridge.



Watch Video Solution

54. State the principle of working of a potentiometer.



Watch Video Solution

55. If the length of a wire is doubled and cross-sectional area is halved, what happens to the resistance?



Watch Video Solution

56. Two ends of a conducting wire of non-uniform cross-section are connected to a battery. Explain why the electric field at the

thinner section is different from the electric field at the thicker section.



[Watch Video Solution](#)

57. The magnitude of drift velocity of free electrons in a conductor is very low, but an electric bulb glows instantly when the current is switched on. Explain the reason.



[Watch Video Solution](#)

58. Why are the car lights dimmed when the starter is operated?



Watch Video Solution

59. Why is it easier to start a car engine on a warm day than on a chilly day ?



Watch Video Solution

60. What is rolling friction ?



[Watch Video Solution](#)

61. When is Wheatstone bridge most sensitive ?



[Watch Video Solution](#)

62. Why do we prefer a potentiometer with longer wire?



[Watch Video Solution](#)

63. Why do we prefer a potentiometer with longer wire?



Watch Video Solution

64. Why should the balance point be obtained in the middle of the wire of a metre bridge?



Watch Video Solution

65. Define friction.





[Watch Video Solution](#)

66. A potential difference of 5 V is applied across a conductor of length 10 cm. If drift velocity of the electron is $2.5 \times 10^{-4} \text{ ms}^{-1}$ find the mobility of electron.



[Watch Video Solution](#)

67. Specific resistance of the material of a wire is $44 \times 10^6 \Omega \text{ cm}$. If the resistance of the wire is

14Ω and its diameter 1 mm, calculate the length of the wire.



[Watch Video Solution](#)

68. A cylindrical metallic wire is stretched to increase its length by 5%. Calculate the percentage change in its resistance.



[Watch Video Solution](#)

69. A cell of emf 4V and internal resistance 0.5 is connected across a load resistance (i) 7.52, (ii) 11.50, calculate (i) the ratio of difference in emf of the cell and the potential drop across the load.(ii) the ratio of current in the two cases.



Watch Video Solution

70. A battery gives a current of 0.5A with an external resistor of 12Ω and 0.25 A with

resistor of 25Ω Calculate the

emf



[Watch Video Solution](#)

71. battery gives a current of 0.5A with an external resistor of 12Ω and 0.25A with resistor of 25Ω Calculate the internal resistance of the battery.



[Watch Video Solution](#)

72. A cell can be balanced against 110 cm and 100 cm of potentiometer wire respectively when in open circuit and when short circuited through a resistance of 10Ω . Find the internal resistance of the cell.



Watch Video Solution

73. A resistance wire connected in the left gap of a metre bridge balances a 10Ω resistance in the right gap at a point which divides the

bridge wire in the ratio 3:2. If the length of the resistance wire is 1.5m, then find the length of 1Ω of the resistance wire.



[Watch Video Solution](#)

74. In a potentiometer arrangement, a cell of emf 1.25 V gives a balance point at 35.0 cm length of the wire. If the cell is replaced by another cell and the balance point shifts to 63.0 cm, what is the emf of the second cell?



[Watch Video Solution](#)

75. With a certain cell, the balance point is obtained at 65 cm from the end of a potentiometer wire. With another cell whose emf differs from that of the first by 0.1V the balance point is obtained at 60cm. Find the emf of each cell.



Watch Video Solution

76. Two wires of same metal have same length, but their cross sections are in the ratio 3 : 1.

They are joined in series. The resistance of the thicker wire is 10Ω The total resistance of the combination is

A. $\frac{5}{2}\Omega$

B. $\frac{40}{3}\Omega$

C. 40Ω

D. 100Ω

Answer: A::D



Watch Video Solution

77. A wire of resistance R is cut into n equal parts. These parts are connected in parallel. The equivalent resistance of the combination is

A. nR

B. R/n

C. n/R

D. $\frac{R}{n^2}$

Answer: B



Watch Video Solution

78. The resistance of a 10m long wire is $10\ \Omega$. Its length is increased by 25% by stretching. The resistance of the wire is now

A. $12.5\ \Omega$

B. $14.5\ \Omega$

C. $15.6\ \Omega$

D. $16.6\ \Omega$

Answer: A



Watch Video Solution

79. If there is an increase in length by 0.1% due to stretching the percentage increase in its resistance will be

A. 0.001

B. 0.002

C. 0.01

D. 0.02

Answer: B



80. How many electrons constitute current of one ampere?

A. 6.25×10^9

B. 6.25×10^{18}

C. 6.25×10^5

D. 6.25×10^6

Answer: A::B



81. A car battery has emf 12V and internal resistance $5 \times 10^{-2} \Omega$. it draws 60A current. The terminal voltage of the battery in

A. 3 V

B. 5 V

C. 9 V

D. 15 V

Answer:



Watch Video Solution

82. The internal resistance of a cell of emf 2V is 0.1Ω . It is connected to a resistance of 3.9Ω .
The voltage across the cell is

A. 0.5 V

B. 1.9 V

C. 1.95 V

D. 2 V

Answer: A



83. The resistance in two gaps of a meter bridge are 10Ω and 30Ω respectively. If the resistances are interchanged the balance point shifts by

A. 33.3 cm

B. 66.67 cm

C. 25 cm

D. 50 cm

Answer: C



Watch Video Solution

84. What is a potentiometer? Why is it most accurate device in measuring emf of a cell?

A. it uses sensitive galvanometer for null

deflection

B. it uses high resistance potentiometer

wire

C. it measures the potential in the closed circuit

D. it measures the potential in open circuit.

Answer:



Watch Video Solution

85. In a potentiometer experiment the balancing length with a cell is 560 cm. When an external resistance of 10Ω is connected in parallel to the cell, the balancing length

changes to 60 cm. The internal resistance of the cell is

A. 3.6Ω

B. 2.4Ω

C. 1.2Ω

D. 0.6Ω

Answer: A::C



Watch Video Solution

86. Two resistances are joined in parallel whose resultant is $\frac{6}{5}$ ohms. One of the resistance wire is broken and the effective resistance becomes 2 ohms. The resistance in ohms of the wire that got broken

A. 2

B. 3

C. $\frac{3}{5}$

D. $\frac{6}{5}$

Answer: B



Watch Video Solution

87. The smallest resistance obtained by connecting 50 resistance of $\frac{1}{4}$ ohm each is

A. $\left(\frac{50}{4}\right)\Omega$

B. $\left(\frac{4}{50}\right)\Omega$

C. 200Ω

D. $\left(\frac{1}{200}\right)\Omega$

Answer: D



88. How many different combinations of three equal resistors can be made ?

A. three

B. four

C. five

D. six

Answer: B



89. A steady current flows in a metallic conductor of non uniform cross-section. The quantity quantities constant along the length of the conductor is / are

A. drift speed

B. drift speed and current

C. current and electric field

D. current only

Answer: D



Watch Video Solution

90. A metallic wire of resistance 40Ω is stretched to twice its length. The new resistance approximately

A. 20Ω

B. 80Ω

C. 120Ω

D. 160Ω

Answer: D



Watch Video Solution

91. A metallic wire is drawn to reduce its diameter to half its original value. Its resistance becomes

A. two times

B. four times

C. eight times

D. sixteen times

Answer: D



Watch Video Solution

92. Three resistances each of 4Ω are connected to form a triangle. The resistance between any two terminals is

A. 12Ω

B. 2Ω

C. 6Ω

D. $\frac{8}{3}\Omega$

Answer: D



Watch Video Solution

93. Four wires of equal length and of resistance 10Ω each are connected square.

The equivalent resistance between two opposite corners is

A. 10Ω

B. 40Ω

C. 20Ω

D. $\frac{5}{2}\Omega$

Answer: A



Watch Video Solution

94. Assuming that the charge of an electron is 1.6×10^{-19} C. The number of electrons passing through a section of wire per second, when the wire carries a current of 1A is

A. 0.625×10^{19}

B. 1.6×10^{-19}

C. 1.6×10^{19}

D. 0.625×10^{17}

Answer: A



Watch Video Solution

95. The electrical resistance of metals

- A. increases with increases in temperature.
- B. decreases with increase in temperature
- C. is independent of temperature

D. sometimes increases, sometimes

decreases with temperature

Answer: A



Watch Video Solution

96. The resistance of a conductor is 5Ω at 50°C and 6Ω at 100°C . What is its temperature at 0°C ?

A. 1Ω

B. 2Ω

C. 3Ω

D. 4Ω

Answer: D



Watch Video Solution

97. A piece of copper and another of germanium are cooled from room temperature to 80K. The resistance of

A. each of them increases

B. each of them decreases

C. copper increases and germanium
decreases

D. copper decreases and germanium
increases

Answer: D



Watch Video Solution

98. What is the order of the drift velocity of electrons?

A. few millimeter per second

B. $3 \times 10^{10} \text{ m} \frac{\text{m}}{\text{sec}}$

C. $3 \times 10^{10} \text{ m} \frac{\text{m}}{\text{sec}}$

D. none of the above

Answer: A



Watch Video Solution

99. A wire of 4Ω resistance is bent at 180° at its mid point and twisted together. Then the resistance between the ends is

A. 8Ω

B. 1Ω

C. 2Ω

D. 5Ω

Answer: B



Watch Video Solution

100. A and B are two wires of copper of equal cross-section and A is longer than B. The specific resistance of

A. A is greater than B

B. B is greater than A

C. A and B are same

D. none of the above

Answer: C



Watch Video Solution

101. If a wire of uniform cross sectional area is cut equally into two parts the resistivity part

A. is halved

B. is doubled

C. remains same

D. none of the above

Answer: C



Watch Video Solution

102. Ampere second is the unit of

A. power

B. energy

C. emf

D. charge

Answer: D



Watch Video Solution

103. The temperature co-efficient of resistance of a wire is $0.00125^{\circ}C^{-1}$. At 300K its resistance is 1 ohm. The resistance of the wire will be 2 ohm at which temperature?

A. 154 K

B. 1100K

C. 1400K

D. 1127 K

Answer: B



Watch Video Solution

104. Krichhoff's first law deals with conservation of

A. energy

B. charge

C. momentum

D. angular momentum

Answer: B



Watch Video Solution

105. The instrument for accurate measurement of emf of a cell is

- A. a voltmeter
- B. an ammeter
- C. a metre bridge
- D. a potentiometer

Answer: D



Watch Video Solution

106. In a metre bridge, the balancing length from the left end is 20 cm. The resistance in the right gap is 1Ω . The value of the unknown resistance is

A. 0.8Ω

B. 0.5Ω

C. 0.25Ω

D. 0.4Ω

Answer: C



Watch Video Solution

107. The sensitivity of a potentiometer can be increased by

A. increasing the emf of the primary cell

B. increasing the length of the wire

C. decreasing the length of the wire.

D. increasing the potential gradient.

Answer: B



View Text Solution

