




## PHYSICS

### BOOKS - AAKASH SERIES

### CAPACITORS

#### Lecture Sheet Exercise I Level I Main Straight Objective Type Questions

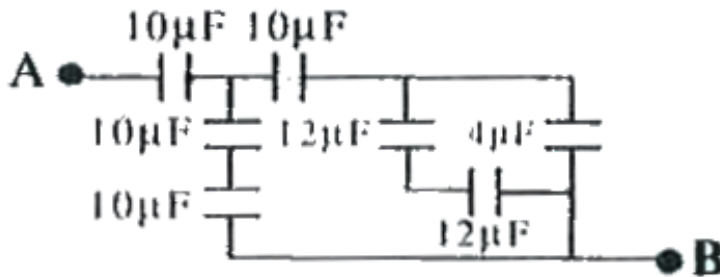1. In the given circuit the effective capacity between A and B is



A.  $20\mu\text{F}$

B.  $5\mu\text{F}$


C.  $30\mu F$

D.  $10\mu F$

**Answer: B**

[▶ Watch Video Solution](#)

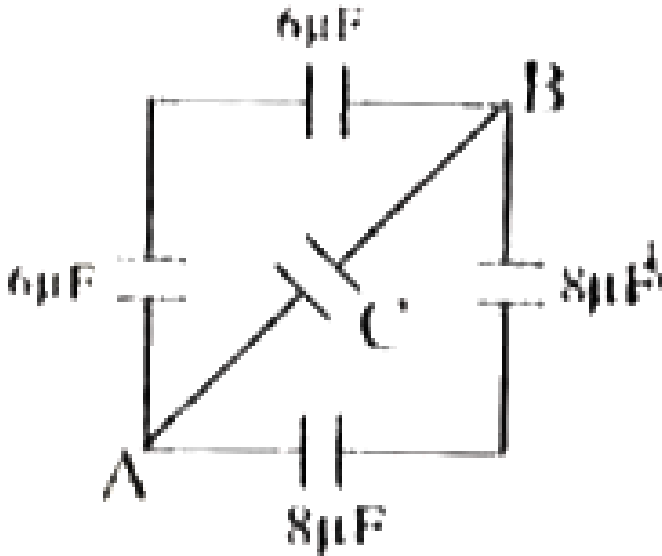2. If the equivalent capacity between A and B in the circuit is  $12\mu F$ , the capacity C is



A.  $5\mu F$

B.  $3\mu F$

C.  $4\mu F$


D.  $8\mu F$

Answer: A



Watch Video Solution

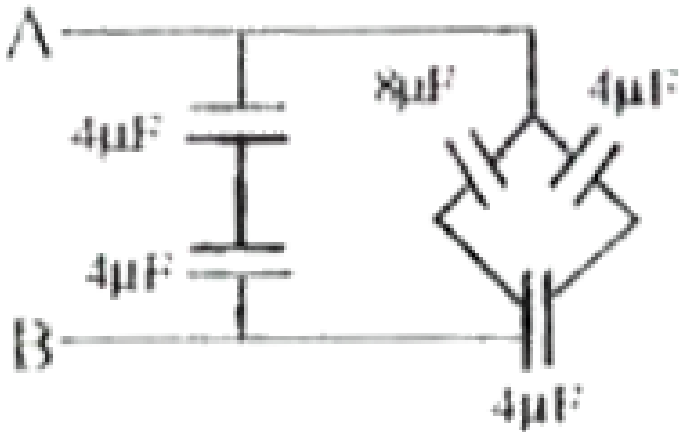3. The net capacity across AB in \_\_\_\_  $\mu F$



A.  $8\mu F$

B.  $6\mu F$


C.  $2\mu F$

D.  $4\mu F$

**Answer: A**

 [Watch Video Solution](#)

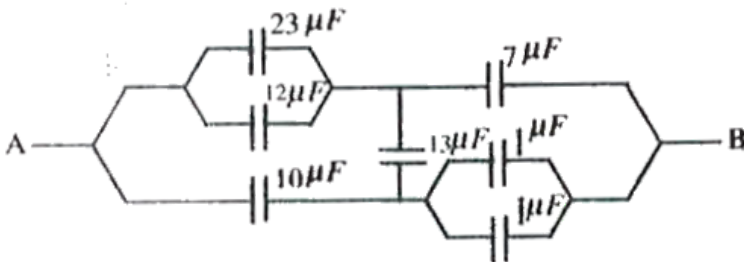4. Find the equivalent capacitance across A & B



A.  $\frac{28}{3}mF$

B.  $\frac{15}{2}mF$

C.  $15mF$


D. none

**Answer: B**





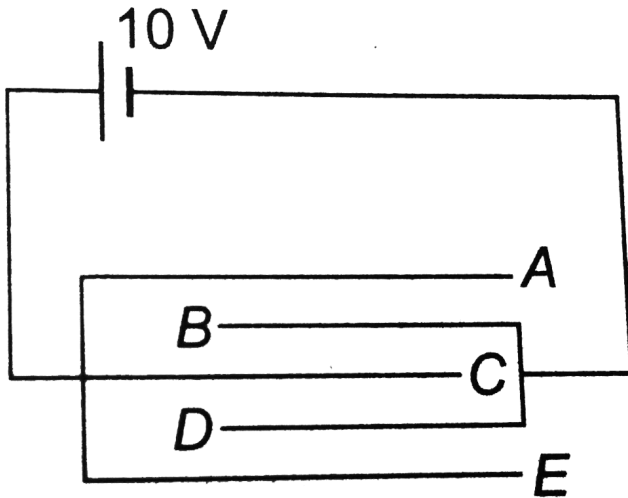5. Five identical capacitor plates are arranged such that they make four capacitors each of  $2\mu F$ . The plates are connected to a source of emf  $10V$ . The charge on plate  $C$  is



- A.  $+20\mu C$
- B.  $+40\mu C$
- C.  $+60\mu C$
- D.  $+80\mu C$

**Answer: B**



[Watch Video Solution](#)

## Lecture Sheet Exercise I Level II Advanced Straight Objective Type Questions

1. Find the capacitance of a system of two identical metal balls of radius  $a$ . if the distance between their centres is equal to  $b$ , with  $b > 2a$

The system is located in a uniform dielectric with relative permittivity  $\epsilon$

A.  $C = \pi\epsilon_0\epsilon a$

B.  $C = 5\pi\epsilon_0\epsilon a$

C.  $C = 2\pi\epsilon_0\epsilon a$

D.  $C = 2\pi\epsilon_0\epsilon / a$

**Answer: C**



[Watch Video Solution](#)

2. Two long straight wires with equal cross-sectional radii  $a$  are located parallel to each other in air. The distance between their axes equal  $b$ . Find the mutual capacitance of the wires per unit length under the condition  $b \gg a$ .

A.  $C \approx \pi \epsilon_0 / \ln(b/a)$

B.  $C \approx \frac{\pi \epsilon_0}{\ln(a/b)}$

C.  $C \approx \pi / \epsilon_0 \ln(b/a)$

D.  $C \approx \pi \epsilon_0 \ln(ba)$


**Answer: A**



**Watch Video Solution**

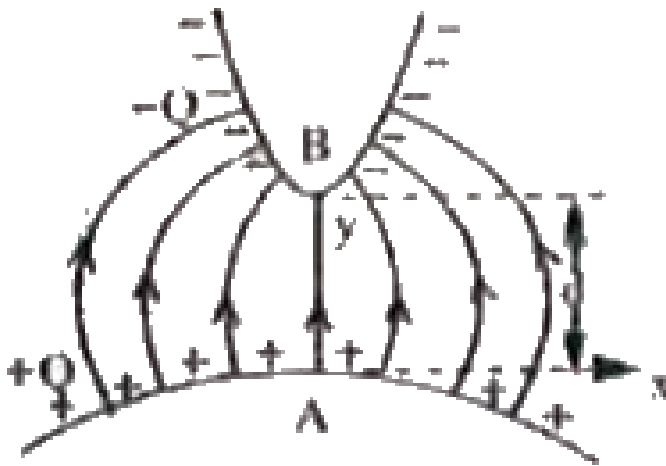3. Two conductors carrying equal and opposite charges create a non-uniform field as shown in fig. What is the capacity of this capacity if the

field along Y-axis varies as  $E = \frac{Q}{\epsilon_0 A} [1 + By^2]$  with B = constant



A. A)  $C = \frac{\epsilon_0 A}{d}$

B. B)  $C = \frac{\epsilon_0 A}{d \left[ 1 + \frac{1}{3} B d^2 \right]}$

C. C)  $C = \frac{\epsilon_0 A B}{2d}$

D. D)  $C = \frac{\epsilon_0 A}{d \left[ 1 + \frac{1}{2} B d^2 \right]}$


**Answer: B**



**Watch Video Solution**

4. A capacitor is made of a flat plate of area  $A$  and B second plate having a stair-like structure as shown in. The area of each stair is  $A/3$ , and the height is

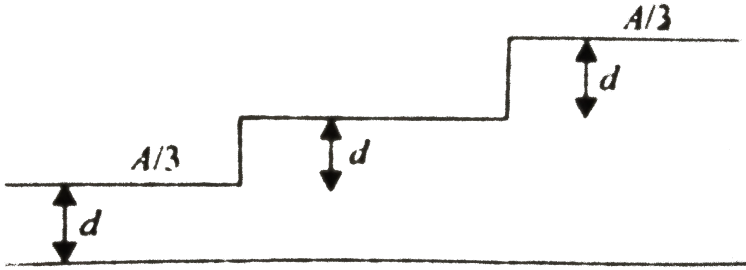d. Find the capacitance of this arrangement.




- A.  $\frac{\epsilon_0 A (3d^2 + 6bd + 2b^2)}{3d(d+b)(d+2b)}$
- B.  $\frac{\epsilon_0 A (3d^2 - 6bd - 2b^2)}{3d(d-b)(d-2b)}$
- C.  $\frac{\epsilon_0 A (2d^2 - bd - 2b^2)}{3d(d+b)(d+2b)}$
- D.  $\frac{\epsilon_0 A (d^2 - bd - b^2)}{3d(d+b)(d+b)}$

Answer: A



Watch Video Solution

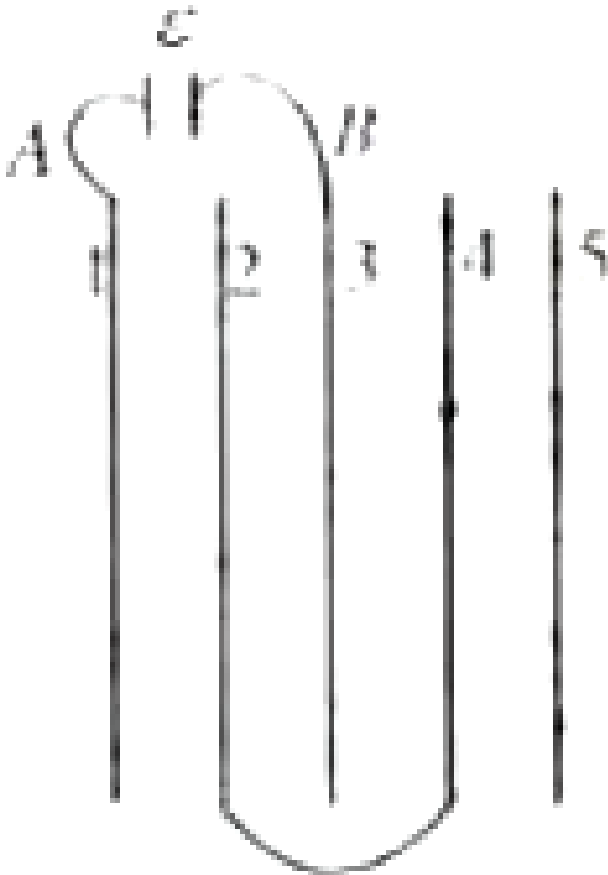5. Five conducting parallel plates having area  $A$  and separation between them  $d$ , are placed as shown in the fig. Plate number 2 and 4 are connected with a conducting wire and between point A and B a cell of emf.  $\epsilon$  is connected. The charge flows through the cell is



A.  $\frac{3}{4} \frac{\epsilon_0 A \epsilon}{d}$

B.  $\frac{2}{3} \frac{\epsilon_0 A \epsilon}{d}$


C.  $\frac{4\epsilon_0 A \epsilon}{d}$

D.  $\frac{\epsilon_0 A \epsilon}{2d}$

Answer: B

 Watch Video Solution

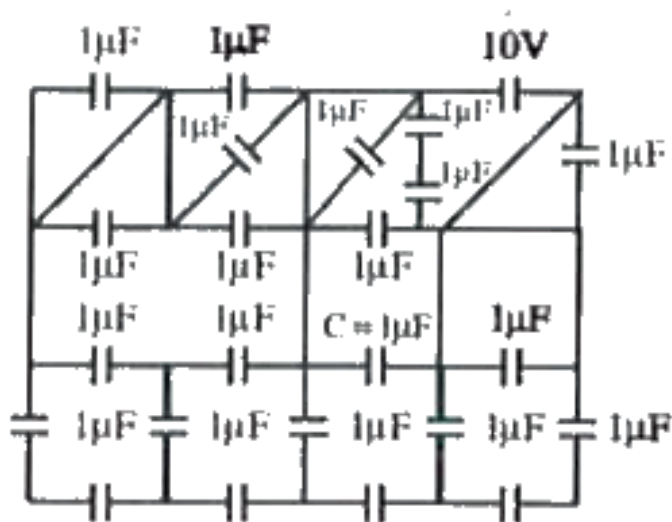6. Find the change on the capacity  $C = 1\mu F$  in the circuit shown in the figure .



A.  $10\mu C$

B.  $13\mu C$

C.  $12\mu C$

D.  $24\mu C$

**Answer: A**



[Watch Video Solution](#)

## Lecture Sheet Exercise I Level II Advanced Matrix Matching Type Questions

1. Six identical capacitors of each capacitance  $C_0$  are arranged as shown in fig .In column-I, equivalent capacitance between two selected points is defined . Match them for their value given in Column-II




COLUMN - I COLUMN - II

A)  $C_{AB}$  p)  $2C_0$

B)  $C_{AC}$  q)  $\frac{3}{2}C_0$

C)  $C_{OA}$  r)  $\frac{5}{3}C_0$


D)  $C_{OB}$  s)  $\frac{4}{3}C_0$

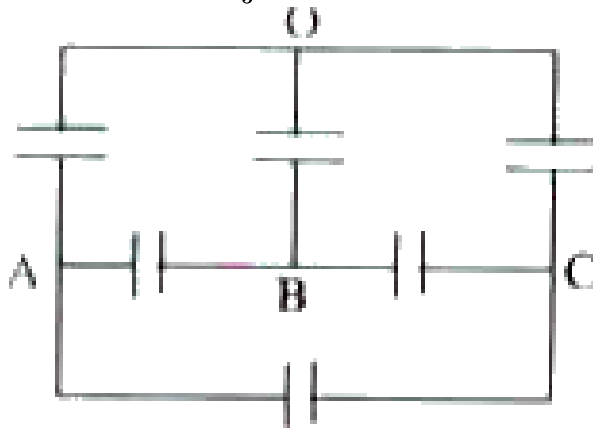

[▶ Watch Video Solution](#)

2. Five identical conducting plates 1,2,3,4 and 5 are fixed parallel to and equidistant from each other as shown in figure. Plate 2 and 5 are connected by a conductor while 1 and 3 are joined by another conductor. The junction of 1 and 3 and the plate 4 are connected to a source of constant emf  $V_0$ .

Match the following :

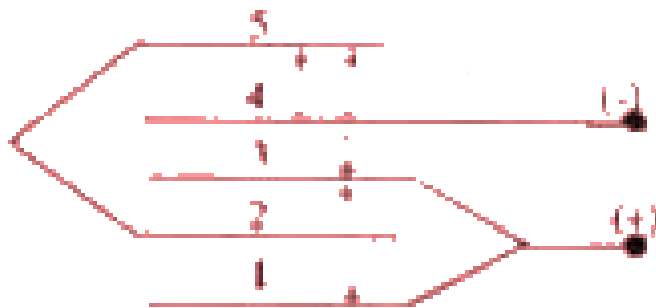

**COLUMN - I**

- A) Charge on plate - 3
- B) Charge on plate - 5
- C) Charge on plate - 1
- D) Charge on plate - 4

**COLUMN - II**


- p)  $+\frac{CV_0}{3}$
- q)  $\frac{2\epsilon_0 AV_0}{3d}$
- r)  $-\frac{5\epsilon_0 AV_0}{3d}$
- s)  $\frac{4\epsilon_0 AV_0}{3d}$

[▶ Watch Video Solution](#)

**Lecture Sheet Exercise I Level II Advanced Integer Type Questions**

1. Six identical capacitors of each capacitance  $.C.$  are arranged as shown in fig .The equivalent capacitance between A and B is  $\frac{KC}{8}$  . The value of  $.K.$


is .....

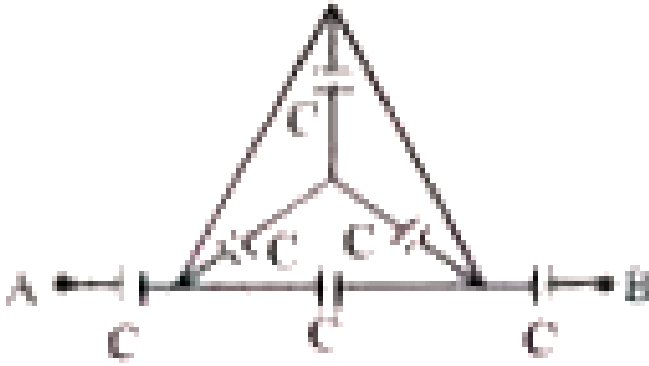

[▶ Watch Video Solution](#)

### Lecture Sheet Exercise II Level I Main Straight Objective Type Questions

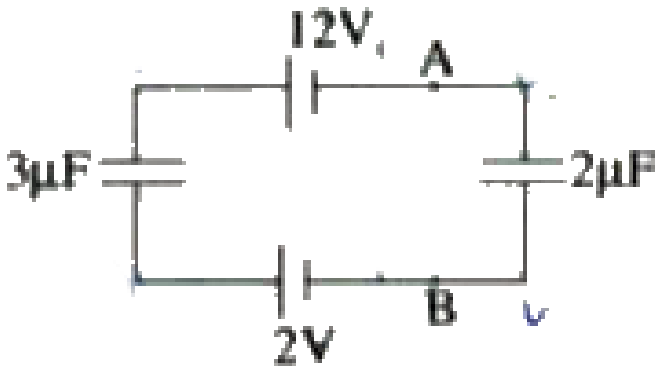1. The P.D in volts between the points A and B is



A. 6V

B. 4V


C. 8V

D. 10V

Answer: A

 Watch Video Solution

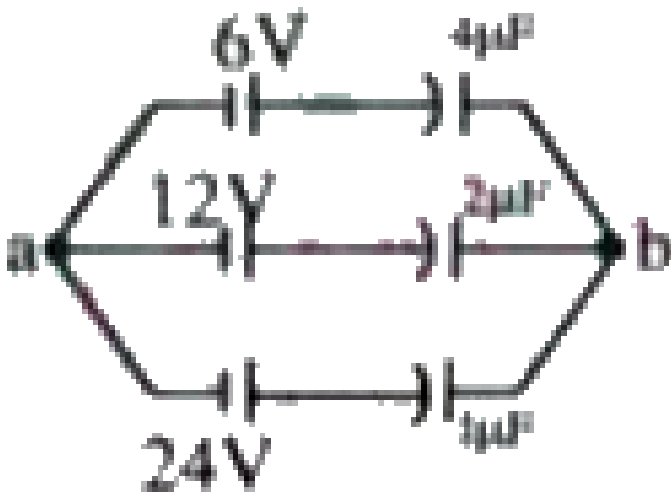2. Find the potential difference  $V_a - V_b$ , between the points a and b shown in each part of the figure.



A.  $-5.2V$

B.  $-6.3V$

C.  $-10.3V$

D.  $-12.5V$


**Answer: C**



**Watch Video Solution**

3. In the circuit, all capacitors are identical, each of capacity  $2\mu F$  and they are infinite in number. If AB is connected to a battery of 10V then the

charge drawn from the battery is :

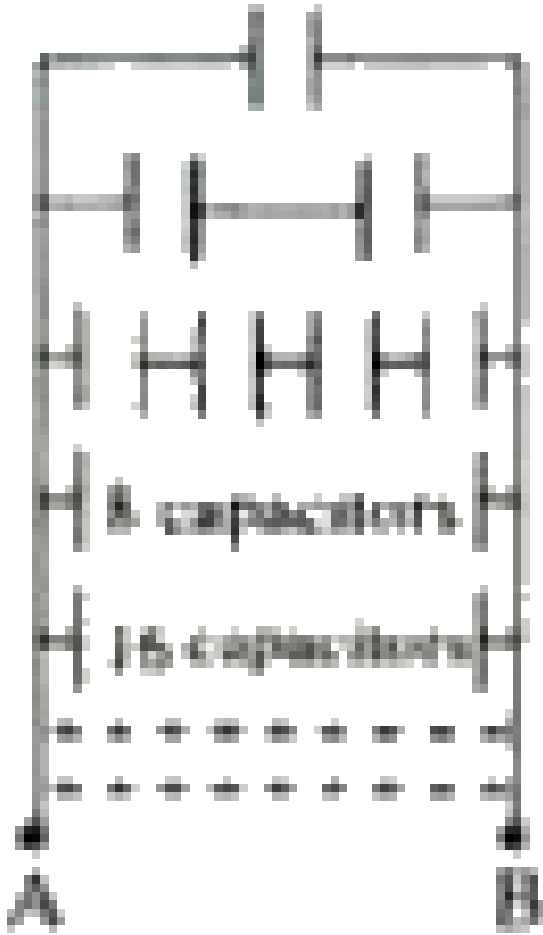

A.  $40\mu C$

B.  $20\mu C$

C.  $10\mu C$

D.  $5\mu C$

**Answer: A**



**Watch Video Solution**

4. Three capacitors with capacitances of  $1\mu F$ ,  $2\mu F$  and  $3\mu F$  are connected in series. Each capacitor gets punctured, if a potential difference just exceeding 100 volt is applied. If the group is connected across 220 volt circuit then the capacitor most likely to puncture first is

- A. capacitance  $1\mu F$
- B. capacitance  $2\mu F$
- C. capacitance  $3\mu F$
- D. capacitance  $1\mu F$  (or)  $2\mu F$  (or)  $3\mu F$

**Answer: A**



**Watch Video Solution**

5. A parallel plate capacitor of capacity  $C_0$  is charged to a potential  $V_0$ ,  $E_1$  is the energy stored in the capacitor when the battery is disconnected and the plate separation is doubled, and  $E_2$  is the energy stored in the capacitor when the charging battery is kept connected and the separation between the capacitor plates is doubled. find the ratio  $E_1 / E_2$ .

A. 4

B.  $3/2$

C. 2

D.  $1/2$

**Answer: A**



**Watch Video Solution**

6. A capacitor of capacitance  $C_1 = 1\mu F$  withstand a maximum voltage of  $V_1 = 6KV$ , and another capacitor of capacitance  $C_2 = 2\mu F$ , can with



stand a maximum voltage of  $V_2 = 4KV$ . If they are connected in series, what maximum voltage will the system withstand?

A. 2 KV

B. 4 KV

C. 6 KV

D. 9 KV

**Answer: D**



[Watch Video Solution](#)

## Lecture Sheet Exercise II Level I Advanced Straight Objective Type Questions

1. A condenser of  $21\mu F$  is charged to 100V and then discharged through a wire of mass 0.25 gm and specific heat  $0.1 \text{ cal gm}^{-1} \text{ } ^\circ C^{-1}$ . The rise in temperature of the wire is

A.  $0.5^\circ C$

B.  $1^\circ C$

C.  $1.5^\circ C$

D.  $2^\circ C$

**Answer: B**



[Watch Video Solution](#)

2. When a number of liquid drops each of surface charge density  $\sigma$  and energy  $E$  combine, a large drop is formed. If the charge density of the large drop is  $3\sigma$ , its energy is

A.  $81E$


B.  $3E$

C.  $27E$

D.  $243 E$

**Answer: D**

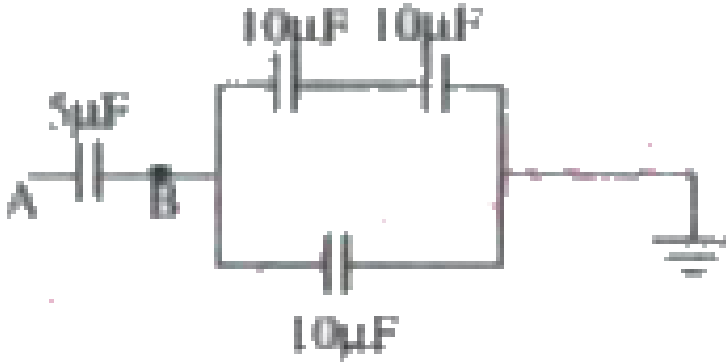3. If the potential at A is 2000V the potential at B is



A. 1500V


B. 1000V

C. 500V

D. 400V

**Answer: C**

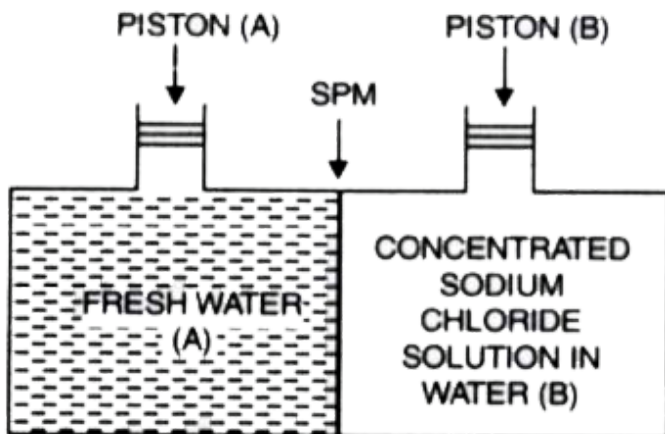1. Consider the Fig. and make the correct option.




- A. Both the  $4\mu F$  capacitors carry equal charges in opposite sense.
- B. Both the  $4\mu F$  capacitors carry equal charges in same sense.
- C.  $V_B - V_D > 0$
- D.  $V_D - V_B > 0$

Answer: B::C



Watch Video Solution

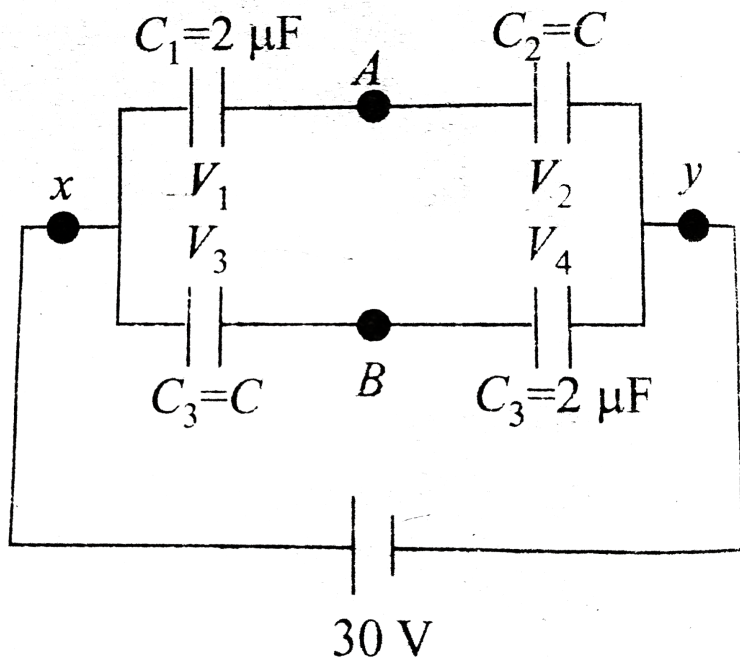1. The given circuit shows an arrangement of four capacitors. A potential difference  $30V$  is applied across the combination. It is observed that potentials at connected between  $A$  and  $B$  differ by  $5V$ . Also if a conducting wire is connected between  $A$  and  $B$ , electrons will flow from  $A$  to  $B$ . Of course, we have not actually connected any wire between  $A$  and  $B$ , we have described only an if situation. Answer the following question.




Potential difference across  $C_4$  is.

- A. 12.5 V
- B. 15.5 V
- C. 17.5 V
- D. 22.5 V

**Answer: C**

[Watch Video Solution](#)

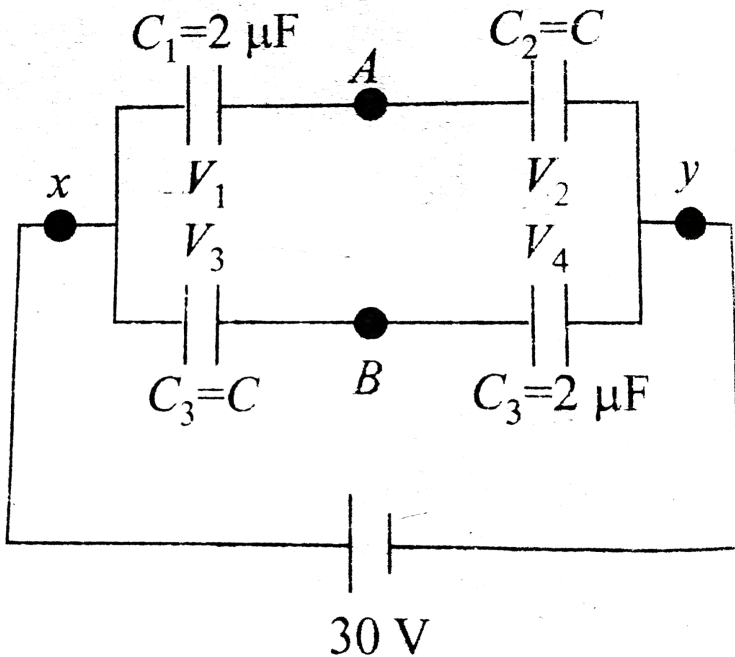2. The given circuit shows an arrangement of four capacitors. A potential difference  $30V$  is applied across the combination. It is observed that potentials at connected between  $A$  and  $B$  differ by  $5V$ . Also if a conducting wire is connected between  $A$  and  $B$ , electrons will flow from  $A$  to  $B$ . Of course, we have not actually connected any wire between  $A$  and  $B$ , we have described only an if situation. Answer the following question.



Equivalent capacitor between  $X$  and  $Y$  is.

A.  $2.34 \mu F$

B.  $1.54\mu F$

C.  $1.22\mu F$

D.  $0.77\mu F$


**Answer: A**



**Watch Video Solution**

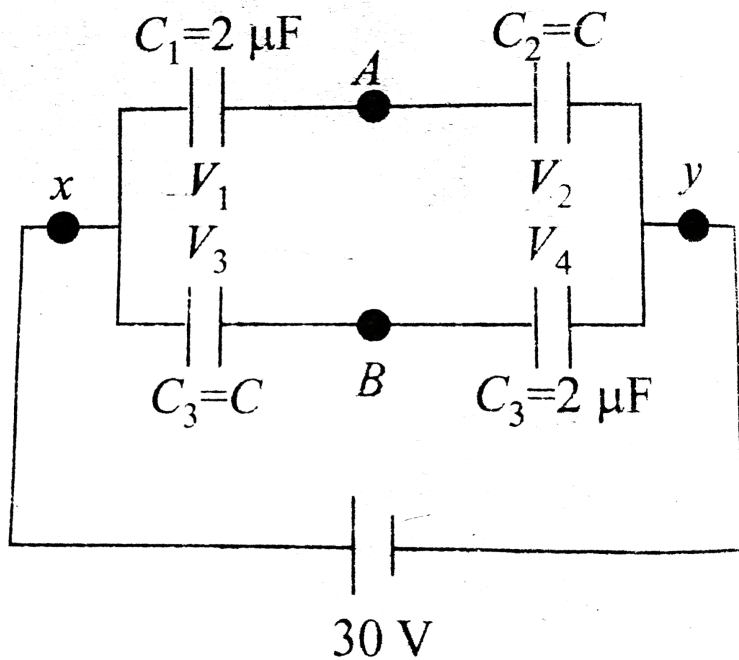3. The given circuit shows an arrangement of four capacitors. A potential difference  $30V$  is applied across the combination. It is observed that potentials at connected between  $A$  and  $B$  differ by  $5V$ . Also if a conducting wire is connected between  $A$  and  $B$ , electrons will flow from  $A$  to  $B$ . Of course, we have not actually connected any wire between  $A$  and  $B$ , we have described only an if situation. Answer the following question.





Equivalent capacitor between  $X$  and  $Y$  is.


- A.  $60 \mu\text{C}$
- B.  $52 \mu\text{C}$
- C.  $42 \mu\text{C}$
- D.  $35 \mu\text{C}$

Answer: D

[Watch Video Solution](#)

4. The figure shows a diagonal symmetric arrangement of capacitors and a battery.

Identify the correct statements

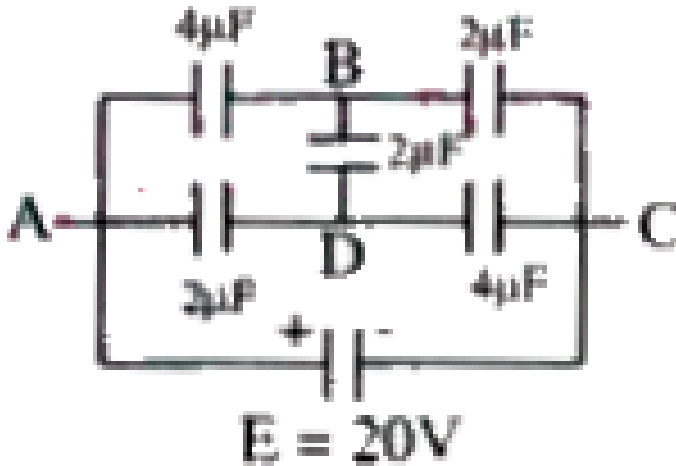


- A. Both the  $4\mu F$  capacitors carry equal charges in opposite sense
- B. Both the  $4\mu F$  capacitors carry equal charges in same sense
- C.  $V_B - V_D < 0$
- D.  $V_D - V_B > 0$

Answer: B::C::D



Watch Video Solution

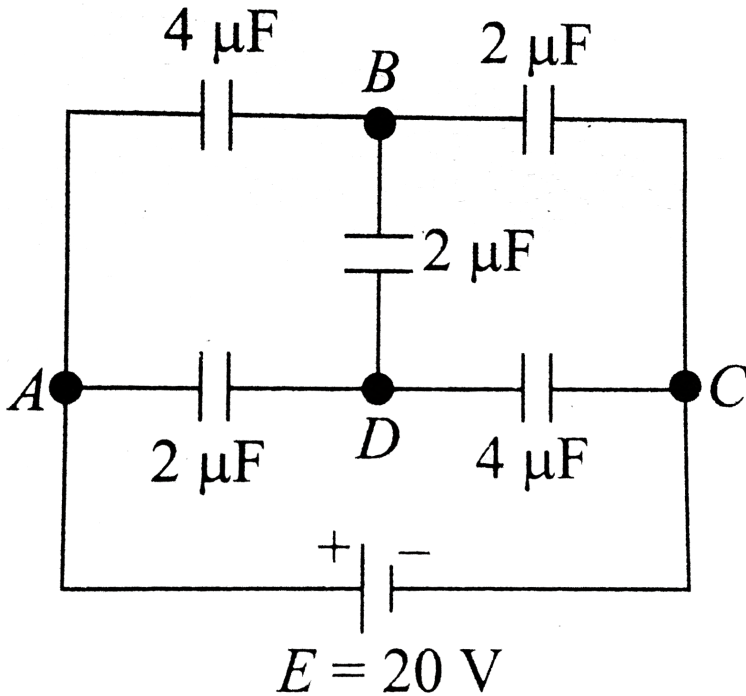5. Shows a diagonal symmetric arrangement of capacitors and a battery.




If the potential of  $C$  is zero, then identify the incorrect statement.

- A.  $V_A = +20\text{V}$
- B.  $4(V_A - V_B) + 2(V_D - V_B) = 2V_B$
- C.  $2(V_A - V_D) + 2(V_B - V_D) = 4V_D$
- D.  $V_A = V_B + V_D$

Answer: A::B::C::D

 Watch Video Solution

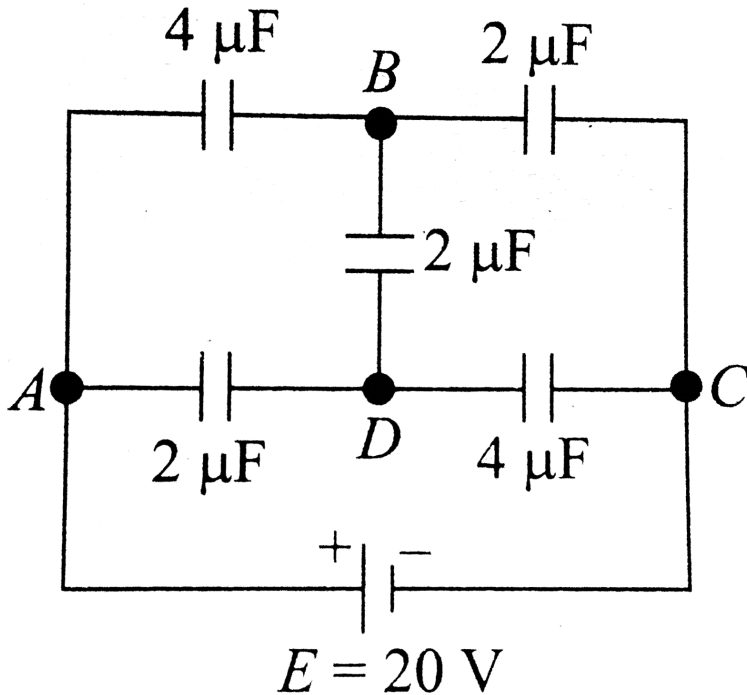6. Shows a diagonal symmetric arrangement of capacitors and a battery.



If the potential of  $C$  is zero, then identify the incorrect statement.

A.  $V_B = 8\text{ V}$

B.  $V_B = 12\text{ V}$

C.  $V_D = 8V$


D.  $V_D = 12V$

**Answer: B::C**



**Watch Video Solution**

7. Name the process shown in the figure.

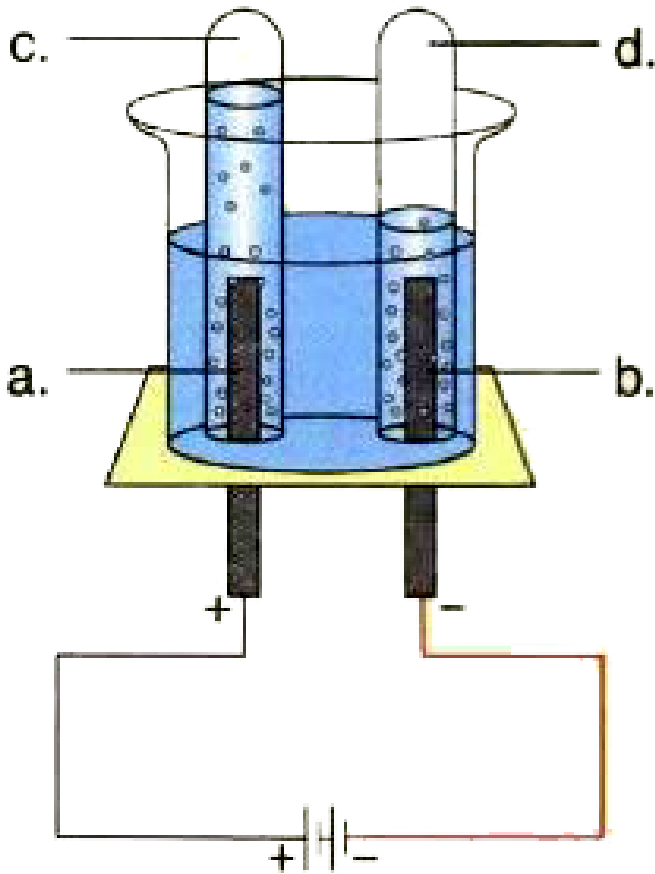

A.  $q_1 = 32\mu C, q_2 = 24\mu C, q_3 = - 8\mu C$

B.  $q_1 = 48\mu C, q_2 = 16\mu C, q_3 = + 8\mu C$

C.  $q_1 = 32\mu C, q_2 = 24\mu C, q_3 = + 8\mu C$

D.  $VA=+15V$

Answer: C



Watch Video Solution

## Lecture Sheet Exercise Ii Level I Advanced Integer Type Questions

1. In the circuit shown in the figure, the potential difference across the  $4.5\mu F$  capacitor is




Watch Video Solution

## Lecture Sheet Exercise Iii Level I Main Straight Objective Type Questions

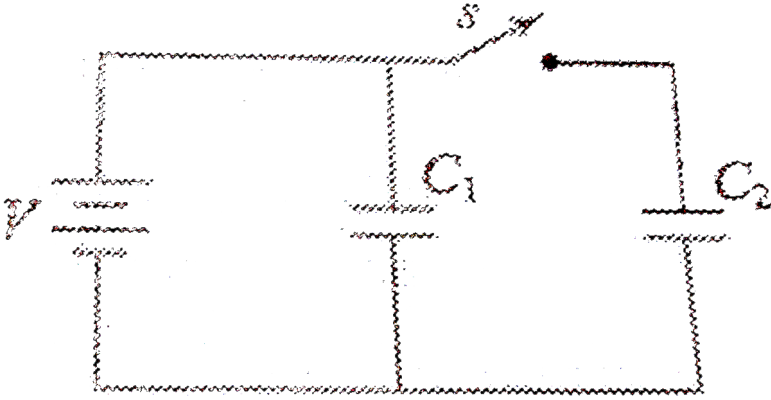1. Two capacitors of equal capacitance ( $C_1 = C_2$ ) are as shown in the figure. Initially, while the switch is open (as shown) one of the capacitors is uncharged and the other carries charge  $Q_0$ . The energy stored in the charged capacitor is  $U_0$ . Sometime after the switch is closed, the

capacitors  $C_1$  and  $C_2$  carry charges  $Q_1$  and  $Q_2$  respectively, the energy stored in the capacitors are  $U_1$  and  $U_2$  respectively. Which of the following expression is correct?



A.  $Q_0 = \frac{1}{2}(Q_1 + Q_2)$

B.  $Q_1 = Q_2$

C.  $V_1 = V_2$

D.  $U_0 = U_1 + U_2$


**Answer: D**



**Watch Video Solution**



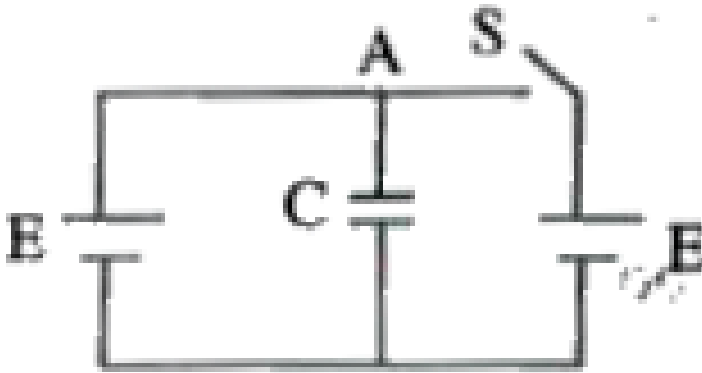2. Initially the circuit is in steady state. When the switch S is closed, the heat generated in the circuit will be




- A.  $\frac{\epsilon^2 C}{2}$
- B.  $2\epsilon^2 C$
- C.  $\frac{3\epsilon^2 C}{2}$
- D. Zero

**Answer: D**

[▶ Watch Video Solution](#)

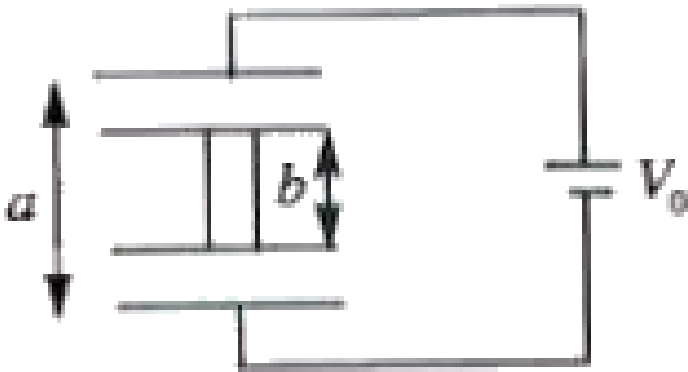3. Figure shows two capacitors in series. The rigid center section of length  $b$  is movable. The area of each plate is  $S$ . If the voltage difference between the plates is maintained constant at  $V_0$  The change in stored energy if the center section is removed is



- A.  $\frac{S\epsilon_0 V_0^2 a}{2b(a-b)}$   
 B.  $\frac{S\epsilon_0 V_0^2 b}{2a(a-b)}$   
 C.  $\frac{S\epsilon_0 V_0^2 b}{a(a-b)}$   
 D.  $\frac{S\epsilon_0 V_0^2 b}{b(a-b)}$

**Answer: B**



**Watch Video Solution**

Lecture Sheet Exercise Iii Level Ii Advanced More Than One Correct Answer  
Type Questions

1. Two capacitors of  $2\mu F$  and  $3\mu F$  are charged to 150 V and 120 V respectively. The plates of capacitor are connected as shown in the figure. A discharged capacitor of capacity  $1.5\mu F$  falls to the free ends of the wire. Then,



- A. charge on the  $1.5\mu F$  capacitors is  $180\mu F$
- B. charge on the  $2\mu F$  capacitor is  $120\mu C$
- C. charge flows through A from right to left.
- D. charge flows through A from left to right.

Answer: A::B::C

 [Watch Video Solution](#)

2. A parallel plate capacitor is charged and then the battery is disconnected. When the plates of the capacitor are brought closer, then


- A. Charge from the battery flows into the capacitor after reconnection
- B. Charge from capacitor flows into the battery after reconnection.
- C. The potential difference between the plates increases when the plates are pulled apart.
- D. After reconnection of battery potential difference between the plate will immediately becomes half of the initial potential difference. (Just after disconnecting the battery)

**Answer: B::C**



[Watch Video Solution](#)

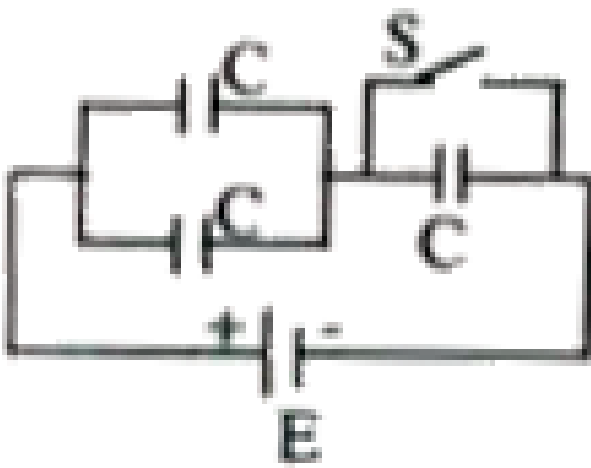3. In the circuit shown, each capacitor has a capacitance  $C$ . The emf of the cell is  $E$ . If the switch  $S$  is closed



- A. positive charge will flow out of the positive terminal of the cell
- B. positive charge will enter the positive terminal of the cell
- C. the amount of charge flowing through the cell will be  $CE$ .
- D. the amount of charge flowing through the cell will be  $\frac{4}{3} CE$ .

**Answer: A:D**

 [Watch Video Solution](#)

4. Two identical capacitors are charged to different potentials  $\varphi_1$  and  $\varphi_2$  relative to the negative earthed electrodes. The capacitors are then connected in parallel (Fig. 24.21). Find the potential of the battery after the connection was made and the change in the energy of the system.

A. net charge on connected plates is less than the sum of initial individual charges.

B. net charge on connected plates equals the sum of initial charges.

C. the net potential difference across them is different from the sum of the individual initial potential differences.

D. the net energy stored in the two capacitors is less than the sum of the initial individual energies.

**Answer: A::C::D**




**Watch Video Solution**

Lecture Sheet Exercise iii Level ii Advanced Linked Comprehension Type  
Questions Passage

1. (i) In an isolated system (neither connected to the terminal of a battery nor to any other source of charge e.g each) net charge remains constant.

(ii) From two terminal of a battery or from two plates of a capacitor equal and opposite charges enter or leave.

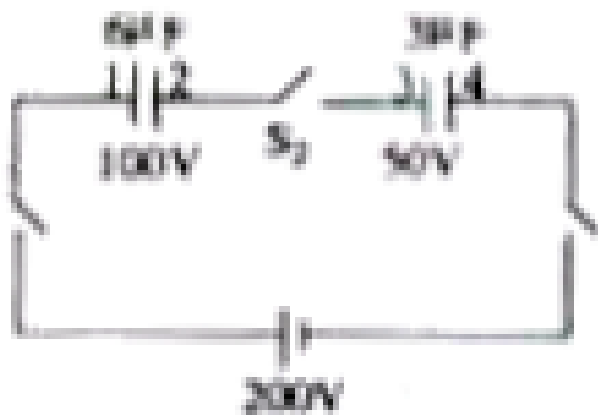Question : Two capacitors of capacity  $6\mu F$  and  $3\mu F$  are charged to 100 V and 50 V separately and connected as shown. Now all the three switches  $S_1$ ,  $S_2$  and  $S_3$  are closed.



Which plate (s) form an isolated system .

A. plate 1 and plate 4 separately

B. plate 1 and 4 jointly

C. plates 1 and 3 jointly

D. plates 2 and 3 jointly

**Answer: D**



**Watch Video Solution**

2. Two capacitors of capacity  $6$  and  $3\mu F$  are charged to  $100$  V and  $50$  V separately and connected as shown. Now all the three switches  $S_1$ ,  $S_2$  and  $S_3$  are closed.



Charges on both the capacitors in steady state will be (on  $6\mu F$  first)

A.  $400\mu C$ ,  $400\mu C$

B.  $700\mu C$ ,  $250\mu C$

C.  $800\mu C$ ,  $350\mu C$

D.  $300\mu C$ ,  $350\mu C$




Answer: B

 Watch Video Solution

3. (i) In an isolated system (neither connected to the terminal of a battery nor to any other source of charge e.g each) net charge remains constant.

(ii) From two terminal of a battery or from two plates of a capacitor equal and opposite charges enter or leave.

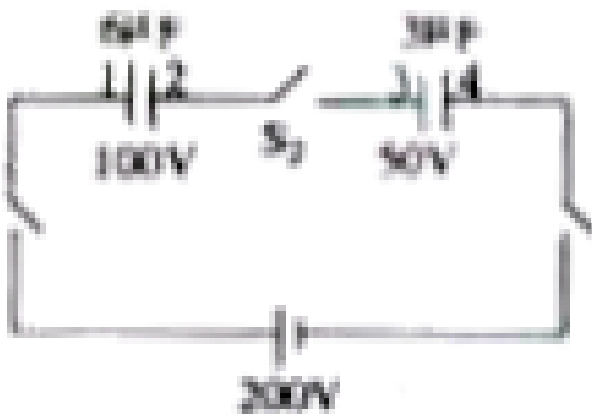Question : Two capacitors of capacity  $6\mu F$  and  $3\mu F$  are charged to 100 V and 50 V separately and connected as shown. Now all the three switches  $S_1$ ,  $S_2$  and  $S_3$  are closed.



Which plate (s) form an isolated system .

A.  $q_1 = q_3$  and  $q_2 = 0$

B.  $q_1 = q_3 = \frac{q_2}{2}$

C.  $q_1 = q_3 = 2q_2$


D.  $q_1 = q_2 = q_3$

**Answer: D**



**Watch Video Solution**

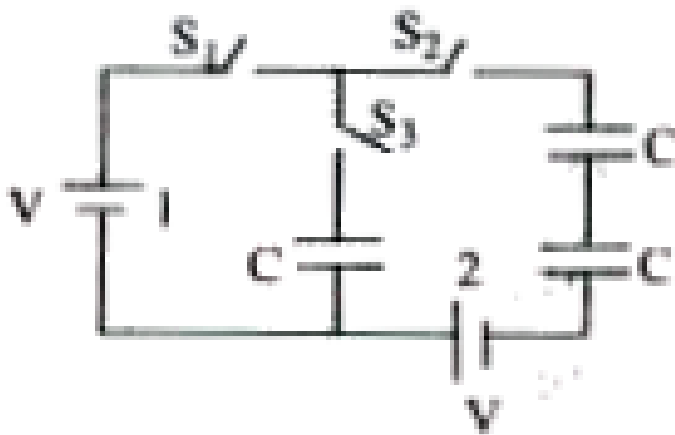4. Three identical capacitors and two identical batteries of negligible internal resistance are connected as shown in figure. Neglect the resistance of the wires and all the three switches are initially open. There is no charge on any capacitor initially




In the above situation, what is work done by battery 2 due to closing of switch  $S_1$  ?

- A.  $CV^2$
- B.  $\frac{2}{3}CV^2$
- C.  $\frac{4}{3}CV^2$
- D.  $2CV^2$

**Answer: D**

[▶ Watch Video Solution](#)

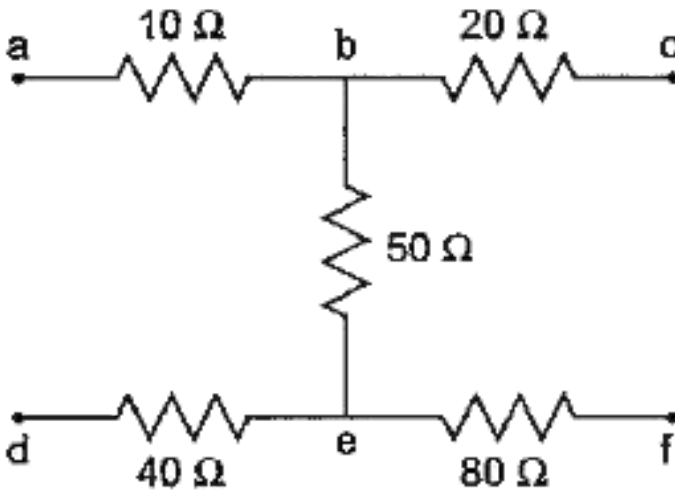5. The equivalent resistance between points a and f of the network shown in figure below is



A. Zero

B.  $-\frac{2}{3}CV^2$

C.  $\frac{2}{3}CV$

D.  $\frac{CV^2}{3}$

**Answer: C**



**Watch Video Solution**

1. A capacitor of capacitance  $C$  is initially charged to a potential difference of  $V$ . Now it is connected to a battery of  $2V$  with opposite polarity. The ratio of heat generated to the final energy stored in the capacitor will be

 [Watch Video Solution](#)

2. A parallel plate capacitor of capacity  $C_0$  is charged to a potential  $V_0$ ,  $E_1$  is the energy stored in the capacitor when the battery is disconnected and the plate separation is doubled, and  $E_2$  is the energy stored in the capacitor when the charging battery is kept connected and the separation between the capacitor plates is halved. find the ratio  $E_1 / E_2$ .

 [Watch Video Solution](#)

3. Calculate the amount of energy consumed in carrying a charge of 1 coulomb through a battery of 3 V.



[Watch Video Solution](#)

## Lecture Sheet Exercise Iv Level I Main Straight Objective Type Questions

1. A parallel -plate capacitor having plate area  $400\text{cm}^2$  and separation between the plate 1.0mm is connected to a power supply of 100V. A dielectric slab of thickness 1.0mm and dielectric constant 5.0 is inserted into the gap .(a)Find the increase in electrostatic energy .(b) If the power supply is now disconnected and the dielectric slab is taken out , find the further increase in energy. (c) Why does the energy increase in inserting the slab as well as in taking it out?

A.  $5.1\mu\text{J}$

B.  $1.1\mu\text{J}$

C.  $7.1\mu\text{J}$


D.  $9.1\mu J$

Answer: C




Watch Video Solution

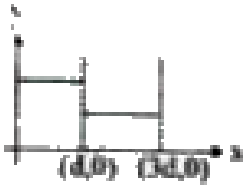
2. A parallel plate capacitor has two layers of dielectrics as shown in figure. This capacitor is connected across a battery, then the ratio of potential difference across the dielectric layers is




A.

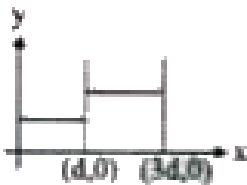

B.

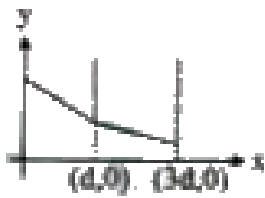

C.

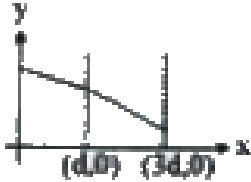

D.

Answer: A

[▶ Watch Video Solution](#)

3. Calculate the capacitance of a parallel plate condenser, with plate area  $A$  and distance between plates  $d$ , when filled with a dielectric whose dielectric constant varies as,

$$K(x) = 1 + \frac{\beta x}{\epsilon_0} \quad 0 < x < \frac{d}{2}, \quad K(x) = 1 + \frac{\beta}{\epsilon_0}(d - x) \quad \frac{d}{2} < x < d$$

For what value of  $\beta$  would the capacity of the condenser be twice that when it is without any dielectric?



- A.  $\frac{\beta \frac{A}{2}}{\log_e \left( \frac{\epsilon_0}{\frac{\beta d}{2}} \right)}$
- B.  $\frac{A}{2} \log_e \left( \frac{\epsilon_0}{\frac{\beta d}{2}} \right)$
- C.  $\frac{A}{2} \log_e \left( \frac{\epsilon_0}{\epsilon_0 - \frac{\beta d}{2}} \right)$
- D.  $\frac{\beta \frac{A}{2} \epsilon_0}{\log_e \left( \frac{\epsilon_0 + \frac{\beta d}{2}}{\epsilon_0} \right)}$

Answer: D

[Watch Video Solution](#)

4. A capacitor has square plates each of side  $a$ , making an angle small  $\theta$ , the capacitance is given by:



$$\text{A. } C = \frac{\epsilon_0 a^2}{d} \left[ 1 - \frac{\theta a}{2d} \right]$$

$$\text{B. } C = \frac{\epsilon_0 a^2}{d} \left[ 1 - \frac{\theta a}{d} \right]$$


$$\text{C. } C = \frac{\epsilon_0 a}{d^2} \left[ 1 - \frac{\theta a}{d} \right]$$

$$\text{D. } C = \frac{\epsilon_0 a^2}{d}$$

**Answer: A**

 [Watch Video Solution](#)

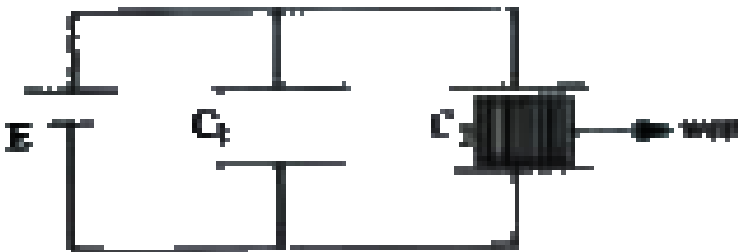5. When capacitors are fully charged, an external agent removes the dielectric slab from the capacitor  $C_2$ . Find the change in potential energy of capacitor  $C_1$  ( $E = 10V$ ,  $C_1 = 2\mu F$ ,  $C_2 = 4\mu F$  and  $k = 2$ )



A. 0J

B. 1J

C. 5J


D. 10J

**Answer: A**



[Watch Video Solution](#)

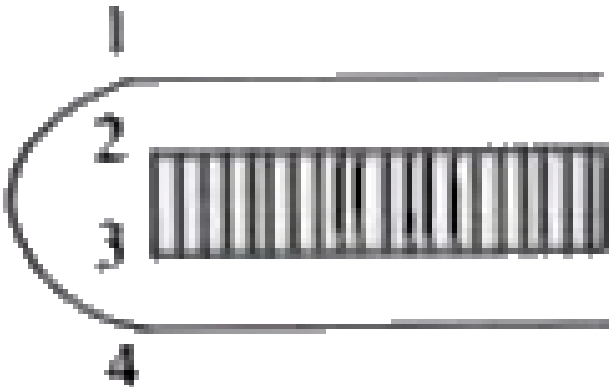6. Four identical plates 1, 2, 3 and 4 are placed parallel to each other at equal distance as shown in the figure. Plates 1 and 4 are joined together and the space between 2 and 3 is filled with a dielectric of dielectric constant  $k = 2$ . The capacitance of the system between 1 and 3 & 2 and 4 are  $C_1$  and  $C_2$  respectively. The ratio  $\frac{C_1}{C_2}$  is



A.  $\frac{5}{3}$

B. 1


C.  $\frac{3}{5}$

D.  $\frac{5}{7}$

Answer: B

 Watch Video Solution

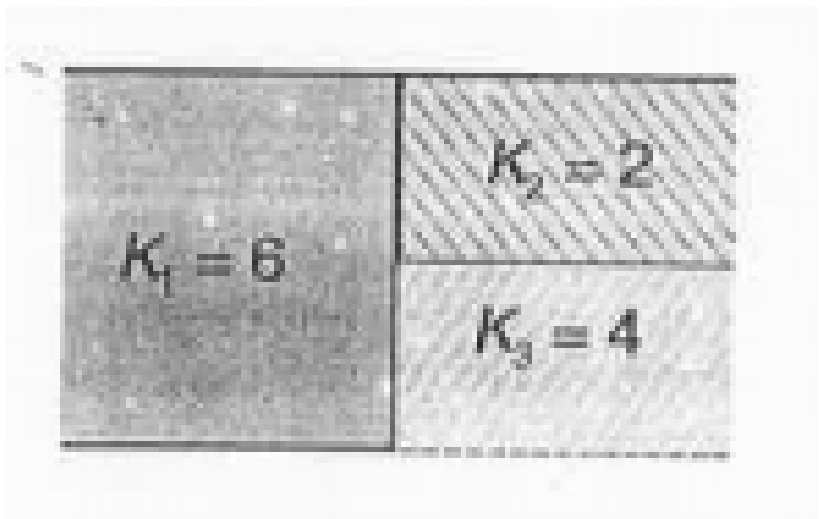7. A parallel plate capacitor of capacitance  $C$  (without dielectric) is filled by dielectric slabs as shown in figure. Then the new capacitance of the



capacitor is

A. 3.9 C

B. 4 C

C. 2.4 C

D. 3 C

**Answer: A**



[Watch Video Solution](#)

8. Figure shows two parallel plate capacitors with fixed plates and connected to two batteriers. The separation between the plates is the same for the two capacitors. The plates are rectangular in shape with width  $b$  and lengths  $l_1$  and  $l_2$ . The left half of the dielectric slab has a dielectric constant  $K_1$  and the right half  $K_2$  Neglecting any friction, find the ratio of the emf of the left battery to that of the right battery for

which the dielectric slab may remain in equilibrium



A.  $\sqrt{\frac{K_2 - 1}{K_1 - 1}}$

B.  $\sqrt{\frac{K_1 - 1}{K_2 - 1}}$

C.  $\sqrt{\frac{K_1 + 1}{K_2 + 1}}$


D.  $\sqrt{\frac{K_2 + 1}{K_1 + 1}}$

Answer: A

[Watch Video Solution](#)

Lecture Sheet Exercise Iv Level Ii Advanced Straight Objective Type Questions

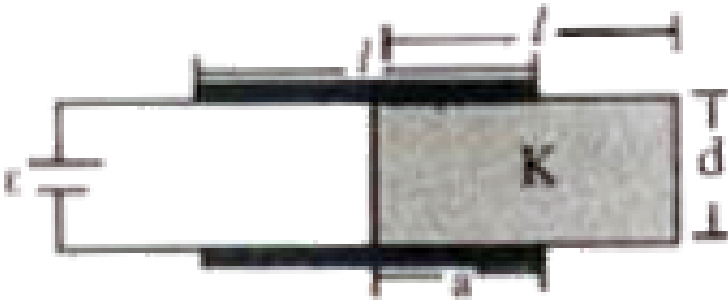1. Consider the situation shown in figure. The plates of the capacitor have plate area  $A$  and are clamped in the laboratory, the dielectric slab is released from rest with a length  $a$  inside the capacitor. Neglecting any effect of friction or gravity . Show that the slab will execute periodic motion and find its time period.



A.  $8\sqrt{\frac{(l-a)lmd}{\epsilon_0 A \epsilon^2 (K-1)}}$

B.  $8\sqrt{\frac{(l-a)lmd}{\epsilon_0 A \epsilon^2 (K+1)}}$

C.  $8\sqrt{\frac{(l+a)lmd}{\epsilon_0 A \epsilon^2 (K+1)}}$


D.  $8\sqrt{\frac{(l+a)md}{\epsilon_0 A \epsilon^2 (K+1)}}$

**Answer: A**



**Watch Video Solution**

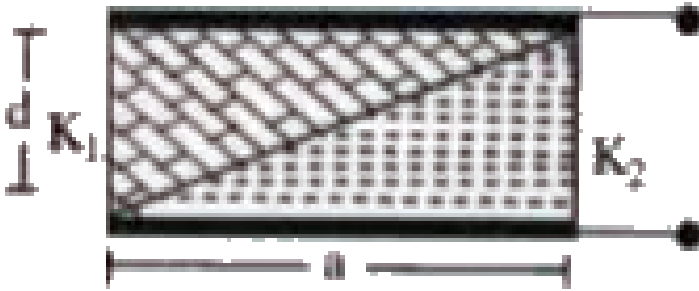2. A capacitor is formed by two square metal-plates of edge  $a$ , separated by a distance  $d$ . Dielectrics of dielectric constants  $K_1$  and  $K_2$  are filled in the gap as shown in fig. Find the capacitance.



- A.  $\frac{\epsilon_0 K_1 K_2 a^2 \ln\left(\frac{K_1}{K_2}\right)}{(K_1 - K_2)d}$
- B.  $\frac{\epsilon_0 (K_1 + K_2) a^2 \ln\left(\frac{K_1}{K_2}\right)}{(K_1 - K_2)d}$
- C.  $\frac{\epsilon_0 (K_1 + K_2) a^2 \ln\left(\frac{K_2}{K_1}\right)}{(K_1 - K_2)d}$
- D.  $\frac{\epsilon_0 K_1 K_2 a^2 \ln\left(\frac{K_2}{K_1}\right)}{(K_1 - K_2)d}$

**Answer: A**



**Watch Video Solution**



3. A parallel plate capacitor of plate area  $a$  and plate separation  $d$  is charged to potential difference  $V$  and then the battery is disconnected. A slab of dielectric constant  $K$  is then inserted between the plates of the capacitor so as to fill the space between the plates. If  $Q, E,$  and  $W$  denote, respectively, the magnitude of charge on each plate, the electric field between the plates (after the slab is inserted) and work done on the system, in question, in the process of inserting the slab, then

A.  $Q = \frac{\epsilon_0 AV}{d}$

B.  $Q = \frac{\epsilon_0 KAV}{d}$

C.  $E = \frac{V/K}{d}$

D.  $W = \frac{\epsilon_0 AV^2}{2d} \left(1 - \frac{1}{K}\right)$

**Answer: A::C::D**



**Watch Video Solution**

4. Assertion: Capacity of a parallel plate capacitor increases when distance between the plates is decreased.

Reason : Capacitance of capacitor is inversely proportional to distance between them.

A.  $\frac{\epsilon_0 A (K_2 - K_1)}{d \ln(K_2 / K_1)}$

B.  $\frac{2\epsilon_0 A (K_2 - K_1)}{d \ln(K_2 - K_1)}$

C.  $\frac{3}{2} \frac{\epsilon_0 A (K_2 - K_1)}{d \ln(K_2 / K_1)}$

D.  $\frac{3}{2} \frac{\epsilon_0 A (K_2 - K_1)}{d \ln(K_2 - K_1)}$

**Answer: A**



**Watch Video Solution**

Lecture Sheet Exercise Iv Level Ii Advanced More Than One Correct Answer  
Type Questions

1. An LR circuit with a battery connected at  $t = 0$ . Which of the following quantities will be zero just after the connection?

A. A are  $25C_0$  and  $25V$

B. A are  $25C_0$  and  $5V$

C. B are  $5C_0$  and  $5V$

D. B are  $5C_0$  and  $25V$

**Answer: B::C**



[Watch Video Solution](#)

2. A parallel plate air-core capacitor is connected across a source of constant potential difference. When a dielectric plate is introduced between the two plates then:

A. some charge from the capacitor will flow back into the source.

B. some extra charge from the source will flow back into the capacitor.

C. the electric field intensity between the two plate does not change.

D. the electric field intensity between the two plates will decrease.

**Answer: B::C**



[Watch Video Solution](#)

3. A parallel plate capacitor has a parallel sheet of copper inserted between and parallel to the two plates, without touching the plates. The capacity of the capacitor after the introduction of the copper sheet is :

A. minimum when the copper sheet touches one of the plates.

B. maximum when the copper sheet touches one of the plates.

C. invariant for all positions of the sheet between the plates.

D. greater than that before introducing the sheet.

**Answer: C::D**



[Watch Video Solution](#)

## Lecture Sheet Exercise Iv Level Ii Advanced Matrix Matching Type Questions

1. In Column some operation performed on capacitor are given, while in Column-II are given some probable effects on capacitor. Match the entries of Column with the entries of Column-II

### COLUMN - I

- A) A dielectric slab is inserted into the capacitor slowly keeping the charge constant
- B) The plates of capacitor are moved apart keeping the charge constant
- C) A dielectric slab is inserted into the capacitor slowly keeping the voltage constant
- D) The plates of capacitor are moved apart keeping the voltage constant

### COLUMN - II

- p) Work done by external agent is negative
- q) Work done by external agent is positive
- r) Electric potential energy stored in the electric field in between the capacitor plates is decreasing
- s) Electric potential energy stored in the electric field in between the capacitor plates is increasing




[Watch Video Solution](#)

## Lecture Sheet Exercise Iv Level Ii Advanced Integer Type Questions

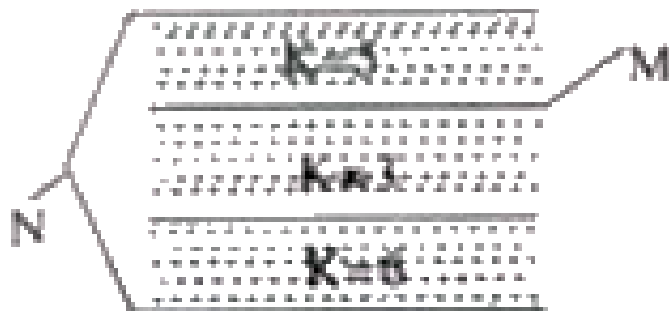1. In the given arrangement of parallel plates area  $A$  and distance between two consecutive plates is  $d$ . Equivalent capacitance of the structure

between MN is  $n$  times of  $\frac{\epsilon_0 A}{d}$  then the value of  $n$  is




[Watch Video Solution](#)

2. A parallel plate capacitor is filled by a dielectric whose relative permittivity varies with the applied voltage ( $U$ ) as  $\epsilon = \alpha U$  where  $\alpha = 2V^{-1}$ . A similar capacitor with no dielectric is charged to  $U_0 = 78V$ . It is then is connected to the uncharged capacitor with the dielectric. Find the final voltage on the capacitors.

[Watch Video Solution](#)

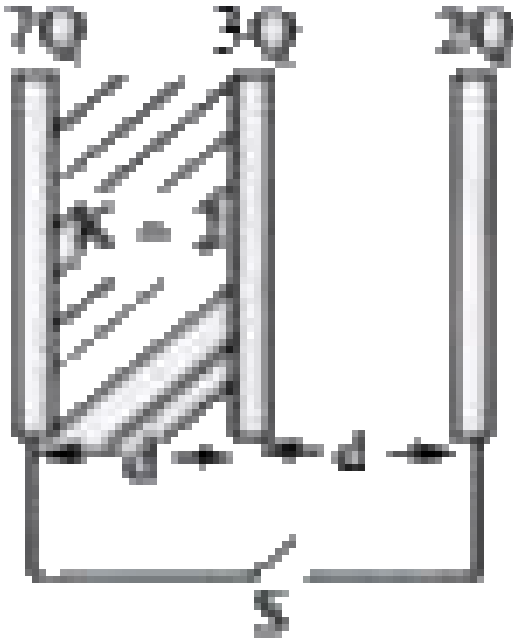
3. Three large identical conducting plates are placed at a distance  $d$  in air. The space between the first two plates is filled completely with dielectric of dielectric constant 2 as shown. The plates are given charges  $7Q, 3Q$  and  $2Q$  respectively. The outer plates are connected by good conducting wire through switch  $S$ . When  $S$  is closed, the charge that flows through switch is  $nQ$ . Find the value of  $n$ ?



[▶ Watch Video Solution](#)

## Lecture Sheet Exercise V Level I Main Miscellaneous Straight Objective Type Questions

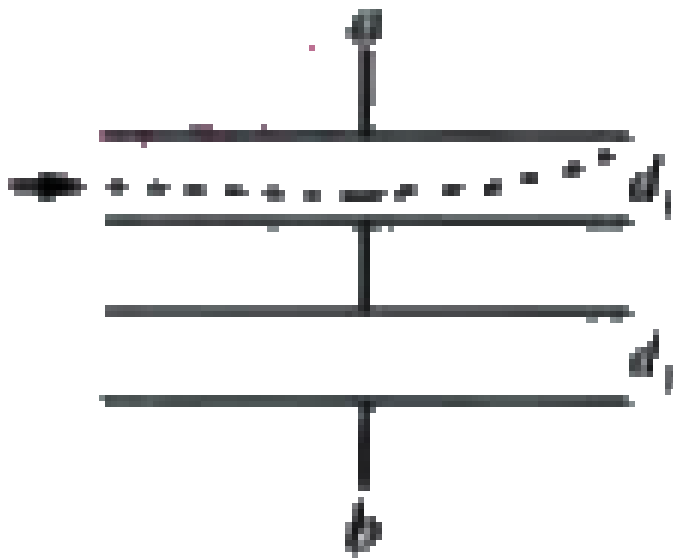1. Both the capacitors shown in figure are made of square plates of edge  $a$ . The separation between the plates of the capacitors are  $d_1$  and  $d_2$  as shown in the figure. A potential difference  $V$  is applied between the points a and b. An electron is projected between the plates of the upper capacitor along the central line. With what minimum speed should the electron be projected so that it does not collide with any plate? Consider only the electric forces.





- A.  $\left[ \frac{Vea^2}{md_2(d_1 - d_2)} \right]^{1/2}$
- B.  $\left[ \frac{Vea^2}{md_1(d_1 + d_2)} \right]^{1/2}$
- C.  $\left[ \frac{Vea^2}{md_2(d_1 - d_2)} \right]^2$
- D.  $\left[ \frac{Vea^2}{md_1(d_1 + d_2)} \right]^{1/2}$

**Answer: B**



**Watch Video Solution**

2. If an electron enters into a space between the plates capacitor at an angle  $\alpha$  with the plates and leaves at an angle  $\beta$  to the plates. The ratio of its kinetic energy while entering the capacitor to that while leaving will be


- A.  $\left[ \frac{\cos \alpha}{\cos \beta} \right]^2$
- B.  $\left[ \frac{\cos \beta}{\cos \alpha} \right]^2$
- C.  $\left[ \frac{\sin \alpha}{\sin \beta} \right]^2$

D.  $\left[ \frac{\sin \beta}{\sin \alpha} \right]^2$

Answer: B

 Watch Video Solution

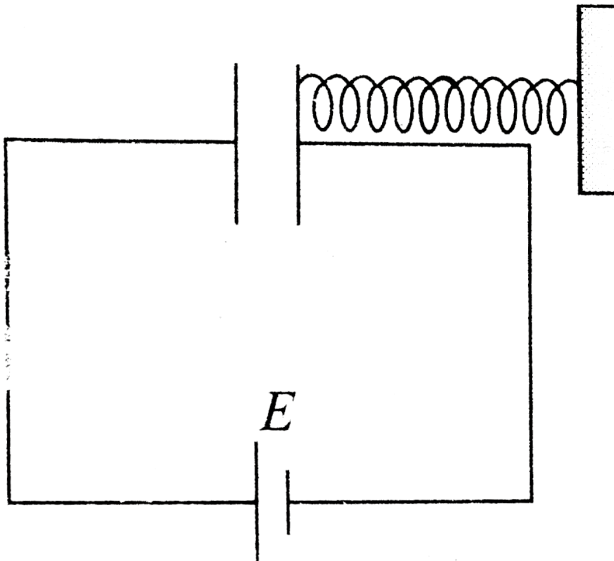3. One plate of a capacitor is fixed, and the other is connected to a spring as shown in. Area of both the plates is  $A$ . In steady state (equilibrium), separation between the plates is  $0.8d$  (spring was unstretched, and the distance between the plates was  $d$  when capacitor was uncharged). The force constant of the spring is approximately.



A.  $\frac{\epsilon_0 A E^2}{2d^3}$

B.  $\frac{2\epsilon_0 A E}{d}$


C.  $\frac{6\epsilon_0 A E^2}{2d^3}$

D.  $\frac{4\epsilon_0 A E^2}{d}$

Answer: D

[▶ Watch Video Solution](#)

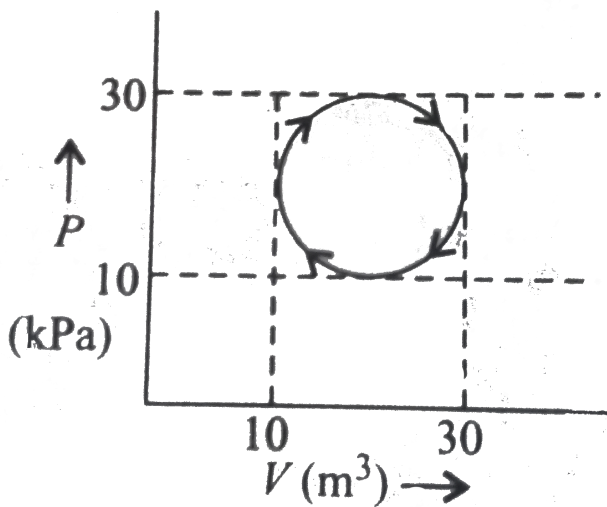4. Which one is not correct for a cyclic process as shown in the figure ?



A.  $\sqrt{2mgA \epsilon_0}$

$$B. \sqrt{\frac{4mgA \epsilon_0}{k}}$$

$$C. \sqrt{mgA \epsilon_0}$$

$$D. \sqrt{\frac{2mgA \epsilon_0}{k}}$$

**Answer: A**



**Watch Video Solution**

5. Two parallel plate capacitors are arranged perpendicular to the common axis. The separation  $d$  between the capacitors is much larger than the separation  $l$  between their plates and than their size. The capacitors are charged to  $q_1$  and  $q_2$  respectively (figure). Find the force of interaction between the capacitors.




$$A. \frac{1}{2} \frac{q_1 q_2}{\pi \epsilon_0 d^4} l^2$$

- B.  $\frac{2}{3} \frac{q_1 q_2}{\pi \epsilon_0 d^4} l^2$
- C.  $\frac{3}{2} \frac{q_1 q_2}{\pi \epsilon_0 d^4} l^2$
- D.  $\frac{1}{3} \frac{q_1 q_2}{\pi \epsilon_0 d^4} l^2$

Answer: C

 Watch Video Solution

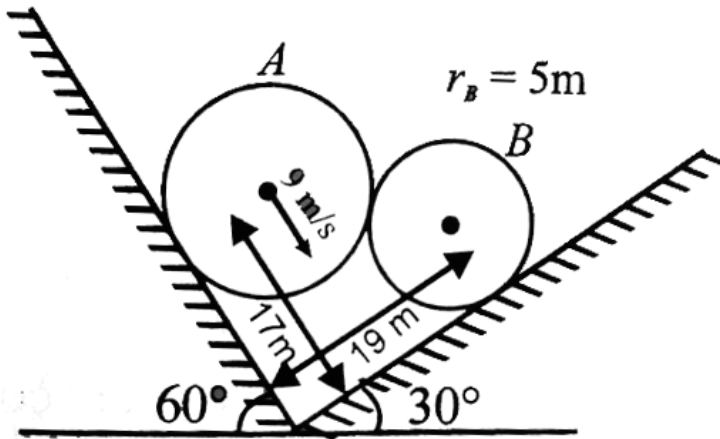

6.

System is shown in the figure. Velocity of sphere A is  $9 \frac{\text{m}}{\text{s}}$ . Find the speed of sphere B.

A.  $\frac{4\pi \epsilon_0 ac}{c + a}$

B.  $\frac{\pi \epsilon_0 ac}{c + a}$

C.  $\frac{\pi \epsilon_0 ac}{c - a}$

D.  $\frac{4\pi \epsilon_0 ac}{c - a}$

**Answer: D**



**Watch Video Solution**

7. Three long concentric conducting cylindrical shells have radii  $R$ ,  $2R$  and  $2\sqrt{2}R$ . Inner and outer shells are connected to each other. The capacitance across middle and inner shells per unit length is:

A.  $\frac{\frac{1}{3} \epsilon_0}{\ln 2}$

B.  $\frac{6\pi \epsilon_0}{\ln 2}$

C.  $\frac{\pi \epsilon_0}{\ln 2}$

D. None

**Answer: B**



Watch Video Solution

## Practice Sheet Exercise I Level I Main Straight Objective Type Questions

1. The capacities of three capacitors are in ratio 1:2:3. Their equivalent capacity when connected in parallel is  $\frac{60}{11}\mu F$  more than that when they are connected in series. The individual capacitors are of capacities in  $\mu F$ .

A. 4, 6, 7

B. 1, 2, 3

C. 2, 3, 4

D. 1, 3, 6

**Answer: B**



Watch Video Solution

2. Three condensers of capacity  $4mF$ ,  $2mF$  and  $3mF$  are connected such that 2 mF and 3 mF are in series and 4 mF is parallel to them. The equivalent capacity of the combination is

- A. 9 mF
- B. 5.2 mF
- C. 2.6 mF
- D. 10 mF


**Answer: B**



[Watch Video Solution](#)



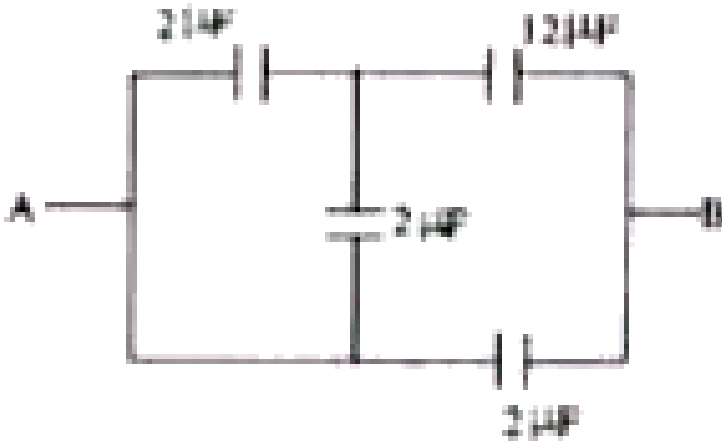3. The effective capacitance in  $\mu F$  in between A and B will be



A.  $28/9$

B. 4

C. 5

D. 18


Answer: C



Watch Video Solution

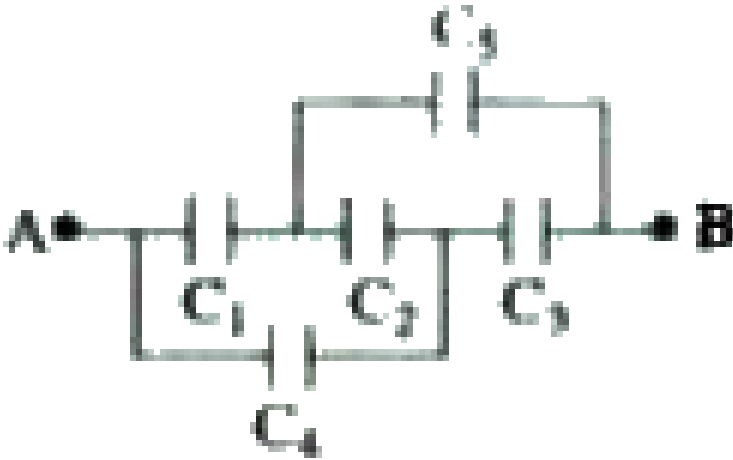4. The equivalent capacity between A and B in the given circuit is

$$(C_1 = 4\mu F, C_2 = 12\mu F, C_3 = 8\mu F, C_4 = 4\mu F, C_5 = 8\mu F)$$




- A.  $24\mu F$
- B.  $36\mu F$
- C.  $\frac{16}{3}\mu F$
- D.  $\frac{8}{3}\mu F$

Answer: C



Watch Video Solution

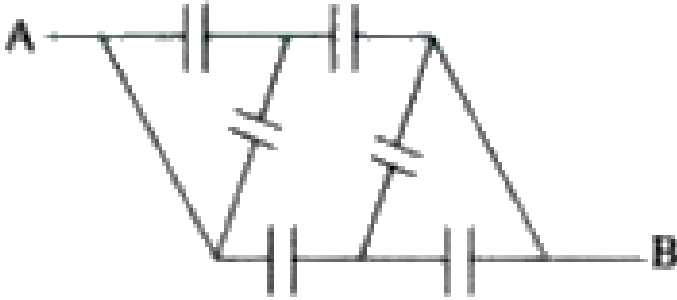5. The capacity of each condenser in the following fig. is  $C$ . Then the equivalent capacitance across A and B is




- A.  $C/4$
- B.  $3C/4$
- C.  $4C/3$
- D.  $3C$

**Answer: C**

[Watch Video Solution](#)

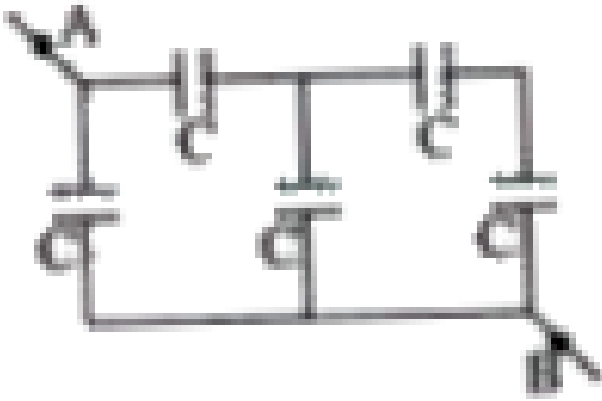6. What is the equivalent capacitance of the system of capacitor between A & B



A.  $\frac{7}{6}C$

B.  $1.6C$

C.  $C$

D. none

**Answer: B**



**Watch Video Solution**

7. Minimum number of capacitors each of  $8\mu F$  and 250 V used to make a composite capacitor of  $16\mu F$  and 1000 V are

A. 2

B. 4


C. 16

D. 32

Answer: D

 Watch Video Solution

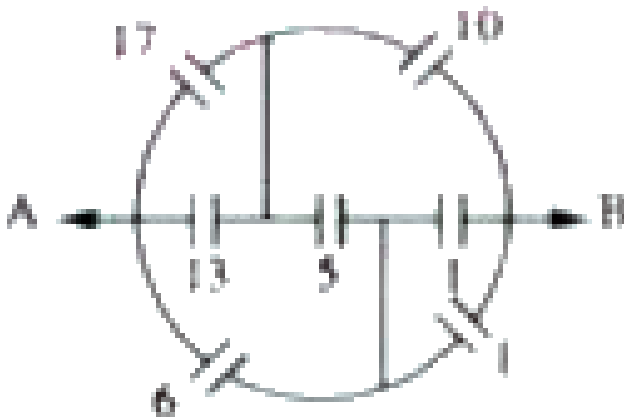8. Find equivalent capacitance across AB (all capacitances in  $\mu F$ )



A.  $\frac{20}{3} \mu F$

B.  $9\mu F$


C.  $48\mu F$

D. none

**Answer: B**

 [Watch Video Solution](#)

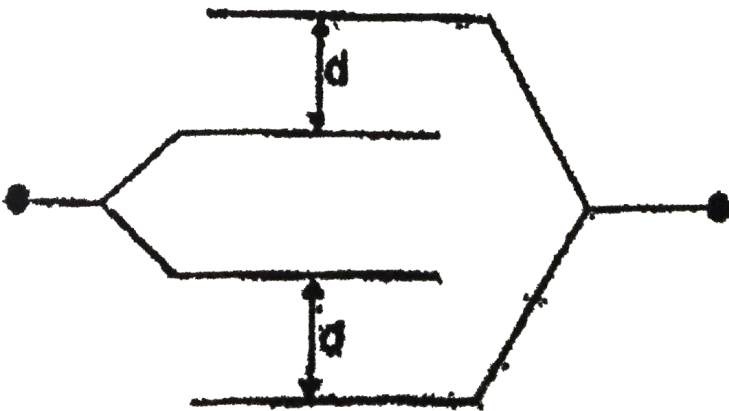9. Four plates are arranged as shown in the diagram. If area of each plate is  $A$  and the distance between two neighbouring parallel plates is  $d$ , then the capacitance of this system will be



A.  $\frac{\epsilon_0 A}{d}$

B.  $\frac{2\epsilon_0 A}{d}$

C.  $\frac{3\epsilon_0 A}{d}$


D.  $\frac{4\epsilon_0 A}{d}$

Answer: B

 Watch Video Solution

## Practice Sheet Exercise I Level II Advanced Straight Objective Type Questions

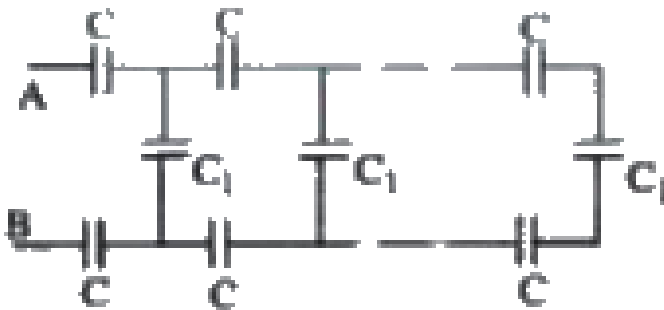1. If in the infinite series circuit  $C = 9\mu F$  and  $C_1 = 6\mu F$  then the capacity across AB is in .....  $\mu F$



A.  $3\mu F$

B.  $6\mu F$

C.  $9\mu F$

D.  $4.5\mu F$

**Answer: A**




**Watch Video Solution**

2. Five identical conducting plates each of face area  $A$ , are arranged as shown in figure. If a potential difference of  $V_0$  is created between



plate A and C then the charge on plate .E. will be [Given  $C = \frac{\epsilon_0 A}{d}$  ]

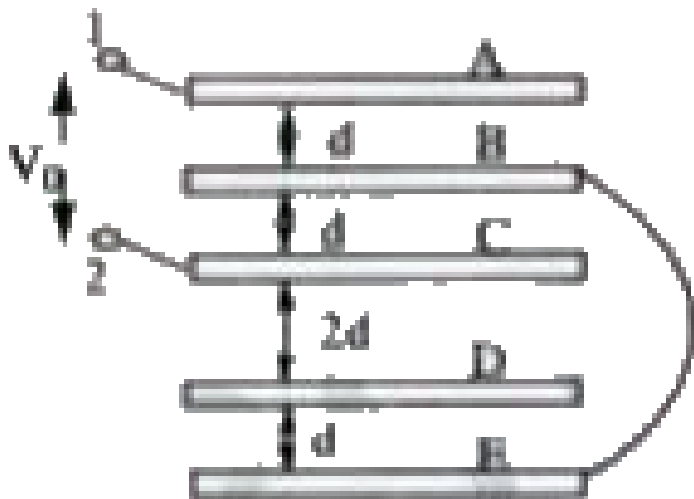


- A.  $\frac{3CV_0}{8}$
- B.  $\frac{5CV_0}{7}$
- C.  $\frac{5CV_0}{8}$
- D.  $\frac{CV_0}{7}$

**Answer: D**



**Watch Video Solution**

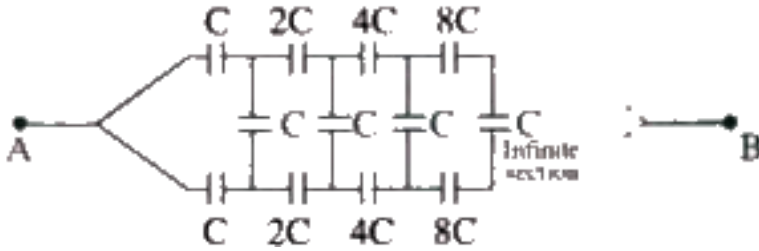3. Find the equivalent capacitance of the circuit between point A and B.



A.  $2C$

B.  $4C$

C.  $C$

D.  $5C$

Answer: C

[▶ Watch Video Solution](#)

4. In the pure inductive circuit, the curves between frequency  $f$  and reciprocal of inductive reactance  $1/X_L$  is

A.  $\frac{32}{23} \mu F$

B.  $\frac{11}{23}\mu F$

C.  $6\mu F$

D.  $1\mu F$

**Answer: A**




**Watch Video Solution**

## Practice Sheet Exercise I Level II Advanced More Than One Correct Answer Type Questions

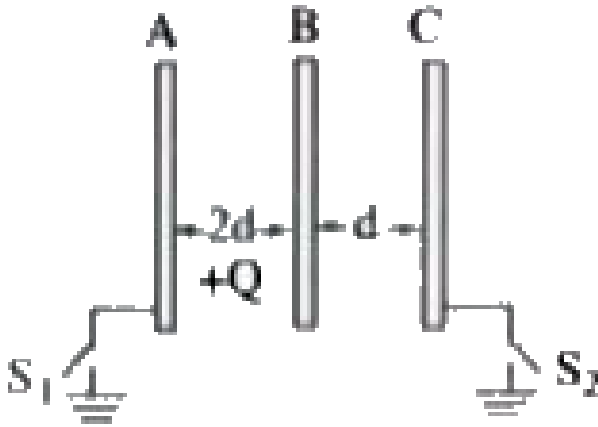1. Three identical parallel conducting plates A, B and C are placed as shown. Switches  $S_1$  and  $S_2$  are opened and connect A and C to earth

when closed.  $+Q$  charge is given to B.



A. If  $S_1$  is closed with  $S_2$  open, a charge of amount will pass through

$S_1$

B. If  $S_2$  is closed with  $S_1$  open, a charge of amount  $Q$  will pass through

$S_2$

C. If  $S_1$  and  $S_2$  are closed together, a charge of amount  $\frac{Q}{3}$  will pass

through  $S_1$  and a charge of amount  $\frac{2Q}{3}$  will pass through  $S_2$

D. All the above statements are incorrect

**Answer: A::B::C**



Watch Video Solution

## Practice Sheet Exercise I Level II Advanced Matrix Matching Type Questions

1. Three identical point masses, each of mass 1 kg lie in the  $xy$ -plane at points  $(0, 0)$ ,  $(0, 0.2 \text{ m})$  and  $(0, 2\text{m}, 0)$ . The net gravitational force on the mass at the origin is:



Watch Video Solution

## Practice Sheet Exercise II Level II Main Straight Objective Type Questions

1. Three condensers of capacities 3 mF, 6 mF, 12mF are connected in series with a battery. If the charge on 12 mF condenser is 24 mC, the P.D. across the battery is

A. 2 V

B. 4 V

C. 8 V

D. 14 V

**Answer: D**



[Watch Video Solution](#)

2. Three condensers of same capacity connected in series has effective capacity  $2\text{mF}$ . If they are connected in parallel and charged using a battery of emf  $12\text{V}$ , the total energy stored in the combination is

A.  $1296\text{ mJ}$

B.  $648\text{ mJ}$

C.  $162\text{ mJ}$

D.  $48\text{ mJ}$

**Answer: A**



[Watch Video Solution](#)

### 3. Match the columns

- |                                   |              |
|-----------------------------------|--------------|
| 1. Smallest unit of a compound    | a. molecule  |
| 2. Sulphur                        | b. noble gas |
| 3. Helium                         | c. non-metal |
| 4. A diatomic molecule            | d. carbon    |
| 5. An element having valency four | e. hydrogen  |
|                                   | f. metalloid |

A.  $250 \times 10^{-6}$ ,  $36 \times 10^{-4}$

B.  $250 \times 10^{-6}$ ,  $240 \times 10^{-4}$

C.  $250 \times 10^{-6}$ ,  $240 \times 10^{-4}$

D.  $250 \times 10^{-6}$ ,  $50 \times 10^{-4}$

**Answer: A**



**Watch Video Solution**

4. Two capacitors are in parallel and when connected to a source of 3000 V, store 250 J of energy. When they are connected in series to the same

source, the energy stored decreases by 190 J for the same potential. Their capacities are in the ratio

A. 3:2

B. 2:7

C. 4:3

D. 3:5

**Answer: A**

 [Watch Video Solution](#)

5. A and B are two points in a closed circuit. The potential difference across the condenser of capacity  $5\mu F$  is



A. 6V



B. 10V

C. 16V

D. 4V

**Answer: A**



**Watch Video Solution**

6.  $n$  identical condensers are joined in parallel and are charged to potential  $V$  so that energy stored in each condenser is  $E$ . If they are separated and joined in series, then the total energy and total potential difference of the combination will be

A.  $nE$  and  $\frac{V}{n}$

B.  $n^2E$  and  $nV$

C.  $\frac{E}{n^2}$  and  $\frac{V}{n^2}$


D.  $nE$  and  $nV$

Answer: D

 Watch Video Solution

Practice Sheet Exercise II Level II Advanced Straight Objective Type Questions

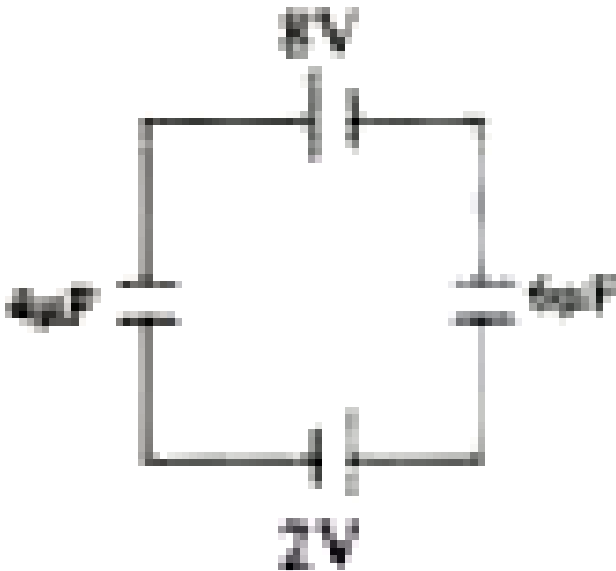1. Two condensers of capacities  $4\text{mF}$  and  $6\text{mF}$  are connected to two cells as shown. Then



A. P.D. of  $6\mu F$  condenser is  $4V$

B. charge of  $4\mu F$  condenser is  $24\mu C$

C. both of the above are true

D. none of the above is true

Answer: C

[▶ Watch Video Solution](#)

2. The potential drop across  $7\mu F$  capacitor is  $6V$ . Then



A. potential drop across  $3\mu F$  capacitor is  $10V$

B. charge on  $3\mu F$  capacitor is  $21\mu F$

C. emf of the cell is 30V


D. P.D across  $12\mu F$  capacitor is 5V

**Answer: C**

 [Watch Video Solution](#)

3. The capacitors in are initially uncharged and are connected as in the diagram with switch S open. The applied potential difference is

$$V_{ab} = + 360V.$$

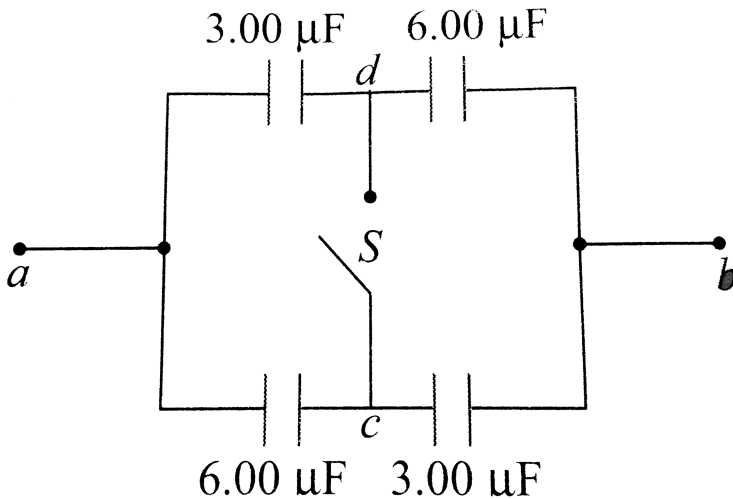

a. What is the potential difference  $V_{cd}$

b What is the potential difference across each capacitor after switch S is

closed?

c. How much charge will flow through the switch after it is closed?

A. 120 V

B. 100 V

C. 150 V

D. 115 V


**Answer: A**



[Watch Video Solution](#)

4. The capacitors in are initially uncharged and are connected as in the diagram with switch S open. The applied potential difference is

$$V_{ab} = + 360V.$$

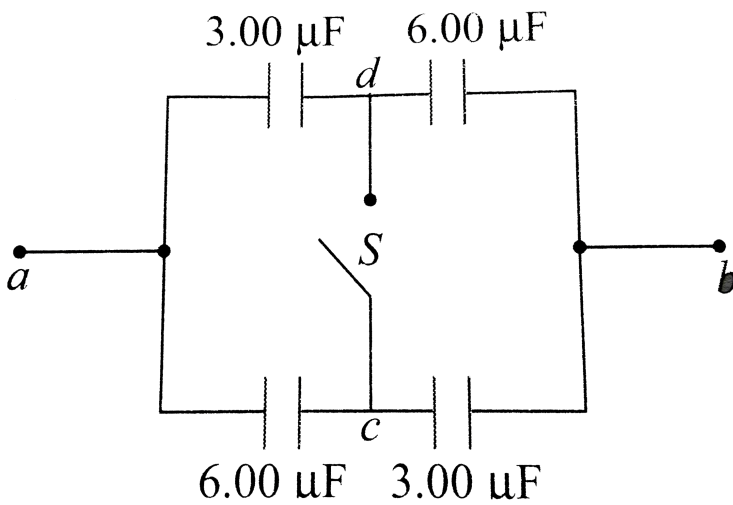

- What is the potential difference  $V_{cd}$
- What is the potential difference across each capacitor after switch S is closed?
- How much charge will flow through the switch after it is closed?


- A. 100 V
- B. 180 V
- C. 200 V
- D. 300 V

**Answer: B**



**Watch Video Solution**

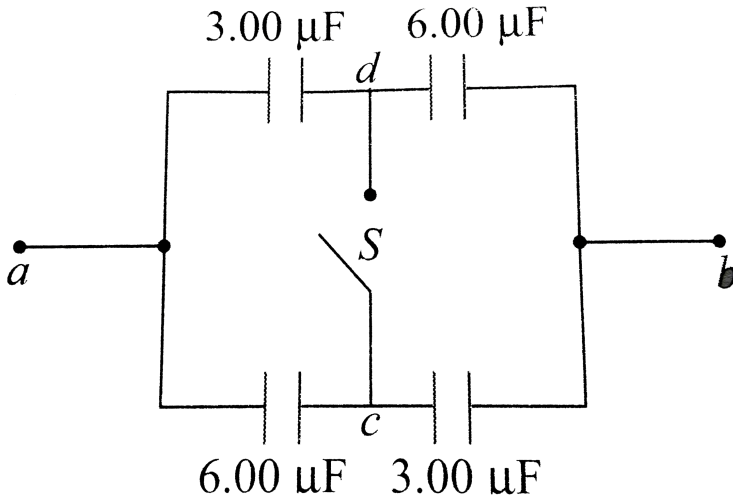5. The capacitors in are initially uncharged and are connected as in the diagram with switch  $S$  open. The applied potential difference is  $V_{ab} = +360V$ .



- What is the potential difference  $V_{cd}$
- What is the potential difference across each capacitor after switch  $S$  is closed?
- How much charge will flow through the switch after it is closed?

A.  $140 \mu\text{C}$  from C to D

B.  $240 \mu\text{C}$  from C to D

C.  $540\mu$  from C to D

D.  $120\mu C$  from C to D

**Answer: C**




**Watch Video Solution**

### Practice Sheet Exercise Iii Level I Main Straight Objective Type Questions

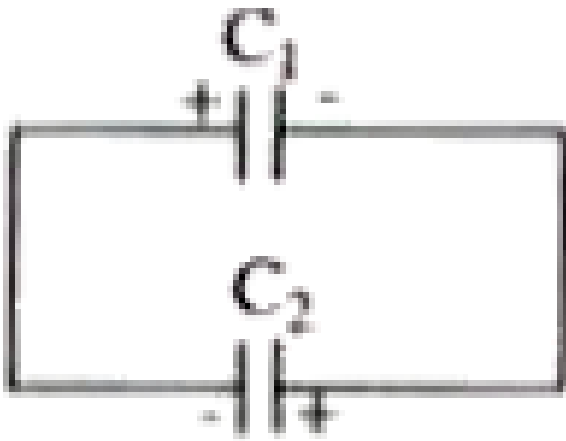1. A condenser of capacity  $16\text{ mF}$  charged to a potential of  $20\text{ V}$  is connected to a condenser of capacity  $C$  charged to a potential of  $10\text{ V}$  as shown in the figure.





If the common potential is 14 V. the capacity C is equal to

- A. 18 mF
- B. 24 mF
- C. 8 mF
- D. 4 mF

**Answer: D**



[Watch Video Solution](#)

2. A  $4\mu F$  capacitor is charged by a 200 V battery. It is then disconnected from the supply and is connected to another uncharged  $2\mu F$  capacitor. During the process loss of energy (in J) is

- A. Zero
- B.  $5.33 \times 10^{-2}$
- C.  $4 \times 10^{-2}$
- D.  $2.67 \times 10^{-2}$

**Answer: D**



[Watch Video Solution](#)

3. A charged sphere is connected to a similar uncharged sphere. Then the percentage loss of energy is

- A. 50 %
- B. 25 %

C. 20 %

D. 10 %

**Answer: A**



**Watch Video Solution**

4. The work done in increasing the P.D. across the plates of a capacitor from 4V to 6V is  $W$  then work done in increasing the P.D. from 6V to 8V is

A.  $\frac{4W}{3}$

B.  $\frac{3W}{4}$

C.  $\frac{7W}{5}$

D.  $\frac{5W}{7}$

**Answer: C**



**Watch Video Solution**

5. A  $10\mu F$  capacitor and a  $20\mu F$  capacitor are connected in series across a 200 v supply line. The charged capacitors are then disconnected from the line and reconnected such that those same polarities are connected to each other and no external voltage is applied. The potential difference across capacitors is

A.  $\frac{800}{9}$  volt

B.  $\frac{800}{3}$  volt

C. 400 volt

D. 200 volt


**Answer: A**



[Watch Video Solution](#)

Practice Sheet Exercise Iii Level Ii Advanced More Than One Correct Answer  
Type Questions

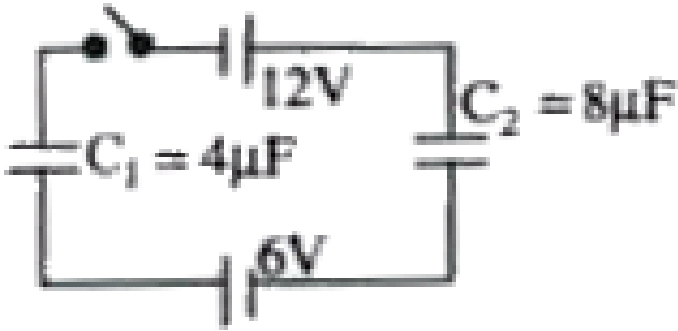1. In the circuit shown initially  $C_1, C_2$  are uncharged. After closing the switch



- A. The charge on  $C_2$  is greater than that on  $C_1$
- B. The charge on  $C_1$  and  $C_2$  are the same
- C. The potential drops across  $C_2$  and  $C_1$  are the same
- D. The potential drops across  $C_2$  is greater than that across  $C_1$

**Answer: B**



**Watch Video Solution**

2. The two plates X and Y of a parallel plate capacitor of capacitance  $C$  are given a charge of amount  $Q$  each. X is now joined to the positive terminal and Y to the negative terminal of a cell of emf  $E = Q/C$  :-

- A. Charge of amount  $Q$  will flow from the negative terminal to the positive terminal of the cell inside
- B. The total charge on the plate X will be  $2Q$ .
- C. The total charge on the plate Y will be zero.
- D. The cell will supply  $CE^2$  amount of energy.


**Answer: A::B::C::D**



[Watch Video Solution](#)

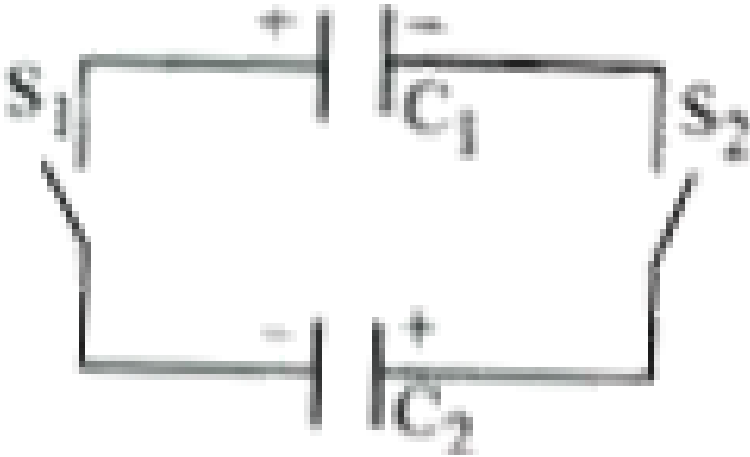3. Two capacitors  $C_1 = 4\mu F$  and  $C_2 = 2\mu F$  are charged to same potential  $V = 500$  Volt, but with opposite polarity as shown in the figure.

The switches  $S_1$  and  $S_2$  are closed.



A. The potential difference across the two capacitors are same and is

given by  $\frac{500}{3}V$

B. The potential difference across the two capacitors are same and is

given by  $\frac{1000}{3}V$

C. The ratio of final energy to initial energy of the system is  $1/9$ .


D. The ratio of final energy to initial energy of the system is  $4/9$ .

**Answer: A::C::D**



**Watch Video Solution**

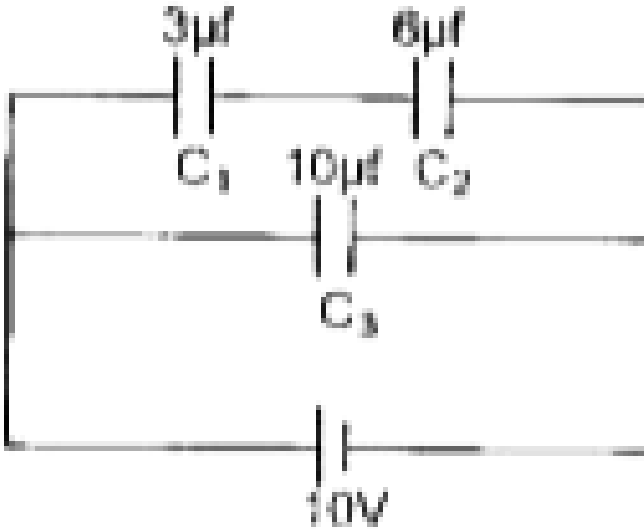4. Three capacitors of capacitance  $C_1 = 3\mu f$ ,  $C_2 = 6\mu f$  and  $C_3 = 10\mu f$ , are connected to a 10V battery as shown in Figure 3 below



Calculate:

Equivalent capacitance

- A. The amount of the charge flown through the battery is  $20\mu C$
- B. The heat generated in the circuit is 0.6 mJ
- C. The energy supplied by the battery is 0.6 mJ
- D. The amount of charge flown through the switch S is  $60\mu C$


**Answer: A::C::D**





Watch Video Solution

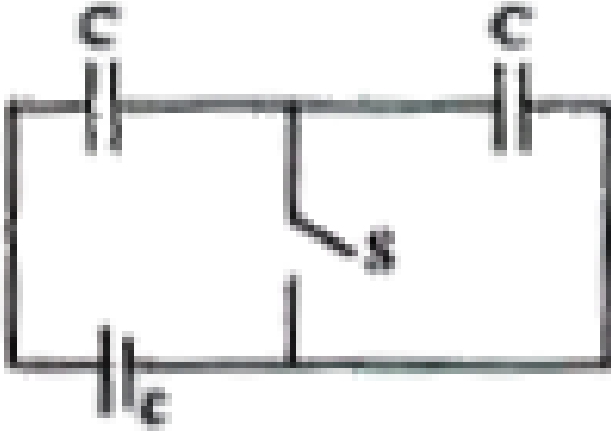5. Consider the situation shown in figure. The switch  $S$  is open for a long time and then closed.



Find the work done by the battery .

A.  $2C\epsilon / 2$


B.  $C\epsilon^2 / 2$

C.  $C\epsilon / 2$

D.  $C\epsilon / 3$

**Answer: B**

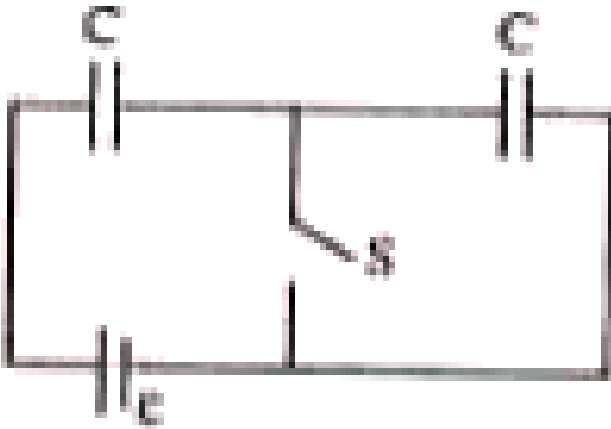6. Consider the situation shown in figure. The switch  $S$  is open for a long time and then closed.




Find the change in energy stored in the capacitors.

- A.  $C\mathcal{E}^2 / 2$
- B.  $C\mathcal{E} / 2$
- C.  $C\mathcal{E}^2 / 4$
- D.  $C / \mathcal{E}$

**Answer: C**



Watch Video Solution

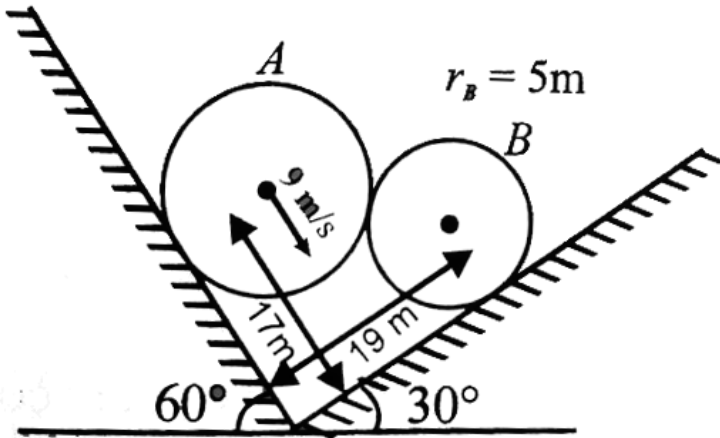

7.

System is shown in the figure. Velocity of sphere A is  $9 \frac{\text{m}}{\text{s}}$ . Find the speed of sphere B.

- A.  $C\epsilon^2$
- B.  $2C\epsilon^2$
- C.  $C\epsilon^2/2$
- D.  $C\epsilon^2/4$

Answer: D



Watch Video Solution

## Practice Sheet Exercise iii Level Ii Advanced Linked Comprehension Type Questions

1. A capacitor having a capacitance of  $100\mu F$  is charged to a potential difference of  $24V$ . The charging battery is disconnected and the capacitor is connected to another battery of emf  $12V$  with the positive plate of the capacitor joined with the positive terminal of the battery. (a) Find the charges on the capacitor before and after the reconnection. (b) Find the charge flown through the  $12V$  battery. (c) Is work done by the battery or is it done on the battery? find its magnitude. (d) Find the decrease in electrostatic field energy. (e) Find the best developed during the flow of charge after reconnection.

A.  $1400\mu C$ ,  $1200\mu C$

B.  $4400\mu C$ ,  $1000\mu C$

C.  $5400\mu C$ ,  $3400\mu C$

D.  $2400\mu C$ ,  $1200\mu C$

Answer: D



Watch Video Solution

2. A capacitor having a capacitance of  $100\mu F$  is charged to a potential difference of  $24V$ . The charging battery is disconnected and the capacitor is connected to another battery of emf  $12V$  with the positive plate of the capacitor joined with the positive terminal of the battery. (a) Find the charges on the capacitor before and after the reconnection. (b) Find the charge flown through the  $12V$  battery. (c) Is work done by the battery or is it done on the battery? find its magnitude. (d) Find the decrease in electrostatic field energy. (e) Find the best developed during the flow of charge after reconnection.

A.  $1200\mu C$

B.  $1600\mu C$

C.  $1800\mu C$

D.  $2400\mu C$

**Answer: A**



**Watch Video Solution**

3. A capacitor having a capacitance of  $100\mu F$  is charged to a potential difference of  $24V$ . The charging battery is disconnected and the capacitor is connected to another battery of emf  $12V$  with the positive plate of the capacitor joined with the positive terminal of the battery. (a) Find the charges on the capacitor before and after the reconnection. (b) Find the charge flown through the  $12V$  battery. (c) Is work done by the battery or is it done on the battery? find its magnitude. (d) Find the decrease in electrostatic field energy. (e) Find the best developed during the flow of charge after reconnection.

A. 12.4 mj

B. 10.4 mj

C. 14.4 mj

D. 14.4 mj

Answer: C



Watch Video Solution

4. A capacitor having a capacitance of  $100\mu F$  is charged to a potential difference of  $24V$ . The charging battery is disconnected and the capacitor is connected to another battery of emf  $12V$  with the positive plate of the capacitor joined with the positive terminal of the battery. (a) Find the charges on the capacitor before and after the reconnection. (b) Find the charge flown through the  $12V$  battery. (c) Is work done by the battery or is it done on the battery? find its magnitude. (d) Find the decrease in electrostatic field energy. (e) Find the best developed during the flow of charge after reconnection.

A. 11.6 mJ

B. 21.6 mJ

C. 31.6 mJ

D. 41.6 mJ

**Answer: B**



**Watch Video Solution**

5. A capacitor having a capacitance of  $100\mu F$  is charged to a potential difference of  $24V$ . The charging battery is disconnected and the capacitor is connected to another battery of emf  $12V$  with the positive plate of the capacitor joined with the positive terminal of the battery. (a) Find the charges on the capacitor before and after the reconnection. (b) Find the charge flown through the  $12V$  battery. (c) Is work done by the battery or is it done on the battery? find its magnitude. (d) Find the decrease in electrostatic field energy. (e) Find the best developed during the flow of charge after reconnection.

A. 6.2 mJ

B. 4.2 mJ

C. 2.2 mJ


D. 7.2 mJ



Answer: D

 Watch Video Solution

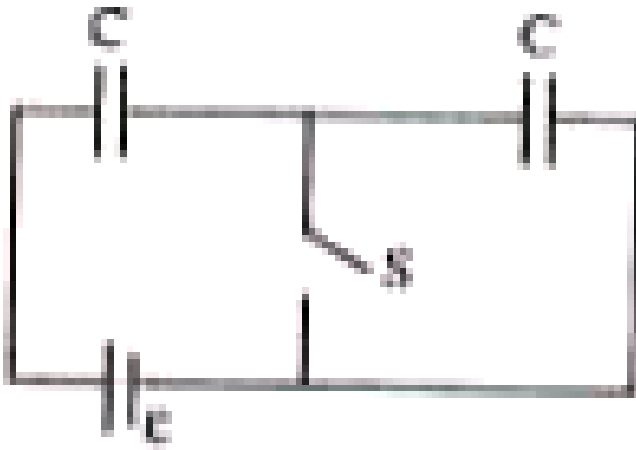6. Consider the situation shown in figure. The switch S is open for a long time and then closed.



Find the charge flown through the battery when the switch S is closed.

A.  $C\epsilon/2$

B.  $C\epsilon/5$

C.  $C/\epsilon$

$$D. 2C/\epsilon$$

Answer: A

 [Watch Video Solution](#)


## Practice Sheet Exercise Iii Level Ii Advanced Matrix Matching Type Questions

1. Match the Column A with Column B

Column A	Column B
(a) Elements short by 1 electron in octet	(i) Transition elements
(b) Highly reactive metals	(ii) Noble gases
(c) Non-reactive elements	(iii) Alkali metals
(d) Elements of groups 3 to 12	(iv) Alkaline earth metals
(e) Radioactive elements	(v) Halogens
(f) Elements with 2 electrons in the outmost orbit.	(vi) Actinides

 [Watch Video Solution](#)

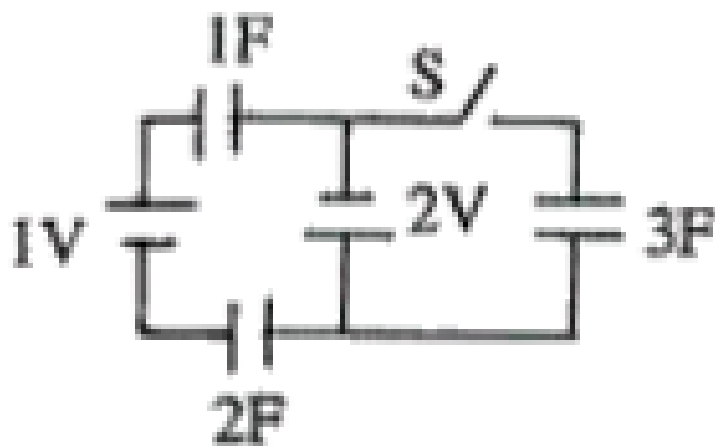1. There is no charge on  $3F$  capacitor when  $S$  is open. How Much heat (in Joule) is developed in circuit after  $S$  is closed ?



[Watch Video Solution](#)

1. The capacity of a parallel plate capacitor formed by the plates of same area  $A$  is  $0.02\mu F$  with air as dielectric. Now one plate is replaced by a

plate of area  $2A$  and dielectric ( $k=2$ ) is introduced between the plates, the capacity is

A.  $0.04\mu F$

B.  $0.08\mu F$


C.  $0.01\mu F$

D.  $2\mu F$

**Answer: A**

 [Watch Video Solution](#)

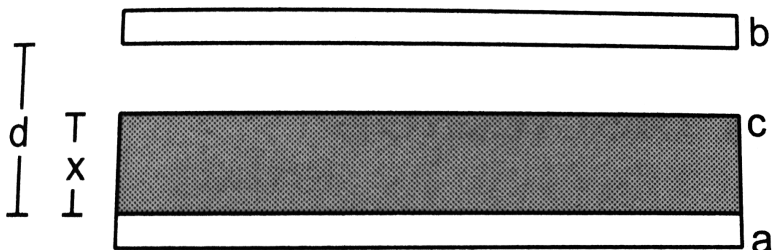2. A parallel plate capacitor has plate area  $A$  and plate separation  $d$ . The space between the plates is filled up to a thickness  $x$  ( $x < d$ ) with a dielectric constant  $K$ . Calculate the capacitance of the system.



A.  $1.6 \times 10^{-5} J$

B.  $2 \times 10^{-6} J$

C.  $12.4 \times 10^{-5} J$


D.  $1.6 \times 64 \times 10^{-5} J$

**Answer: C**

 [Watch Video Solution](#)

3. Three plates A, B and C are placed close to each other with  $+Q$  charge given to the middle plate. The inner surfaces to A and C can be connected to earth through plate D and keys  $K_1$  and  $K_2$ . The plates D is a dielectric slab with dielectric constant  $K_1$  then the charge that will flow through plate D and keys  $K_1$  and  $K_2$ . The plate D is a dielectric slab with dielectric constant K, then the charge that will flow through plate D when  $K_2$  is

closed and  $K_2$  is open is

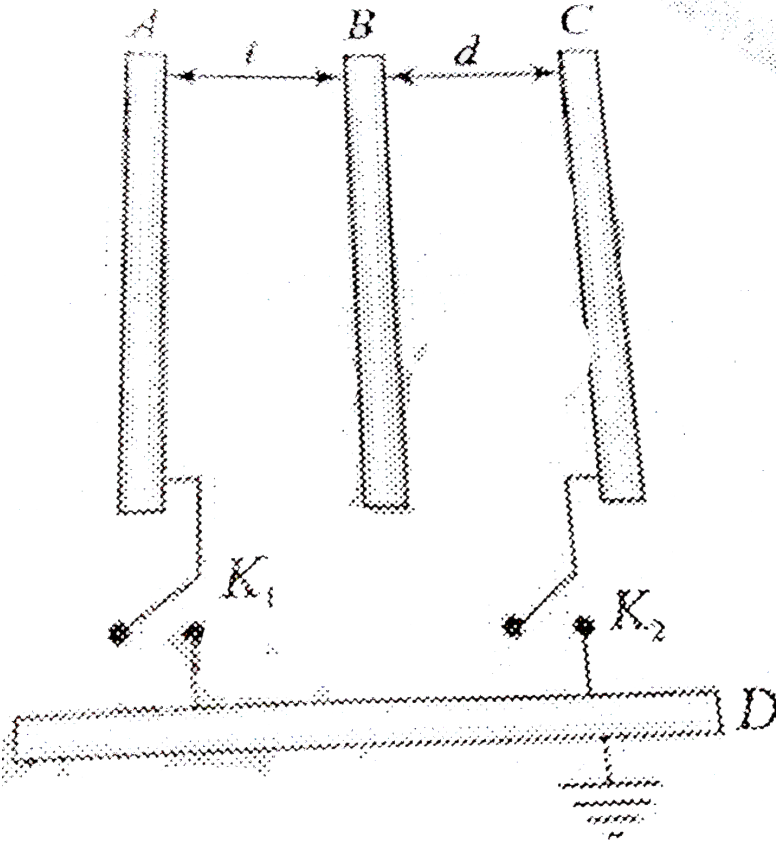

A. 2

B. 2.5

C. 4

D. 10

**Answer: B**



[Watch Video Solution](#)

4. When a dielectric slab of thickness 6 cm is introduced between the plates of parallel plate condenser, it is found that the distance between the plates has to be increased by 4 cm to restore to capacity original value. The dielectric constant of the slab is

A. 1.5

B.  $2/3$

C. 3

D. 4

**Answer: C**



[Watch Video Solution](#)

5. A parallel plate capacitor with air as medium between the plates has a capacitance of  $10\mu F$ . The area of capacitor is divided into equal halves

and filled with two media as shown in the figure having dielectric constant  $K_1 = 2$  and  $K_2 = 4$ . The capacitance of the system will now be



- A. 10 mF
- B. 20 mF
- C. 30 mF
- D. 40 mF

**Answer: C**



[Watch Video Solution](#)

6. Two identical parallel plate capacitors are connected in series to a battery of  $100V$ . A dielectric slab of dielectric constant 4.0 is inserted between the plates of second capacitor. The potential difference across the capacitors will now be respectively.

- A. 10 V, 40 V



B. 70V,30 V

C. 75 V,25 V

D. 80V,20 V

**Answer: D**



[Watch Video Solution](#)

7. The ratio between masses of two planets is 3 : 5 and the ratio between their radii is 5 : 3. The ratio between their acceleration due to gravity will be

A. 1.8pF

B. 45 pF

C. 40.5 pF

D. 20.25 pF

**Answer: C**



[Watch Video Solution](#)

8. A parallel plate capacitor with air as dielectric is charged to a potential  $V$  using a battery. Removing the battery. The charged capacitor is then connected across an identical uncharged parallel plate capacitor filled with dielectric constant  $k$ . The common potential of both the capacitor is

A.  $V$  volts

B.  $kV$  volts

C.  $(k+1)V$  volts

D.  $\frac{V}{k+1}$  volts

**Answer: D**



[Watch Video Solution](#)

9. The capacity of a parallel plate condenser with air as dielectric is  $2\mu F$ . The space between the plates is filled with dielectric slab with  $K = 5$ . It is charged to a potential of 200V and disconnected from cell. Work done in removing the slab from the condenser completely

A. 0.8 J

B. 0.6 J

C. 1.2J

D. 1.6J

**Answer: A**



**Watch Video Solution**

10. A parallel - plate capacitor of plate area  $A$  and plate separation  $d$  is charged to a potential difference  $V$  and then the battery is disconnected . A slab of dielectric constant  $K$  is then inserted between the plate of the

capacitor so as to fill the space between the plate .Find the work done on the system in the process of inserting the slab.

A.  $\frac{\epsilon_0 AV^2}{d} \left(1 - \frac{1}{K}\right)$

B.  $\frac{\epsilon_0 AV}{2d} \left(\frac{1}{K} - 1\right)$

C.  $\frac{\epsilon_0 AV^2}{2d} \left(\frac{1}{K} - 1\right)$

D.  $\frac{\epsilon_0 AV^2}{2d} \left(1 - \frac{1}{K}\right)$

**Answer: C**



**Watch Video Solution**

**11.** A dielectric slab of length  $l$ , width  $b$ , thickness  $d$  and dielectric constant  $K$  fills the space inside a parallel plate capacitor. At  $t = 0$ , the slab begins to be pulled out slowly with speed  $y$ . At time  $t$ , the capacity of the capacitor is

A.  $\frac{\epsilon_0 b}{d} [Kl - (K - 1)vt]$

B.  $\frac{\epsilon_0 b}{b} [Kl + (K + 1)vt]$

C.  $\frac{\epsilon_0 b}{b} [(Kl + 1)vt]$

D.  $\frac{\epsilon_0 b}{b} [l + (K - 1)vt]$

**Answer: A**




**Watch Video Solution**

## Practice Sheet Exercise Iv Level Ii Advanced Straight Objective Type Questions

1. The figure shows a parallel-plate capacitor having square plates of edge  $a$  and plate-separation  $d$ . The gap between the plates is filled with a dielectric of dielectric constant  $k$  which varies as  $K = K_0 + \alpha x$  parallel to an edge as where  $K$  and  $\alpha$  are constants and  $x$  is the distance from the

left end. Calculate the capacitance.

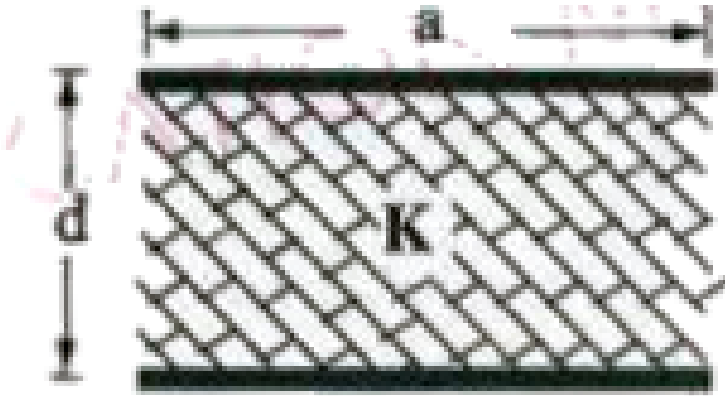

A.  $\frac{\epsilon_0 a^2}{d} \left( K_0 + \frac{a\alpha}{2} \right)$

B.  $\frac{\epsilon_0 a^2}{d} \left( K_0 - \frac{a\alpha}{2} \right)$

C.  $\frac{\epsilon_0 a}{d} \left( K_0 - \frac{a\alpha}{2} \right)$


D.  $\frac{\epsilon_0 a}{d} \left( K_0 + \frac{a\alpha}{2} \right)$

**Answer: A**

[▶ Watch Video Solution](#)

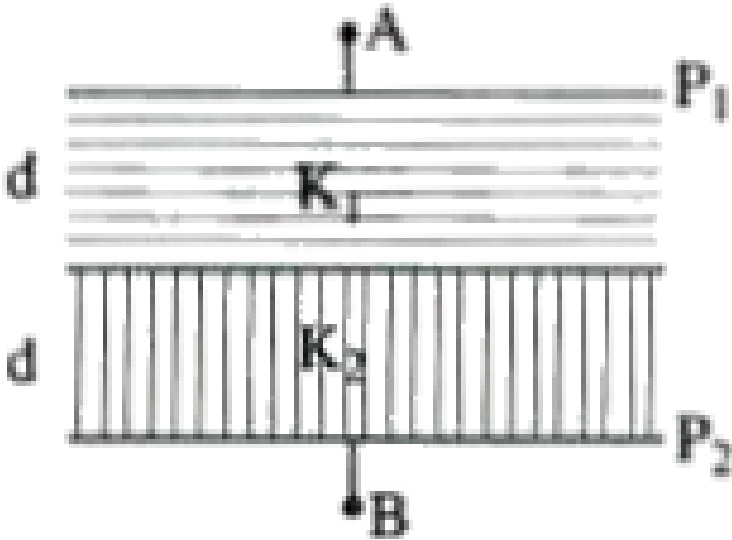2. In the figure shown  $P_1$  and  $P_2$  are two conducting plates having charges of equal magnitude and opposite sign. Two dielectrics of

dielectric constant  $K_1$  and  $K_2$  fill the space between the plates as shown in the figure. The ratio of electrical energy in 1<sup>st</sup> dielectric to that in the 2<sup>nd</sup> dielectric is :




- A. 1 : 1
- B.  $K_1 : K_2$
- C.  $K_2 : K_1$
- D.  $K_2^2 : K_1^2$

**Answer: C**



**Watch Video Solution**

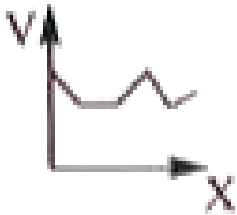3. The distance between plates capacitor is  $5d$ . The positively charged plate is at  $x = 0$  and negatively charged plate is at  $x = 5d$ . Two slabs one of conductor and the other of a dielectric of same thickness  $d$  are inserted between the plates as shown in figure. Potential ( $V$ ) versus distance  $x$  graph will be



A.




B.



C.



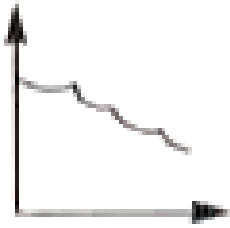


D.

Answer: B

[▶ Watch Video Solution](#)

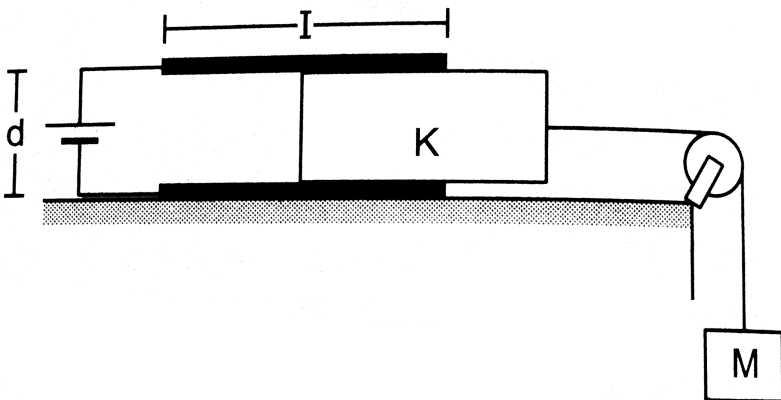4. Consider the situation shown in figure .The width of each plate is  $b$ .The capacitor plates are rigidly clamped in the laboratory and connected to be a battery of emf  $\varepsilon$  All surfaces are friction less .Calculate the value of  $M$  for which the dielectric slab will stay in equilibrium.



A.  $\frac{\epsilon_0 b E^2 (K - 1)}{2dg}$

B.  $\frac{\epsilon_0 b E^2 (K - 1)}{dg}$


C.  $\frac{2\epsilon_0 b E^2 (K - 1)}{dg}$

D.  $\frac{\epsilon_0 b E^2 (K + 1)}{dg}$

Answer: A

 Watch Video Solution

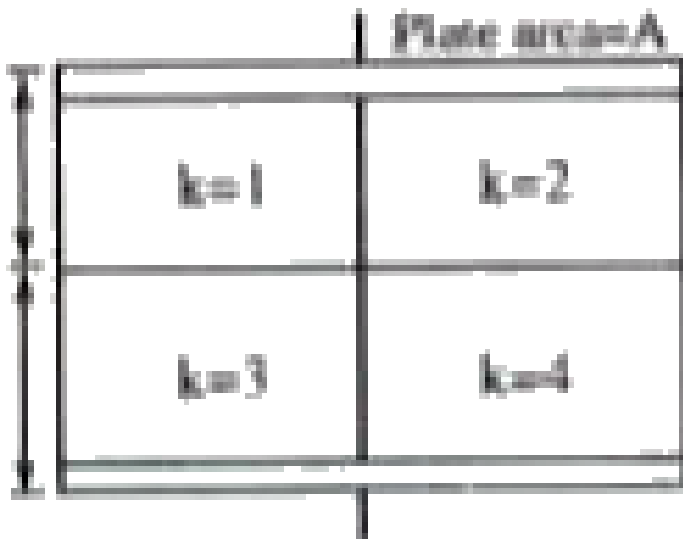5. Find the capacitance of the system shown in figure.



A.  $\frac{25}{12} \frac{\epsilon_0 A}{d}$

B.  $\frac{19}{24} \frac{\epsilon_0 A}{d}$

C.  $\frac{21}{24} \frac{\epsilon_0 A}{d}$

D.  $\frac{11}{7} \frac{\epsilon_0 A}{d}$

**Answer: A**



**Watch Video Solution**

## Practice Sheet Exercise Iv Level Ii Advanced More Than One Correct Answer Type Questions

1. Following operations can be performed on a capacitor :

X - connect the capacitor to a battery of emf. E.Y - disconnect the battery

Z - reconnect the battery with polarity reversed. W - insert a dielectric slab

in the capacitor

- A. In XYZ (perform X, then Y, then Z) the stored electric energy remains unchanged and no thermal energy is developed.
- B. The charge appearing on the capacitor is greater after the action XWY than after the action XYW.
- C. The electric energy stored in the capacitor is greater after the action WXY than after the action XYW .
- D. The electric field in the capacitor after the action XW is the same as that after WX.

**Answer: B::C::D**



**Watch Video Solution**

2. The plates of a parallel plate capacitor with no dielectric are connected to a voltage source. Now a dielectric of dielectric constant  $K$  is inserted to fill the whole space between the plates with voltage source remaining connected to the capacitor

- A. the energy stored in the capacitor will become K-times
- B. the electric field inside the capacitor will decrease to K-times
- C. the force of attraction between the plates will increase to  $K^2$  - times
- D. the charge on the capacitor will increase to K-times

**Answer: A::C::D**

 [Watch Video Solution](#)

3. The capacitance of a parallel plate capacitor is  $C_0$  when the plates has air between them. This region is now filled with a dielectric slab of dielectric constant K and capacitor is connected with battery of EMF E and zero internal resistance. Now slab is taken out, then during the removal at slab :

- A. charge  $CE(k - 1)$  flows through the cell
- B. energy  $E^2C(k - 1)$  is absorbed by the cell.

C. the energy stored in the capacitor is reduced by  $E^2 C(k - 1)$

D. the external agent has to do  $\frac{1}{2} E^2 C(k - 1)$  amount of work to take the slab out.

**Answer: A::B::D**



**Watch Video Solution**

4. A parallel plate capacitor of plate area  $a$  and plate separation  $d$  is charged to potential difference  $V$  and then the battery is disconnected. A slab of dielectric constant  $K$  is then inserted between the plates of the capacitor so as to fill the space between the plates. If  $Q, E,$  and  $W$  denote, respectively, the magnitude of charge on each plate, the electric field between the plates (after the slab is inserted) and work done on the system, in question, in the process of inserting the slab, then

A.  $Q = \frac{\epsilon_0 AV}{d}$

B.  $Q = \frac{\epsilon_0 KAV}{d}$

$$C. E = \frac{V/K}{d}$$

$$D. W = \frac{\epsilon_0 AV^2}{2d} \left(1 - \frac{1}{K}\right)$$

**Answer: A::C::D**



**Watch Video Solution**

### Additional Practice Exercise Level I Main Straight Objective Type Questions

1. A thick conducting slab is introduced between the plates of an isolated charged capacitor to fill the free space partially and without touching any plate. Which of the following is wrong statement regarding the points inside the capacitor


- A. Electric field at some points will change and at some points remains unchanged
- B. Electric field is zero at all the points

- C. Electrostatic energy density at some points will change and that at some points remains unchanged
- D. Total electrostatic energy of the capacitor will decrease

Answer: B

 [Watch Video Solution](#)

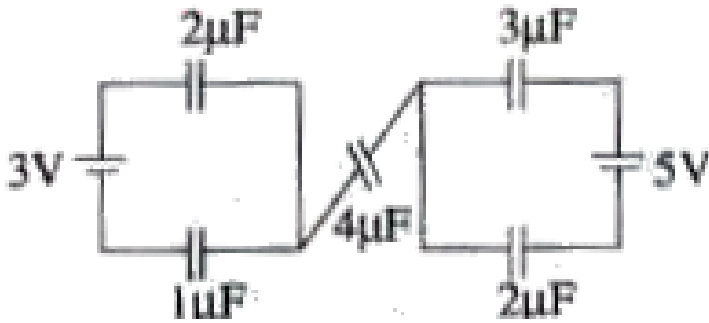2. All the capacitors were uncharged before they are connected in circuit.  
Now the charge on  $4\mu F$  capacitor is



- A. Zero
- B.  $4\mu F$
- C.  $8\mu F$




D.  $12\mu F$

Answer: A

 Watch Video Solution

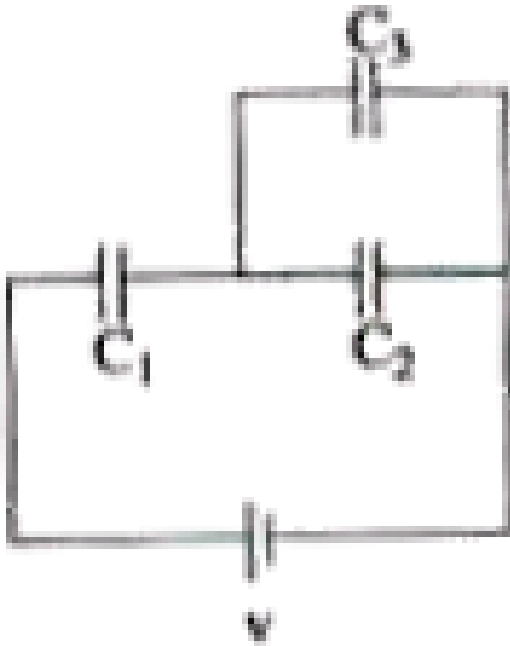3. Three uncharged capacitors are connected across a battery as shown. It is known that the energy stored in all the capacitors is same. Which of the following is not correct?



A.  $C_1 = 4C_2$

B.  $C_2 = C_3$

C.  $C_1 > C_2 + C_3$

D. none

**Answer: D**



[Watch Video Solution](#)

4. The ratio between masses of two planets is 3 : 5 and the ratio between their radii is 5 : 3. The ratio between their acceleration due to gravity will be

A. 4


B. 6

C. 8

D. 2

**Answer: C**

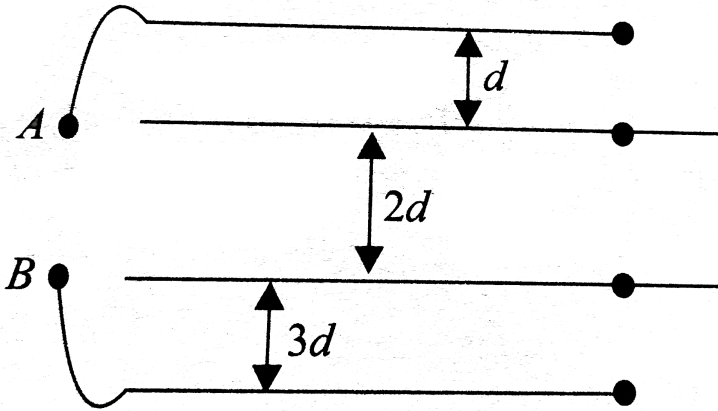5. If the area of each plate is  $A$  and then successive separations are  $d$ ,  $2d$  and  $3d$ , then find the equivalent capacitance across A and B.



A.  $\frac{\epsilon_a A}{6d}$


B.  $\frac{\epsilon_0 A}{4d}$

C.  $\frac{3\epsilon_0 A}{4d}$

D. None

Answer: B

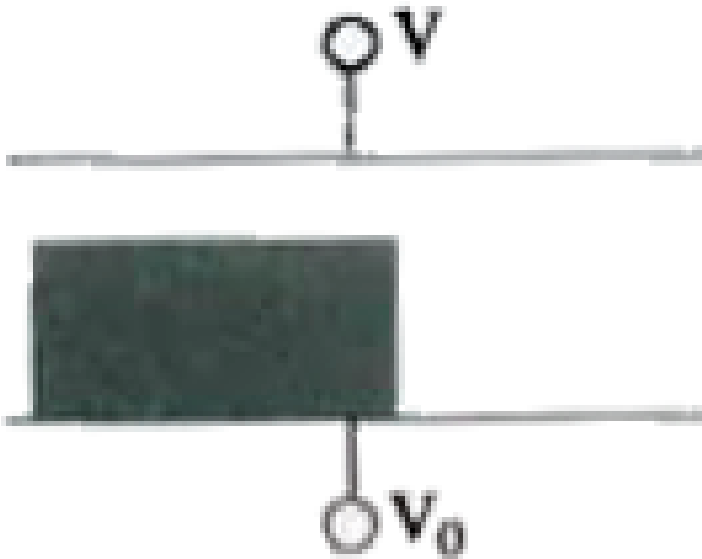6. The capacitor shown has square plates of side  $L$  and has gap  $d$  between the plates. In the dielectric constant of the material of the slab is  $k$ , the capacitance of the capacitor is



A.  $C_{eq} = \frac{\epsilon_0 L^2 (1 + 2K)}{d(1 + K)}$

B.  $C_{eq} = \frac{\epsilon_0 L^2 (1 + 3K)}{d(1 + 2K)}$


C.  $C_{eq} = \frac{\epsilon_0 L^2 (1 + 2K)}{d(1 + 2K)}$

D.  $C_{eq} = \frac{\epsilon_0 L^2 (1 + 3K)}{d(1 + K)}$

Answer: B

 Watch Video Solution

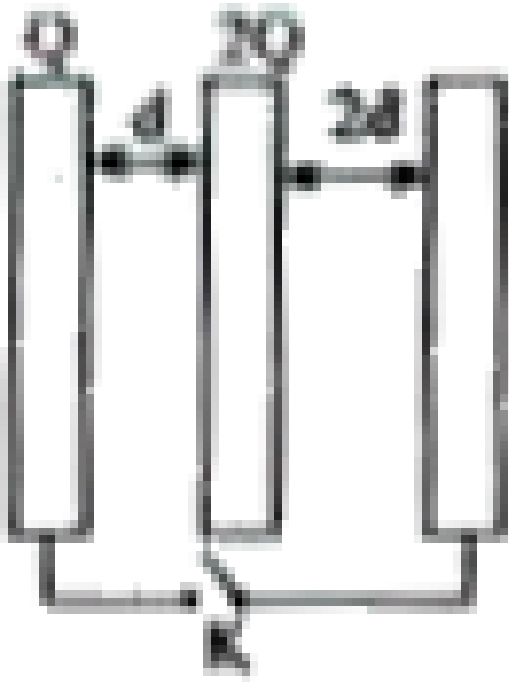7. Three large plates are arranged as shown. How much charge will flow through the key k if it is closed?



A.  $\frac{5Q}{6}$

B.  $\frac{4Q}{3}$

C.  $\frac{3Q}{2}$


D. None

**Answer: A**



**Watch Video Solution**

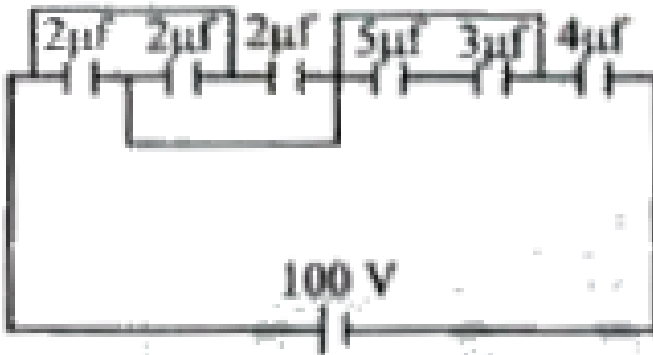8. In the circuit shown in figure charge stored in the capacitor of capacity  $5\mu f$  is



A.  $16\mu C$

B.  $20\mu C$

C.  $30\mu C$


D. zero

**Answer: D**



[Watch Video Solution](#)

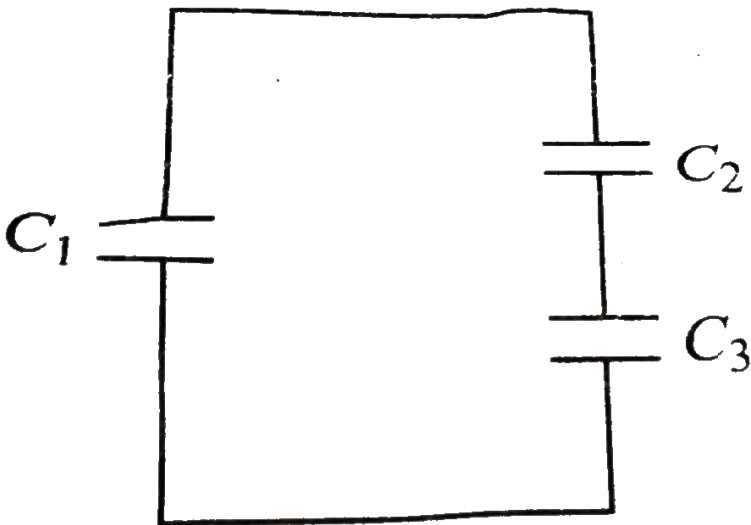9. Capacitor  $C_1$  is connected to a battery and charged till the magnitude of the charge on each plate is  $q_0$ . Then, the battery is disconnected and  $C_1$  is connected to two other uncharged capacitors  $C_2$  and  $C_3$  as shown in figure. Final charges on the capacitors ( $q_1$ ,  $q_2$  and  $q_3$ ) are related by .



A.  $14\mu C$

B.  $8\mu C$


C.  $7\mu C$

D.  $6\mu C$

Answer: B

 Watch Video Solution

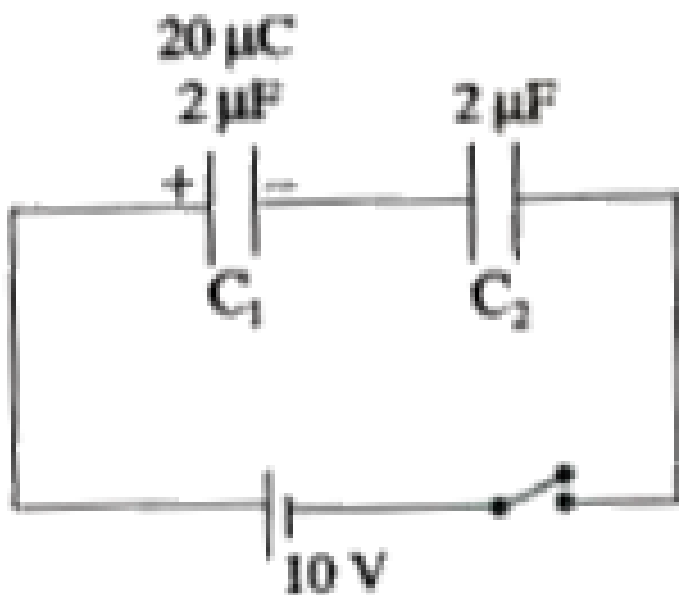10. When switch is closed , charges on  $C_1$  and  $C_2$  are





A.  $20\mu C, 0$

B.  $10\mu C, 10\mu C$

C.  $30\mu C, 10\mu C$

D.  $0, 20\mu C$

**Answer: A**



**Watch Video Solution**

11. The plates of a parallel plate capacitor have surface area  $A$  and are initially separated by a distance  $d$ . They are connected to a battery of voltage  $v_0$ . Now, the plates of the capacitor are pulled apart with a separation  $2d$ . Then, increase in the energy of the battery is

A.  $\frac{\epsilon_0 AV_0^2}{4d}$

B.  $\frac{\epsilon_0 AV_0^2}{2d}$


C.  $\frac{\epsilon_0 AV_0^2}{8d}$

D. there will be no change in the energy of the battery

Answer: B

 Watch Video Solution

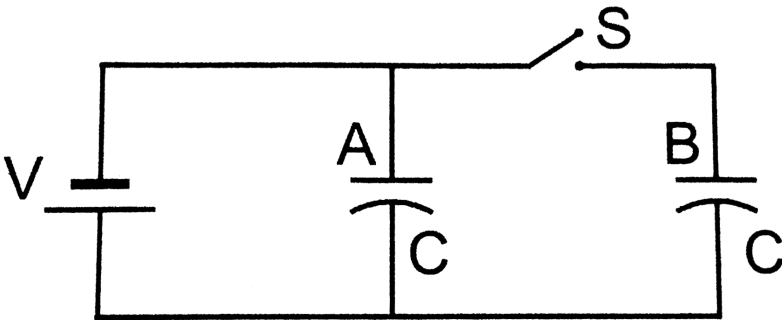12. Figure shows two identical parallel plate capacitors connected to a switch  $S$ . Initially, the switch is closed so that the capacitors are completely charged. The switch is now opened and the free space between the plates of the capacitors is filled with a dielectric of dielectric constant 3. Find the ratio of the initial total energy stored in the capacitors to the final total energy stored.



A. 3:5

B. 1:1


C. 5 : 3

D. non of these

Answer: A

[▶ Watch Video Solution](#)

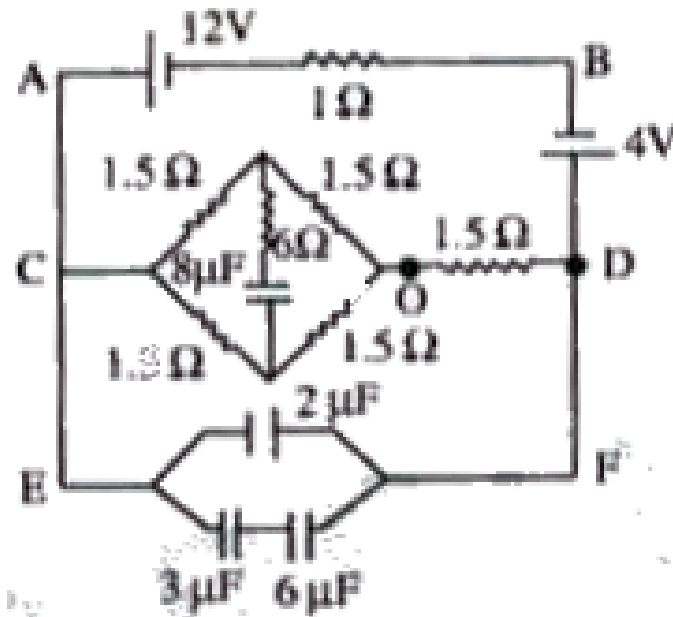13. In the given circuit, the potential difference across the  $6\mu F$  capacitor in steady state is



A. 1V

B. 4V


C. 3V

D. 2V

Answer: D

 Watch Video Solution

14. In the given circuit find the  $|V_A - V_B|$  where  $V_A, V_B$  are electric potentials at the points A and B.

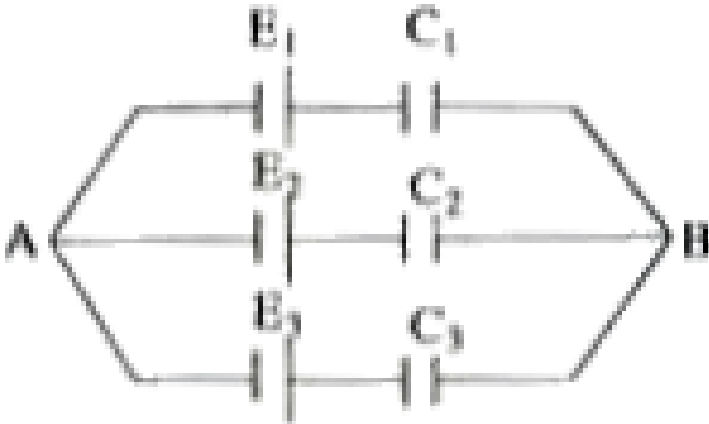

A.  $\frac{E_1 + E_2 + E_3}{3}$


- B.  $\frac{3}{\frac{1}{E_1} + \frac{1}{E_2} + \frac{1}{E_3}}$
- C.  $\frac{E_1 C_1 + E_2 C_2 + E_3 C_3}{C_1 + C_2 + C_3}$
- D.  $\frac{\frac{E_1}{C_1} + \frac{E_2}{C_2} + \frac{E_3}{C_3}}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}}$

**Answer: C**

 [Watch Video Solution](#)

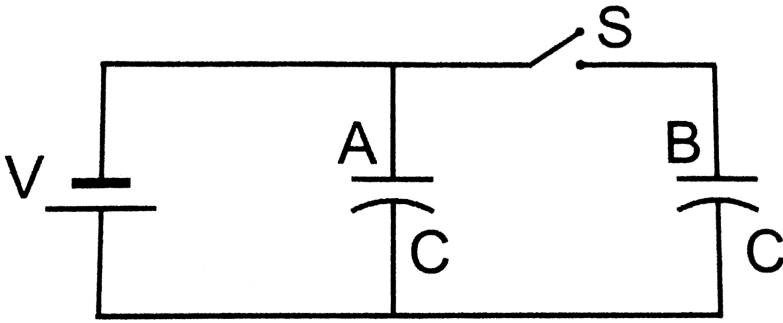15. Figure shows two identical parallel plate capacitors connected to a switch  $S$ . Initially, the switch is closed so that the capacitors are completely charged. The switch is now opened and the free space between the plates of the capacitors is filled with a dielectric of dielectric constant 3. Find the ratio of the initial total energy stored in the

capacitors to the final total energy stored.






- A. 2 : 3
- B. 3 : 4
- C. 3 : 5
- D. 5 : 36

**Answer: C**

[▶ Watch Video Solution](#)

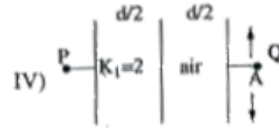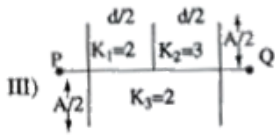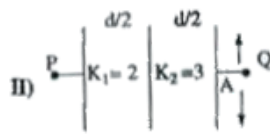16. Arrange the following in decreasing order effective capacitor between P and Q



A. IV,III,II,I

B. I,II,III,IV

C. II,IV,III,I

D. I,III,II,IV


Answer: B



Watch Video Solution

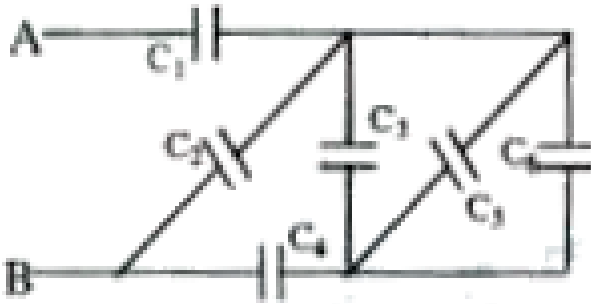17. In the accompanying diagram, if  $C_1 = 3\mu F$ ,  $C_2 = 6\mu F$ ,  $C_3 = 9\mu F$ ,  $C_4 = 12\mu F$ ,  $C_5 = 15\mu F$  and  $C_6 = 18\mu F$

, then the equivalent capacitor between the ends A and B is



- A.  $1.22\mu F$
- B.  $5.16\mu F$
- C.  $2.25\mu F$
- D.  $2.51\mu F$


**Answer: D**

[▶ Watch Video Solution](#)

18. Consider a capacitor as shown in figure. If we pull the plates of capacitor apart to a final position as shown in figure, then we must perform some work against the electric force. For this situation, mark out



the correct statements.

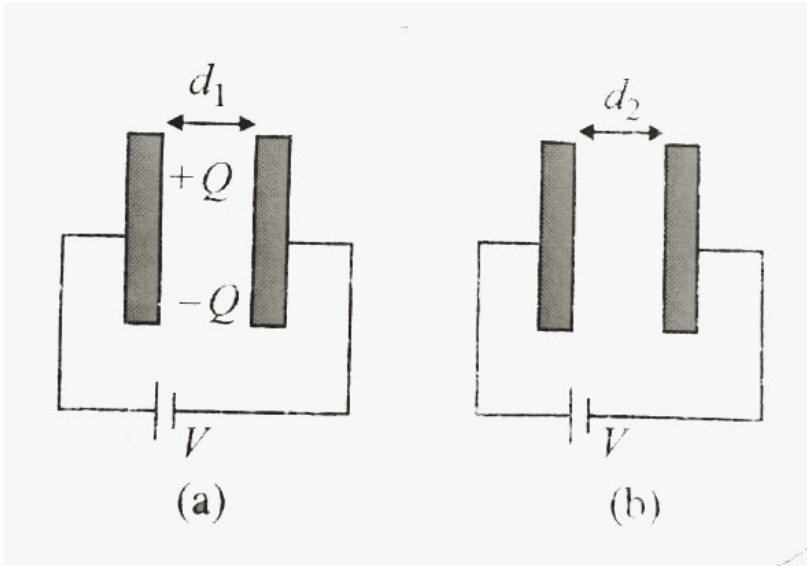


- A. Work done is  $\frac{Q^2}{2\epsilon_0 A}(d_2 - d_1)$  and is stored in volume  $A(d_2 - d_1)$
- B. Work done is  $+\frac{Q^2}{2\epsilon_0 A}(d_2 - d_1)$  and is stored in volume  $Ad_2$ .
- C. Work done is  $+\frac{\epsilon_0 AV^2}{2}\left(\frac{d_2 - d_1}{d_1 d_2}\right)$  and is stored in volume  $A(d_2 - d_1)$
- D. Work done is  $+\frac{\epsilon_0 AV^2}{2}\left(\frac{d_2 - d_1}{d_1 d_2}\right)$  and is stored in volume  $Ad_2$

**Answer: C**

 [Watch Video Solution](#)


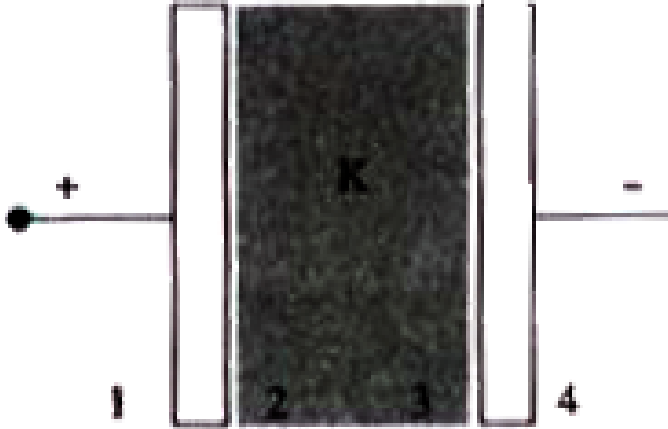
19. An isolated capacitor of capacitance  $C$  is charged to a potential  $V$ . Then a dielectric slab of dielectric constant  $K$  is inserted as shown. The net charge on four surfaces 1, 2, 3 and 4 would be respectively.



- A.  $0, CV - CV, 0$
- B.  $0, \frac{CV}{K}, \frac{-CV}{K}, 0$
- C.  $CV, 0, 0, -CV$
- D.  $CV, \frac{-CV}{K}, \frac{CV}{K}, -CV$

Answer: B

[Watch Video Solution](#)

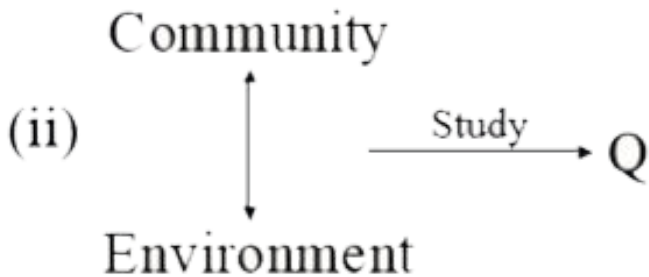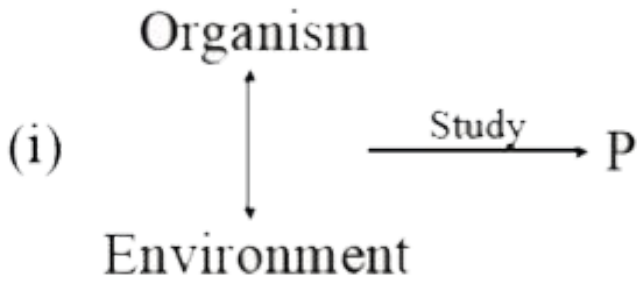

20.

then P and Q are respectively called as.

A.  $Q_1 > Q_4$

B.  $Q_1 = 2.5\mu C$

C.  $Q_1 < Q_4$


D.  $Q_4 = 5\mu C$

**Answer: B**



**Watch Video Solution**

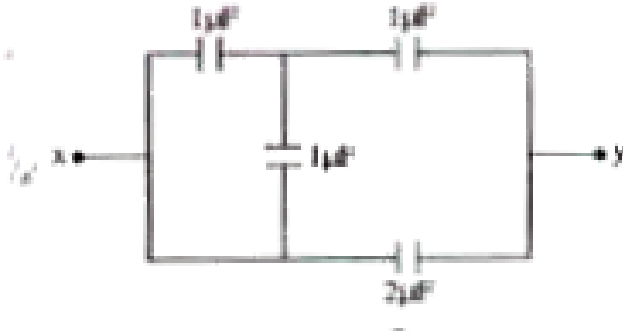21. Four capacitors are connected as shown in figure. Their capacities are indicated in the figure. The effective capacitance between points x and y is (in  $\mu F$ )




- A.  $\frac{5}{6}$
- B.  $\frac{7}{6}$
- C.  $\frac{8}{3}$
- D. 2

Answer: C



Watch Video Solution

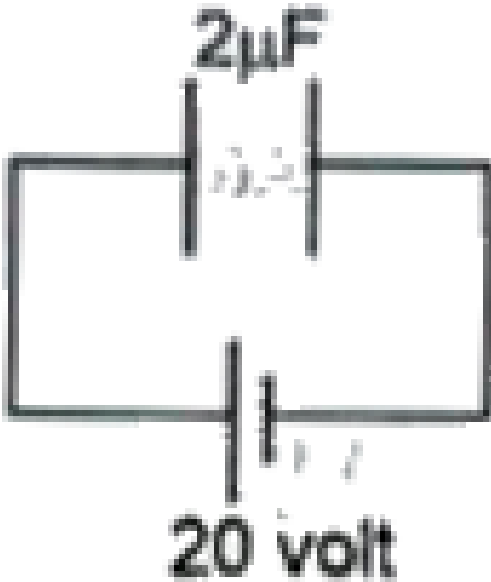22. In the figure a capacitor of capacitance  $2\mu F$  is connected to a cell of emf 20 volt. The plates of the capacitor are drawn apart slowly to double the distance between them. The work done by the external agent on the plates is:



- A.  $-200\mu J$
- B.  $200\mu J$
- C.  $400\mu J$
- D.  $-400$


Answer: B



Watch Video Solution

Additional Practice Exercise Level II Lecture Sheet Advanced Straight Objective Type Questions

1. Find AB.

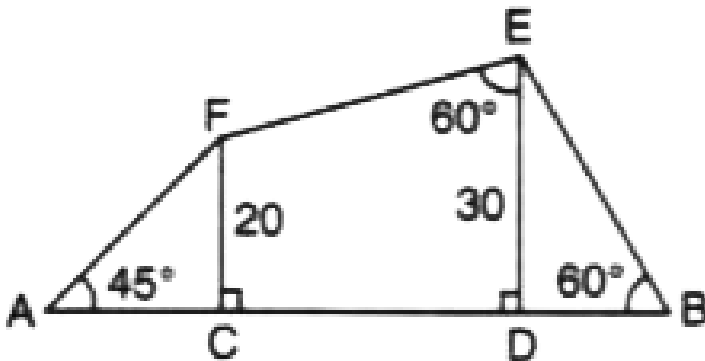

A.  $\frac{10}{3}$  pF

B.  $\frac{1}{2}$  pF


C. 1 pF

D.  $\frac{1}{30}$  pF

Answer: A

 Watch Video Solution

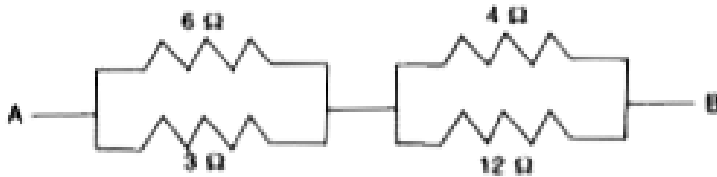2. Find the equivalent resistance between A and B.



A.  $48\pi\epsilon_0 a$

B.  $\frac{36}{11}\pi\epsilon_0 a$


C.  $\frac{72}{11}\pi\epsilon_0 a$

D.  $\frac{48}{11}\pi\epsilon_0 a$

Answer: C

 Watch Video Solution

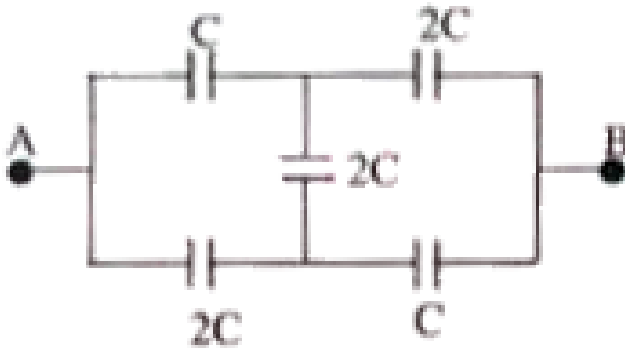3. Find the equivalent capacitance between A and B



A.  $7C$

B.  $10/7C$

C.  $10C$

D.  $20C$


**Answer: B**



[Watch Video Solution](#)



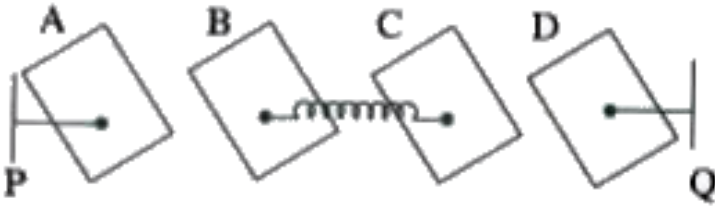4. Four identical conducting plates are placed parallel to each other at equal separations as shown below:



Plates A and D are fixed while B and C are connected with the help of a conducting spring of spring constant  $k$ . Initially, the spring is in relaxed position and B and C are at rest, now the spring is compressed slightly by displacing B and C and then plates B and C are released to perform SHM. Now the capacitance of the system across PQ [ Mass of each plate is  $m$ ]

A. remain constant

B. Increase continuously

C. decreases continuously


D. is varying sinusoidally with frequency  $\frac{1}{2\pi} \sqrt{\frac{2k}{m}}$

**Answer: D**



**Watch Video Solution**

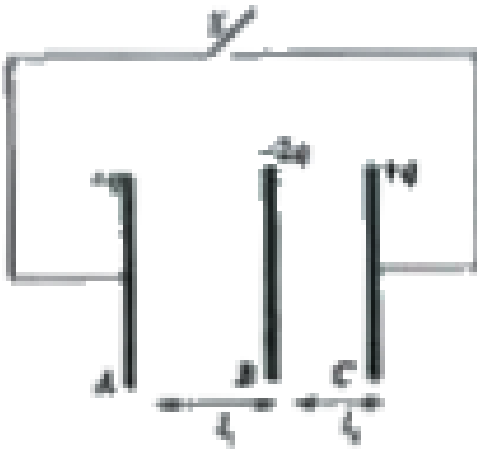5. Three large conducting plates A, B and C having charges  $+q, -2q$  and  $+q$  as shown in fig. The gaps  $l_1$  and  $l_2$  are small and  $l_1 > l_2$ . The plates A and C are fixed and B is free to move. Neglect gravity. If switch S is closed, the plate B will start moving towards



A. Left

B. Right


C. will not move

D. First move towards left and then towards right

Answer: B

[Watch Video Solution](#)

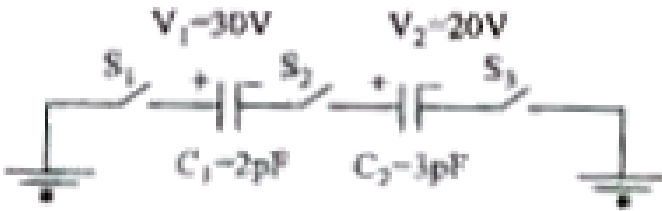6. First move towards left and then towards right For the circuit shown, which of the following statements is true ?




- A. with  $S_1$  closed,  $V_1 = 15V$ ,  $V_2 = 20V$
- B. with  $S_3$  closed,  $V_1 = V_2 = 25V$
- C. with  $S_1$  &  $S_2$  closed  $V_1 = V_2 = 0$
- D. with  $S_1$  &  $S_2$  closed  $V_1 = 30V$ ,  $V_2 = 20V$

Answer: D

[Watch Video Solution](#)

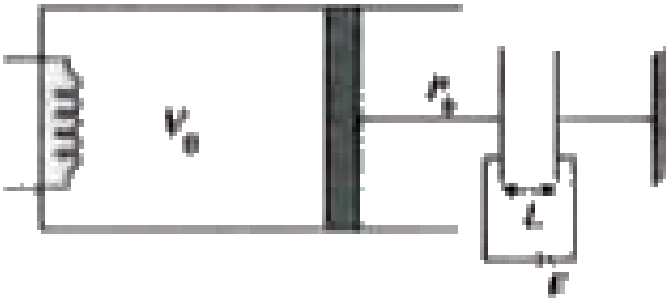
7. An ideal gas is enclosed in a cylinder fitted with a frictionless piston. The piston is connected with a light rod to one plate of capacitor whose other plate is fixed as shown. Initially volume of the gas inside the cylinder is  $V_0$  Atmospheric pressure is  $P_0$  separation between the plates is  $L$ , area of the piston as well as of the capacitor plates is  $A$  and emf of battery is  $\varepsilon$ . A heater supplies heat to the gas so that pressure of the gas is given as  $P = P_0 - \frac{n\varepsilon_0\varepsilon^2}{L^2}$  when piston is displaced by a distance  $\frac{L}{2}$ . Find value of  $n$ .



[▶ Watch Video Solution](#)

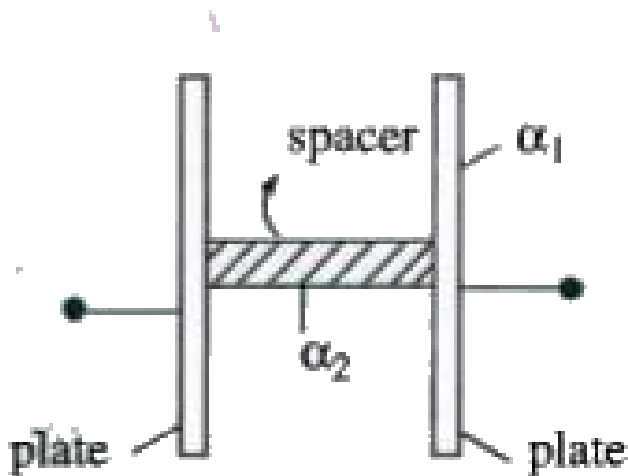8. A capacitor is to be designed to operate, with constant capacitance, even when temperature varies. The distance between plates is adjusted by


spacer to compensate temperature effect. Let  $\alpha_1$  and  $\alpha_2$  be the coefficient of thermal expansion of plate and spacer respectively. Find the ratio of  $\frac{\alpha_2}{\alpha_1}$ . So that no change in capacitance of capacitor with change in temperature.



[Watch Video Solution](#)

9. The initial charge across capacitors A and B are shown with  $Q=CE$ . Find the ratio of final charge in capacitor A to the final charge in capacitor B,

when cells are switched on.

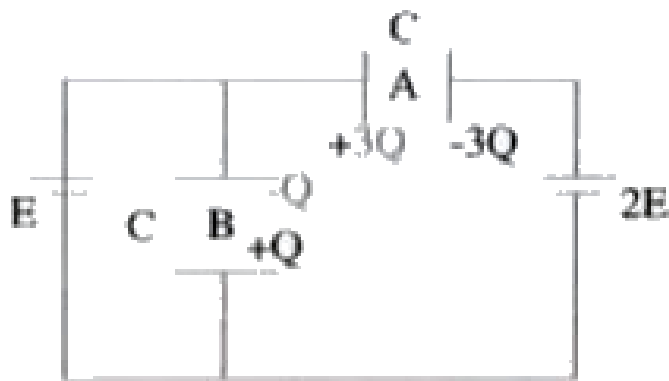

[Watch Video Solution](#)

## Additional Practice Exercise Level Ii Lecture Sheet Advanced Matrix Matching Type Questions


1. Match the refining methods (Column I) with (Column II).

Column I (Refining methods)	Column II (Metals)
I. Liquation	(a) Zr
II. Zone Refining	(b) Ni
III. Mond Process	(c) Sn
IV. Van Arkel Method	(d) Ga

[Watch Video Solution](#)

## Additional Practice Exercise Level II Lecture Sheet Advanced Integer Type Questions

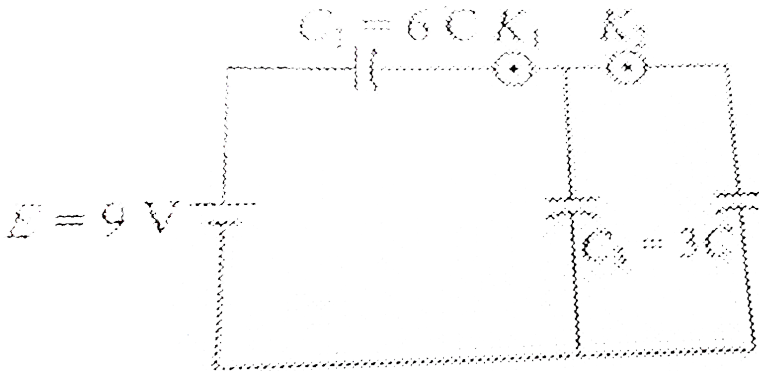1. In the circuit shown in the figure initially  $K_1$  is closed and  $K_2$  is open. What are the charges on each capacitor? Now  $K_1$  was opened and  $K_2$  was closed (order is important) what will be the charge on each capacitor now? [ $C = 1\mu F$ ]



[Watch Video Solution](#)


2. Two balls, each of radius  $R$ , equal mass and density, are placed in contact. Then the force of gravitation between them is proportional to:



[Watch Video Solution](#)

3. What amount of heat in micro joule will be generated in the circuit , after the switch is shifted from position 1 to position 2?

$$(C = C_0 = 2\mu F, E = \sqrt{6}V)$$

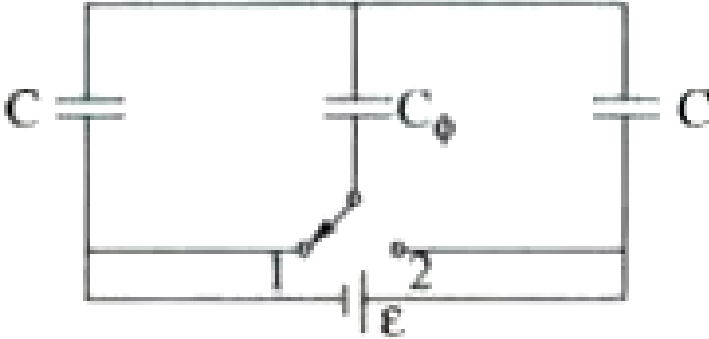


 [Watch Video Solution](#)

### Practice Sheet Advanced Straight Objective Type Questions

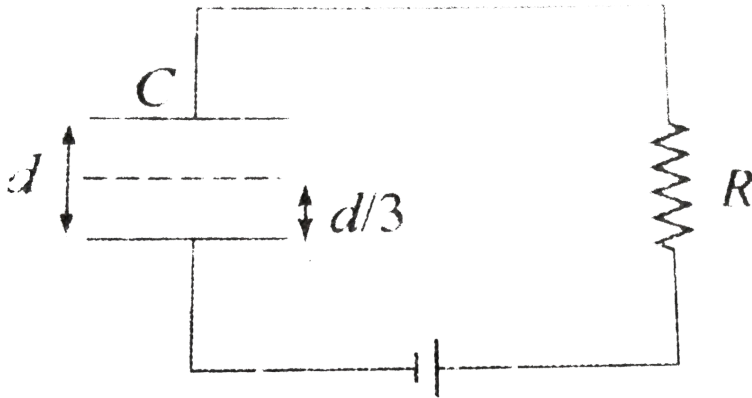1. A parallel plate capacitor  $C$  with plates of unit area and separation  $d$  is filled with a liquid of dielectric constant  $K = 2$ . The level of liquid is  $d/3$  initially. Suppose the liquid level decreases at a constant speed  $V$ . the



time constant as a function of time  $t$  is




- A.  $\frac{6\epsilon_0}{5d + 3vt}$
- B.  $\frac{(15d + 9vt)\epsilon_0}{2d^2 - 3dvt - 9v^2t^2}$
- C.  $\frac{6\epsilon_0}{5d - 3vt}$
- D.  $\frac{(15d - 9vt)\epsilon_0}{2d^2 + 3dvt - 9v^2t^2}$

Answer: A



Watch Video Solution

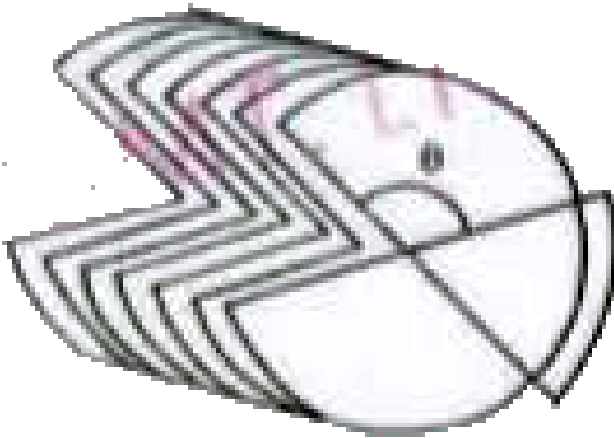2. A variable air capacitor used in radio tuning circuit is made of  $N$  semi-circular plates each of radius  $R$  and positioned a distance  $d$  from its neighboring plates. A second set of similar plates is enmeshed with its plates half-way between those of first set. Second set of plates can rotate as a complete unit. capacitance of arrangement is



- A.  $\frac{N\epsilon_0(\pi - \theta)R^2}{d}$
- B.  $\frac{(N - 1)\epsilon_0(\pi - \theta)R^2}{d}$
- C.  $\frac{(N - 2)\epsilon_0(\pi - \theta)R^2}{d}$
- D.  $\frac{(2N - 1)\epsilon_0(\pi - \theta)R^2}{d}$

**Answer: D**

 [Watch Video Solution](#)

3. A spherical capacitor composed of two concentric metal spheres one having a radius twice as large as the other. The region in which the energy is stored has a volume of

A.  $\frac{1}{4} \frac{c^3}{\pi^2 \epsilon_0^3}$

B.  $\frac{1}{16} \frac{c^3}{\pi^2 \epsilon_0^2}$

C.  $\frac{1}{384} \frac{c^3}{\pi^2 \epsilon_0^3}$


D.  $\frac{7c^3}{384\pi^2 \epsilon_0^2}$

**Answer: D**

 [Watch Video Solution](#)

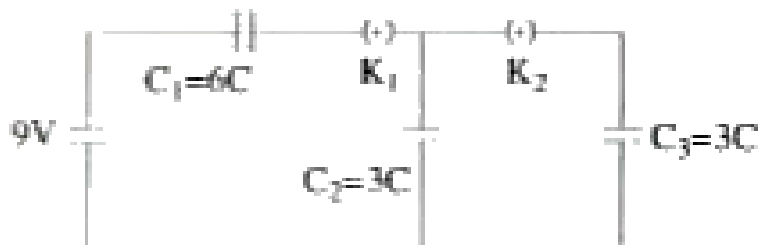4. In the circuit shown in figure, Initially  $K_1$  is closed and  $K_2$  is open, let charge on capacitor  $C_2$  is  $Q_2$  Then  $K_1$  was opened while  $K_2$  kept closed,

let charge on capacitor  $C_2$  is  $Q_2$  (Take,  $C = 1\mu F$ ) Then ratio  $\frac{Q_2}{Q_1}$  is




- A. 1 : 1
- B. 2 : 1
- C. 3 : 1
- D. 1 : 3

**Answer: B**

[Watch Video Solution](#)

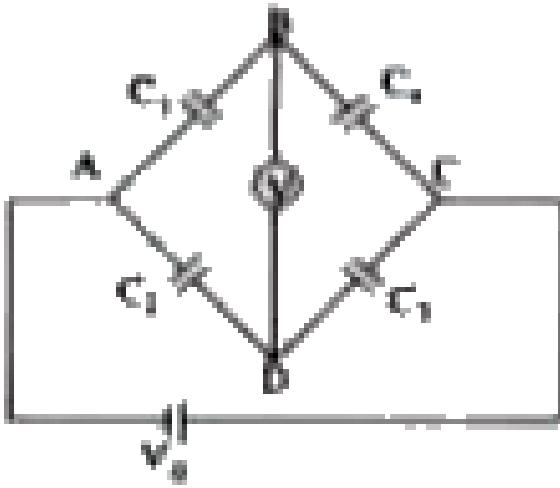5. In capacitor bridge, a voltage  $V_0$  is applied and the variable capacitor  $C_1$  has been adjusted till voltmeter shown zero reading. If

$C_1 = 8.9\mu F$ ,  $C_2 = 18\mu F$ ,  $C_3 = 4.8\mu F$  at balance point, then  $C_x$  is



A.  $5.4\mu F$

B.  $7.4\mu F$

C.  $2.4\mu F$


D.  $3.8\mu F$

**Answer: C**




**Watch Video Solution**

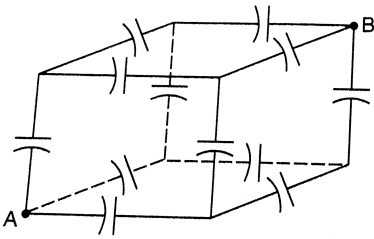6. Twelve capacitors, each having a capacitance  $C$ , are connected to form a cube. Find the equivalent capacitance between the diagonally opposite corners such as A and B.



(a)

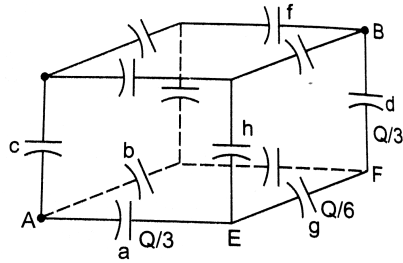

(b)

- A.  $\frac{3C}{4}$
- B.  $\frac{4C}{4}$
- C.  $\frac{3C}{2}$
- D.  $\frac{C}{2}$

Answer: B




Watch Video Solution

7. A combination of capacitors given is charged by a cell of emf  $E$  as shown :

If it is given that  $V_{ab}$  i.e. potential difference between points a and b is 4V, then answer the given questions.

EMF  $E$  of the charging battery is:

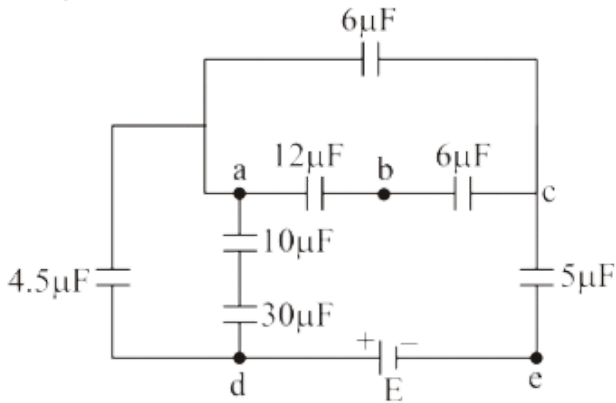


- A. 4V
- B. 12V
- C. 10V
- D. 8V

**Answer: C**

8. A combination of capacitors given is charged by a cell of emf  $E$  as shown :

If it is given that  $V_{ab}$  i.e. potential difference between points a and b is 4V, then answer the given questions.

EMF  $E$  of the charging battery is:

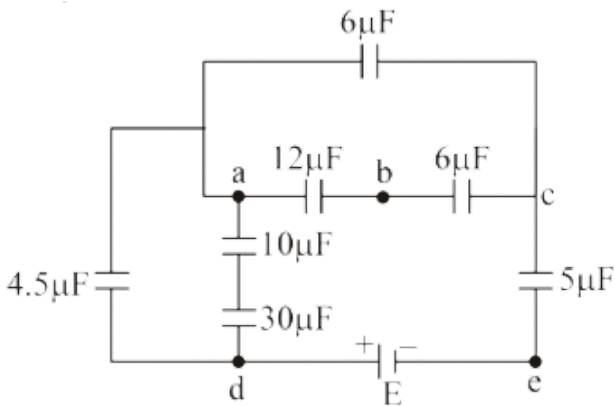

- A. 46V
- B. 12V
- C. 20V
- D. 18V

**Answer: A**



 [Watch Video Solution](#)

9. Match the refining methods (Column I) with (Column II).

Column I (Refining methods)	Column II (Metals)
I. Liquation	(a) Zr
II. Zone Refining	(b) Ni
III. Mond Process	(c) Sn
IV. Van Arkel Method	(d) Ga

 [Watch Video Solution](#)

## Practice Sheet Advanced Linked Comprehension Type Questions Passage

1. The liquid used in car radiator is primarily a mixture of ethylene glycol is that

A.  $\frac{2\pi\epsilon_0 l}{\ln(R_0 l R_i)} \left\{ (K_f - K_v) \frac{h}{l} + K_v \right\}$

B.  $\frac{2\pi\epsilon_0 l}{\ln(R_0 l R_i)} \left\{ (K_v - K_f) \frac{h}{l} + K_i \right\}$

C.  $\frac{2\pi\epsilon_0 l}{\ln(R_i l R_0)} \left\{ (K_v - K_l) \frac{h}{l} + K_v \right\}$

$$D. \frac{2\pi\epsilon_0 l}{\ln(R_i l R_0)} \left\{ (K_v - K_l) \frac{h}{l} + K_v \right\}$$


Answer: A



Watch Video Solution

### Practice Sheet Advanced Integer Type Questions

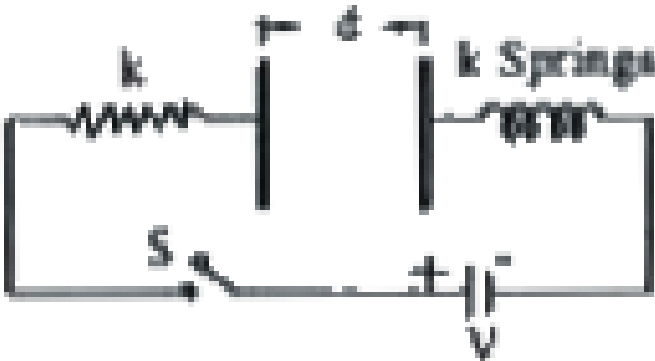1. In the given circuit, When switch S is opened, the plates are uncharged and are separated by distance  $d=8.00\text{mm}$ . Battery is of  $100\text{V}$  and springs are identical with spring constant  $K$ . Capacitance of capacitor with separation  $d=8\text{mm}$  is  $2\mu\text{F}$ . When switch S is closed, the distance between plates is reduced to  $4\text{mm}$ . Find the sum of spring constants of springs.





[Watch Video Solution](#)

2. A parallel plate capacitor is charged by a DC supply of 500V. Plate separation is 1mm. If capacitor is lowered into water with water filling in the gap between the plates, then change in pressure at any point between the plates is  $k\varepsilon_0 \times 10^{13} (N/m)^2$ . Find the value of K, given  $\varepsilon_r$  (for water)=81.



[Watch Video Solution](#)