



## PHYSICS

### BOOKS - AAKASH SERIES

### CURRENT ELECTRICITY

LECTURE SHEET (EXERCISE-I LEVEL-1(MAIN) (Straight Objective Type Questions))

1. An electron of mass  $m$ , moves around the nucleus in a circular orbit of radius  $r$ . under the action of centripetal force  $F$ . The equivalent electric current is

A.  $\frac{e}{2\pi} \sqrt{\frac{F}{mr}}$

B.  $2\pi e \sqrt{\frac{F}{mr}}$

C.  $\frac{e}{\pi} \sqrt{\frac{F}{mr}}$

D.  $\frac{e}{2\pi} \sqrt{\frac{mr}{F}}$

**Answer: A**



**Watch Video Solution**

2. A copper conductor of area of cross-section  $40 \text{ mm}^2$  on a side carries a constant current of  $32 \times 10^{-6} \text{ A}$ . Then the current density is (in  $\text{amp}/\text{m}^2$ )

A. 1.6

B. 0.8

C. 0.4

D. 3.2

**Answer: B**



**Watch Video Solution**

3. Positive and negative ions are produced in the atmosphere due to cosmic rays from space and also due to radioactive elements in the soil. In some region in the atmosphere, the electric field strength is  $100V/m$  in the vertically downward direction. This field exerts force on the positive and negative ions in

the given region in atmosphere. As a result, positive ions, having a density  $500/cm^3$  drift downward while negative ions, having a density  $300/cm^3$  drift upward. All these ions are singly charged. It is observed that the conductivity in the given region is  $4 \times 10^{-13}(\Omega - m)^{-1}$ . Find the average speed of ions, assuming it to be the same for positive and negative ions.

A.  $1.3m/s$

B.  $0.31m/s$

C.  $0.93m/s$

D.  $1.6 m/s$

**Answer: B**



Watch Video Solution

4. Electric current through a conductor varies with time as  $I(t) = 50 \sin(100\pi t)$ . Here  $I$  is in amperes and  $t$  in seconds. Total charge that passes any point from  $t = 0$  to  $t = \frac{1}{200}$  s is

A. 1.2 C

B. 0.36 C

C. 0.159 C

D. 0.02 C

**Answer: C**



Watch Video Solution

5. A current of  $(2.5 \pm 0.05)$  A flows through a wire and develops a potential difference of  $(10 \pm 0.07)$  volt.

Resistance of the wire in ohm, is

A.  $4 \pm 0.108$

B.  $4 \pm 0.04$

C.  $4 \pm 0.1104$

D.  $4 \pm 0.02$

**Answer: C**



Watch Video Solution

6. The current in a conductor varies with time  $t$  as  $I = 3t + 4t^2$ . Where  $I$  in amp and  $t$  in sec. The electric charge flows through the section of the conductor between  $t = 1\text{s}$  and  $t = 3\text{s}$

A.  $\frac{14}{3}$  C

B.  $\frac{3}{14}$  C

C.  $\frac{140}{3}$  C

D.  $\frac{3}{140}$  C

**Answer: C**



**Watch Video Solution**



# LECTURE SHEET (EXERCISE-I LEVEL- II (ADVANCED) (Straight Objective Type Questions))

1. The charge flowing in a conductor varies with time as

$$Q = at - \frac{1}{2}bt^2 + \frac{1}{6}ct^3 \text{ where } a, b \text{ and } c \text{ are positive constants.}$$


If at time  $t$ , the current in the conductor is  $i$ ,

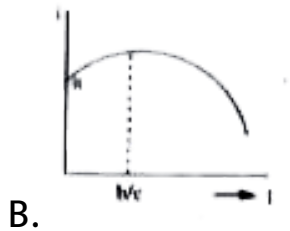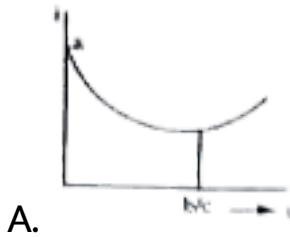which of the following graphs is correct ?






C.

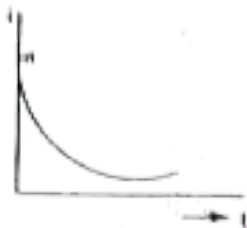

D.

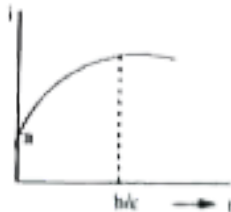

**Answer: A**



**Watch Video Solution**

2. Potential difference that is applied across a conductor of resistance  $R$  varies with time  $t$  according to the equation  $V(t) = V_0 e^{-t/z}$  where  $z$  is a constant that has dimensions of time. Obviously, the

applied potential difference decreases exponentially with time. Charge that passes through any fixed observation point within the conductor between  $t=0$  and  $t=z$  will be

A.  $\frac{V_0}{R}$

B.  $0.368 \frac{V_0}{R}$

C.  $0.632 \frac{V_0 z}{R}$

D.  $0.368 \frac{V_0 z}{R}$

**Answer: C**



**Watch Video Solution**

3. An electric current passes through a circuit containing two wires of the same material connected in parallel. If the lengths of the wires are in the ratio of  $4/3$  and radius of the wires are in the ratio of  $2/3$ , then the ratio of the currents passing through the wires will be :

A. 3

B. 2

C.  $8/9$

D.  $1/3$

**Answer: D**



**Watch Video Solution**

4. Two wires of the same material have length 6cm and 10cm and radii 0.5 mm and 1.5 mm respectively. They are connected in series across a battery of 16 V. The p.d. across the shorter wire is

- A. 5V
- B. 13.5 V
- C. 27 V
- D. 10 V


**Answer: B**



**Watch Video Solution**

LECTURE SHEET (EXERCISE-I LEVEL- II (ADVANCED) (More than one correct answer type Questions))

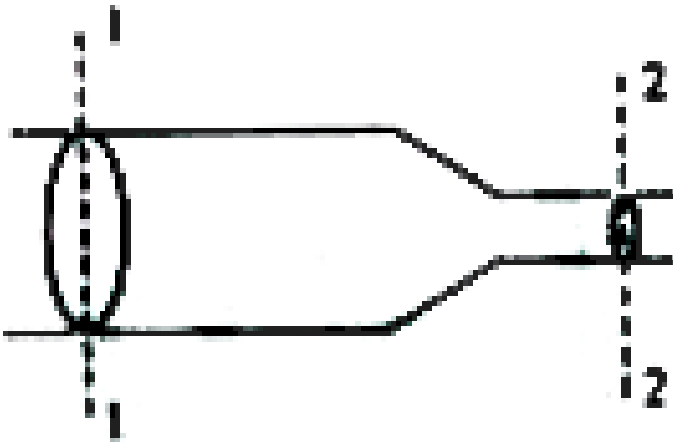1. The area of cross section of a current carrying conductor is  $A_0$  and  $\frac{A_0}{4}$  at section (1) and (2) respectively. If  $v_{\alpha_1}$ ,  $v_{\alpha_2}$  and  $E_1$ ,  $E_2$  be the drift velocity and electric field at sections 1 and 2 respectively then :



A.  $v_{\alpha_1} : v_{\alpha_2} = 1 : 4$

B.  $v_{\alpha_1} : v_{\alpha_2} = 4 : 1$

C.  $E_1 : E_2 = 4 : 1$

D.  $E_1 : E_2 = 1 : 4$

**Answer: A::D**



**Watch Video Solution**

2. A current passes through a wire of nonuniform cross-section. Which of the following quantities are independent of the cross section?

A. the charge crossing in a given time interval

B. drift speed

C. current density

## D. free- electron density

Answer: A::D

 [Watch Video Solution](#)

### 3. Match Column - I with Column - II

#### COLUMN - I

- A) Electrical conductivity of a conductor depends on
- B) Conductance of a conductor depends on
- C) For a given conductor and at a given temperature, current density depends on
- D) For a given potential difference applied across a conductor, current in it will depend on

#### COLUMN - II

- p) dimensions (length and area of cross-section)
- q) temperature
- r) nature of conductor
- s) electric field strength

 [Watch Video Solution](#)

LECTURE SHEET (EXERCISE- II LEVEL-I (MAIN) (Straight Objective Type Questions))

1. The resistance of the wire is 121 ohm. It is divided into  $n$  equal parts and they are connected in parallel, then effective resistance is 1 ohm. The value of  $n$  is

A. 12

B. 13

C. 11

D. 3

**Answer: C**



**Watch Video Solution**



2. The resultant resistance of two resistance in series is  $50\ \Omega$  and it is  $12\ \Omega$  , when they are in parallel. The individual resistances are

A.  $20\ \Omega$  and  $15\ \Omega$

B.  $15\ \Omega$  and  $30\ \Omega$

C.  $20\ \Omega$  and  $30\ \Omega$

D.  $10\ \Omega$  and  $15\ \Omega$

**Answer: C**



**Watch Video Solution**

3. A conductor of resistance  $3\Omega$  is stretched uniformly till its length is doubled . The wire is now bent in the form of an equilateral triangle . The effective resistance between the ends of any side of the triangle in ohms is

A.  $\frac{9}{2}\Omega$

B.  $\frac{8}{3}\Omega$

C.  $2\Omega$


D.  $1\Omega$

**Answer: B**



**Watch Video Solution**

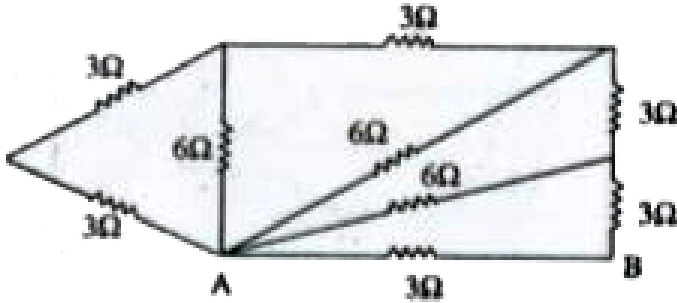4. The effective resistance between A and B is the given circuit is




- A.  $2\Omega$
- B.  $3\Omega$
- C.  $9\Omega$
- D.  $6\Omega$

Answer: A

 Watch Video Solution

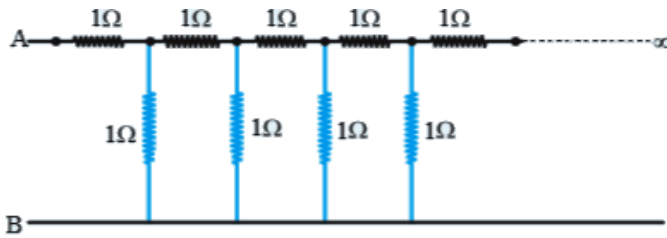5. The equivalent resistance between points A and B of an infinite network of resistance, each of  $1\Omega$  connected as shown is`



A. infinite

B.  $2\Omega$

C. zero


D.  $\left( \frac{1 \pm \sqrt{5}}{2} \right)$

**Answer: D**



**Watch Video Solution**

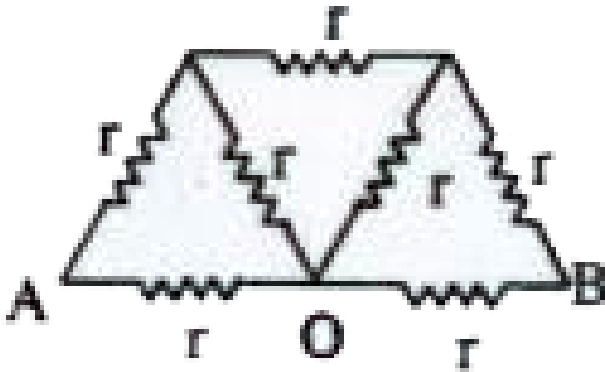6. Equivalent resistance across A and B in the given circuit is




- A.  $7r$
- B.  $8r/7$
- C.  $4r/7$
- D.  $7r/8$

Answer: B

 Watch Video Solution

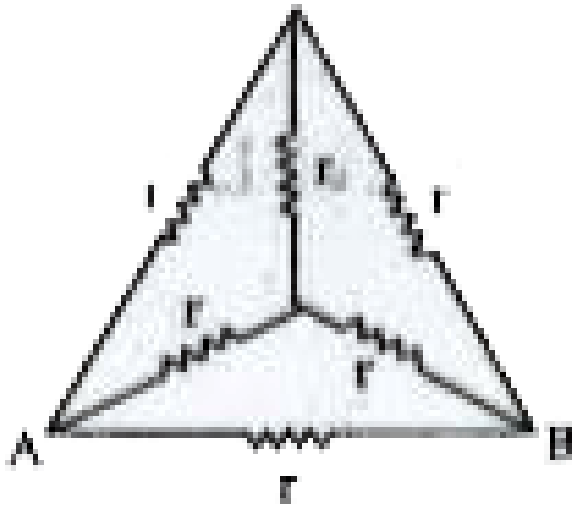7. Effective resistance between A and B in the given circuit it is



A.  $6r$

B.  $r$


C.  $2r$

D.  $r/2$

**Answer: D**

 [Watch Video Solution](#)

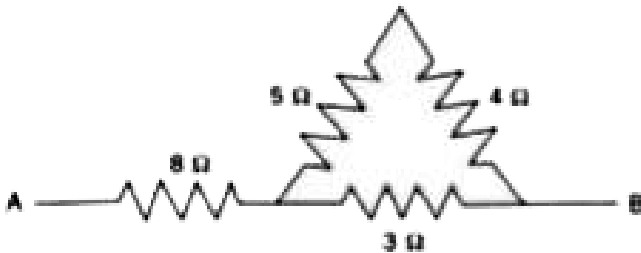**8.** Calculate the effective resistance across AB :



A.  $r$

B.  $2r$


C.  $r/2$

D.  $r/4$

**Answer: C**

 [Watch Video Solution](#)

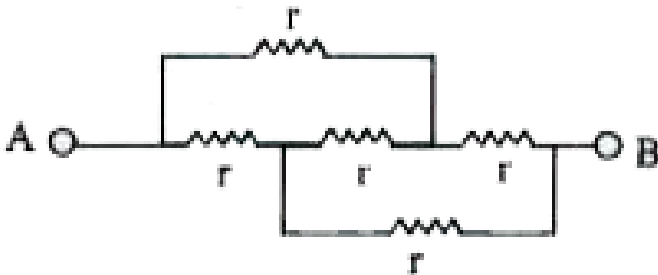9. Effective resistance between A and B in the given circuit is



A.  $r$



B.  $3r$

C.  $5r$


D.  $4r$

**Answer: A**



**Watch Video Solution**

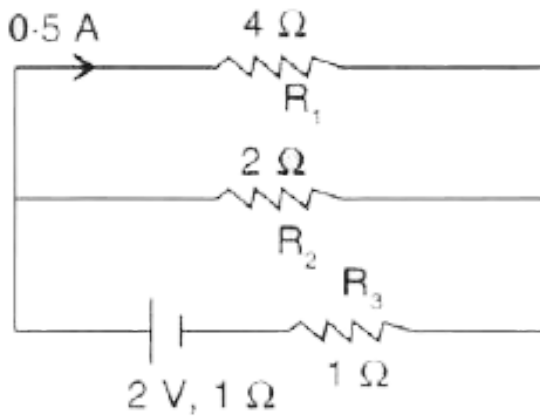**10.** In an electric circuit shown alongside, find



terminal voltage of the battery

A.  $4\Omega$

B.  $2\Omega$

C.  $3\Omega$

D.  $1\Omega$

**Answer: C**



[Watch Video Solution](#)

11. An aluminium ( $\alpha_{Al} = 4 \times 10^{-3} / ^\circ C$ ) wire resistance  $. R_1.$  and carbon wire ( $\alpha_c = 0.5 \times 10^{-3} / ^\circ C$ ) resistance  $. R_2.$  are connected in series to have a

resultant resistance of 18 ohm at all temperatures The values of  $R_1$  and  $R_2$  in ohms

A. 2, 16

B. 12, 6

C. 13, 5

D. 14, 4

**Answer: A**



**Watch Video Solution**

**12.** A carbon and an aluminium wire are connected in series. If the combination has resistance of  $30\Omega$  at

$30^\circ C$ , what is the resistance of each wire at  $0^\circ C$  so that resistance of the combination does not change with temperature.

$$(a_c = -0.5 \times 10^{-3} / ^\circ C, a_A = 4 \times 10^{-3} / ^\circ C)$$

A.  $120\Omega$

B.  $15\Omega$

C.  $60\Omega$

D.  $210\Omega$

**Answer: B**



**Watch Video Solution**

13. The resistance of a metal wire is  $10\Omega$ . A current of 30 mA is flowing in it at  $20^\circ\text{C}$ . If p.d. across its ends is constant, then its temperature is increased to  $120^\circ\text{C}$ , then the current flowing in the wire will be in mA  $(\alpha = 5 \times 10^{-3}/^\circ\text{C})$

A. 20

B. 15

C. 10

D. 40

**Answer: A**



**Watch Video Solution**

14. Two resistors with temperature coefficients of resistance  $\alpha_1$  and  $\alpha_2$  have resistances  $R_{01}$  and  $R_{02}$  at  $0^\circ C$ . Find the temperature coefficient of the compound resistor consisting of the two resistors connected.

a.. In series and

b. in parallel

A.  $\frac{R_1\alpha_1 + R_2\alpha_2}{R_1 + R_2}$

B.  $\frac{\alpha_1 + \alpha_2}{2}$

C.  $\frac{2\alpha_1\alpha_2}{\alpha_1 + \alpha_2}$

D.  $\frac{R_1\alpha_2 + R_2\alpha_1}{R_1 + R_2}$

**Answer: D**



Watch Video Solution

**LECTURE SHEET (EXERCISE- II LEVEL- II (ADVANCED))**  
**(Straight Objective Type Questions)**

1. A coaxial cable is made up of two conductors. The inner conductor is solid is of radius  $R_1$  and the outer conductor is hollow of inner radius  $R_2$  and outer radius  $R_3$  . The space between the conductors are carrying currents of equal magnitudes and in oppsite direactions. then the variation of magnetic field with distance form the axis is best plotted as :



A.  $\frac{\rho}{4\pi} \frac{ab}{(b-a)}$

B.  $\frac{\rho(b-a)}{4\pi ab}$

C.  $\frac{4\pi ab}{\rho(b-a)}$

D.  $\frac{\rho(b-a)}{2\pi ab}$

**Answer: B**



**Watch Video Solution**

2. A material of resistivity  $\rho$  is formed in the shape of a truncated cone of altitude  $h$ . The top end has a radius  $a$  while bottom  $b$ . Assuming a uniform current density through any circular cross-section of the cone. Find the



resistance between the two ends.



A.  $\frac{\rho}{2\pi} \frac{h}{ab}$

B.  $\frac{2\rho}{\pi} \frac{h}{ab}$

C.  $\frac{\rho}{\pi} \frac{h}{ab}$

D.  $\frac{\rho}{\pi} \frac{h}{(a + b)}$

**Answer: C**



**Watch Video Solution**

3. The cross-section area and length of cylindrical conductor are  $A$  and  $l$  respectively. The specific conductivity varies as  $\sigma(x) = \sigma_0 \frac{l}{\sqrt{x}}$ , where  $x$  is the distance along the axis of the cylinder from one of its ends. Compute the resistance of the system along the cylindrical axis.

A.  $\frac{3\sqrt{l}}{2A\sigma_0}$

B.  $\frac{2l}{3A\sigma_0}$

C.  $\frac{2\sqrt{l}}{3A\sigma_0}$

D.  $\frac{\sqrt{l}}{A\sigma_0}$

Answer: C



Watch Video Solution

4. Potential in the x-y plane is given as  $V = 5(x^2 + xy)$  volts. Find the electric field at the point (1, -2).

A.  $j_-(0)A/3$

B.  $\frac{\sigma_0 V_0}{\sqrt{x}}, \frac{V_0 \sqrt{x}}{2l^{3/2}}$

C.  $\frac{2}{3} \frac{\sigma_0 V_0}{\sqrt{x}}, \frac{2}{3} \frac{V_0 \sqrt{x}}{l^{3/2}}$

D.  $\frac{3\sigma_0 V_0}{2\sqrt{l}}, \frac{3V_0 \sqrt{x}}{2l^{3/2}}$

**Answer: D**



**Watch Video Solution**

5. A thin wire of length  $L$  and cross-sectional area  $A$  oriented in the  $x$ -direction is made up of an ohmic material whose resistivity varies along the wire according to the empirical law  $\rho = \rho_0 e^{-x/lL}$

(i) Determine how the field within wire varies with position if the end at  $x=0$  is at potential  $V_0$  greater than the end at  $x=L$ .

(ii) How does potential varies as you move along the wire ?

(lii) What is resistance of the wire ?

A.  $\frac{\rho_0 L}{A} \left( \frac{1}{e} \right)$

B.  $\frac{\rho_0 L}{A} (e)$

C.  $\frac{\rho_0 L}{A} \left( 1 - \frac{1}{e} \right)$

D.  $\frac{\rho_0 L}{A} (e - 1)$


**Answer: C**



**Watch Video Solution**

6. In the diagram, resistance between any two junction is R. Equivalent resistance across terminals A and B is

(assume P and Q also as junction)

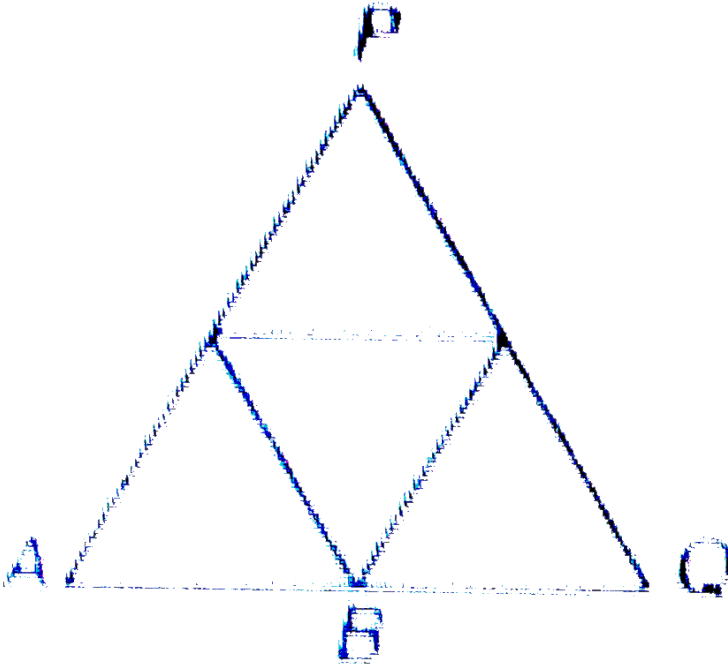

A.  $\frac{11R}{7}$

B.  $\frac{18R}{11}$

C.  $\frac{7R}{11}$

D.  $\frac{11R}{18}$


**Answer: D**



**Watch Video Solution**

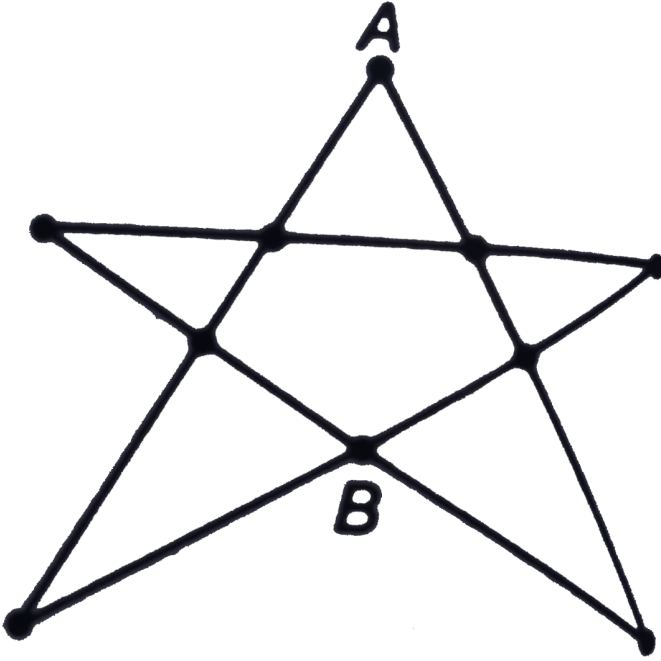7. The resistance of all the wires between any two adjacent dots is  $R$ . Then, equivalent resistance

between  $A$  and  $B$  as shown in figure is



A.  $7/3R$

B.  $7/6R$

C.  $14/8R$

D. None of these




Answer: B



Watch Video Solution

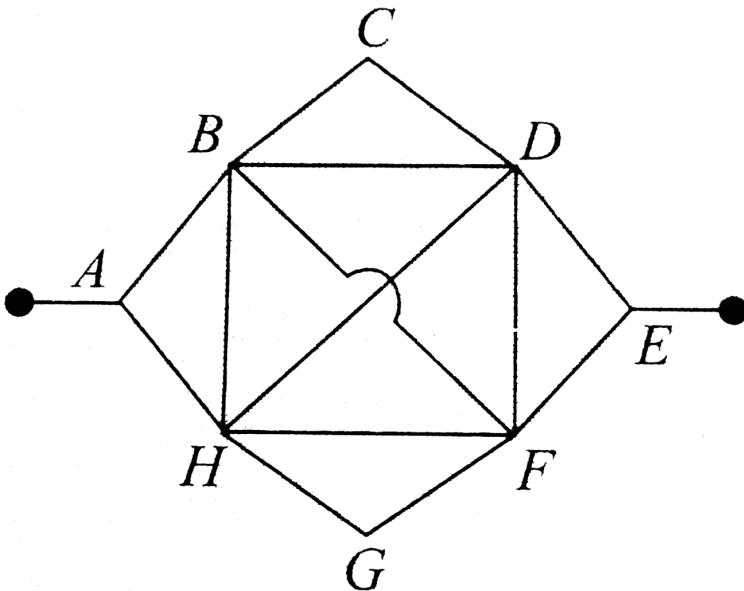8. Identical resistor each of resistance  $r$  are connected as shown in figure. Calculate equivalent resistance between A and E.



A.  $\frac{r}{2}$

B.  $3r$

C.  $1.2 r$


D.  $1.5 r$

**Answer: C**



**Watch Video Solution**

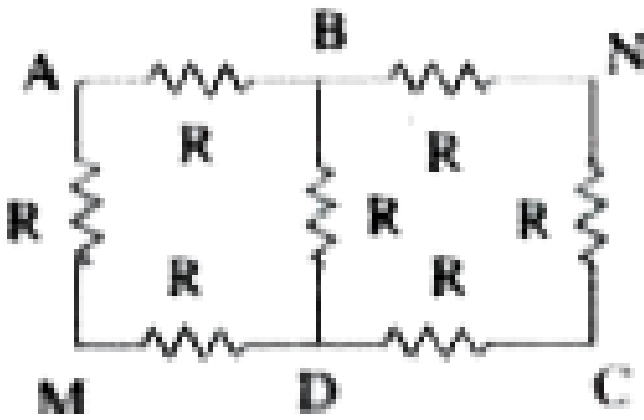**9.** What is the equivalent resistance between point A and C in the circuit shown in fig. ?



A.  $\frac{4R}{3}$

B.  $\frac{11R}{15}$

C.  $2R$


D.  $\frac{7R}{5}$

**Answer: D**



**Watch Video Solution**

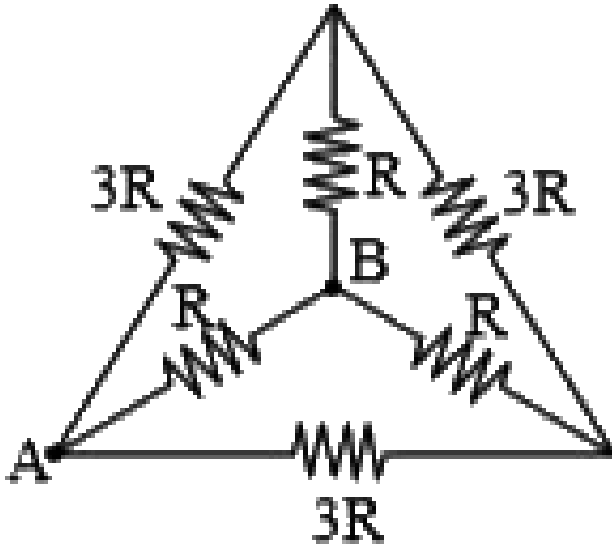10. Six resistances are connected as shown here. The effective resistance between points A and B is -




- A.  $\frac{18}{11} \Omega, \frac{621}{550} \Omega, \frac{12}{11} \Omega$
- B.  $\frac{18}{11} \Omega, \frac{441}{550} \Omega, \frac{621}{550} \Omega$
- C.  $\frac{36}{11} \Omega, \frac{25}{630} \Omega, \frac{13}{11} \Omega$
- D.  $\frac{9}{11} \Omega, \frac{22}{55} \Omega, \frac{62}{55} \Omega$

Answer: B




Watch Video Solution

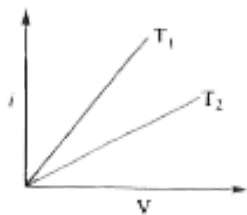
11. If  $k_1$  rate constant at temperature  $T_1$  and  $k_2 =$  rate constant at temperature  $T_2$  for a first order reaction, then which of the following relations is correct? ( $E_a$  : activation energy)




A.

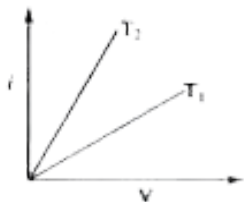

B.

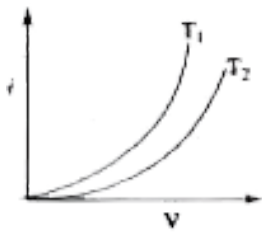

C.

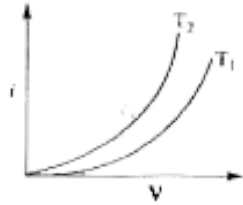

D.

**Answer: A**



**Watch Video Solution**

**LECTURE SHEET (EXERCISE- II LEVEL- II (ADVANCED) (Linked Comprehension Type Questions))**

### 1. Passage :

The thermal coefficient of resistivity is given by

$\alpha = \frac{1}{\rho} \frac{d\rho}{dT}$  where  $\rho$  is resistivity at a temperature T.  $\alpha$

is not constant, rather varies as  $\alpha = \frac{-n}{T}$ , where T is

temperature in Kelvin and n is a constant. For carbon

$\alpha = -0.0005K^{-1}$  and  $\rho = 3.5 \times 10^{-5}(\Omega - m)$  at  $27^\circ C$

Find the value of .n. for carbon

A.  $\rho \propto T^n$

B.  $\rho \propto T^{n-1}$

C.  $\rho \propto T^{-n}$

D.  $\rho \propto \frac{n}{T}$

**Answer: C**



Watch Video Solution

## 2. Passage :

The thermal coefficient of resistivity is given by

$\alpha = \frac{1}{\rho} \frac{d\rho}{dT}$  where  $\rho$  is resistivity at a temperature T.  $\alpha$

is not constant, rather varies as  $\alpha = \frac{-n}{T}$ , where T is

temperature in Kelvin and n is a constant. For carbon

$\alpha = -0.0005K^{-1}$  and  $\rho = 3.5 \times 10^{-5}(\Omega - m)$  at  $27^\circ C$

Find the value of .n. for carbon

A. 0.15

B. 0.3

C. 0.9



D. 0.6

**Answer: A**







**Watch Video Solution**

## LECTURE SHEET (EXERCISE- II LEVEL- II (ADVANCED) (Matrix Matching Type Questions))

1. Each figure in Column - I shows the variation of resistance with temperature. Some materials are mentioned in Column - II. Match Column - I with

## Column - II.

### COLUMN - I

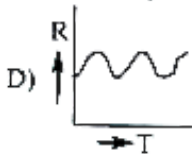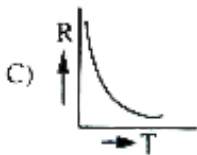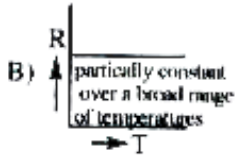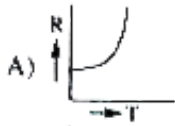

### COLUMN - II

p) Manganin

q) Graphite

r) Copper

s) Silicon

t) none.



[Watch Video Solution](#)

LECTURE SHEET (EXERCISE-III LEVEL- I (MAIN) (Straight Objective Type Questions))

1. The emf of a storage battery is  $90V$  before charging and  $100V$  after charging. When charging began the current was  $10A$ . What is the current at the end of charging if the internal resistance of the storage battery during the whole process of charging may be taken as constant and equal to  $2\Omega$ ?

- A.  $5A$
- B.  $10A$
- C.  $15 A$
- D.  $20 A$

**Answer: A**



**Watch Video Solution**

2. How will you connect ( series and parallel ) 24 cells each of internal resistance  $1\Omega$  to get maximum power output across a load of  $10\Omega$ ?

A.  $a = 6, b = 4$

B.  $a = 8, b = 3$

C.  $a = 2, b = 12$


D.  $a = 1, b = 24$

**Answer: C**



**Watch Video Solution**

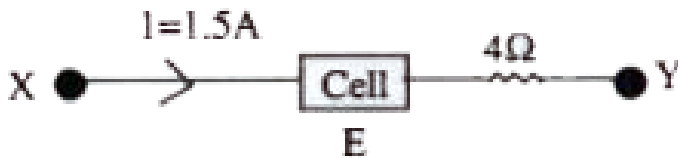3. Fig. shows a part of circuit. When a current  $I = 1.5 \text{ A}$  passes through it in the direction shown, power delivered to it (section XY) is  $75 \text{ W}$ . Potential difference between X and Y and also the emf  $E$  of the cell are respectively (assume that the cell has a negligible internal resistance)





- A.  $50 \text{ V}, 44 \text{ V}$
- B.  $50 \text{ V}, 48 \text{ V}$
- C.  $36 \text{ V}, 50 \text{ V}$
- D.  $48 \text{ V}, 50 \text{ V}$



Answer: A



Watch Video Solution

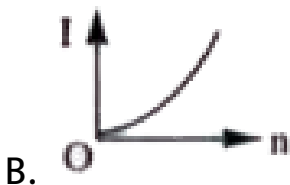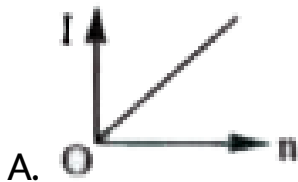4. A battery consists of a variable number ( $n$ ) of identical cells, each having an internal resistance  $r$  connected in series. The terminals of the battery are short - circuited. A graph of current versus the number of cell will be:





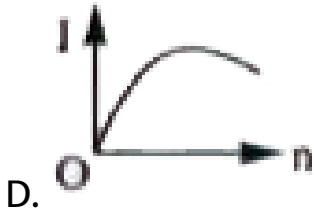
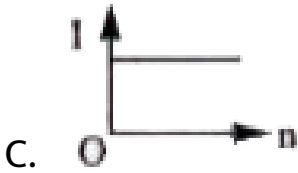


**Answer: D**



**Watch Video Solution**

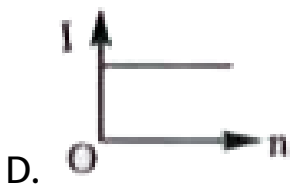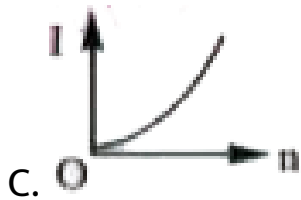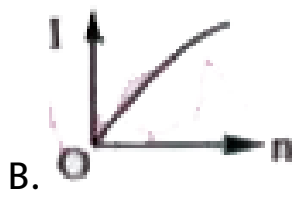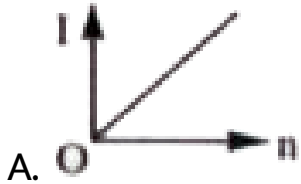5. if the cell had been connected in parallel (instead of in series) which of the graphs would have shown the relationship between total current  $I$  and  $n$ ?







**Answer: A**

 [Watch Video Solution](#)



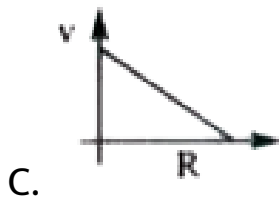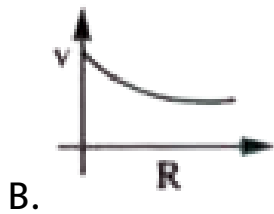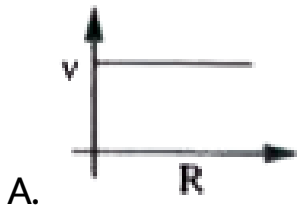6. A cell having an emf  $E$  and internal resistance  $r$  is connected across a variable external resistance  $R$ . As the resistance  $R$  is increased, the plot of potential difference  $V$  across  $R$  is given by



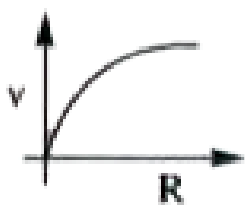


D.

Answer: D

 Watch Video Solution

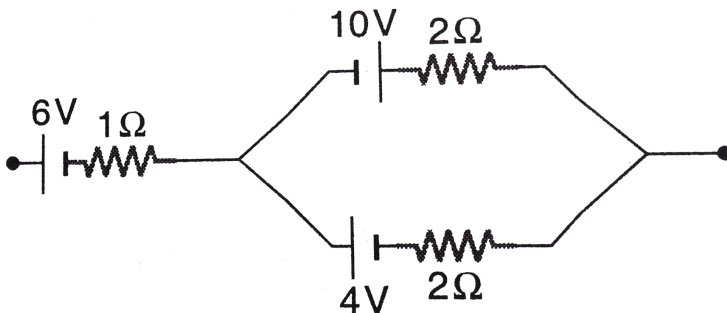7. Find the emf and internal resistance of a single battery which is equivalent to a combination of three batteries as show in figure.



A.  $3\text{V}, 5\Omega$

B.  $3\text{V}, 2\Omega$

C.  $7\text{V}, 2\Omega$

D.  $20\text{V}, 5\Omega$

**Answer: B**




**Watch Video Solution**

**LECTURE SHEET (EXERCISE-III LEVEL- II (ADVANCED))  
(Straight Objective Type Questions)**

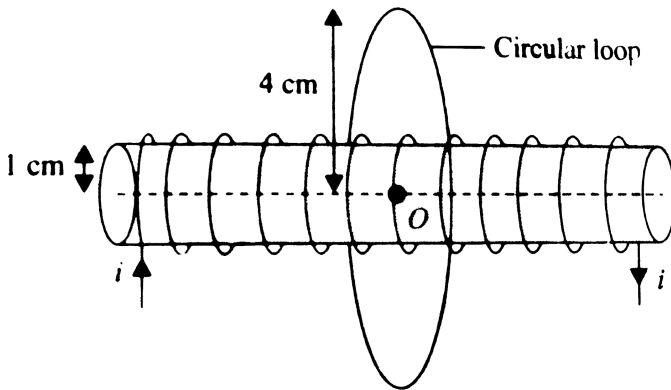1. A long solenoid having  $n = 200$  turns per metre has a circular cross-section of radius  $a_1 = 1\text{cm}$ . A circular

conducting loop of radius  $a_2 = 4\text{cm}$  and resistance  $R = 5(\Omega)$  encircles the solenoid such that the centre of circular loop coincides with the midpoint of the axial line of the solenoid and they have the same axis as shown in Fig.



A current 't' in the solenoid results in magnetic field along its axis with magnitude  $B = (\mu)ni$  at points well inside the solenoid on its axis. We can neglect the insignificant field outside the solenoid. This results in a magnetic flux  $(\phi)_B$  through the circular loop. If the

current in the winding of solenoid is changed, it will also change the magnetic field  $B = (\mu)_0 ni$  and hence also the magnetic flux through the circular loop. Obviously, it will result in an induced emf or induced electric field in the circular loop and an induced current will appear in the loop. Let current in the winding of solenoid be reduced at a rate of  $75A / \text{sec}$ .

When the current in the solenoid becomes zero so that external magnetic field for the loop stops changing, current in the loop will follow a differential equation given by [You may use an approximation that field at all points in the area of loop is the same as at the centre

A. Only one value of R exist for which potential difference across battery having internal

resistance  $r_1$  is zero

B. Only one value of R exist for which potential difference across battery having internal

resistance  $r_2$  is zero

C. No value of R exist for which potential difference across any of the battery is zero

D. For all values of R potential difference across both the batteries would be zero

**Answer: A**



**Watch Video Solution**

2. The two batteries of emf  $E_1$  and  $E_2$  having internal resistances  $r_1$  and  $r_2$  respectively are connected in series to an external resistor  $R$ . Both the batteries are getting discharged. The above described combination of these two batteries has to produce a weaker current than when any one of the battery is connected to same resistor. For this requirement to be fulfilled.


- A.  $\frac{E_2}{E_1}$  must not lie between  $\frac{r_2}{r_1 + R}$  and  $\frac{r_2 + R}{r_1}$
- B.  $\frac{E_2}{E_1}$  must lie between  $\frac{r_2}{r_1 + R}$  and  $\frac{r_2 + R}{r_1}$
- C.  $\frac{E_2}{E_1}$  must lie between  $\frac{r_2}{r_1 + R}$  and  $\frac{r_1}{r_2 + R}$
- D.  $\frac{E_2}{E_1}$  must not lie between  $\frac{r_2}{r_1 + R}$  and  $\frac{r_1}{r_2 + R}$

**Answer: A**



Watch Video Solution

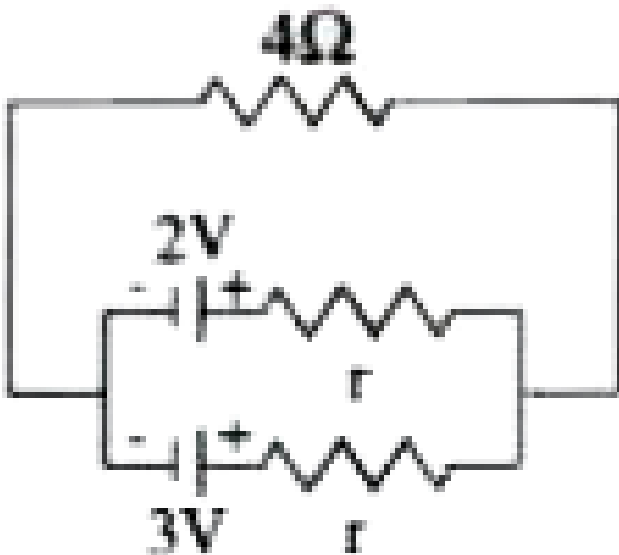3. Two cell with unequal emfs of 2V and 3V are connected as shown in the figure. If each cell has an internal resistance  $r = 0.45\Omega$  and external resistance is of  $4\Omega$ . Then, Potential drop across resistor  $4\Omega$  is



A. 5.32V



B. 2.37V

C. 3.28V


D. 1.5V

**Answer: B**



**Watch Video Solution**

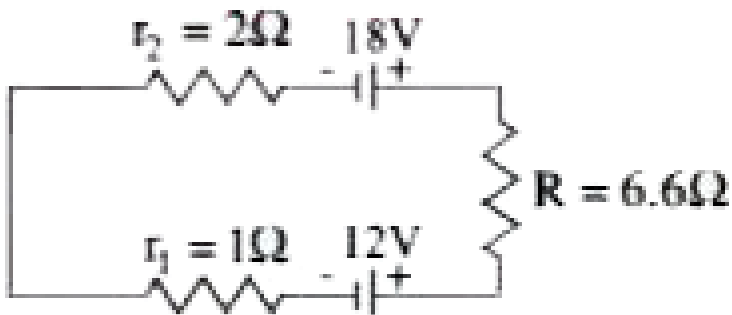4. For the given circuit, terminal potential differences of cells are around



A. 15V,10V

B. 12V, 15V

C. 6V, 12V


D. 17V, 13V

**Answer: D**



**Watch Video Solution**

5. For the given circuit,

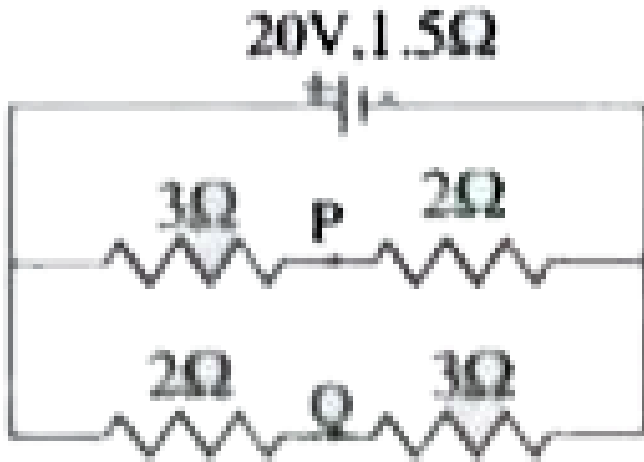

If internal resistance of cell is  $1.5\Omega$ , then

- A.  $V_P - V_Q = 0$
- B.  $V_P - V_Q = 4V$
- C.  $V_P - V_Q = -4V$
- D.  $V_P - V_Q = -2.5V$

**Answer: D**




**Watch Video Solution**

## **LECTURE SHEET (EXERCISE-III LEVEL- II (ADVANCED) (Linked Comprehension Type Questions)**

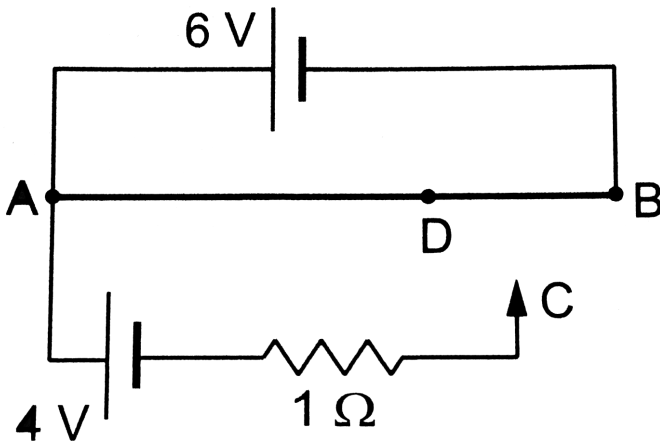1. A 6-volt battery of negligible internal resistance is connected across a uniform wire AB of length 100cm. The positive terminal of another battery of emf 4V and internal resistance  $1(\Omega)$  is joined to the point A as shown in figure. Take the potential at B to be zero. (a) What are the potentials at the points A and C ? (b) At which point D of the wire AB, the potential is equal to

the potential at C? (c) If the point C and D are connected by a wire, what will be the current through it? (d) If the 4V battery is replaced by 7.5V battery, what would be the answer of parts (a) and (b)?



- A. 6V, 2V
- B. 8V, 4V
- C. 6V, 4V
- D. 8V, 3V


**Answer: A**



**Watch Video Solution**

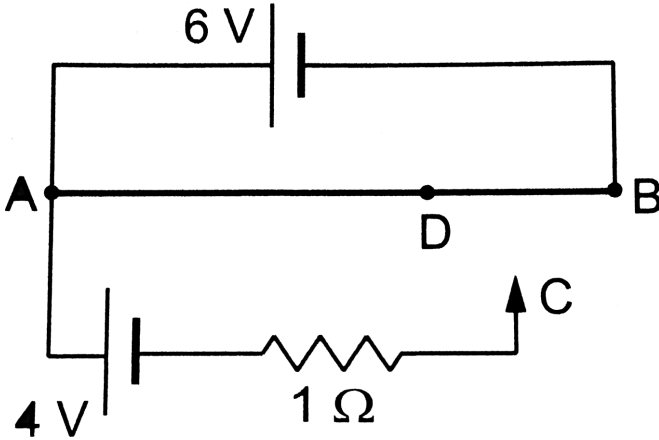2. A 6-volt battery of negligible internal resistance is connected across a uniform wire AB of length 100cm. The positive terminal of another battery of emf 4V and internal resistance  $1(\Omega)$  is joined to the point A as shown in figure. Take the potential at B to be zero. (a) What are the potentials at the points A and C? (b) At which point D of the wire AB, the potential is equal to the potential at C? (c) If the point C and D are connected by a wire, what will be the current through it? (d) If the 4V battery is replaced by 7.5V battery, what

would be the answer of parts (a) and (b) ?



A.  $AD = 60 \text{ cm}$

B.  $AD = 50 \text{ cm}$

C.  $AD = 40 \text{ cm}$


D.  $AD = \frac{200}{3} \text{ cm}$

**Answer: D**

 [Watch Video Solution](#)

LECTURE SHEET (EXERCISE-IV LEVEL - I (MAIN) (Straight Objective Type Questions))

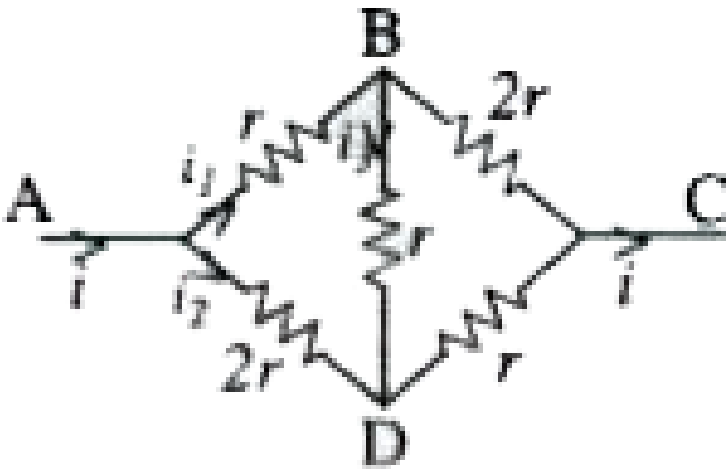1. The value of current  $i_1$  in the given circuit is



A.  $\frac{i}{5}$

B.  $\frac{2i}{5}$

C.  $\frac{3i}{5}$




D.  $\frac{4i}{5}$

Answer: C

 Watch Video Solution

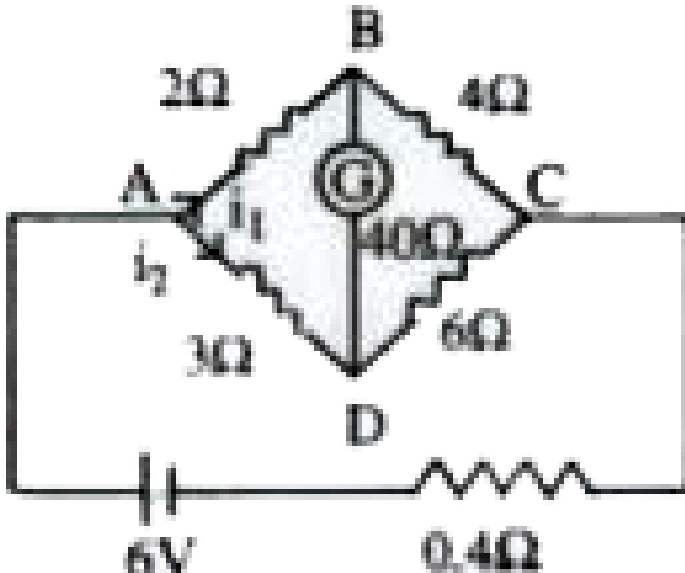2. A balanced wheatstone bridge is shown the values of currents  $i_1$  and  $i_2$  are



A. 0.9A, 0.6A

B. 0.3A, 0.2A

C. 0.5A, 0.7A

D. 0.7A, 0.6A

**Answer: A**



**Watch Video Solution**

3. A metallic conductor at  $10^{\circ}C$  connected in the left gap of Meter Bridge given balancing length 40cm. When the conductor is at  $60^{\circ}C$ , the balancing point shifts by \_\_cm, (temperature coefficient of resistance of the material of the wire is  $(1/220)/^{\circ}C$ )

A. 4.8

B. 8.7

C. 15

D. 7

**Answer: A**



**Watch Video Solution**

4. Two unknown resistances  $X$  and  $Y$  are connected to left and right gaps of a meter bridge and the balancing point is obtained at 80cm from left. When a  $10\Omega$  resistance is connected parallel to  $X$ , the balancing

point is 50cm from left. The values of X and Y respectively are

A.  $40\Omega$ ,  $9\Omega$

B.  $30\Omega$ ,  $7.5\Omega$

C.  $20\Omega$ ,  $6\Omega$

D.  $10\Omega$ ,  $3\Omega$

**Answer: B**



**Watch Video Solution**

5. In a metre bridge, the balance length from left end (standard resistance of  $1\Omega$  is in the right gap) is found

to be 20cm the length of Resistance in left gap is  $\frac{1}{2}m$   
and radius is 2mm its specific resistance is

A.  $\pi \times 10^{-6} \text{ohm} - m$

B.  $2\pi \times 10^{-6} \text{ohm} - m$

C.  $\frac{\pi}{2} \times 10^{-6} \text{ohm} - m$

D.  $3\pi \times 10^{-6} \text{ohm} - m$


**Answer: B**



**Watch Video Solution**

**LECTURE SHEET (EXERCISE-IV LEVEL- II (ADVANCED))  
(Straight Objective Type Questions)**

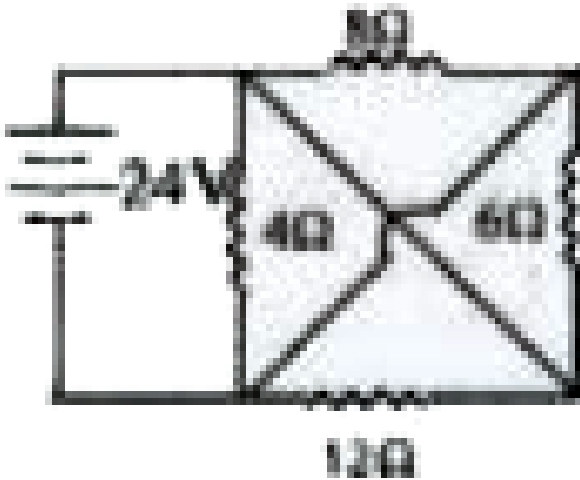1. Calculate battery current and equivalent resistance of the network shown in figure.



A. 20V,  $5\Omega$


B.  $5A$ ,  $\frac{8}{5}\Omega$

C.  $15A$ ,  $\frac{8}{5}\Omega$

D.  $9A$ ,  $\frac{8}{3}\Omega$

**Answer: C**

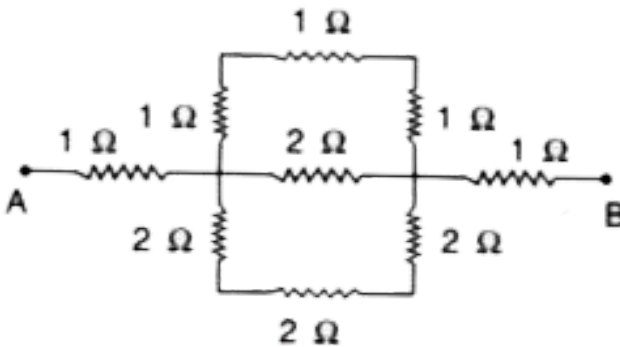2. Calculate the effective resistance between the points A and B in the circuit shown in Fig.



A.  $2V, i = I_1 + I_2 + I_3 = 2\text{amp}$

B.  $5V, I_1 = I_2 = I_3 = 0$

C.  $2V, I_1 = I_3 = 1A, I_2 = 0$

D.  $2V, I_1 = 1A, I_2 = 2A, I_3 = 3A$


Answer: C



Watch Video Solution

## LECTURE SHEET (EXERCISE-IV LEVEL- II (ADVANCED) (Linked Comprehension Type Questions))

1. In the circuit shown in figure

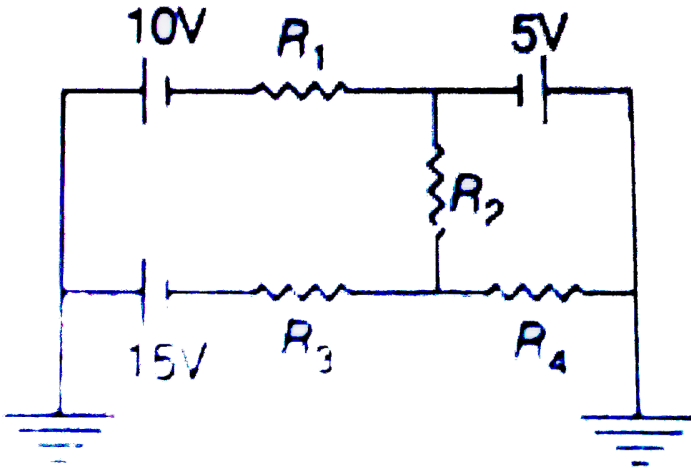



Current through  $R_2$  is zero if  $R_4 = 2\Omega$  and  $R_3 = 4\Omega$

In this case

- A. current through  $R_3$  is 2A
- B. current through  $R_4$  is 3A
- C. both (a) and (b) are correct
- D. both (a) and (b) wrong


**Answer: D**



[Watch Video Solution](#)

**2. Passage :**

In the circuit shown in figure :

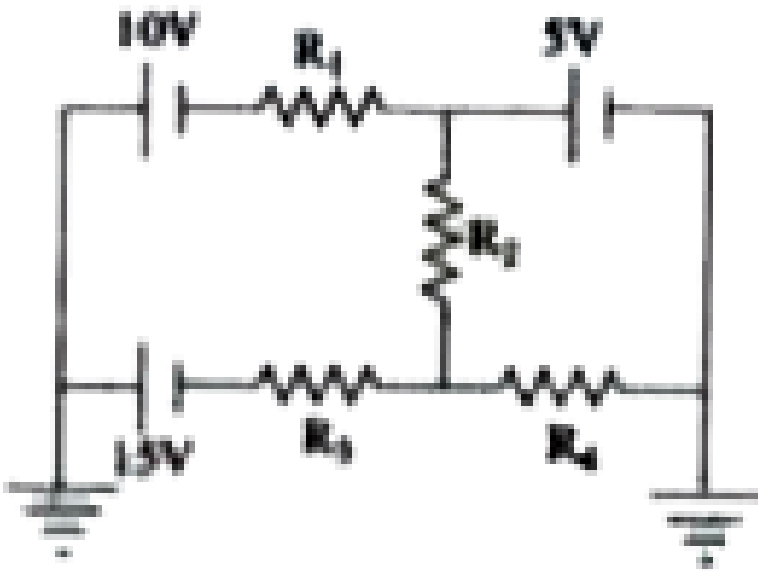


Current through  $R_1$  is independent of :

- A.  $R_2$
- B.  $R_3$
- C.  $R_4$
- D. all of these

**Answer: D**

3. In the circuit shown in figure

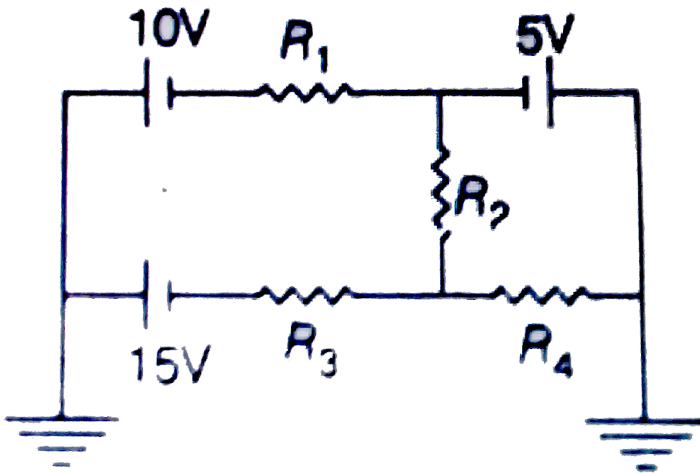

For what ratio  $\frac{R_2}{R_4}$ , current through  $R_3$  will be zero

A. 1 : 1

B. 1 : 2

C. 1 : 3

D. Not possible

**Answer: D**




**Watch Video Solution**

**LECTURE SHEET (EXERCISE-IV LEVEL- II (ADVANCED))  
(Integer Type Questions))**


**1. In the circuit shown, what is the potential difference**

**$V_{PQ}$  in volts ?**

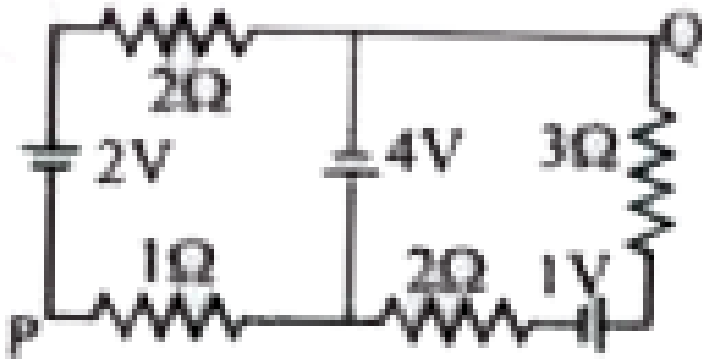


[▶ Watch Video Solution](#)

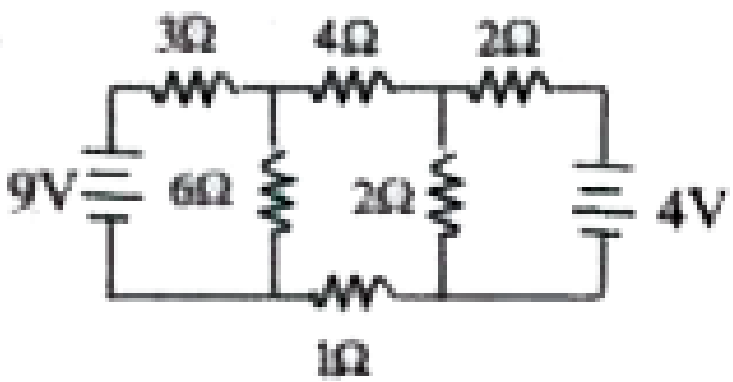2. For the circuit shown in figure, determine the voltage across  $4\Omega$  resistors in volt ?




[▶ Watch Video Solution](#)

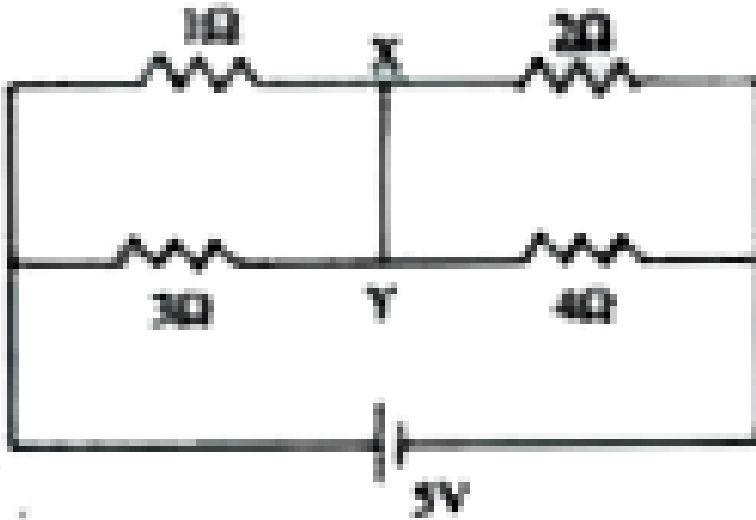3. The circuit shown in figure, find the current through wire XY in ampere



[Watch Video Solution](#)

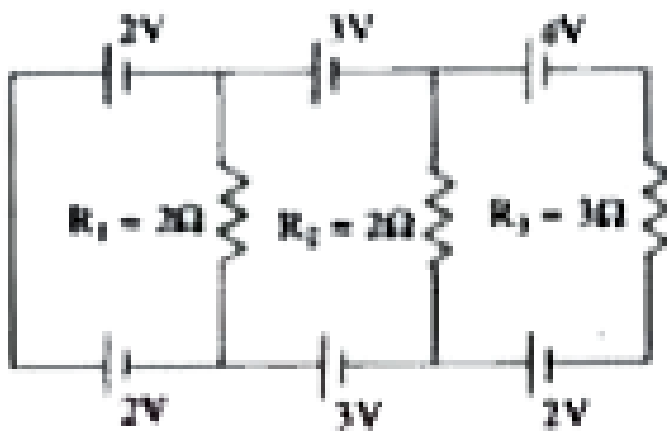4. The current in resistance  $R_3$  in the given circuit is  $\frac{2}{x}$   
A Find the value of x.



[Watch Video Solution](#)

## LECTURE SHEET (EXERCISE-V LEVEL - I (MAIN) (Straight Objective Type Questions))

1. The scale of a galvanometer is divided into 150 equal divisions. The galvanometer has a current sensitivity of 10 divisions per mA and a voltage sensitivity of 2

divisions per mV . The galvanometer be designed to read (i) 6 A per division and (ii) 1V per division?

A.  $40\mu\Omega$  is connected in parallel,  $1000\Omega$  is connected in series

B.  $20\mu\Omega$  is connected in parallel,  $9995\Omega$  is connected in series

C.  $8.3\mu\Omega$  is connected in parallel,  $9995\Omega$  is connected in series

D.  $8.3 \times 10^{-5}\Omega$  is connected in parallel,  $9995\Omega$  is connected in series

**Answer: D**



Watch Video Solution



2. A moving coil galvanometer of resistance  $20\Omega$  gives a full scale deflection when a current of  $1mA$  is passed through it. It is to be converted into an ammeter reading  $20A$  on full scale. But the shunt of  $0.005\Omega$  only is available. What resistance should be connected in series with the galvanometer coil?

- A.  $59.995\Omega$
- B.  $79.995\Omega$
- C.  $69.995\Omega$
- D.  $89.995\Omega$


**Answer: B**



**Watch Video Solution**

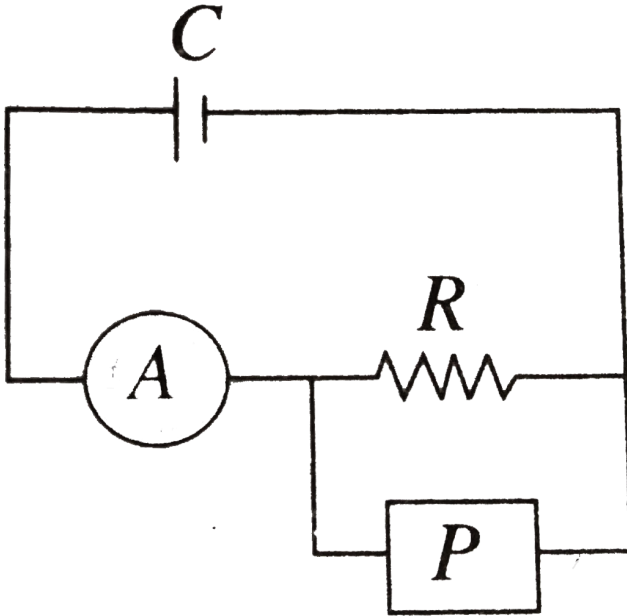3. An ammeter A of finite resistance and a resistor R are joined in series to an ideal cell C. A potentiometer P is joined in parallel to R. The ammeter reading is  $I_0$  and the potentiometer reading is  $V_0$ . P is now replaced by a voltmeter of finite resistance. The ammeter reading

now is  $I$  and the voltmeter reading is  $V$ . Then



A.  $I > I_0, V < V_0$

B.  $I > I_0, V = V_0$

C.  $I = I_0, V < V_0$

D.  $I < I_0, V = V_0$

**Answer: A**



Watch Video Solution

4. An ammeter is connected to measure the current intensity in a circuit with a resistance  $R$ . What relative error will be made if connection of the ammeter does not change the current intensity in the circuit? The voltage across the ends of the circuit is kept constant.

A.  $\frac{R}{R_0}$

B.  $\frac{R_0}{R}$

C.  $\frac{1}{1 + \frac{R}{R_0}}$

D.  $\frac{1}{1 + \frac{R_0}{R}}$

**Answer: C**



**Watch Video Solution**

5. The voltage across a resistance  $R$  is determined using a voltmeter connected to its ends. What relative error will be made if the readings of the voltmeter are taken as the voltage applied before it was switched on ? The current intensity in the circuit is constant.

A.  $\frac{R}{R_0}$

B.  $\frac{R_0}{R}$

C.  $\frac{1}{1 + \frac{R}{R_0}}$

D.  $\frac{1}{1 + \frac{R_0}{R}}$

**Answer: D**



**Watch Video Solution**


6. shows a circuit used in an experiment to determine the emf and internal resistance of the battery C. A graph was plotted of the potential difference  $V$  between the terminals of the battery against the current  $I$ , which was varied by adjusting the rheostat. The graph is shown in x and y are the intercepts of the graph with the axes as shown. What is the internal

resistance


of

the

battery?

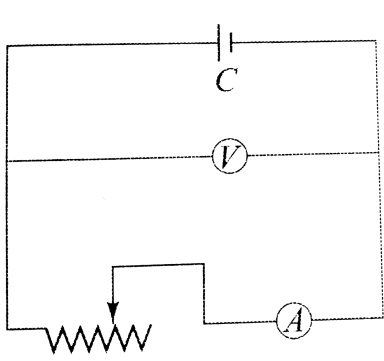

(a)

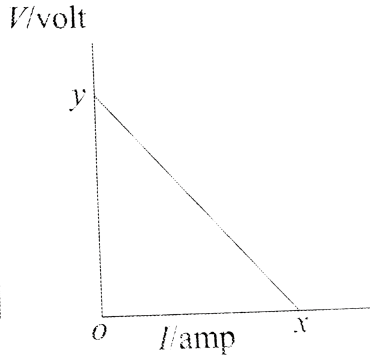

(b)

A.  $x$

B.  $y$

C.  $x/y$

D.  $y/x$

**Answer: D**



**Watch Video Solution**

## LECTURE SHEET (EXERCISE-V LEVEL-II (ADVANCED) (Straight Objective Type Questions))

1. A galvanometer has a current sensitivity of 1 mA per division. A variable shunt is connected across the galvanometer and the combination is put in series with a resistance of  $500\Omega$  and cell of internal resistance  $1\Omega$ . It gives a deflection of 5 division for shunt of 5 ohm and 20 division for shunt of 25 ohm. The emf of cell is

- A. 50V,  $100\Omega$
- B. 47.1V,  $882\Omega$
- C. 68.4V,  $23.4\Omega$
- D. 23.5V,  $90.3\Omega$



**Answer: B**



**Watch Video Solution**

2. The weight of an object on the surface of the Earth is 40 N. Its weight at a height equal to the radius of the Earth is

A.  $\frac{V_0}{R + r}$


B.  $\frac{V_0(R + r)}{Rr}$

C.  $\frac{V_0R}{r(r + R/4)}$

D.  $\frac{V_0r}{R(r + R/4)}$

**Answer: D**

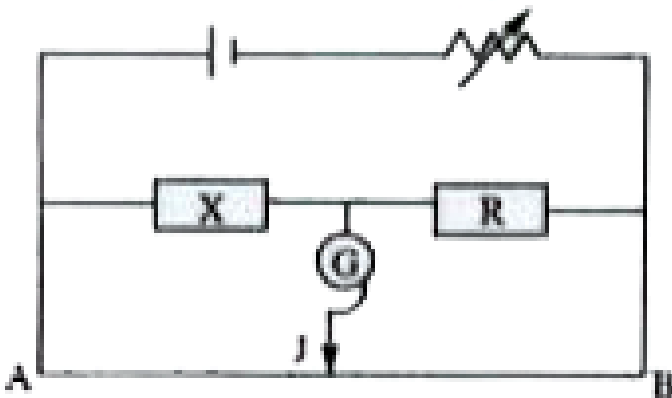3. Figure shows a metre bridge in which a known resistance  $R$  and an unknown resistance  $X$  connected to it. The length of the total wire  $AB$  is  $100\text{cm}$ . Then the balancing length for which the percentage error in measuring the value of  $x$  is minimum (neglect end corrections)



A. 0 cm

B. 33.3 cm


C. 50 cm

D. 100 cm

**Answer: C**



**Watch Video Solution**

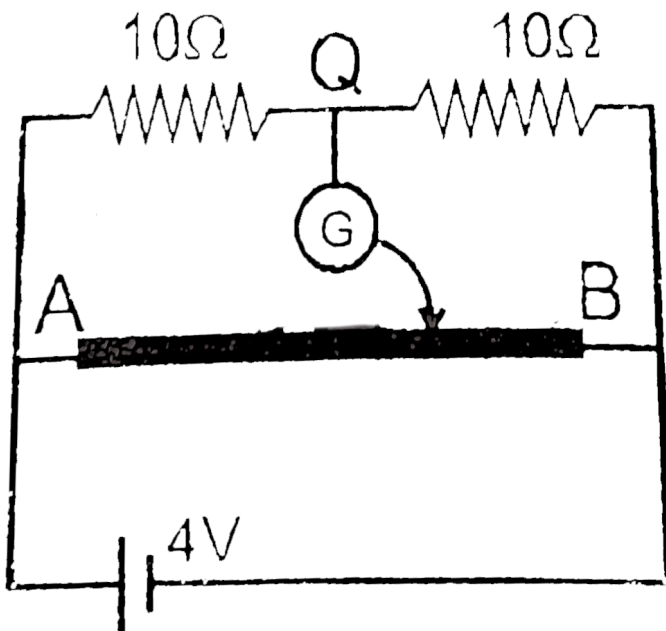

4.

A potentiometer wire AB as shown in 40 cm long of resistance  $50\Omega/m$  free end of an ideal galvanometer is touching the potentiometer wire with the help of a jockey. What should be the velocity of the jockey as a function of time so that potential difference across the galvanometer is varying with time as  $(2 \sin \pi t)V$

A.  $10\pi \sin \pi t \text{ cm} / \text{s}$

B.  $10\pi \cos \pi t \text{ cm} / \text{s}$

C.  $20\pi \sin \pi t \text{ cm} / \text{s}$

D.  $20\pi \cos \pi t \text{ cm} / \text{s}$


**Answer: D**



**Watch Video Solution**

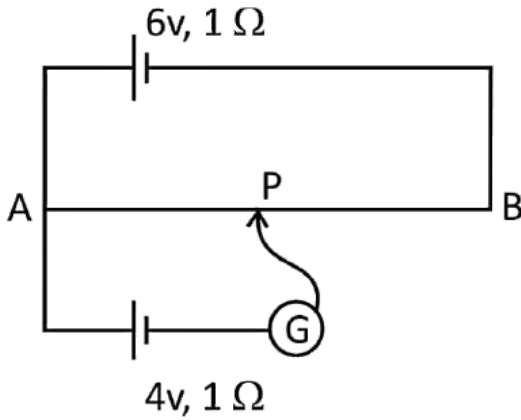5. A 6V battery of internal resistance  $1\Omega$  is connected across a uniform wire AB of length 100 cm. The positive terminal of another battery of E.M.F 4V and internal resistance  $1\Omega$  is joined to the point A as shown. The distance of point P from A is  $\alpha \times 10\text{cm}$ . Find the value

of  $\alpha$ , for which there is no current through the galvanometer. (resistance of AB wire is  $5\Omega$ )



- A. 80 cm
- B. 60 cm
- C. 75 cm
- D. 40 cm

**Answer: A**





Watch Video Solution

## LECTURE SHEET (EXERCISE-VI LEVEL - I (MAIN) (Straight Objective Type Questions))

1. A 100 watt immersion heater is placed in a pot containing 1 litre of water at  $20^{\circ}$  C. How long will it take to heat water to boiling temperature if 20% of the available energy is lost to surroundings?

- A. 60 minutes
- B. 70 minutes
- C. 44 minutes
- D. 32 minutes

**Answer: A**



**Watch Video Solution**

2. The same mass of aluminium is drawn into two wires 1mm and 2mm thick. Two wires are connected in series and current is passed through them. Heat produced in the wires is in the ratio.

A. 16 : 1

B. 1 : 1

C. 4 : 1

D. 9 : 1



**Answer: A**



**Watch Video Solution**

3. A long wire is divided into  $2n$  parts . Then  $n$  parts are connected in series and the other  $n$  parts are connected in parallel . Both the combinations are given the same voltage. Supply. The ratio of heat produced in series to the parallel combination will be

A.  $1 : 1$

B.  $1 : n^2$

C.  $1 : n^4$

D.  $n^2 : 1$

**Answer: B**



**Watch Video Solution**

4. A resistance coil of 60 ohm is immersed in 42000 gm of water. A current of 7A is passed through it. Calculate the rise in temperature per minute. The sp. Heat of

$$\text{water} = 4200 \frac{J}{kg - ^\circ K}$$

A.  $5^\circ C$

B.  $3^\circ C$

C.  $2^\circ C$

D.  $1^\circ C$

**Answer: D**



**Watch Video Solution**

5. The maximum voltage that can be applied to  $5K\Omega$  and 8W resistor without exceeding its heat dissipating capacity is

A. 100 V

B. 400 V

C. 160 V


D. 200 V

**Answer: D**



Watch Video Solution

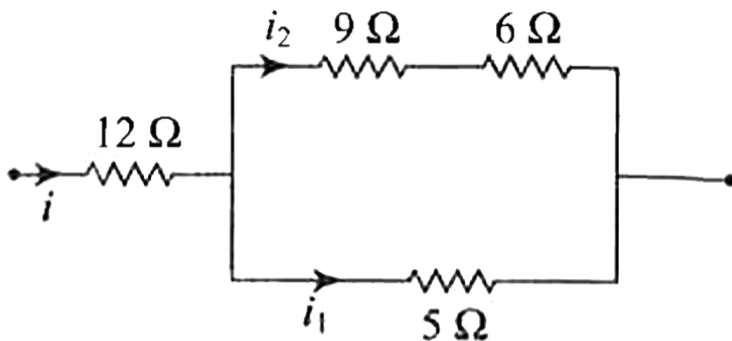6. In the following circuit,  $5\Omega$  resistor develops  $45\frac{J}{s}$  due to current flowing through it. The power developed per second across  $12\Omega$  resistor is



- A. 16 W
- B. 192 W
- C. 36 W

D. 64 W

**Answer: B**



**Watch Video Solution**

7. Two wires A and B of the same material and mass have their length in the ratio 1 : 2. On connecting them to the same source, the ratio of heat dissipation in B is found to be 5W. The rate of heat dissipation in A is

A. 10W

B. 5W

C. 20W

D. None of these


**Answer: C**



**Watch Video Solution**

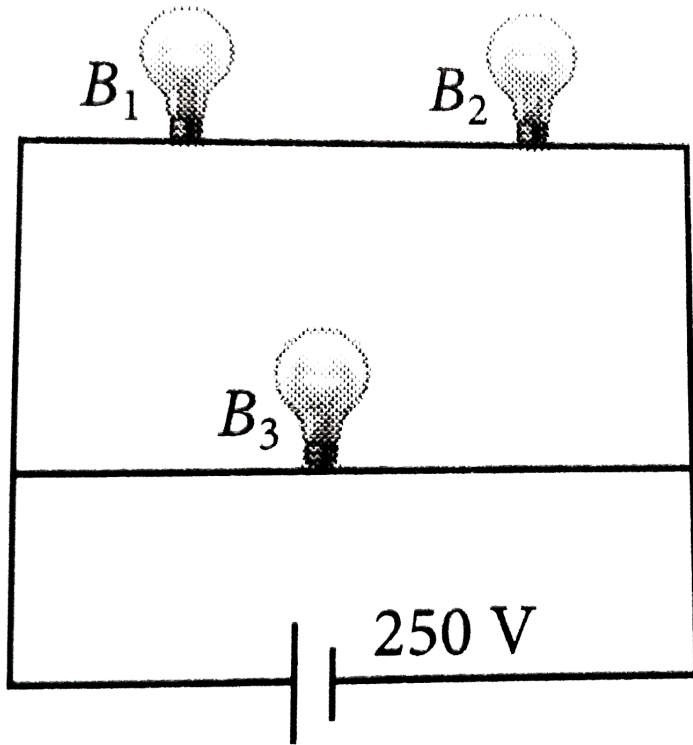**8.** A 100 W bulb  $B_1$  and two 60W bulbs  $B_2$  and  $B_3$ , are connected to a 250 V source, as shown in figure. Now  $W_1$ ,  $W_2$  and  $W_3$  are the output powers of the bulbs

$B_1$ ,  $B_2$  and  $B_3$ , respectively. Then




- A.  $W_1 > W_2 = W_3$
- B.  $W_1 > W_2 > W_3$
- C.  $W_1 < W_2 = W_3$
- D.  $W_1 < W_2 < W_3$

Answer: D

 Watch Video Solution

9. In the circuit diagram, all the bulbs are identical.

Which bulb will be the brightest?

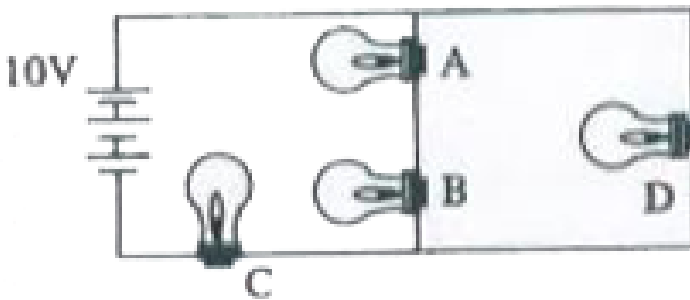

A. A

B. B

C. C



D. D

**Answer: C**



**Watch Video Solution**

**LECTURE SHEET (EXERCISE-VI LEVEL- II (ADVANCED))  
(Straight Objective Type Questions)**

1. A total charge  $Q$  flows across a resistor  $R$  during a time interval  $T$  in such a way that the current versus time graph for  $0$  to  $T$  is like the loop of a sine curve in the range  $0$  to  $\pi$ . The total heat generated in the resistor is

A.  $Q^2 \pi^2 R / 8T$

B.  $2Q^2 \pi^2 R / T$

C.  $2Q^2 \pi^2 R / 4T$

D.  $Q^2 \pi^2 R / 4T$



**Answer: D**




**Watch Video Solution**


2. The variation of current (I) and voltage (V) across a resistance R is as shown in figure. The variation of power P with current I is best shown by which of the

following graph

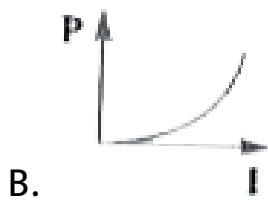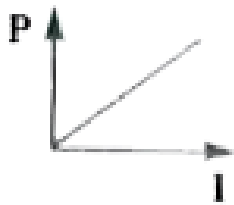

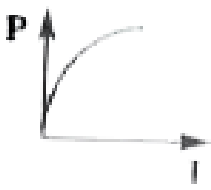

C.

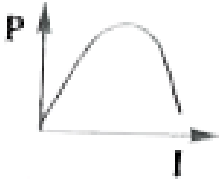

D.

**Answer: B**



**Watch Video Solution**

3. The current  $I$  through a rod of a certain metallic oxide is given by  $I = 0.2V^{1/2}$ , where  $V$  is the potential difference across it. The rod is connected in series with a resistance to a 6 volt battery of negligible internal resistance. What value should the series

resistance have so that :

A) the current in the circuit is 0.4 A

B) the power dissipated in the rod is twice that dissipated in the resistance.

A.  $10\Omega$ ,  $10\Omega$

B.  $10\Omega$ ,  $5\Omega$

C.  $5\Omega$ ,  $10\Omega$


D.  $5\Omega$ ,  $5\Omega$

**Answer: D**



**Watch Video Solution**

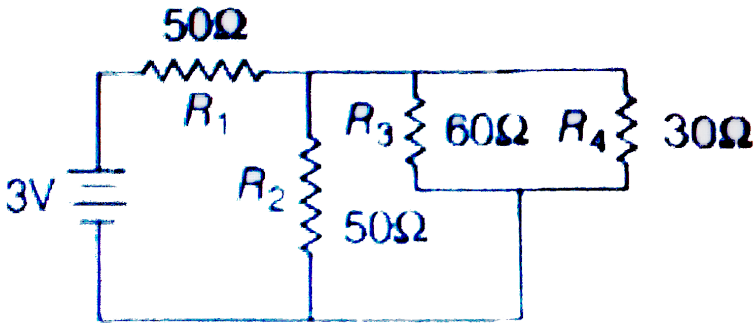4. In the circuit shown, the resistance are given ohms and the battery is assumed ideal with end equal to 3.0 volts. The resistance that dissipates the maximum power is




- A.  $R_1$
- B.  $R_2$
- C.  $R_3$
- D.  $R_4$

Answer: A

 Watch Video Solution

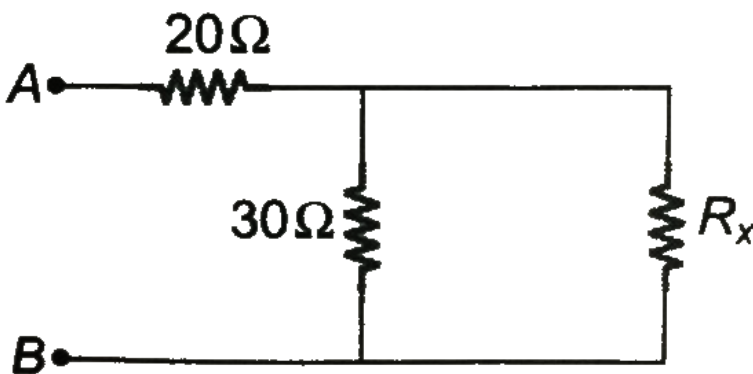5. A circuit shown in the figure has resistances  $20\Omega$  and  $30\Omega$ . At what value of resistance  $R_x$  will the thermal power generated in it be practically independent of small variations of that resistance? The voltage between points  $A$  and  $B$  is supposed to be constant in this case.



A.  $3\Omega$

B.  $7\Omega$

C.  $12\Omega$

D.  $20\Omega$

**Answer: C**



**Watch Video Solution**

6. Two identical electric heaters each marked  $1000\text{ W}$   $220\text{ V}$  are connected in series . This combination is connected to an AC supply of  $220\text{ V}$  . What will be their combined rate of heating? (Assume resistance of each heater remains constant)



A. 1000 W

B. 2000 W

C. 500 W

D. 4000 W


**Answer: C**



**Watch Video Solution**

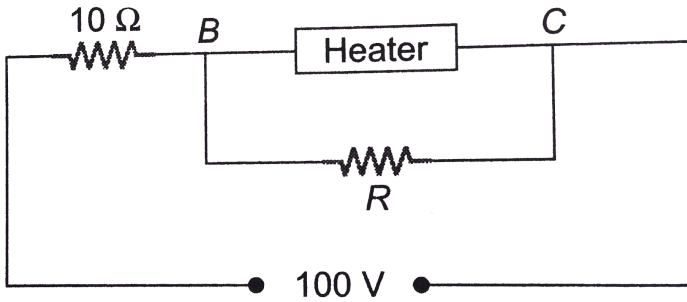7. A heater is designed to operate with a power of  $1000W$  in a  $100V$  line. It is connected in combination with a resistance of  $10\Omega$  and a resistance  $R$ , to a  $100V$  mains as shown in figure. What will be the value of  $R$

so that the heater operates with a power of  $62.5\text{W}$ ?



- A.  $10\Omega$
- B.  $62.5\Omega$
- C.  $\frac{1}{5}\Omega$
- D.  $5\Omega$


**Answer: D**



**Watch Video Solution**

LECTURE SHEET (EXERCISE-VII LEVEL - I (MAIN) (Straight Objective Type Questions))

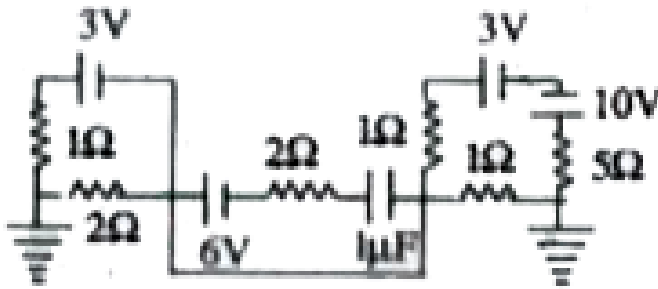1. For the circuit shown in the figure, determine the charge of capacitor in steady state.



A.  $4\mu C$

B.  $6\mu C$

C.  $1\mu C$



D. Zero


Answer: B




Watch Video Solution

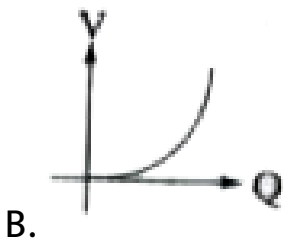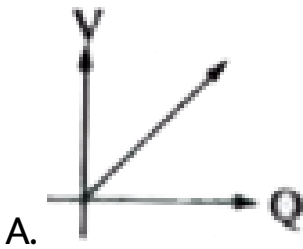2. A capacitor is charged steadily from a DC source. Correct variation of potential difference across the plates of capacitor with charge on the plates of capacitor is



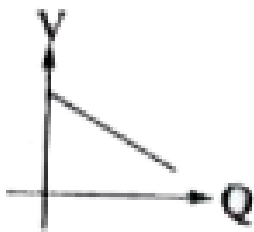

C.

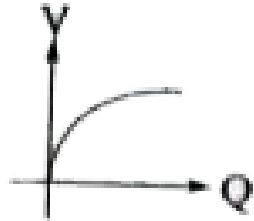


D.

**Answer: A**



[Watch Video Solution](#)

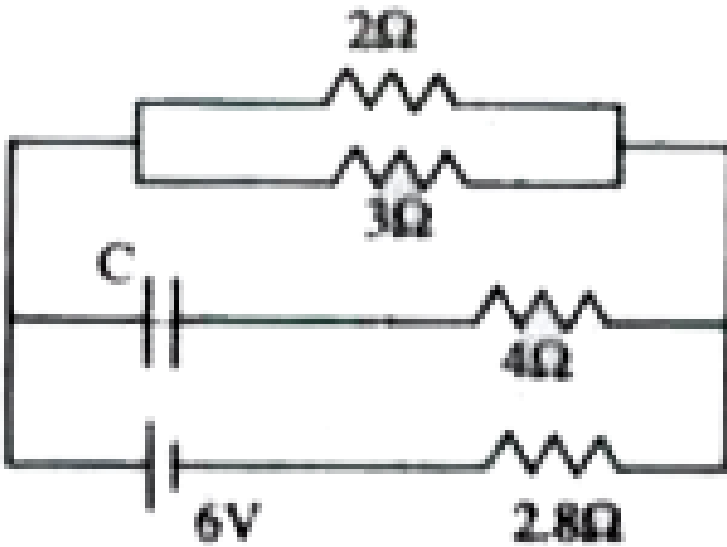3. In the steady state, the charge on the capacitor capacity  $0.2\mu F$  is




- A. zero
- B.  $0.36\mu\text{c}$
- C.  $0.2\mu\text{c}$
- D.  $1.2\mu\text{c}$

**Answer: B**

 **Watch Video Solution**

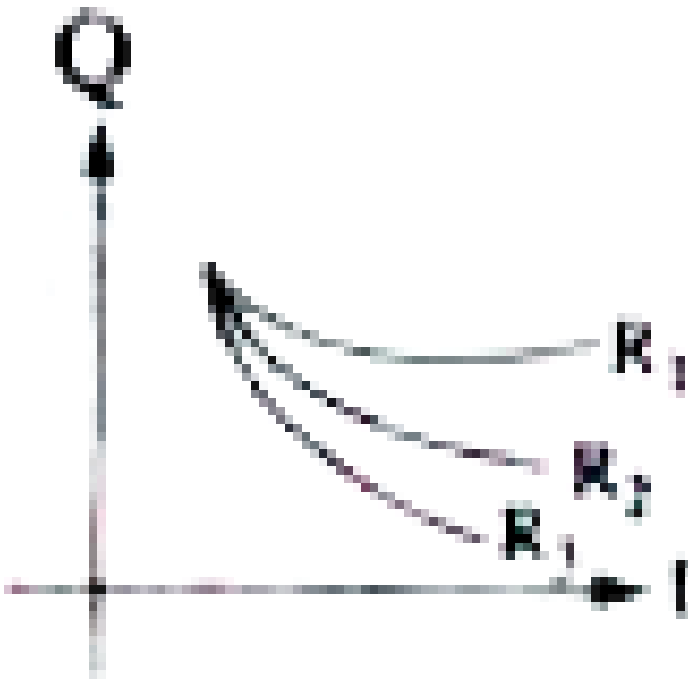4. Three identical capacitors are charged by connecting them in parallel across a battery of  $V$  volt. They are then allowed to discharge via resistor  $R_1$ ,  $R_2$  and  $R_3$ .

Here,  $Q$  charge versus  $t$  time graphs are shown. Then,



A. A)  $R_1$  is smallest

B. B)  $R_2$  is smallest

C. C)  $R_3$  is smallest

D. D)  $R_3 > R_2 > R_1$

**Answer: A**




**Watch Video Solution**

5. For the circuit shown in figure below, at  $t = 0$ , switch is closed, the initial current through resistor and final



charge on capacitor are

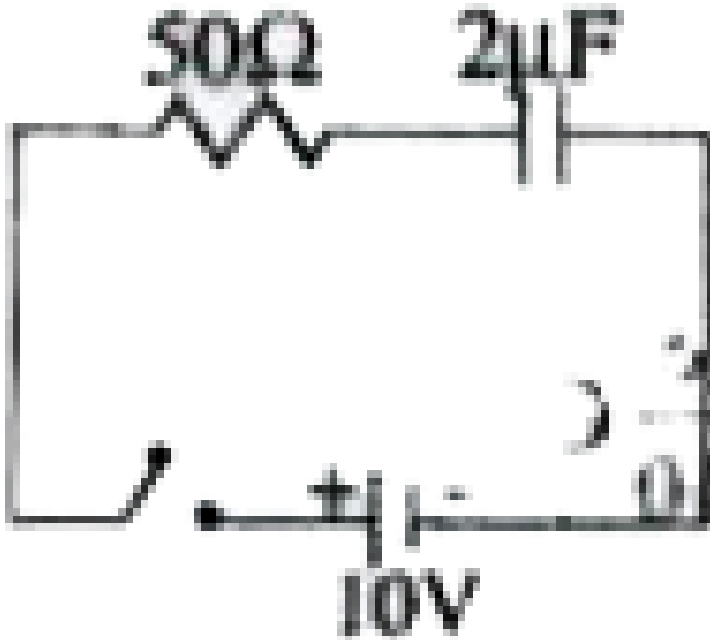


- A.  $5\text{A}$ ,  $5\mu\text{C}$
- B.  $5\text{A}$ ,  $20\mu\text{C}$
- C.  $0.2\text{A}$ ,  $5\mu\text{C}$
- D.  $0.2\text{A}$ ,  $20\mu\text{C}$

Answer: D



Watch Video Solution

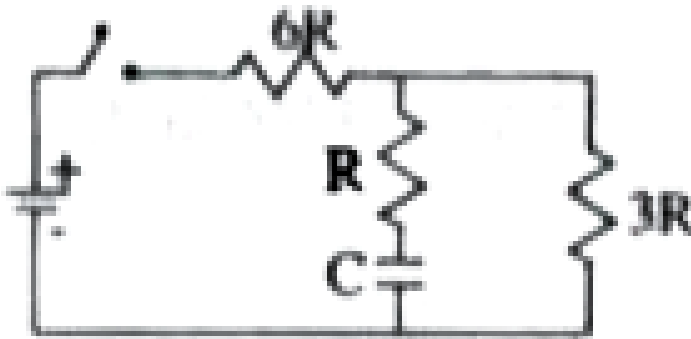6. For the given circuit shown in figure below, time constant is



A.  $\tau = RC$

B.  $\tau = 2.1RC$


C.  $\tau = 27/4RC$

$$D. \tau = 3RC$$

Answer: D


 [Watch Video Solution](#)

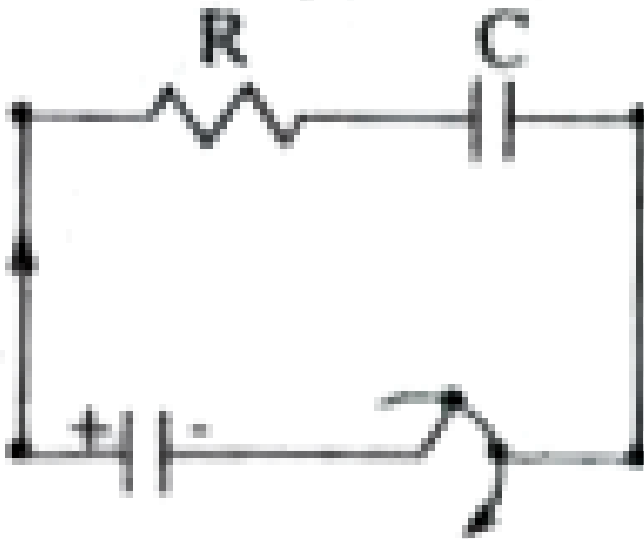7. During charging of capacitor in the circuit shown,



Circuit current versus time graph is


A.

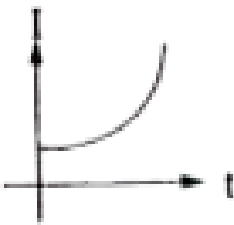


B.



C.

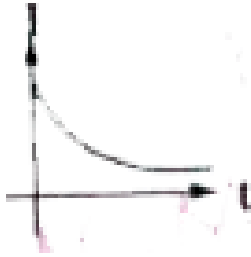

D.

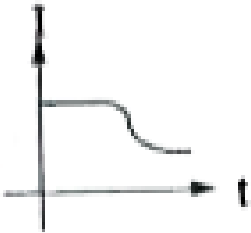


**Answer: C**






**Watch Video Solution**

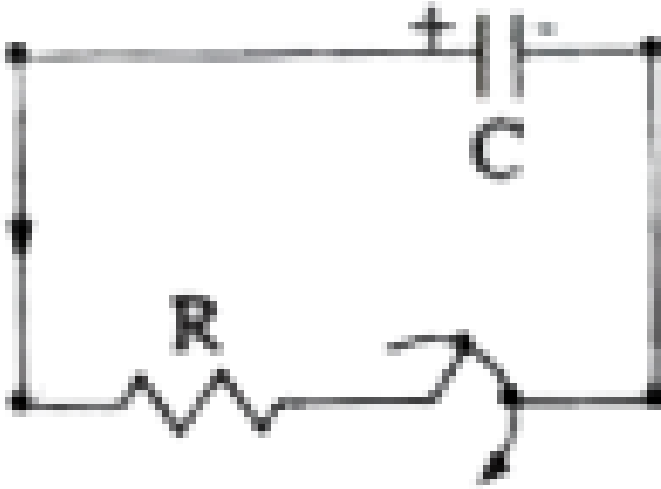8. During discharging of a capacitor via a resistor




Circuit current varies with time as

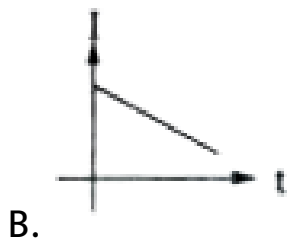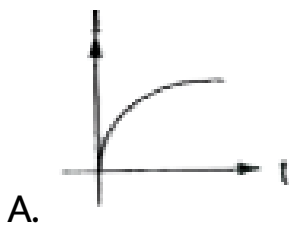

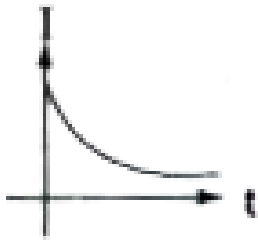

C.

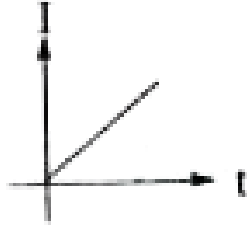

D.


**Answer: C**



**Watch Video Solution**

9. If the capacitor shown in the circuit is charged to 5V and left in the circuit, in 12s the charge on the

capacitor will become:

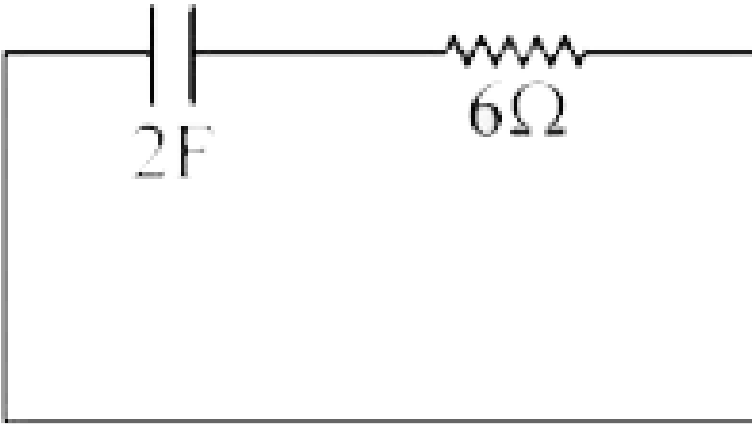

A.  $\frac{10}{e} C$

B.  $\frac{e}{10} C$

C.  $\frac{10}{e^2} C$

D.  $\frac{e^2}{10} C (e = 2.718)$


**Answer: A**



**Watch Video Solution**

## (Straight Objective Type Questions))

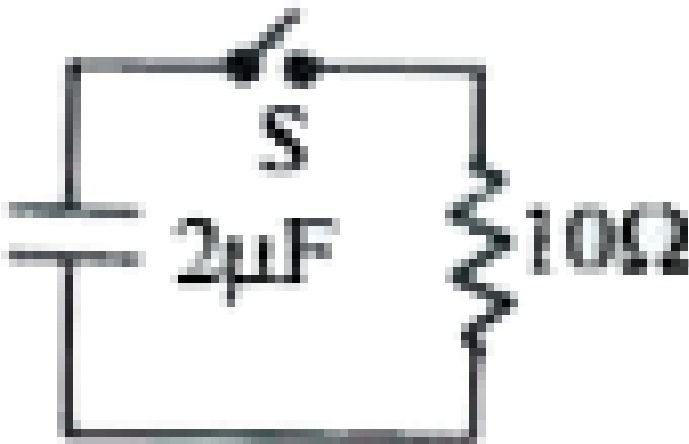1. In the R-C circuit shown in the figure the total of  $3.6 \times 10^{-3} J$  is dissipated in the 10 ohms resistor when the switch S is closed. The initial charge on the capacitor is



A.  $60 \mu C$

B.  $120 \mu C$




C.  $60\sqrt{2}\mu C$

D.  $\frac{60}{\sqrt{2}}\mu C$

**Answer: B**

 [Watch Video Solution](#)

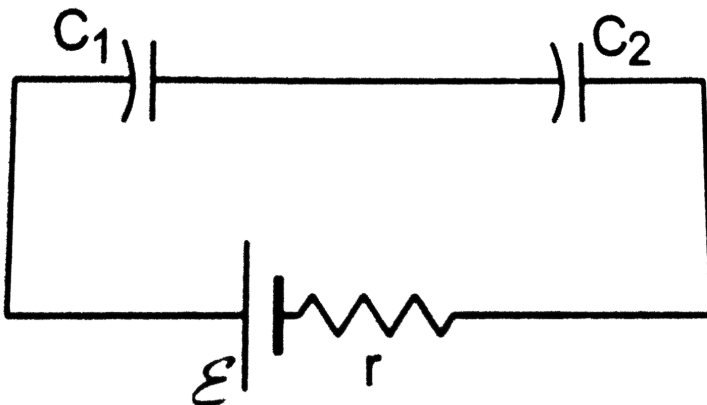2. Consider the situation shown in figure. The switch is closed at  $t = 0$  when the capacitors are uncharged. Find the charge on the capacitor  $C_1$  as a function of time  $t$ .



A.  $q = \varepsilon C \left(1 - e^{-\frac{t}{rC}}\right)$  where  $C = \frac{C_1 C_2}{C_1 + C_2}$

B.  $q = \frac{\varepsilon C}{2} \left(1 - e^{-\frac{t}{rC}}\right)$  where  $C = C_1 + C_2$

C.  $q = \varepsilon C \left(1 - e^{-\frac{t}{rC}}\right)$  where  $C = C_1 + C_2$

D.  $q = \varepsilon C e^{-\frac{t}{nC}}$  where  $C = \frac{C_1 C_2}{C_1 + C_2}$


**Answer: A**



**Watch Video Solution**

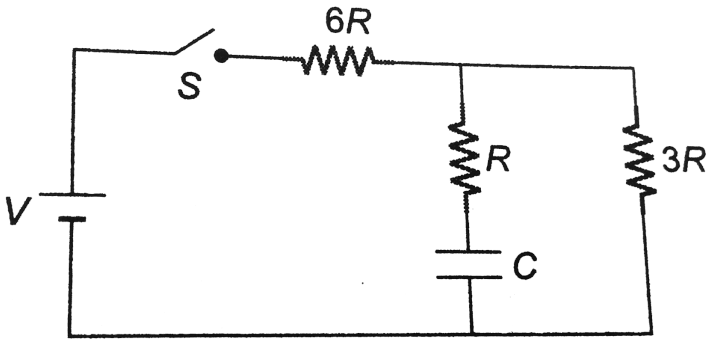3. In the circuit shown in figure switch  $S$  is closed at time  $t=0$ . Find the current through different wire and

charge stored on the capacitor at any time  $t$ .



A.  $q = \frac{CV}{3} \left(1 - e^{-\frac{t}{3RC}}\right)$

B.  $q = \frac{CV}{3} \left(1 - e^{-\frac{4t}{27RC}}\right)$

C.  $q = CV \left(1 - e^{-\frac{t}{RC}}\right)$


D.  $q = CV \left(1 - e^{-\frac{t}{7RC}}\right)$

**Answer: A**



**Watch Video Solution**

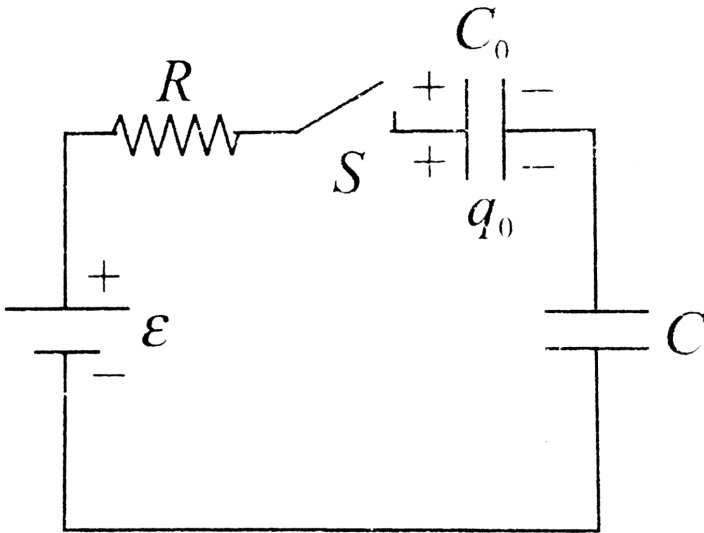4. The switch  $S$  is closed at  $t = 0$ . the capacitor  $C$  is uncharged but  $C_0$  has a charge  $q_0$  at  $t = 0$ . Calculate the current  $i(t)$  in the circuit



A.  $\left[ \frac{E - \frac{q_0}{C_0}}{R} \right] e^{-\frac{t}{RC_{eq}}}$

B.  $\frac{E}{R} \left( e^{-\frac{t}{RC_{eq}}} \right)$

C.  $\frac{q_0}{C_0} \left[ e^{-\frac{t}{RC_{eq}}} \right]$

D.  $\left[ \frac{E + \frac{q_0}{C_0}}{R} \right] e^{-\frac{t}{RC_{eq}}}$  where  $C_{eq} = \frac{C_0 C}{C_0 + C}$

**Answer: A**

 [Watch Video Solution](#)

5. A capacitor given a charge  $Q_0$  is connected across a resistor  $R$  at  $t = 0$ . The separation between the plates changes according to  $d = \frac{d}{(1+t)}$  ( $0 \leq t < 1$ ) Find the variation of charge on capacitor with time.



$$\text{A. } Q = Q_0(1 + t)e^{\frac{-1}{RC_0}}$$

$$\text{B. } Q = Q_0(1 + t)^{\frac{-1}{RC_0}}$$

$$\text{C. } Q = Q_0e^{\frac{-1}{RC_0}}$$

$$\text{D. } Q = Q_0e(1 + t)^2e^{\frac{-1}{RC_0}}$$

**Answer: B**



**Watch Video Solution**


**LECTURE SHEET (EXERCISE-VII LEVEL-II (ADVANCED) (Linked Comprehension Type Questions))**

**1. Passage :**

Suppose the switch S has been sufficiently long time

for the capacitor to become fully charged. Find (where
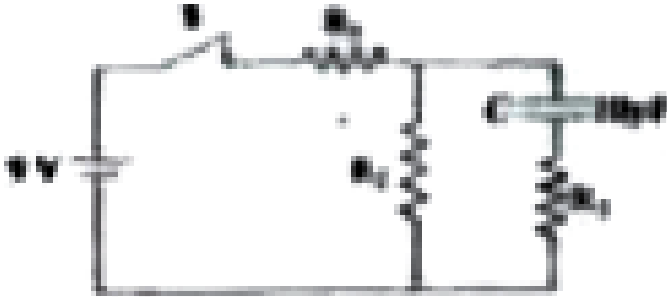
$$R_1 = 12k\Omega, R_2 = 15k\Omega, R_3 = 5k\Omega)$$



The steady-state current through each resistor

A.  $I_1 = I_2 = 3mA, I_3 = 0$

B.  $I_1 = 1A, I_2 = 2A, I_3 = 3A$

C.  $I_1 = I_2 = I_3 = 1/3A$

D.  $I_1 = I_2 = 1/3mA, I_3 = 0$

**Answer: D**




**Watch Video Solution**
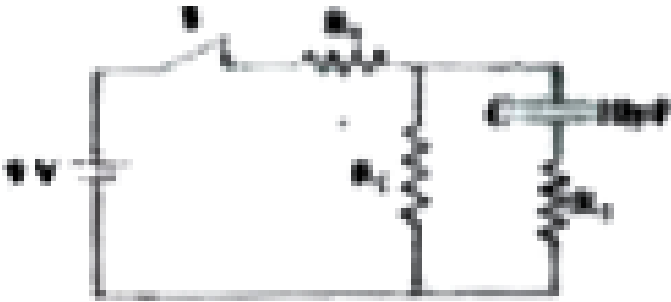
## 2. Passage :

Suppose the switch  $S$  has been sufficiently long time for the capacitor to become fully charged. Find (where

$$R_1 = 12k\Omega, R_2 = 15k\Omega, R_3 = 5k\Omega)$$



In the above question the charge on the capacitor is

A.  $50\mu C$

B.  $100\mu C$

C.  $90\mu C$



D.  $40\mu C$


**Answer: A**

 [Watch Video Solution](#)

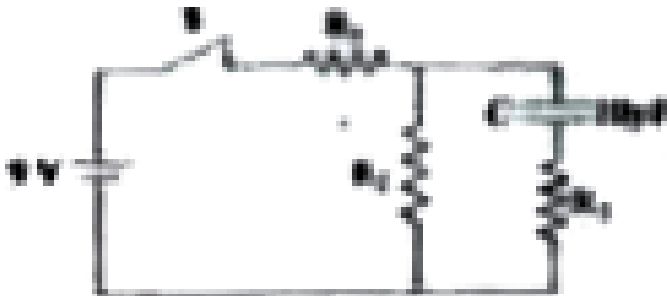**3. Passage :**

Suppose the switch  $S$  has been sufficiently long time for the capacitor to become fully charged. Find (where

$R_1 = 12k\Omega$ ,  $R_2 = 15k\Omega$ ,  $R_3 = 5k\Omega$ )



The steady-state current through each resistor

A. 0.3s

B. 0.1386 s

C. 0.693 s

D. 0.367 s

**Answer: B**



**Watch Video Solution**

## **PRACTICE SHEET (EXERCISE - I LEVEL-I (MAIN) (Straight Objective Type Questions))**

1. A current of 4.8 A is flowing in a conductor the number of electrons passing per sec through the

conductor will be

A.  $3 \times 10^{19}$

B.  $7.68 \times 10^{20}$

C.  $76.8 \times 10^{19}$

D.  $3 \times 10^{20}$

**Answer: A**



**Watch Video Solution**

2. In a hydrogen atom, an electron is revolving with an angular frequency  $6.28 \text{ rad/s}$  around the nucleus. Then the equivalent electric current is \_\_\_\_  $10^{-19} \text{ A}$

A. 0.16

B. 1.6


C. 0.016

D. 16

**Answer: B**

 [Watch Video Solution](#)

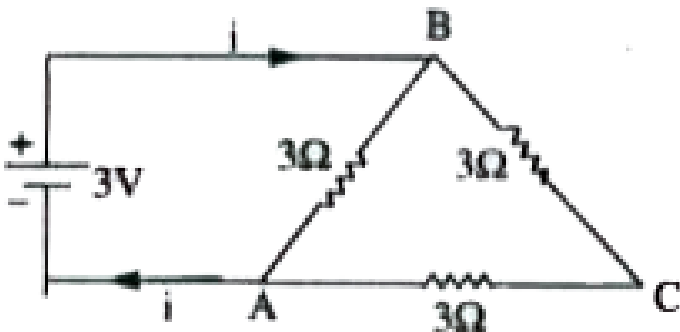3. The current  $i$ . in the circuit as shown in fig. is



A. 2A

B.  $\frac{1}{3}A$

C. 1A


D. 1.5A

**Answer: D**



**Watch Video Solution**

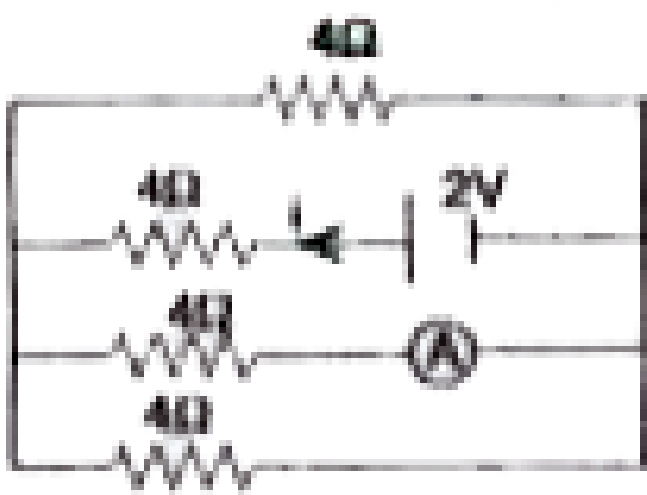4. Current coming from the battery and ammeter reading are



- A.  $\frac{3}{8}A, \frac{1}{8}A$
- B.  $\frac{1}{8}A, \frac{1}{8}A$
- C.  $2A, \frac{2}{3}A$
- D.  $2A, \frac{1}{8}A$

**Answer: A**



**Watch Video Solution**

5. A uniform copper wire carries a current  $i$  amperes and has  $p$  carriers per metre<sup>3</sup>. The length of the wire is 1 metro and its cross-section area is  $s$  metre<sup>2</sup>. If the charge on a carrier is  $q$  coulombs, the drift velocity in  $\text{ms}^{-1}$  is given by

A.  $1/lsq$

B.  $i/psq$

C.  $psq/i$

D.  $i/pslq$

**Answer: B**



**Watch Video Solution**

6. If a current of 0.5 ampere flows through a metallic wire for 2 hour then how many electrons flow through the wire ?

A. 2: 1

B. 1: 2

C. 4: 1

D. 1: 4

**Answer: B**



**Watch Video Solution**



7. A copper wire of diameter 1 mm carries a current of 1.1A. The drift speed of electrons in (given, density of  $Cu = 9g/cm^3$ , atomic weight of Cu = 63 g and one electron is contributed by each Cu atom)

A. 0.1 mm/s

B. 0.2 mm/s

C. 0.3 mm/s

D. 0.2 cm/s

**Answer: A**



**Watch Video Solution**

1. When a current passes through a resistor, its temperature increases. Is it an adiabatic process?

A. may increase or decrease

B. remains constant

C. increases


D. decreases

**Answer: C**




**Watch Video Solution**

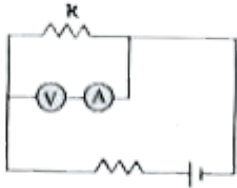
2. Which of the following diagrams could be used to experimentally determine  $R$  using ohm's law? Assume an ideal voltmeter and an ideal ammeter.




A.

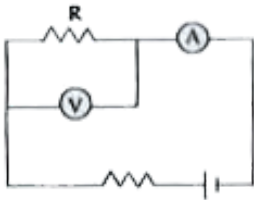

B.

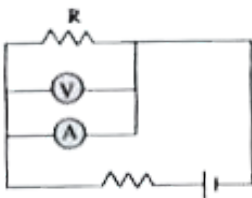

C.

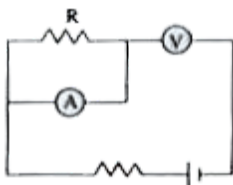

D.

**Answer: B**



**Watch Video Solution**

**3. Chose the correct statement:**

A. Number of collisions per second between free electrons in a wire is a measure of electric resistance of the wire

B. When a finite current passes through a conductor, no heat can be dissipated in it

C. e.m.f can never be electrostatic in nature

D. An Ohmic resistor must obey Ohm's law

**Answer: B**



**Watch Video Solution**

**PRACTICE SHEET (EXERCISE - I LEVEL-II (ADVANCED) (More than One correct answer Type Questions))**

1. Temperature dependence of drift velocity depends on the following factors.

A. Number of charge carriers can change with temperature

B. Time interval between two successive collisions can depend on the temperature

C. Length of a material is a function of temperature

D. Mass of a material is a function of temperature

**Answer: A::B**



**Watch Video Solution**

## **PRACTICE SHEET (EXERCISE - I LEVEL-II (ADVANCED) (Linked Comprehension Type Questions))**

### **1. Passage-I :**

Two large plates are located in vacuum. One of them serves as a cathode, a source of electrons whose initial velocity is negligible. An electron flow directed toward

the opposite plate produces a space charge causing the potential in the gap between the plates to vary as  $V = ax^{4/3}$ , where  $a$  is a positive constant, and  $x$  is the distance from the cathode.



The electric field between the plate as a function of  $x$  is

A.  $E = ax^{1/3}$

B.  $E = -ax^{2/3}$

C.  $E = \frac{-4a}{3}x^{1/3}$

D. None

Answer: C



Watch Video Solution

2. A proton is moving along the negative direction of X-axis in a magnetic field directed along the positive direction of Y-axis. The proton will be deflected along the negative direction of

A.  $a \epsilon_0 x^{1/3}$

B.  $\frac{4}{9}ax^{1/3}$

C.  $-\frac{4}{9}a \epsilon_0 x^{-2/3}$

D.  $\frac{4}{9}a \epsilon_0 x^{4/3}$



**Answer: C**



**Watch Video Solution**

### **3. Passage-I :**

Two large plates are located in vacuum. One of them serves as a cathode, a source of electrons whose initial velocity is negligible. An electron flow directed toward the opposite plate produces a space charge causing the potential in the gap between the plates to vary as  $V = ax^{4/3}$ , where  $a$  is a positive constant, and  $x$  is the distance from the cathode.



The current density

A.  $-\frac{2}{3} \epsilon_0 a^{3/2} \sqrt{\frac{2e}{m}}$

B.  $-\frac{4}{9} \epsilon_0 a^{3/2} \sqrt{\frac{2e}{m}}$

C.  $-\frac{2}{3} \epsilon_0 a^{3/2} \sqrt{\frac{2e}{m}}$


D. None.

**Answer: B**



**Watch Video Solution**

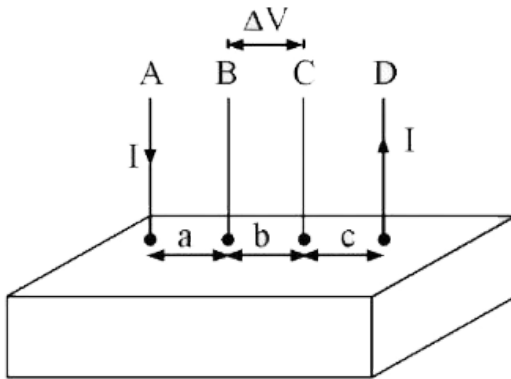4. Consider a block of conducting material of resistivity  $\rho$  shown in the figure. Current  $I$  enters at A and leaves from D. We apply superposition principle to find voltage  $\Delta v$  developed between B and C. The calculation is done in the following steps :



(i) Take current  $I$  entering from A and assume it to spread over a hemispherical surface in the block.

(ii) Calculate field  $E(r)$  at distance  $r$  from A by using

Ohm's law  $E = \rho j$  where  $j$  is the current per unit area at

$r$ .

(iii) From the  $r$  dependence of  $E(r)$ , obtain the potential

$V(r)$  at  $r$ .

(iv) Repeat (i), (ii) and (iii) for current  $I$  leaving  $D$  and

superpose result for  $A$  and  $D$ .

$\Delta v$  measured between  $B$  and  $C$  is :

A.  $\frac{\rho l}{\pi a} - \frac{\rho l}{\pi(a + b)}$

B.  $\frac{\rho l}{a} - \frac{\rho l}{(a + b)}$

C.  $\frac{\rho l}{2\pi a} - \frac{\rho l}{2\pi(a + b)}$

D.  $-\frac{\rho l}{2\pi(a - b)}$

**Answer: C**




**Watch Video Solution**

## 5. Passage-II:

Consider a block conducting material of resistivity  $\rho$  shown in the figure. Current  $I$  enters at  $A$  and leaves from  $D$ . We apply superposition principle to find voltage  $\Delta V$  developed between  $B$  and  $C$ . The calculation is done in the following steps :

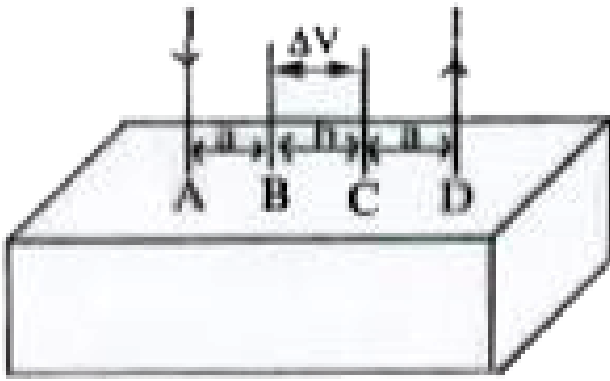- i) Take current  $I$  entering from  $A$  and assume it to spread over a hemispherical surface in the block.
- ii) Calculate field  $E(r)$  at distance  $r$  from  $A$  by using Ohm's law  $E = \rho j$ , where  $j$  is the current per unit area at  $r$ .
- iii) From the  $r$  dependence of  $E(r)$ , obtain the potential  $V(r)$  at  $r$ .
- iv) Repeat (i), (ii), (iii) for current  $I$  leaving  $D$  and superpose results for  $A$  and  $D$ .



For current entering at A the electric field at a distance  $r$  from A is

A.  $\frac{\rho I}{8\pi r^2}$

B.  $\frac{\rho I}{r^2}$

C.  $\frac{\rho I}{2\pi r^2}$

D.  $\frac{\rho I}{4\pi r^2}$

**Answer: C**




**Watch Video Solution**

## PRACTICE SHEET (EXERCISE - I LEVEL-II (ADVANCED) (Matrix Matching Type Questions))

1. Column - I gives physical quantities of a situation in which a current  $I$  passes through two rods I and II of equal length that are joined in series. The ratio of free electron density ( $n$ ), resistivity ( $\rho$ ) and cross-section area ( $A$ ) of both are in ratio  $n_1:n_2 = 2:1$  and  $A_1:A_2 = 1:2$  respectively. Column II gives corresponding results. Match the ratios in the column I

with the values in column II

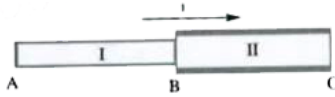

COLUMN - I

- A)  $\frac{\text{Drift velocity of free electron in rod I}}{\text{Drift velocity of free electron in rod II}}$
- B)  $\frac{\text{Electric field in rod I}}{\text{Electric field in rod II}}$
- C)  $\frac{\text{potential difference across rod I}}{\text{potential difference across rod II}}$
- D)  $\frac{\text{Average time taken by free electron to move from A to B}}{\text{Average time taken by free electron to move from B to C}}$

COLUMN - II

- p) 0.5
- q) 1
- r) 2
- s) 4



Watch Video Solution

## PRACTICE SHEET (EXERCISE - I LEVEL-II (ADVANCED)) (Integer Type Questions))

1. The area of cross-section, length and density of a piece of a metal of atomic weight 60 are  $10^{-6}m^2$ ,  $1.0m$  and  $5 \times 10^3 kg/m^3$  respectively, every atom contributes one free electron. (Given Avogadro number




$=6 \times 10^{23} / \text{mol}$ ). Find the drift velocity of electrons in the metal when the current of  $16\text{A}$  passes through:

 [Watch Video Solution](#)

2. A straight copper-wire of length  $l = 1000\text{ m}$  and cross-sectional area  $A = 1.0\text{ mm}^2$  carries a current  $i=4.5\text{A}$ . The sum of electric forces acting on all free electrons in the given wire is  $M \times 10^6\text{ N}$ . Find  $M$ . Free electron density and resistivity of copper are  $8.5 \times 10^{28} / \text{m}^3$  and  $1.7 \times 10^{-8}\Omega\cdot\text{m}$  respectively.

 [Watch Video Solution](#)

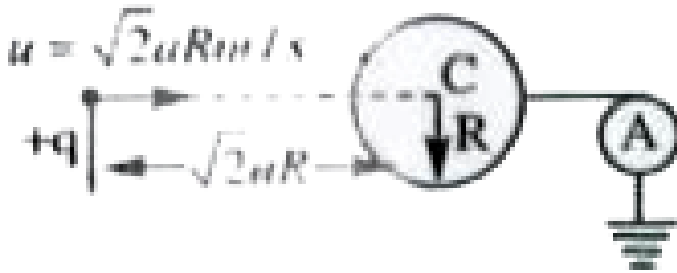3. If a charge  $q$  is moving towards the centre of an earthed conducting sphere of radius  $R$  with a velocity  $\sqrt{2}aR$  m/s. Where  $a$  is positive constant. If current flowing in the ammeter shown in figure when  $q$  is at a distance  $aR\sqrt{2}$  from centre of sphere. Is  $\frac{q}{a\sqrt{x}}$  find  $x$ .



[Watch Video Solution](#)

**PRACTICE SHEET (EXERCISE - II LEVEL-I (MAIN) (Straight Objective Type Questions))**

1. A copper wire of cross - sectional area  $3.4 \text{ mm}^2$  and length of the wire 400m, specific resistivity of copper is  $1.7 \times 10^{-8} \Omega - m$ . Then the resistance of the wire is

A.  $20\Omega$

B.  $200\Omega$

C.  $2\Omega$

D.  $2k\Omega$

**Answer: C**



**Watch Video Solution**

2. Four wires made of same material have different lengths and radii, the wire having more resistance in the following case is

A.  $l = 100\text{cm}, r = 1\text{mm}$

B.  $l = 50\text{cm}, r = 2\text{mm}$

C.  $l = 100\text{cm}, r = \frac{1}{2}\text{mm}$

D.  $l = 50\text{cm}, r = \frac{1}{2}\text{mm}$

**Answer: C**



**Watch Video Solution**

3. The resistance of the series combination of two resistances is  $S$ . When they are joined in parallel, the total resistance is  $P$ . If  $S = nP$ , then the minimum possible value of  $n$  is :

A. 4

B. 1

C. 2

D. 3

**Answer: A**



**Watch Video Solution**

4. Three resistances  $2\Omega$ ,  $3\Omega$  and  $4\Omega$  are connected in parallel. The ratio of currents passing through them when a potential difference is applied across its ends will be

A. 2: 3: 6

B. 1: 2: 3

C. 1: 1: 1

D. 6: 3: 2

**Answer: D**



**Watch Video Solution**

5. You are given several identical resistors each of value  $5\Omega$  and each capable of carrying a maximum current of 2A. It is required to make a suitable combination of these resistance to produce a resistance of  $2.5\Omega$  which can carry current of 4A. The minimum number of resistances required for this job is

A. 2

B. 4

C. 6


D. 8

**Answer: A**



**Watch Video Solution**

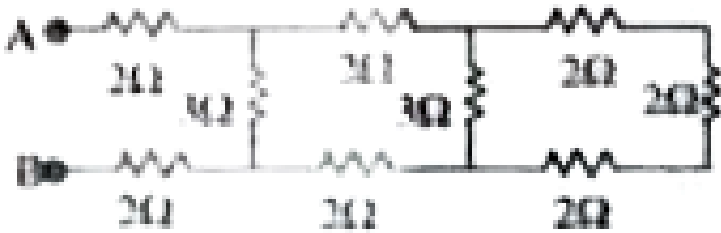6. The effective resistance between A and B in the given circuit is



A.  $20\Omega$

B.  $7\Omega$

C.  $3\Omega$

D.  $6\Omega$


**Answer: D**



Watch Video Solution



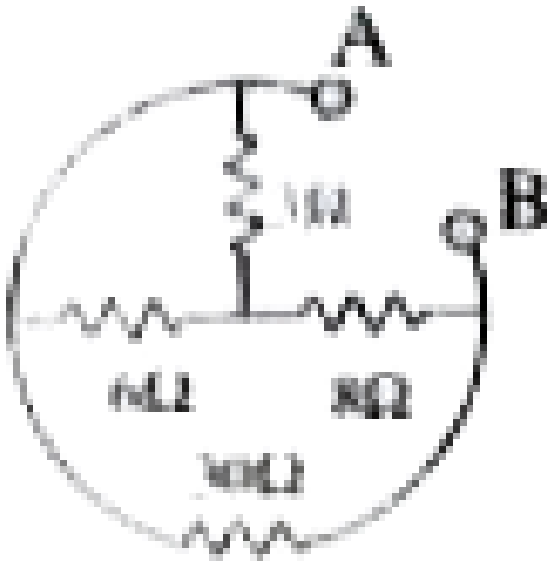7. The effective resistance between A and B in the given circuit is




- A.  $1.5\Omega$
- B.  $7.5\Omega$
- C.  $4.7\Omega$

D.  $12\Omega$

Answer: B

 Watch Video Solution

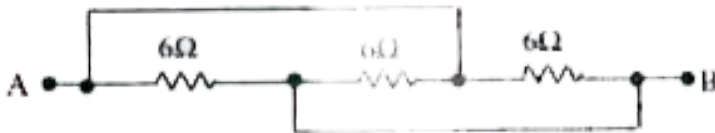8. The effective resistance between A and B in the given circuit is



A.  $18\Omega$

B.  $6\Omega$

C.  $2\Omega$

D.  $3\Omega$

**Answer: C**



**Watch Video Solution**

9. A hollow cylinder ( $\rho = 2.2 \times 10^{-8}\Omega - m$ ) of length 3 m has inner and outer diameters are 2 mm and 4 mm respectively. The resistance of the cylinder is

A.  $0.35 \times 10^{-3}\Omega$

B.  $3 \times 10^{-3}\Omega$

C.  $7 \times 10^{-3}\Omega$

D.  $3.1 \times 10^{-3}\Omega$

**Answer: C**



**Watch Video Solution**

**10.** A metal block has lengths 50 cm, breadth 30cm and thickness 20cm. When current passes through it parallel to its length and parallel to its breadth, the ratio of maximum to minimum resistance of that block is

A. 4: 25

B. 25: 4

C. 25: 9

D. 9: 25

**Answer: C**



**Watch Video Solution**

**11.** Two wires of same dimension but resistivity  $\rho_1$  and  $\rho_2$  are connected in series. The equivalent resistivity of the combination is

A.  $\frac{\rho_1 X_1 + \rho_2 X_2}{X_1 + X_2}$

B.  $\frac{\rho_1 X_2 + \rho_2 X_1}{X_1 - X_2}$

C.  $\frac{\rho_1 X_2 + \rho_2 X_1}{X_1 + X_2}$

D.  $\frac{\rho_1 X_1 + \rho_2 X_2}{X_1 - X_2}$

**Answer: A**



Watch Video Solution

12. The temperature coefficient of resistivity of material is  $0.0004/\text{k}$ . When the temperature of the material is increased by  $50^\circ\text{C}$ , its resistivity increases by  $2 \times 10^{-8}$  ohm-m. The initial resistivity of the material in ohm-m is

A.  $50 \times 10^{-8}$

B.  $90 \times 10^{-8}$

C.  $100 \times 10^{-8}$

D.  $200 \times 10^{-8}$

**Answer: C**



Watch Video Solution

13. The resistance of a bulb filament is  $100\Omega$  at a temperature of  $100^\circ C$ . If its temperature coefficient of resistance be  $0.005 \text{ per } ^\circ C$ , its resistance will become  $200\Omega$  at a temperature of

A.  $300^\circ C$

B.  $400^\circ C$

C.  $500^\circ C$

D.  $200^\circ C$

**Answer: B**



Watch Video Solution

**14.** This question contains Statement-1 and Statement-2. Of the four choices given after the statement, choose the one that best describes the two statements.

Statement-1 : The temperature dependence of resistance is usually given as  $R = R_0(1 + \alpha\Delta t)$ . The resistance of a wire changes from  $100\Omega$  to  $150\Omega$  when its temperature is increased from  $27^\circ C$  to  $227^\circ C$ .

This implies that  $\alpha = 2.5 \times 10^{-3} / .^\circ C$ .

Statement -2 :  $R = R_1(1 + \alpha\Delta T)$  is valid only when the change in the temperature  $\Delta T$  is small and

$$\delta R = (R - R_0) \ll R_0$$



- A. Statement-1 is true, statement-2 is true,  
Statement-2 is the correct explanation of  
statement-1.
- B. Statement-1 is true, statement-2 is true,  
Statement-2 is not the correct explanation of  
statement-1.
- C. Statement-1 is false, Statement-2 is true
- D. Statement-1 is true, Statement-2 is false


**Answer: D**



**Watch Video Solution**

**PRACTICE SHEET (EXERCISE - II LEVEL-II (ADVANCED) (More than One correct answer Type Questions))**

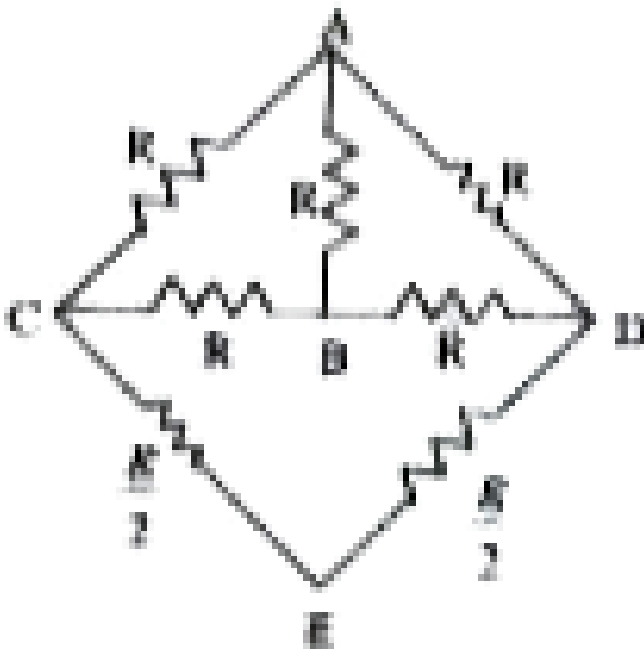1. The adjacent figure shows a resistance network with value of each resistance is  $R$ . The equivalent resistance across  $A$  and  $B$ .,  $A$  and  $C$ . and  $C$  and  $B$ . are  $R_{AB}$ ,  $R_{AC}$  and  $R_{CB}$  respectively then



A.  $R_{AB} = R_{AC} = R_{CB}$

B.  $R_{AB} = 2R_{AC}$


C.  $R_{AB} = R_{CB}$

D.  $R_{AB} = \frac{R}{2}$

Answer: A::C::D

 Watch Video Solution

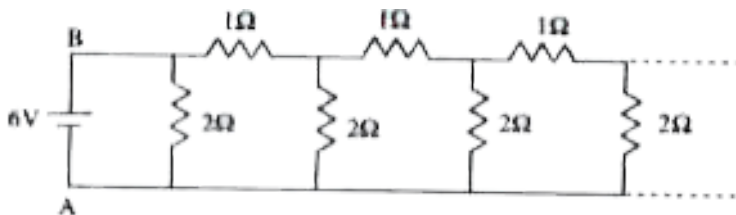2. An infinite ladder network of resistances is constructed with  $1\Omega$  and  $2\Omega$  resistances as shown



A. Effective resistance between A & B is  $2\Omega$

B. Effective resistance between A & B is  $1\Omega$

C. Current through  $2\Omega$  resistor nearest to battery is

6A

D. Current through  $2\Omega$  resistor nearest to battery is

3A


**Answer: B::C**



**Watch Video Solution**

3. In the circuit shown some potential difference is applied between A and B. The equivalent resistance

between A and B is  $R$ . Then

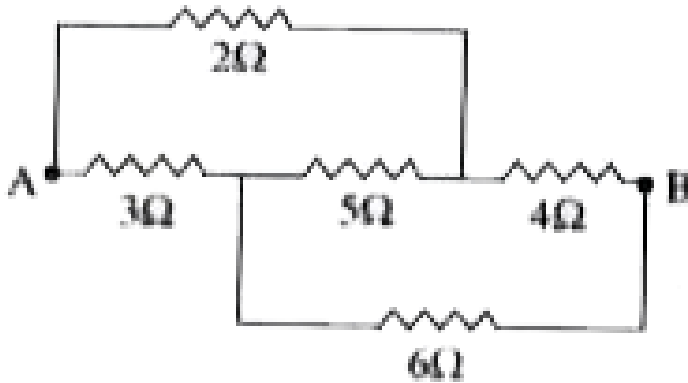

A. no current flows through  $5\Omega$  resistor

B.  $R = 15\Omega$

C.  $R = 12.5\Omega$

D.  $R = \frac{18}{5}\Omega$

**Answer: A::D**



**Watch Video Solution**

# PRACTICE SHEET (EXERCISE - II LEVEL-II (ADVANCED) (Matrix matching Type Questions))


1. Wires each of resistance  $R$  form a cubical wire frame as shown in figure. Match the following.

## COLUMN-I

- A) Resistance across AB
- B) Resistance across AC
- C) Resistance across AE
- D) Resistance across AB, if the wire AB is removed
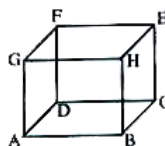
## COLUMN-II


- p)  $\frac{5R}{6}$
- q)  $\frac{7R}{12}$
- r)  $\frac{3R}{4}$
- s)  $\frac{7R}{5}$



Watch Video Solution

# PRACTICE SHEET (EXERCISE - II LEVEL-II (ADVANCED) (Integer Type Questions))

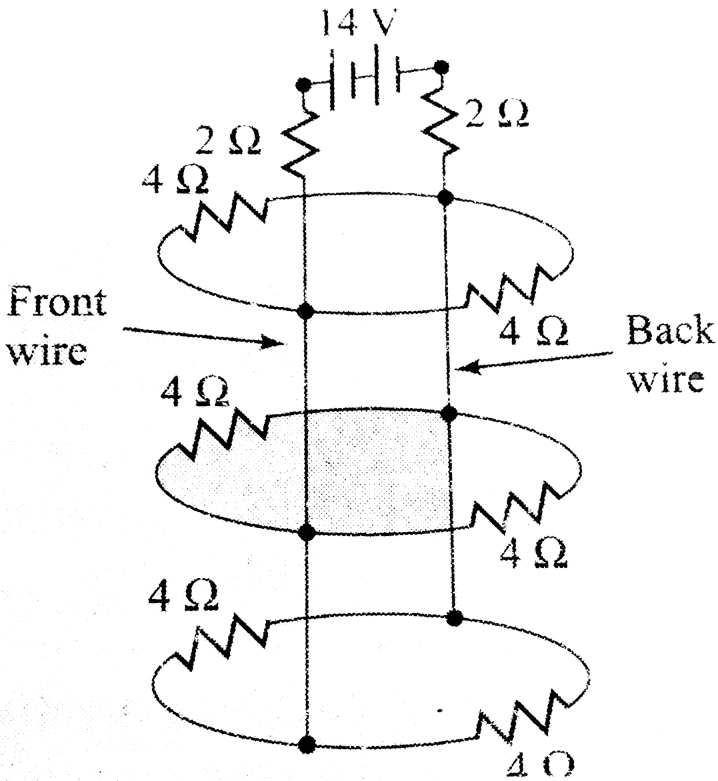1. Find the current supplied by the source in fig. The resistors are mounted around in a cylindrical form.



[Watch Video Solution](#)

2. The resistance of a wire is  $5\Omega$  at  $50^\circ C$  at  $6\Omega$  at 100.



Watch Video Solution

**PRACTICE SHEET (EXERCISE - III LEVEL-I (MAIN) (Straight Objective Type Questions))**

1. A 50V battery is connected across a 10 ohm resistor.

The current is 4.5A is flowing through the resistor then

the internal resistance of the battery is

A. zero

B.  $0.5\Omega$

C.  $1.1\Omega$



D.  $5\Omega$

**Answer: C**



**Watch Video Solution**

2. A cell whose e.m.f. is 2V and internal resistance is  $0.1\Omega$  is connected with a resistance of  $3.9\Omega$  the voltage across the cell terminal will be

A. 0.5 V

B. 1.9 V

C. 1.95 V

D. 72 V

**Answer: C**



**Watch Video Solution**

3. The emf of a daniel cell is 1.08V. When the terminals of the cell are connected to resistance of  $3\Omega$ , the potential difference across the terminals is found to be 0.6 V. Then , the internal resistance of the cell is

A.  $1.8\Omega$

B.  $2.4\Omega$

C.  $3.24\Omega$

D.  $0.2\Omega$

**Answer: B**



**Watch Video Solution**

4. A student is asked to connect four cells of e.m.f of 1 V and internal resistance 0.5 ohm in series with a external resistance of 1 ohm. But one cell is wrongly connected by him with its terminal reversed, the current in the circuit is

A.  $\frac{1}{3} A$

B.  $\frac{2}{3} A$

C.  $\frac{3}{4} A$

D.  $\frac{4}{3} A$

**Answer: B**



**Watch Video Solution**

5. When two identical cells are connected either in series or in parallel across a 4 ohm resistor, they send the same current through it. The internal resistance of the cell in ohm is

A. 1.2


B. 2

C. 4

D. 4.8

Answer: C

 Watch Video Solution

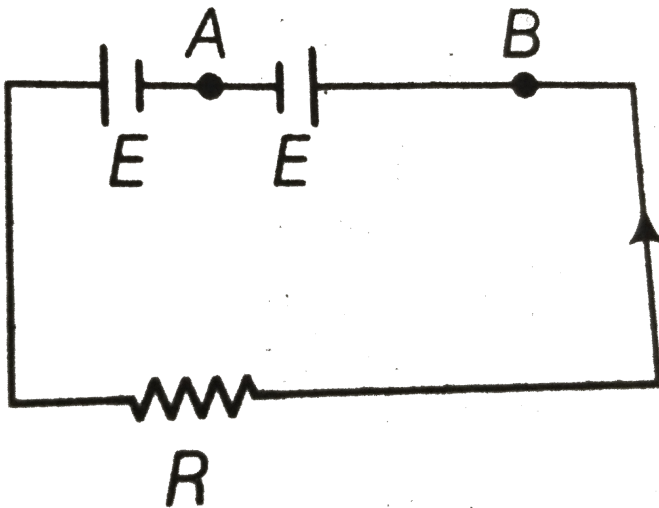

6.

Two cells of same emf  $E$  but internal resistance  $r_1$  and  $r_2$  are connected in series to an external resistor  $R$ (figure). What should be the value of  $R$  so

that the potential difference across the terminals of the first cell becomes zero?

A.  $\sqrt{r_1 r_2}$

B.  $r_1 + r_2$

C.  $r_1 - r_2$

D.  $\frac{r_1 + r_2}{2}$

**Answer: C**



**Watch Video Solution**

7. the current in a circuit containing a battery connected to  $2\Omega$  resistance is  $0.9A$ . When ana

additional resistance of  $8\Omega$  is connected to the same battery the current observed in the circuit is  $0.3A$ . Then the internal resistance of the battery is  $x\Omega$ . Find value of  $x$ .

A.  $0.1\Omega$

B.  $0.5\Omega$

C.  $1\Omega$

D. zero

**Answer: B**



**Watch Video Solution**

8. A 6 V cell with  $0.5\Omega$  internal resistance , a 10 v cell with  $1\Omega$  internal resistance and a  $12\Omega$  external resistance are connected in parallel . The current (in amper) through the 10 V cell is

- A. 0.6
- B. 2.27
- C. 2.87
- D. 5.14


**Answer: C**



**Watch Video Solution**



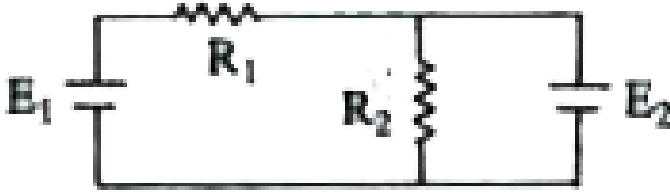9. Two cells of emf  $E_1$  and  $E_2$  are connected to two resistors  $R_1$  and  $R_2$  as shown. If  $E_2$  is short circuited then current through  $R_1$  and  $R_2$  are



- A.  $\frac{E_1}{E_2}, 0$
- B.  $0, \frac{E_1}{R_2}$
- C.  $\frac{E_1}{R_1}, 0$
- D.  $0, \frac{E_1}{R_1}$

**Answer: C**

 [Watch Video Solution](#)

10. When two cells of different emf's are connected in series to an external resistance the current is 5A. When the poles of one cell are interchanged, the current is 3A. The ratio of emf's of two cell is

A. 2:1

B. 1:3

C. 5:1


D. 4:1

**Answer: D**



**Watch Video Solution**

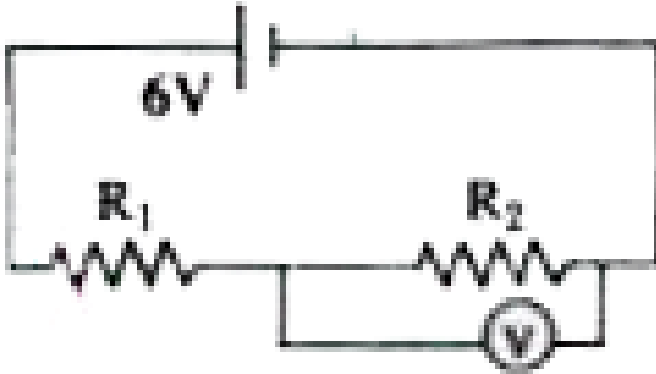11. In the circuit  $R_1 = 400$  ohm and  $R_2 = 200$  ohm. If the resistance of the voltmeter  $R = 10,000$  ohm, voltmeter reading is




- A. 2V
- B. greater
- C. greater than 3V
- D. less than 2V

**Answer: D**



Watch Video Solution

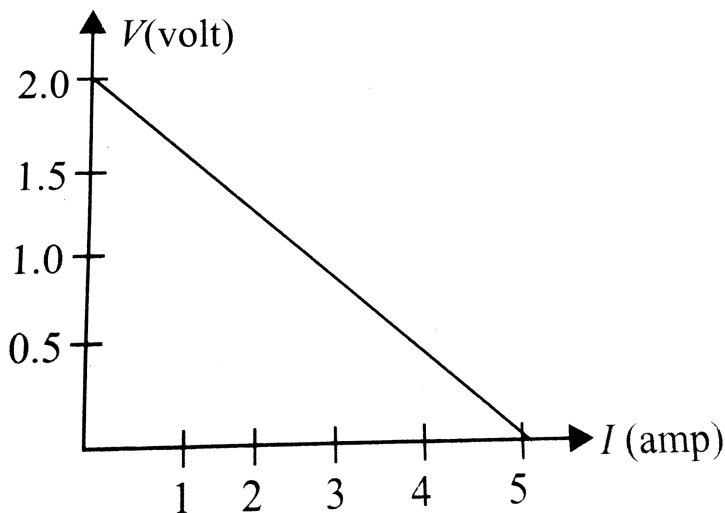12. For a cell, a graph is plotted between the potential difference  $V$  across the terminals of the cell and the current  $I$  drawn the cell. The emf and the internal resistance of the cell are  $E$  and  $r$ , respectively. Then



A.  $E = 2V, r = 0.5\Omega$

B.  $E = 2V, r = 0.4\Omega$

C.  $E > 2V, r = 0.5\Omega$

D.  $E > 2V, r = 0.4\Omega$

**Answer: B**



**Watch Video Solution**

**13.** How many cells each marked  $(6V - 12A)$  should be connected in mixed grouping so that it may be marked  $(24V - 24A)$

A. 4

B. 8

C. 12

D. 6

**Answer: B**



**Watch Video Solution**

**14.** Find the minimum number of cells required to produce an electric current of 1.5 A through a resistance of  $30\Omega$ . Given that the emf of each cell is 1.5 V and internal resistance  $1.0\Omega$ .

A. 30

B. 120

C. 40

D. 60

**Answer: B**



**Watch Video Solution**

**15.** Three equal resistance each of  $3\Omega$  are in series and connected to cell of internal resistance one ohm. If three resistances are parallel and connected to the same cell. Then the ratio of the respective currents through the electric circuits in the two cases is

A.  $1/8$

B.  $1/7$


C.  $1/5$

D.  $1/3$

**Answer: C**

 [Watch Video Solution](#)

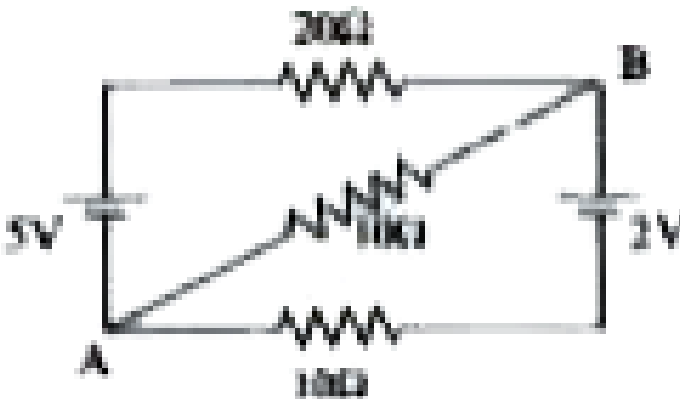16. The P.d between the terminals A&B is \_\_\_\_\_





A. 2V

B. 3V

C. 3.6V

D. 1.8V

**Answer: D**



**Watch Video Solution**

**PRACTICE SHEET (EXERCISE - III LEVEL-II (ADVANCED) (More than One correct answer Type Questions))**

**1. Choose the correct statement from the following**

A. If  $n$  identical cells, each of emf  $E$  and internal resistance  $r$  are connected in series, the emf of combination is  $nE$  and the internal resistance of the combination is  $nr$ .

B. If  $n$  identical cells, each of emf  $E$  and internal resistance  $r$  are connected in parallel, the emf of the combination is  $E/n$  and the internal resistance of the combination is  $r/n$

C. Cells should be connected in series, if the external resistance  $R$  is greater than internal resistance  $r$

D. Cells should be connected in parallel if  $R$  is smaller than  $r$

**Answer: A::C::D**



**Watch Video Solution**

2. 24 cells, each of emf 1.5V and internal resistance is  $2\Omega$  connected to  $12\Omega$  series external resistance. Then,

A. in order to send the maximum current through a  $12\Omega$  resistor, connect the two rows of 12 cells in series

B. the current in each row is  $0.375A$

C. the current in each cell is 0.75A

D. potential difference across  $12\Omega$  resistor is 4.5V


**Answer: A::B**



**Watch Video Solution**

3. Both terminals of a battery of emf  $E$  and internal resistance  $r$  are grounded as shown. Select the correct

alternative(s).

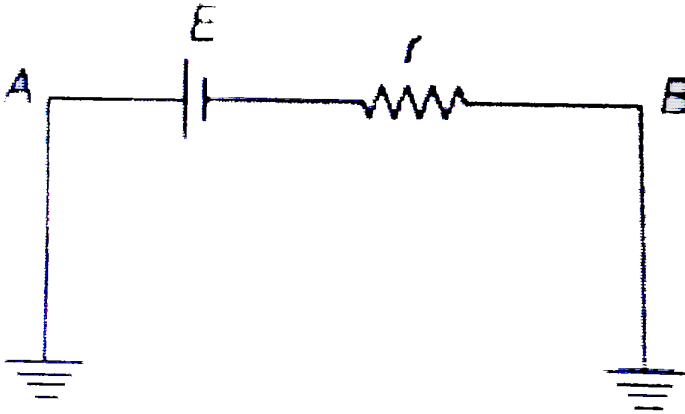

- A. Potential difference across A and B is Zero
- B. Potential difference across A and B is  $E$ .
- C. Current through the battery is zero
- D. Current through the battery is  $\frac{E}{r}$


**Answer: A::D**

 [Watch Video Solution](#)

# PRACTICE SHEET (EXERCISE - III LEVEL-II (ADVANCED))

## (Linked Comprehension Type Questions))

### 1. Passage :

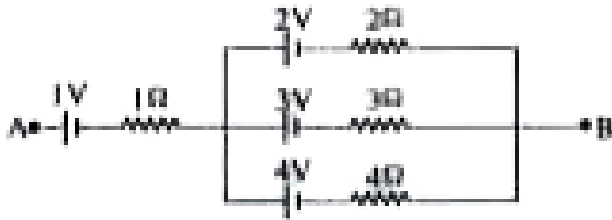

From the above circuit, the equivalent emf between the terminals A and B is


- A.  $\frac{49}{13} V$
- B.  $\frac{36}{13} V$
- C.  $\frac{37}{13} V$
- D.  $\frac{24}{13} V$

Answer: A



Watch Video Solution

2. Passage :

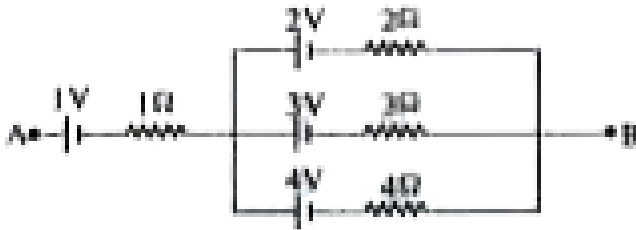

From the above circuit, equivalent internal resistance of the combination is

A.  $\frac{13}{12} \Omega$

B.  $\frac{25}{13} \Omega$


C.  $\frac{13}{24} \Omega$

D.  $\frac{24}{13} \Omega$

Answer: B

 Watch Video Solution

3. Passage :

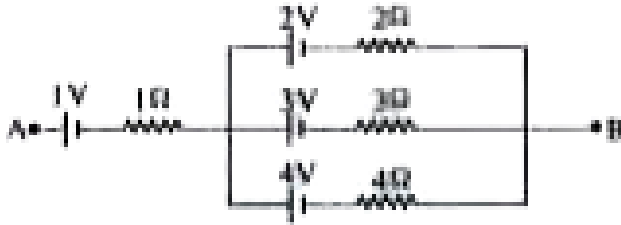

If the polarity of cell of 4V is reversed, the equivalent resistance between the terminals A and B is

A.  $\frac{12}{13} V$



B.  $\frac{25}{13}V$

C.  $\frac{37}{13}V$

D.  $\frac{1}{13}V$


**Answer: B**



**Watch Video Solution**

**PRACTICE SHEET (EXERCISE - III LEVEL-II (ADVANCED))  
(Matching Type Questions))**

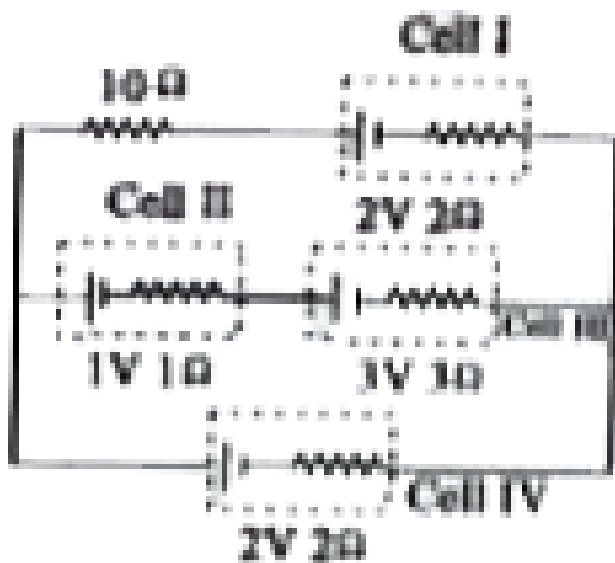1. For the circuit shown in fig. 4 cells are arranged.



In Column-I, the cell number is given while in Column-II, some statements related to cells are given. Match the entries of Column-I with the entries of Column-II.

**COLUMN-I**

- A) Cell I
- B) Cell II
- C) Cell III
- D) Cell IV

**COLUMN-II**

- p) Chemical energy of cell is decreasing
- q) Chemical energy of cell is increasing
- r) Work done by cell is +Ve
- s) Thermal energy developed in cell is +Ve



**Watch Video Solution**

# PRACTICE SHEET (EXERCISE - III LEVEL-II (ADVANCED))

## (Integer Type Questions))

1. Cells of emfs 10V and 20V are connected as shown.

When an ammeter is connected across A and B its

reads 1A, when connected across B and C it reads 5,


when connected across A and C it reads 3A, find the

resistance of the ammeter (in  $\Omega$ )



[Watch Video Solution](#)

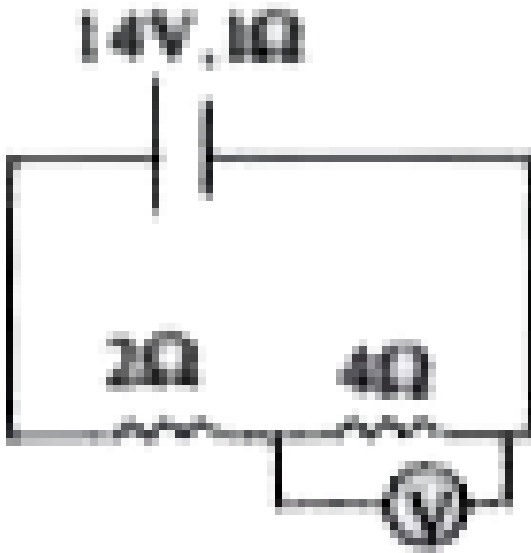
2. Voltmeter reading in the given circuit is (voltmeter is ideal)



[▶ Watch Video Solution](#)

**PRACTICE SHEET (EXERCISE - IV LEVEL-I (MAIN) (Straight Objective Type Questions))**

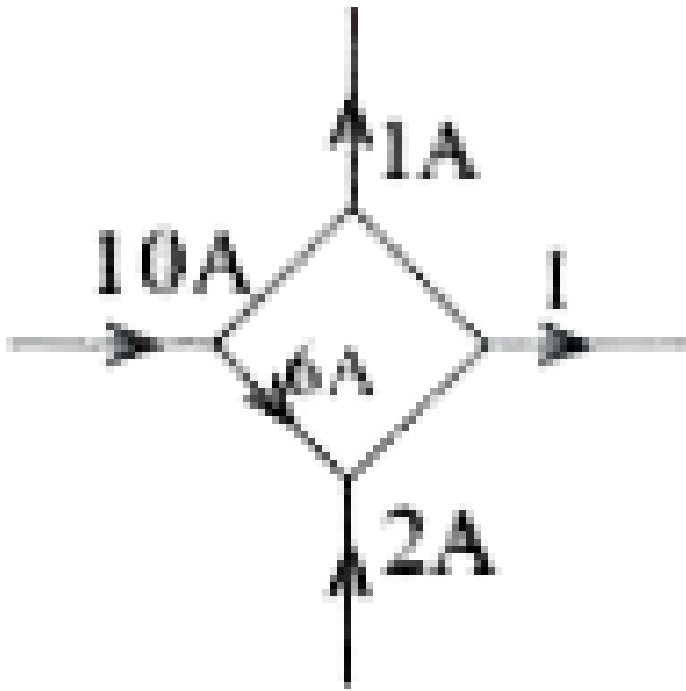1. The value of current  $I$ , in the figure shown will be



A. 11A

B. 19A

C. 13A


D. 9A

Answer: A



Watch Video Solution

2. Find E for the Given Loop

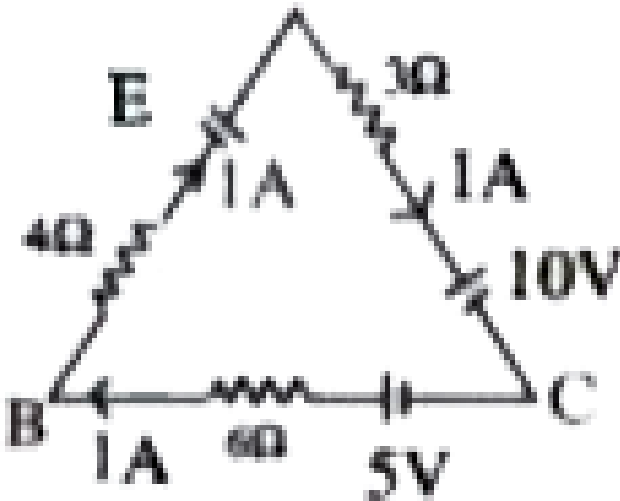

A. -24v

B. 18v


C. 4v

D. 0v

Answer: B

 Watch Video Solution

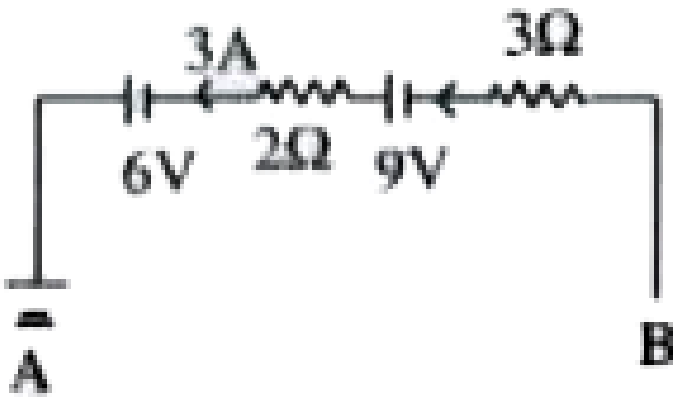3. The potential difference between points A and B is



A. 10v

B. 12v

C. 14v

D. 0v

**Answer: D**



**Watch Video Solution**

4. Four resistors A, and D form a Wheatstone bridge.

The bridge is balanced , when  $C = 100\Omega$  If A and B are interchanged the bridge balances for  $C = 121\Omega$ . The value of D is

A.  $100\Omega$

B.  $200\Omega$



C.  $300\Omega$

D.  $110\Omega$


**Answer: D**



**Watch Video Solution**

5. In the circuit shown in the figure, the value of Resistance X, when potential difference between the

point B and D is zero will be

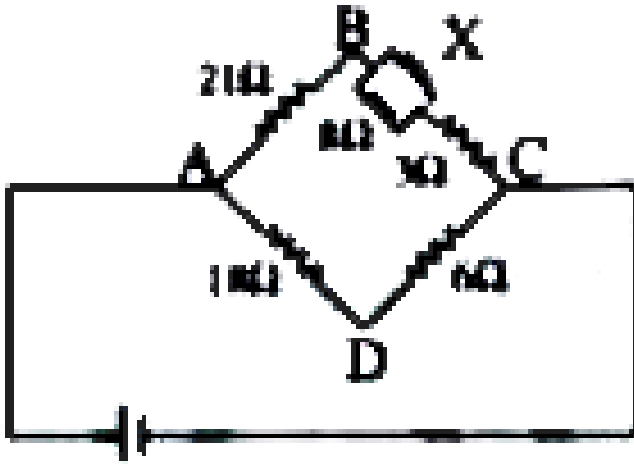

- A.  $9\Omega$
- B.  $8\Omega$
- C.  $6\Omega$
- D.  $4\Omega$

**Answer: B**

 [Watch Video Solution](#)

6. A  $6\Omega$  resistance is connected in the left gap of a meter bridge. In the second gap  $3\Omega$  and  $6\Omega$  are joined in parallel. The balance point of the bridge is at \_\_\_\_\_

A. 75 cm

B. 60 cm

C. 30 cm

D. 25 cm

**Answer: A**



**Watch Video Solution**

7. When an unknown resistance and a resistance of  $4\Omega$  are used in the left and right gaps of a meter bridge, the balance point is 50cm. The shift in the balance point if a  $4\Omega$  resistance is now connected parallel to the resistor in right gap \_\_\_\_\_

A.  $\frac{100}{3} \text{ cm}$

B.  $\frac{50}{3} \text{ cm}$

C.  $\frac{300}{3} \text{ cm}$

D.  $\frac{400}{5} \text{ cm}$

**Answer: B**



**Watch Video Solution**

8. When a conducting wire is connected in the left gap and known resistance in the right gap, the balance length is 75cm. If the wire is cut into 3 equal parts and one part is connected in the left gap, the balance length

- A. shifts left by 25cms
- B. shifts right by 25cms
- C. shifts left by 50cms
- D. shifts right by 50cms

**Answer: A**



**Watch Video Solution**

9. When a metal conductor connected to left gap of a meter bridge is heated, the balancing point

A. 50cm

B. 80cm

C. 40cm


D. 70cm

**Answer: A**



**Watch Video Solution**

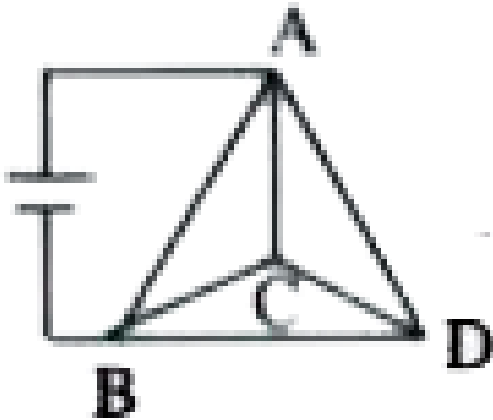10. A tetrahedron is consisting of 6 identical wires as shown in figure. Each wire is having a resistance of  $2\Omega$ . When an ideal cell of emf  $2V$  is connected across  $AB$ , as shown then the current through  $CD$  is



- A. 1A
- B.  $\frac{6}{19}A$
- C. 4A


D. Zero

Answer: D

 Watch Video Solution

**PRACTICE SHEET (EXERCISE - IV LEVEL-II (ADVANCED) (More than One correct answer Type Questions))**

1. Consider the given DC circuit.

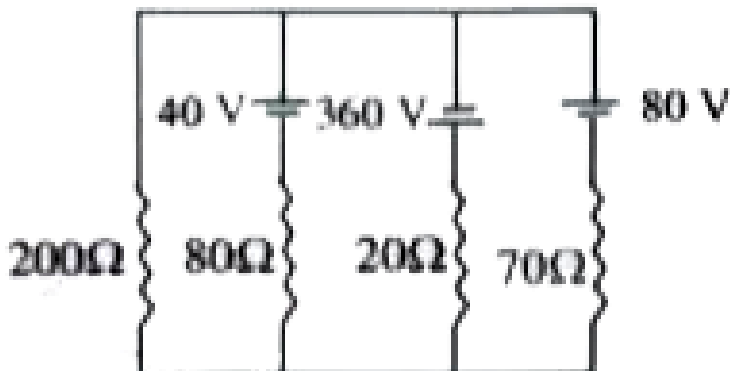



A. current in  $70\Omega$  resistance is 4A

B. Current in  $80\Omega$  resistance is 5A

C. potential drop across  $200\Omega$  resistance is 200V

D. current through  $200\Omega$  resistor is 0.5A

**Answer: A::C**



[Watch Video Solution](#)

2. In the circuit shown in the figure (A),  $R_3$  is a variable resistance. As the value  $R_3$  is changed, the current  $I$  through the cell varies as shown in the figure (B). As  $R_3 \rightarrow \infty$ , the current  $I \rightarrow 6$  A. What is the value. of

the sum of the resistances  $R_1$  and  $R_2$  in ohms?

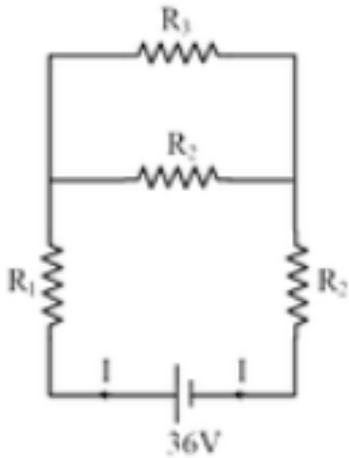


Figure (A)

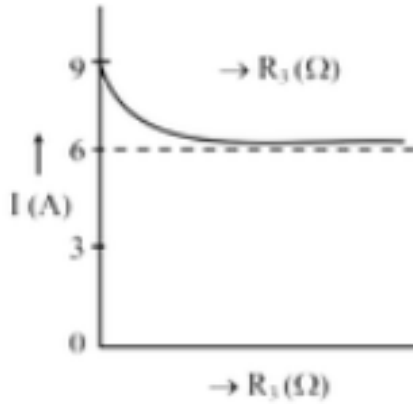


Figure (B)

A.  $R_1 = 2$

B.  $R_2 = 2$

C.  $R_1 = 3$

D.  $R_2 = 4$

**Answer: A::B**




**Watch Video Solution**

**PRACTICE SHEET (EXERCISE - IV LEVEL-II (ADVANCED))**  
**(Linked Comprehension Type Questions))**

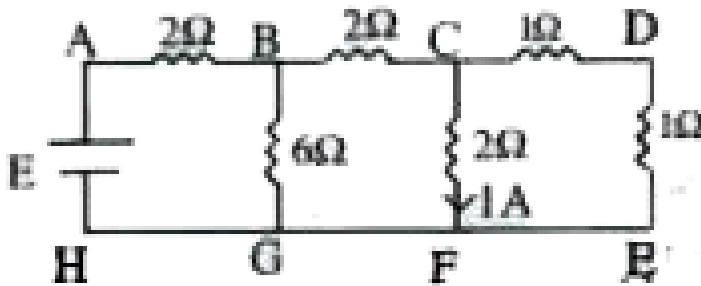**1. Passage:**

The figure shows a network of resistors and a battery. If 1A current flows through the branch CF, then answer the following questions



The current through

A. branch DE is 1A

B. branch BC is 2A

C. branch BG is 4A

D. branch HG is 6A


**Answer: A::B**



**Watch Video Solution**

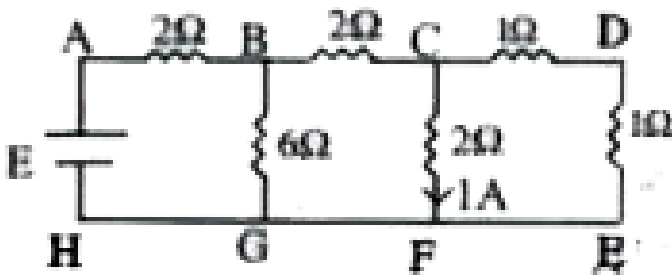**2. Passage:**

The figure shows a network of resistors and a battery. If 1A current flows through the branch CF, then answer the following questions



The emf  $E$  of the battery is

- A. 24V
- B. 12V
- C. 18V
- D. 6V


**Answer: B**



**Watch Video Solution**
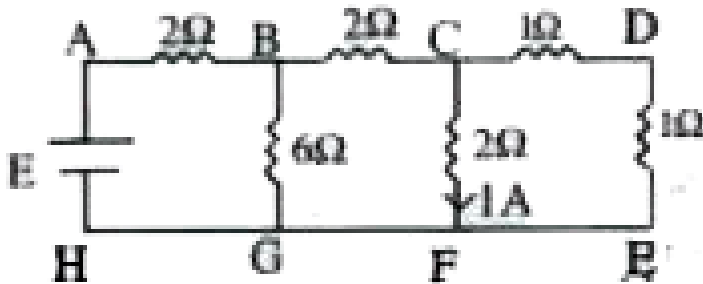
### 3. Passage:

The figure shows a network of resistors and a battery. If 1A current flows through the branch CF, then answer the following questions



The current through


- A. branch  $DE$  is zero
- B. branch  $BC$  is zero
- C. branch  $BG$  is  $0.5\text{A}$
- D. branch  $AB$  is  $1.5\text{A}$

Answer: A

 Watch Video Solution


**PRACTICE SHEET (EXERCISE - IV LEVEL-II (ADVANCED))**  
**(Integer Type Questions)**

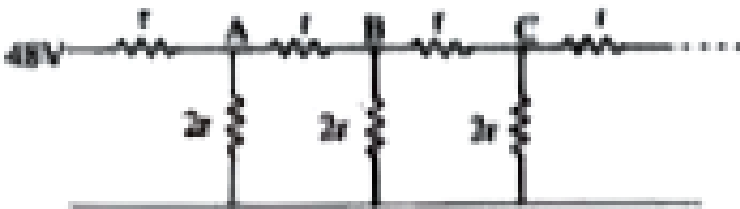1. At the end of the infinite network shown, 48V is applied. What is the voltage at C in volts?



 Watch Video Solution

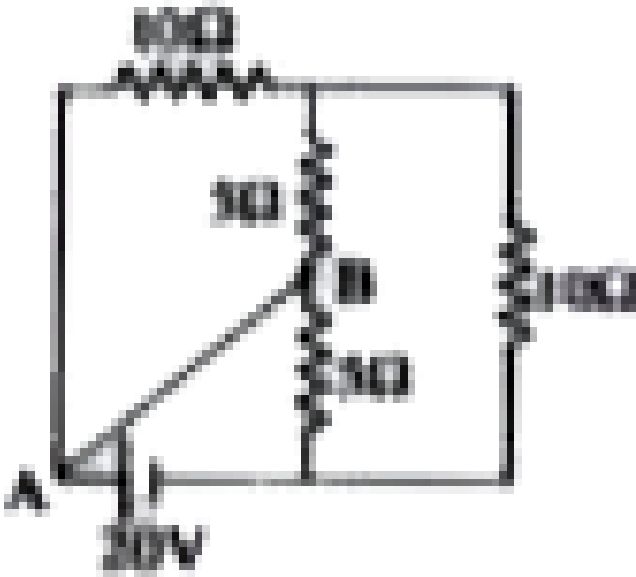2. Find the current in amperes in the branch AB in the circuit shown in the figure.



[▶ Watch Video Solution](#)

**PRACTICE SHEET (EXERCISE - V LEVEL-I (MAIN) (Straight Objective Type Questions))**



1. The emf of a battery A is balanced by a length of 80cm on a potentiometer wire. The emf of a standard cell 1v is balanced by 50cm. The emf of A is

A. 2v

B. 1.4v

C. 1.5v

D. 1.6v

**Answer: D**



**Watch Video Solution**

2. The balancing lengths of potentiometer wire are 800 cm and 600cm when two cells of emf's  $E_1$  and  $E_2$  are connected in the secondary circuit first in series and then terminals of one cell is reversed,  $\frac{E_1}{E_2}$  is equal to

A.  $1/11$

B.  $14/11$

C.  $7/1$

D.  $4/3$

**Answer: C**



**Watch Video Solution**

3. When 6 identical cells of no internal resistance are connected in series in the secondary circuit of a potentiometer, the balancing length is  $l$ , balancing length becomes  $1/3$  when some cells are connected wrongly, the number of cells connected wrongly are

A. 1

B. 3

C. 2

D. 4

**Answer: C**



**Watch Video Solution**

4. A battery of unknown emf connected to a potentiometer has balancing length 560 cm. If a resistor of resistance 10 ohm, is connected in parallel with the cell the balancing length change by 60 cm. If the internal resistance of the cell is  $\frac{n}{10}$  ohm, the value of 'n' is

A. 3.6

B. 2.4

C. 1.2

D. 0.6

**Answer: C**



**Watch Video Solution**

5. The resistivity of a potentiometer wire is, if the area of cross section of the wire is  $4\text{cm}^2$ . The current flowing in the circuit is 1A, the potential gradient is 7.5 v/m \_\_\_\_\_

A.  $3 \times 10^{-3} \Omega - m$

B.  $2 \times 10^{-6} \Omega - m$

C.  $4 \times 10^{-2} \Omega - m$

D.  $5 \times 10^{-4} \Omega - m$

**Answer: A**



**Watch Video Solution**

6. The length of potentiometer wire is 200 cm and the emf of standard cell in primary circuit is  $E$  volts. It is employed to a battery of emf 0.4 v the balance point is obtained at  $l = 40$  cm from positive end, the  $E$  of the battery is (cell in primary is ideal and series resistance is zero)

A. 4v

B. 2v

C. 5v

D. 7v

**Answer: B**



**Watch Video Solution**

7. The emf of a cell is 2V and its internal resistance is 2 ohm. A resistance of 8 ohm is joined to battery in parallel. This is contacted in secondary circuit of potentiometer. If IV standard cell balances for 100cm of potentiometer wire, the balance point of above cell is

A. 120cm

B. 240cm

C. 160cm

D. 116cm

**Answer: C**



Watch Video Solution

8. A galvanometer has coil of resistance  $50\Omega$  and shows full deflection at  $100\mu A$ . The resistance to be added for the galvanometer to work as an ammeter of range  $10\text{mA}$  is nearly

- A.  $0.5\Omega$  in series
- B.  $0.5\Omega$  in parallel
- C.  $5.0\Omega$  series
- D.  $5.0\Omega$  in parallel

**Answer: B**



Watch Video Solution



9. A galvanometer of resistance  $1000\Omega$  gives full-scale deflection for a current of  $1\text{mA}$ . To measure a P.D of  $10\text{V}$ , the resistance to be connected with the galvanometer is

- A.  $9k\Omega$  in series
- B.  $9k\Omega$  is parallel
- C.  $10k\Omega$  in series
- D.  $1k\Omega$  parallel.

**Answer: A**



Watch Video Solution

10. A galvanometer of 25 ohm resistance can read a maximum current of 6mA. It can be used as a voltmeter to measure maximum potential difference of 6V by connecting a resistance to galvanometer. Identify the correct choice from the following

- A.  $1025\Omega$  in series
- B.  $1025\Omega$  is parallel
- C.  $975\Omega$  is series
- D.  $975\Omega$  in parallel

**Answer: C**



**Watch Video Solution**

11. A galvanometer has a current range of 15mA and voltage range of 750mv. To convert this galvanometer into an ammeter of range 25A, the shunt resistance required is nearly

A.  $0.2\Omega$

B.  $0.02\Omega$

C.  $0.03\Omega$

D.  $0.5\Omega$

**Answer: B**



**Watch Video Solution**

12. If a current of 0.5 ampere flows through a metallic wire for 2 hour then how many electrons flow through the wire ?

A.  $12.5\mu A$

B.  $12.5mA$

C.  $12.5 \times 10^{-7} A$

D.  $12.5 \times 10^{-3} mA$

**Answer: A**



**Watch Video Solution**

13. two galvanometers of resistance  $100\Omega$  and  $50\Omega$ , are  $10^{-8} A/\text{div}$  and  $2 \times 10^{-5} A/\text{div}$  respectively. In which case the voltage sensitivity is more ?

- A. more in case I
- B. more in case II
- C. same in both cases
- D. can't say

**Answer: A**



**Watch Video Solution**

14. When 0.005A current flows through a moving coil galvanometer, it gives fullscale deflection. It is converted into a voltmeter to read 5 Volt, using an external resistance of  $975\Omega$ . The resistance of galvanometer in ohms is

A. 5

B. 10

C. 15

D. 25

**Answer: D**



**Watch Video Solution**

15. A galvanometer of resistance  $40\Omega$  and current passing through it is  $100\mu A$  per division. The full scale has 50 divisions. If it is converted into an ammeter of range 2A by using a shunt, then the resistance of ammeter is

A.  $\frac{40}{399}\Omega$

B.  $\frac{4}{399}\Omega$

C.  $0.01\Omega$

D.  $0.4\Omega$

**Answer: A**



**Watch Video Solution**

16. In the process of electroplating  $m$  gram of silver is deposited when 4 amp of current flows for 2 min. The amount in (gm) of silver deposited by 6 amp of current flowing for 40 second will be

A. 10

B. 8

C. 6

D. 4

**Answer: C**



**Watch Video Solution**



17. The weight of a body at earth's surface is  $W$ . At a depth half way to the centre of earth it will weight

A.  $4W$

B.  $W/4$

C.  $2W$

D.  $W/2$

**Answer: A**



**Watch Video Solution**

18. In an experiment for calibration of voltmeter, a standard cell of emf 1.5V is balanced at 300cm length

of potentiometer wire. The P.D across a resistance in the circuit is balanced at 1.25m. If a voltmeter is connected across the same resistance. It reads 0.65V. The error in the volt meter is

A. 0.05V

B. 0.025V

C. 0.5V

D. 0.25V

**Answer: B**



**Watch Video Solution**

**19.** A potentiometer wire of length 10m and resistance 30 ohm is connected in series with a battery of emf 2.5V, internal resistance 5 ohm and external resistance R. If the fall of potential along the potentiometer wire is 50mV/m, the value of R is ohms is

A. 115

B. 80

C. 50

D. 100

**Answer: A**



**Watch Video Solution**

## PRACTICE SHEET (EXERCISE - V LEVEL-II (ADVANCED))

### (Straight Objective Type Questions))

1. A galvanometer having a resistance of  $50\Omega$  , gives a full scale deflection for a current of  $0.05\text{ A}$ . The length in metre of a resistance wire of area of cross- section  $2.97 \times 10^{-2}\text{ cm}^2$  that can be used to convert the galvanometer into an ammeter which can read a maximum of  $5\text{ A}$  current is (specific resistance of the wire  $= 5 \times 10^{-7}\Omega - m$ )

A. 9

B. 6

C. 3

D. 1.5

**Answer: C**



**Watch Video Solution**

2. A galvanometer has a resistance  $G$  and current  $I_g$  flowing in it. Produces full scale deflection. If  $S_1$  is the value of shunt which converts it into an ammeter of range  $0-I$  and  $S_2$  is the value of the shunt for the range  $0.2 I$ , then the ratio  $\frac{S_1}{S_2}$  will be:

A.  $\frac{1}{2} \left( \frac{I - I_g}{2I - I_g} \right)$

B.  $\frac{2I - I_g}{I - I_g}$

C.  $1/2$

D. 2


**Answer: B**



**Watch Video Solution**

3. Deflection of galvanometer in the circuit is 71 divisions. A shunt of  $15\Omega$  is connected parallel to galvanometer and value of R is adjusted such that main current remains the same. If the deflection in the galvanometer falls to 15 divisions then the resistance G

of galvanometer in (in ohm)

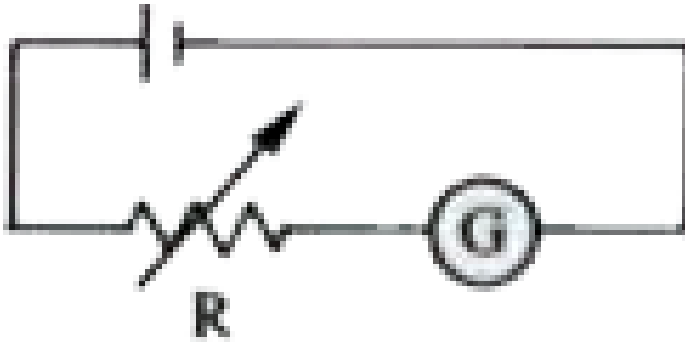

A.  $\frac{112}{3}$

B. 40

C. 56

D.  $\frac{142}{3}$

**Answer: C**



**Watch Video Solution**

4. The deflection of a galvanometer falls to  $1/10^{th}$  when a resistance of  $5\Omega$  is connected in parallel with it. If an additional resistance of  $2\Omega$  is connected in parallel to the galvanometer, the deflection is

A.  $\frac{1}{6}$  th

B.  $\frac{1}{16}$  th

C.  $\frac{2}{65}$  th

D.  $\frac{3}{36}$  th

**Answer: C**



**Watch Video Solution**



## PRACTICE SHEET (EXERCISE - V LEVEL-II (ADVANCED) (More than One correct answer Type Questions))

1. Mark out the correct options.

A. An ammeter should have small resistance

B. An ammeter should have large resistance

C. A voltmeter should have small resistance

D. A voltmeter should have large resistance

**Answer: A::D**



[Watch Video Solution](#)

2. An ammeter has a resistance of  $50\Omega$  and a full scale deflection current  $50\mu A$ . It can be used as a voltmeter or as a higher range ammeter provided that a resistance is added to it. Which of the following is/are true?

A. 10 V range with approximately  $200k\Omega$  resistance in series

B. 30 V range with approximately  $200k\Omega$  resistance in series

C. 1 mA range with  $50\Omega$  resistance in parallel

D. 0.1 mA range with  $50\Omega$  resistance in parallel

Answer: A::D



Watch Video Solution

3. Which of the following statements is/are correct for potentiometer circuit ?

A. Sensitivity varies inversely with the length of the potentiometer wire

B. Sensitivity is directly proportional to the potential difference applied across the potentiometer wire

C. Accuracy of a potentiometer can be increased only by increasing the length of wire

D. Range of the voltages to be measured depends upon the potential difference applied across the potentiometer wire

**Answer: C::D**



**Watch Video Solution**

**PRACTICE SHEET (EXERCISE - V LEVEL-II (ADVANCED))  
(Integer Type Questions))**

1. In meter bridge when P is kept in left gap, Q is kept in right gap, the balancing length is 40cm. If Q is shunted by  $10\Omega$ , the balance point shifts by 10cm. Resistance Q is

 [Watch Video Solution](#)

2. The length of potentiometer wire is 1m and its resistance is  $4\Omega$ . A current of 5mA is flowing in it. An unknown emf is balanced on 40 cm length of this wire. The unknown emf is x mv. What is the value of x. ?

 [Watch Video Solution](#)

## PRACTICE SHEET (EXERCISE - VI LEVEL-I (MAIN) (Straight Objective Type Questions))

1. 60W-220V and 100W-220V bulbs are connected in series to 220V mains. The power consumption is more in the bulb of :

- A. 60W
- B. 100W
- C. same for both the bulbs
- D. none

**Answer: A**



[Watch Video Solution](#)

2. 60 W- 220 bulb and 100 W- 220 V bulb are connected in parallel to main supply . Which bulb will draw more current ?

A. 60W

B. 100W

C. 1000W

D. all are equally bright

**Answer: C**



**Watch Video Solution**

3. A bulb of 100W - 250V is connected to 250V mains. If another similar bulb is connected to it in series , the total power consumption is :

A. 100 W

B. 200 W

C. 50 W

D. 400 W

**Answer: C**



**Watch Video Solution**



4. The power of a heating coil is  $P$ . It is cut into two equal parts. The power of one of them across same mains is :

A.  $P$

B.  $2P$

C.  $4P$

D.  $P/2$

**Answer: B**



**Watch Video Solution**

5. In a house there are four bulbs each of 50W and 5 fans each of 60W. If they are used at the rate of 6 hours a day. The electrical energy consumed in a month of 30 days is

A. 90000 units

B. 90 units

C. 0.9 units

D. 900 units

**Answer: B**



**Watch Video Solution**

6. An electric kettle has two coils. When one coil is switched on it takes 15 minutes and the other takes 30 minutes to boil certain mass of water. The ratio of times taken by them, when connected in series and in parallel to boil the same mass of water is :

A. 1 : 3

B. 5 : 2

C. 7 : 3

D. 9 : 2

**Answer: D**



**Watch Video Solution**

7. The ratio of distance of two satellites from the centre of earth is 1 : 4. The ratio of their time periods of rotation will be :

A. 1 : 2

B. 1 : 1

C. 2 : 1

D. 1 : 4

**Answer: C**



**Watch Video Solution**

8. A 10 V storage battery of negligible internal resistance is connected across a  $50\Omega$  resistor. How much heat energy is produced in the resistor in 1 hour

A. 7200J

B. 6200J

C. 5200J


D. 4200J

**Answer: A**



**Watch Video Solution**

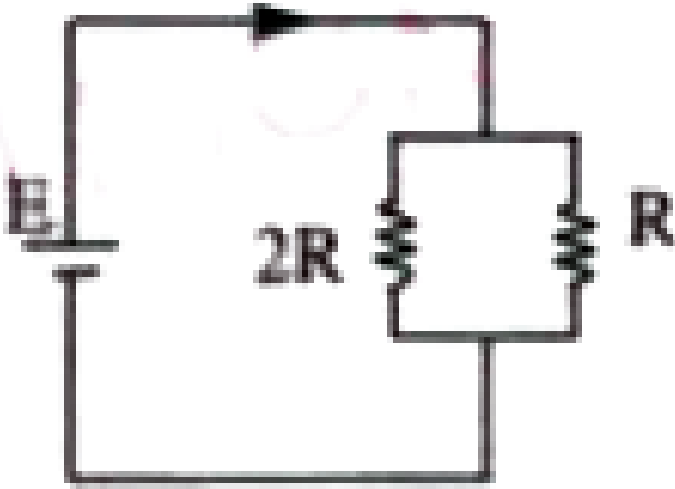9. What is the ratio of heat generated in  $R$  and  $2R$



A. 2:1

B. 1:2

C. 4:1

D. 1:4

**Answer: A**

 [Watch Video Solution](#)

10. The frequency of oscillation of current in the inductor is



A.  $5^0 C$

B.  $10^0 C$

C.  $20^0 C$

D.  $40^0 C$


**Answer: C**

 [Watch Video Solution](#)

# PRACTICE SHEET (EXERCISE - VI LEVEL-II (ADVANCED))

## (Straight Objective Type Questions))

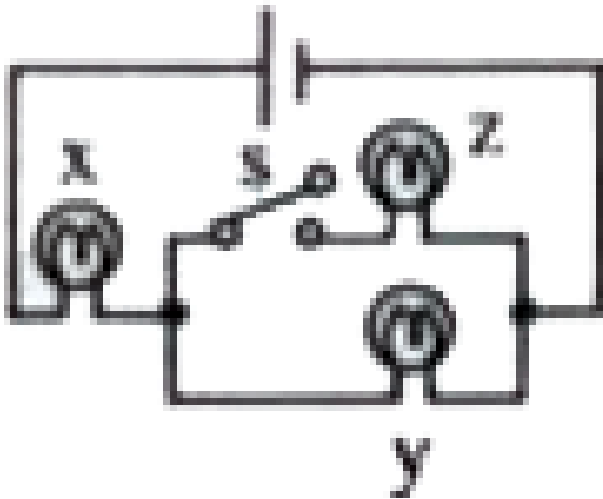1. If X, Y and Z in figure are identical lamps, which of the following changes to the brightnesses of the lamps occur when switch S is closed?



A. X stays the same, Y decreases

B. X increases, Y decreases



C. X increases, Y stays the same

D. X decreases, Y increases

**Answer: B**



**Watch Video Solution**

2. What will be genotypic ratio in the  $F_2$  generation of a monohybrid cross ?

A.  $\frac{4}{3} \frac{q^2 R}{t_0}$

B.  $\frac{2}{3} \frac{q^2 R}{t_0}$

C.  $\frac{8}{3} \frac{q^2 R}{t_0}$


D.  $\frac{q^2 R}{t_0}$

Answer: A



Watch Video Solution

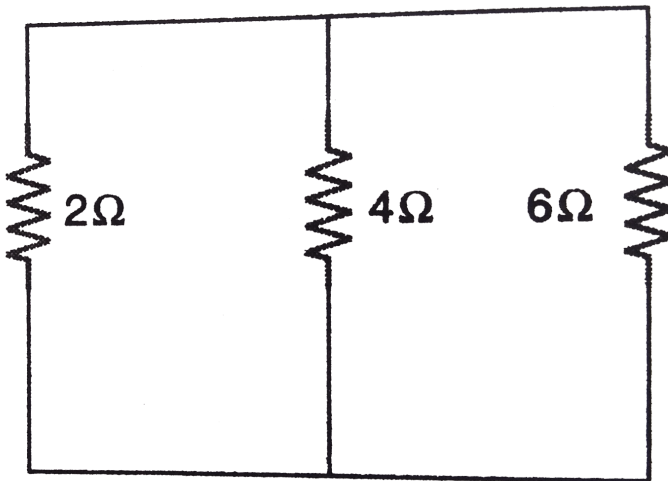3. In which branch of the circuit shown in figure a  $11V$  battery be inserted so that it dissipates minimum power. What will be the current through the  $2\Omega$  resistance for this potential of the battery?



A.  $6\Omega$  branch, 1A

B.  $4\Omega$  branch, 1A

C.  $2\Omega$  branch, 1A

D.  $6\Omega$  branch, 2A

**Answer: A**




[Watch Video Solution](#)

**PRACTICE SHEET (EXERCISE - VI LEVEL-II (ADVANCED) (More than One correct Type Questions))**

1. The value of the resistance R in figure is adjusted such that power dissipated in the  $2\Omega$  resistor is

maximum. Under this condition

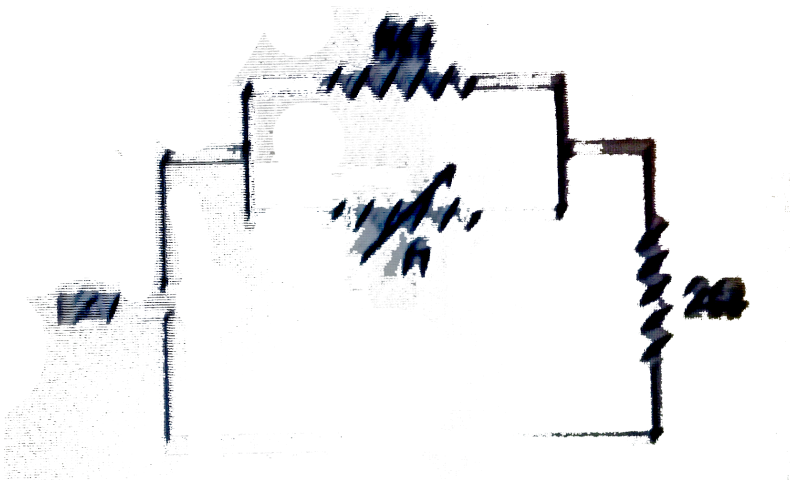

A.  $R = 0$

B.  $R = 8\Omega$

C. power dissipated in the  $2\Omega$  resistor is 72watts.


D. power dissipated in the  $2\Omega$  resistor is 8 watts.





**Answer: A::C**



**Watch Video Solution**

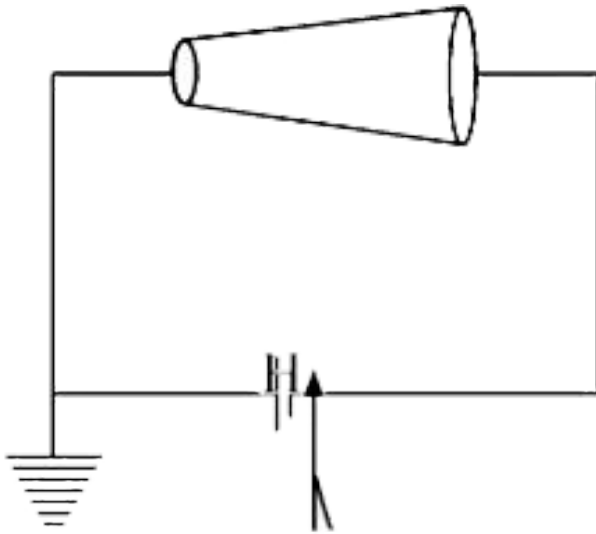2. A conductor is made of an isotropic material and has shape of a truncated cone. A battery of constant emf is connected across it and its left end is earthed as shown. If at a certain section at a distance  $x$  from left end, electric field intensity and the rate of generation of heat per unit length are  $E$  and  $H$  respectively, which of the following graphs is (are) correct?



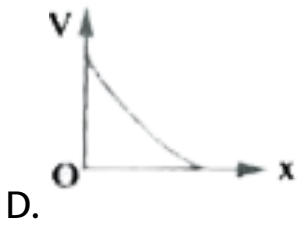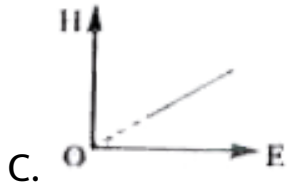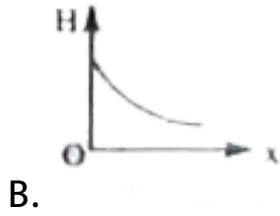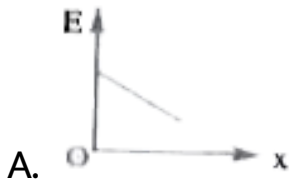

**Answer: B::C**



**Watch Video Solution**

3. Vocal cords occurs in

A. in parallel, the combination acts as a fuse of rating 20A

B. in parallel, the combination acts as a fuse of rating 5A

C. in series, the combination acts as a fuse of rating 10A.

D. in series, the combination acts as a fuse of rating 20A

**Answer: A::C**




**Watch Video Solution**

**PRACTICE SHEET (EXERCISE - VI LEVEL-II (ADVANCED))**  
**(Linked Comprehension Type Questions))**

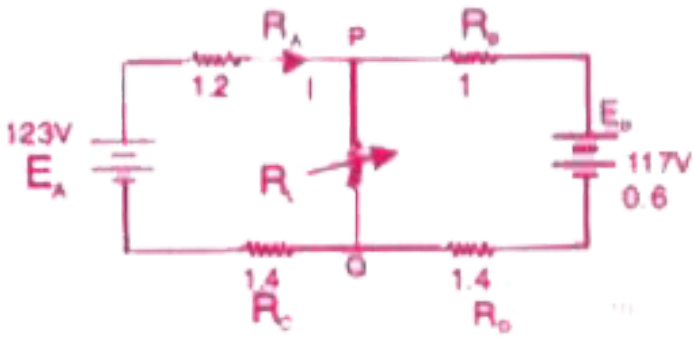**1. Passage :**

A battery  $E_A$  of 123 volts emf internal resistance  $0.4\Omega$  and a battery  $E_B$  of 117 V emf and internal resistance  $0.6\Omega$  supplies a current to load resistance  $R_L$  through four wires of resistors  $R_A = 1.2\Omega$ ,  $R_B = 1\Omega$ ,  $R_C = 1.4\Omega$  and  $R_D = 1.4\Omega$  as shown in figure.





The value of load resistance for maximum load power is


- A.  $1.5\Omega$
- B.  $3\Omega$
- C.  $4.5\Omega$
- D.  $6\Omega$

**Answer: A**

 [Watch Video Solution](#)
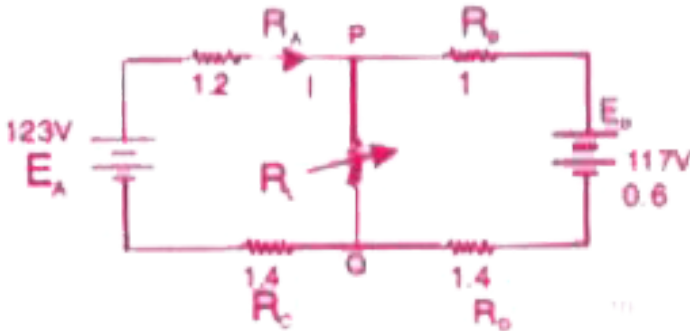
## 2. Passage :

A battery  $E_A$  of 123 volts emf internal resistance  $0.4\Omega$  and a battery  $E_B$  of 117 V emf and internal resistance  $0.6\Omega$  supplies a current to load resistance  $R_L$  through four wires of resistors  $R_A = 1.2\Omega$ ,  $R_B = 1\Omega$ ,  $R_C = 1.4\Omega$  and  $R_D = 1.4\Omega$  as shown in figure.



The value of load resistance for maximum load power is

A. 800 W

B. 1600 W

C. 2400 W

D. 3200 W


**Answer: C**



**Watch Video Solution**

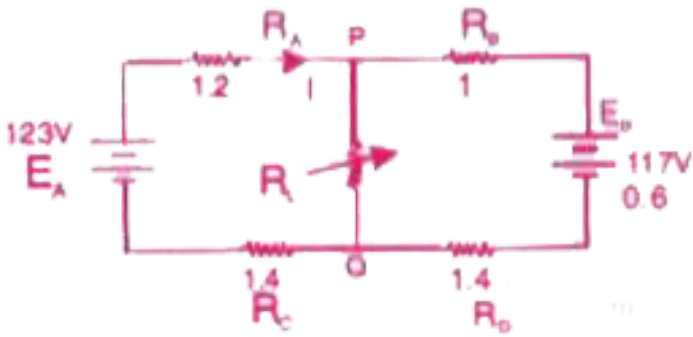**3. Passage :**

A battery  $E_A$  of 123 volts emf internal resistance  $0.4\Omega$  and a battery  $E_B$  of 117 V emf and internal resistance  $0.6\Omega$  supplies a current to load resistance  $R_L$  through four wires of resistors  $R_A = 1.2\Omega$ ,  $R_B = 1\Omega$ ,  $R_C = 1.4\Omega$  and  $R_D = 1.4\Omega$  as shown in figure.



The value of load resistance for maximum load power is


- A. 25 %
- B. 50 %
- C. 75 %
- D. 100 %

**Answer: B**

[Watch Video Solution](#)

**PRACTICE SHEET (EXERCISE - VII LEVEL-I (MAIN) (Straight Objective Type Questions))**

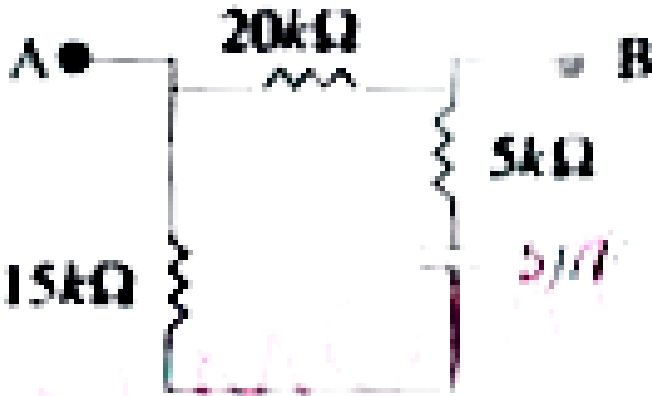1. The value of the resistance as measured across terminals A and B in fig would be at steady state



A.  $5k\Omega$

B.  $10k\Omega$

C.  $15k\Omega$

D.  $20k\Omega$

**Answer: D**



**Watch Video Solution**

2. How many time constants will elapse before the current in a charging RC circuit drops to half of its initial value? Answer the same question for a discharging RC circuit.

A. 1.9

B. 1.23

C. 0.69

D. 0.79

**Answer: D**



**Watch Video Solution**

3. How many time constants will elapse before the energy stored in the capacitor reaches half of its equilibrium value in a charging RC circuit ?

A. 1.23

B. 0.69

C. 2.46

D. 3.69

**Answer: A**



**Watch Video Solution**

4. how many time constants will elapse before the power delivered by the battery drops to half of its maximum value in an RC circuit ?

A. 1.23

B. 0.69

C. 2.46

D. 3.69


**Answer: B**





Watch Video Solution

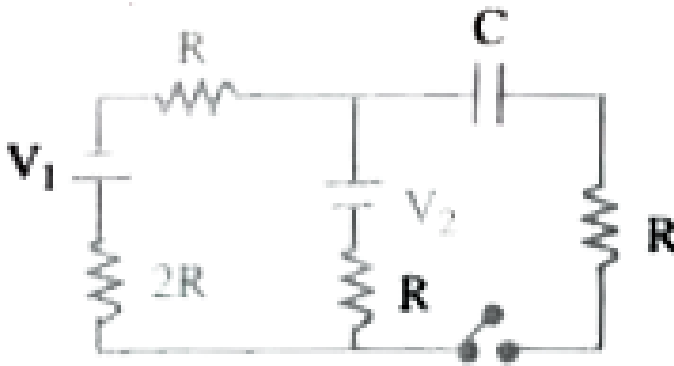5. In the transient circuit shown, the time constant of the circuit is :



- A.  $\frac{5}{3}RC$
- B.  $\frac{5}{2}RC$
- C.  $\frac{7}{4}RC$
- D.  $\frac{7}{3}RC$

**Answer: C**



**Watch Video Solution**

**PRACTICE SHEET (EXERCISE - VII LEVEL-II (ADVANCED)  
(Straight Objective Type Questions))**

1. An LR circuit with a battery connected at  $t = 0$ . Which of the following quantities will be zero just after the connection?

A.  $51\mu V / m$

B.  $17\mu V / m$

C.  $1.7 \times 10^4 V / m$

D.  $34\mu V / m$

Answer: C



Watch Video Solution

2. At the trophic level of consumers, the rate at which food energy is assimilated, is called ?

A.  $E^2 / 4R, 2CR \ln 2$

B.  $E^2 R, 2CR \ln 2$


C.  $\frac{E^2}{4R}, CR \ln 2$

D.  $\frac{E^2}{2R}, Cr \ln 2$

Answer: C

 Watch Video Solution

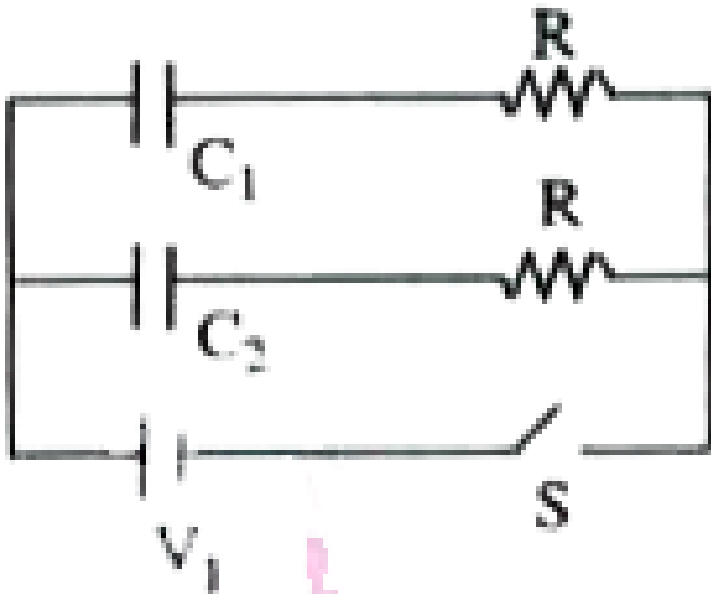3. In the circuit shown in figure  $C_1 = 2C_2$ , Switch S is closed at time  $t = 0$ , Let  $i_1$  and  $i_2$  be the currents flowing through  $C_1$  and  $C_2$  at any time  $t$ , then the ratio  $i_1/i_2$



A. is constant

B. increases with increase in time  $t$

C. decreases with increase in time  $t$

D. first increases then decreases


**Answer: B**



**Watch Video Solution**

4. In the circuit shown, when the key  $k$  is pressed at time  $t = 0$ , which of the following statements about

current  $I$  in the resistor AB is true

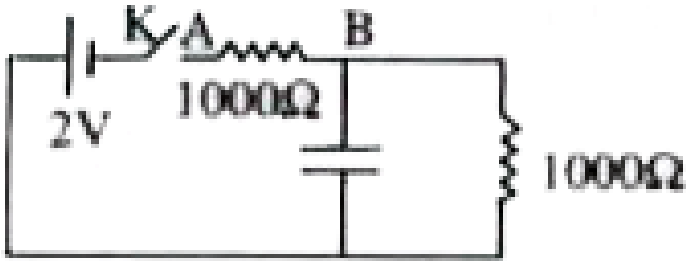

- A.  $I = 2\text{mA}$  at all  $t$
- B.  $I$  oscillates between  $1\text{mA}$  and  $2\text{mA}$
- C.  $I = 1\text{mA}$  at all  $t$
- D. At  $t = 0$ ,  $I = 2\text{mA}$  and with time it goes to  $1\text{mA}$

**Answer: D**




**Watch Video Solution**

# PRACTICE SHEET (EXERCISE - VII LEVEL-II (ADVANCED))

(More than One correct answer Type Questions))

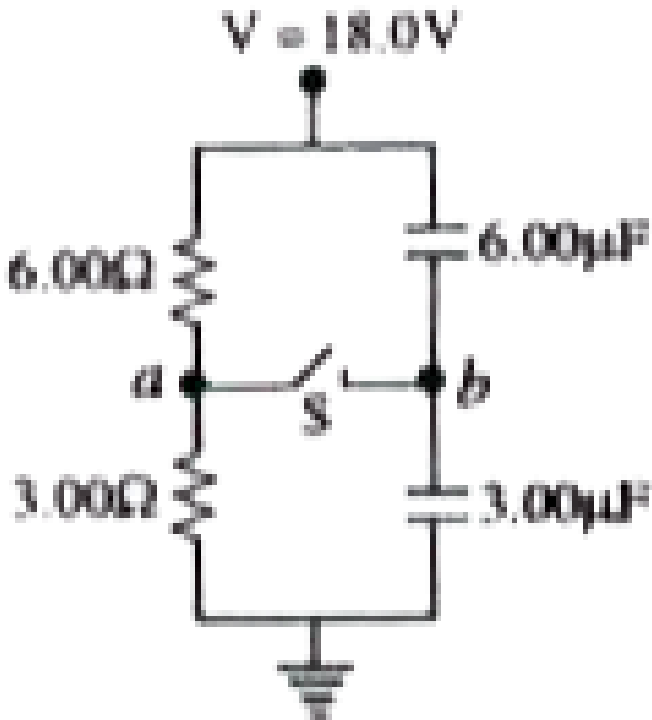1. Study the following circuit diagram and mark the correct options.



- A. The potential of point a with respect to point b in figure when switch S is open is  $-6V$ .
- B. The points a and b are at the same potential, when S is opened.
- C. The charge flown through the switch S when it is closed is  $54\mu C$ .
- D. The final potential of b with respect to ground when switch S is closed is  $8V$ .


**Answer: A::C**



**Watch Video Solution**



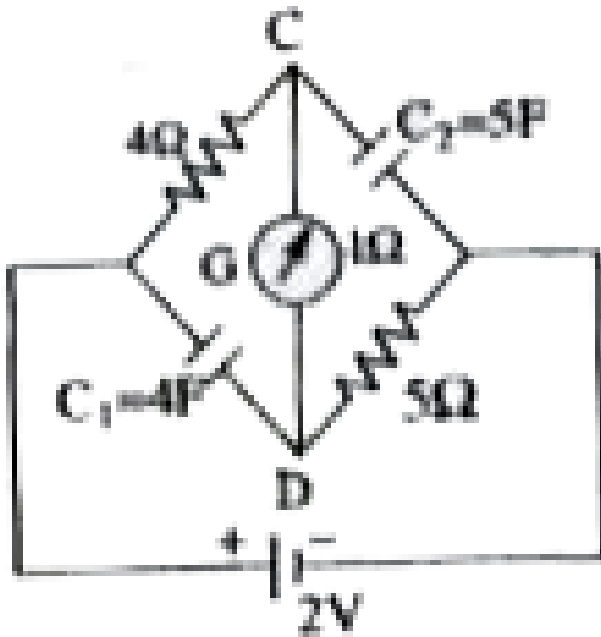2. In the circuit shown in Fig., the cell is ideal with e.m.f = 2V. The resistance of the coil of the galvanometer G is  $1\Omega$ . Then



- A. initially no current flows in G
- B. in steady state 0.2 A current flows in G
- C. potential difference across  $C_1$  is 1V

D. potential difference across  $C_2$  is 1.2 V


**Answer: B::C::D**



**Watch Video Solution**

**PRACTICE SHEET (EXERCISE - VII LEVEL-II (ADVANCED))  
(Integer Type Questions))**

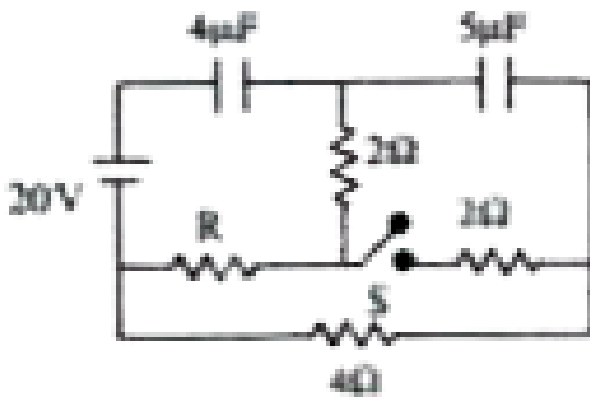1. Find heat produced in the capacitors on closing the switch S after long time (in joules).



[Watch Video Solution](#)

## ADDITIONAL PRACTICE EXERCISE (LEVEL -I(MAIN) (Straight Objective Type Questions))

1. The current through a wire depends on time as

$$I = i_0 + \alpha t,$$

where  $i_0 = 10A$  and  $\alpha = 4As^{-1}$ . Find the charge crossed through a section of the wire in 10 second

A. 100 C

B. 200 C

C. 300 C

D. 400 C

**Answer: C**



**Watch Video Solution**

2. The space between the plates of a parallel plate capacitor is completely filled with a material of resistivity  $2 \times 10^{11} \Omega m$  and dielectric constant 6. Capacity of the capacitor with the given dielectric medium between the plates is  $20 \mu F$ . Find the leakage

current if a potential difference  $2500V$  is applied across the capacitor.

A.  $4.7\mu A$

B.  $1.2\mu A$

C.  $8.3\mu A$

D.  $10.5\mu A$

**Answer: A**



**Watch Video Solution**

3. A cylindrical tube of length  $L$  has inner radius  $a$  and outer radius  $b$ . What is the resistance of the tube

between its inner and outer surface ? Given that the resistivity of its material is  $\rho$ .

A.  $\rho(2\pi L)\ln\left(\frac{b}{a}\right)$

B.  $\frac{\rho}{4\pi L}\ln\left(\frac{b}{a}\right)$

C.  $\frac{\rho}{2\pi L}\ln\left(\frac{2b}{a}\right)$

D.  $\frac{\rho}{\pi L}\ln\left(\frac{b}{a}\right)$

**Answer: B**



**Watch Video Solution**

4. The conductance of a solution of an electrolyte is equal to that of its specific conductance The cell

constant of the conductivity cell is equal to

A.  $\frac{\rho_0 l}{A} \left[ 1 + \frac{\alpha l}{2} \right]$

B.  $\frac{\rho_0 l}{A} [1 + \alpha l]$


C.  $\frac{\rho_0 l}{A} \left[ 1 + \frac{\alpha l^2}{2} \right]$

D.  $\frac{\rho_0 l}{A} [1 + 2\alpha l]$

**Answer: A**



**Watch Video Solution**

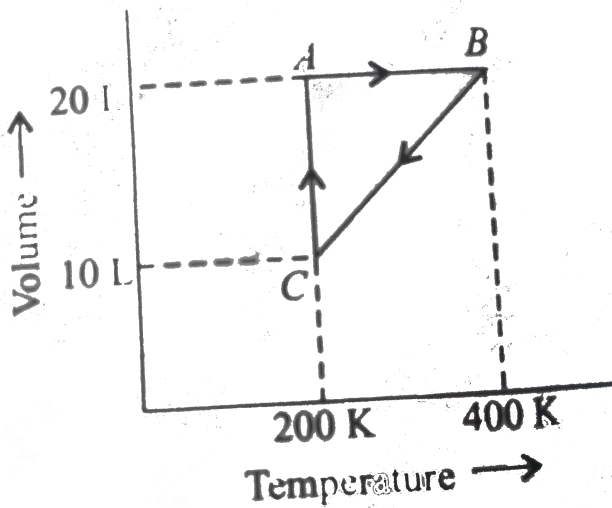

5.

The pressures at  $A$  and  $B$  in the atmosphere are, respectively,

A. 
$$\frac{\sigma_1 V_1 + \sigma_2 V_2}{(\sigma_1 / L_1) + (\sigma_1 / L_2)}$$

B. 
$$\frac{\frac{\sigma_1 V_1}{L_1} + \frac{\sigma_2 V_2}{L_2}}{(\sigma_1 / L_1) + (\sigma_1 / L_2)}$$

C. 
$$\frac{(\sigma_1 / V_1) + (\sigma_2 / V_2)}{\sigma_1 V_1 + \sigma_2 V_2}$$


D. 
$$\frac{\sigma_1 V_1 - \sigma_2 V_2}{(\sigma_1 / L_1) - (\sigma_1 / L_2)}$$



Answer: B

 Watch Video Solution

6. The resistance between OA is given by

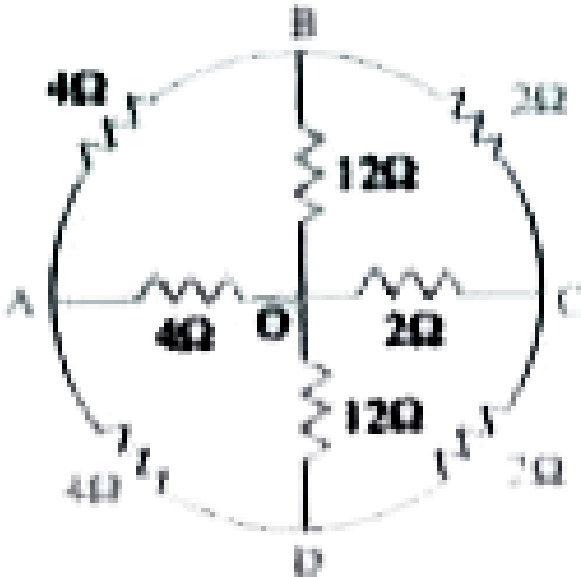

A.  $1\Omega$

B.  $2\Omega$

C.  $3\Omega$


D.  $4\Omega$

**Answer: B**



**Watch Video Solution**

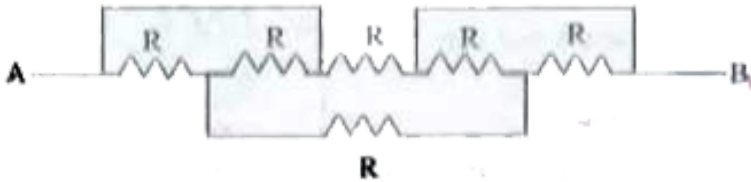7. Find the equivalent resistance between A and B in the following circuit.



A.  $\frac{5R}{3}$

B.  $\frac{5R}{2}$

C.  $\frac{2R}{3}$

D.  $\frac{5R}{6}$


**Answer: C**



**Watch Video Solution**

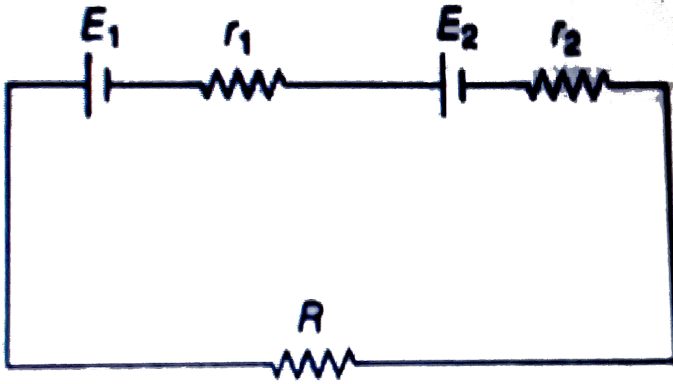**8.** Under what conditions current passing through the resistance  $R$  can be increased by short circuiting the battery of emf  $E_2$ . The internal resistances of the two

batteries are  $r_1$  and  $r_2$  respectively



A.  $E_2 r_1 > E_1 (R + r_2)$

B.  $E_1 r_2 > E_2 (R + r_1)$


C.  $E_2 r_2 > E_1 (R + r_2)$

D.  $E_1 r_1 > E_2 (R + r_1)$

**Answer: B**



**Watch Video Solution**

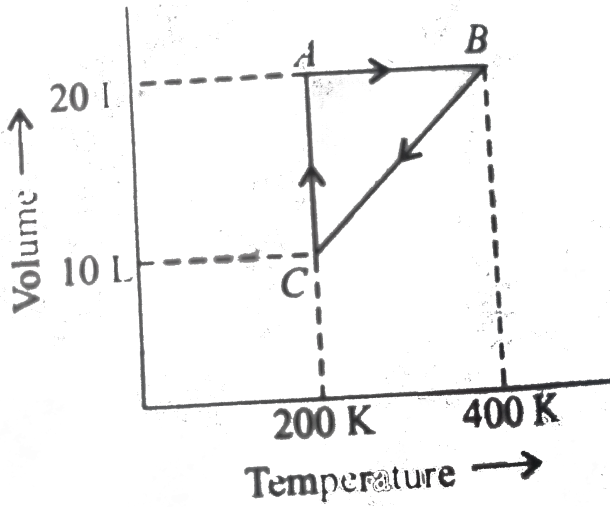

9.


The pressures at  $A$  and  $B$  in the atmosphere are, respectively,

- A. 1
- B. 6
- C. 4
- D. 8

Answer: A

 Watch Video Solution

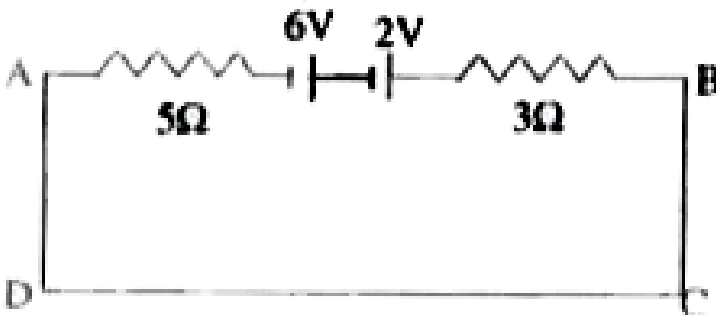10. The internal resistances of cells in the circuit shown in the figure are negligible. The current in the circuit is




- A.  $0.5A$  flowing from A to D
- B.  $0.5A$  flowing from B to C
- C.  $1.0A$  flowing from A to B

D. 1.0A flowing from B to A

Answer: B

 Watch Video Solution

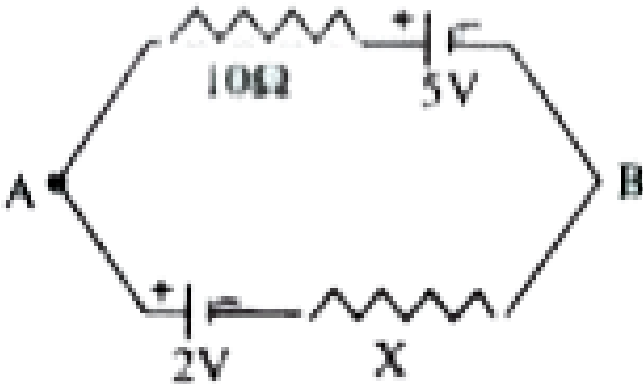11. In the given circuit, if potential difference between points A and B is 4V. Then, resistance X is



A.  $5\Omega$

B.  $10\Omega$

C.  $15\Omega$

D.  $20\Omega$


**Answer: D**



**Watch Video Solution**

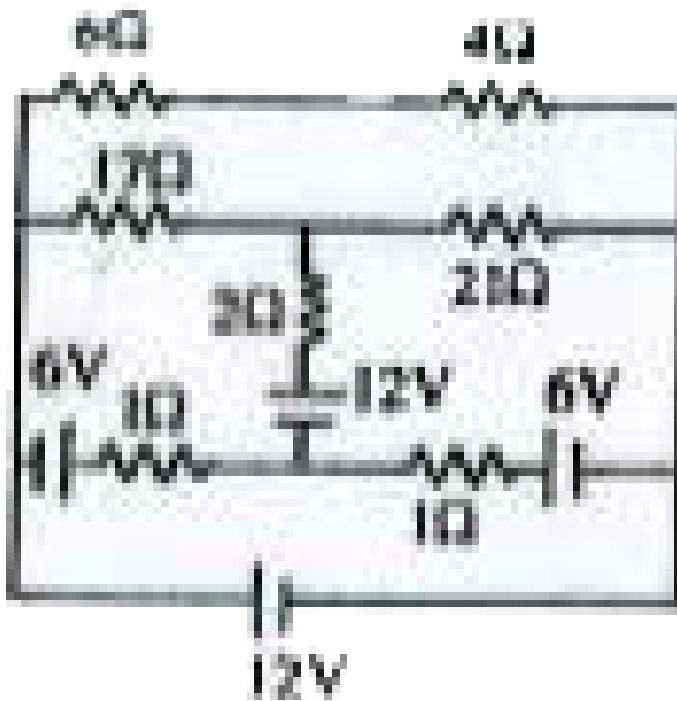**12.** Choose the correct statement(s) from the following option for given diagram






- A. potential drop across  $6\Omega$  is  $3.2\text{ V}$
- B. potential drop across  $4\Omega$  is  $4.8\text{ V}$
- C. potential drop across  $6\Omega$  is  $4.8\text{ V}$
- D. potential drop across  $4\Omega$  is zero

**Answer: B**

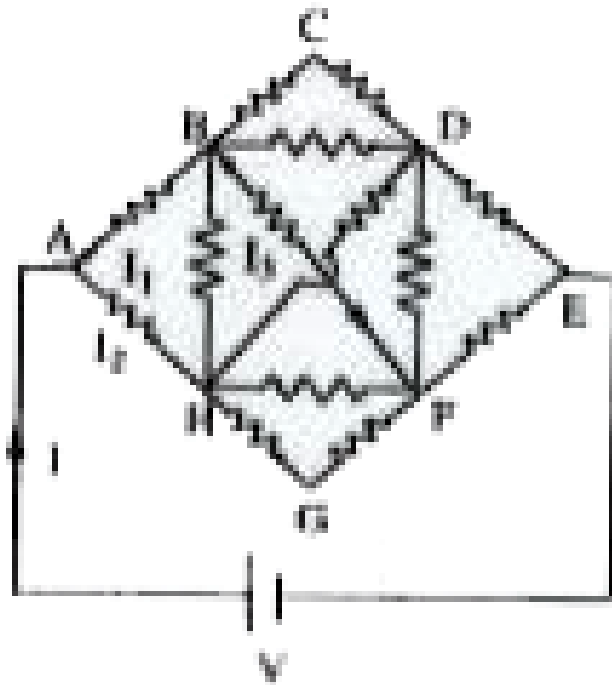13. Fourteen identical resistors, each of resistance  $r$  each connected as shown in figure. Pick the incorrect alternative(s)



A. Relation between  $I$  and  $I_3$  is  $I = 5I_3$

B. Effective resistance between A and E is  $1.6r$

C. The value of  $I_3$  in terms of  $I_1$  is  $\frac{2I_1}{5}$


D. Effective resistance between A and E is  $1.2r$

**Answer: B**



[Watch Video Solution](#)

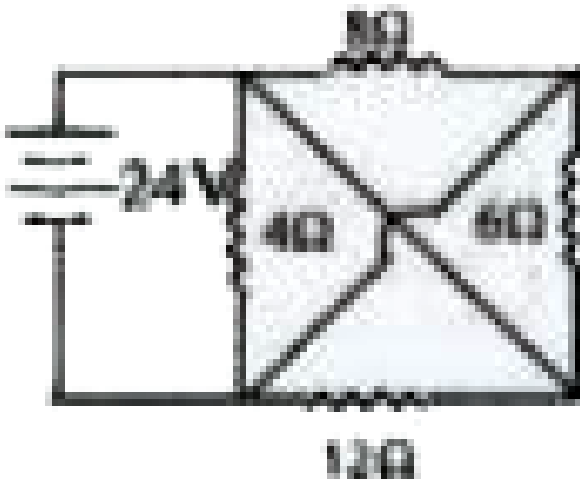**14.** Calculate battery current and equivalent resistance of the network shown in figure.



A.  $20V, 5\Omega$

B.  $5A, \frac{8}{5}\Omega$


C.  $15A, \frac{8}{5}\Omega$

D.  $9A, \frac{8}{3}\Omega$

**Answer: C**

 **Watch Video Solution**

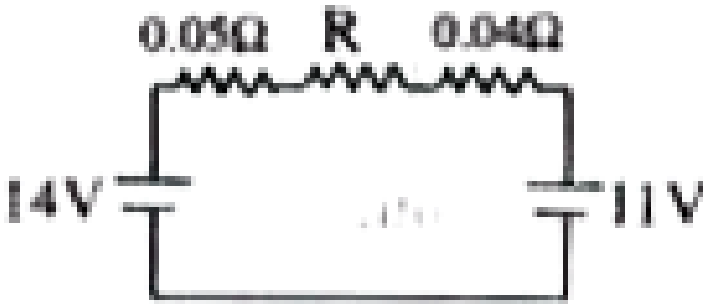15. For the circuit shown in figure the value of  $R$  so that  $25\text{W}$  of electrical energy is delivered to a combination of  $11\text{V}$  battery and  $0.04\Omega$  resistor is




- A.  $1.11\Omega$
- B.  $1.24\Omega$
- C.  $1.18\Omega$
- D. None of these

**Answer: B**



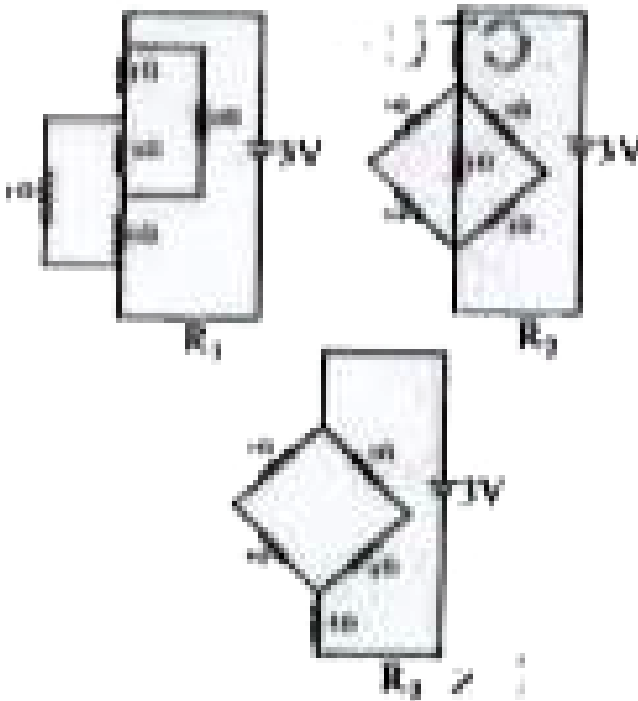16. Fig shows three resistor configuration  $R_1$ ,  $R_2$  and  $R_3$  connected to 3V battery. If the power dissipated by the configuration  $R_1$ ,  $R_2$  and  $R_3$  is  $P_1$ ,  $P_2$  and  $P_3$  respectively, then



A.  $P_1 > P_2 > P_3$

B.  $P_1 > P_3 > P_2$


C.  $P_2 > P_1 > P_3$

D.  $P_3 > P_2 > P_1$

**Answer: C**



**Watch Video Solution**

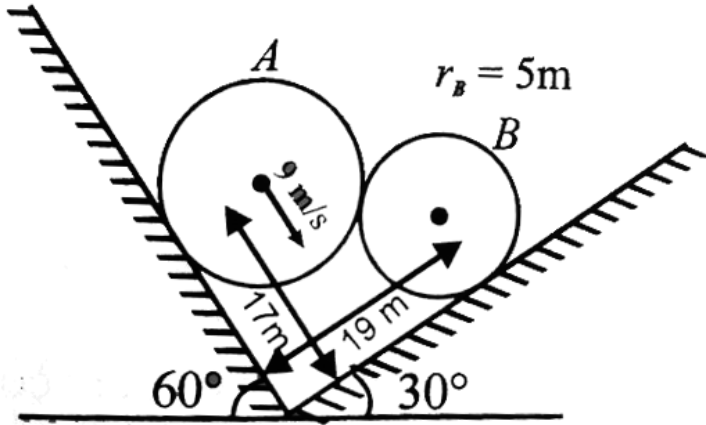

17.

System is shown in the figure. Velocity of sphere A is  $9 \frac{m}{s}$ . Find the speed of sphere B.

- A. 7 mA
- B. 8 mA
- C. 10 mA
- D. 11 mA

**Answer: D**



**18.** Two motor boats A and B move from same point along a circle of radius 10 m in still water. The boats are so designed that they can move only with constant speeds. The boats A and B take 16 and 8 sec respectively to complete one circle in stationary water. Now water starts flowing at  $t = 0$  with a speed  $4\frac{m}{s}$  in a fixed direction. Find the distance between the boats after  $t = 8$  sec.

A.  $\frac{1}{6}m$

B.  $\frac{1}{3}m$

C. 25 cm

D. 50 cm


**Answer: C**



**Watch Video Solution**

**19.** A potential difference of 220 V is maintained across a 12000 ohm rheostat AB. The voltmeter V has a resistance of 6000 ohm and point C is at one fourth of the distance from A to B. What is the reading in the

voltmeter ?

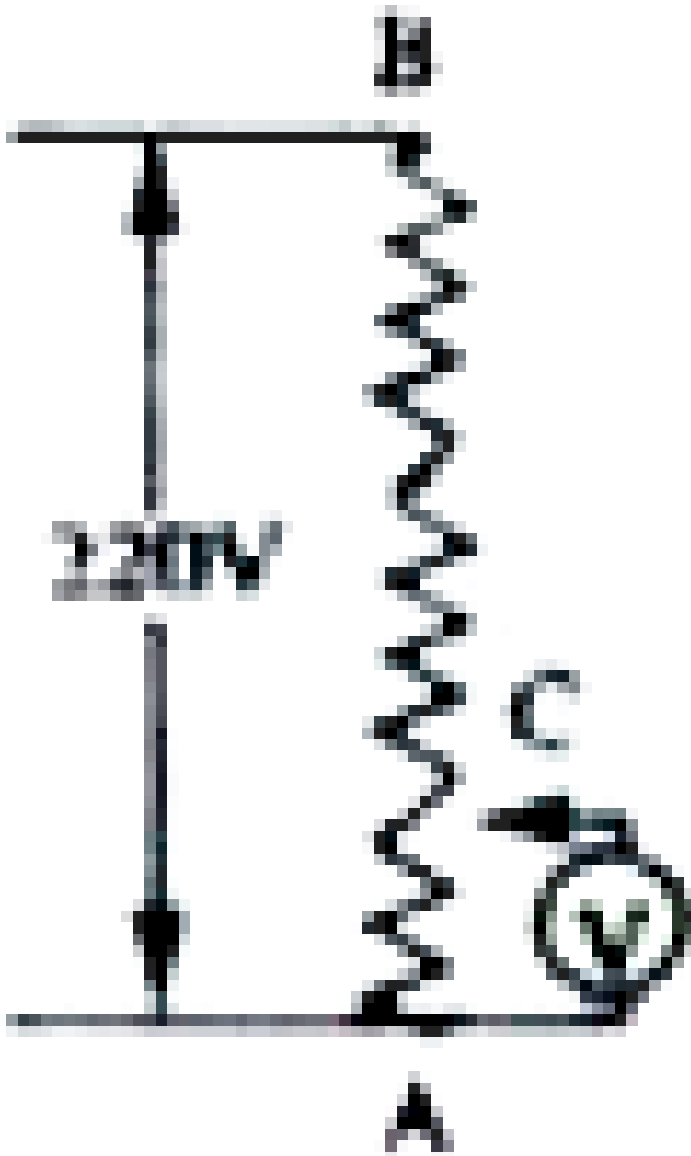

A. 40 V

B. 80 V

C. 20 V

D. 100 V


**Answer: A**



**Watch Video Solution**

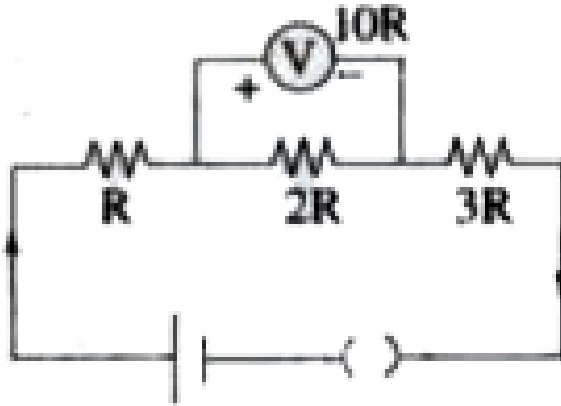**20.** A battery of emf  $E$  is connected in series with three resistances  $R$ ,  $2R$  and  $3R$ . The voltage across  $2R$  is measured with a voltmeter whose resistance is  $10 R$ .

What is the percentage error in the reading?



- A. 11.76 % more than the true value
- B. 6.3 % more than the true value
- C. 11.76 % less than the true value
- D. 6.3 % less than the true value

**Answer: C**



**Watch Video Solution**

**ADDITIONAL PRACTICE EXERCISE (LEVEL -II LECTURE SHEET  
(ADVANCED) (Straight Objective Type Questions))**

1. A n-type silicon sample of width  $4 \times 10^{-3}m$ , thickness  $25 \times 10^{-5}m$  and length  $6 \times 10^{-2}m$  carries a current of 4.8 mA when the voltage is applied across the length of the sample. If the free electron density is  $10^{22}m^{-3}$ , then find how much time does it take for the electrons to travel the full length of the sample? Given that charge on an electron  $e = 1.6 \times 10^{-19}C$

A. 0.02 s

B. 0.01 s

C. 0.04 s

D. 0.06 s

**Answer: A**



**Watch Video Solution**

2. A potential difference of 30V is applied between the ends of a conductor of length 100 m and resistance  $0.5\Omega$  . The conductor has a uniform cross-section. Find the total linear momentum of free electrons.

A.  $10^{-9} \text{ kg. m / s}$

B.  $6.8 \times 10^{-8} \text{ kg. m / s}$

C.  $3.4 \times 10^{-9} \text{ kg. m / s}$

$$D. 3.4 \times 10^{-8} \text{ kg. m / s}$$

**Answer: D**



**Watch Video Solution**

3. A long round conductor of cross-sectional area  $S$  is made of material whose resistivity depends only on a distance  $r$  from the axis of the conductor as  $\rho = \alpha / r^2$ , where  $\alpha$  is a constant. Find the total resistance per unit length of the rod when potential difference is applied across its length.

A.  $\frac{\pi\alpha}{S^2}$

B.  $\frac{2\pi\alpha}{S^2}$



C.  $\frac{\pi\alpha}{2S^2}$


D.  $\frac{\alpha}{S^2}$

**Answer: B**



**Watch Video Solution**

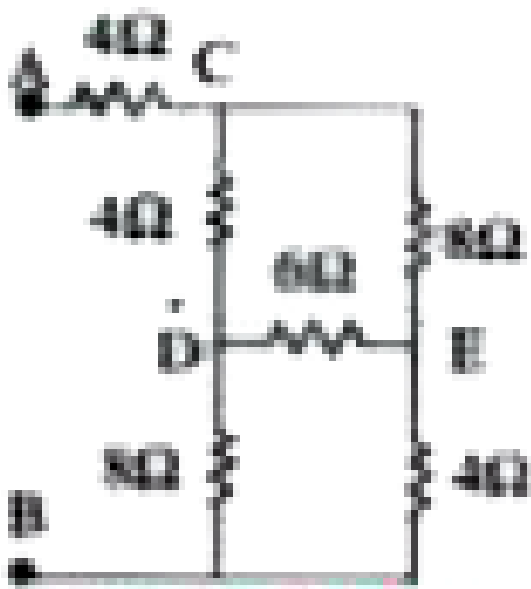4. Find the input resistance of the circuit between the points A and B of fig. shown



A.  $\frac{87}{9} \Omega$

B.  $\frac{87}{3} \Omega$

C.  $\frac{24}{9} \Omega$


D.  $\frac{12}{9} \Omega$

Answer: A



Watch Video Solution

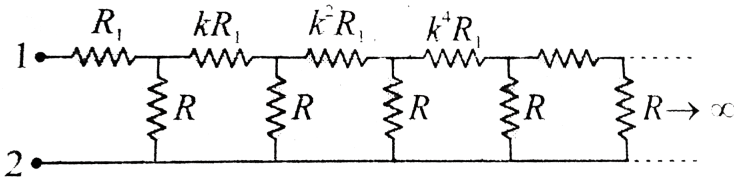5. The circuit diagram shown in the figure consists of a large number of elements (each element has two resistors  $R_1$  and  $R_2$ ). The resistance of the resistors in each subsequent element differs by a factor of  $k = \frac{1}{2}$  from the resistance of the resistors in previous elements. Find the equivalent resistance between A and B shown in



A.  $\frac{R_1 - R_2}{2}$

B.  $\frac{(R_1 - R_2) + \sqrt{6R_1R_2}}{2}$

C.  $\frac{(R_1 - R_2) + \sqrt{R_1^2 + R_2^2 + 6R_1R_2}}{2}$

D. None of these

**Answer: A**




**Watch Video Solution**

6. Find the equivalent resistance of the triangular bipyramid between the points

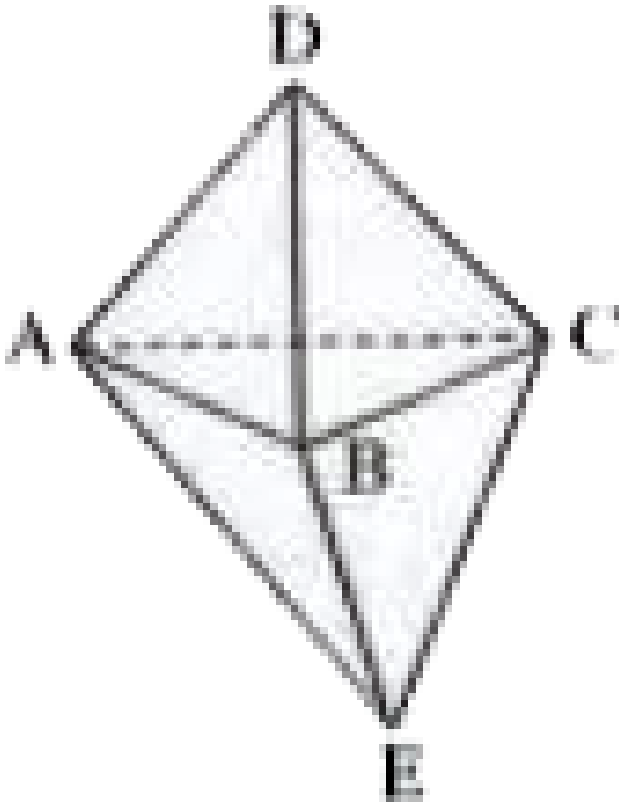A) A and C B) D and E

Assume the resistance of each brach to be  $R$ .



A.  $\frac{4R}{5}, \frac{2R}{3}$

B.  $\frac{2R}{5}, \frac{4R}{3}$


C.  $\frac{4R}{5}, \frac{4R}{3}$

D.  $\frac{2R}{5}, \frac{2R}{3}$

Answer: D

 Watch Video Solution

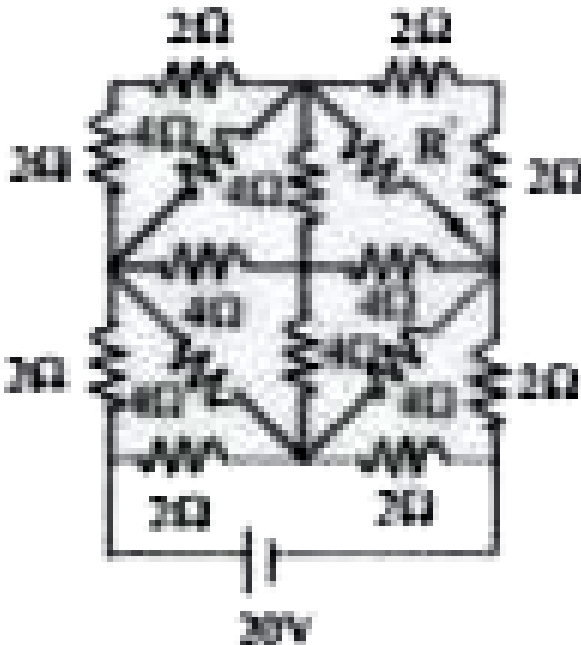7. In the circuit shown, all the side resistances are of value  $2\Omega$  and all inner resistances are of value  $4\Omega$ . Find the current via branch  $R$ .  $R = 4\Omega$ .



A. 5.2A

B. 6.7A

C. 0.833A

D. 10.5A



**Answer: C**



**Watch Video Solution**

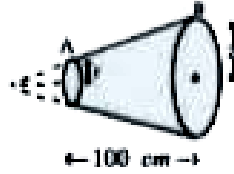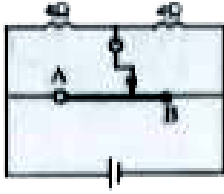**8.** The wire AB of a meter bridge changes linearly from radius  $r$  to  $2r$  from left end to right end. Where should the free end of the galvanometer be connected on AB

so that the deflection in the galvanometer is zero?



- A. 33.33 cm from A
- B. 66.66 cm from A
- C. 50 cm from A
- D. 20 cm from B


**Answer: A**



**Watch Video Solution**



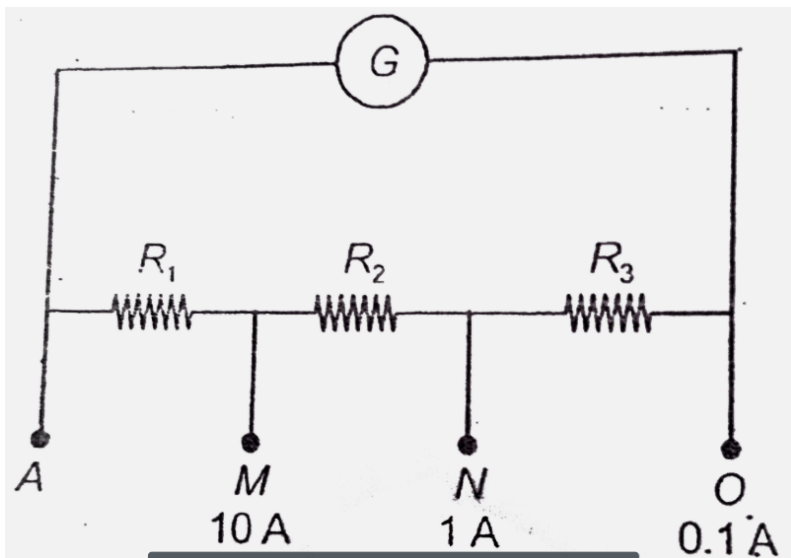9. The galvanometer shown in figure has resistance  $50\ \Omega$  and current required for full scale deflection is  $1\text{mA}$ . Find the resistance  $R_1$ ,  $R_2$  and required to convert to convert it into ammeter having ranges as indicated.



A.  $\frac{1}{22}\ \Omega$ ,  $\frac{15}{33}\ \Omega$ ,  $\frac{1}{100}\ \Omega$

B.  $\frac{1}{22}\ \Omega$ ,  $\frac{1}{33}\ \Omega$ ,  $\frac{1}{44}\ \Omega$

C.  $\frac{1}{22}\ \Omega$ ,  $\frac{1}{33}\ \Omega$ ,  $\frac{1}{44}\ \Omega$

D.  $\frac{1}{198}\Omega, \frac{1}{22}\Omega, \frac{15}{33}\Omega$

**Answer: D**







**Watch Video Solution**

**ADDITIONAL PRACTICE EXERCISE (LEVEL -II LECTURE SHEET  
(ADVANCED) (Matrix Matching Type Questions))**

1. Three bulbs A, B and C having rated power  $P_A, P_B$  and  $P_C$ , respectively. Each bulb is designed to operate at rated voltage of V volts. It is given that  $P_A > P_B > P_C$ . In column I, different configurations of bulbs are given while in Column II, intensities are mentioned. Match entries of Column I with entries of

Column II, neglecting the change of resistances of bulbs due to temperature change.

**COLUMN - I**

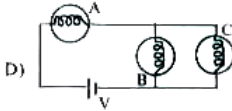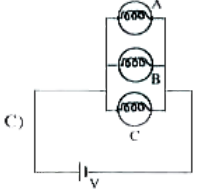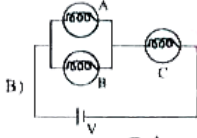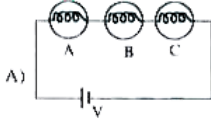

**COLUMN - II**

p) A glows with minimum intensity

q) C is glowing with maximum intensity


r) B is glowing with minimum intensity

s) A is glowing with maximum intensity

**Watch Video Solution**

2. Six batteries of increasing emf and increasing internal resistance are as shown in figure. Match the

following:

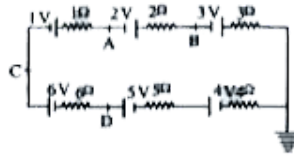

**COLUMN - I**

- A) Potential of point A
- B) Potential of point B
- C) Potential of point C
- D) Potential of point D

**COLUMN - II**

- p) Zero
- q) 2V
- r) 6 V
- s) 6V
- t) None



**Watch Video Solution**

**ADDITIONAL PRACTICE EXERCISE (LEVEL -II LECTURE SHEET  
(ADVANCED) (Integer Type Questions))**

1. Current density in a cylindrical wire of radius  $R$  is

$$\text{given as } J = \begin{cases} J_0 \left( \frac{x}{R} - 1 \right) & \text{for } 0 \leq x < \frac{R}{2} \\ J_0 \frac{x}{R} & \text{for } \frac{R}{2} \leq x \leq R \end{cases} .$$

If the current flowing in the wire is  $\frac{k}{12}\pi J_0 R^2$ , find the value of k.



[Watch Video Solution](#)

2. A copper rod (resistivity  $2.2 \times 10^{-8} \Omega - m$ ) and an iron (resistivity  $1.1 \times 10^{-8} \Omega - m$ ) rod of same length 70 cm each and same diameter 1.4 mm each are joined in series, then the combined resistance is



[Watch Video Solution](#)

3. Consider a copper cylinder of volume  $x$ , resistivity  $f$ , resistance across its length is  $r$ . If diameter of

cylindrical conductor is  $\left(\frac{16fx}{\pi^2 r}\right)^{1/k}$ , then find the value of k.


 [Watch Video Solution](#)

4. One kilowatt electric heater is to be used with 220V DC supply. It converts  $\frac{N \times 10}{3}$  g of water at  $100^{\circ}C$  into steam at  $100^{\circ}C$  in one minute. find the value N.

 [Watch Video Solution](#)

5. In the circuit shown in figure  $R_1 = R_2 = 10\Omega$ ,  $E_1 = 20V$ ,  $E_2 = 40V$ . For what value of R, the thermal power developed in it will be

maximum (in  $\Omega$ )?

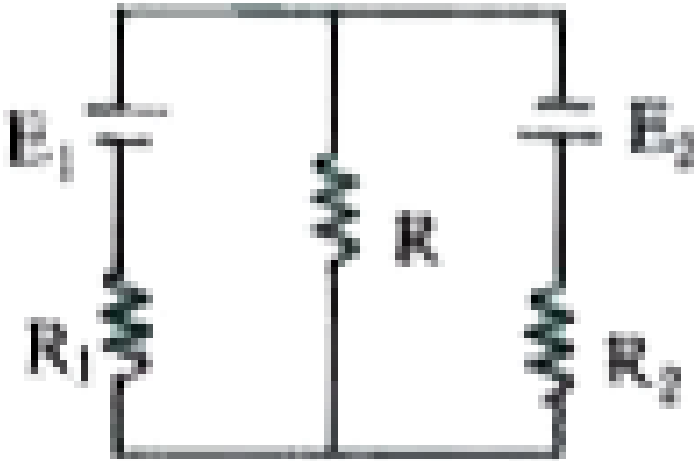

Watch Video Solution

6. A capacitor  $C = 100\mu F$  is connected to three resistance each of resistance  $1k\Omega$  and a battery of emf  $9V$  switch  $S$  has been closed for long time so as to the capacitor. When switch  $S$  is opened capacitor

discharges with time constant




 [Watch Video Solution](#)

7. A galvanometer having a resistance of  $50\Omega$ , gives a full scale deflection for a current of  $0.05\text{A}$ . The length in metre of a resistance wire of area of cross - section  $2.97 \times 10^{-2}\text{cm}^2$  that can be used to convert the galvanometer into an ammeter which can read a maximum of  $5\text{A}$  current is (Specific resistance wire  $= 5 \times 10^{-7}\Omega - m$ )

 [Watch Video Solution](#)



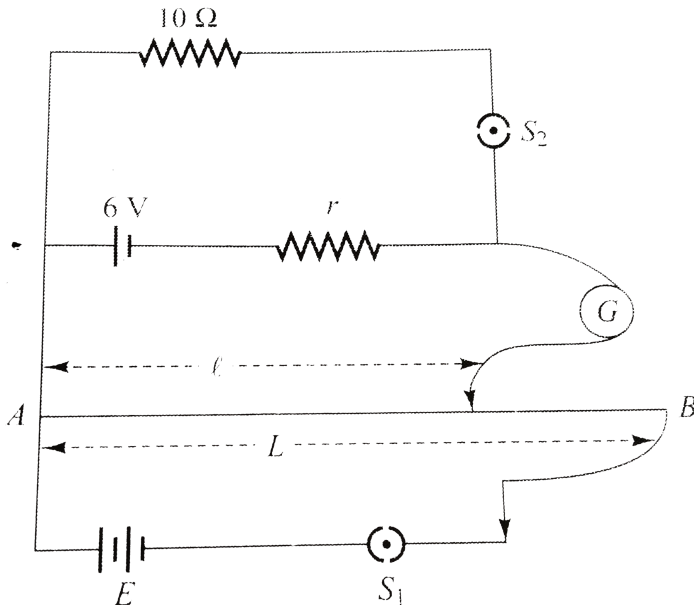8. In the arrangement shows in fig. , when the switch  $S_2$  is open, the galvanometer shows no deflection for  $l = L/2$ . When the switch  $S_2$  is closed, the galvanometer shows no deflection for  $l = 5/12L$ . The internal resistance ( $r$ ) of 6 V cell and the emf  $E$  of the other battery are, respectively




[Watch Video Solution](#)

**ADDITIONAL PRACTICE EXERCISE (LEVEL -II PRACTICE SHEET  
(ADVANCED) (Straight Objective Type Questions))**

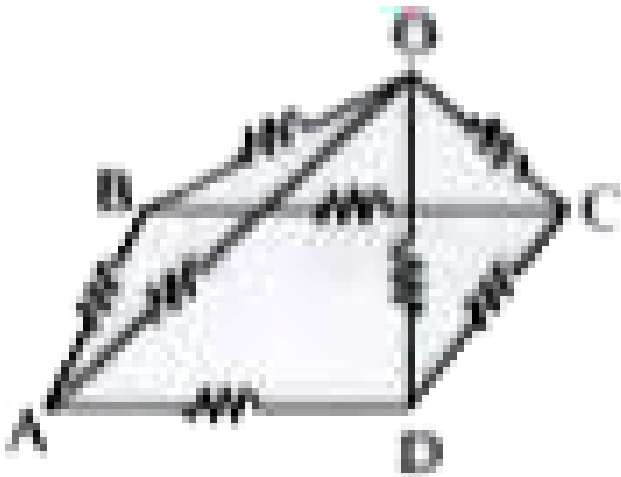1. Eight identical resistances  $r$  are connected along edges of a pyramid having square base ABCD as shown.

Calculate equivalent resistance between A and D.



A.  $\frac{5r}{6}$

B.  $\frac{7r}{12}$

C.  $\frac{4r}{3}$

D.  $\frac{8r}{15}$


**Answer: D**



**Watch Video Solution**

2. The circuit in figure is made of a homogeneous wire of uniform cross-section. 1234 is a square. Find the ratio  $Q_{12}/Q_{34}$  of the amounts of heat liberated per

unit time in conductor 1-2 and 3-4

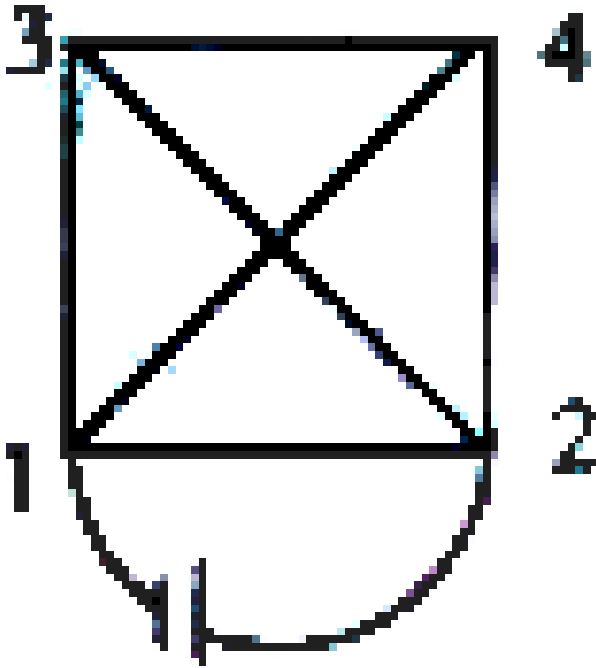

A.  $3 - \sqrt{2}$

B.  $2 + \sqrt{2}$

C.  $11 + 6\sqrt{2}$

D.  $\sqrt{2} + 3$

**Answer: C**



Watch Video Solution

3. A block of metal is heated directly by dissipating power in the internal resistance of block. Because of temperature rise, the resistance increases exponentially with time and is given by  $R(t) = 0.5e^{2t}$ , where  $t$  is in seconds. The block is connected across a 110 V source and dissipates 7644 J heat over a certain period of time. Calculate this period of time.

A. 0.5 s

B. 1s

C. 1.5 s

D. 2s

**Answer: A**



**Watch Video Solution**

4. A conductor has a temperature independent resistance  $R$  and a total heat capacity  $C$ . At the moment  $t = 0$  it is connected to a  $DC$  voltage  $V$ . Find the times dependence of the conductors temperature  $t$  assuming the thermal power dissipated into surrounding space to vary as  $q = k(T - T_0)$  where  $k$  is a constant  $T_0$  is the surrounding temperature (equal to conductor's temperature at the initial moment).

$$\text{A. } T = \frac{V^2}{kR} e^{-\frac{kt}{C}}$$

$$\text{B. } T = T_0 + \frac{V^2}{KR} \left[ 1 - e^{-\frac{Kt}{C}} \right]$$

$$\text{C. } T = T_0 + \frac{V^2}{kR} e^{-\frac{kt}{C}}$$

$$\text{D. } T = \left( T_0 + \frac{V^2}{kR} \right) e^{-\frac{kt}{C}}$$


**Answer: B**



**Watch Video Solution**

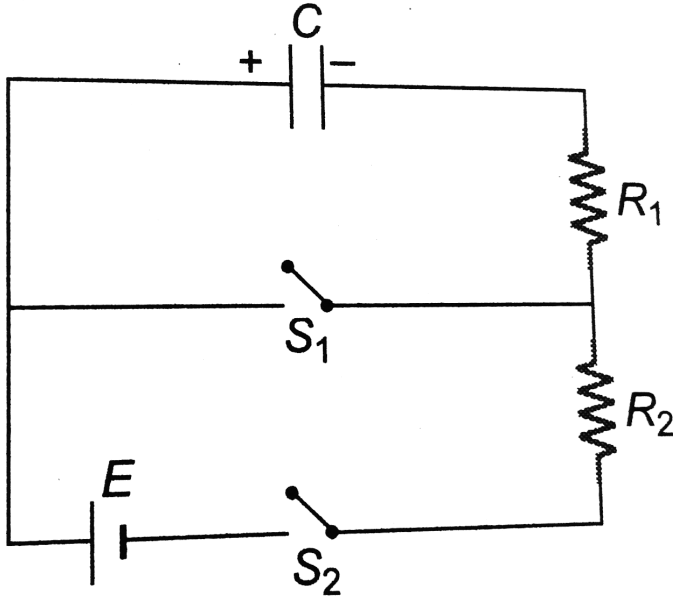5. The capacitor shown in figure has been charged to a potential difference of  $V$  volt, so that it carries a charge  $CV$  with both the switches  $S_1$  and  $S_2$  remaining open. Switch  $S_1$  is closed at  $t = 0$ . At  $t = R_1C$  switch  $S_1$  is opened and  $S_2$  is closed. Find the

charge on the capacitor at  $t = 2R - 1C + R_2C$ .



- A.  $CD(e - 1) + \frac{CV}{e}$
- B.  $CE(1 - e^2) + \frac{CV}{e}$
- C.  $CE\left(1 - \frac{1}{e}\right) + \frac{CV}{e^2}$
- D.  $CE\left(1 - \frac{1}{e}\right) - \frac{CV}{e^2}$

**Answer: C**



**ADDITIONAL PRACTICE EXERCISE (LEVEL -II PRACTICE SHEET  
(ADVANCED) (More than One correct answer Type  
Questions))**

1. A metallic conductor of irregular cross-section is as shown in the figure. A constant potential difference is applied across the ends (1) and (2). Then :



A. the current at the cross-section P equals the current at the cross-section Q

- B. the electric field intensity at P is less than that at Q.
- C. the rate of heat generated per unit time per unit length at Q is greater than that at P
- D. the number of electrons crossing per unit area of cross-section at P is less than that at Q.

**Answer: A::B::C::D**



**Watch Video Solution**

2. The resistivity of cylindrical conductor carrying steady current along its length varies linearly with the

distance from the current carrying end as given by

$$\rho = \rho_0 \left( 1 + \frac{x}{l} \right)$$

where  $l$  is the length of the conductor and  $x$  is the distance from the current entry and  $\rho_0$  is a positive constant.

A. Electric field varies linearly with  $x$

B. Electric potential difference across the length varies linearly with  $x$

C. Volume charge density in the conductor is zero

D. volume charge density in the conductor is non zero.

**Answer: A::B**



**Watch Video Solution**

3. A wire of 5.8 m long, 2 mm diameter carries 750 mA current when 22 mV potential difference is applied at its ends. If drift speed of electrons is found  $1.7 \times 10^{-5}$  m/s then

A. currenty density is  $2.4 \times 10^{+5} A / m^2$

B. current density is  $1.6 \times 10^{+4} A / m^2$

C. number of free electrons per unit volume is

$$2.7 \times 10^{16} m^{-3}$$


D. number of free electrons per unit volume is

$$8.8 \times 10^{28} m^{-3}$$

Answer: A::D

 Watch Video Solution

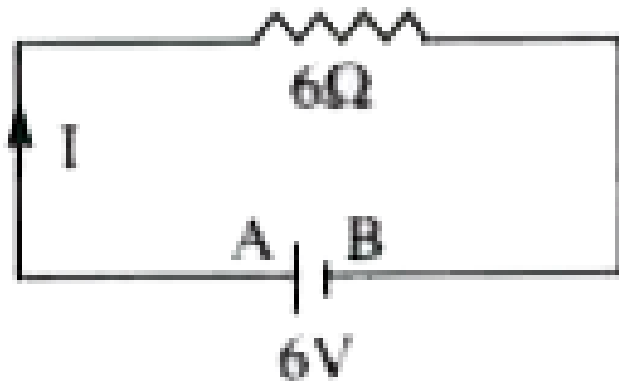4. In the given circuit, AB is a wire of resistance  $6\Omega$ , length 10 cm, number of electrons per unit volume in material of wire is  $10^{29}m^{-3}$ . If cross-sectional area of wire is  $1mm^2$ , then which of the following options are correct?



A. Energy absorbed by electrons is  $2 \times 10^{-17} J$

B. Ohmic loss in wire is  $16J/s$

C. Ohmic loss in wire is  $6J/s$

D. Energy absorbed by electrons is  $2 \times 10^{-16} J$


**Answer: A::C**



**Watch Video Solution**

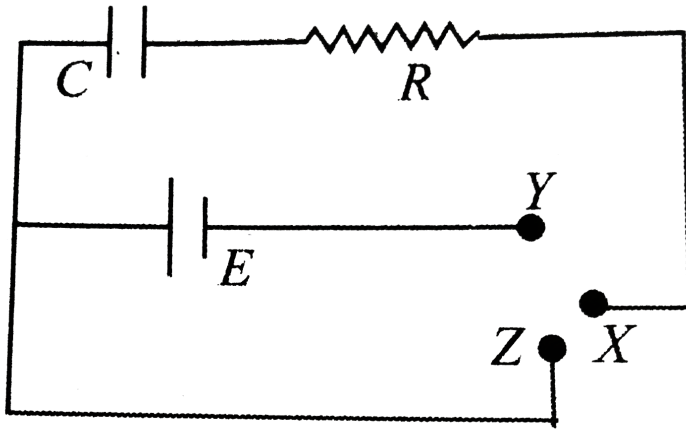5. The capacitor C is initially without charge. X is now joined to Y for a long time, during which  $H_1$  heat is produced in the resistance R. X is now joined to Z for a

long time, during which  $H_2$  heat is produced in R



A.  $H_1 = H_2$

B.  $H_1 = \frac{1}{2}H_2$

C.  $H_1 = 2H_2$

D. The maximum energy stored in C at any time is

$H_1$ .

Answer: A::D




**ADDITIONAL PRACTICE EXERCISE (LEVEL -II PRACTICE SHEET  
(ADVANCED) (Linked Comprehension Type Questions))**

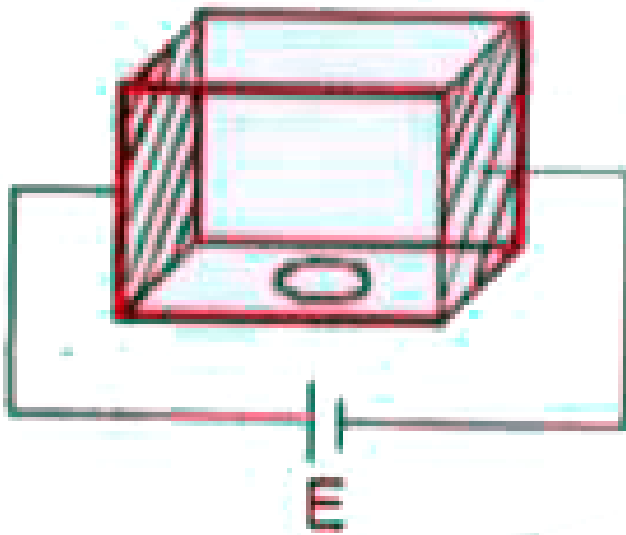**1. Passage-I :**

A hollow cube of side  $L$  has two parallel sides conducting and remaining four sides are non conducting. It is filled with a liquid of dielectric constant  $K$ . A small hole of area  $A$  at bottom of cube is open at  $t = 0$  and liquid starts leaking through it. The two conducting sides are connected by a battery of emf  $E$

$$\left( L = 9mA = \frac{18}{\sqrt{20}} m^2 k = 10E = 81v, g = 10m / \text{sec} \right)$$





Capacitance of capacitor as a function of time

A.  $\left[3 - \frac{t}{3}\right]^2$

B.  $\left[3 - \frac{t}{9}\right]^2$

C.  $(3 - t)^2$

D.  $\left[3 - \frac{t}{4}\right]^2$

**Answer: B**




**Watch Video Solution**
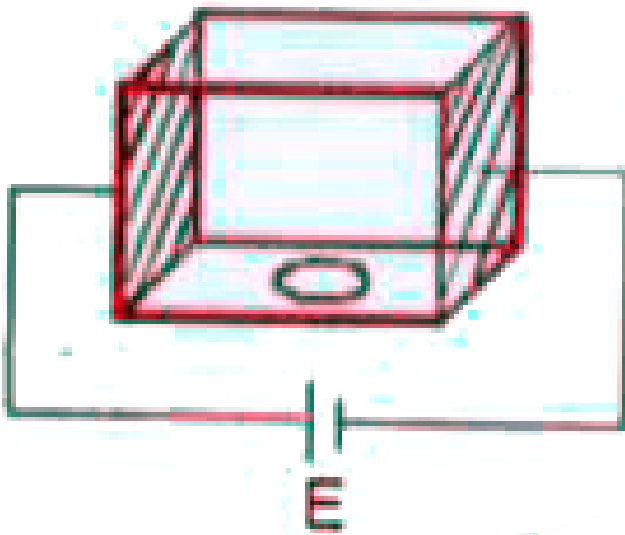
## 2. Passage-I :

A hollow cube of side  $L$  has two parallel sides conducting and remaining four sides are non conducting. It is filled with a liquid of dielectric constant  $K$ . A small hole of area  $A$  at bottom of cube is open at  $t = 0$  and liquid starts leaking through it. The two conducting sides are connected by a battery of emf  $E$

$$\left( L = 9mA = \frac{18}{\sqrt{20}} m^2 k = 10E = 81v, g = 10m / \text{sec} \right)$$



Capacitance of capacitor as a function of time

- A.  $\frac{\epsilon_0}{9} (t^2 - 54t + 64)$
- B.  $\frac{\epsilon_0}{9} (t^2 - 54t + 810)$
- C.  $\frac{\epsilon_0}{9} (t^2 + 54t + 810)$
- D.  $\frac{\epsilon_0}{9} (t^2 + 54t + 64)$

**Answer: B**




**Watch Video Solution**
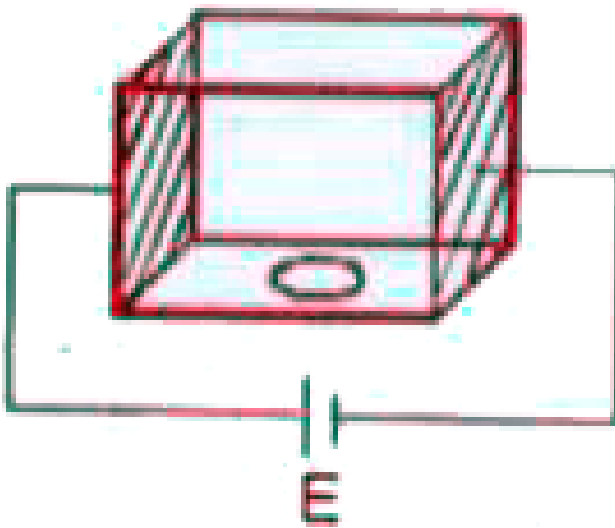
### 3. Passage-I :

A hollow cube of side  $L$  has two parallel sides conducting and remaining four sides are non conducting. It is filled with a liquid of dielectric constant  $K$ . A small hole of area  $A$  at bottom of cube is open at  $t = 0$  and liquid starts leaking through it. The two conducting sides are connected by a battery of emf  $E$

$$\left( L = 9mA = \frac{18}{\sqrt{20}} m^2 k = 10E = 81v, g = 10m/sec \right)$$




Current through the connecting wire of a time is given by

- A.  $\epsilon_0 (54 - 2t)$
- B.  $9 \epsilon_0 (54 + 2t)$
- C.  $9 \epsilon_0 (54 - 2t)$
- D.  $\frac{\epsilon_0}{9} (54 - 2t)$

**Answer: C**
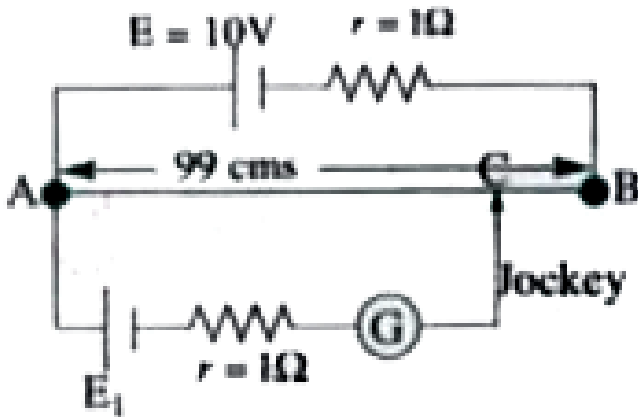
#### 4. Passage - II :

Consider a potentiometer arrangement having a uniform wire AB of resistance  $99\Omega$



A driving battery of  $10\text{V}$  emf and  $1\Omega$  internal resistance is used in the potentiometer. A cell of unknown emf  $E_1$  and internal resistance of  $1\Omega$  is balanced against AC length of potentiometer wire.

When jockey is touched with wire AB at point C such that  $AC = 40$  cm, there is no deflection in galvanometer.

The emf of cell is

A. 4V

B. 5V

C.  $\frac{5}{4}V$

D. 6V


**Answer: A**



**Watch Video Solution**
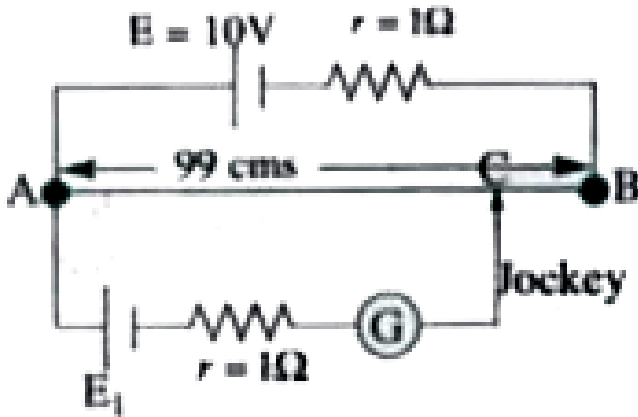
### 5. Passage - II :

Consider a potentiometer arrangement having a uniform wire AB of resistance  $99\Omega$



A driving battery of 10V emf and  $1\Omega$  internal resistance is used in the potentiometer. A cell of unknown emf  $E_1$  and internal resistance of  $1\Omega$  is balanced against AC length of potentiometer wire.

When jockey is touched with wire AB at point C such that  $AC = 40\text{ cm}$ , there is no deflection in galvanometer.

The emf of cell is



A. 6.93V

B. 8.93V

C. 9.93V

D. 0V


**Answer: A**



**Watch Video Solution**

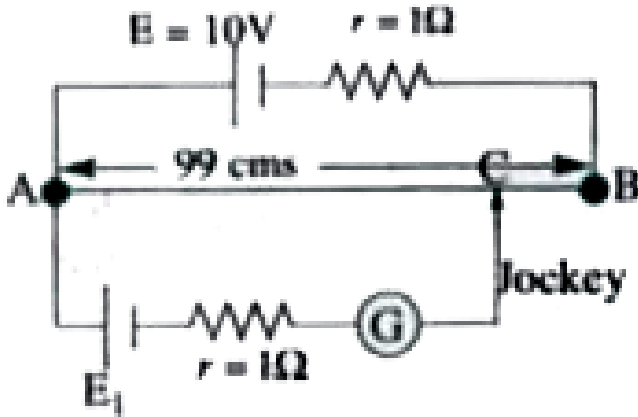**6. Passage - II :**

Consider a potentiometer arrangement having a uniform wire AB of resistance  $99\Omega$



A driving battery of 10V emf and  $1\Omega$  internal resistance is used in the potentiometer. A cell of unknown emf  $E_1$  and internal resistance of  $1\Omega$  is balanced against AC length of potentiometer wire.

When jockey is touched with wire AB at point C such that  $AC = 40\text{ cm}$ , there is no deflection in galvanometer.

The emf of cell is

A. 3V

B. 2.5V

C.  $2v$

D. None of these


**Answer: D**



**Watch Video Solution**
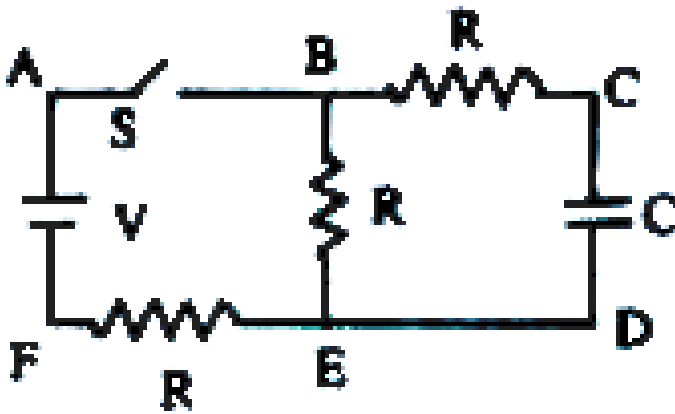
### 7. Passage-III

In the circuit shown, the battery is ideal with emf  $V$ . The capacitor is initially uncharged. The switch is closed at time  $t = 0$



The current in the branch BE at  $t = \infty$  is


- A.  $\frac{VC}{2} \left(1 - e^{-2t/3RC}\right)$
- B.  $\frac{VC}{2} \left(1 - e^{-t/3RC}\right)$
- C.  $\frac{VC}{3} \left(1 - e^{-2t/3RC}\right)$
- D.  $\frac{VC}{3} \left(1 - e^{-t/3RC}\right)$

**Answer: A**

 [Watch Video Solution](#)
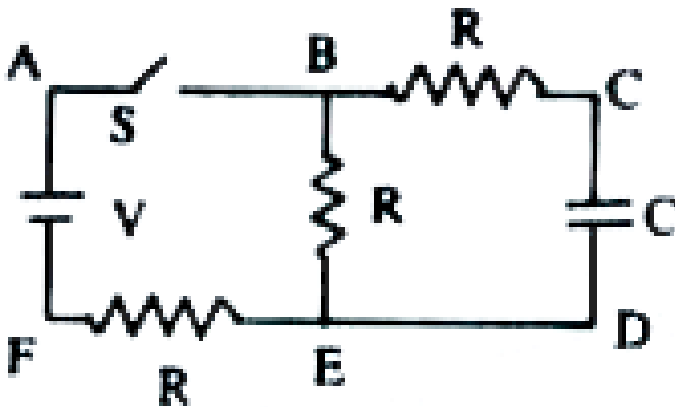
### 8. Passage-III

In the circuit shown, the battery is ideal with emf  $V$ . The capacitor is initially uncharged. The switch is closed at time  $t = 0$



The current in branch containing capacitors at any time  $t$  is

A.  $\frac{V}{3R}e^{-2t/3RC}$

B.  $\frac{V}{2R}e^{-2t/3RC}$

C.  $\frac{V}{3R}e^{-t/3RC}$

D.  $\frac{V}{2R}e^{-t/3RC}$


**Answer: A**



**Watch Video Solution**
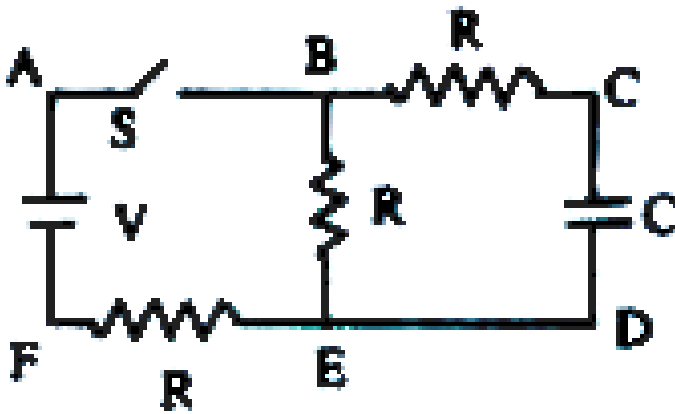
### 9. Passage-III

In the circuit shown, the battery is ideal with emf  $V$ . The capacitor is initially uncharged. The switch is closed at time  $t = 0$



The current in the branch BE at  $t = \infty$  is

- A.  $\frac{V}{2R}$
- B.  $\frac{V}{3R}$
- C.  $\frac{2V}{3R}$
- D.  $\frac{3V}{R}$

**Answer: A**

 [Watch Video Solution](#)

## PROBLEMS

1. A total of  $6.0 \times 10^{16}$  electrons pass through any cross - section of a conducting wire per second. Find the current.



[Watch Video Solution](#)

2. In a hydrogen atom, electron moves in an orbit of radius  $5 \times 10^{-11}$  m with a speed of  $2.2 \times 10^6$  m/s . Calculate the equivalent current.



[View Text Solution](#)



3. The current through a wire depends on time as

$i = i_0 + \alpha t$ , where  $i_0 = 10A$  and  $\alpha = 4A/s$ . Find the

charge crossed through a section of the wire in 10

seconds.



[View Text Solution](#)

4. A current is established in a discharge tube of cross

section  $8 \times 10^{-4}m^2$  when a sufficiently high potential

difference (say 32 kV) is applied across the two

electrodes in the tube. The gas ionises, electrons move

towards the positive terminal and positive ions

towards the negative terminal. What are the

magnitude and sense of the current in a hydrogen

discharge tube in which  $3 \times 10^{18}$  electrons and  $2 \times 10^{18}$  protons move past the cross - sectional area of the tube in each second?

 [View Text Solution](#)

5. Consider a wire of length 4m and cross - sectional area  $1\text{mm}^2$  carrying a current of 2A. If each cubic metre of the material contains  $10^{29}$  free electrons, find the average time taken by an electron to cross the length of the wire.

 [View Text Solution](#)

6. Potential difference of 100 V is applied to the ends of a copper wire one metre long. Calculate the average drift velocity of the electrons ? Compare it with thermal velocity at  $27^{\circ}C$ . Consider there is one conduction electron per atom. The density of copper is  $9.0 \times 10^3$ , Atomic mass of copper is 63.5g. Avogadro's number =  $6.0 \times 10^{23}$  per gram - mole. Conductivity of copper is  $5.81 \times 10^7 \Omega^{-1}$ . Boltzmann constant =  $1.38 \times 10^{-23} KJ^{-1}$ .



[View Text Solution](#)

7. A wire has a resistance of  $2.5\Omega$  at  $100^{\circ}C$ . Temperature coefficient of resistance of the material

$\alpha = 3.6 \times 10^{-3} K^{-1}$ . Find its resistance at  $0^\circ C$ .



[View Text Solution](#)

8. The temperature coefficient of resistance of platinum is  $\alpha = 3.92 \times 10^{-3} K^{-1}$  at  $0^\circ C$ . Find the temperature at which the increase in the resistance of platinum wire is 10% of its value of  $0^\circ C$ .



[View Text Solution](#)

9. Resistance of a wire at temperature  $t^\circ C$  is  $R = R_0(1 + at + bt^2)$  Here,  $R_0$  is the resistance at  $0^\circ C$ .

$0^{\circ}C$ . Find the temperature coefficient of resistance at temperature  $t$  is



[View Text Solution](#)

10. A silver wire has a resistance of  $2.1\Omega$  at  $27.5^{\circ}C$ , and a resistance of  $2.7\Omega$  at  $100^{\circ}C$ . Determine the temperature coefficient of resistivity of silver.



[View Text Solution](#)

11. A heating element using nichrome connected to a 230V supply draws an initial current of 3.2 A which settles after a few seconds to a steady value of 2.8A.

What is the steady temperature of the heating element if the heating the room temperature is  $27.0^{\circ}C$ ? Temperature coefficient of resistance of nichrome averaged over the temperature range involved is  $1.70 \times 10^{-4} .^{\circ} C^{-1}$ .

 [View Text Solution](#)

12. V - I graph of a conductor at temperature  $T_1$  and  $T_2$  are shown in the figure ( $T_2 - T_1$ ) is proportional to

 [View Text Solution](#)

**13.** A wire of silver has a resistance of 1 ohm. Specific resistance of constantan is 30 times the specific resistance of silver. Find the resistance of a constantan wire whose length is one third length of the silver wire and radius half the radius of the silver wire.

 [View Text Solution](#)

**14.** A rectangular block has dimensions  $5\text{ cm} \times 5\text{ cm} \times 10\text{ cm}$ . Calculate the resistance measured between (a) two square ends and (b) the opposite rectangular ends specific resistance of the material is  $3.5 \times 10^{-5} \Omega\text{ m}$

 [View Text Solution](#)

 [View Text Solution](#)

**15.** Two wires of same material have their lengths in the ratio 2:3 and radii 8:9 . Equal value of p.d is applied between their ends (separately). Calculate the ratio of current through those two



[View Text Solution](#)

**16.** Figure shows a conductor of length  $l$  having a circular cross - section. The radius of cross - section varies linearly from  $a$  to  $b$ . The resistivity of the materia is  $\rho$ . Assuming that  $b - a \ll l$ , find the resistance of the conductor.



 [View Text Solution](#)

17. Two wires A and B of same mass and material are taken. Diameter of wire A is half of wire B. If resistance of wire A is  $24\Omega$  find the resistance of wire B.

 [View Text Solution](#)

18. What will be the resistance of a semi circle shown in fig., between its two end faces. Given that radial thickness is 3cm, axial thickness is 4 cm, inner radius is 6 cm and specific resistance is  $4 \times 10^{-6} \text{ ohm} - \text{cm}$

 [View Text Solution](#)

**19.** A hollow cylinder of specific resistance  $\rho$ , inner radius  $R$ , outer radius  $2R$  and length  $l$  is as shown in figure. What is the net resistance between the inner and outer surface?



[View Text Solution](#)

**20.** There are two concentric spheres of radius  $(a)$  and  $(b)$  respectively. If the space between them is filled with medium of resistivity  $\rho$ , then the resistance of the intergap between the two spheres will be



[View Text Solution](#)

21. A hollow copper cylinder is of inner radius 4cm and outer radius 5cm. Now hollow portion is completely filled with suitable copper wires. Find percentage change in its electric resistance.



[View Text Solution](#)

22. Resistivity of the material of a conductor of uniform cross-section varies along its length as  $\rho = \rho_0(1 + \alpha x)$ . Find the resistance of the conductor, if its length is  $l$  and area of cross-section  $A$ .



[View Text Solution](#)

23. How many number of turns of nichrome wire of specific resistance  $10^{-6}\Omega m$  and diameter 2mm that should be wound on a cylinder of diameter 5cm to obtain a resistance of ?



[View Text Solution](#)

24. Suppose the colours on the resistor as shown in Figure are brown, yellow, green and gold as read from left to right. Using the table, find the resistance of the resistor




[View Text Solution](#)

25. What is the color code for a resistor of resistance  $350m\Omega$  with 5% tolerance?

[View Text Solution](#)

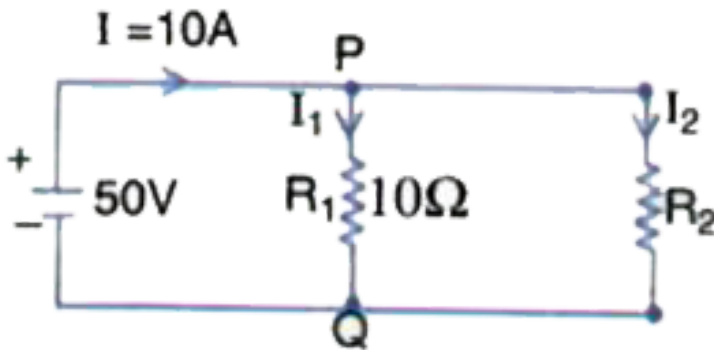26. For a circuit shown in Fig. find the value of resistance  $R_2$  and current  $I_2$  flowing through  $R_2$



[View Text Solution](#)


27. Two wires of equal diameters of resistivities  $p_1$  and  $p_2$  and length  $x_1$  and  $x_2$  respectively are joined in series. The equivalent resistivity of the combination is

 [View Text Solution](#)

28. An electric current is passed through a circuit containing two wires of the same material, connected in parallel. If lengths and radii of the wires are in the ratio of 4 : 3 and 2 : 3 , then ratio of the currents passing through the wires will be

 [View Text Solution](#)

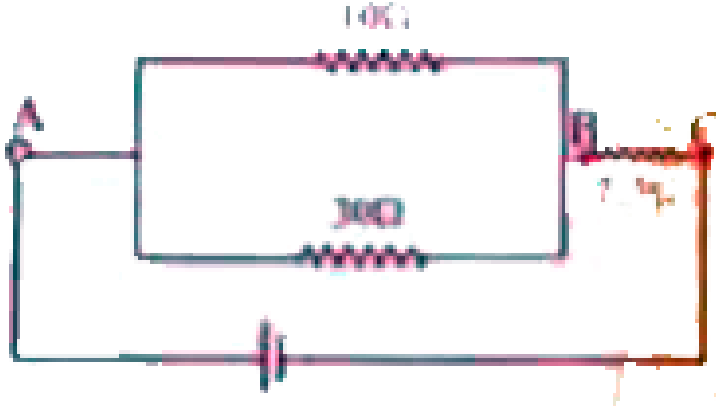
29. Find equivalent resistance of the network in Fig. between points (i) A and B and (ii) and C.



[View Text Solution](#)

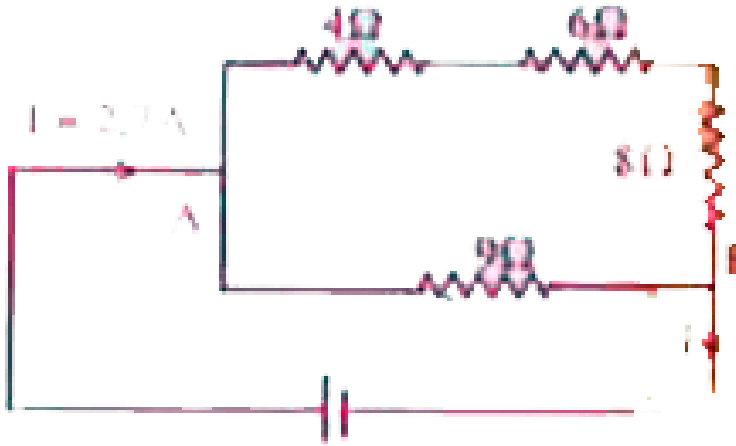30. Find potential difference between points A and B of the network shown in Fig. and distribution of given

main current through different resistors.




[View Text Solution](#)

31. P and Q are two points on a uniform ring of resistance R. The equivalent resistance between P and




Q is

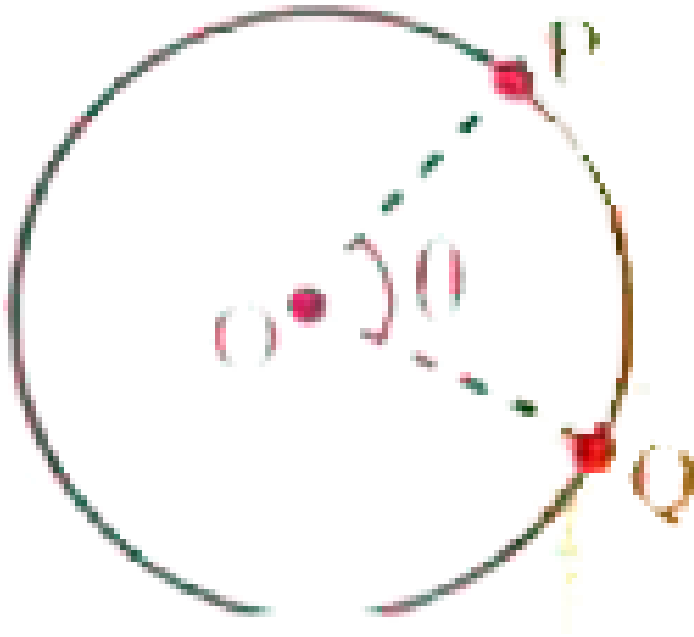

[View Text Solution](#)

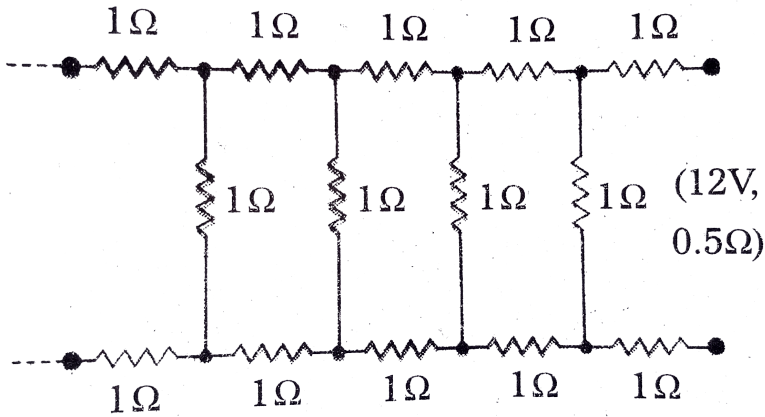
32. Determine the current drawn from a 12 V supply with internal resistance  $0.5\Omega$  by the infinite network

shown in Fig. Each resistor has  $1\Omega$  resistance.



[View Text Solution](#)

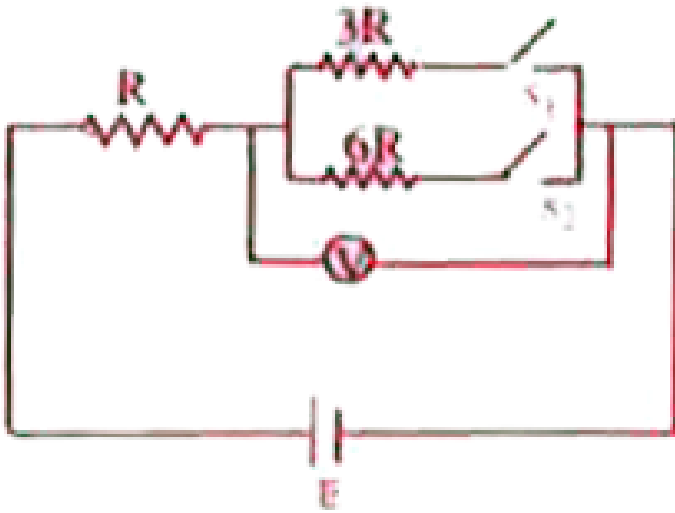**33.** In the circuit shown in figure reading of voltmeter is  $V_1$  when only  $S_1$  is closed, reading of voltmeter is  $V_2$  when only  $S_2$  is closed and reading of voltmeter is  $V_3$  when both  $S_1$  and  $S_2$  are closed. Then




- 1)  $V_3 > V_2 > V_1$
- 2)  $V_2 > V_1 > V_3$
- 3)  $V_3 > V_1 > V_2$
- 4)  $V_1 > V_2 > V_3$




[View Text Solution](#)

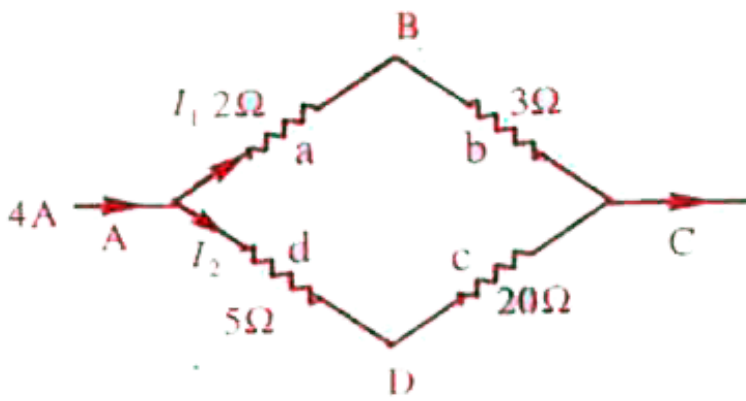**34.** In the given network, calculate the potential difference between the points B and D



[View Text Solution](#)

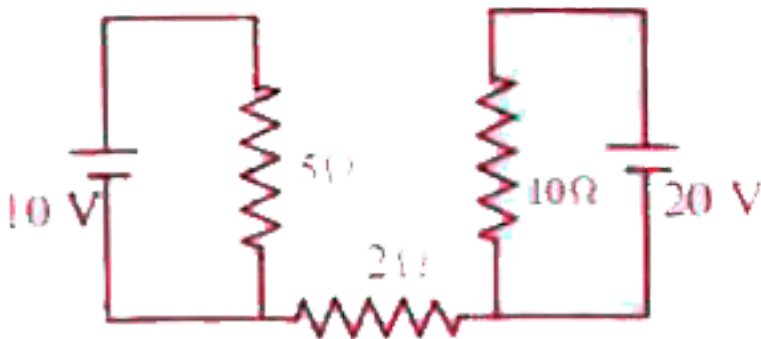35. Find out the value of current through  $2\Omega$  resistance for the given circuit.



[View Text Solution](#)

**36.** A 1kW heater is meant to operate at 200 V. (a) What is its resistance ? (b) How much power will it consume if the line voltage drops to 100 V ? (c ) How many units of electrical energy will it consume in a month (of 30 days) if it operates 10 hr daily at the specified voltage?



[View Text Solution](#)

**37.** Three equal resistors connected in series across a source of emf together dissipate 10 watt of power. What would be the power dissipated if the same

resistances are connected in parallel across the same source of emf?

 [View Text Solution](#)

**38.** To boil a certain mass of water, a coil will take a time of  $t_1$  and another coil will take a time of  $t_2$ . What will be the time taken when the coils are connected in (i) series (ii) in parallel?

 [View Text Solution](#)

**39.** A lamp of 100 W works at 220 volts. What is its resistance and current capacity?

 [View Text Solution](#)

**40.** A  $100W - 220V$  bulb is connected to  $110 V$  source.

Calculate the power consumed by the bulb.

 [View Text Solution](#)

**41.** A  $100 W$  and a  $500 W$  bulbs are joined in series and connected to the mains. Which bulb will glow brighter ?

 [View Text Solution](#)

**42.** A cell develops the same power across two resistance  $R_1$  and  $R_2$  separately. The internal resistance of the cell is



**Watch Video Solution**


**43.** A wire of length  $L$  and 3 identical cells of negligible internal resistance are connected in series. Due to the current, the temperature of the wire is raised by  $\Delta t$  in a time  $t$ . A number  $N$  of similar cells is now connected in series with a wire of the same material and cross-section but of length  $2L$ . The temperature of the wire is raised by the same amount  $\Delta t$  in the same time  $t$ . The value of  $N$  is





Watch Video Solution

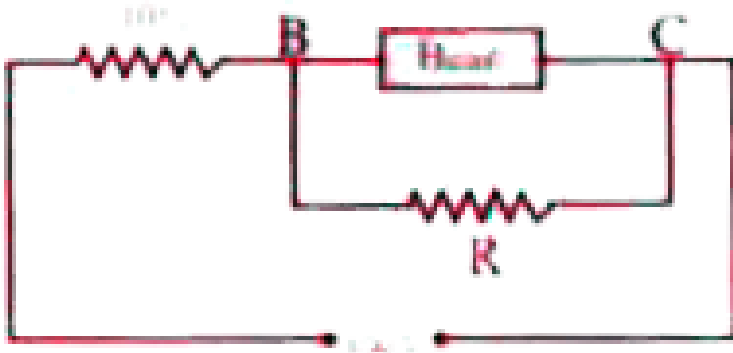44. A heater is designed to operate with a power of 1000 watt in a 100 V line. It is connected in combination with a resistance of  $10\Omega$  and a resistance  $R$ . to a 100 V mains as shown in the figure. What will be the value of  $R$  so that the heater operates with a power of 62.5 W?



View Text Solution


**45.** In the circuit shown in figure the heat produced in the 5 ohm resistor due to the current flowing through it is 10 calorie per second. The heat generated in the 4 ohm resistor is



**View Text Solution**

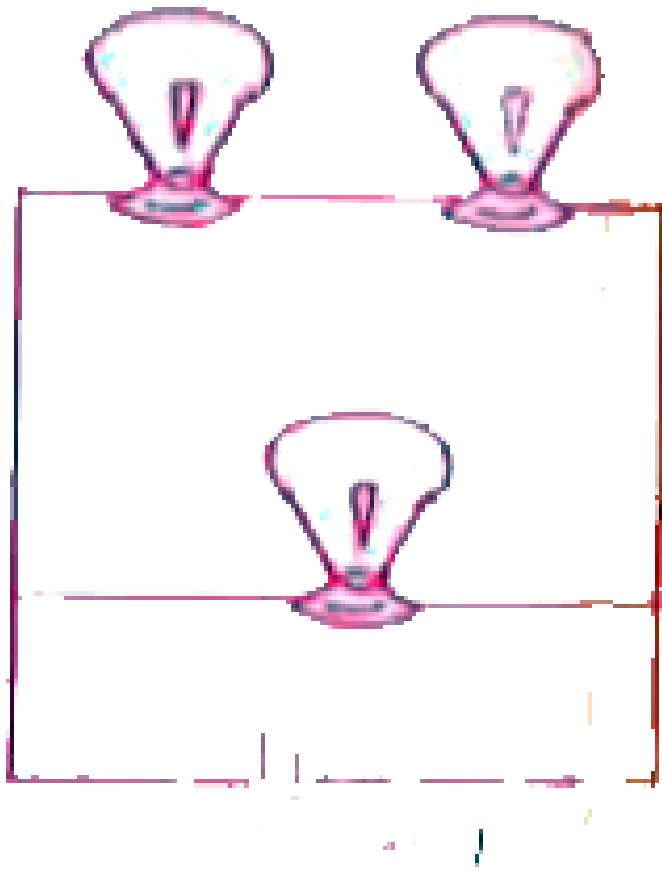**46.** A 100 W bulb  $B_1$  and two 60 W bulbs  $B_2$  and  $B_3$  are connected to a 250 V source, as shown in the figure. Now  $W_1$ ,  $W_2$  and  $W_3$  are the output powers of

the bulbs  $B_1$ ,  $B_2$  and  $B_3$  respectively. Then



[View Text Solution](#)

**47.** An electric bulb rated for 500 watt at 100 volt is used in a circuit having a 200 volt supply. The resistance  $R$  that must be put in series with the bulb, so that the bulb delivers 500 watt is ..... Ohm.



[View Text Solution](#)

**48.** An electric tea kettle has two heating coils. When one of the coils is switched on, boiling begins in 6 min. When the other coil is switched on, the boiling begins in 8 min. In what time, will the boiling begin if both coils are switched on simultaneously (i) in series and (ii) in parallel.



[View Text Solution](#)


 [View Text Solution](#)

**49.** If two bulbs of 25 W and 100 W rated at 220 V are connected in series across 440 V supply. Will both the bulbs fuse? If not which one?

 [View Text Solution](#)

**50.** A battery of internal resistance  $4\Omega$  is connected to the network of resistances as shown. What must be the value of R so that maximum power is delivered to the

network? Find the maximum power?

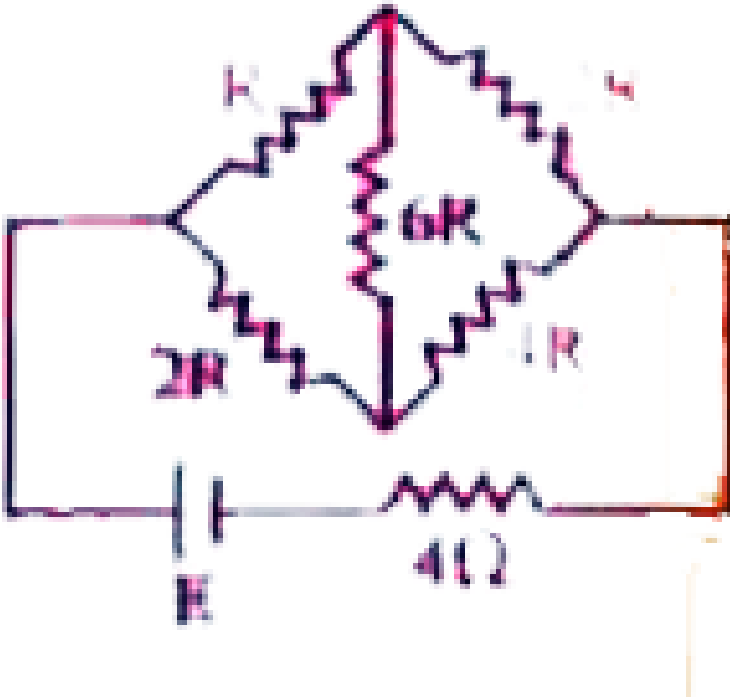

[View Text Solution](#)

51. A fuse wire with radius of 0.2mm blows off with a current of 5 Amp. The fuse wire of same material, but of radius 0.3 mm will blow off with a current of

1)  $5 \times \frac{3}{2}$  Amp

2)  $\frac{5\sqrt{3}}{2}$  Amp

3)  $5\sqrt{\frac{27}{8}}$  Amp

4) 5 Amp



[View Text Solution](#)

**52.** A battery of emf 10 V and internal resistance  $3\Omega$  is connected to a resistor. If the current in the circuit is 0.5 A, what is the resistance of the resistor? What is the terminal voltage of the battery when the circuit is closed?



[Watch Video Solution](#)

53. When a current drawn from a battery is 0.5A, its terminal potential difference is 20V. And when current drawn from it is 2.0A, the terminal voltage reduces to 16V. Find out, e.m.f and internal resistance of the battery.



[View Text Solution](#)

54. An ideal battery passes a current of 5A through a resistor. When it is connected to another resistance of  $10\Omega$  in parallel, the current is 6A. Find the resistance of the first resistor.



[View Text Solution](#)



**55.** When a resistor of  $11\Omega$  is connected in series with an electric cell in series, the current increases by  $0.4\text{ A}$ . The internal resistance of the cell is

 [Watch Video Solution](#)

**56.** When a battery is connected to the resistance of  $10\Omega$  the current in the circuit is  $0.12\text{ A}$ . The same battery gives  $0.07\text{A}$  current with  $20\Omega$  Calculate e.m.f. and internal resistance of the battery.

 [View Text Solution](#)

57. The potential difference across the terminals of battery is 10 V when there is a current of 3A in battery from the negative to the positive terminate when the current is 2A in the reverse direction, potential difference becomes 15 V. The inter resistance of the battery is

 [Watch Video Solution](#)

58. Two cells A and B with same e.m.f of 2 V each and with internal resistances  $r_A = 3.5\Omega$  and  $r_B = 0.5\Omega$  are connected in series with an external resistance  $R = 3\Omega$ . Find the terminal voltage across the two cells.

 [View Text Solution](#)


 [View Text Solution](#)

**59.** Two cells A and B each of 2V are connected in series to an external resistance  $R = 1$  ohm. The internal resistance of A is  $r_A = 1.9$  ohm and B is  $r_B = 0.9$  ohm. Find the potential difference between the terminals of A.



[View Text Solution](#)

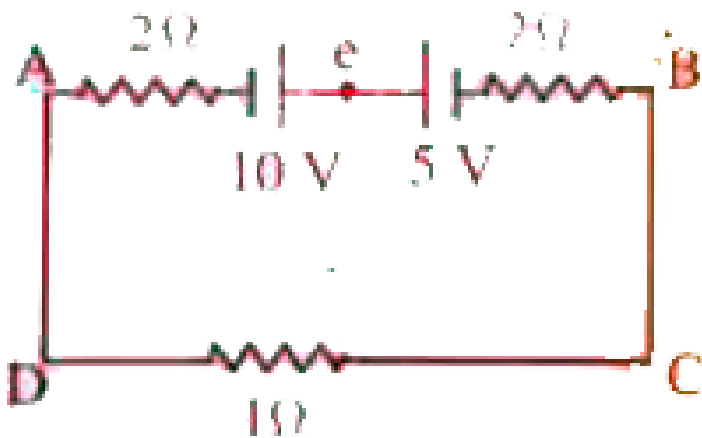**60.** In the given circuit as shown below, calculate the magnitude and direction of the current




[View Text Solution](#)

61. Two batteries each of emf  $E$  and internal resistance  $r$  are connected in series and in parallel, and are used to find current in an external resistance  $R$ . If the current in series is equal to that in parallel, the internal resistance of each battery is

[View Text Solution](#)

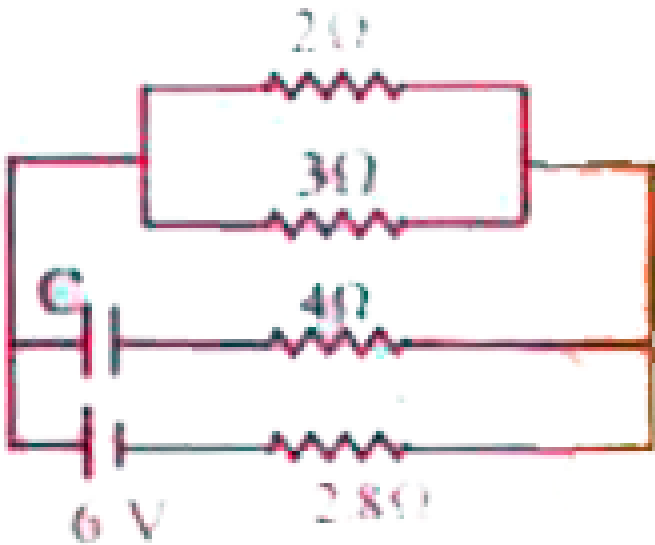62. In the steady state of the below given circuit, find the charge on the capacitor of capacity  $0.2\mu F$ .



[View Text Solution](#)

63. Twelve cells each having the same emf are connected in series and are kept in a closed box. Some


of the cells are wrongly connected. This battery is connected in series with an ammeter and two cells identical with each other. The current is 3A when the cells and battery aid each other and 2A when the cells and battery oppose each other. How many cells are wrongly connected?

 [View Text Solution](#)

64. A voltmeter with resistance  $500\Omega$  is used to measure the emf of a cell of internal resistance  $4\omega$ , percentage error in the reading of the voltmeter will be

 [Watch Video Solution](#)

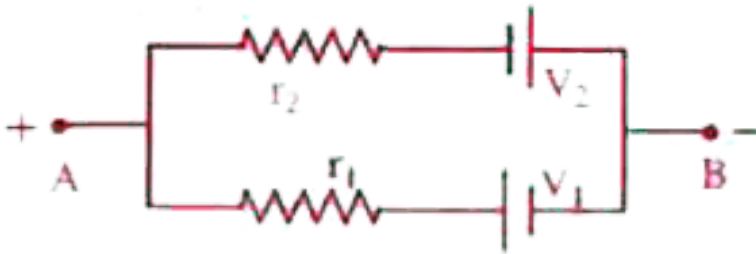65. Find the emf (V) and internal resistance ( $r$ ) of a single battery which is equivalent to a parallel combination of two batteries of emfs  $V_1$  and  $V_2$  and internal resistances  $r_1$  and  $r_2$  respectively, with polarities as shown in figure




 [View Text Solution](#)

66. Consider the network as shown in Fig. Current is supplied to the network by two batteries as shown.

Find the values of currents  $I_1$ ,  $I_2$ ,  $I_3$ . The direction of the currents are as indicated by the arrows.


[View Text Solution](#)

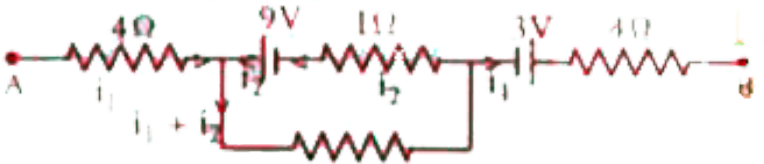67. For the circuit shown in the figure, potential difference between points A and B is 16 V. Find the current passing through  $2\Omega$ .



[View Text Solution](#)



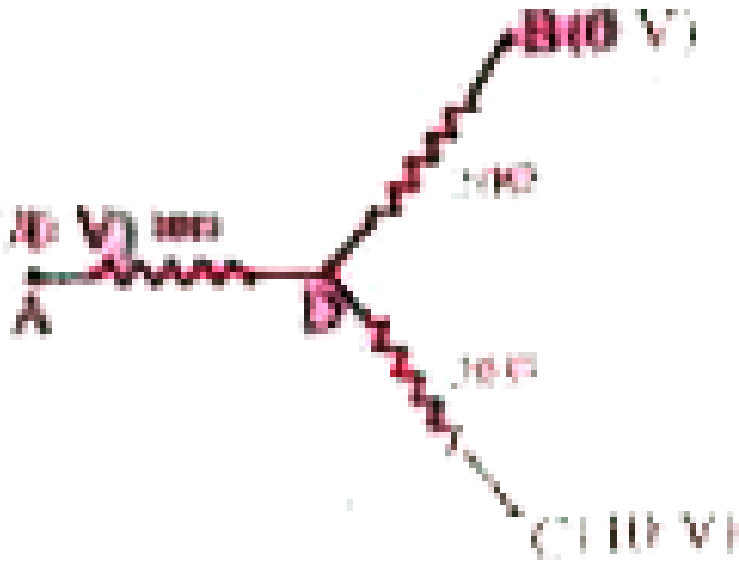

68.

In the network shown A, B and C are at potentials of 70 V, zero V and 10 V respectively. The false one is

- 1) Point D is at a potential of 40 V
- 2) The currents in the sections AD, DB, DC are in the ratio 3: 2: 1
- 3) The current in the section AD, DB, DC are in the ratio

1 : 2 : 3


4) The network draws a total power of 200 W

[View Text Solution](#)

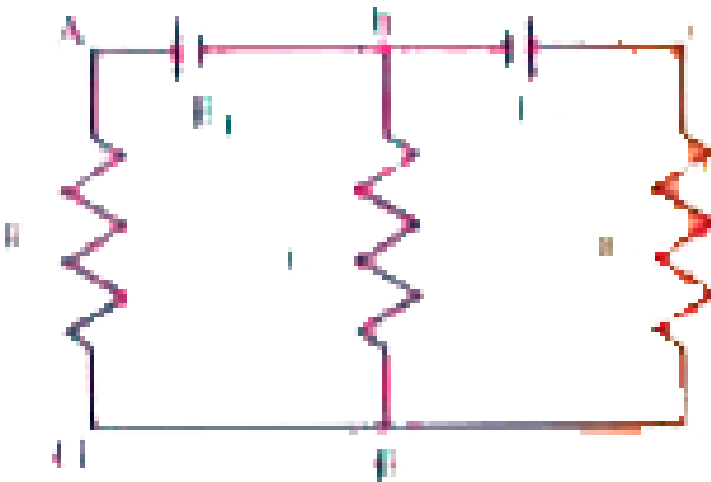69. In the given circuit values are as follows


$$\varepsilon_1 = 2V, \varepsilon_2 = 4V, R_1 = 1\Omega \quad \text{and} \quad R_2 = R_3 = 1\Omega.$$

Calculate the Currents through  $R_1$ ,  $R_2$  and  $R_3$ .




[View Text Solution](#)

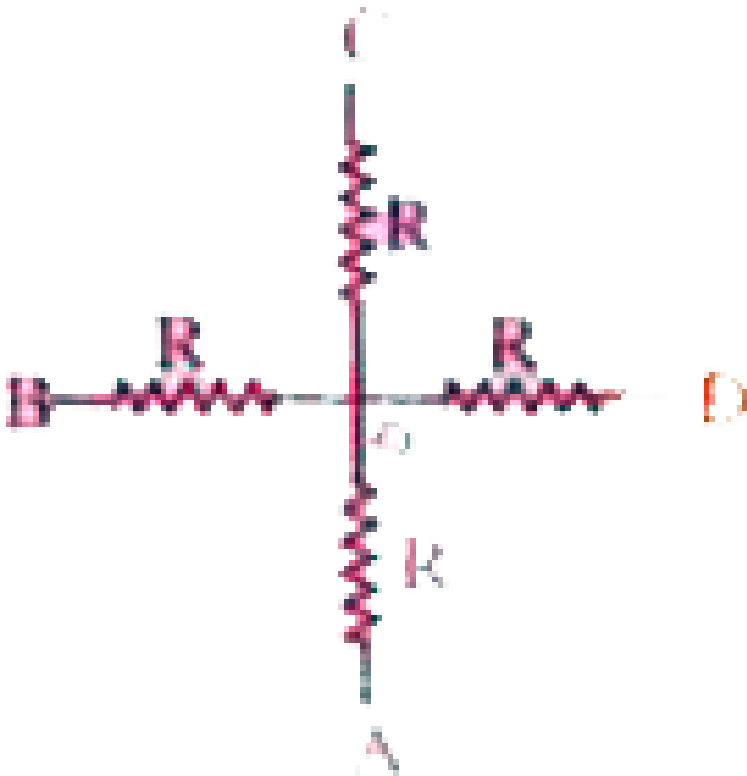70. The given four terminal net work is a part of larger circuit. The points A, B, C are at the same potential. The P.E. between any one of A, B or C and D is 40 V. Find the P.D. between A & O.




71. Solve for current values in figure.

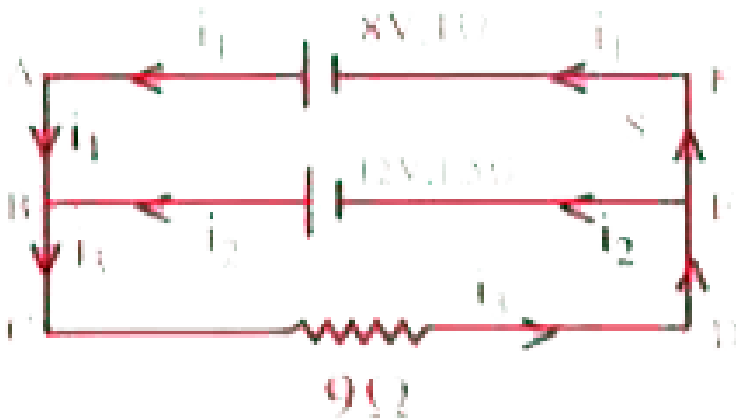

[View Text Solution](#)

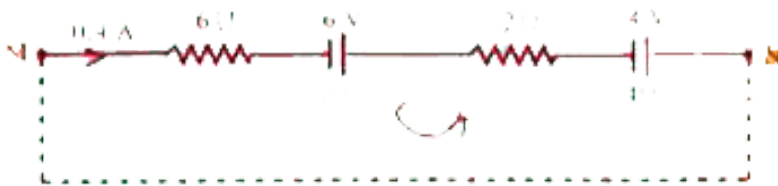72. Find the potential difference between and N in the given branch of a circuit figure.




[View Text Solution](#)

73. Two cells  $E_1$  (with emf  $4\text{ V}$  and internal resistance  $2\ \Omega$ ) and  $E_2$  (with emf  $2\text{ V}$  and internal resistance  $2\ \Omega$ ) are connected in parallel. The combination is connected in parallel with a  $8\ \Omega$  resistance  $R$  as shown in figure. Calculate the currents passing through  $2\text{ V}$  cell and through the resistance  $R$ .

[View Text Solution](#)

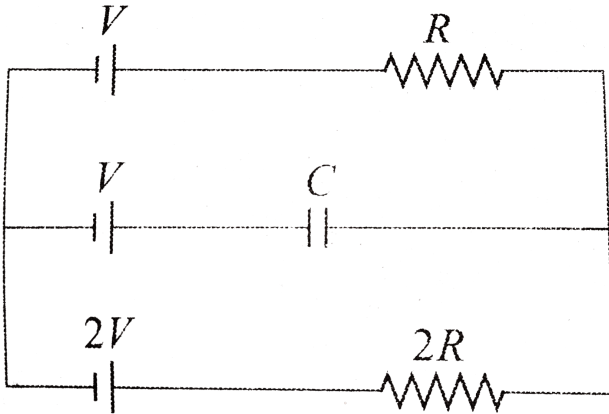
74. In the given circuit, with steady current, the potential drop across the capacitor must be



[Watch Video Solution](#)

75. Find the equivalent resistance of the circuit of the previous problem between the ends of an edge such as


a and b in figure.

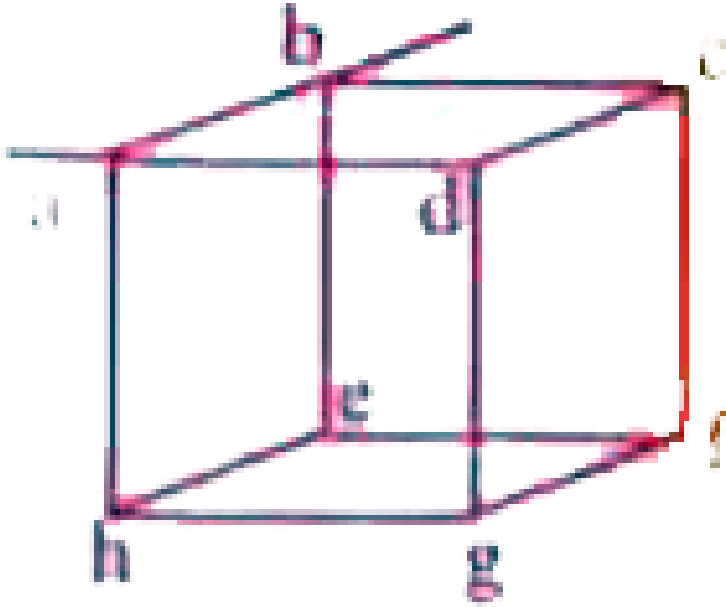

[View Text Solution](#)

76. Twelve equal wires, each of resistance  $r$  ohm are connected so as to form a skeleton cube. Find the equivalent resistance between the diagonally opposite

points 1 and 7.

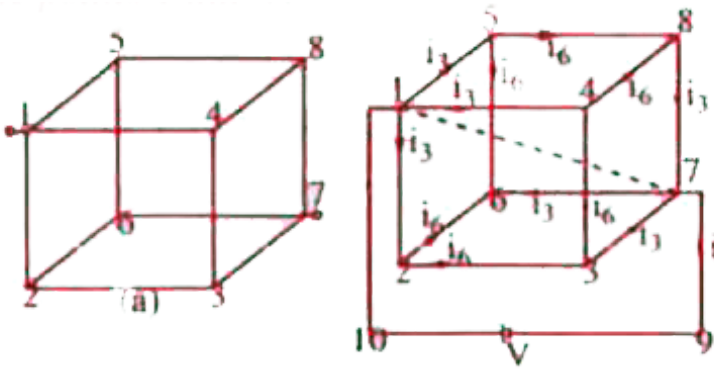


[View Text Solution](#)

77. Twelve wires, each having resistance  $r$ , are joined to form a cube as shown in figure. Find the equivalent resistance between the ends of a face diagonal such as




a and c.

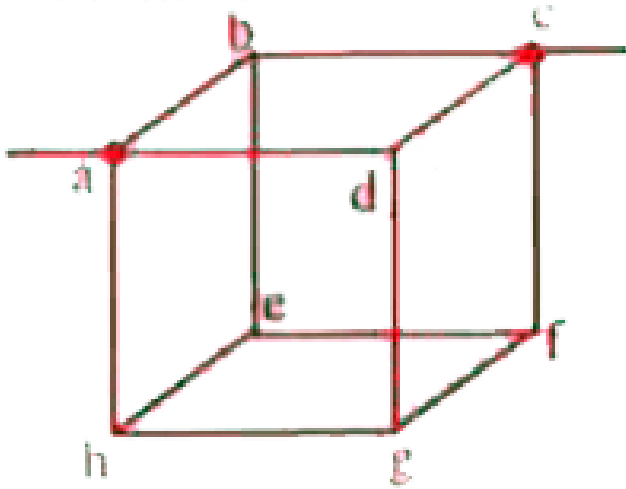


[View Text Solution](#)

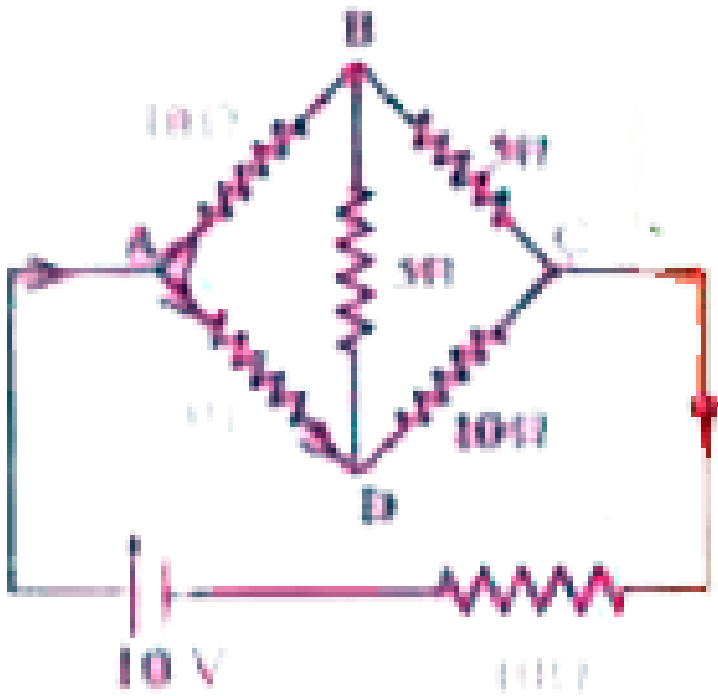**78.** Determine the current in each branch of the network shown in fig.



[View Text Solution](#)

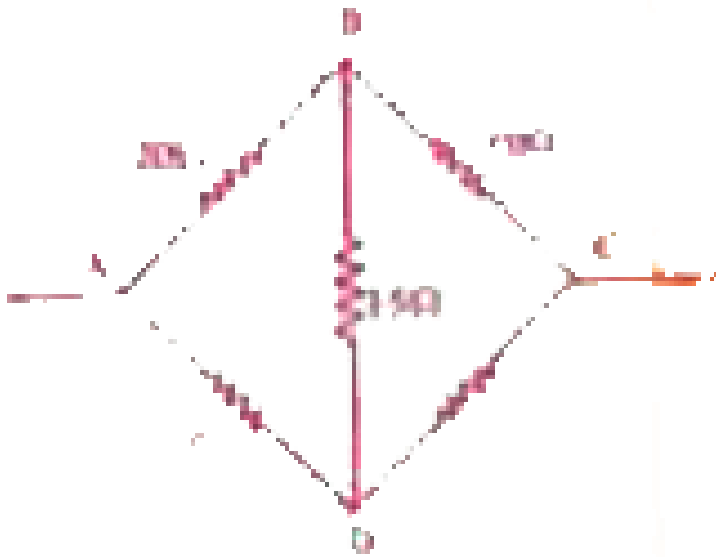79. Find the value of  $R$  in Fig. so that there is no current in the  $15\Omega$  resistor.




[View Text Solution](#)

80. Find the Equivalent resistance across A and R in the given circuit if  $r = 10\Omega$ ,  $R = 20\Omega$ .

[View Text Solution](#)

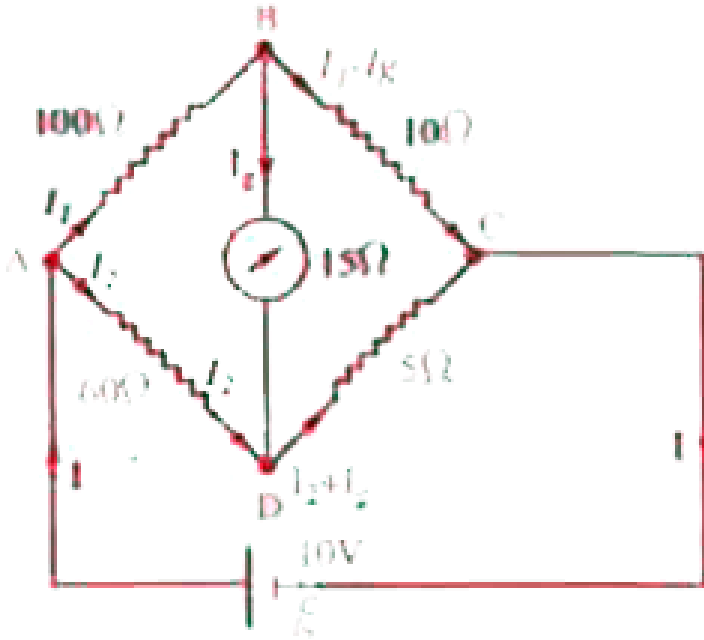81. The four arms of a Wheatstone bridge (Figure) have the following resistance :

$$AB = 100\Omega, BC = 10\Omega, CD = 5\Omega \text{ and } DA = 60\Omega$$



A galvanometer of  $15\Omega$  resistance is connected across BD. Calculate the current through the galvanometer when a potential difference of 10 V is maintained across AC,



[View Text Solution](#)


**82.** Find the effective resistance between P and Q points P and Q of the electrical circuit shown in the figure



[View Text Solution](#)

**83.** Twelve equal resistance are connected as shown in the diagram. Find the effective resistance between A

and B

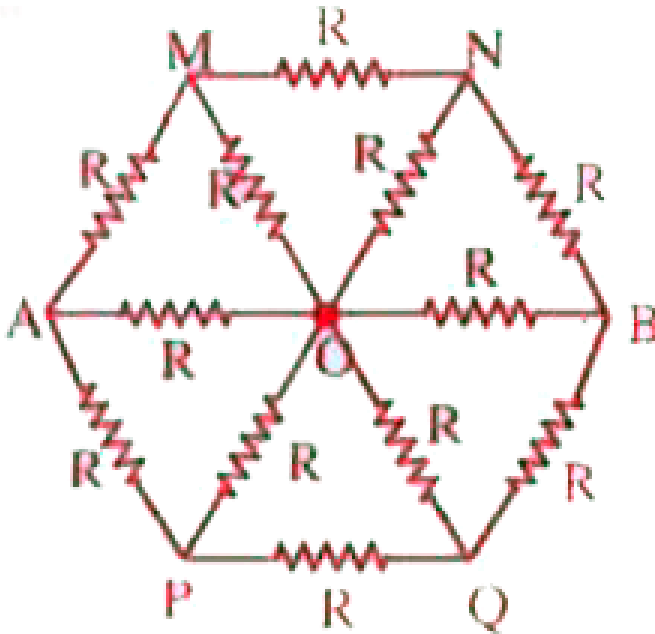

[View Text Solution](#)

**84.** In the given circuit it is observed that the current  $I$  is independent of the value of the resistance  $R_5$ . Then what is the relation the resistance values must satisfy.



[View Text Solution](#)

**85.** A balance point in a meter bridge experiment is obtained at 30 cm from the left. If right gap contains  $3.5\Omega$ , what is the resistance in the left gap?




**View Text Solution**

**86.** In a meter bridge (Fig. 3.27), the null point is found at a distance of 33.7 cm from A. If now a resistance of  $12\Omega$  is connected in parallel with S, the null point occurs at 51.9 cm. Determine the values of R and S.



**Watch Video Solution**

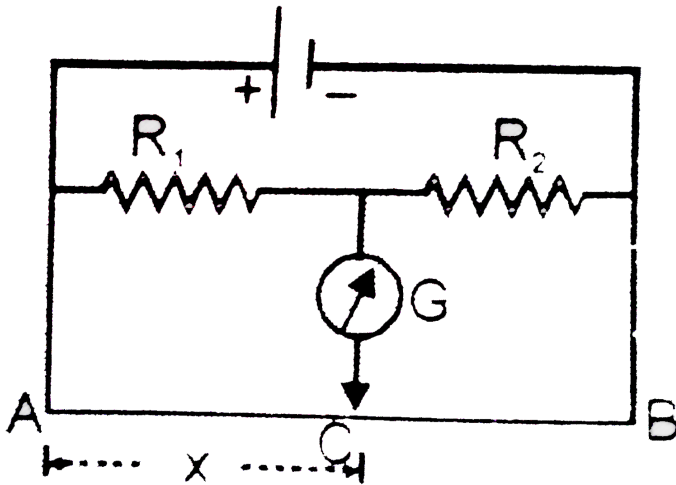87. In the shown arrangement of the experiment of the meter bridge if AC corresponding to null deflection of galvanometer is  $x$ . what would be its value if the radius of the wire AB is doubled:-



[▶ Watch Video Solution](#)



**88.** A resistance of  $2\Omega$  is connected across one gap of a metre-bridge (the length of the wire is 100 cm) and an unknown resistance, greater than  $2\Omega$ , is connected across the other gap. When these resistances are interchanged, the balance point shifts by 20 cm. Neglecting any corrections, the unknown resistance is

 [View Text Solution](#)

**89.** The length of a potentiometer wire is 1m and its resistance is  $4\Omega$ . A current of 5mA is flowing in it. An unknown source of e.m.f is the source.

 [View Text Solution](#)

90. A resistance of  $R_w$  draws current from a potentiometer. The potentiometer has a total resistance  $R_0 \Omega$  (Fig). A voltage  $V$  is supplied to the potentiometer.

Derive an expression for the voltage across  $R$  when the sliding contact is in the middle of the potentiometer.



[View Text Solution](#)

91. A battery of unknown emf connected to a potentiometer has balancing length 560 cm. If a resistor of resistance 10 ohm, is connected in parallel with the cell the balancing length change by 60 cm. If the internal resistance of the cell is  $\frac{n}{10}$  ohm, the value of 'n' is

 [Watch Video Solution](#)

92. A cell of e.m.f 2 volt and internal resistance  $1.5\Omega$  is connected to the ends of 1m long wire. The resistance of wire is  $0.5\Omega/m$ . Find the value of potential gradient on the wire.

 [View Text Solution](#)


**93.** In a potentiometer experiment when a battery of e.m.f. 2 V is included in the secondary circuit, the balance point is 500 cm. Find the balancing length of the same end when a cadmium cell of e.m.f. 1.018V is connected to the secondary circuit.



[View Text Solution](#)

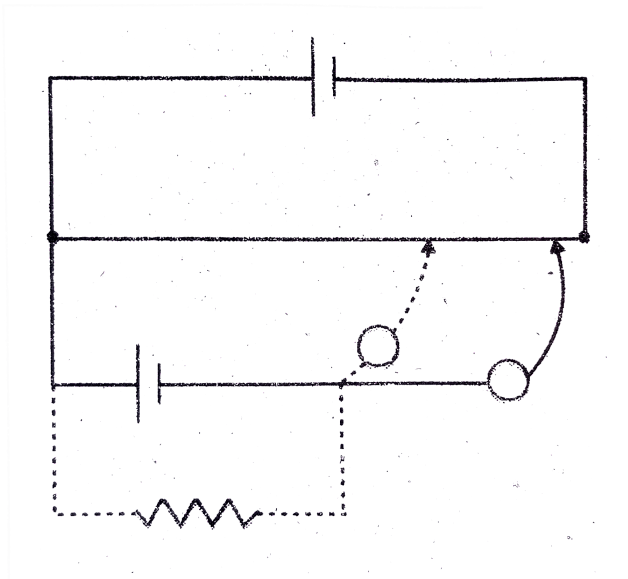**94.** Figure shows a 2.0 V potentiometer used for the determination of internal resistance of a 1.5 V cell. The balance point of the cell in open circuit is 76.8 cm. when a resistor of  $9.5\Omega$  is used in the external circuit of the

cell, the balance point shifts to 64.8 cm length of the potentiometer wire. Determine the internal resistance of the cell.



[View Text Solution](#)

EXERCISE - IA

1. Typical drift velocity in conductor wire is  $10^{-2} \text{ m/s}$ ,  
i.e. it takes 100 sec to drift 1 m while bulb glows  
instantaneously, how

A. The random speed of electrons is very high, of  
the order of  $10^6 \text{ m/s}$

B. The electrons transfer their energy very quickly  
through collisions

C. Electric field is set up in the wire very quickly,  
producing a current through each cross section,  
almost instantaneously

D. All of above

**Answer: C**



**Watch Video Solution**

2. Mobility of free electrons in a conductor is

- A. directly proportional to electron density
- B. directly proportional to relaxation time
- C. inversely proportional to electron density
- D. inversely proportional to relaxation time

**Answer: B**



**Watch Video Solution**

