



## PHYSICS

### BOOKS - RESNICK AND HALLIDAY PHYSICS (HINGLISH)

## CIRCUITS

#### Sample Problems

1. The emf and resistances in the circuit of Fig 27-8a have the following values:

$$\varepsilon_1 = 4.4V, \varepsilon_2 = 2.1V,$$

$$r_1 = 2.3\Omega, r_2 = 1.8\Omega, R = 5.5\Omega$$

(a) What is the current  $I$  in the circuit?

(b) What is the potential difference between the terminals of battery 1 in Fig. 27 8a?



[Watch Video Solution](#)

2. Figure 27-11a shows a multiloop circuit containing one ideal battery and four resistances with the following values:

$$R_1 = 20\Omega, R_2 = 20\Omega, \varepsilon = 12V,$$

$$R_3 = 30\Omega, R_4 = 8.0\Omega$$

(a) What is the current through the battery?

(b) What is the current  $i_2$  through  $R_2$ ?

(c) What is the current  $i_3$  through  $R_3$ ?



[Watch Video Solution](#)

3. Figure 27-12 shows a circuit whose elements have the following values:  $\varepsilon_1 = 3.0V, \varepsilon_2 = 6.0V, R_1 = 2.0\Omega, R_2 = 2.0\Omega$ . The three

batteries are ideal batteries. Find the magnitude and direction of the current in each of the three branches



[View Text Solution](#)

4. Twelve wires, each having resistance  $r$ , are joined to form a cube as shown in Fig. 27-18. Find the equivalent resistance between the ends of a face diagonal such as  $a$  and  $c$ .

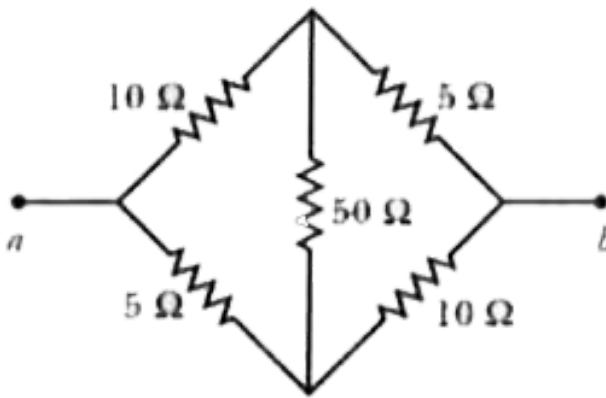


Figure 27.18 Twelve equal resistors are arranged in the shape of a cube. The battery is connected between points  $a$  and  $c$ .



[View Text Solution](#)

5. Find the equivalent resistance between points  $a$  and  $b$  of the circuit shown in Fig 27-20.



A network of five resistances.

[View Text Solution](#)

6. As a car rolls along pavement, electrons move from the pavement first onto the tires and then onto the car body. The car stores this excess charge and the associated electric potential energy as if the car body were one plate of a capacitor and the pavement were the other plate (Fig. 27-35a). When the car stops, it discharges its excess charge and energy through the tires, just as a capacitor can discharge through a resistor. If a conducting object

comes within a few centimeters of the car before the car is discharged, the remaining energy can be suddenly transferred to a spark between the car and the object. Suppose the conducting object is a fuel dispenser. The spark will not ignite the fuel and cause a fire if the spark energy is less than the critical value

$$U_{\text{fire}} = 50\text{mJ}.$$

When the car of Fig. 27-35a stops at time  $t=0$ , the car ground potential difference is  $V_0 = 30\text{kV}$ . The car-ground capacitance is  $C = 500\text{pF}$ , and the resistance of each tire is  $R_{\text{tire}} = 100\text{G}\Omega$ .

How much time does the car take to discharge through the tires to drop below the critical value  $U_{\text{fire}}$ ?




[View Text Solution](#)

7. (a) Find the current  $I$  supplied by the battery in the network as shown in steady state. (b) Find the steady state charge on the capacitor. (c) Find the initial current through the battery.

## Checkpoints

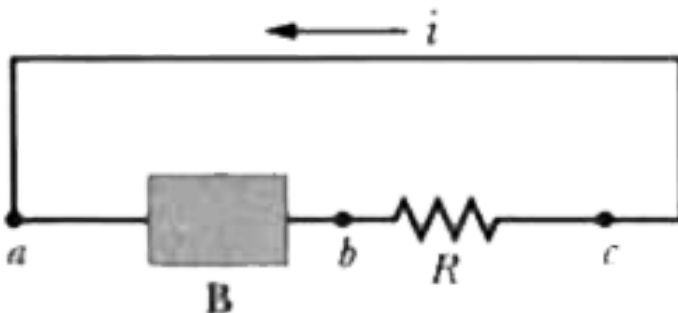1. The figure shows the current  $I$  in a single-loop circuit with a battery  $B$  and a resistance  $R$  (and wires of negligible resistance). (a) Should the emf arrow at  $B$  be a drawn pointing leftward or rightward? At points  $a, b$  and  $c$  rank (b) the magnitude of the current )c the electric potential, and (d) the electric potential energy of the charge carriers greatest first.



2. If  $R_1 > R_2 > R_3$ , rank the three resistances according to (a) the current through them and (b) the potential across them, greatest first.

 [View Text Solution](#)

3. A battery has an emf of 12 V and an internal resistance of  $2\Omega$ . Is the terminal-to-terminal potential difference greatest then less than, or equal to 12V if the current in the battery is (a) from the negative to the positive terminal, (b) from the positive to the negative terminal, and (c) zero?


 [Watch Video Solution](#)

4. A battery, with potential  $V$  across it, is connected to a combination of two identical resistors and then has current  $I$

through it. What are the potential difference across and the current through either resistor if the resistors are (a) in series and (b) in parallel?

[View Text Solution](#)

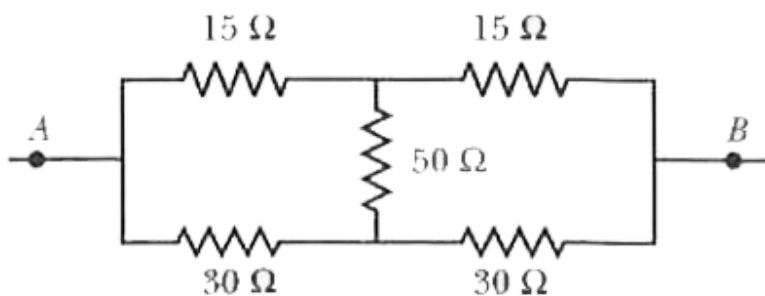5. In the adjoining circuit, find the branches in which the current is the same. Hence, redraw the circuit so that we can find the equivalent resistance of the circuit by simple series parallel



analysis.

[Watch Video Solution](#)



6. A galvanometer has a coil of resistance  $100\Omega$  showing a full-scale deflection at  $50\mu A$ . What resistance should be added to use it as (a) a voltmeter of range 50V and (b) an ammeter of range 10mA?

 [Watch Video Solution](#)

7. The table gives four sets of values for the circuit elements in Fig 27.33. Rank the sets according to (a) the initial current (as the switch is closed on a) and (b) the time required for the current to decrease to half its initial value, greatest first.

|                         | <b>1</b> | <b>2</b> | <b>3</b> | <b>4</b> |
|-------------------------|----------|----------|----------|----------|
| $\mathcal{E}(\text{V})$ | 12       | 12       | 10       | 10       |
| $R(\Omega)$             | 2        | 3        | 10       | 5        |
| $C(\mu\text{F})$        | 3        | 2        | 0.5      | 2        |

 [View Text Solution](#)


## Problems

1. An isolated charged capacitor may gradually discharge as charge leaks from one plate to the other through the intermediate material, as if it were discharging through an external resistor. (a) What is the resistance of such an external resistor if a  $2.00\mu F$  capacitor's potential difference decreases to 60.0% of its initial value of 50.0 V in 2.40 d? (b) What is the corresponding loss of potential energy in that time interval? (c) At the end of that interval, at what rate is the capacitor losing potential energy?

[View Text Solution](#)

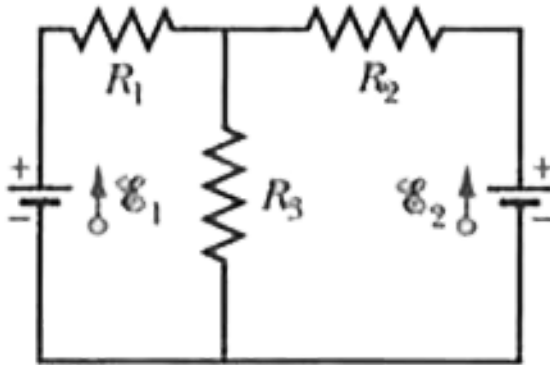2. In Fig. 27-37, the ideal batteries have emfs  $\varepsilon_1 = 12.0V$  and  $\varepsilon_2 = 0.500\varepsilon_1$  and the resistances are each

$4.00\Omega$ . What is the current in (a) resistance 2 and (b) resistance 3?




[Watch Video Solution](#)

3. In Fig 27.37,  $\mathcal{E}_1 = 1.00V$ ,  $\mathcal{E}_2 = 3.00V$ ,  $R_1 = 4.00\Omega$ ,  $R_2 = 2.00\Omega$ ,  $R_3 = 5.00\Omega$ , both batteries are ideal. What is the latest which energy is dissipated in (a)  $R_1$ , (b)  $R_2$  and (c)  $R_3$ ? What is the power of (d) battery 1 and (e) battery 2? Is energy being absorbed or provided in (f) battery 1 and (g) battery 2?

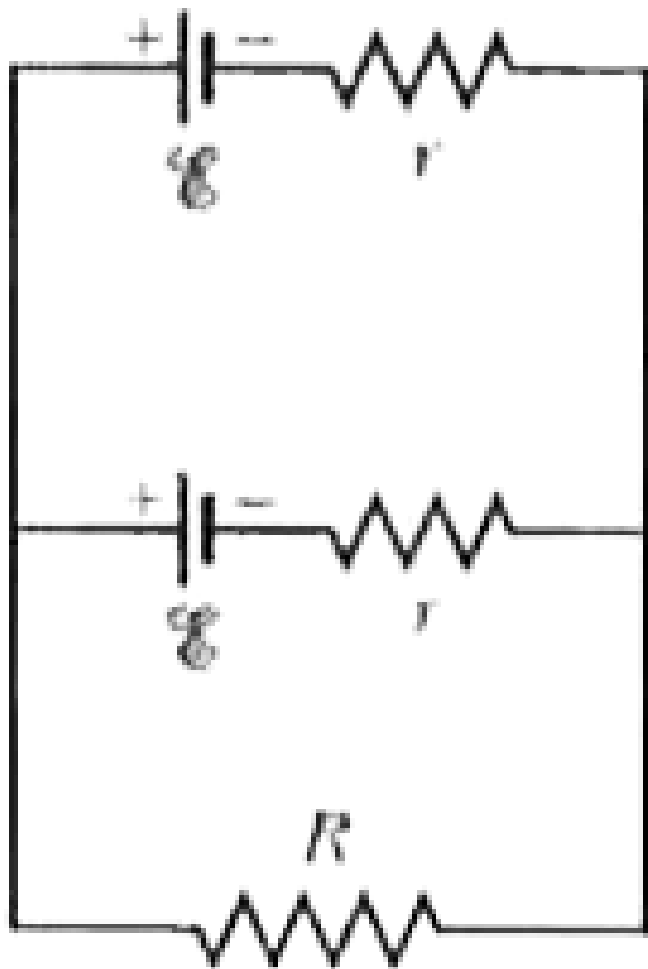
4. In Fig. 27-38, two batteries with an emf  $\varepsilon = 12.0V$  and an internal resistance  $r=0.500 \Omega$  are connected in parallel across a resistance  $R$ . (a) For what value of  $R$  is the dissipation rate in the resistor a maximum? (b) What is that maximum? and (c) what is the total dissipation rate in the batteries? In terms of  $r$ , what are (d) the effective  $R$  (internal) resistance of the two-battery system and (e) the resistance  $R$  that is required to maximize the

dissipation rate? This is a general result.



[View Text Solution](#)

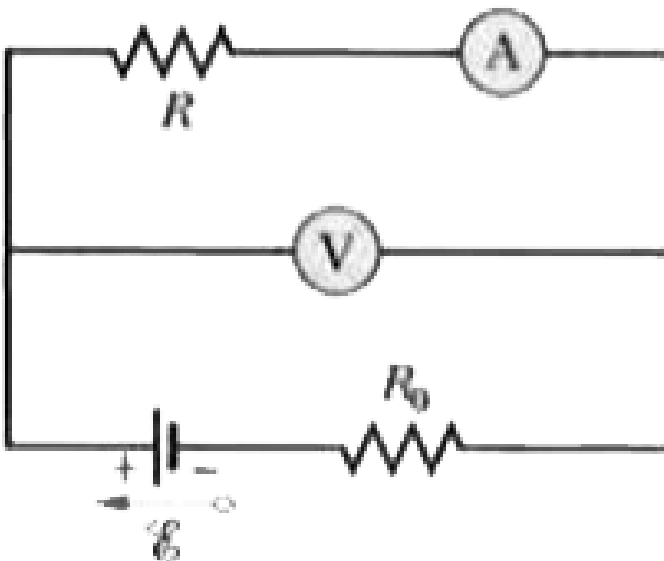5. In Fig. 27-39, a voltmeter of resistance  $R_v = 300\Omega$  and ammeter of resistance  $R_A = 3.00\Omega$  are being used to measure a resistance  $R$  in a circuit that also contains a resistance  $R_0 = 100\Omega$  and an ideal battery with an emf of  $\mathcal{E} = 18.0V$ . Resistance  $R$  is given by  $R = V/i$ , where  $V$  is the potential across  $R$  and  $i$  is the ammeter reading. The voltmeter reading is  $V'$ , which is  $V$  plus the potential difference across the ammeter. Thus, the ratio of the two meter readings is not  $R$  but only an apparent resistance  $R' = V'/i$ . If  $R = 85.0\Omega$  what are (a) the ammeter reading,




(b) the voltmeter reading, and (c)  $R'$ ? (a) If  $R_A$  is decreased, does

the difference between  $R'$  and  $R$  increase, decrease, or remain the same?

[View Text Solution](#)

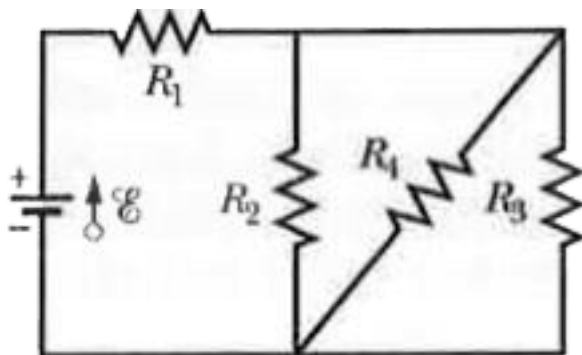6. In Fig. 27-40,  $R_1 = 100\Omega$ ,  $R_2 = R_3 = 50.00\Omega$ ,  $R_4 = 75.0\Omega$ , and the ideal battery has emf  $\mathcal{E} = 12.0V$ . (a) What is the equivalent resistance? What is  $i$  in (b) resistance 1, (c) resistance 2, (d) resistance 3, and (e) resistance 4?



[View Text Solution](#)


7. In Fig. 27-40, the resistors have the values  $R_1 = 700\Omega$ ,  $R_2 = 12.0\Omega$ , and  $R_3 = 4.00\Omega$  and the ideal battery's emf is 22.0 V. For what value of  $R_4$  Will the rate at which the battery transfers energy to the resistors equal (a) 60.0 W, (b) the maximum possible rate  $P_{\max}$  and (c) the minimum possible rate  $P_{\min}$ ? What are (d)  $P_{\max}$  and (e)  $P_{\min}$ ?

 [View Text Solution](#)

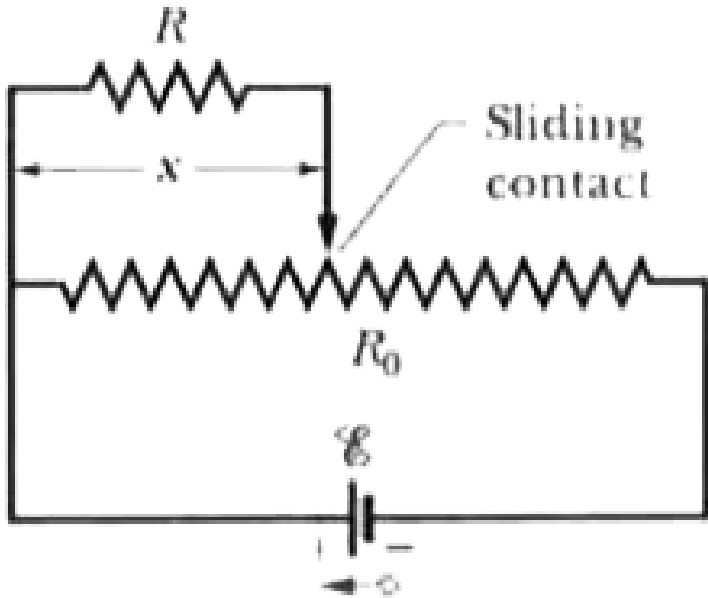8. Figure 27-41 shows a battery connected across a uniform resistor  $R_0$ . A sliding contact can move across the resistor from  $x=0$  at the left  $x= 10$  cm at the right. Moving the contact changes how much resistance is to the left of the contact and how much is to the right. Find the rate at which energy is dissipated resistor R as a function of  $x$ . Plot the function for




$$\varepsilon_0 = 50V, R = 2000\Omega \text{ and } R_0 = 100\Omega$$



[View Text Solution](#)

9. In Fig. 27-42, the resistances are  $R_1 = 3.00\Omega$ ,  $R_2 = 700\Omega$ . and the battery is ideal. What value of  $R_3$  maximizes the dissipation

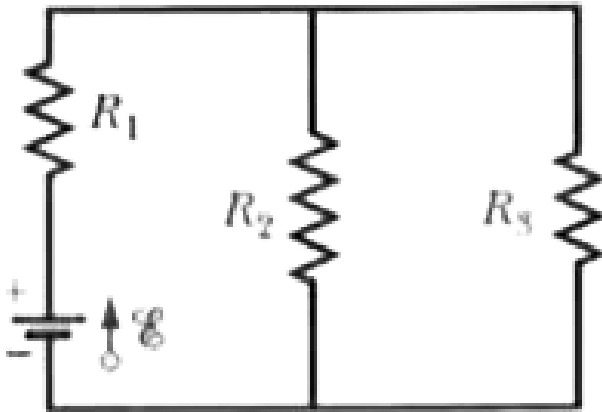[View Text Solution](#)


10. A capacitor with an initial potential difference of 80.0 V is discharged through a resistor when a switch between them is closed at  $t=0$ . At  $t= 10.0s$ , the potential difference across the capacitor is 1.00V (a) What is time constant of the circuit? (b) What is the potential difference across the capacitor

[View Text Solution](#)

11. In Fig. 27-43, the current in resistance 6 is  $i_6 = 2.80\text{A}$  the resistances are

$$R_1 = R_2 = R_3 = 2.00\Omega, R_4 = 16.0\Omega, R_5 = 8.00\Omega \text{ and } R_6 = 4.00\Omega$$

What is the emf of the ideal battery?

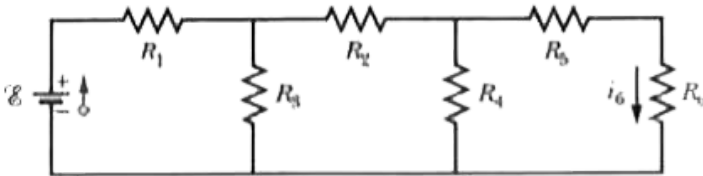


[Watch Video Solution](#)

12. In Fig. 27-44,

$$\varepsilon_1 = 8.00\text{V}, \varepsilon_2 = 12.0\text{V}, R_1 = 100\Omega, R_2 = 200\Omega, R_3 = 300\Omega.$$

One point of the circuit is grounded ( $V = 0$ ). What are the (a) size and (b) direction (up or down) of the current through resistance 1, the (c) size and (d) direction (left or right) of the current through resistance 2, and the (e) size and (f) direction of the current

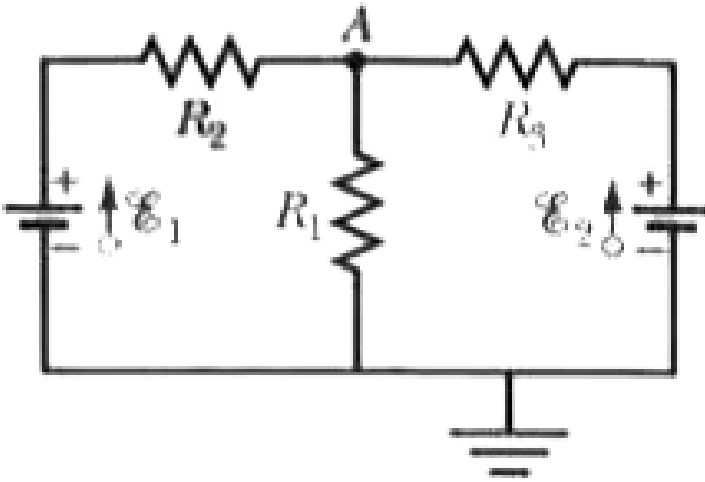
through resistance 3? (g) What is the electric potential at point A?



[View Text Solution](#)

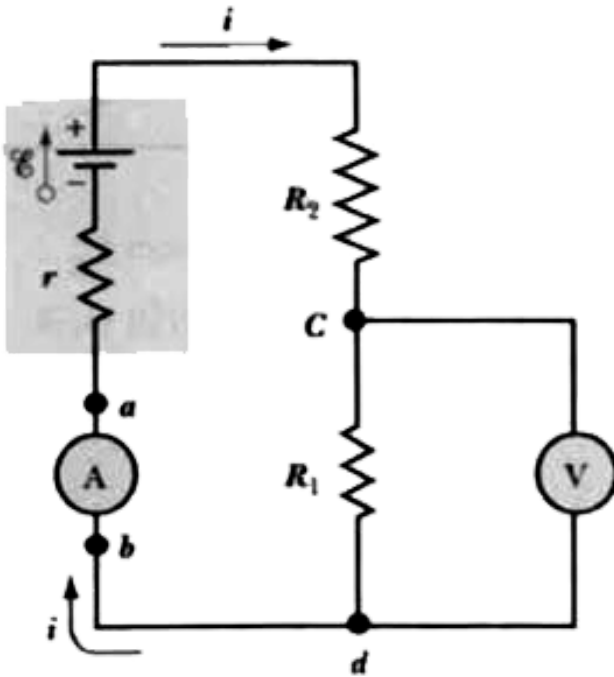13. In Fig. 27-45, assume that  $\mathcal{E} = 3.0\text{V}$ ,  $r = 100\Omega$ ,  $R_1 = 250\Omega$  and  $R_2 = 300\Omega$ . If the voltmeter resistance  $R_V$  is  $5.0\text{k}\Omega$ , what percent error does it introduce into the measurement of the potential difference across


$R_1$ ?. Ignore the presence of the ammeter.



[View Text Solution](#)

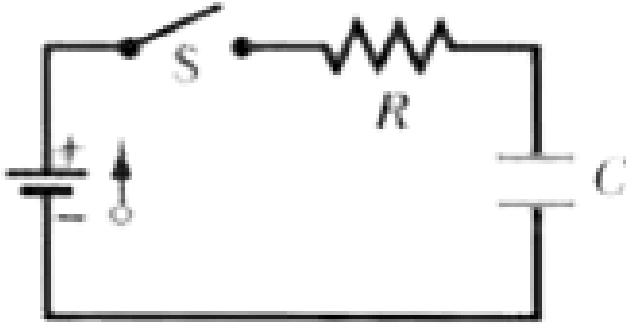14. Switch S in Fig. 27-46 is closed at time  $t = 0$ , to begin charging an initially uncharged capacitor of capacitance  $C = 49.0 \mu\text{F}$  through a resistor of resistance  $R = 32.0 \Omega$ . At what time is the

potential across the capacitor equal to that across the resistor?



[View Text Solution](#)


15. In the circuit shown in Fig. 27-47, there is a cube of resistances which are all having the same resistance of  $R$ . Find the equivalent resistance of the network between diagonally opposite points as

shown

in

the


figure.

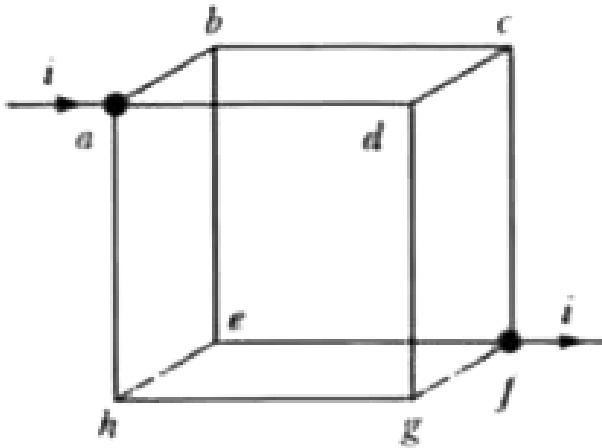

[View Text Solution](#)


16. Find the equivalent resistance of the network as shown in Fig

27.48 between points a and b

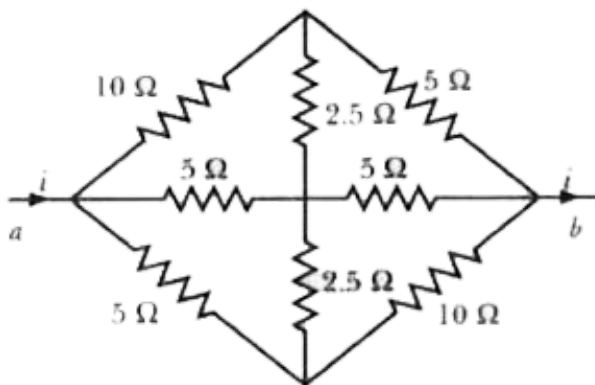

[View Text Solution](#)

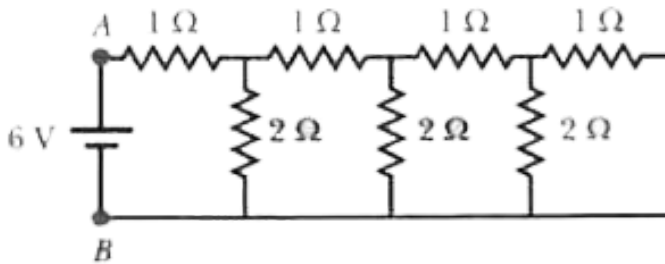17. An infinite ladder is constructed with  $1\Omega$  and  $2\Omega$  resistors as shown in Fig 27-49. Find the effective resistance between the points A and B.




[Watch Video Solution](#)

18. In Fig 27-50,  $\varepsilon = 24.0V$ ,  $R_1 = 2000\Omega$ ,  $R_2 = 3000\Omega$  and  $R_3 = 4000\Omega$ . What are the potential differences (a)  $V_A - V_B$  (b)  $V_B - V_C$  (c)



$V_C - V_D$  and (d)  $V_A - V_C$ ?

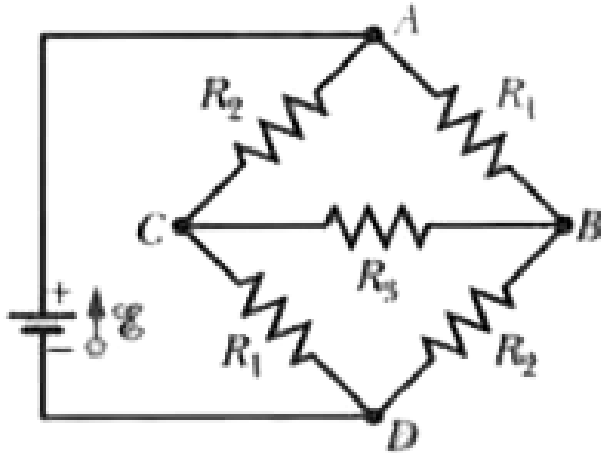

[View Text Solution](#)

19. In Fig. 27-51, battery 1 has emf  $\mathcal{E}_1 = 12.0V$  and internal resistance  $r_1 = 0.025\Omega$  and battery 2 has  $emf_2 = 12.0V$  and internal resistance  $r_2 = 0.012\Omega$ . The batteries are connected in series with an external resistance  $R$ . (a) What  $R$  value makes the terminal-to-terminal potential difference of one of the batteries

zero?


(b)

Which

battery

is

that?

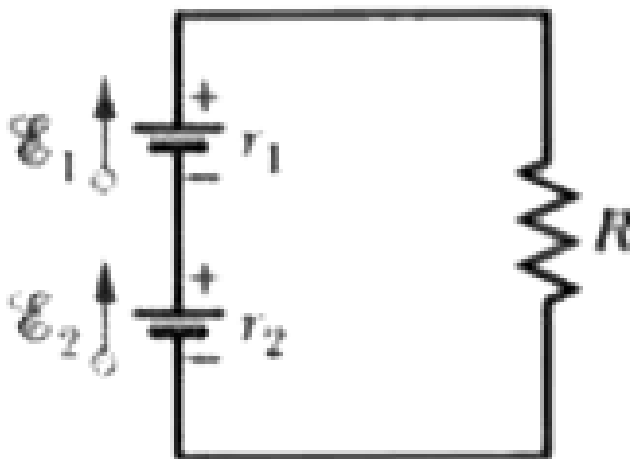


[Watch Video Solution](#)

20. A capacitor with initial charge  $q_0$ , is discharged through a resistor. What multiple of the time constant  $\tau$  gives the time the capacitor takes to lose (a) the first 25% of its charge and (b) 50% of its charge?

[View Text Solution](#)

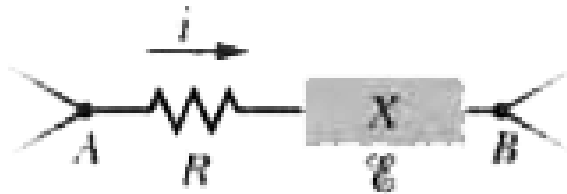21. In Fig 27-52, circuit section AB absorbs energy at a rate of 50W when current  $i=2.0\text{A}$  through it is in the indicated direction. Resistance  $R = 2.0\Omega$ , (a) What is the potential difference between A and B? Emf device X lacks internal resistance. (b) What is its emf? (c) is pont B connected the positive terminal of X or to the negative negative terminat?




[View Text Solution](#)

22. Sixteen copper wires of length  $l$  and diameter  $d$  are connected in parallel to form a single composite conductor of resistance  $R$ . What must the diameter  $D$  of a single copper wire of length  $l$  be if it is to have the same resistance?

[View Text Solution](#)

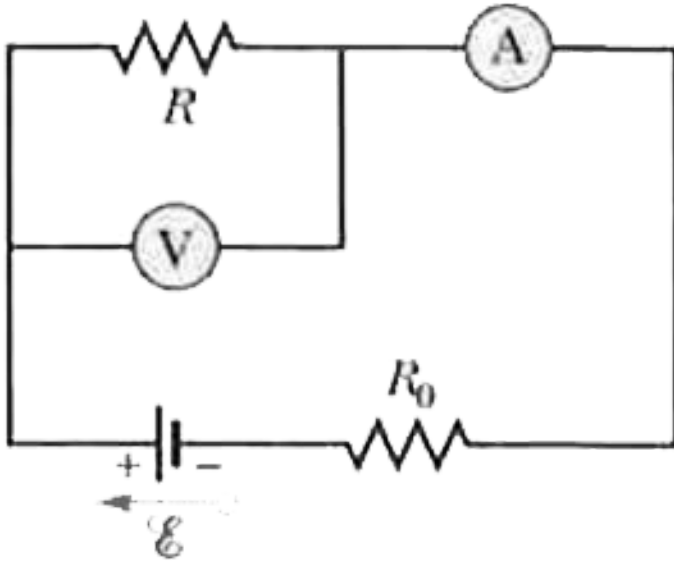**23.** In Fig 27-53, a voltmeter of resistance  $R_v = 300\Omega$  and an ammeter of resistance  $R_A = 3.00\Omega$  are being used to measure a resistance  $R$  in a circuit that also contains a resistance  $R_0 = 100\Omega$  and an ideal battery of emf  $\varepsilon = 28.5V$ . Resistance  $R$  is given by  $R = V/i$  where  $V$  is the voltmeter reading and  $i$  is the current in resistance  $R$ . However, the ammeter reading is not  $i$  but rather  $i'$ , which is  $i$  plus the current through the voltmeter. Thus, the ratio of the two meter readings is not  $R$  but only an apparent resistance  $R' = V/i'$ . If  $R = 85.0\Omega$  what are (a) the ammeter reading, (b) the voltmeter reading, and (c)  $R'$  (d) If  $R_v$  is increased does the


difference between  $R'$  and  $R$  increase, decrease or on the same?



[View Text Solution](#)

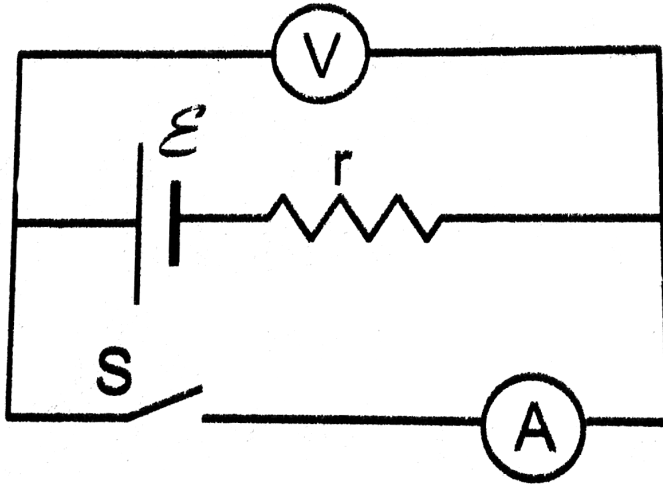24. Shown an arrangement to measure the emf ( $\mathcal{E}$ ) and internal resistance  $r$  of a battery. The voltmeter has a very high resistance and the ammeter also has some resistance. The voltmeter reads 1.52 V when the switch  $S$  is open. When the switch is closed the voltmeter reading drops to 1.45 V and the ammeter reads 1.0 A. Find

the emf and the internal resistance of the battery.



[▶ Watch Video Solution](#)

25. A voltmeter consists of a  $25\Omega$  coil connected in series with a  $575\Omega$  resistor. The coil takes  $10\text{ mA}$  for full-scale deflection. What maximum potential difference can be measured on this voltmeter?

[▶ Watch Video Solution](#)

**26.** An ammeter is to be constructed which can read currents up to 2.0 A. If the coil has a resistance of  $25\Omega$  and takes 1 mA for full-scale deflection, what should be the resistance of the shunt used?

 [Watch Video Solution](#)

**27.** A voltmeter coil has resistance  $50.0\Omega$  and a resistor of  $1.15k\Omega$  is connected in series. It can read potential differences upto 12 V. If this same coil is used to construct an ammeter which can measure currents up to 2.0 A, what should be the resistance of the shunt used?

 [Watch Video Solution](#)

**28.** A  $3.00M\Omega$  resistor and a  $1.00\mu F$  capacitor are connected in series with an ideal battery of emf  $\varepsilon = 4.00V$ . At 6.00 s after the

connection is made, what is the rate at which (a) the charge of the capacitor is increasing, (b) energy is being stored in the capacitor, (c) thermal energy is appearing in the resistor, and (d) energy is being delivered by the battery?

 [View Text Solution](#)


**29.** In an RC series circuit, emf  $\varepsilon = 12.0V$ , resistance  $R = 1.40M\Omega$  and capacitance  $C = 2.70\mu F$ . (a) Calculate the time constant. (b) Find the maximum charge that will appear on the capacitor during charging. (c) How long does it take for the charge to build up to  $16.0\mu C$ ?

 [View Text Solution](#)

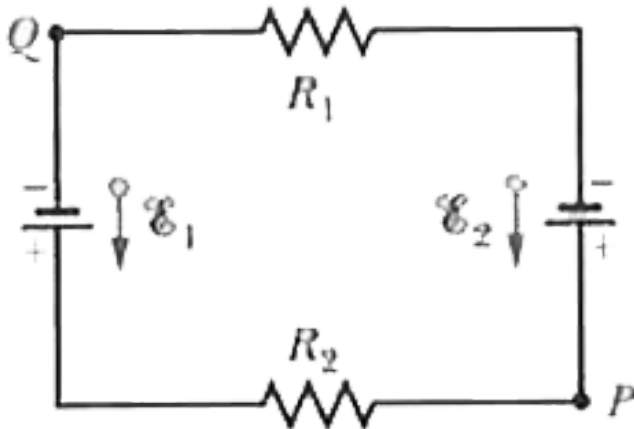**30.** In Fig 27-56, the ideal batteries have emf  $\varepsilon_1 = 200V$  and  $\varepsilon_2 = 50V$  and the resistances are



$R_1 = 3.0\Omega$  and  $R_2 = 2.0\Omega$ . If the potential at P is 100 V, what is




at at Q?

[▶ Watch Video Solution](#)

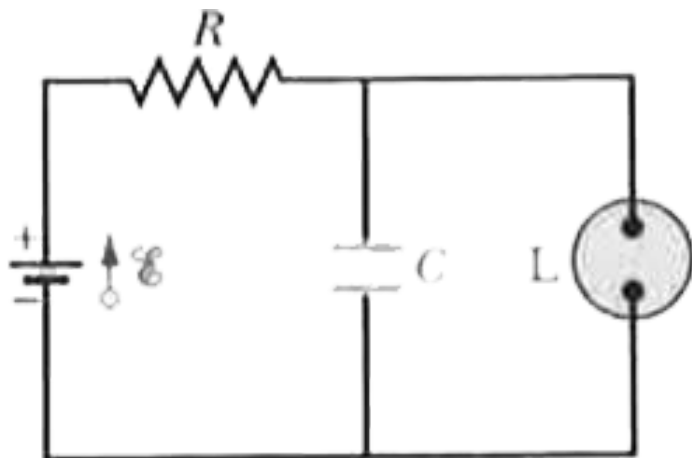**31.** Figure 27-56 shows the circuit of a flashing lamp, like those attached to barrels at highway construction sites. The fluorescent lamp L (of negligible capacitance) is connected in parallel, across the capacitor C of an RC circuit. There is a current through the lamp only when its potential difference reaches the breakdown voltage  $V_L$ , then the capacitor discharges completely through the lamp and the lamp flashes briefly. For a lamp with

breakdown voltage  $V_L = 75.0\text{V}$ , wired to a  $95.0\text{V}$  ideal battery and a  $0.150\mu\text{F}$  capacitor, what resistance  $R$  is needed for two flashes per second?



[View Text Solution](#)

**32.** Six  $18.0\Omega$  resistors are connected in parallel across a  $12.0\text{V}$  ideal battery. What is the current through the battery?

[Watch Video Solution](#)


**33.** In Fig. 27-9, what is the potential difference  $V_d - V_c$  between points  $d$  and  $c$  if  $\varepsilon_1 = 4.0V$ ,  $\varepsilon_2 = 1.0V$ ,  $R_1 = R_2 = 10\Omega$ , and  $R_3 = 8.0\Omega$ , and the battery is ideal?



[View Text Solution](#)

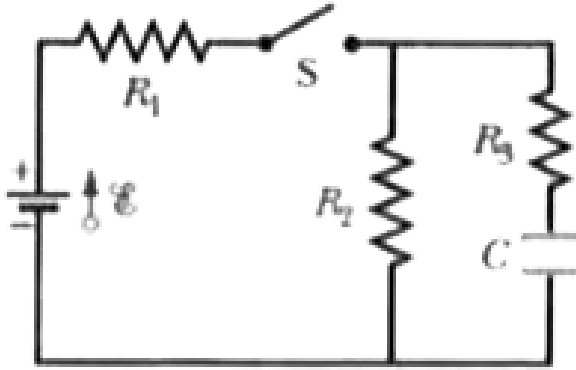**34.** In the circuit of Fig 27-57  $\varepsilon = 1.2kV$ ,  $C = 6.5\mu F$ ,  $R_1 = R_2 = R_3 = 0.73M\Omega$ . With  $C$  completely uncharged switch  $S$  is suddenly closed (at  $t=0$ ). At  $t=0$ , what are (a) current  $i_1$  in resistor 1, (b) current  $i_2$  in resistor 2, and (c) current  $i_3$  in resistor 3? At  $t = \infty$  (that is after many time constants). what are (d)  $i_1$ , (e)  $i_2$  and (f)  $i_3$ ? What is the potential difference  $V_2$  across resistor 2 at (g)  $t=0$  and (h)  $t = \infty$ ?

Sketch  $V_2$  versus  $t$  between these two extreme times.



[View Text Solution](#)


**35.** When resistors 1 and 2 are connected in series, the equivalent resistance is  $20.0\Omega$ . When they are connected in parallel, the equivalent resistance is  $3.75\Omega$ . What are (a) the smaller resistance and (b) the larger resistance of these two resistors?

[Watch Video Solution](#)

**36.** A car battery with a 12 V emf and an internal resistance of  $0.030\Omega$  is being charged with a current of 40 A. What are (a) the potential difference  $V$  across the terminals, (b) the rate  $P_r$  of energy dissipation inside the battery, and (c) the rate  $P_{\text{emf}}$  of energy conversion to chemical form? When the battery is used to supply 40 A to the starter motor, what are (d)  $V$  and (e)  $P$ ?


 [View Text Solution](#)

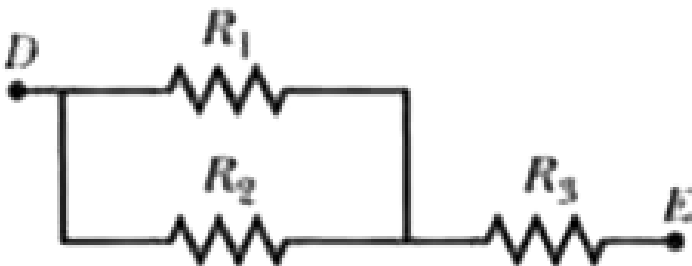**37.** In Fig. 27-58,  $R_1 = R_2$ ,  $4.00\Omega$  and  $R_3 = 1.50\Omega$ . Find the equivalent resistance between points D and E. (Hint : Imagine that a battery is connected across those points).



 [Watch Video Solution](#)

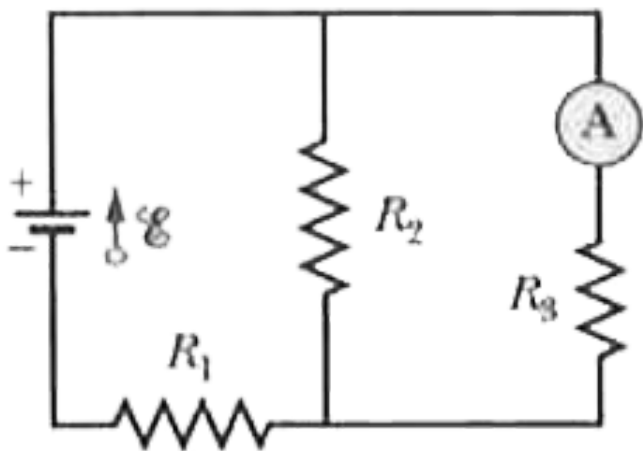**38.** In Fig 27-59, what current does the ammeter read if  $\varepsilon = 5.0V$  (ideal battery),  $R_1 = 2.0\Omega$ ,  $R_2 = 9.0\Omega$  and  $R_3 = 6.0\Omega$ ? (b) The ammeter and battery are now interchanged. Show that the ammeter reading is unchanged.



[Watch Video Solution](#)

**39.** A total resistance of  $5.00\Omega$  is to be produced by connecting an unknown resistance. a) What must be the value of the unknown

resistance and (b) should it be connected in series or in parallel (c)

What is the total resistance if the unknown resistance is connected the other way?




[View Text Solution](#)

**40.** A 5.7 A current is set up in a circuit for 15.0 min by a rechargeable battery with a 6.0 V emf. By how much is the chemical energy of the battery reduced?



[Watch Video Solution](#)

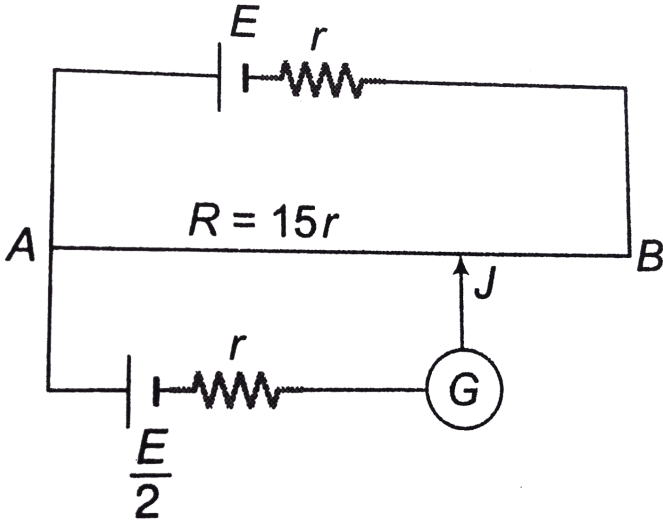41. The potentiometer wire  $AB$  is 600 cm long.



- a. At what distance from  $A$  should the jockey  $J$  touch the wire to get zero deflection in the galvanometer.
- b. If the jockey touches the wire at a distance  $560\text{cm}$  from  $A$ , what will be the current through the galvanometer.


[▶ Watch Video Solution](#)

42. A 6 volt battery of negligible internal resistance is connected across a uniform wire  $AB$  of length  $100\text{cm}$ . The positive terminal of



another battery of emf  $4\text{V}$  and internal resistance  $1\Omega$  is joined to the point A as shown in figure. Take the potential at B to be zero.

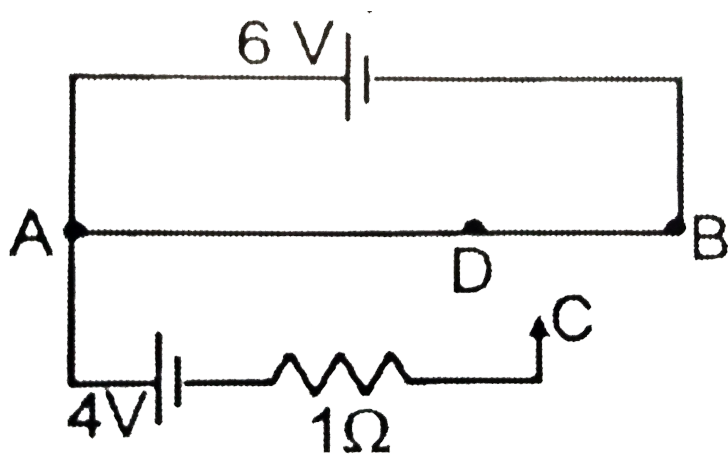
- (a) What are the potentials at the points A and C ? (b) At which D of the wire AB, the potential is equal to the potential at C. (c) If the point C and D are connected by a wire. What will be the current through is ? (d) If the  $4\text{V}$  battery is replaced by  $7.5\text{V}$  battery, what would be the answers of parts (a) and (b) ?



[Watch Video Solution](#)

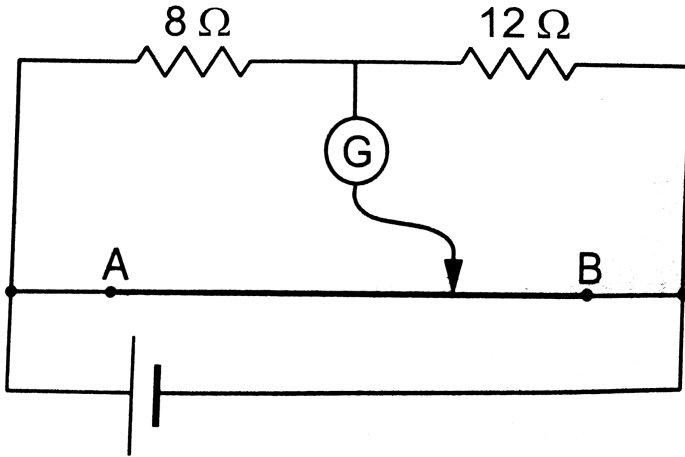- 43.** The potentiometer wire AB shown in figure is  $40\text{ cm}$  long. Where should the free end of the galvanometer be connected on


AB so that the galvanometer may show zero deflection?



[▶ Watch Video Solution](#)

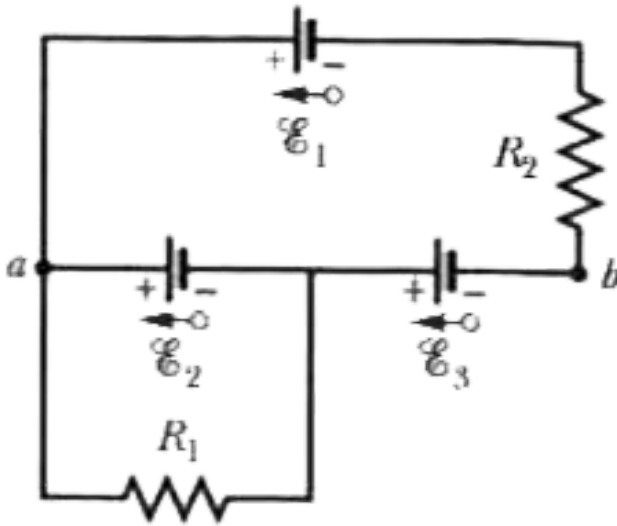**44.** In Fig. 27-63,  $R_1 = 100\ \Omega$ ,  $R_2 = 50\ \Omega$ , and the ideal batteries have emfs,  $\varepsilon_1 = 6.0\text{V}$ ,  $\varepsilon_2 = 10\text{V}$ , and  $\varepsilon_3 = 4.0\text{V}$ . Find (a) the current in resistor 1, (b) the current in resistor 2, and (c) the


potential difference between points  $a$  and  $b$ .



[Watch Video Solution](#)

45. A conductor of length  $l$  has a non-uniform cross-section. The radius of cross-section varies linearly from  $a$  to  $b$ . The resistivity of the material is  $\rho$ . Find the resistance of the conductor across its


ends.

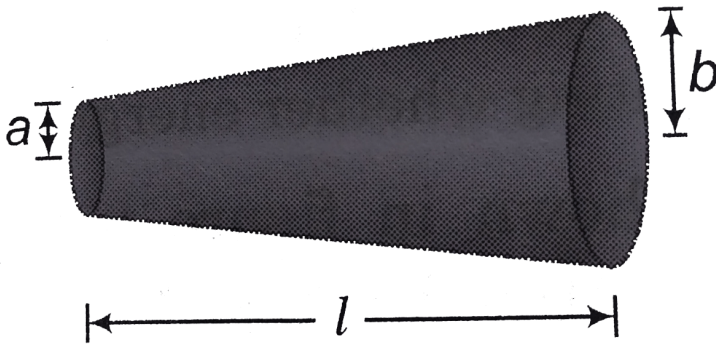

[▶ Watch Video Solution](#)

### Practice Questions Single Correct Choice Type

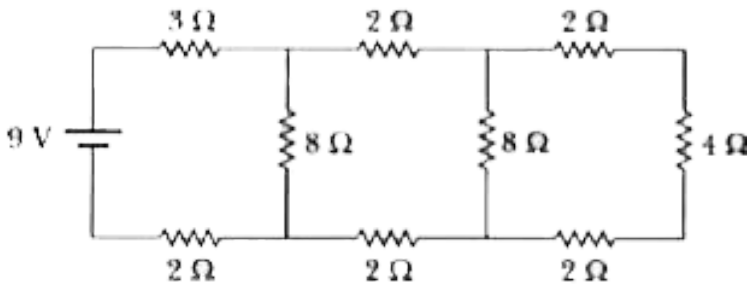1. In the circuit shown in the figure, the current through



A. The  $3\ \Omega$  resistor is  $0.50\text{A}$

B. The  $3\Omega$  resistor is 0.25A

C. The  $4\Omega$  resistor is 0.50A


D. The  $4\Omega$  resistor is 0.25A

**Answer: D**



[Watch Video Solution](#)

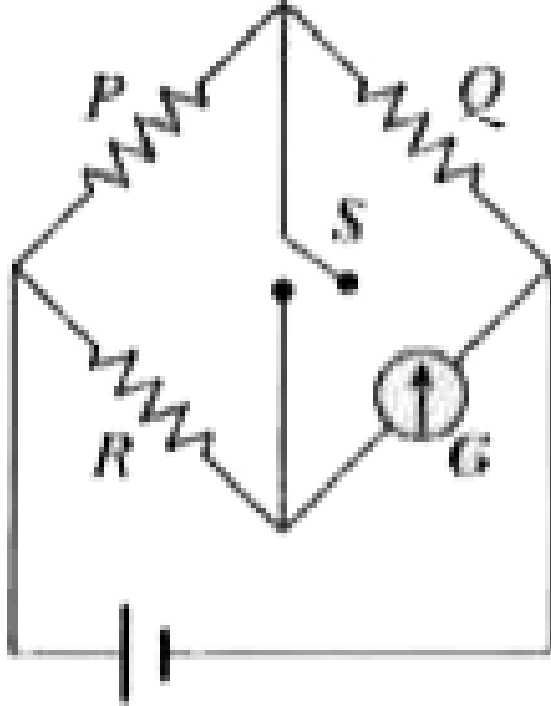2. In the circuit shown  $P \neq R$  the reading of galvanometer is same switch S open or closed. Then



A.  $I_R = I_G$

B.  $I_P = I_G$

C.  $I_Q = I_G$


D.  $I_Q = I_S$

**Answer: A**



**Watch Video Solution**

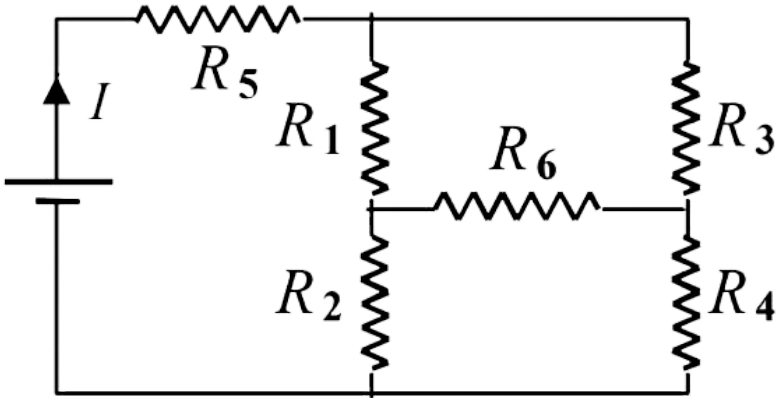3. In the given circuit, it is observed that the current  $I$  is independent of the value of the resistance  $R_6$ . Then the resistance values must satisfy



A.  $R_1 R_2 R_5 = R_3 R_4 R_6$

B.  $\frac{1}{R_5} + \frac{1}{R_6} = \frac{1}{R_1 + R_2} + \frac{1}{R_3 + R_4}$




C.  $R_1 R_4 = R_2 R_3$

D.  $R_1 R_3 = R_2 R_4 = R_5 R_6$

**Answer: C**



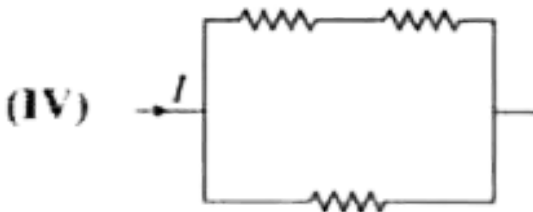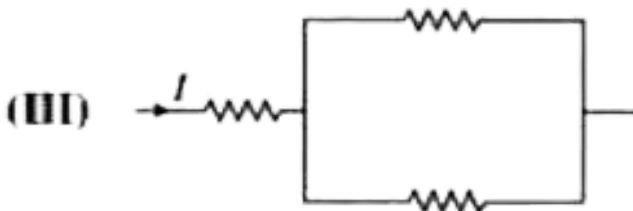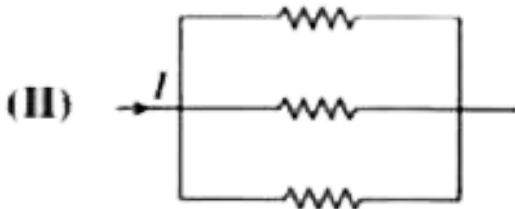4. The three resistances of equal values are arranged in the different combination shown in the figure. Arrange them in the increasing order of dissipation of power.



A.  $II < IV < I < III$



B.  $II < IV < III < I$



C.  $IV < II < I < III$

D.  $IV < I < II < III$

Answer: B

 Watch Video Solution

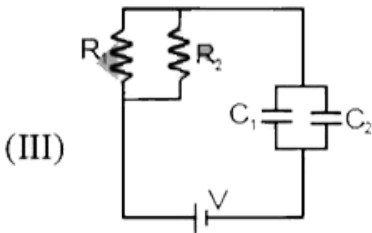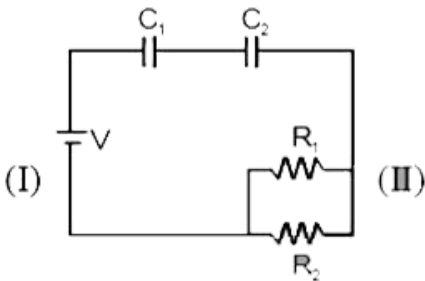5. Given :  $R_1 = 1\text{ohm}$ ,  $R_2 = 2\text{ohm}$ ,  $C_1 = 2\mu\text{F}$ ,  $C_2 = 4\mu\text{F}$  The time constants (in  $\mu\text{S}$ ) for the circuits I, II, III are respectively



A. 18, 8/9, 4

B. 18, 4, 8/9

C. 4, 8/9, 18

D. 8/9, 18, 4

**Answer: D**

 [Watch Video Solution](#)

6. Somewhere in a circuit is a resistor. A constant current is flowing in the direction as indicated in the following figure. In going from

A to B, we measure  $\int_A^B \vec{E} \cdot d\vec{l}$  What do we find?



A. A positive value

B. A negative value

C. Zero

D. We do not have enough information to answer

**Answer: A**



**Watch Video Solution**

7. If we go from A to B through the wire to the resistor, or choose a random routing through free space (thus not through the resistor itself), starting at A and ending at B. Which of the following statement is correct?

A. There is no difference in both cases

B. There is a major difference due to path chosen

C. We cannot choose a random routine path

D. None of these

**Answer: A**

 [Watch Video Solution](#)

8.  $10\text{C}$  of charge start from the negative terminal of a battery, flow through the battery and then leave the positive terminal through a wire, flow through a resistor and then return to the starting point on this circuit. In this complete process, the  $10\text{C}$ ....

- A. Have no net change in potential energy
- B. Receive heat energy from the resistor
- C. Have a net loss of potential energy
- D. Do positive work on the battery


**Answer: A**

9. A battery of emf  $E$  has an internal resistance  $r$ . A variable resistance  $R$  is connected to the terminals of the battery. A current  $i$  is drawn from the battery.  $V$  is the terminal potential difference. If  $R$  alone is gradually reduced to zero, which of the following best describes  $i$  and  $V$ ?

- A.  $i$  decreases to zero,  $V$  approaches  $\varepsilon$
- B.  $i$  approaches an infinite value,  $V$  decreases to zero
- C.  $i$  approaches  $\varepsilon/r$ ,  $V$  approaches  $\varepsilon$
- D.  $i$  approaches  $\varepsilon/r$ ,  $V$  approaches zero

**Answer: D**

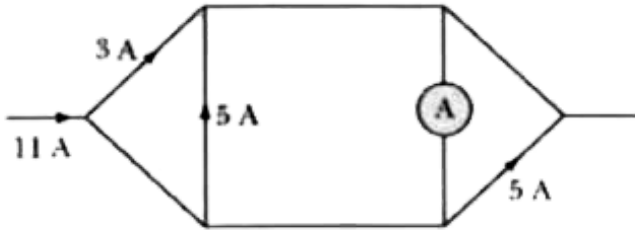10. The given figure shows a network of wires carrying various currents. What is the current through A?




- A. 1A
- B. 2A
- C. 6A
- D. 8A

**Answer: B**

 [Watch Video Solution](#)

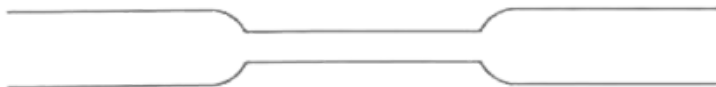11. A current-carrying wire got pulled, stretching it and making it thinner in its middle. The cross-section of that wire is shown in the following figure. Which of the following statements about the current and the temperature of the wire is true?



- A. The current and temperature at the thin section of the wire is higher than at the thick section
- B. The current and temperature at the thick section of the wire is higher than at the thin section
- C. The current and temperature at the wire is the same everywhere
- D. The current in the wire is the same everywhere, but the temperature of the wire is higher in the thin section

**Answer: D**

 [Watch Video Solution](#)

**12.** Four unequal resistors are connected in parallel. Which one of the following statements is correct?

- A. The total resistance is less than the smallest resistor
- B. The total resistance is equal to the average of the individual resistances
- C. The total resistance is more than the largest resistor
- D. The total resistance is in between the smallest and largest resistor but not the average of the individual resistances

**Answer: A**

 [Watch Video Solution](#)




13. Three 100 W light bulbs are connected in series to a 220V power source. If two of the light bulbs are replaced by 60 W bulbs, the brightness of the remaining on w bulb is

- A. Brighter than it was before
- B. Dimer than it was before
- C. The same brightness as it was before
- D. will not illuminate

**Answer: A**

 [Watch Video Solution](#)

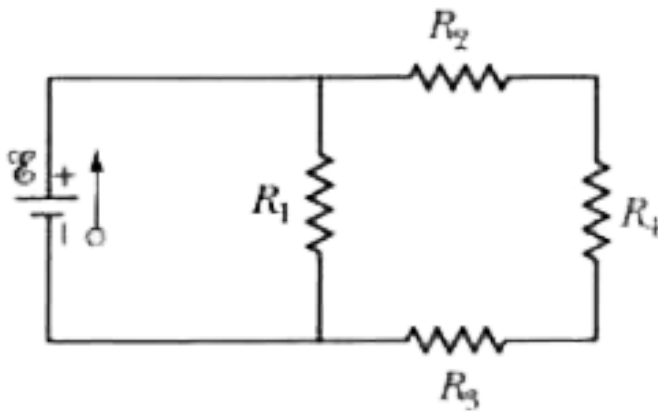14. An ideal battery is connected to a circuit of four resistors as shown in the following figure. If the resistance  $R_4$  is increased,



then


- A. The current through  $R_1$  decreases
- B. The potential difference across  $R_1$  increases
- C. The potential difference across  $R_4$  increases
- D. The potential difference across  $R_2$  decreases

**Answer: A**



[Watch Video Solution](#)

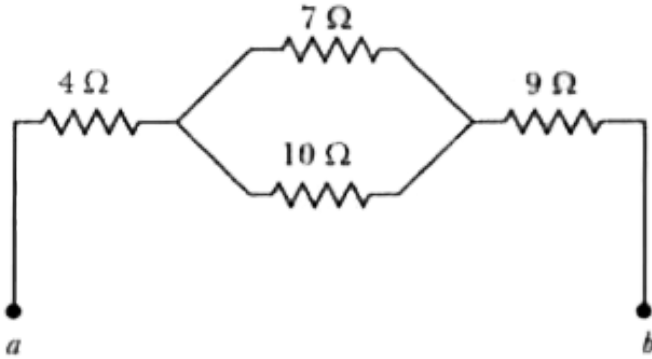15. If voltage  $V$  is applied across terminals  $a$  and  $b$  of the circuit shown in the following figure, which of the statements below is true? (Notation:  $i_4$  is current through  $4.00\Omega$  resistor,...)





- A.  $i_7 < i_{10} < i_9$
- B.  $i_4 = i_7 = i_9$
- C.  $i_4 > i_7 + i_{10} > i_9$
- D.  $i_{10} < i_7$

**Answer: D**

 [Watch Video Solution](#)

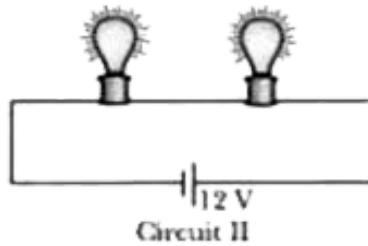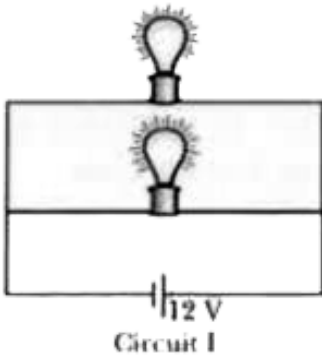16. If the four light bulbs in the following figure are identical which circuit gives out more light?




- A. I
- B. The two emit the same amount of light
- C. II
- D. None of these


**Answer: A**

 [Watch Video Solution](#)

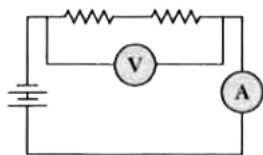
17. Which circuit diagram shows voltmeter V and ammeter A correctly positioned to measure the total potential difference of the circuit and the current through each resistor?




A.

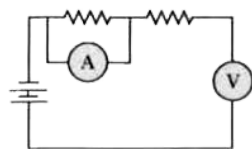

B.

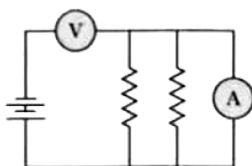

C.

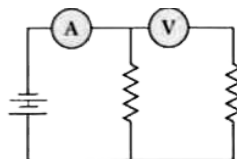

D.

**Answer: A**

 [Watch Video Solution](#)

18. When a capacitor is discharged through a resistor, which of the following is false?

- A. The current in the capacitor is equal to the current in the resistor
- B. The capacitor voltage decreases by half after a time equal to  $RC$
- C. The voltage across the capacitor is equal to the voltage across the resistor at any instant
- D. The current in the circuit takes an infinite time to reach zero

**Answer: D**



**Watch Video Solution**

19. Two identical resistors of magnitude  $R$  and two identical capacitors of magnitude  $C$  are used to form an RC circuit. In which case the time constant of that RC circuit is the highest?

- A. Two resistors and two capacitors connected in series with a power supply
- B. Two resistors and two capacitors connected in parallel with a power supply
- C. Two resistors connected in parallel, two capacitors connected in parallel, and those two combinations are connected in series with a power supply
- D. Two resistors connected in series, two capacitors connected in parallel, and those two combinations are connected in series with a power supply

**Answer: D**




**Watch Video Solution**

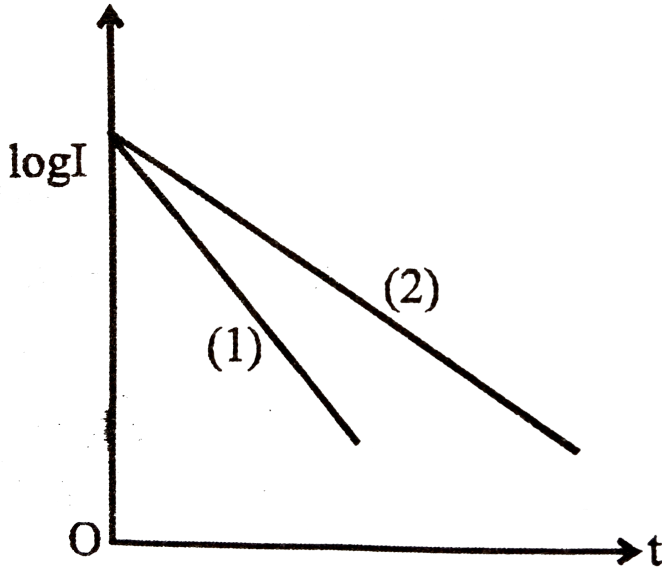**20.** A capacitor of capacity  $C$  is charged to a steady potential difference  $V$  and connected in series with an open key and a pure resistor 'R'. At time  $t = 0$ , the key is closed. If  $I =$  current at time  $t$ , a plot of  $\log I$  against 't' is as shown in (1) in the graph. Later one of the parameters i.e.  $V$ ,  $R$  or  $C$  is changed keeping the other two



constant, and graph (2) is recorded. then-




- A. C is reduced
- B. C is increased
- C. R is reduced
- D. R is increased

**Answer: B**

 [Watch Video Solution](#)

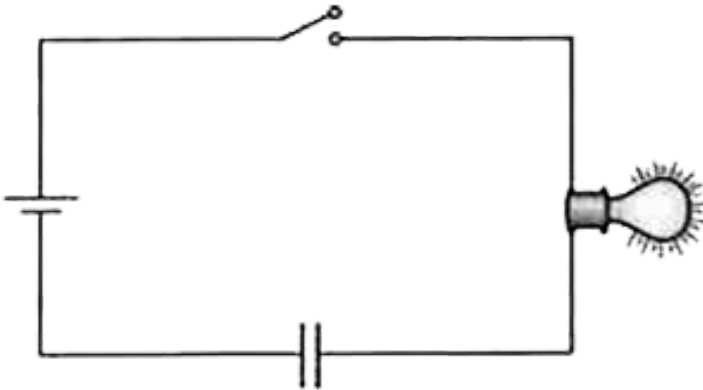21. When the switch is closed in the circuit as shown in the following figure, the light bulb become bright in an imperceptibly short-time interval, and then gradually goes out. We interpret this to mean that




- A. Electrons on the negative terminal of the battery reach a capacitor plate almost instantaneously
- B. Electrons from a capacitor plate travel to the positive terminal of the battery almost instantaneously
- C. The capacitor must already have had charge on its plates

D. The battery establishes an electric field in the circuit almost instantaneously

Answer: D

 Watch Video Solution

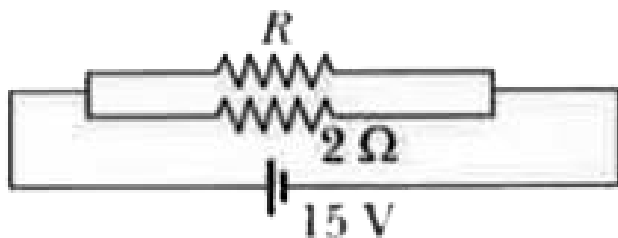22. If in the circuit, power dissipation is 150 W. then R is



A.  $2\Omega$

B.  $6\Omega$

C.  $5\Omega$

D.  $4\Omega$

**Answer: B**



**Watch Video Solution**

**23.** A wire when connected to 220 V mains supply has power dissipation  $P_1$ . Now the wire is cut into two equal pieces which are connected in parallel to the same supply. Power dissipation in this case is  $P_2$ . Then  $P_2 : P_1$  is

A. 1

B. 4

C. 2

D. 3

**Answer: B**



**Watch Video Solution**

24. The mass of product liberated on anode in an electrochemical cell depends on

(where  $t$  is the time period for which the current is passed.)

A.  $(It)^{1/2}$

B.  $It$

C.  $I/t$

D.  $I^2t$

**Answer: B**

 [Watch Video Solution](#)

25. The negative Zn pole of a Daniell cell, sending a constant current through a circuit, decreases in mass by 0.13 g in 30 minutes. If the electrochemical equivalent of Zn and Cu are 32.5

and 31.5 respectively, the increase in the mass of the positive. Cu pole in this time is

A. 0.180 g

B. 0.141 g

C. 0.126 g

D. 0.242 g

**Answer: C**



**Watch Video Solution**

**26.** An ammeter reads upto 1 ampere. Its internal resistance is 0.81 ohm. To increase the range to 10 A the value of the required shunt is

A.  $0.03\Omega$

B.  $0.3\Omega$

C.  $0.9\Omega$

D.  $0.09\Omega$

**Answer: D**



[Watch Video Solution](#)

27. The length of a given cylindrical wire is increased by 100%. Due to the consequent decrease in diameter the change in the resistance of the wire will be

A. 2

B. 1

C. 0.5

D. 3

**Answer: D**



**Watch Video Solution**

**28.** The thermo e.m.f. of a thermo- couple is  $25\mu V / ^\circ C$  at room temperature. A galvanometer of 40 ohm resistance, capable of detecting current as low as  $10^{-5}A$ , is connected with the thermo couple. The smallest temperature difference that can be detected by this system is

A.  $16^\circ C$

B.  $12^\circ C$

C.  $8^\circ C$

D.  $20^\circ C$

**Answer: A**



**Watch Video Solution**



29. The length of a wire of a potentiometer is 100 cm, and the emf of its stand and cell is  $E$  volt. It is employed to measure the emf of a battery whose internal resistance is  $0.5\Omega$ . If the balance point is obtained at  $l = 30$  cm from the positive end, the emf of the battery is

A.  $\frac{30E}{100.5}$

B.  $\frac{30E}{100 - 0.5}$

C.  $\frac{30(E - 0.5i)}{100}$  where  $i$  is the current in the potentiometer

wire

D.  $\frac{30E}{100}$

**Answer: D**



**Watch Video Solution**

30. The electrochemical equivalent of a metal is  $3.35109^{-7}$  kg per Coulomb. The mass of the metal liberated at the cathode when a 3A current is passed for 2 seconds will be

A.  $19.8 \times 10^{-7} kg$

B.  $9.9 \times 10^{-7} kg$

C.  $6.6 \times 10^{-7} kg$

D.  $1.1 \times 10^{-7} kg$

**Answer: A**



[Watch Video Solution](#)

31. The thermistors are usually made of

A. Metals with low temperature coefficient of resistivity

B. Metals with high temperature coefficient of resistivity

C. Metal oxides with high temperature coefficient of resistivity

D. Semiconducting materials having low temperature coefficient of resistivity

**Answer: C**



[Watch Video Solution](#)

**32.** If a given volume of water in a  $220V$  heater is boiled in 5 min , then how much time will it take for the same volume of water in a  $110V$  heater to be boiled?

A. 1000s

B. 1200s

C. 1100s

D. 1250s

**Answer: B**



[Watch Video Solution](#)

**33.** If two bulbs of wattage 25 and 100 respectively each rated at 220 volt are connected in series with the supply of 440 volt , then which bulbs will fuse

A. 100 W

B. 25 W

C. Both of them

D. None of them


**Answer: B**



[Watch Video Solution](#)

## Practice Questions More Than One Correct Choice Type

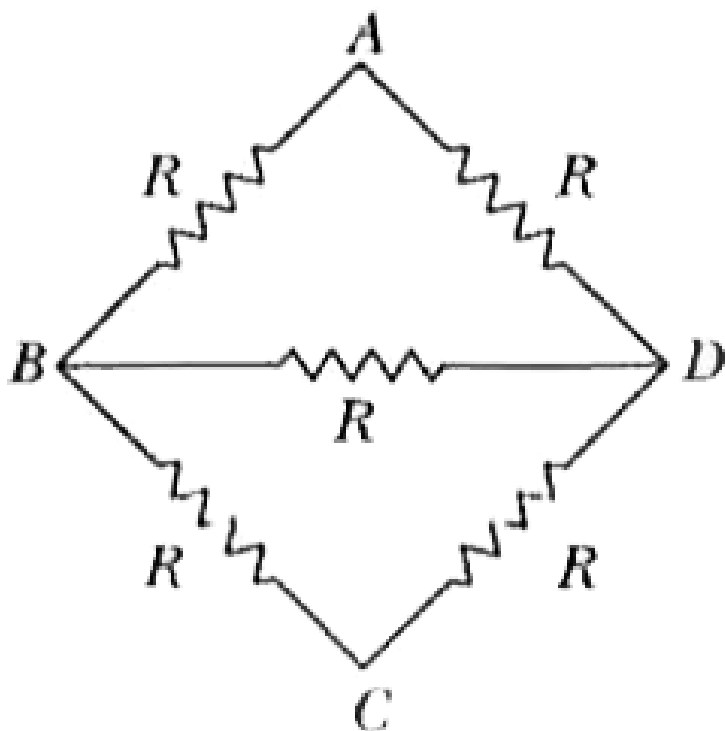1. Five equal resistances each of value  $R$  are connected in a form shown in the following figure. The equivalent resistance of the



network

A. Between points B and D is  $R/2$

B. Between points A and C is  $R$


C. Between points B and D is  $R$

D. Between points A and C is  $R/2$

**Answer: A:B**

 [Watch Video Solution](#)

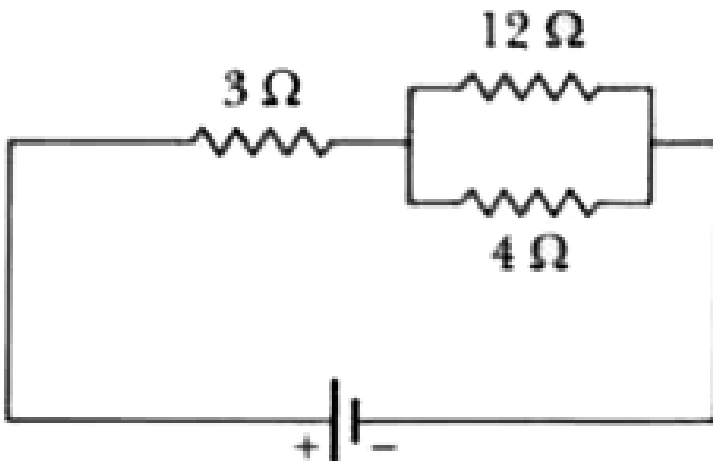2. For the circuit shown in the following figure.



- A. The heat dissipated in  $4\Omega$  resistance is more than that dissipated in  $12\Omega$  resistance
- B. Maximum heat is dissipated in  $3\Omega$  resistance
- C. The heat dissipated in  $12\Omega$  resistance is more than that dissipated in  $4\Omega$  resistance
- D. The power dissipated in  $3\Omega$  resistance is 18 W


**Answer: A::B**



[Watch Video Solution](#)

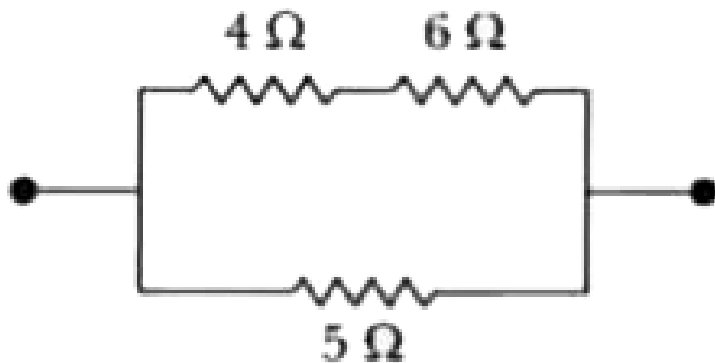3. In the circuit shown in the following figure, the heat product in the  $5\Omega$  resistance due to the current flowing it is 10 cal/s. The heat

generated in  $4\Omega$  resistance and  $6\Omega$  resistor is



- A. 1 cal/s
- B. 2 cal/s
- C. 3 cal/s
- D. 4 cal/s


**Answer: B::C**



[Watch Video Solution](#)



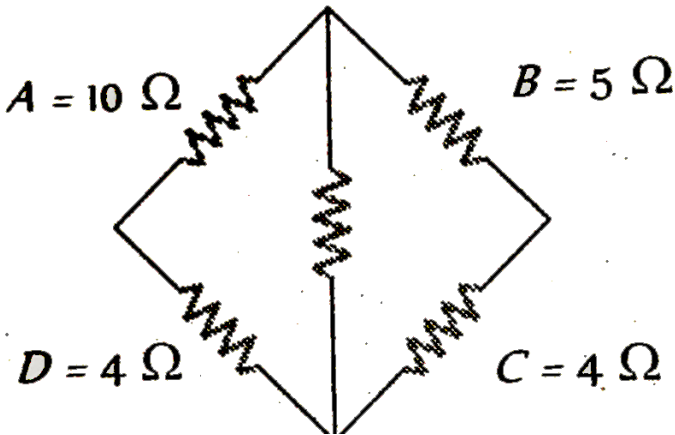4. In a typical Wheatstone network, the resistances in cyclic order are  $A = 10\Omega$ ,  $B = 5\Omega$ ,  $C = 4\Omega$ ,  $D = 4\Omega$  for the bridge to be balanced




- A.  $10\Omega$  should be connected in series with P
- B.  $10\Omega$  should be connected in parallel with P
- C.  $5\Omega$  should be connected in series with Q
- D.  $5\Omega$  should be connected in parallel with Q

**Answer: B::C**



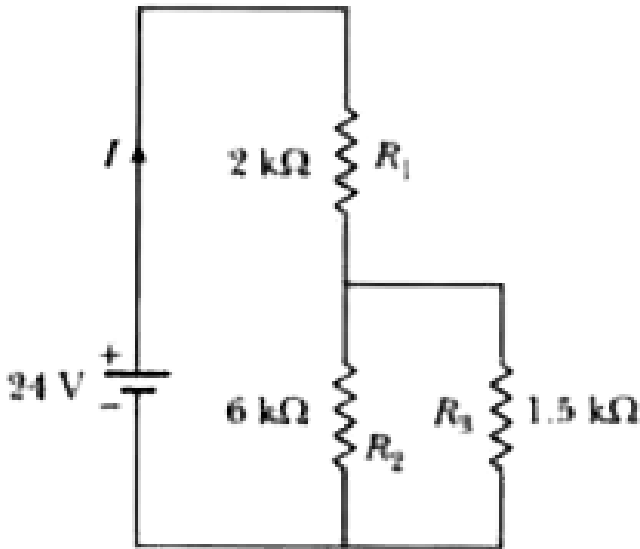5. For the circuit shown in the following figure,




- A. The current  $I$  through the battery is  $7.5\text{ mA}$
- B. The potential difference across  $R_3$  is  $18\text{ V}$
- C. Ratio of powers dissipated in  $R_1$  and  $R_2$  is  $3$
- D. If  $R_1$  and  $R_2$  are interchanged, magnitude of the power dissipated in  $R_3$  will decrease by a factor of  $9$

Answer: A::D

 Watch Video Solution

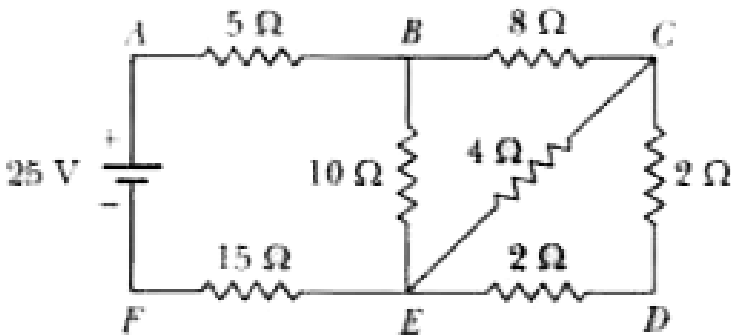6. For the circuit shown in the following figure, the



- A. Potential difference between points B and E is 5 V
- B. Potential difference between points A and B is 10 V
- C. Current in the  $4\Omega$  resistor is 0.25A
- D. Current in the  $4\Omega$  resistor is 0.5 A

Answer: A::D



7. Which of the following statements is/are correct?


- A. If  $n$  identical cells are connected in series and then the battery thus formed is short circuited by a conduction wire, current through the wire will be independent of  $n$
- B. If  $n$  identical cells are connected in parallel and then the battery thus formed is short circuited by conducting wire, the current through the wire will be proportional to  $n$
- C. If  $n$  identical cells are connected in parallel are then the battery thus formed is short circuited by a wire having a constant resistance, the current through the wire will increase as  $n$  increases

D. None of these

Answer: A::B::C

 Watch Video Solution

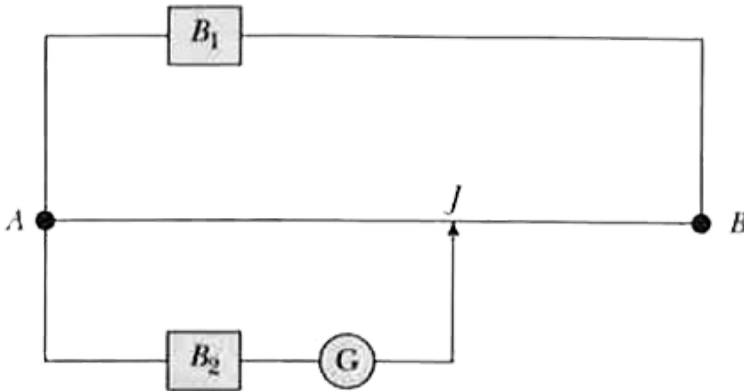8. The below figure shows a potentiometer arrangement, where  $B_1$  is the driving cell,  $B_2$  is the cell whose emf is to be determined. AB is the potentiometer wire and G is the galvanometer. J is a sliding contact which can touch any point on AB. Which of the following are essential conditions for obtaining balance?




- A. The emf of  $B_1$  must be greater than the emf of  $B_2$
- B. Either the positive terminals of both  $B_1$  and  $B_2$  or the negative terminals of both  $B_1$  and  $B_2$  must be joined at A
- C. The positive terminals of  $B_1$  and  $B_2$  must be joined to A
- D. The resistance of G must be less than the resistance of AB

**Answer: A::B**



**View Text Solution**

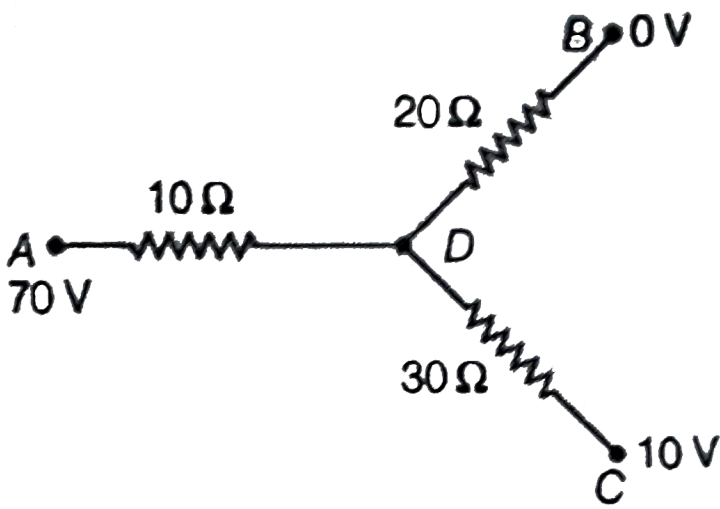9. For the network shown in figure, points A, B and C are at potentials of 70 V, zero and 10 V respectively




- A. The potential of point D is 40 V
- B. The currents in the sections AD, DB, and DC are in the ratio  
3:2:1
- C. The currents in the sections AD, DB, and DC are in the ratio of  
1:2:3
- D. The network draws a total power of 200 W

**Answer: A::B::D**

 [Watch Video Solution](#)

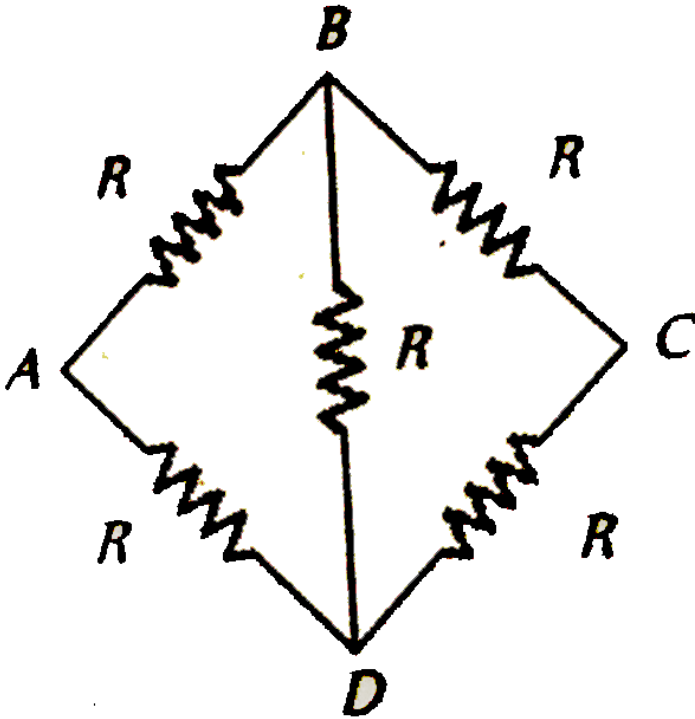10. Five equal resistances each of value  $R$  are connected in a form shown alongside. The equivalent resistance of the network




- A. Between the points B and D is  $R$
- B. Between the points B and D is  $R/2$
- C. Between the points A and C is  $R$
- D. Between the points A and C is  $R/2$



Answer: B::C

 Watch Video Solution

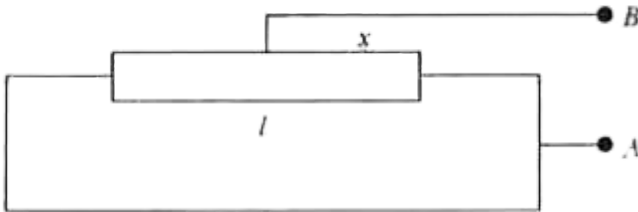11. Two ends of an  $0.1M\Omega$  potentiometer are connected in the way as shown in the following figure.



- A.  $R_{AB} = 0.1M\Omega$  for all values of x
- B.  $R_{AB} > 0.1M\Omega$  for all values of x
- C.  $R_{AB} \leq 0.1M\Omega$  for all values of x
- D.  $R_{AB} \leq 0.1M\Omega$  for all values of x

Answer: C::D



12. Capacitor  $C_1$  of capacitance 1 micro-farad and capacitor  $C_2$  of capacitance 2 microfarad are separately charged fully by a common battery. The two capacitors are then separately allowed to discharged through equal resistors at time  $t = 0$ .

- A. The current in each of the two discharging circuits is zero at  $t=0$
- B. The current in the two discharging circuits at  $t= 0$  are equal but not zero
- C. The current in the two discharging circuits at  $t= 0$  are unequal
- D. Capacitor  $C_1$  loses 50% of its initial charge sooner than  $C_2$  loses 50% of its initial charge

Answer: B::D

 [Watch Video Solution](#)

## Practice Questions Linked Comprehension

1. An electrolytic cell containing a solution of  $CuSO_4$  has an internal resistance of  $1\Omega$ . It is connected in series with 3 V battery of negligible resistance and a  $4\Omega$  resistance. The mass of copper which will be deposited on the copper electrode in 30 min is calculated. If  $4\Omega$  resistance is connected in parallel across the electrolytic cell and the same battery is used, the amount of copper deposited in 30 min is calculated ECE of Cu= 0.00033 g/C. Using Faraday's first law of electrolysis, the mass deposited on the copper electrode can be calculated.

For series connection of  $4\Omega$  resistor, the current flowing through electrolyte is

A. 6A

B. 0.6A

C. 0.2A

D. 1A

**Answer: B**



[View Text Solution](#)

2. An electrolytic cell containing a solution of  $CuSO_4$  has an internal resistance of  $1\Omega$ . It is connected in series with 3 V battery of negligible resistance and a  $4\Omega$  resistance. The mass of copper which will be deposited on the copper electrode in 30 min is calculated. If  $4\Omega$  resistance is connected in parallel across the electrolytic cell and the same battery is used, the amount of copper deposited in 30 min is calculated ECE of Cu= 0.00033 g/C.

Using Faraday's first law of electrolysis, the mass deposited on the copper electrode can be calculated.

Mass of copper deposited in 30 min when resistance of  $4\Omega$  is in series is

A. 0.214g

B. 0.156g

C. 0.356g

D. 0.653g

**Answer: C**



[View Text Solution](#)

3. An electrolytic cell containing a solution of  $CuSO_4$  has an internal resistance of  $1\Omega$ . It is connected in series with 3 V battery of negligible resistance and a  $4\Omega$  resistance. The mass of copper

which will be deposited on the copper electrode in 30 min is calculated. If  $4\Omega$  resistance is connected in parallel across the electrolytic cell and the same battery is used, the amount of copper deposited in 30 min is calculated ECE of Cu= 0.00033 g/C. Using Faraday's first law of electrolysis, the mass deposited on the copper electrode can be calculated.

For the resistance of  $4\Omega$  connected in parallel to cell, the current in the circuit is

- A. 3.75A
- B. 7.35A
- C. 5.73A
- D. 5A

**Answer: A**



**View Text Solution**

4. An electrolytic cell containing a solution of  $CuSO_4$  has an internal resistance of  $1\Omega$ . It is connected in series with 3 V battery of negligible resistance and a  $4\Omega$  resistance. The mass of copper which will be deposited on the copper electrode in 30 min is calculated. If  $4\Omega$  resistance is connected in parallel across the electrolytic cell and the same battery is used, the amount of copper deposited in 30 min is calculated ECE of Cu= 0.00033 g/C. Using Faraday's first law of electrolysis, the mass deposited on the copper electrode can be calculated.

Mass of copper deposited in 30 min when resistance of  $4\Omega$  is in parallel is

- A. 4.214g
- B. 3.337g
- C. 2.227g
- D. 1.117g

**Answer: C**



**View Text Solution**

5. The alternate discs of iron and carbon, having same area of cross-section are cemented together to make a cylinder whose temperature coefficient of resistivity is zero. The change in temperature in two alternate discs is same. The ratio of their thickness and ratio of heat produced in them is found out. The resistivity of iron and carbon at  $20^{\circ}C$  are  $1 \times 10^{-7}$  and  $3 \times 10^{-5} \Omega m$  and their temperature coefficient of resistance are  $5 \times 10^{-3} / ^{\circ}C$  and  $-7.5 \times 10^{-4} / ^{\circ}C$ , respectively. Thermal expansion is neglected. Here,  $\Delta R_1 + \Delta R_2 = 0$  (where  $\Delta R_1$  and  $\Delta R_2$  are the increase in resistances of iron and carbon, respectively, with the rise in temperature) because combined temperature coefficient of



resistivity is given as zero.

Ratio of their thickness is

A. 54

B. 45

C. 35

D. 21

**Answer: B**



[View Text Solution](#)

6. The alternate discs of iron and carbon, having same area of cross-section are cemented together to make a cylinder whose temperature coefficient of resistivity is zero. The change in temperature in two alternate discs is same. The ratio of their thickness and ratio of heat produced in them is found out. The

resistivity of iron and carbon at  $20^{\circ}C$  are  $1 \times 10^{-7}$  and  $3 \times 10^{-5} \Omega m$  and their temperature coefficient of resistance are  $5 \times 10^{-3} / ^{\circ}C$  and  $-7.5 \times 10^{-4} / ^{\circ}C$ , respectively.

Thermal expansion is neglected. Here,

$\Delta R_1 + \Delta R_2 = 0$  (where  $\Delta R_1$  and  $\Delta R_2$  are the increase in resistances of iron and carbon, respectively, with the rise in temperature) because combined temperature coefficient of resistivity is given as zero.

Ratio of heat produced in them is

- A. 0.51
- B. 1
- C. 0.15
- D. 2

**Answer: C**



[View Text Solution](#)

7. The alternate discs of iron and carbon, having same area of cross-section are cemented together to make a cylinder whose temperature coefficient of resistivity is zero. The change in temperature in two alternate discs is same. The ratio of their thickness and ratio of heat produced in them is found out. The resistivity of iron and carbon at  $20^{\circ}C$  are  $1 \times 10^{-7}$  and  $3 \times 10^{-5} \Omega m$  and their temperature coefficient of resistance are  $5 \times 10^{-3} / ^{\circ}C$  and  $-7.5 \times 10^{-4} / ^{\circ}C$ , respectively. Thermal expansion is neglected. Here,  $\Delta R_1 + \Delta R_2 = 0$  (where  $\Delta R_1$  and  $\Delta R_2$  are the increase in resistances of iron and carbon, respectively, with the rise in temperature) because combined temperature coefficient of resistivity is given as zero.

A copper wire is stretched to make it 1% longer. The percentage change in its resistance is

A. 0.002

B. 0.01

C. 0.015


D. 0.025

**Answer: A**



**View Text Solution**

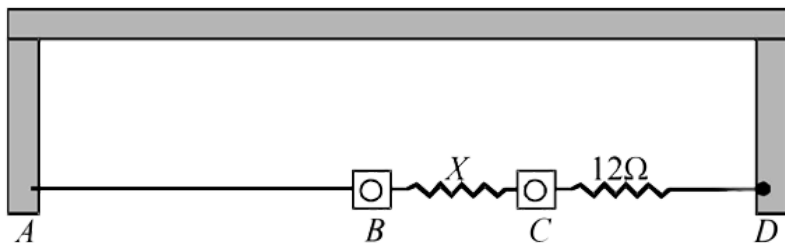8. A thin uniform wire  $Ab$  of length  $1\text{m}$ , an unknown resistance  $X$  and a resistance of  $12\Omega$  are connected by thick conducting strips, as shown in the figure. A battery and a galvanometer (with a sliding jockey connected to it) are also available. Connections are to be made to measure the unknown resistance  $X$  using the principle of Wheatstone bridge. Answer the following questions.



- (a) Are there positive and negative terminals on the galvanometer?
- (b) Copy the figure in your answer book and show the battery and the galvanometer (with jockey) connected at appropriate points.

- A. Positive terminal marked on it
- B. Negative terminal marked on it
- C. Both A and B
- D. None of these

**Answer: C**

 [Watch Video Solution](#)

9. A thin uniform wire  $AB$  of length  $1m$ , an unknown resistance  $X$  and a resistance of  $12\Omega$  are connected by thick conducting strips, as shown in the figure. A battery and a galvanometer (with a sliding jockey connected to it) area also available. Connections are to be made to measure the unknown resistance  $X$  using the principle of Wheatstone bridge. Answer the following questions.



- (a) Are there positive and negative terminals on the galvanometer ?
- (b) Copy the figure in your answer book and show the battery and the galvanometer (with jockey) connected at appropriate points.
- (c) After appropriate connections are made, it is found that no deflection takes place in the galvanometer when the sliding jockey

touches the wire at a distance of  $60\text{cm}$  from  $A$ . Obtain the value of the resistance  $X$ .

A.  $6\Omega$

B.  $8\Omega$

C.  $12\Omega$

D.  $9\Omega$

**Answer: B**



[Watch Video Solution](#)

**10.** A resistor, capacitor, switch, and ideal battery are in series. Originally the capacitor is uncharged. The switch is then closed, allowing current of flow

While the current is flowing, the potential difference across the resistor is

- A. Increasing
- B. Decreasing
- C. Fixed
- D. First increase then decreases

**Answer: B**

 [Watch Video Solution](#)

**11.** A resistor, capacitor, switch, and ideal battery are in series. Originally the capacitor is uncharged. The switch is then closed, allowing current of flow

While the current is flowing, the potential difference across the capacitor is

- A. Increasing
- B. Decreasing



C. Fixed

D. First increase then decreases

**Answer: A**

 [Watch Video Solution](#)

## Practice Questions Matrix Match

1. Match the following

| <b>Column I</b>  | <b>Column II</b>  |
|--|-------------------|
| (a) The capacity of supplying the current in the circuit         | (p) Voltmeter     |
| (b) The electric energy consumed in the circuit                  | (q) Potentiometer |
| (c) emf of the cell in a closed circuit                          | (r) watt-hour     |
| (d) Maximum potential difference between two points of a circuit | (s) ampere-hour   |

 [Watch Video Solution](#)

2. Electrical current is the flow of charged particles. The electric current flows through a wire the same way as how water moves in a river. The electricity is nothing but the flow of electrons. There are two main combinations of resistors in circuit, that is series and parallel. In the given table, Column I shows different combinations of resistors, Column II shows voltages of different arrangements of resistors and Column III shows currents and voltage division needed or not in different arrangements of resistors.

| <b>Column I</b>                                 | <b>Column II</b>                                       | <b>Column III</b>                      |
|---|--|--|
| <b>(I)</b> Series connected resistors           | <b>(i)</b> voltage is different while current is same  | <b>(J)</b> voltage division needed     |
| <b>(II)</b> Parallel connected resistors        | <b>(ii)</b> voltage and current are different          | <b>(K)</b> voltage division not needed |
| <b>(III)</b> When resistors are equal           | <b>(iii)</b> voltage and current are same              | <b>(L)</b> current division not needed |
| <b>(IV)</b> Both series and parallel resistors. | <b>(iv)</b> voltage is same while current is different | <b>(M)</b> current division needed     |

When does the voltage division problem arise?

A. (I) (i) (J)

B. (IV) (i) (M)

C. (III) (ii) (L)

D. (I) (iii) (L)

**Answer: A**



**Watch Video Solution**

**3.** Electrical current is the flow of charged particles. The electric current flows through a wire the same way as how water moves in a river. The electricity is nothing but the flow of electrons. There are two main combinations of resistors in circuit, that is series and parallel. In the given table, Column I shows different combinations of resistors, Column II shows voltages of different arrangements of resistors and Column III shows currents and voltage division needed or not in different arrangements of resistors.

| Column I                                 | Column II                                       | Column III                      |
|--|---|---------------------------------|
| (I) Series connected resistors           | (i) voltage is different while current is same  | (J) voltage division needed     |
| (II) Parallel connected resistors        | (ii) voltage and current are different          | (K) voltage division not needed |
| (III) When resistors are equal           | (iii) voltage and current are same              | (L) current division not needed |
| (IV) Both series and parallel resistors. | (iv) voltage is same while current is different | (M) current division needed     |

When there is no voltage division problem arise?

- A. (II) (iv) (K)
- B. (IV) (i) (M)
- C. (III) (ii) (L)
- D. (III) (iv) (K)

**Answer: A**



**Watch Video Solution**

4. Electrical current is the flow of charged particles. The electric current flows through a wire the same way as how water moves in a river. The electricity is nothing but the flow of electrons. There are two main combinations of resistors in circuit, that is series and parallel. In the given table, Column I shows different combinations of resistors, Column II shows voltages of different arrangements of resistors and Column III shows currents and voltage division needed or not in different arrangements of resistors.

| <b>Column I</b>                                 | <b>Column II</b>                                       | <b>Column III</b>                      |
|---|--|--|
| <b>(I)</b> Series connected resistors           | <b>(i)</b> voltage is different while current is same  | <b>(J)</b> voltage division needed     |
| <b>(II)</b> Parallel connected resistors        | <b>(ii)</b> voltage and current are different          | <b>(K)</b> voltage division not needed |
| <b>(III)</b> When resistors are equal           | <b>(iii)</b> voltage and current are same              | <b>(L)</b> current division not needed |
| <b>(IV)</b> Both series and parallel resistors. | <b>(iv)</b> voltage is same while current is different | <b>(M)</b> current division needed     |

When does the current division problem arise?

A. (III) (i) (K)

B. (IV) (i) (J)

C. (III) (iii) (M)

D. (II) (iv) (M)

**Answer: D**



[Watch Video Solution](#)

### Practice Questions Integer Type

1. When two identical batteries of internal resistance  $1\Omega$  each are connected in series across a resistor  $R$ , the rate of heat produced in  $R$  is  $J_1$ . When the same batteries are connected in parallel across  $R$ , the rate is  $J_2 = 2.25 J_1$  then the value of  $R \in \Omega$  is



[Watch Video Solution](#)

2. A battery of emf  $E$  and internal resistance  $r$  is connected to external resistance  $R$ . The maximum power in the external circuit is  $9W$ . The current flowing in the circuit under this condition is  $3A$ . What is the value of  $E$  in volt ?

 [Watch Video Solution](#)

3. 32 cells each of emf  $3V$  are connected in series. The combination as shown and the total emf is  $84V$ . How many number of cells are connected reversely?

 [Watch Video Solution](#)