




PHYSICS

AAKASH INSTITUTE ENGLISH

Mock test 26

Example

1. The equivalent capacitance between the points A and B in given circuit is 

A. $1\mu F$

B. $2\mu F$

C. $3\mu F$

D. $4\mu F$


Answer: A



Watch Video Solution

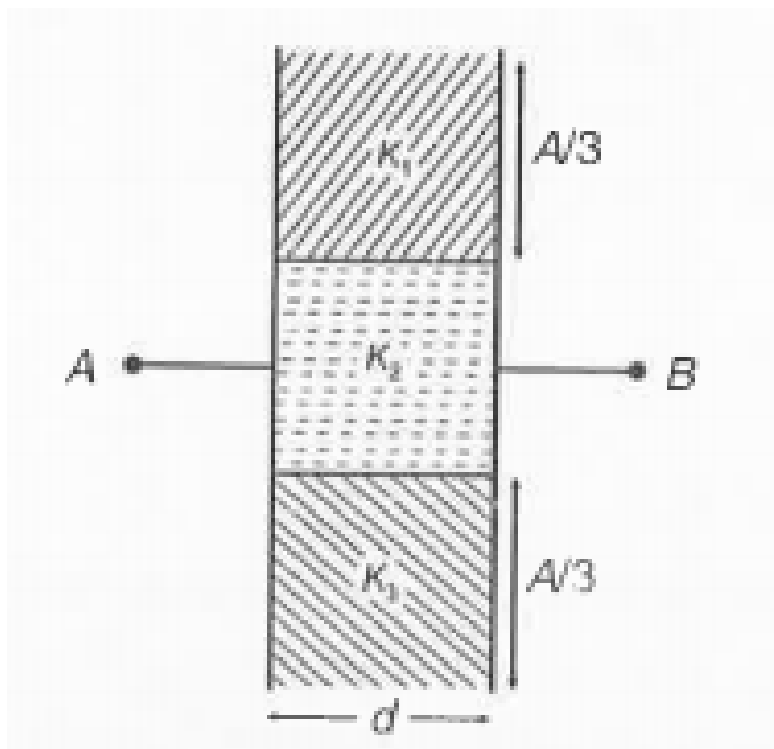2. A parallel plate capacitor of plate area A and separation d filled with three dielectric materials as show in figure. The dielectric

constants are K_1 , K_2 and K_3 respectively. The capacitance across AB will be :



A. $\frac{\epsilon_0 A}{d} \left(\frac{K_1 K_2 K_3}{K_1 + K_2 + K_3} \right)$

B. $\frac{\epsilon_0 A}{d} (K_1 + K_2 + K_3)$

C. $\frac{\epsilon_0 A}{3d} (K_1 + K_2 + K_3)$

$$D. \frac{3\epsilon_0 A}{2d} (K_1 + K_2 + K_3)$$

Answer: C



Watch Video Solution

3. Six equal capacitors each of capacitance $10\mu F$ are connect as shown in the figure. Then the equivalent capacitance between A and B is



A. $20\mu F$

B. $30\mu F$

C. $15\mu F$

D. $10\mu F$


Answer: A



Watch Video Solution

4. A parallel plate capacitor of capacitance C (without dielectric) is filled by dielectric slabs as shown in figure. Then the new capacitance

of the capacitor is

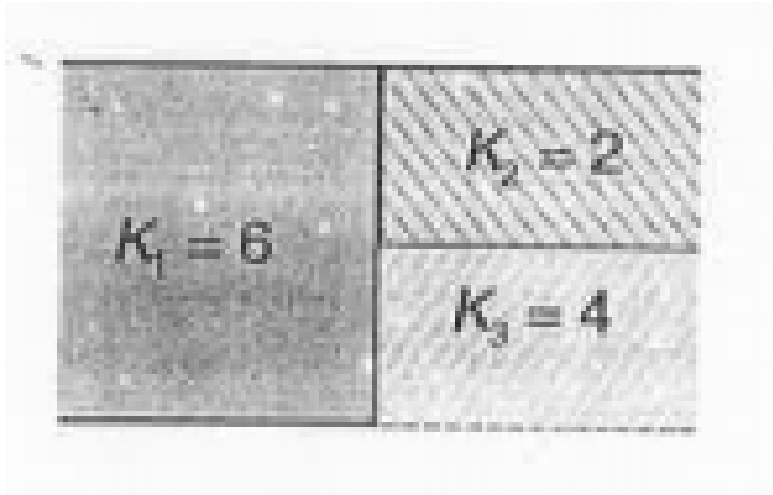

A. $5 C$

B. $\frac{13}{3} C$

C. $\frac{3}{13} C$

D. $2.4 C$

Answer: B



5. The energy required to charge a parallel plate condenser of plate separation d and plate area of cross-section A such that the uniform electric field between the plates E , is

A. $\frac{\frac{1}{2}\epsilon_0 E^2}{Ad}$

B. $\frac{1}{2}\epsilon_0 E^2 Ad$

C. $\epsilon_0 E^2 Ad$


D. $\frac{\epsilon_0 E^2}{Ad}$

Answer: C



Watch Video Solution

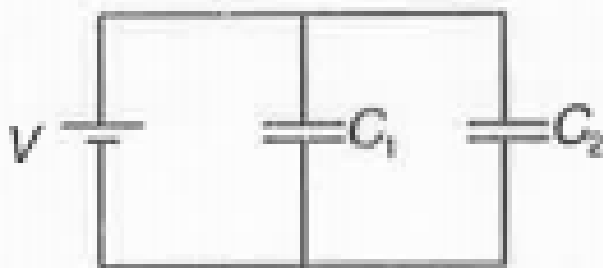6. Two capacitors C_1 and C_2 of capacitances $\frac{C}{2}$ and $\frac{C}{4}$ are connected to a V volt battery, as shown in figure. The ratio of energy stored in capacitors C_1 and C_2 is



A. 1 : 1`

B. 1 : 2`

C. 2 : 1`

D. 2 : 3`

Answer: C



Watch Video Solution

7. A capacitor of capacitance $15\mu F$ has a charge $30\mu C$ and stored energy is W . If charge increased to $60\mu C$ the energy stored will be.

A. W

B. 4W

C. 6W


D. $\frac{1}{2}$ W`

Answer: B



Watch Video Solution

8. Six identical capacitors are connected as shown in figure. Capacitance of each

capacitors is $5\mu F$ The effective capacitance between point A and B is 

A. $7.5\mu F$

B. $10\mu F$


C. $5\mu F$

D. $1.5\mu F$

Answer: A



Watch Video Solution

9. The charge supplied by the battery in the circuit shown in the figure 

A. $\frac{300}{11} \mu C$

B. $60 \mu C$

C. $50 \mu C$

D. $110 \mu C$

Answer: D



Watch Video Solution

10. The energy stored in $4\mu F$ capacitors is 

A. $8\mu J$

B. $12\mu J$

C. $16\mu J$

D. $20\mu J$

Answer: A



Watch Video Solution

11. Two identical parallel plate air capacitors are connected in series to a battery of emf V . If one of the capacitor is completely filled with dielectric material of constant K , then potential difference of the other capacitor will become

A. $110\mu J$

B. $112\mu J$


C. $114.5\mu J$

D. $115.2\mu J$

Answer: D



Watch Video Solution

12. Six identical capacitors each of capacitance $2\mu F$ are connected as shown below. The equivalent capacitance between the points A and B is 

A. $\frac{3}{8}\mu F$

B. $3\mu F$

C. $\frac{8}{3}\mu F$

D. $8\mu F$

Answer: C



Watch Video Solution

13. Van de Graaff generator is

A. The phenomenon of corona discharge

B. The property of hollow conductor is transferred to outer surface

C. Fact that conductor can conduct heat
and electricity

D. Both (1) and (2)

Answer: D



Watch Video Solution

14. Two capacitors $C_1 = C$ and $C_2 = 3C$ are connected as shown in figure, Initially, key K is open and capacitor C_1 holds charge Q . After

closing the key K, the charge on each capacitor

at steady state will be 

A. $\frac{Q}{4}, \frac{Q}{4}$

B. $\frac{Q}{4}, \frac{3Q}{4}$

C. $\frac{3Q}{4}, \frac{3Q}{4}$

D. $Q, \frac{Q}{3}$

Answer: B



Watch Video Solution

15. A capacitor of capacitance C is initially charged to a potential difference of V . Now it is connected to a battery of $2V$ with opposite polarity. The ratio of heat generated to the final energy stored in the capacitor will be

A. $\frac{3}{2}CV^2$

B. $\frac{9}{2}CV^2$

C. CV^2

D. $\frac{9}{4}CV^2$

Answer: B



Watch Video Solution

16. A current of 4 A is flowing in a cylindrical conductor. The number of free electrons passing per second through the cross-section of conductor is

A. $2 \cdot 10^{19}$

B. $3 \cdot 10^{20}$

C. $2.5 \cdot 10^{19}$

D. $4 \cdot 10^{18}$

Answer: C



Watch Video Solution

17. A current 0.5 amperes flows in a conductor of cross-sectional area of $10^{-2}m^2$. If the electron density is $0.3 \cdot 10^{28}m^{-3}$, then the drift velocity of free electrons is

A. $2.1 \cdot 10^{-5}ms^{-1}$

B. $2.5 \cdot 10^{-3}ms^{-1}$

C. $1.5 \cdot 10^{-6}ms^{-1}$

$$D. 1.04 \cdot 10^{-7} \text{ms}^{-1}$$

Answer: D




Watch Video Solution

18. The plot represents the flow of current through a wire at three different times. The ratio of charges flowing through the wire at

different

time

is

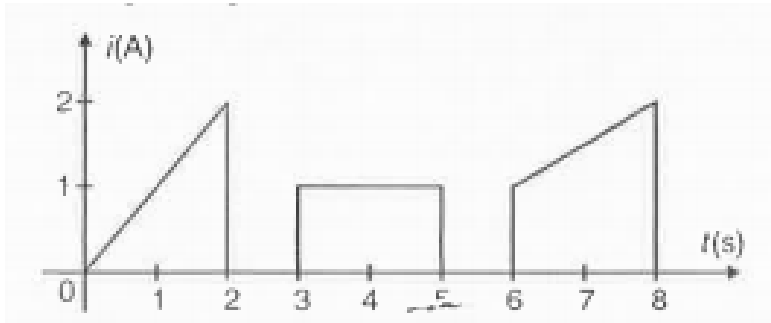

A. $2 : 1 : 2$

B. $1 : 1 : 1$

C. $1 : 3 : 3$

D. $2 : 2 : 3$

Answer: D



Watch Video Solution

19. The specific resistance of a conductor increases with

A. Decrease in temperature

B. Increase in temperature

C. Decreases in cross-sectional area

D. Both (2) & (3)

Answer: B



Watch Video Solution

20. Copper and silicon is cooled from 300 K to 60 K, the specific resistance : -

A. Increases in both

B. Decreases in both

C. Increases in aluminium but decreases in germanium

D. Decreases in aluminium and increases in germanium

Answer: D





[Watch Video Solution](#)

21. The resistance of a metallic conductor increases with temperature due to.

- A. Electron density increases
- B. Relaxation time decreases
- C. Length of wire decreases
- D. All of these

Answer: B



[Watch Video Solution](#)

22. The resistivity of a wire at $20^{\circ}C$ and $100^{\circ}C$ is $3\Omega - m$ and $4\Omega - m$ respectively.

The resistivity of the wire at $0^{\circ}C$ is

A. $\frac{11}{4}\Omega - m$

B. $\frac{4}{11}\Omega - m$

C. $\frac{3}{4}\Omega - m$

D. $\frac{11}{3}\Omega - m$

Answer: A



Watch Video Solution

23. The drift velocity of free electrons in a conductor of length 6 m is 0.25 ms^{-1} under the application of potential difference of 100 V. The mobility of free electrons is

A. $2 \cdot 10^{-3} \text{ m}^2 \text{ V}^{-1} \text{ s}^{-1}$

B. $2.5 \cdot 10^{-2} \text{ m}^2 \text{ V}^{-1} \text{ s}^{-1}$

C. $1.5 \cdot 10^{-2} \text{ m}^2 \text{ V}^{-1} \text{ s}^{-1}$

D. $1.5 \cdot 10^{-3} \text{ m}^2 \text{ V}^{-1} \text{ s}^{-1}$

Answer: C



Watch Video Solution

24. Resistivity of a material of wire is $3 \cdot 10^{-6} \Omega - m$ and resistance of a particular thickness and length of wire is 2Ω . If the diameter of the wire gets doubled then the resistivity will be

A. $1.1 \cdot 10^{-2} \Omega - m$

B. $1.5 \cdot 10^{-3} \Omega - m$

C. $2 \cdot 10^{-6} \Omega - m$

D. $3 \cdot 10^{-6} \Omega - m$

Answer: D



Watch Video Solution


25. Two conductors of equal volumes having non-uniform cross-section are joined as show in figure. The number density of free electrons is more in conductor 2. As current passes through the system. Which of the following

option

is

correct

?

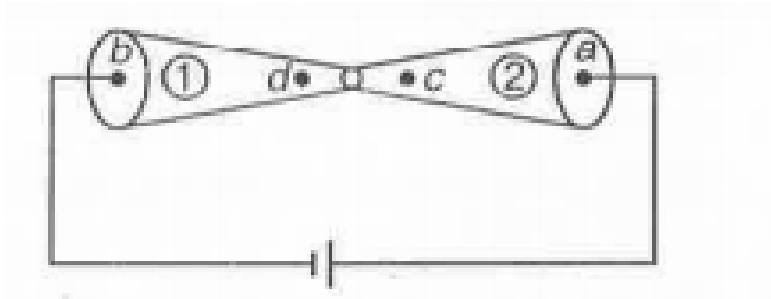

A. Drift speed of electrons at a = Drift speed of electrons at b

B. Drift speed of electrons at c = Drift speed of electrons at d

C. Drift speed of electrons at c is Drift speed of electrons at a

D. Drift speed of electrons at b gt Drift
speed of electrons at a

Answer: D



Watch Video Solution

26. A resistance R of thermal coefficient of resistivity α is connected in parallel with a resistance $3R$ having thermal coefficient of resistivity 2α . Find the value of α_{eff}

A. $\frac{5\alpha}{2}$

B. 3α

C. $\frac{2\alpha}{3}$


D. $\frac{5\alpha}{4}$

Answer: D



Watch Video Solution

27. The area of cross-section of a current carrying conductor is A_0 and $\frac{A_0}{4}$ at section (1) and (2) respectively. If V_1 , V_2 and E_1 , E_2 be

the drift velocity and electric field at section 1 and 2 respectively then 

A. $V_1 : V_2 = 1 : 4$ and $E_1 : E_2 = 4 : 1$

B. $V_1 : V_2 = 4 : 1$ and $E_1 : E_2 = 1 : 2$

C. $V_1 : V_2 = 2 : 1$ and $E_1 : E_2 = 1 : 4$

D. $V_1 : V_2 = 1 : 4$ and $E_1 : E_2 = 1 : 4$

Answer: D



Watch Video Solution