



# PHYSICS

## AAKASH INSTITUTE ENGLISH

### Mock Test 40: PHYSICS

#### Example

1. The symbol of p-n-p transistor is

A. 

B. 

C. 






D. 

**Answer: C**



**Watch Video Solution**

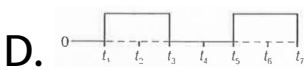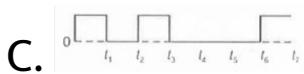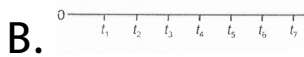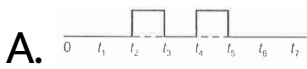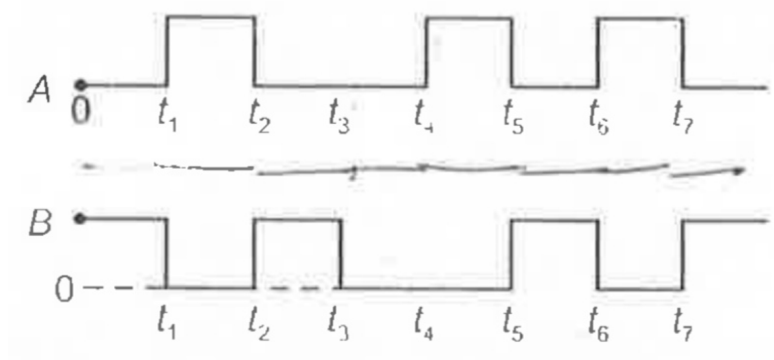2. The output waveform of AND gate for the following input waveforms is



**Answer: B**



**Watch Video Solution**

3. The following truth table corresponds to

<i>A</i>	<i>B</i>	<i>Y</i>
0	0	1
1	0	1
0	1	1
1	1	0

A. AND Gate

B. OR Gate


C. NOR Gate

## D. NAND Gate

**Answer: D**

 [Watch Video Solution](#)

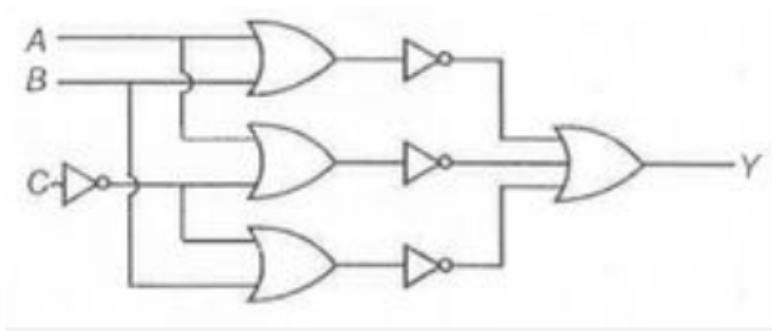**4.** The output Y for logic diagram shown below is



A.  $Y = \bar{A} + \bar{B} + \bar{C}$

B.  $Y = \bar{A} \cdot \bar{B} + \bar{A} \cdot C + \bar{B} \cdot C$


C.  $Y = (\overline{A + B}) + (\overline{B + C}) + (\overline{C + A})$

D.  $Y = \bar{A}B + \bar{B} \cdot C + \bar{C}A$

**Answer: B**

 [Watch Video Solution](#)

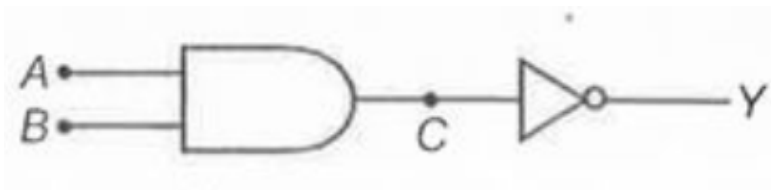5. The output of the following logic circuit is



A.  $Y = A + \overline{B}$

B.  $Y = \overline{A \cdot B}$

C.  $Y = \overline{A} + B$


D.  $Y = \overline{A} \cdot \overline{B}$

**Answer: B**



**Watch Video Solution**

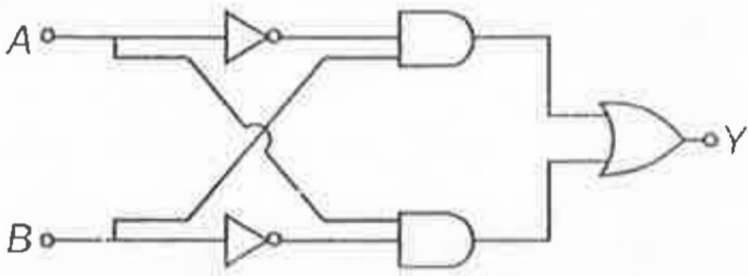**6.** The logic circuit (figure) represents which logic gate?



A. NAND gate

B. AND gate

C. XOR gate

D. NOR gate

**Answer: C**



**Watch Video Solution**



7. In a common emitter amplifier, the input and output voltage are out of phase by

A.  $30^\circ$

B.  $90^\circ$

C.  $120^\circ$

D.  $180^\circ$

**Answer: D**



**Watch Video Solution**

8. A CE amplifier has voltage gain of 50, an input impedance of 2000 ohm and an output impedance of 400 ohm. The power gain of the amplifier will be

A. 22500

B. 12500

C. 32500

D. 4100

**Answer: B**



Watch Video Solution

9. The number of terminals in  $n - p - n$  transistor is

A. 2

B. 3

C. 4

D. 5

**Answer: B**



**Watch Video Solution**

10. An AND gate can be prepared by repetitive use of

A. NOT gate

B. XOR gate

C. OR gate

D. NAND gate

**Answer: D**



**Watch Video Solution**

11. For a transistor, in a common emitter arrangement, the alternating current gain  $\beta$  is given by

A.  $\left. \frac{\Delta I_C}{\Delta I_B} \right]_{V_{CE}}$

B.  $\left. \frac{\Delta I_B}{\Delta I_E} \right]_{V_{BE}}$

C.  $\left. \frac{\Delta I_B}{\Delta I_C} \right]_{V_{CE}}$

D.  $\left. \frac{\Delta I_C}{\Delta I_E} \right]_{V_{CE}}$

**Answer: A**



**Watch Video Solution**

12. Transistors can work as a switch in

A. Saturation region

B. Active region

C. Cut off region

D. Both (1) and (3)

**Answer: D**



**Watch Video Solution**

**13.** Transconductance in CE amplifier circuit is defined as

- A. Ratio of change in collector current to the change in emitter current
- B. Ratio of change in input base-emitter voltage to the change in emitter current
- C. Ratio of change in collector current to the change in input base-emitter voltage

D. Ratio of change in emitter current to the change in input base-emitter voltage

**Answer: C**



**Watch Video Solution**

**14.** Power Gain of CE amplifier circuit is given by

A. Voltage gain  $\times$  current gain

B. Voltage gain/Current gain



C. Current gain/Voltage gain

D. (Voltage gain)<sup>2</sup> × current gain

**Answer: A**



**Watch Video Solution**

**15.** The following gate is equivalent to



A. OR gate

B. AND gate


C. NOT gate

D. XOR gate

**Answer: C**

 **Watch Video Solution**

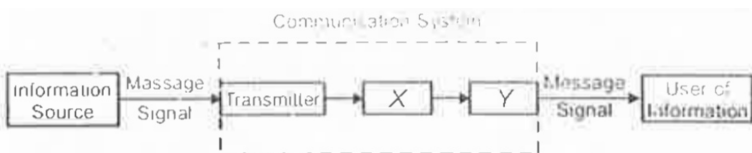**16.** The element X and Y in the communication system (figure) are respectively



A. Noise, channel

B. Receiver, channel

C. Receiver, noise

D. Channel, receiver

**Answer: D**



**Watch Video Solution**

**17.** The length of half wave dipole antenna at 50 MHz is

A. 5 m

B. 4 m

C. 3 m

D. 2 m

**Answer: C**



**Watch Video Solution**

**18.** The process of increasing the strength of a signal using an electronic circuit is called.

A. Attenuation

B. Amplification

C. Modulation

D. Demodulation

**Answer: B**



**Watch Video Solution**

**19.** A device that converts one form of energy into another form is termed as

A. Transducer

B. Channel

C. Repeater

D. All of these

**Answer: A**



**Watch Video Solution**

**20.** The power radiated by linear antenna of length 'l' is proportional to ( $\lambda$ =wavelength)

A.  $P \propto \left(\frac{l}{\lambda}\right)$

B.  $P \propto \left(\frac{\lambda}{l}\right)^2$

C.  $P \propto \left(\frac{l}{\lambda}\right)^2$

D.  $P \propto \left(\frac{\lambda}{l}\right)$

**Answer: C**



**Watch Video Solution**

**21.** One of the components of frequency of amplitude modulated wave (AM) formed by the superposition of message signal of

frequency  $\omega_1$  on a carrier wave of frequency  $\omega_2$

is

A.  $\omega_1$

B.  $\frac{\omega_1}{2}$

C.  $\omega_2$

D.  $\frac{\omega_1 + \omega_2}{2}$

**Answer: C**



**Watch Video Solution**



22. Amplitude modulation index  $\mu$  determines

- A. The quality of received signal
- B. The quality of transmitted signal
- C. The quality of carrier wave
- D. Both (1) and (3)

**Answer: B**



**Watch Video Solution**

23. If  $A_m$  and  $A_c$  are the amplitudes of modulating signal and carrier wave respectively, then modulation index is given by

A.  $\mu = \frac{A_m}{A_c}$

B.  $\mu = \frac{A_c}{A_m}$

C.  $\mu = \frac{A_c^2}{A_m}$

D.  $\mu = \frac{A_m^2}{A_c}$

**Answer: A**



**Watch Video Solution**

24. The maximum line-of-sight distance  $d_M$  between two antennas having heights  $h_T$  and  $H_R$  above the earth is

A.  $d_m = \sqrt{2Rh_T} - \sqrt{2Rh_R}$

B.  $d_m = (\sqrt{2Rh_T} - \sqrt{2Rh_R})^2$

C.  $d_m = \sqrt{2Rh_T} + \sqrt{2Rh_R}$

D.  $d_m = (\sqrt{2Rh_T} + \sqrt{2Rh_R})^2$

**Answer: C**



**Watch Video Solution**

25. The amplitude modulated signal consists of two sinusoidal waves of frequencies, ( $\omega_c \rightarrow$  angular frequency of carrier wave) ( $\omega_m \rightarrow$  angular frequency of modulating signal)

A.  $\frac{\omega_c}{2}, \frac{\omega_m}{2}$

B.  $\frac{\omega_c + \omega_m}{2}, \frac{\omega_c - \omega_m}{2}$

C.  $\frac{\omega_c}{\omega_m}, \frac{\omega_c^2}{\omega_m^2}$

D.  $\omega_c + \omega_m, \omega_c - \omega_m$

**Answer: D**



**Watch Video Solution**

26. An AM transmitter radiates 70 kW of carrier power. The radiated power at 75% modulation would be

A. 89.69 kW

B. 79.20 kW

C. 85.59 kW

D. 83.69 kW

**Answer: A**



27. If  $\omega_c$  and  $\omega_m$  are angular frequencies of carrier wave and modulating signal respectively, then Band width of amplitude modulated waves is equal to

A.  $\frac{\omega_c + \omega_m}{2}$

B.  $2\omega_m$

C.  $2\omega_c$

D.  $\frac{\omega_c - \omega_m}{2}$

**Answer: B**



**Watch Video Solution**

**28.** Communication through free space using radio waves takes place over frequency range of

A. Few tens of MHz to a few GHz

B. Few tens of KHz to a few hundreds of  
KHz

C. Few tens of GHz to a few hundreds of GHz

D. Few hundreds of GHz to few thousands of GHz

**Answer: A**



**Watch Video Solution**

**29.** During the process of modulation, if phase of the carrier wave is varied in accordance with



information/message signals then it would result in

- A. Amplitude modulation
- B. Frequency modulation
- C. Phase modulation
- D. All of these

**Answer: C**



**Watch Video Solution**