




PHYSICS

AAKASH INSTITUTE ENGLISH

Mock Test27

Example

1. A wire of resistance 20Ω is bent to form a complete circle. The resistance between two

diametrically opposite points A and B as shown in the figure, is 

A. 5Ω

B. 20Ω

C. 10Ω


D. 15Ω

Answer: A



Watch Video Solution

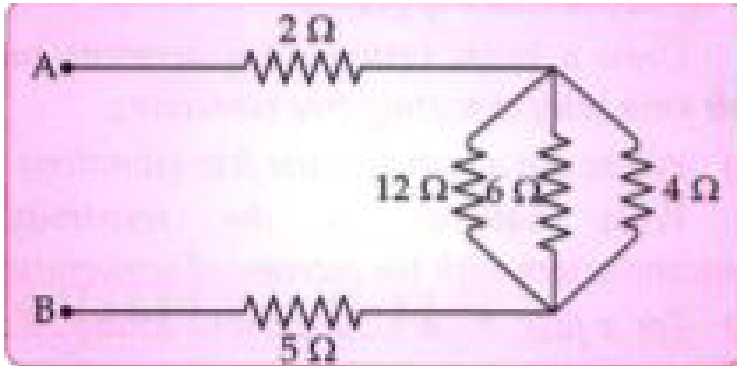2. Find the equivalent resistance between points A and B.



A. Zero

B. $R_1 + R_3$

C. $R_2 + R_3$


D. $R_1 + \frac{R_2 \cdot R_3}{R_2 + R_3}$

Answer: A



Watch Video Solution

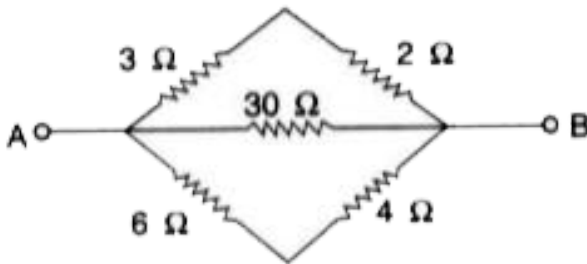3. Calculate the equivalent resistance between the points A and B in Fig.



A. $\frac{2}{3} \Omega$

B. $\frac{4}{3} \Omega$


C. 1Ω

D. 2Ω

Answer: A



Watch Video Solution

4. In the given figure, equivalent resistance between points P and Q is 

A. $\frac{1}{3}\Omega$

B. $\frac{4}{3}\Omega$

C. $\frac{2}{3}\Omega$

D. 2Ω

Answer: B



Watch Video Solution

5. If the ammeter in given circuit reads 1 A, then resistance R is 

A. 4Ω

B. 2Ω

C. 3Ω

D. 1Ω

Answer: A



Watch Video Solution

6. If the power dissipated in the 27Ω resistor in the circuit shown is 108 watt, the potential difference across the 4Ω resistor is



A. 20volt

B. 10 volt

C. 5 volt

D. 4 volt

Answer: A



Watch Video Solution

7. The resistance between the terminal points P and Q of the given infinitely long circuit will

be



A. $2(\sqrt{3} - 1)\Omega$

B. $2(\sqrt{3} + 1)\Omega$

C. $(\sqrt{3} - 1)\Omega$

D. $(\sqrt{3} + 1)\Omega$

Answer: B



Watch Video Solution

8. A battery of EMF 10 V, with internal resistance 1Ω is being charged by a 120 V d.c. supply using a series resistance of 10Ω . The terminal voltage of the battery is

A. 20 V

B. 10 V

C. Zero

D. 30 V

Answer: A



Watch Video Solution

9. A battery of EMF E produces currents 4 A and 3 A when connected to external resistance 1Ω and 2Ω respectively. The internal resistance of the battery is

A. 0.5Ω

B. 2Ω

C. 1.5Ω

D. 1Ω

Answer: B



Watch Video Solution

10. A 5 V battery with internal resistance 1Ω and a 2 V battery with internal resistance 0.5Ω are connected to a 3Ω resistor as shown in the figure. The current in the 3Ω resistor is



A. 0.1 A, A to B

B. 0.1 A, B to A

C. 0.01A, A to B

D. 0.01 A, B to A

Answer: B



Watch Video Solution

11. n identical cells each of e.m.f. E and internal resistance r are connected in series. An external resistance R is connected in series to this combination. The current through R is

A. $\frac{nE}{R + nr}$

B. $\frac{nE}{nR + r}$

C. $\frac{E}{R + nr}$

D. $\frac{nE}{R + r}$

Answer: A



Watch Video Solution

12. Two sources of equal emf are connected to an external resistance R . The internal resistances of the two sources are R_1 and

$R_2, (R_2 > R_1)$ If the potential difference across the source having internal resistance R_2 is zero then :

A. 1Ω

B. $\frac{2}{3}\Omega$

C. 2Ω

D. 6Ω

Answer: A



Watch Video Solution

13. A cell of internal resistance r drives current through an external resistance R . The power delivered by the cell to the external resistance will be maximum when:

A. The cell supplies a power EI

B. The heat is produced in R at the rate $= EI$

C. The heat is produced in R at the rate $=$

$$(EI) \frac{R}{R + r}$$

D. The heat is produced in cell at the rate $=$

$$(EI) \frac{r}{R + r}$$

Answer: B



Watch Video Solution

14. To get maximum current through a resistance of 2.5Ω , one can use m rows of cells, each row having n cells. The internal resistance of each cell is 0.5Ω what are the values of n and m , if the total number of cells is 45.

A. 3, 15

B. 5, 9

C. 9, 5

D. 15, 3


Answer: D



Watch Video Solution

15. For a cell, a graph is plotted between the potential difference V across the terminals of the cell and the current I drawn the cell. The emf and the internal resistance of the cell are

E and r , respectively. Then

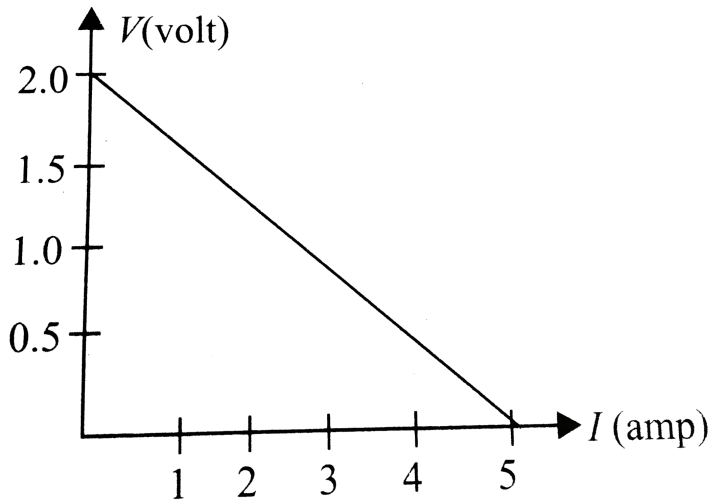

- A. $E = 2 \text{ V}, r = 0.5 \Omega$
- B. $E = 2 \text{ V}, r = 0.4 \Omega$
- C. $E > 2 \text{ V}, r = 0.5 \Omega$
- D. $E > 2 \text{ V}, r = 0.4 \Omega$

Answer: B



Watch Video Solution

16. If electric bulbs having resistances in the ratio $2 : 3$ are connected in parallel to a voltage source of 220 V . The ratio of the power dissipated in them is

A. $2 : 3$

B. $3 : 2$

C. $1 : 1$

D. 2: 5 `

Answer: B



Watch Video Solution

17. Two bulbs $100W, 250V$ and $200W, 250V$ are connected in parallel across a $500V$ line.

Then-

A. $60 W$ bulb will be fused

B. $120 W$ bulb will be fused

C. NO bulb will be fused

D. Both bulbs will be fused

Answer: D



Watch Video Solution

18. Fill in the blanks :

	<i>Volume of cuboid</i>	<i>Length</i>	<i>Breadth</i>	<i>Height</i>
(i)	90 cm ³	...	5 cm	3 cm
(ii)	840 cm ³	15 cm	...	7 cm
(iii)	62.5 m ³	10 m	5 m

A. 4Ω , 12Ω

B. 4Ω , 9Ω

C. 9Ω , 4Ω

D. 9Ω , 9Ω


Answer: C



Watch Video Solution

19. The following figure shows a part of a circuit, the potential difference between C and

$B(V_C - V_B)$ is

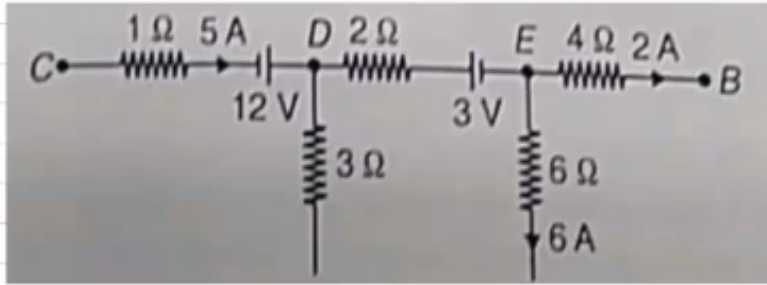

A. + 3 V`

B. + 6 V`


C. + 9 V`

D. -9 V`

Answer: C



Watch Video Solution

20. In the given circuit. If the potential at A is 95 V, then the potential of B is 

A. 12 V

B. 19 V

C. 25 V

D. 5 V


Answer: B



Watch Video Solution

21. Shown is a network of currents. The magnitude of the current is also shown there.

Find the current i .

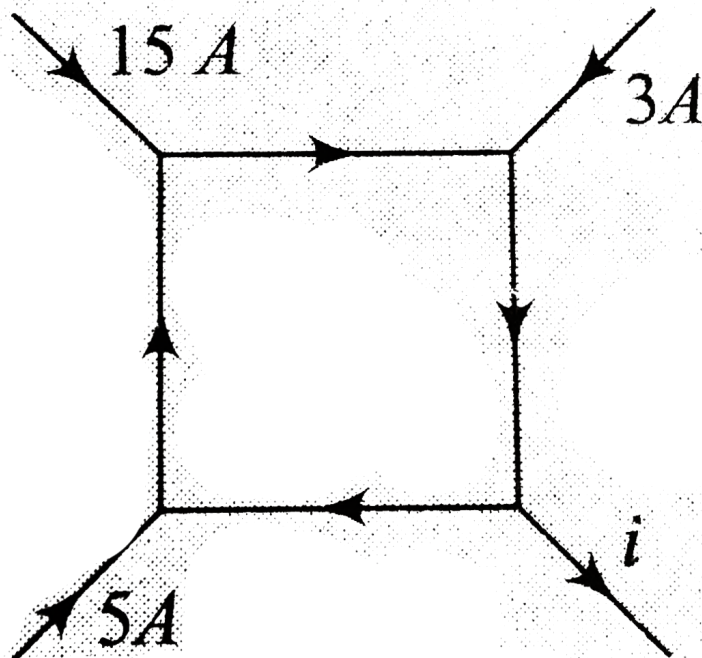

A. 1 A

B. 4 A

C. 8 A^{-1}

D. 10 A^{-1}


Answer: D



Watch Video Solution

22. The following figure shows a part of a circuit, the potential difference between C and

$B(V_C - V_B)$ is

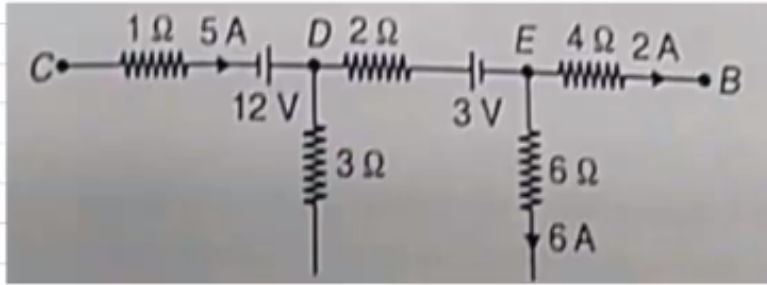

A. 10 V

B. 5 V

C. 15 V


D. 7.5 V

Answer: B



Watch Video Solution

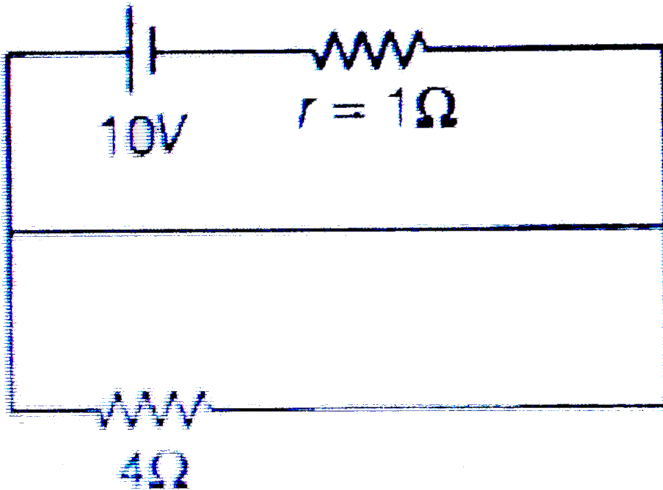23. Potential different across the terminals of the battery shown in figure is




- A. 8 V
- B. 10 V
- C. 5 V
- D. 0 V

Answer: D



Watch Video Solution

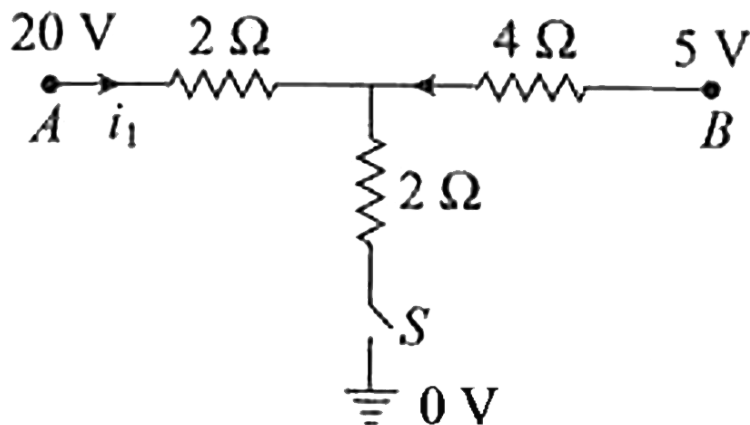24. As the switch S is closed in the circuit shown in figure, current passed through it is



A. 7.5 V

B. 3 V

C. 4.5 V

D. 6.5 V


Answer: C



Watch Video Solution

25. The following figure shows a part of a circuit, the potential difference between C and

$B(V_C - V_B)$ is

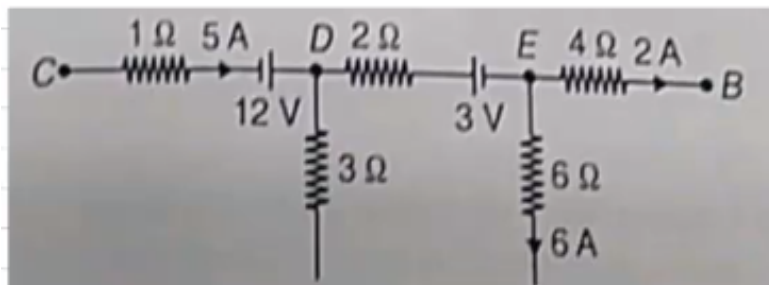

A. 10 V

B. 13 V

C. 20 V

D. 15 V

Answer: C



Watch Video Solution

