



PHYSICS

BOOKS - CENGAGE PHYSICS (ENGLISH)

ALTERNATING CURRENT

Illustrations

1. The electric mains in a house are marked 220V-50Hz. Write down the equation for instantaneous voltage.

 [Watch Video Solution](#)

2. The plate on the back of a personal computer says that it draws 2.7 A from a 120-V, 60-Hz line. For this computer, what is (a)

the average of the square of the current, (b) the current amplitude, (c) the average current for a positive half cycle, and (d) the average current for a full cycle?



[Watch Video Solution](#)

3. An alternating current is given by the following equation:
 $I = 3\sqrt{2} \sin(100\pi t + \pi/4)$. Give the frequency and rms value of the current.



[Watch Video Solution](#)

4. A voltage, $E = 60 \sin(314t)$, is applied across a resistor of 20Ω . What will be the reading of I_{rms} .

(a) in an ac ammeter?

(b) in an ordinary moving coil ammeter in series with the resistor?



[Watch Video Solution](#)

5. Suppose you want the current amplitude in a pure inductor in a radio receiver to be $250\mu A$ when the voltage amplitude is $3.60V$ at a frequency of 1.60 MHz , (corresponding to the upper is 3.60 V AM broadcast band). What inductive reactance is needed? What inductance is required?




[Watch Video Solution](#)

6. A pure inductance of 1.0H is connected across a 110V , 70Hz Source. Find the (a) reactance, (b) current and (c) peak value of current.



[Watch Video Solution](#)

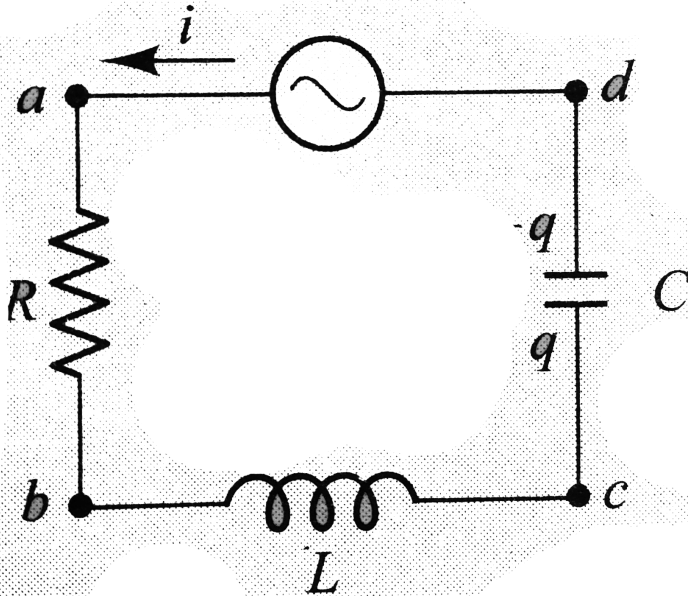7. In the series circuit of fig, suppose $R = 300\Omega$, $L = 60mH$, $C = 0.50(\mu)F$, source amplitude is $E_0 = 50V$ and $\omega = 10000rads^{-1}$. Find the reactances X_L and X_C , the impedance Z and the current amplitude I_0 .



[Watch Video Solution](#)

8. The numerical value of the ratio of instantaneous velocity to instantaneous speed is.

 [Watch Video Solution](#)

9. A 200Ω resistor is connected in series with a $5(\mu)F$ capacitor.

The voltage across the resistor is

$$V_R = (1.20V)\cos(2500\text{rads}^{-1})t.$$

- Derive an expression for the circuit current.
- Determine the capacitive reactance of the capacitor.

 [Watch Video Solution](#)

10. A 200Ω resistor and $1H$ inductor are joined in series with an ac source of emf $10\sqrt{2}\sin(200t)V$. Calculate the phases difference between emf and current.

 [Watch Video Solution](#)

11. A lamp with a resistance of 8Ω is connected to a choke coil. This arrangement is connected to an alternating source of 110V.

The current in the circuit is 11A. The frequency of the ac is 60 Hz.

Find

(a) the impedance of the circuit and

(b) the value of inductive reactance of the choke coil.



[Watch Video Solution](#)

12. A resistor of 200Ω and a capacitor of $15.0\mu F$ are connected in series to a 22V, 50Hz ac source. (a) Calculate the current in the circuit. (b) Calculate the voltage (rms) across the resistor and the capacitor. Is the algebraic sum of these voltages more than the source voltage? if yes, resolve the paradox.



[Watch Video Solution](#)

13. In a series L-R circuit ($L = 35 \text{ mH}$ and $R = 11\Omega$), a variable emf source ($V = V_0 \sin \omega t$) of $V_{rms} = 220V$ and frequency 50 Hz is applied. The current amplitude in the circuit is

 [Watch Video Solution](#)

14. The potential difference E and current I flowing through the ac circuit is given by $E = 5 \cos(\omega t - \pi/6)V$ and $I = 10 \sin(\omega)tA$. Find the average power dissipated in the circuit.

 [Watch Video Solution](#)

15. A series LCR circuit with $L = 0.12 \text{ H}$, $C = 480 \text{ nF}$, $R = 23 \Omega$ is connected to a 230 V variable frequency supply. (a) What is the source frequency for which current amplitude is maximum.

Obtain this maximum value. (b) What is the source frequency for which average power absorbed by the circuit is maximum. Obtain the value of this maximum power. (c) For which frequencies of the source is the power transferred to the circuit half the power at resonant frequency? What is the current amplitude at these frequencies? (d) What is the Q-factor of the given circuit?



[Watch Video Solution](#)

Solved Examples

1. A $25(\mu)F$ capacitor, a 0.1 H inductor and a 25Ω resistor are connected in series with an ac source of emf $E = 310 \sin 314t$.

Find

- the frequency of the emf
- the impedance of the circuit

(c) the current in the circuit.

(d) the phase angle



[Watch Video Solution](#)

2. A circuit containing a 80 mH inductor and a $60 \mu F$ capacitor in series is connected to a 230 V, 50 Hz supply. The resistance of the circuit is negligible. (a) Obtain the current amplitude and rms values. (b) Obtain the rms values of potential drops across each element. (c) What is the average power transferred to the inductor? (d) What is the average power transferred to the capacitor? (e) What is the total average power absorbed by the circuit? ['Average' implies 'averaged over one cycle'.]



[Watch Video Solution](#)

3. An emf $E = 100 \sin 314tV$ is applied across a pure capacitor of $637(\mu)F$. Find

- (a) the instantaneous current I
- (b) the instantaneous power p .

 [Watch Video Solution](#)

4. A radio can be turned over a frequency range from $500kHz \rightarrow 1.5MHz$. If its L-C circuit has an effective inductance of $400(\mu)H$, what is the range of its variable capacitor.

 [Watch Video Solution](#)

5. Obtain the resonant frequency and Q-factor of a series LCR circuit with $L = 3.0H$, $C = 27(\mu)F$, and $R = 7.4\Omega$. How will

you improve the sharpness of resonance of the circuit by a factor of 2 by reducing its full width at half maximum?

 [Watch Video Solution](#)

6. An inductive circuit draws a power 550 W from a 220V-50Hz source. The power factor of the circuit is 0.8. The current in the circuit lags behind the voltage. Show that a capacitor of about $\frac{1}{42\pi} \times 10^{-2} F$ will have to be connected in the circuit to bring its power factor to unity.

 [Watch Video Solution](#)


Exercise 5 1

1. Can we use 15 Hz ac for lighting purpose?




 Watch Video Solution

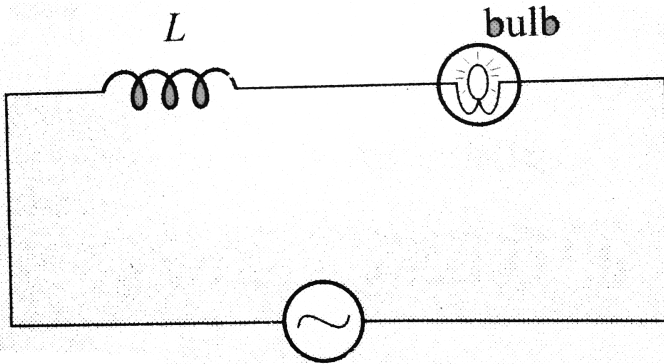2. A soft iron rod is inserted in the solenoid. After this what will be the effect on the brightness of the bulb?




 Watch Video Solution

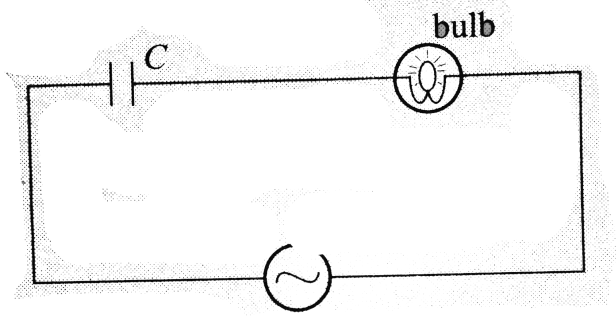3. In the circuit, shown in fig. what will be the effect on the brightness of blub if frequency of the source ω is increased?




[▶ Watch Video Solution](#)

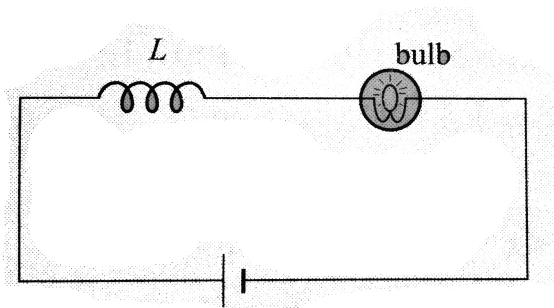4. An soft iron rod is inserted in the inductor, what will be the effect on the brightness of the bulb?



[▶ Watch Video Solution](#)

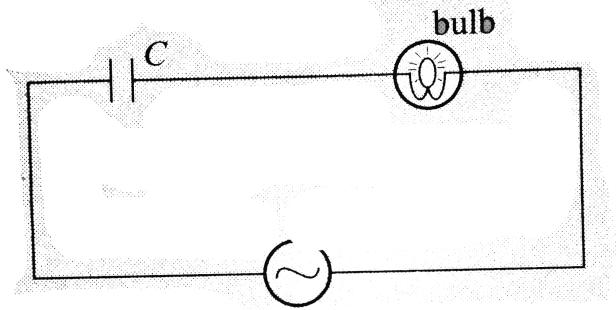5. In the circuit, shown in fig. what will be the effect on the brightness of bulb if frequency of the source ω is increased?



[Watch Video Solution](#)

6. In the above question, what will be the effect on the brightness of bulb if capacitance C is reduced?

[Watch Video Solution](#)

7. An inductor wire has some resistance R when connected to dc. It is connected to an ac source. Now the impedance of the wire will be more than R . (true/false)

 [Watch Video Solution](#)

8. The element of an electric heater is in the form of a coil. Once it is heated by dc voltage and then by ac voltage of equal potential difference. Will the production of heat in both cases be same or different?

 [Watch Video Solution](#)

9. When L and C are in series, voltage across them is in phase (True/false). The current in them is in phase (true/false).

 [Watch Video Solution](#)

[Watch Video Solution](#)

10. In a series LCR circuit, the frequency of the source is more than resonance frequency. The current in the circuit leads the voltage in phases(True/false).

 [Watch Video Solution](#)

11. In a series LCR circuit, voltage drop across L can be more than applied voltage (True/false).

 [Watch Video Solution](#)

12. For circuits used for transporting electric power, a low power factor implies larger power loss in transmission. Explain?

 [Watch Video Solution](#)

13. At very high frequency of ac, capacitor behave like a conductor.

(True/false)



Watch Video Solution

14. For a series LCR circuit the power loss at resonance is : -



Watch Video Solution


15. Can we have resonance in LR or CR circuits?



Watch Video Solution

Exercises Subjective

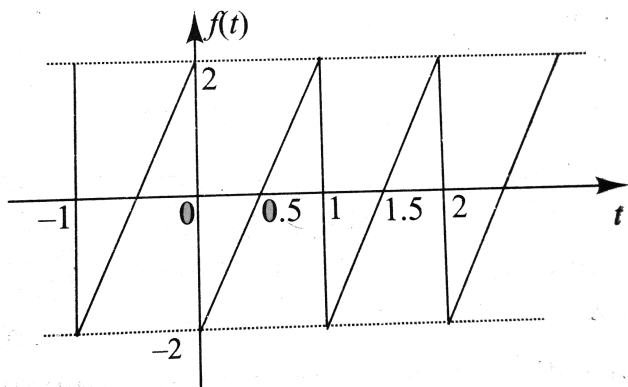1. Find the rms and the average values of the saw tooth waveform shown in fig.



[▶ Watch Video Solution](#)

2. An inductor 20×10^{-3} a capacitor $100(\mu)F$ and a resistor 50Ω are connected in series across a source of emf $V = 10 \sin 314t$. Then the energy dissipated in the circuit in 20 mim is

[▶ Watch Video Solution](#)

3. Show graphically that the average of sinusoidally varying current in half cycle may or may not be zero.



[Watch Video Solution](#)

4. Current in an ac circuit is given by $i = 2\sqrt{2}\sin[(\pi t + ((\pi)/4)]$. Then find the average value of current during time $t=0$ to $t=1$ s.



[Watch Video Solution](#)

5. Find the effective value of current.

$$i = 2 \sin 100(\pi)t + 2 \cos(100\pi t + 30^\circ).$$



[Watch Video Solution](#)

6. When a voltage $V_s = 200\sqrt{2}\sin(100t)V$ is applied to an ac circuit the current in the circuit is found to be $i = 2\sin[\omega t + (\pi/4)]A$. Find the average power consumed in the circuit.

 [Watch Video Solution](#)

7. An alternating voltage $E = 200\sqrt{2}\sin(100t)$ is connected to a μF capacitor through an AC ammeter. The reading of the ammeter shall be

 [Watch Video Solution](#)

8. In an RC series circuit the rms voltage of source is 200V and its frequency is 50 Hz, if $R = 100\Omega$ and $C = \frac{100}{\pi}(\mu)F$, find

(a) impedance of the circuit.

(b) power factor angle,

(c) power factor,

(d) current,

(e) maximum current



[Watch Video Solution](#)

9. An ac source of angular frequency ω is fed across a resistor R and a capacitor C in series. The current registered is I . If now the frequency of source is changed to $(\omega)/3$ (but maintaining the same voltage), the current in the circuit is found to be halved. Calculate the ratio of the reactance to resistance at the original frequency ω .



[Watch Video Solution](#)

10. A $9/100(\pi)$ inductor and a 12Ω resistance are connected in series to a 225 V, 50 Hz ac source. Calculate the current in the circuit and the phase angle between the current and the source voltage.

 [Watch Video Solution](#)

11. When an inductor coil is connected to an ideal battery of emf 10V, a constant current 2.5 A flows. When the same inductor coil is connected to an ac source of 10V and 50 HZ then the current is 2A. Find out the inductance of the coil.

 [Watch Video Solution](#)

12. A bulb is rated at 100V, 100W. It can be treated as a resistor. Find out the inductance of an inductor (called choke coil) that

should be connected in series with the bulb at its rated power with the help of an ac source of 200V and 50Hz.



[Watch Video Solution](#)

13. A choke coil is needed to operate an arc lamp at 160 V (rms) and 50 Hz. The lamp has an effective resistance of 5Ω when running at 10 A (rms). Calculate the inductance of the choke coil. If the same arc lamp is to be operated on 160 V (DC), what additional resistance is required ? Compare the power losses in both cases.



[Watch Video Solution](#)

14. A coil of inductance 0.50H and resistance 100Ω is connected to a 240V. 50Hz ac supply.

(a) What is the maximum current in the coil? (b) What is the time lag between the voltage maximum and the current maximum?

 [Watch Video Solution](#)


15. A $100 \mu F$ capacitor in series with a 40Ω resistance is connected to a 110V, 60Hz supply.

(a) What is the maximum current in the circuit? (b) What is the time lag between the current maximum and the voltage maximum?

 [Watch Video Solution](#)

Exercises Single Correct

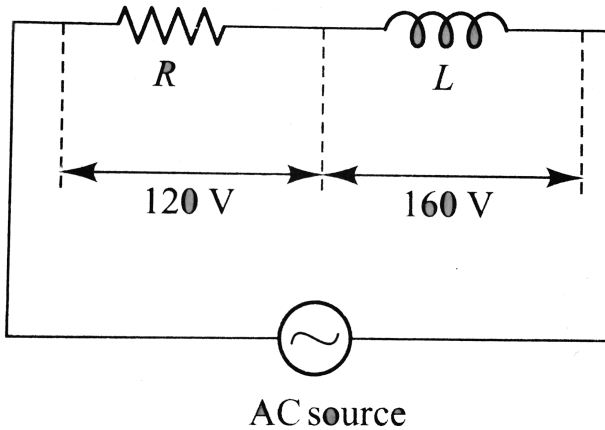
1. The circuit given in fig. has a resistanceless choke coil L and a resistance R . The voltage across R and L are also given in the figure. The virtual value of the applied voltage is



- A. 100V
- B. 200V
- C. 300V
- D. 400V

Answer: B

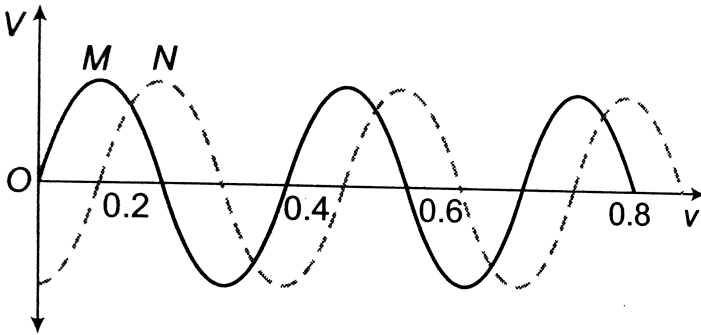2. Two sinusoidal voltage of the same frequency are shown in the diagram. What is the frequency, and the phase relationship between the voltage? Frequency in Hz phase lead of N over M in radian .




- A. Frequency/Hz =0.4, phase lead of N over M in rad $s^{-1} = -\frac{\pi}{4}$
- B. Frequency/Hz =2.5, phase lead of N over M in rad $s^{-1} = -\frac{\pi}{2}$
- C. Frequency/Hz =2.5, phase lead of N over M in rad $s^{-1} = 2\frac{\pi}{2}$
- D. Frequency/Hz =2.5, phase lead of N over M in rad $s^{-1} = -\frac{\pi}{4}$

Answer: B

 Watch Video Solution

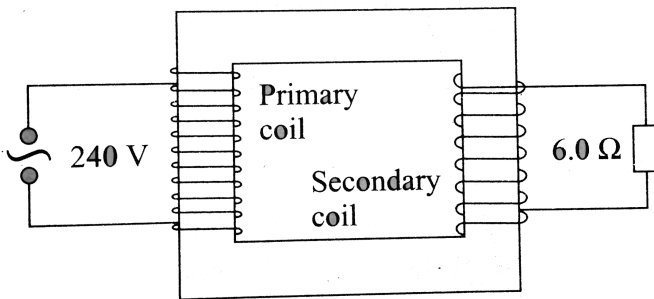3. Figure shows an iron-cored transformer assumed to be 100% efficient. The ratio of the secondary turns to the primary turns is 1:20.



A 240 V ac supply is connected to the primary coil and a 6Ω resistor is connected to the secondary coil. What is the current in the primary coil?

A. 0.10A

B. 0.14A

C. 2A


D. 40A

Answer: A



Watch Video Solution

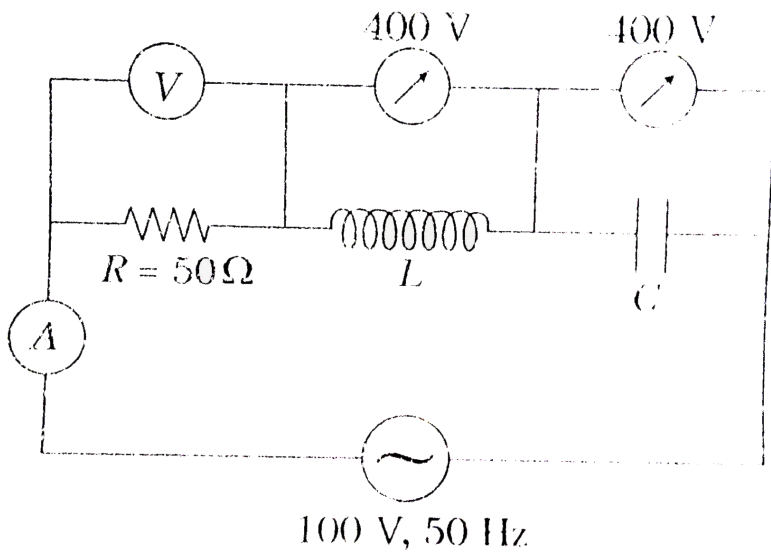4. In the series L-C-R circuit , the voltmeter and ammeter readings are



- A. $V = 100\text{V}, I = 2\text{A}$
- B. $V = 100\text{V}, I = 5\text{A}$
- C. $V = 1000\text{V}, I = 2\text{A}$
- D. $V = 300\text{V}, I = 1\text{A}$

Answer: A

 [Watch Video Solution](#)

5. In an AC - circuit , the current lags behind the voltage by $\pi/3$.

The components in the circuit may be

A. 1A

B. 1.5A

C. 2A

D. 2.5A

Answer: C



[Watch Video Solution](#)

6. The rms value of an AC of 50Hz is 10 A. the time taken by an alternating current in reaching from zero to maximum value and the peak value of current will be

A. $2 \times 10^{-2} s$ and $14.14A$

B. $1 \times 10^{-2} s$ and $7.07A$

C. $5 \times 10^{-3} s$ and $7.07A$

D. $5 \times 10^{-3} s$ and $14.14A$

Answer: D



[Watch Video Solution](#)

7. The peak value of an alternating emf E given by

$$E = \frac{E}{o} \cos \omega t$$

is $10 V$ and frequency is 50 Hz . At time $t = (1/600) s$, the instantaneous value of emf is

A. $10V$

B. $5\sqrt{3}V$

C. $5V$

D. $1V$

Answer: B



Watch Video Solution

8. A coil has a inductance of 0.7π H and is joined in series with a resistance of 220Ω . When an alternating emf of $220V$ at 50 cps is applied to it, then the watt-less component of the current in the circuit is (*take* $0.7\pi = 2.2$)

A. $5A$

B. $0.5A$

C. $0.7A$

D. $7A$

Answer: B



Watch Video Solution

9. When 100V. DC is applied across a solenoid a current of 1A flows in it. When 100V, AC is applied across the same coil, the current drops to 0.5A. The frequency of the AC is 50Hz. The impedance and inductance of the solenoid are

- A. 200Ω and $0.55H$
- B. 100Ω and $0.86H$
- C. 200Ω and $0.1H$
- D. 100Ω and $0.93H$

Answer: A



Watch Video Solution

10. An ideal inductive coil has a resistance of 100Ω When an ac signal of frequency 1000Hz is applied to the coil the voltage leads the current by 45° The inductance of the coil is .

A. 2 mH

B. 3.3 mH

C. 16 mH

D. $\sqrt{5}\text{mH}$


Answer: C



[Watch Video Solution](#)

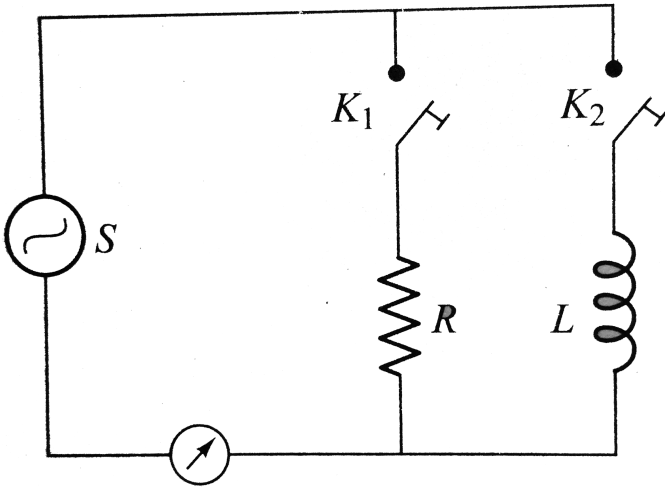11. In the circuit shown in fig. R is a pure resistor, L is an inductor of negligible resistance (as compared to R), S is a 100 V , 50 Hz ac

source of negligible resistance. With either key (K_1) alone or (K_2) alone closed, the current is (I_0) . If the source is changed to 100 V, 100 Hz the current with (K_1) alone closed and with (K_2) alone closed will be, respectively.




- A. $(I_0), \frac{I_0}{2}$
- B. $(I_0), 2(I_0)$
- C. $2(I_0), (I_0)$
- D. $2(I_0), \frac{I_0}{2}$

Answer: A

 Watch Video Solution

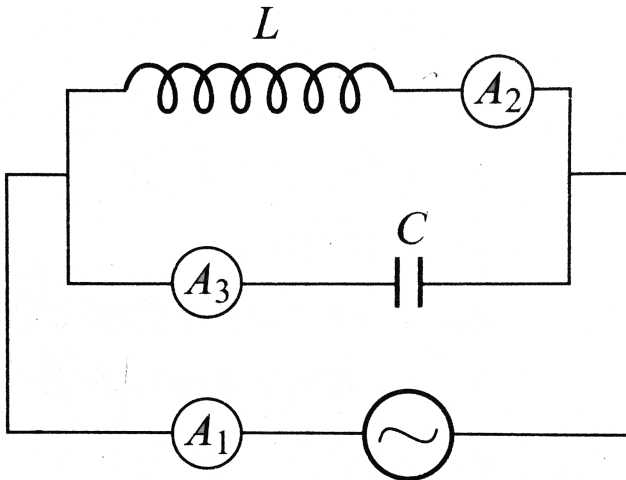12. For the circuit shown in fig, the ammeter A_2 reads 1.6A and ammeter (A_3) reads 0.4A. Then



A. (A) $\omega = \frac{4}{\sqrt{LC}}$

B. (B) $f = \frac{2\pi}{\sqrt{LC}}$

C. (C) The ammeter (A_1) reads 1.2 A

D. (D)the ammeter (A_1) reads 2A

Answer: C





Watch Video Solution

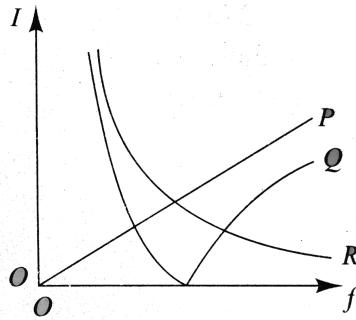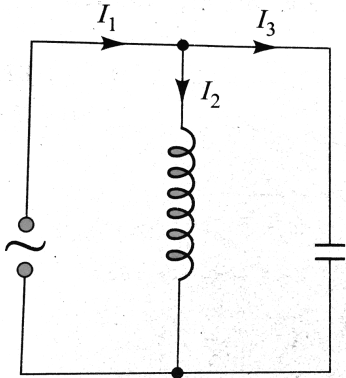13. In the circuit shown in fig, the rms currents (I_1), (I_2) and (I_3) are altered by varying the frequency f of the oscillator. The output voltage of the oscillator remains sinusoidal and has a fixed amplitude.

When curves in figure correctly indicate the variation with

frequency of the currents (I_1), (I_2), and (I_3).




- A. (A) $(I_1) = Q, (I_2) = Q, (I_3) = Q$
- B. (B) $(I_1) = R, (I_2) = Q, (I_3) = Q$
- C. (C) $(I_1) = Q, (I_2) = P, (I_3) = R$
- D. (D) $(I_1) = Q, (I_2) = R, (I_3) = P$

Answer: D

 **Watch Video Solution**

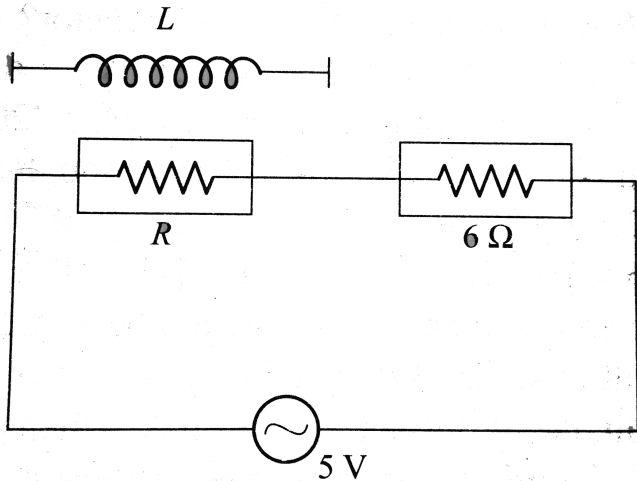14. Two resistor are connected in series across a 5 V rms source of alternating potential. The potential difference across 6Ω resistor is 3V. If R is replaced by a pure inductor L of such magnitude that current reamins same. Then the pontential difference across L is




- A. (A) 1 V
- B. (B) 2 V
- C. (C) 3 V
- D. (D) 4 V

Answer: D

 Watch Video Solution

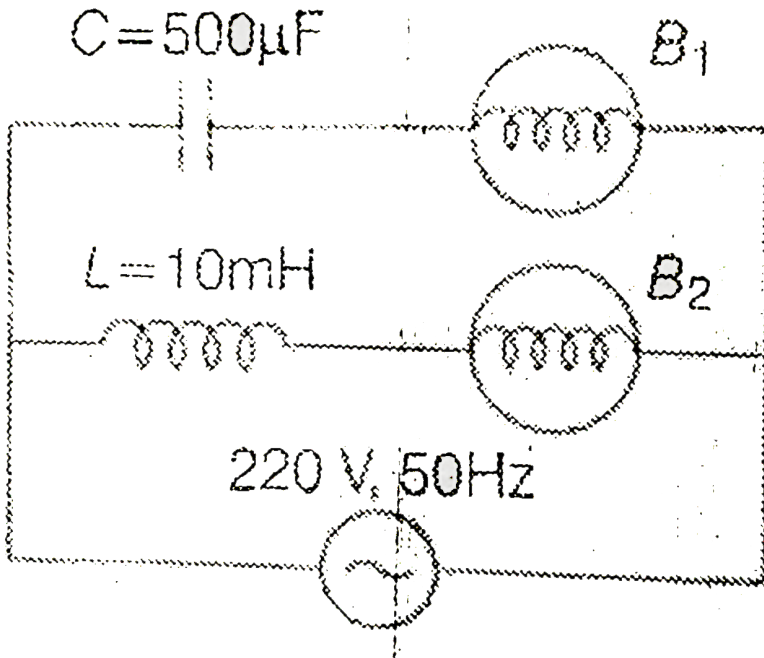15. In the circuit shown in the figure, if both the bulbs B_1 and B_2 are identical



A. (A) their brightness will be the same

B. (B) (B_2) will be brighter than (B_1)

C. (C) (B_1) will be brighter than (B_2)

D. (D) only (B_2) will glow because the capacitor has infinite impedance



Answer: B




Watch Video Solution

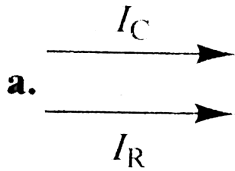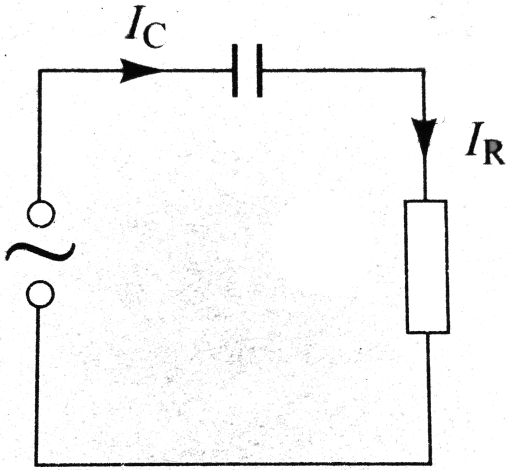16. figure, shows a source of alternating voltage connected to a capacitor and a resistor. Which of the following phasor diagrams correctly describes the phase relationship between (I_C) the current between the source and the capacitor and (I_R) the


current between the source and the resistor?




A.

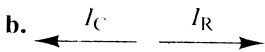

B.

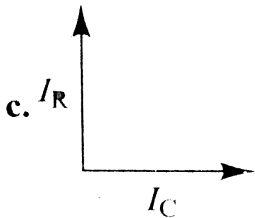

C.

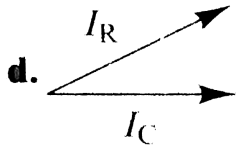

D.

Answer: B

 [Watch Video Solution](#)

17. A sinusoidal alternating current of peak value (I_0) passes through a heater of resistance R . What is the mean power output of the heater?

A. (A) $I_0^2 R$

B. (B) $\frac{I_0^2 R}{2}$

C. (C) $2I_0^2 R$

D. (D) $\sqrt{2}I_0^2 R$

Answer: B

 [Watch Video Solution](#)

18. Power factor is one for

- A. (A) pure resistor
- B. (B) pure inductor
- C. (C) pure capacitor
- D. (D) either an inductor or a capacitor

Answer: A

 [Watch Video Solution](#)

19. A resistance of 20ohms is connected to a source of an alternating potential $V=220 \sin (100 \pi t)$. The time taken by the current to change from its peak value to r.m.s value is

A. (A) $0.2s$

B. (B) $0.25s$

C. (C) $2.5 \times 10^{-3}s$

D. (D) $2.5 \times 10^{-3}s$

Answer: D



[Watch Video Solution](#)

20. In LCR circuit current resonant frequency is 600Hz and half power points are at 650 and 550 Hz. The quality factor is

A. (A) $\frac{1}{6}$

B. (A) $\frac{1}{3}$

C. (C) 6

D. (D) 3

Answer: C



Watch Video Solution

21. An ac voltage is represented by

$$E = 220\sqrt{2} \cos(50\pi)t$$

How many times will the current become zero in 1 s?

A. (A) 50 times

B. (B) 100 times

C. (C) 30 times

D. (D) 25 times

Answer: A



Watch Video Solution

22. A resistor and an inductor are connected to an ac supply of 120 V and 50 Hz, the current in the circuit is 3 A. If the power consumed in the circuit is 108 W, then the resistance in the circuit is

A. (A) 12Ω

B. (B) 40Ω

C. (C) $\sqrt{(52 \times 28)}\Omega$

D. (D) 360Ω

Answer: A



Watch Video Solution

23. A transmitter transmits at a wavelength of 300 m. A condenser of capacitance $2.4(\mu)F$ is being used. The value of the inductance for the resonant circuit is approximately

A. (A) $10^{-4}H$

B. (B) $10^{-6}H$

C. (C) $10^{-8}H$

D. (D) $10^{-10}H$

Answer: C



Watch Video Solution

24. A capacitor of capacitance $1\mu\text{F}$ is charged to a potential of 1V . It is connected in parallel to an inductor of inductance 10^{-3}H . The maximum current that will flow in the circuit has the value

A. (A) $\sqrt{1000}\text{mA}$

B. (B) 1mA

C. (C) $1(\mu)\text{A}$

D. (D) 1000mA

Answer: A



Watch Video Solution

25. Using an AC voltmeter, the potential difference in the electrical line in a house is found to be 234V . If the line frequency

is known to be 50 cycles per second, the equation for the line voltage is

A. (A) $V = 165 \sin(100\pi t)$

B. (B) $V = 331 \sin(100\pi t)$

C. (C) $V = 220 \sin(100\pi t)$

D. (D) $V = 440 \sin(100\pi t)$

Answer: B



Watch Video Solution

26. An inductance and a resistance are connected in series with an AC potential . In this circuit

A. (A) the current and the PD across the resistance lead the PD across the inductance

- B. (B) the current and the PD across the resistance lag behind the PD across the inductance by an angle $(\pi) / (2)$.
- C. (C) the current and the PD across the resistance lag behind the PD across the inductance by an angle (π) .
- D. (D) the PD across the resistance lag behind the PD across the inductance by an angle $(\pi) / (2)$ but the current in resistance leads the PD across the inductance by $(\pi) / (2)$.

Answer: B

 [Watch Video Solution](#)

27. A resistor and a capacitor are connected to an ac supply of 200 V, 50 Hz, in series. The current in the circuit is 2A. If the power

consumed in the circuit is 100 W then the resistance in the circuit is

A. (A) 100Ω

B. (B) 25Ω

C. (C) $\sqrt{125 \times 75}\Omega$

D. (D) 400Ω

Answer: B



Watch Video Solution

28. A resistor and capacitor are connected to an ac supply of 200 V, 50 Hz in series. The current in the circuit is 2 A. If the power consumed in the circuit is 100 W then in the above question, the capacitive reactance in the circuit is

A. 100Ω

B. 25Ω


C. $\sqrt{125 \times 75}\Omega$

D. 400Ω

Answer: C

 [Watch Video Solution](#)

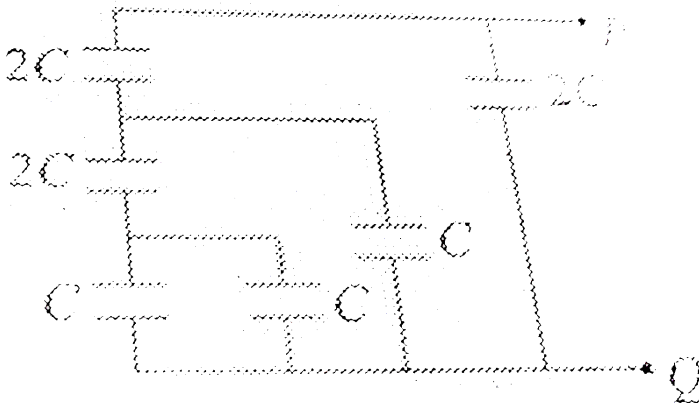29. The resultant capacitance of given circuit is



A. $\frac{100}{100\pi} f$

B. $\frac{25}{100\pi} F$

C. $\frac{\sqrt{125 \times 75}}{100\pi} F$

D. $\frac{1}{100\pi\sqrt{125 \times 75}} F$

Answer: D



Watch Video Solution

30. In a series LCR circuit the voltage across the resistance, capacitance and inductance is 10V each. If the capacitance is short circuited, the voltage across the inductance will be

A. (A) 10 V

B. (B) $10 / (\sqrt{2}) V$

C. (C) $(10/3) V$

D. (D) $20V$

Answer: B



Watch Video Solution

31. An ideal choke takes a current of 10 A when connected to an ac supply of 125 V and 50 Hz. A pure resistor under the same conditions takes a current of 12.5 A. If the two are connected to an ac supply of 100 V and 40 Hz, then the current in series combination of above resistor and inductor is

A. (A) $10/\sqrt{2}A$

B. (B) 12.5 A

C. (C) 20A

D. (D) 10A

Answer: A



Watch Video Solution

32. A direct current of 5 amp is superimposed on an alternating current $I = 10 \sin \omega t$ flowing through a wire. The effective value of the resulting current will be:

A. (A) $(15/2)A$

B. (B) $5\sqrt{3}A$

C. (C) $5\sqrt{5}A$

D. (D) $15A$


Answer: B



Watch Video Solution

33. In the circuit of fig, the source frequency is $\omega = 2000 \text{ rad s}^{-1}$.

The current in the will be

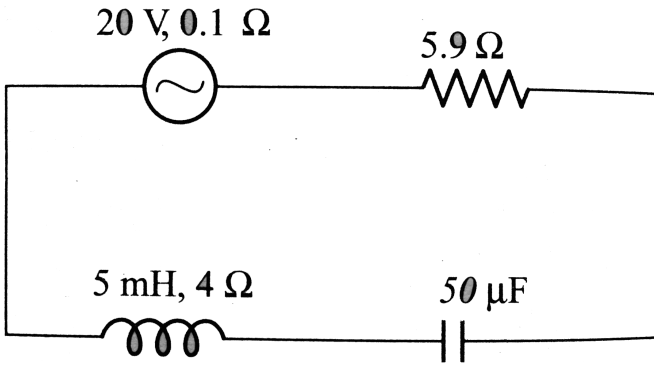

- A. (A) $2A$
- B. (B) $3.3A$
- C. (C) $2/\sqrt{5}A$
- D. (D) $\sqrt{5}A$

Answer: A



Watch Video Solution


34. 110 V_{rms} is applied across a series circuit having resistance 11Ω and impedance 22Ω . The power consumed is

- A. (A) $275W$
- B. (B) $366W$
- C. (C) $550W$
- D. (C) $1100W$

Answer: A

 [Watch Video Solution](#)

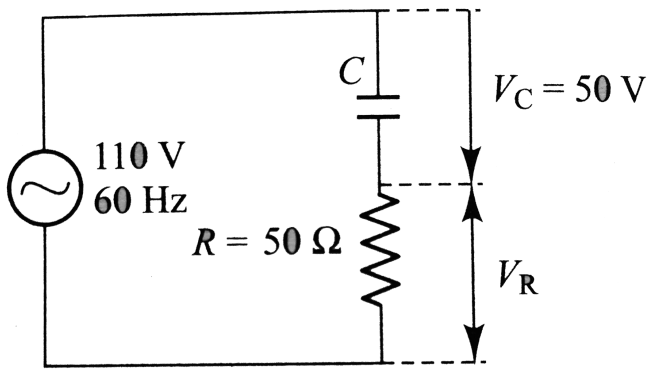35. In the circuit given in fig. $(V_C) = 50V$ and $R = 50\Omega$. The values of C and (V_R) are



- A. (A) 3.3 mF , 60 V
- B. (B) $104 \mu\text{F}$, 98 V
- C. (C) $52 \mu\text{F}$, 98 V
- D. (D) $2 \mu\text{F}$, 60 V

Answer: B



Watch Video Solution

36. A 220-V, 50 Hz, ac generator is connected to an inductor and a 50Ω resistance in series. The current in the circuit is $1.0A$. What is the PD across inductor?

A. (A) $102.2V$

B. (B) $186.4V$

C. (C) $214V$

D. (D) $170V$

Answer: C



[Watch Video Solution](#)

37. An $8(\mu)F$ capacitor is connected across a $220\sqrt{2}$ V, 50 Hz line.

What is the peak value of charge through the capacitor?

A. (A) $2.5 \times 10^{-3} C$

B. (B) $2.5 \times 10^{-4} C$

C. (C) $5 \times 10^{-5} C$

D. (D) $7.5 \times 10^{-2} C$

Answer: A



Watch Video Solution

38. A DC ammeter and an AC thermal ammeter are connected to a circuit in series. When a direct current is passed through the circuit, the DC ammeter shows $i_1 = 6A$. When a sinusoidal alternating current flows through the circuit, the DC ammeter shows $i_2 = 8A$. If both i_1 and i_2 are passed through the circuit

A. dc=6 A, ac=10A

B. $dc=3$ A, $ac=5$ A

C. $dc=5$ A, $ac=8$ A

D. $dc=2$ A, $ac=3$ A

Answer: A



Watch Video Solution

39. Current in an AC circuit is given by $i = 3 \sin \omega t + 4 \cos \omega t$,

then

A. $\frac{I_1 + I_2}{2}$

B. $\left(\frac{I_1 + I_2^2}{\sqrt{2}} \right)$


C. $\sqrt{\frac{I_1^2 + I_2^2}{2}}$

D. $\frac{I_1^2 + I_2^2}{2}$

Answer: C

 Watch Video Solution

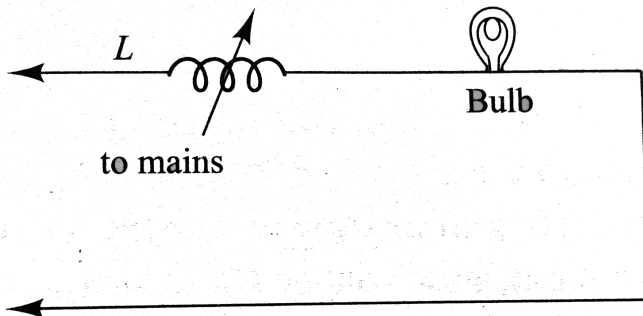40. A typical light dimmer used to dim the stage lights in a theater consists of a variable inductance for L (where inductance is adjustable between zero and L_{\max}) connected in series with a light bulb B as shown in fig. the mains electrical supply is 220 V at 50 Hz, the light bulb is rated at 220 V, 1100 W. What (L_{\max}) is required if the rate of energy dissipated in the light blub is to be varied by a factor of 5 from its upper limits of 1100 W?



A. (A) 0.69H

B. (B) 0.28 H

C. (C) 0.38 H

D. (D) 0.56 H

Answer: B

 [Watch Video Solution](#)

41. Two alternating voltage generators produce emfs of the same amplitude(E_0) but with a phase difference of $(\pi)/3$. The resultant emf is

A. (A) $E_0 \sin[\omega t + (\pi)/3]$

B. (B) $E_0 \sin[\omega t + (\pi)/6]$


C. (C) $\sqrt{3}E_0 \sin[\omega t + (\pi)/6]$

D. (D) $\sqrt{3}E_0 \sin[\omega t + (\pi) / 2]$

Answer: C

 Watch Video Solution

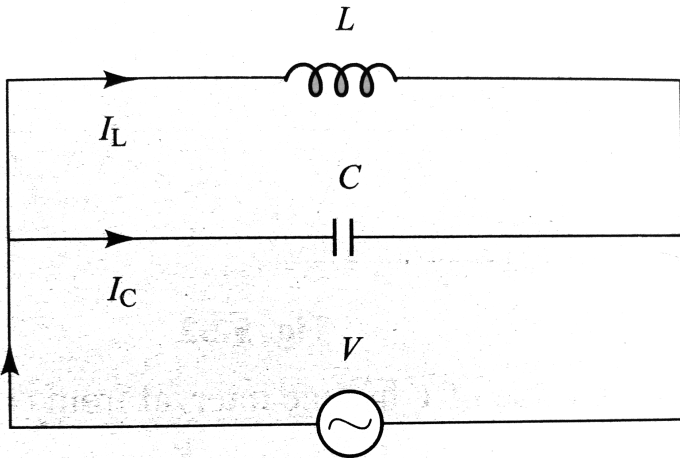42. For the circuit shown in fig, current in inductance is 0.8A while that in capacitance is 0.6 A. What is the current drawn from the source?



A. $0.1A$

B. $0.3A$


C. $0.6A$

D. $0.2A$

Answer: D

 [Watch Video Solution](#)

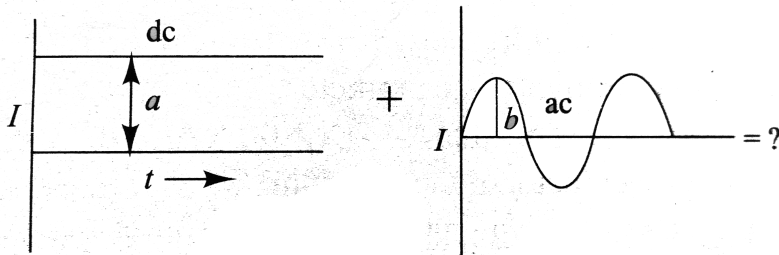43. If a direct current of value a ampere is superimposed on an alternative current $I = b \sin \omega t$ flowing through a wire, what is the effective value of the resulting current in the circuit?



A. $\left[a^2 - \frac{1}{2}b^2 \right]^{1/2}$

B. $[a^2 + b^2]^{1/2}$

C. $\left[\frac{a^2}{2} + b^2 \right]^{1/2}$


D. $\left[a^2 + \frac{1}{2}b^2 \right]^{1/2}$

Answer: D



Watch Video Solution

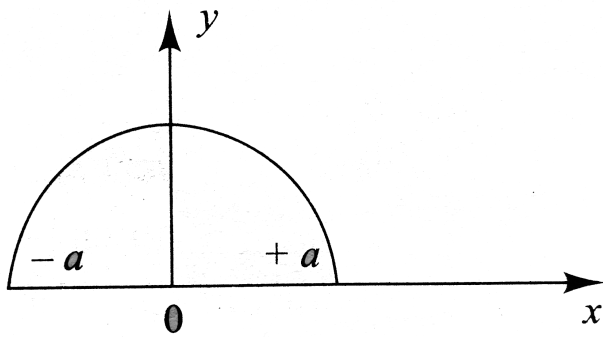44. Determine the rms value of a semi-circular current wave which has a maximum value of a .



- A. $(1/\sqrt{2})a$
- B. $\sqrt{(3/2)}a$
- C. $\sqrt{(2/3)}a$
- D. $(1/\sqrt{3})a$

Answer: C



Watch Video Solution

45. An alternating voltage $E = 200\sqrt{2}\sin(100t)$ is connected to a μ F capacitor through an AC ammeter. The reading of the ammeter shall be


- A. 10mA
- B. 5mA
- C. $5\sqrt{2}\text{mA}$
- D. $10\sqrt{2}\text{mA}$

Answer: B



Watch Video Solution

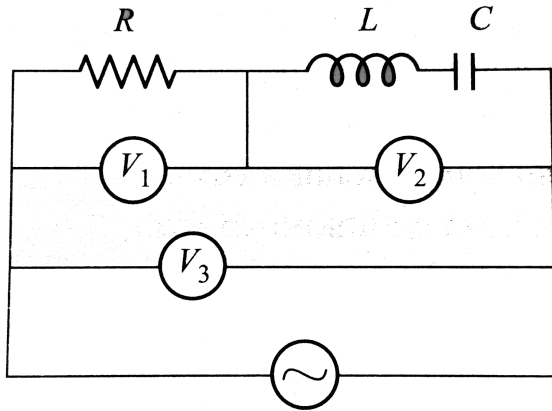46. Which voltmeter will give zero reading at resonance?



- A. (V_1)
- B. (V_2)
- C. (V_3)
- D. None

Answer: B

 [Watch Video Solution](#)

47. A 50 W, 100V lamp is to be connected to an ac mains of 200V, 50 Hz. What capacitor is essential to be put in series with the lamp?

- A. $\frac{25}{\sqrt{2}} (\mu) F$
- B. $\frac{50}{\pi\sqrt{2}} (\mu) F$
- C. $\frac{50}{\sqrt{2}} (\mu) F$
- D. $\frac{100}{\pi\sqrt{3}} (\mu) F$

Answer: B



Watch Video Solution

48. A capacitor of $10(\mu)F$ and an inductor of 1 H are joined in series. An ac of 50 Hz is applied to this combination. What is the impedance of the combination?

A. $\frac{5(\pi^2 - 5)}{\pi} \Omega$

B. $\frac{10(10 - \pi^2)}{\pi} \Omega$

C. $\frac{10(\pi^2 - 5)}{\pi} \Omega$


D. $\frac{5(10 - \pi^2)}{\pi} \Omega$

Answer: B



Watch Video Solution

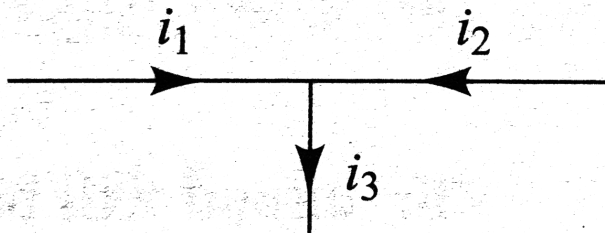49. If $i_1 = 3 \sin \omega t$ and $(i_2) = 4 \cos \omega t$, then (i_3) is



A. $5 \sin(\omega t + 53^\circ)$

B. $5 \sin(\omega t + 37^\circ)$

C. $5 \sin(\omega t + 45^\circ)$

D. $5 \sin(\omega t + 35^\circ)$


Answer: A



Watch Video Solution

50. When an AC source of emf $E = E_0 \sin(100t)$ is connected across a circuit, the phase difference between the emf E and the current I is observed to be $\frac{\pi}{4}$, as shown in the figure. If the circuit consists possibly only of R-C or R-L in series, which of the

following combinations is possible?

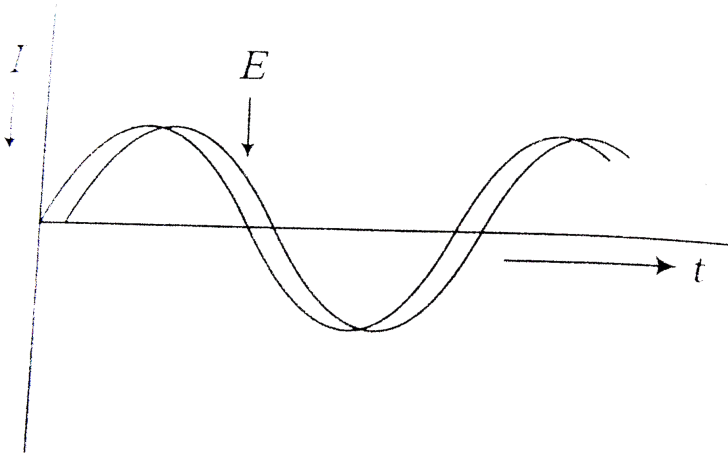

- A. $R = 1k\Omega, C = 10(\mu)F$
- B. $R = 1k\Omega, C = 1(\mu)F$
- C. $R = 1k\Omega, L = 10(\mu)F$
- D. $R = 1k\Omega, L = 1(\mu)F$

Answer: A



Watch Video Solution

51. In an ac circuit the potential differences across an inductance and resistance joined in series are, respectively, 16 V and 20 V. The total potential difference across the circuit is

- A. 20 V
- B. 25.6 V
- C. 31.9 V
- D. 53.5 V

Answer: B



[Watch Video Solution](#)

52. Current in an ac circuit is given by $I = 3 \sin \omega t + 4 \cos \omega t$, then

A. rms value of current is 5A.

B. mean value of this current in any one half period will be $(6/\pi)$.

C. If voltage applied is $V = V_m \sin \omega t$, then the circuit may be containing resistance and capacitance only.


D. If voltage applied is $V = V_m \sin \omega t$, then the circuit may be contain resostamce and inductance only.

Answer: C

 [Watch Video Solution](#)

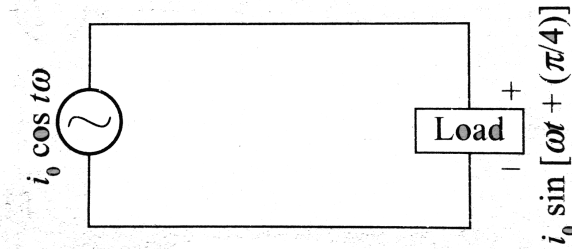53. A current source sends a current $I = (i_0)\cos(\omega t)$, When connected across an unknown load, it gives a voltages output of $v = v_0 \sin[\omega t + (\pi/4)]$ across that load. Then the voltage across

the current source may be brought in phase with the current through it by




- A. Connecting an inductor in series with the load
- B. Connecting an capacitor in series with the load
- C. Connecting an inductor in parallel with the load
- D. Connecting an capacitor in parallel with the load

Answer: A



Watch Video Solution

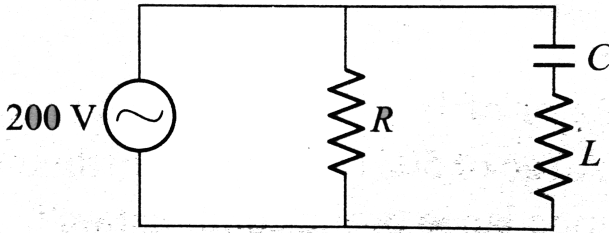54. In the circuit shown in fig. $X_C = 100\Omega$, $(X_L) = 200\Omega$ and $R = 100\Omega$. The effective current through the source is



- A. $2A$
- B. $2\sqrt{2}A$
- C. $0.5A$
- D. $\sqrt{0.4}A$

Answer: B



Watch Video Solution

55. For an LCR series circuit with an aac source of angular frequency ω .

A. circuit will be capacitive if $\omega > \frac{1}{\sqrt{LC}}$

B. circuit will be inductive if $\omega = \frac{1}{\sqrt{LC}}$

C. Power factor of circuit will be unity if capacitive reactance equals inductive reactance

D. circuit will be leading voltage if $\omega > \frac{1}{\sqrt{LC}}$

Answer: C



Watch Video Solution

56. The value of current in two series LCR circuits at resonance is same, then

- A. both circuits must be having same value of capacitance and inductance
- B. in both circuits ratio of L and C will be same
- C. for both the circuits $(X_L)/(X_C)$ must be same at that frequency
- D. both circuits must have same impedance at all frequencies

Answer: C



Watch Video Solution

57. In series L-C-R circuit voltage drop across resistance is 8 V and across inductor is 6 V and across capacitor is 12 V . Then

- A. voltage of the source will be leading current in the circuit
- B. voltage drop across each element will be less than the applied voltage.
- C. power factor of circuit will be $4/3$
- D. none of these.

Answer: D




[Watch Video Solution](#)

58. In a black box of unknown elements (L or R or any other combination), an ac voltage $E = E_0 \sin(\omega t) + \phi$ is applied and current in the circuit was found to be

$I = (I_0)\sin[\omega t + \phi + (\pi/4)]$. Then the unknown elements in the

box may be

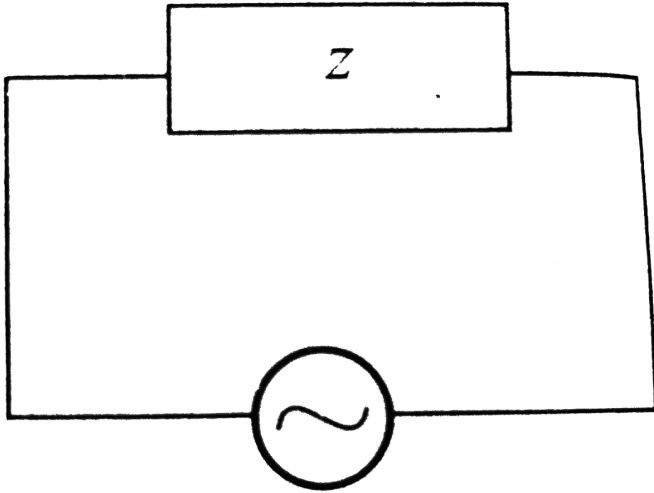

A. only capacitor

B. inductor and resistor both


C. either capacitor, resistor, and inductor or only capacitor
and resistor

D. only resistor

Answer: C

 Watch Video Solution

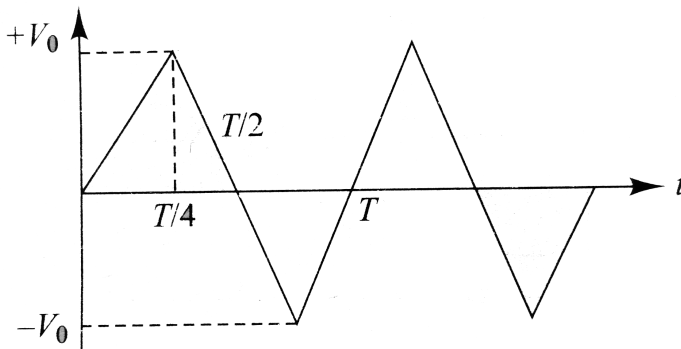59. The voltage time (V-t) graph for triangular wave having peak value (V_0) is as shown in fig. The *rms* value V in time interval $t = 0$ to $t = T/4$ is



A. $\frac{V_0}{\sqrt{3}}$

B. $\frac{V_0}{2}$


C. $\frac{V_0}{\sqrt{2}}$

D. none of these.

Answer: A

 [Watch Video Solution](#)

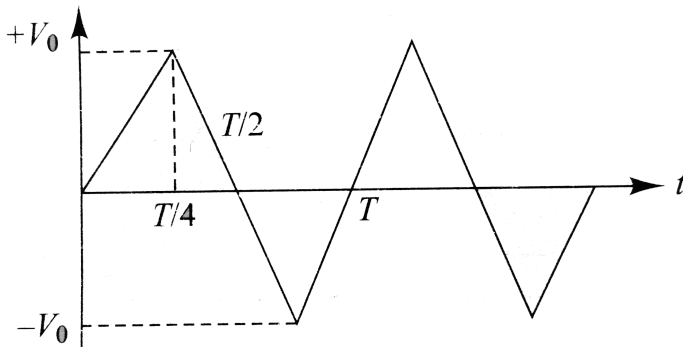60. The average value of voltage (V) in one time period will be



A. $\frac{V_0}{\sqrt{3}}$

B. $\frac{V_0}{2}$

C. $\frac{V_0}{\sqrt{2}}$

D. 0

Answer: D



[Watch Video Solution](#)

61. What reading would you expect of a square-wave current, switching rapidly between +0.5 A and -0.5 A, when passed through an ac ammeter?

A. 0

B. 0.5A

C. 0.25A


D. 1.0A

Answer: B

 Watch Video Solution

62. The power factor of the circuit is $\frac{1}{\sqrt{2}}$. The capacitance of the circuit is equal to

$$2 \sin(1000t)$$

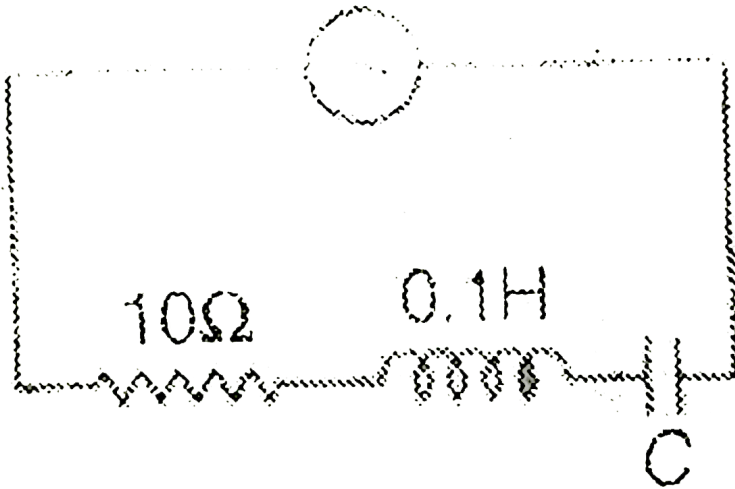

A. $400(\mu)F$

B. $300(\mu)F$

C. $500(\mu)F$

D. $200(\mu)F$

Answer: C



Watch Video Solution

63. In an ideal transformer, the voltage and the current in the primary coil are 200V and 2 A, respectively. If the voltage in the secondary coil is 200 V, then the value of current in the secondary coil will be

A. 0.2A

B. 2A

C. 10A


D. 20A

Answer: A

 Watch Video Solution

Exercises Multiple Correct

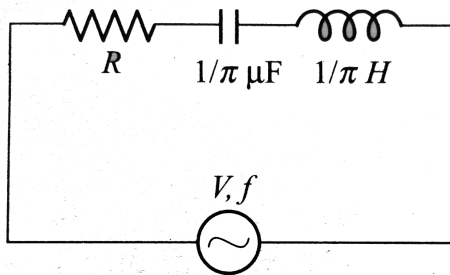1. In an ac circuit shown in fig , the supply voltage has a constant rms value v but variable frequency f . At resonance, the circuit



A. has current I given by $I = \frac{V}{R}$

B. has a resonance frequency $\nu = 500 \text{ Hz}$

C. has a voltage across the capacitor which is 180° out of phase with that across the inductor

D. Has a current given by
$$I = \frac{V}{\sqrt{R^2 + \left(\frac{1}{\pi} + \frac{1}{\pi}\right)^2}}$$

Answer: A::C

 [Watch Video Solution](#)

2. Resonance occurs in a series LCR circuit when the frequency of the applied emf is 1000 Hz.

A. when frequency = 900Hz then the current through the voltage source will be ahead of emf of the source

B. the impedance of the circuit is minimum at $f = 1000\text{Hz}$

C. at only resonance the voltages across L and C differ in phase by 180°

D. if the value of C is double, resonance occurs at $f = 2000\text{Hz}$

Answer: A::B

 [Watch Video Solution](#)

3. Which of the following statements is true? Heat produced in a current carrying conductor depends upon

A. the time for which the current flows in the conductor

B. the resistance of the conductor

C. the strength of the current

D. the nature of current

Answer: A::C::D



Watch Video Solution

4. A choke coil of resistance 5Ω and inductance 0.6 H is in series with a capacitance of $10(\mu)F$. If a voltage of 200 V is applied and the frequency is adjusted to resonance, the current and voltage across the inductance and capacitance are (I_0) , (V_0) and (V_1) respectively. we have

A. $(I_0) = 40A$

B. $(V_0) = 9.8kV$


C. $(V_1) = 9.8kV$

D. $(V_1) = 19.6kV$

Answer: A::B::C



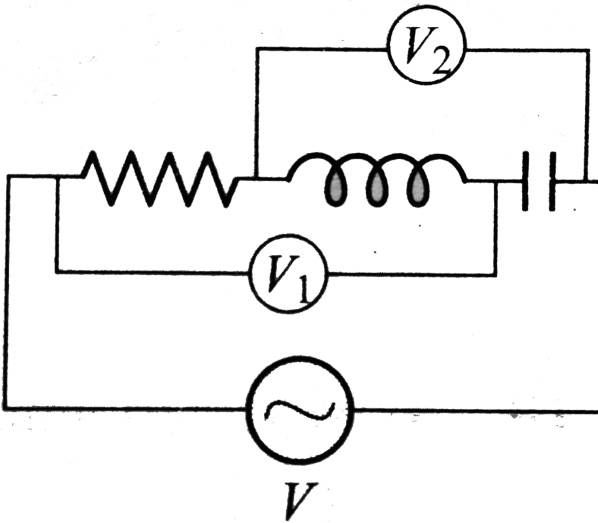5. In an RLC series circuit shown in fig. the reading of voltmeters (V_1) and (V_2) are 100 V and 200 V respectively. The source voltage is 130 V. for this situation, mark out the correct statements (s).



A. Voltage across resistor inductor and capacitor are 50 V

$50\sqrt{3}V$, and $120 + 50\sqrt{3} V$, respectively

B. Voltage across resistor inductor and capacitor are 50 V

$50\sqrt{3}V$, and $120 - 50\sqrt{3}V$, respectively

C. Power factor of the circuit is $\frac{5}{13}$

D. The circuit is capacitive in nature

Answer: A::C::D



Watch Video Solution

Exercises Assertion Reasoning

1. Statement 1: In the purely resistive element of a series LCR, ac circuit the maximum value of rms current increase with increase in the angular frequency of the applied emf.

Statement 2: $I_{\max} = \frac{\varepsilon_{\max}}{Z}$, $Z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$,

where (I_{\max}) is the peak current in a cycle.

- A. Statement 1 is true, statement 2 is true, Statement 2 is the correct explanation for statement 1.
- B. Statemet 1 is True, Statement 2 is true , Statement 2 is NOT the correct explanation for Statement 1
- C. Statement 1 is True, Statement 2 is False.
- D. Statement 1 is False, Statement 2 is true

Answer: D



[Watch Video Solution](#)

2. Statement 1: In a series LCR circuit at resonance condition power consumed by circuit is maximum.

Statement 2 : At resonance condition, the effective resistance of circuit is maximum.


- A. Statement 1 is true, statement 2 is true, Statement 2 is the correct explanation for statement 1.
- B. Statemet 1 is True, Statement 2 is true , Statement 2 is NOT the correct explanation for Statement 1
- C. Statement 1 is True, Statement 2 is False.
- D. Statement 1 is False, Statement 2 is true

Answer: C

 [Watch Video Solution](#)

3. Statement 1: KVL rule is also being applied in ac circuit shown in fig. (V_C) in the circuit =2V

Statement 2:vc in the ckt is 2 volt

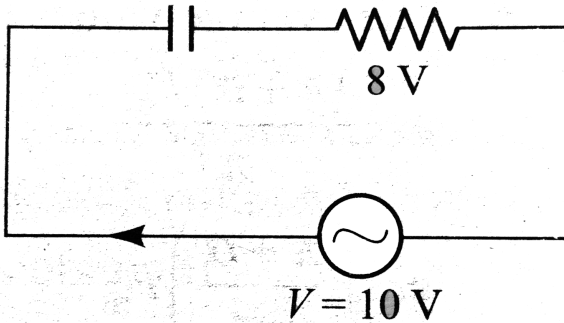

- A. Statement 1 is true, statement 2 is true, Statement 2 is the correct explanation for statement 1.
- B. Statement 1 is True, Statement 2 is true , Statement 2 is NOT the correct explanation for Statement 1
- C. Statement 1 is True, Statement 2 is False.
- D. Statement 1 is False, Statement 2 is true

Answer: C



Watch Video Solution

4. An inductor, a capacitor, and a resistor are connected in series.

The combination is connected across an ac source.

Statement 1: Peak current through each remains same.

Statement 2: Average power delivered by source is equal to average power developed across resistance.

- A. Statement 1 is true, statement 2 is true, Statement 2 is the correct explanation for statement 1.
- B. Statement 1 is True, Statement 2 is true , Statement 2 is NOT the correct explanation for Statement 1
- C. Statement 1 is True, Statement 2 is False.
- D. Statement 1 is False, Statement 2 is true

Answer: B



5. Assertion : An alternating current does not show any magnetic effect.

Reason : Alternating current does not vary with time.

- A. Statement 1 is true, statement 2 is true, Statement 2 is the correct explanation for statement 1.
- B. Statement 1 is True, Statement 2 is true , Statement 2 is NOT the correct explanation for Statement 1
- C. Statement 1 is True, Statement 2 is False.
- D. Statement 1 is False, Statement 2 is true

Answer: B



6. Statement 1: Both dc and ac can be measured by a hot wire instrument.

Statement 2: the hot wire instrument is based on the principle of magnetic effect of current.

- A. Statement 1 is true, statement 2 is true, Statement 2 is the correct explanation for statement 1.
- B. Statemet 1 is True, Statement 2 is true , Statement 2 is NOT the correct explanation for Statement 1
- C. Statement 1 is True, Statement 2 is False.
- D. Statement 1 is False, Statement 2 is true


Answer: C



Watch Video Solution

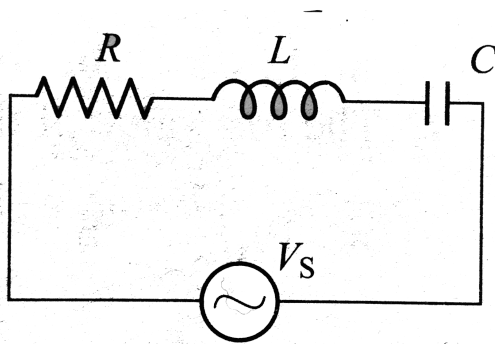7. Statement 1: In a series RLC circuit if (V_R) , (V_L) and (V_C) denote rms voltage across R,L and C respectively and (V_S) is the rms voltage across the source. Then $(V_s) = (V_R) + (V_L) + (V_C)$

Statement 2: In ac circuit, Kirchhoff's voltage law is correct at every instant of same.



A. Statement 1 is true, statement 2 is true, Statement 2 is the correct explanation for statement 1.

B. Statemet 1 is True, Statement 2 is true , Statement 2 is NOT the correct explanation for Statement 1

C. Statement 1 is True, Statement 2 is False.

D. Statement 1 is False, Statement 2 is true

Answer: D



Watch Video Solution

Exercises Linked Comprehension

1. If the voltage in an ac circuit is represented by the equation

$$V = 220\sqrt{2}\sin(314t - \phi), \text{ calculate}$$

rms value of the voltage

A. 220 V

B. 314 V

C. $220\sqrt{2}V$

D. $200 / \sqrt{2}V$

Answer: A



[Watch Video Solution](#)

2. If the voltage in an ac circuit is represented by the equation

$$V = 220\sqrt{2} \sin(314t - \phi), \text{ calculate}$$

average voltage

A. 220 V

B. $622 / (\pi V)$

C. $220 / \sqrt{2}V$

D. $200\sqrt{2}V$

Answer: B



[Watch Video Solution](#)

3. If the voltage in an ac circuit is represented by the equation

$$V = 220\sqrt{2}\sin(314t - \phi), \text{ calculate}$$

frequency of ac

A. $50Hz$

B. $50\sqrt{2}Hz$

C. $50 / \sqrt{2}Hz$

D. $75Hz$


Answer: A



[Watch Video Solution](#)

4. The half cycle of an alternating signal is shown in fig. It increases uniformly from zero at $0^\circ \rightarrow F_m \sin(\alpha)^\circ$ and decrease

uniformly from (F_m) at 180°

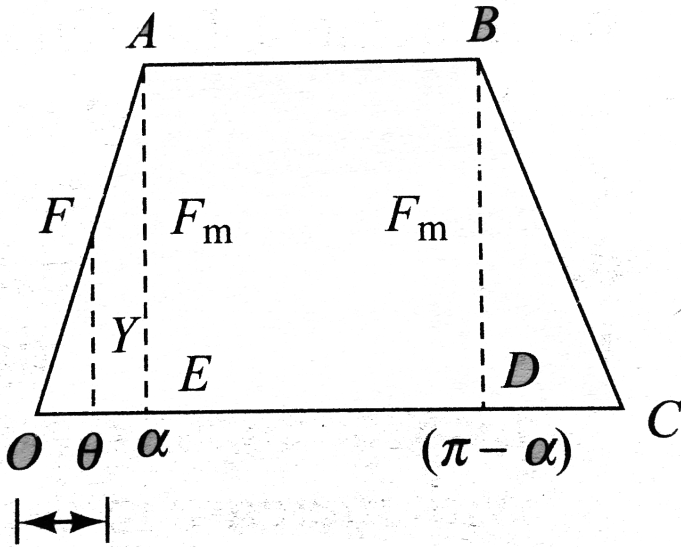

The effective value of the signal is

A. $F_m \sqrt{\left(1 - \frac{4\alpha}{3\pi}\right)}$


B. $F_m \sqrt{\left(1 + \frac{4\alpha}{3\pi}\right)}$

C. $F_m \sqrt{\left(1 - \frac{3\alpha}{4\pi}\right)}$

D. $F_m \sqrt{\left(1 + \frac{3\alpha}{4\pi}\right)}$

Answer: A

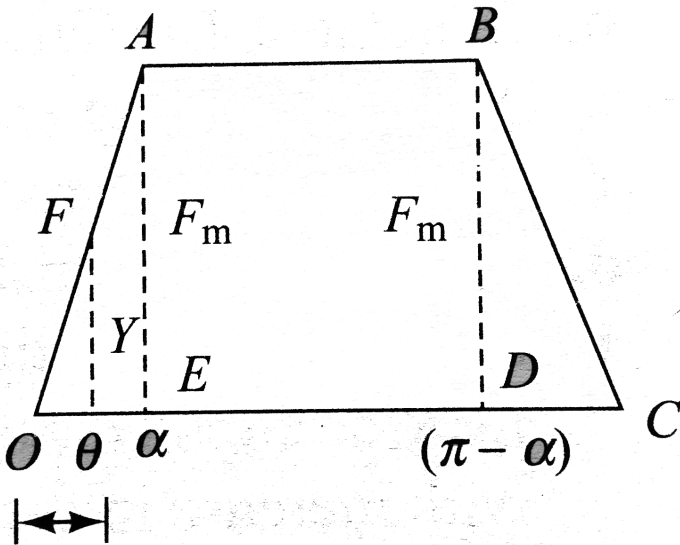5. The half cycle of an alternating signal is shown in fig. It increases uniformly from zero at $0^\circ \rightarrow F_m$ at $(\alpha)^\circ$ and decrease uniformly from (F_m) at 180°



The average value of the signal is

A. $\frac{(\pi + \alpha)F_m}{\pi}$


B. $\frac{(\pi - \alpha)F_m}{\pi}$

C. $\left(\frac{\pi + \alpha}{3\pi}\right) F_m$

D. $\left(\frac{2\pi + \alpha}{2\pi}\right) F_m$

Answer: B

 Watch Video Solution

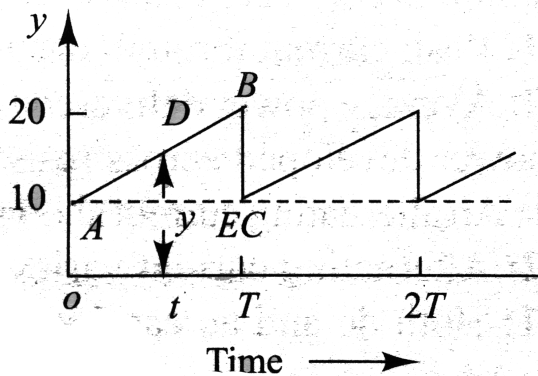

6.

the average value of the wave-form shown in fig. is

A. $15\sqrt{2}$


B. $10\sqrt{2}$

C. 10

D. 15

Answer: D

 Watch Video Solution

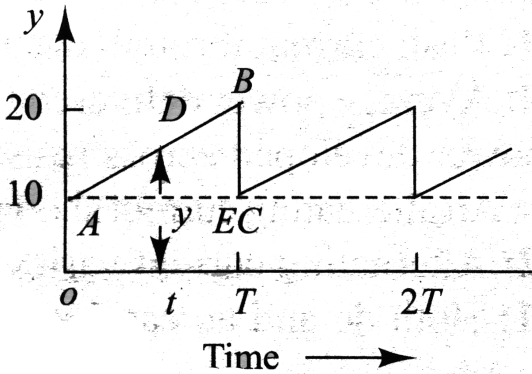

7.

The rms value of the signal is

A. $10\sqrt{\frac{7}{3}}$

B. $\frac{10}{\sqrt{3}}$

C. $10\sqrt{7}$

D. $10\sqrt{3}$

Answer: A

 [Watch Video Solution](#)

8. A 0.21 H inductor and a 12Ω resistance are connected in series to a 220 V, 50 Hz ac source.

The current in the circuit is

A. $\frac{220}{\sqrt{4400}} A$

B. $\frac{22}{3\sqrt{5}} A$

C. $\frac{220}{\sqrt{4600}} A$

D. $\frac{22}{5\sqrt{3}} A$

Answer: B



Watch Video Solution

9. A 0.21 H inductor and a 12Ω resistance are connected in series to a 220 V , 50 Hz ac source.

the phase angle between the current and the source voltage is

A. $\tan^{-1}\left(\frac{7\pi}{4}\right)$

B. $\cos^{-1}\left(\frac{7\pi}{4}\right)$

C. $\tan^{-1}\left(\frac{4\pi}{7}\right)$

D. $\cos^{-1}\left(\frac{4\pi}{7}\right)$

Answer: A



Watch Video Solution

10. When 100 V DC is applied across a solenoid , a current of 1 A flows in it. When 100 V AC is applied across the same solenoid the current drops to 0.5A . If the frequency of the AC source is 50 Hz , the impedance and inductance of the solenoid are

A. 200Ω

B. 50Ω

C. 100Ω

D. $50\sqrt{3}\Omega$

Answer: A



[Watch Video Solution](#)

11. When 100 V DC is applied across a solenoid , a current of 1 A flows in it. When 100 V AC is applied across the same solenoid the


current drops to 0.5A . If the frequency of the AC source is 50 Hz ,
the impedance and inductance of the solenoid are

- A. 5.5 H
- B. $3/(\pi)H$
- C. $\sqrt{3}/(\pi)H$
- D. 2.5H

Answer: C

 [Watch Video Solution](#)

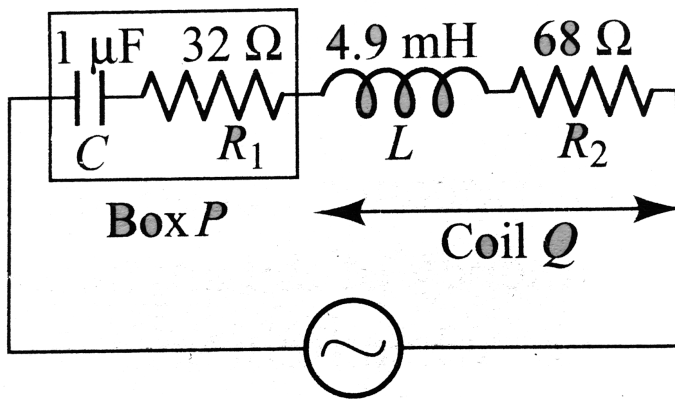12. A box P and a coil Q are connected in series with an ac source of variable frequency. The emf of the source is constant at 10 V. Box P contains a capacitance of 32Ω . Coil Q has a self inductance of 4.9 mH and a resistance of 68Ω in series. The frequency is adjusted so that maximum current flows in P and Q.




The impedance of P at this frequency is

- A. $77\ \Omega$
- B. $36\ \Omega$
- C. $40\ \Omega$
- D. $125\ \Omega$

Answer: A

 [Watch Video Solution](#)

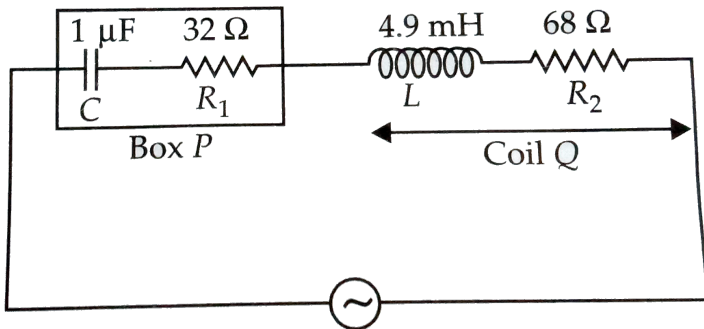13. A box P and a coil Q are connected in series with an ac source of variable frequency. The emf of source is constant at 10 V. Box P contains a capacitance of $1\mu F$ in series with a resistance of 32Ω . Coil Q has self inductance $4.9mH$ and a resistance 68Ω in series. The frequency is adjusted so that the maximum current flows in P and Q . At this frequency the voltage across P and Q respectively




- A. 200Ω
- B. $\sqrt{1350}\Omega$
- C. 55Ω
- D. $\sqrt{9524}\Omega$

Answer: D

 Watch Video Solution

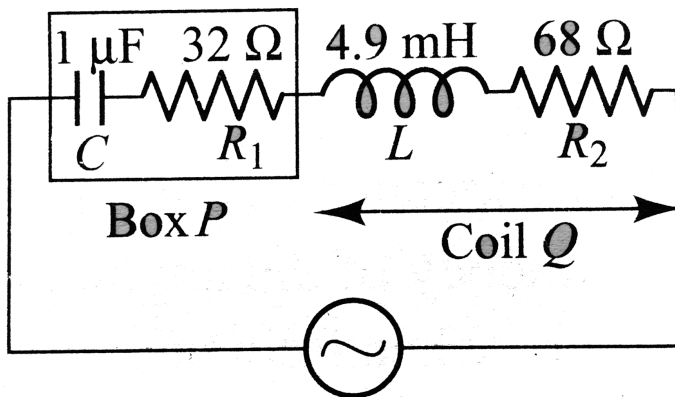14. A box P and a coil Q are connected in series with an ac source of variable frequency. The emf of the source is constant at 10 V. Box P contains a capacitance $1\mu\text{f}$ and a resistance of 32Ω . Coil Q has a self inductance of 4.9 mH and a resistance of 68Ω in series. The frequency is adjusted so that maximum current flows in P and Q. and Q.



The voltage across P is

A. 12 V

B. 7.7 V

C. 10 V

D. 24 V


Answer: B



Watch Video Solution

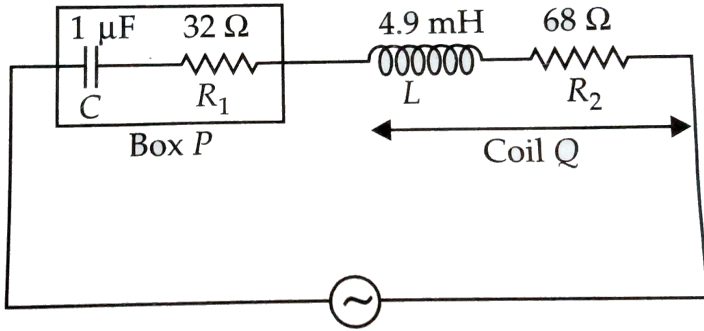15. A box P and a coil Q are connected in series with an ac source of variable frequency. The emf of source is constant at 10 V. Box P contains a capacitance of $1\mu F$ in series with a resistance of 32Ω . Coil Q has self inductance $4.9mH$ and a resistance 68Ω in series. The frequency is adjusted so that the maximum current flows in P

and Q . At this frequency the voltage across P and Q respectively



A. 20 V

B. $\frac{\sqrt{1350}}{10} V$

C. 5.5V

D. $\frac{\sqrt{9524}}{10} V$

Answer: D



Watch Video Solution

16. A series LCR circuit containing a resistance of 120Ω has angular resonance frequency $4 \times 10^5 \text{ rads}^{-1}$. At resonance the voltage across resistance and inductance are 60V and 40 V, respectively,

the value of inductance L is

A. 0.1mH

B. 0.2mH

C. 0.35mH

D. 0.4mH

Answer: B



Watch Video Solution

17. A series LCR circuit containing a resistance of 120Ω has angular resonance frequency $4 \times 10^5 \text{ rads}^{-1}$. At resonance the voltage across resistance and inductance are 60V and 40 V, respectively,

The value of capacitance C is

A. $\frac{1}{32}(\mu)F$

B. $\frac{1}{16}(\mu)F$

C. $32(\mu)F$

D. $16(\mu)F$

Answer: A



[Watch Video Solution](#)

18. A series LCR circuit containing a resistance of 120Ω has angular resonance frequency $4 \times 10^5 \text{ rad s}^{-1}$. At resonance the voltage across resistance and inductance are 60 V and 40 V respectively. The angular frequency at which current in the circuit lags the voltage by 45° is

A. $4 \times 10^5 \text{ rads}^{-1}$

B. $3 \times 10^5 \text{ rads}^{-1}$

C. $8 \times 10^5 \text{ rads}^{-1}$

D. $2 \times 10^5 \text{ rads}^{-1}$

Answer: C



Watch Video Solution

19. When 100 volt DC source is applied across a coil, a current of 1A flows through it. When 100V AC source of 50Hz is applied to the same coil, only 0.5A current flows. Calculate the inductance of the coil

A. 0.02H

B. 0.04H

C. 0.08H

D. 1.0H

Answer: C



[Watch Video Solution](#)

20. When 100 volt DC source is applied across a coil, a current of 1A flows through it. When 100V AC source of 50Hz is applied to

the same coil, only 0.5 A current flows. Calculate the inductance of the coil

A. 17.28 W

B. 8.64 W

C. 10 W

D. 15 W

Answer: A



[Watch Video Solution](#)

21. An inductor 20×10^{-3} a capacitor $100(\mu)\text{ F}$ and a resistor 50Ω are connected in series across a source of emf $V = 10 \sin 314t$.

Then the energy dissipated in the circuit in 20 min is

A. 960 J

B. 900 J

C. 250J

D. 500J

Answer: A



Watch Video Solution

22. An inductor 20×10^{-3} a capacitor $100(\mu)F$ and a resistor 50Ω are connected in series across a source of emf $V = 10 \sin 314t$.

If resistance is removed from the circuit and the value of inductance is doubled, the variation of current with time in the new circuit is

A. $0.52 \cos 314t$

B. $0.52 \sin 314t$

C. $0.52 \sin(314t + \pi/3)$


D. none of these.

Answer: A



[Watch Video Solution](#)

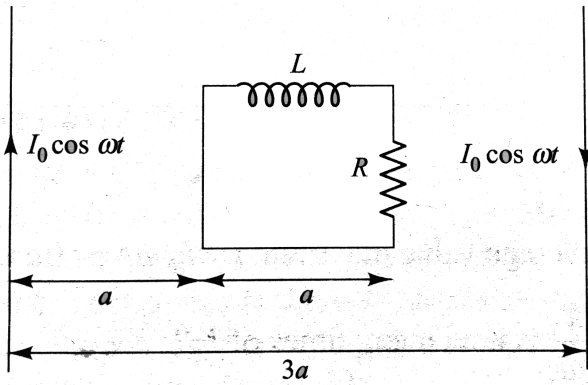23. In fig, a square loop consisting of an inductor of inductance L and resistor of resistance R is placed between two long parallel wires. The two long straight wires have time - varying current of magnitude $I = (I_0)\cos \omega t$ but the direction of current in them are opposite



Total magnetic flux in this loop is


- A. $\frac{\mu_0 I a}{\pi} \ln 2$
- B. $\frac{2\mu_0 I a}{\pi} \ln 2$
- C. $\frac{4\mu_0 I a}{\pi} \ln 2$
- D. $\frac{\mu_0 I a}{2\pi} \ln 2$

Answer: A



Watch Video Solution

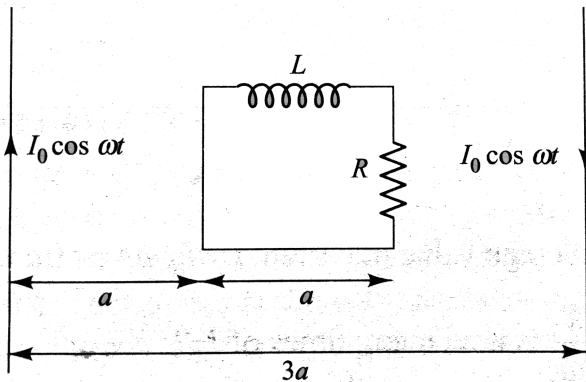24. In fig, a square loop consisting of an inductor of inductance L and resistor of resistance R is placed between two long parallel wires. The two long straight wires have time - varying current of magnitude $I = (I_0)\cos \omega t$ but the direction of current in them are opposite



Magnitude of emf in this circuit only due to flux change associated with two long straight current carrying wires will be

A. $\frac{\mu_0 a^2 n^2 I_0 \omega}{\pi} \sin \omega t$

B. $\frac{2\mu_0 a^2 n^2 I_0 \omega}{\pi} \sin \omega t$

C. $\frac{\mu_0 a 1 n 2 I_0 \omega}{2\pi} \cos \omega t$


D. $\frac{\mu_0 a 1 n 2 I_0 \omega}{\pi} \cos \omega t$

Answer: A

 [Watch Video Solution](#)

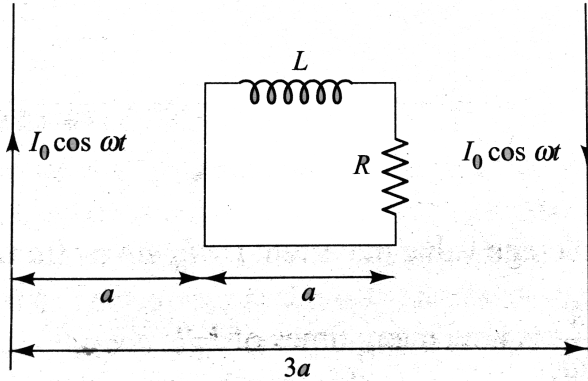25. In fig, a square loop consisting of an inductor of inductance L and resistor of resistance R is placed between two long parallel wires. The two long straight wires have time - varying current of magnitude $I = (I_0) \cos \omega t$ but the direction of current in them are opposite.

The instantaneous current in the circuit will be




- A. $\frac{2\mu_0 a n^2 I_0 \omega}{\pi \sqrt{R^2 + \omega^2 L^2}} \sin(\omega t - \phi)$
- B. $\frac{2\mu_0 a n^2 I_0 \omega}{\pi \sqrt{R^2 + \omega^2 L^2}} \sin(\omega t + \phi)$
- C. $\frac{2\mu_0 a n^2 I_0 \omega}{\pi \sqrt{R^2 + \omega^2 L^2}} \sin(\omega t)$
- D. $\frac{\mu_0 a n^2 I_0 \omega}{\pi \sqrt{R^2 + \omega^2 L^2}} \sin(\omega t - \phi)$

Answer: D



Watch Video Solution

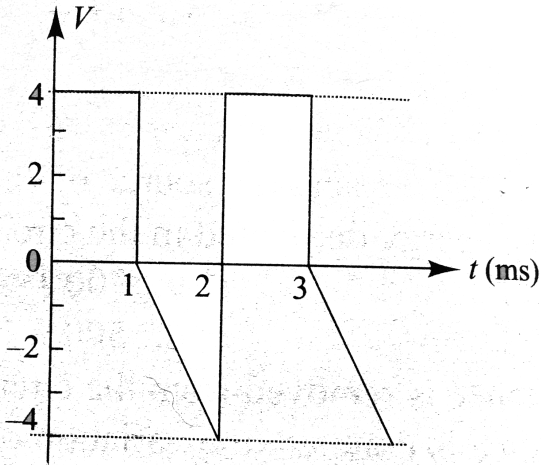1. Variation of voltage with time is shown in fig




(a) The rms voltage is found to be $N\sqrt{\frac{2}{3}}V$. Find N.

 Watch Video Solution

2. Find the average value of current (in A) shown graphically in fig.

From $t = 0 \rightarrow t = 2s$.

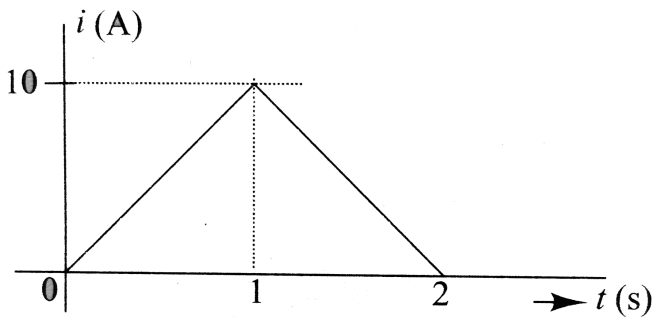

[Watch Video Solution](#)

3. The average value of current $i = I_m \sin \omega t$ from $t = \frac{\pi}{2\omega}$ to $t = \frac{3\pi}{2\omega}$ is how many times of (I_m) ?

[Watch Video Solution](#)

4. An AC ammeter is used to measure current in a circuit. When a given data current passes through the circuit, the AC ammeter reads 3 A. When another alternating current passes through the

circuit, the AC ammeter reads 4A. Then the reading of this ammeter simultaneously is



[Watch Video Solution](#)

Archives Subjective


1. In a series L-R circuit ($L = 35 \text{ mH}$ and $R = 11\Omega$), a variable emf source ($V = V_0 \sin \omega t$) of $V_{rms} = 220V$ and frequency 50 Hz is applied. The current amplitude in the circuit is



[Watch Video Solution](#)

Archives Single Correct

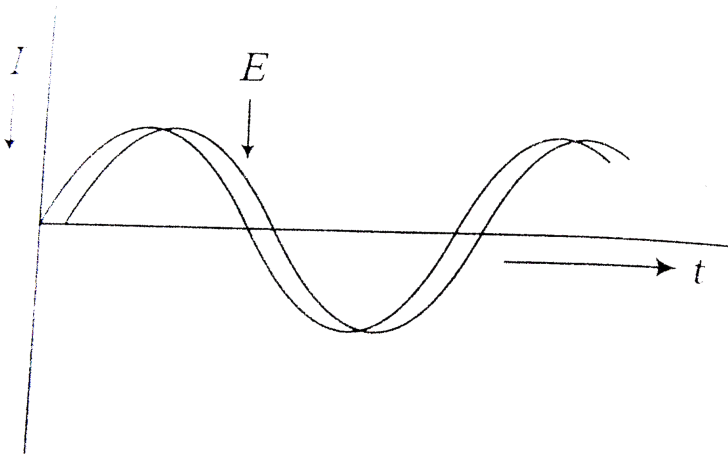1. When an AC source of emf $E = E_0 \sin(100t)$ is connected across a circuit, the phase difference between the emf E and the current I is observed to be $\frac{\pi}{4}$, as shown in the figure. If the circuit consists possibly only of R-C or R-L in series, which of the following combinations is possible?



- A. $R = 1k\Omega, C = 10(\mu)F$
- B. $R = 1k\Omega, C = 1(\mu)F$
- C. $R = 1k\Omega, L = 10H$
- D. $R = 1k\Omega, L = H$

Answer: A

 [Watch Video Solution](#)

2. An AC voltage source of variable angular frequency ω and fixed amplitude V connected in series with a capacitance C and an electric bulb of resistance R (inductance zero). When ω is increased

- A. the bulb glows dimmer
- B. the bulb glows brighter
- C. total impedance of the circuit is unchanged
- D. total impedance of the circuit increases

Answer: B

 [Watch Video Solution](#)

Archives Multiple Correct

1. A series R-C circuit is connected to AC source Consider two cases,(A) When C is without a dielectric medium and (b) When C is filled with dielectric of constant 4. The current I_R through the resistor and voltage V_C across the capacitor are compared in two cases. Which of the following is true?

A. $I_R^A > I_R^B$

B. $I_R^A < I_R^B$

C. $V_C^A > V_C^B$


D. $V_C^A < V_C^B$

Answer: B::C



[Watch Video Solution](#)

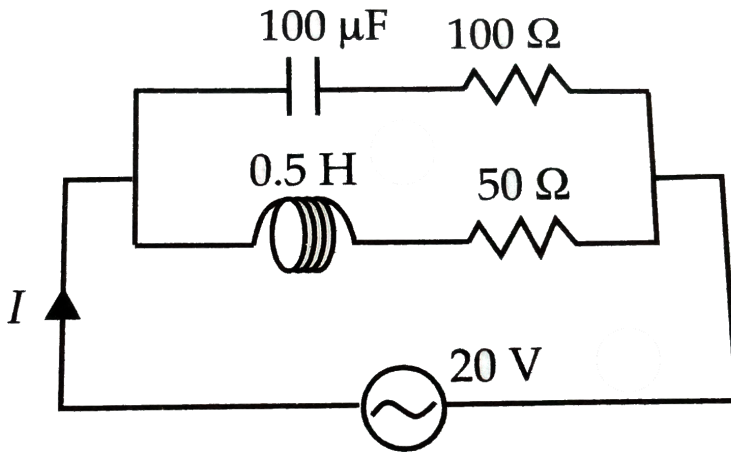2. In the given circuit, the AC source has $\omega = 100 \text{ rad/s}$. Considering the inductor and capacitor to be ideal, the correct choice is




- A. the current through the circuit, I is 0.3 A
- B. the current through the circuit, I is $0.3\sqrt{2} \text{ A}$
- C. the voltage across 100Ω resistor \rightarrow is $10\sqrt{2} \text{ V}$
- D. the voltage across 50Ω resistor \rightarrow is 10 V .

Answer: A::C



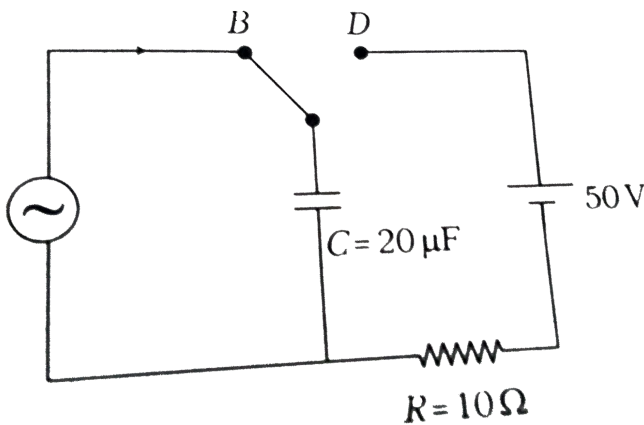3. At time $t = 0$, terminal A in the circuit shown in the figure is connected to B by a key and alternating current $I(t) = I_o \cos(\omega t)$, with $I_o = 1$ A and $\omega = 500 \text{ rad s}^{-1}$ starts flowing in it with the initial direction shown in the figure . At $t = 7\pi/6\omega$, the keys is switched from B to D . Now onwards only A and D are connected . A total charge Q flows from the battery to charge the capacitor fully. If $C = 20 \mu$, $R = 10 \Omega$ and the battery is deal with emf of 50 V , identify the correct statement(s).



A. Magnitude of the maximum charge on the capacitor before

$$t = \frac{7\pi}{6\omega} \text{ is } 1 \times 10^{-3} \text{ C}$$

B. The current in the left part of the circuit just before

$$t = \frac{7\pi}{6\omega} \text{ is clockwise.}$$

C. Immediately after A is connected to D, the current in R is 10

A.

$$D. Q = 2 \times 10^{-3} \text{ C}$$

Answer: C::D



[Watch Video Solution](#)

Archives Integer

1. A series R-C combination is connected to an AC voltage of angular frequency $\omega = 500$ radian/s. If the impedance of the R-C circuit is $R\sqrt{1.25}$, the time constant (in millisecond) of the circuit is

 [Watch Video Solution](#)

Single Correct Answer Type

1. A generator produces a time varying voltage given by $V = 240 \sin 120t$, where t is in second. The rms voltage and frequency are

A. 60Hz and 240V

B. 189Hz and 120V

C. 9Hz and 170V

D. 754Hz and 70V

Answer: C



[Watch Video Solution](#)

2. The peak value of an alternating emf E given by

$$E = E_o \cos \omega t$$

is 10 V and frequency is 50 Hz . At time $t = (1/600)$ s, the instantaneous value of emf is

A. 10V

B. $5\sqrt{3}V$

C. 5V

D. 1V

Answer: B



Watch Video Solution

3. A resistance of 20ohms is connected to a source of an alternating potential $V = 220 \sin(100\pi t)$. The time taken by the current to change from its peak value to r.m.s. value is

A. 0.2sec

B. 0.25sec

C. 25×10^{-3} sec

D. 2.5×10^{-3} sec

Answer: D



Watch Video Solution

4. Voltage and current in an AC circuit are given by $V = 5\sin(100\pi t - \pi/6)$ and $I = 4\sin(100\pi t + \pi/6)$

- A. Voltage leads the current by 30°
- B. Voltage leads the voltage by 30°
- C. Voltage leads the voltage by 60°
- D. Voltage leads the current 60°

Answer: C

 [Watch Video Solution](#)

5. In a certain circuit, current changes with according to

$i = 2\sqrt{t}$. Root mean square value current between $t = 2 \rightarrow t = 4$ will be

$\sqrt{2x}$ A. Find value of x.

A. $3A$

B. $3\sqrt{3}A$

C. $2\sqrt{3}A$

D. $(2 - \sqrt{2})A$

Answer: C



Watch Video Solution

6. Match the following

Currents

r.m.s. values

(1) $x_0 \sin \omega t$

(i) x

(2) $x_0 \sin \omega t \cos \omega t$

(ii) $\frac{x_0}{\sqrt{2}}$

(3) $x_0 \sin \omega t + x_0 \cos \omega t$

(iii) $\frac{x_0}{(2\sqrt{2})}$

A. 1.(i),2.(ii),3.(iii)

B. 1.(ii),2.(iii),3.(i)

C. 1.(i),2.(iii),3.(ii)

D. none of these

Answer: B

 [Watch Video Solution](#)

7. If $i = t^2$, $0 < t < T$ then *r. m. s.* value of current is

A. $\frac{T^2}{\sqrt{2}}$

B. $\frac{T^2}{2}$


C. $\frac{T^2}{\sqrt{5}}$

D. none of these

Answer: C

 [Watch Video Solution](#)

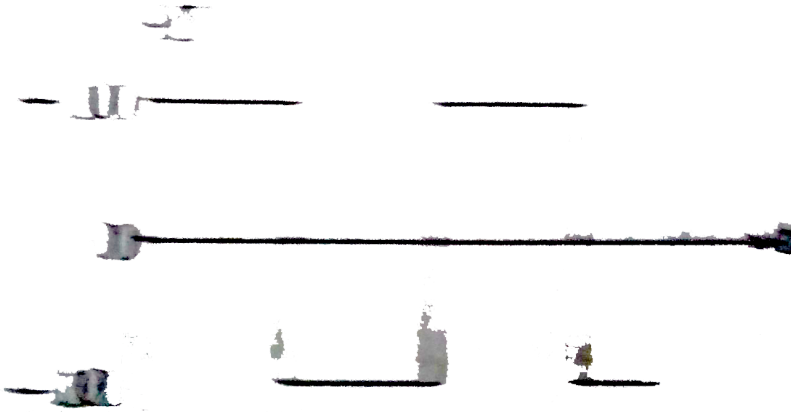8. The rms voltage of the wave form shown is



A. 10V

B. 7V

C. 6.37V


D. none of these

Answer: A



Watch Video Solution

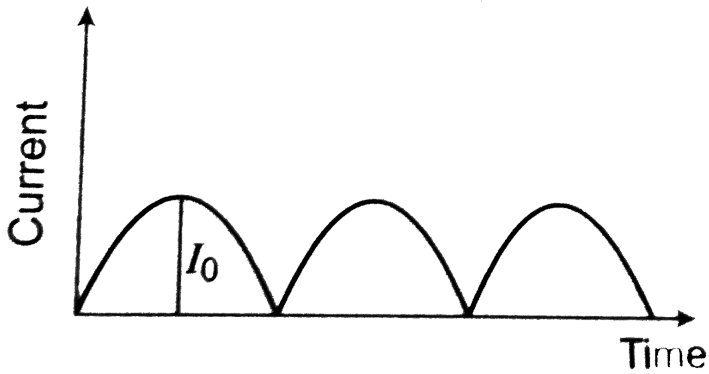9. The output current versus time curve of a rectifier is shown in the figure. The average value of output current in this case is



A. 0

B. $\frac{I_2}{2}$

C. $\frac{2I_2}{\pi}$


D. I_0

Answer: C



Watch Video Solution

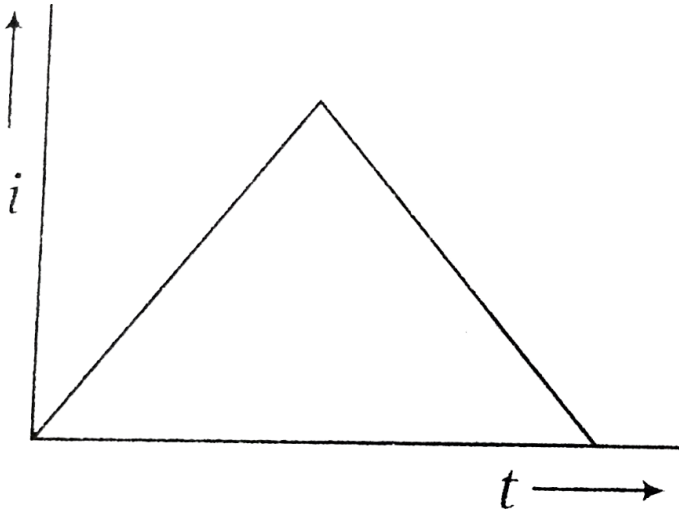10. an alternating current I in an inductance coil with time according to the graph below. We one of the following graphs gives the variation voltage with time?



A. 


B. 

C. 

D. 

Answer: B

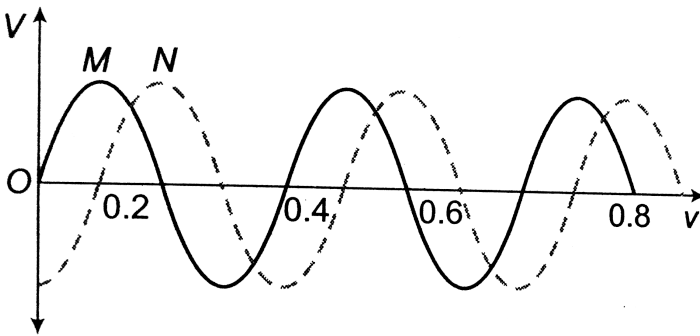11. Two sinusoidal voltage of the same frequency are shown in the diagram. What is the frequency, and the phase relationship between the voltage?




Frequency in Hz phase lead of N over M in radian

- | | | |
|-----|-------------------|--------------------------------------|
| A. | Frequency in Hz | Phase lead of N over M in radian |
| (a) | 0.4 | $-\pi/4$ |
| B. | Frequency in Hz | Phase lead of N over M in radian |
| (b) | 2.5 | $-\pi/2$ |
| C. | Frequency in Hz | Phase lead of N over M in radian |
| (c) | 2.5 | $+\pi/2$ |
| D. | Frequency in Hz | Phase lead of N over M in radian |
| (d) | 2.5 | $-\pi/4$ |

Answer: B

 Watch Video Solution

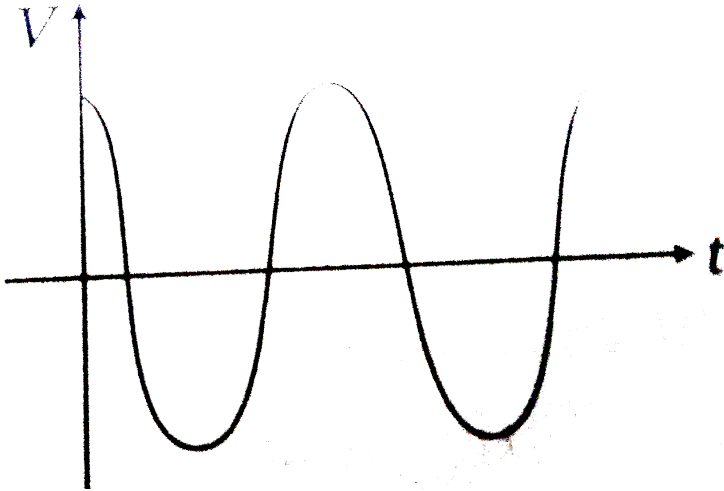12. the voltage across a pure inductor is represent in figure. Which one of the following curves in the figure will represent the current?



A. 

B. 

C. 

D. 

Answer: D

 [Watch Video Solution](#)

13. In pure inductive circuit, the curves between frequency f and reciprocal of inductive reactance $1/X_L$ is

A. 

B. 


C. 

D. 

Answer: C

 [Watch Video Solution](#)

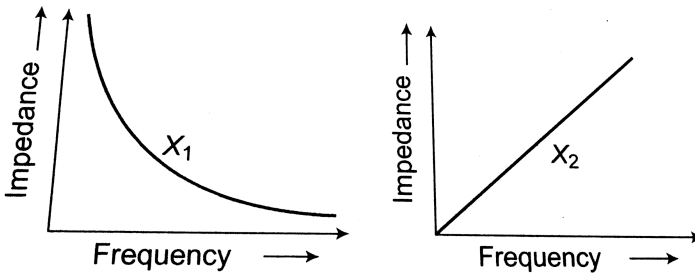14. The graphs given below depict the dependence of two reactive impedances X_1 and X_2 on the frequency of the alternating e.m.f. applied individually to them. We can then say that



- A. X_1 is an inductor and X_2 is a capacitor
- B. X_1 is a resistor and X_2 is a capacitor
- C. X_1 is a capacitor and X_2 is an inductor
- D. X_1 is an inductor and X_2 is a resistor

Answer: C



Watch Video Solution

15. Which of the following graphs represent the correct variation of capacitive reactance X_C with frequency ω ?

A. 

B. 

C. 

D. 

Answer: B



Watch Video Solution

16. Is the following circuit correctly drawn 

A. Yes

B. no

C. cannot be predicted

D. Insufficient data is applied

Answer: A

 [Watch Video Solution](#)

17. An alternating emf is applied across a parallel combination of a resistance R, capacitance C and an inductance L. If I_R , I_L and I_C are the currents through R, L and C respectively, the phase relationship among I_R , I_L and I_C and source emf E, is given by

A. 

B. 

C. 

D. 

Answer: C



Watch Video Solution

18. When 100V. DC is applied across a solenoid a current of 1A flows in it. When 100V, AC is applied across the same coil, the current drops to 0.5A. The frequency of the AC is 50Hz. The impedance and inductance of the solenoid are

A. 200 Ω and 0.55H

B. 100 Ω and 0.86H

C. 200 Ω and 1.0H

D. 100 Ω and 0.93H

Answer: A

 [Watch Video Solution](#)

19. An electric bulb and a capacitor are connected in series with an AC source. On increasing the frequency of the source, the brightness of the bulb

- A. The glow decrease
- B. The glow increase
- C. The glow remains the same
- D. Bulb quenches

Answer: B

 [Watch Video Solution](#)

20. For a series RLC circuit $R = X_L = 2X_C$. The impedance of the current and phase different (between) V and i will be

A. $\frac{\sqrt{5}R}{2}, \tan^{-1}(2)$

B. $\frac{\sqrt{5}R}{2}, \tan^{-1}\left(\frac{1}{2}\right)$

C. $\sqrt{5}X_C, \tan^{-1}\left(\frac{1}{2}\right)$


D. $\sqrt{5}R, \tan^{-1}\left(\frac{1}{2}\right)$

Answer: B

 [Watch Video Solution](#)

21. The figure shows variation of R , $\frac{X}{L}$ and $\frac{X}{C}$ with frequency f in a series L, C, R circuit. Then, for what frequency point, the circuit

is inductive?

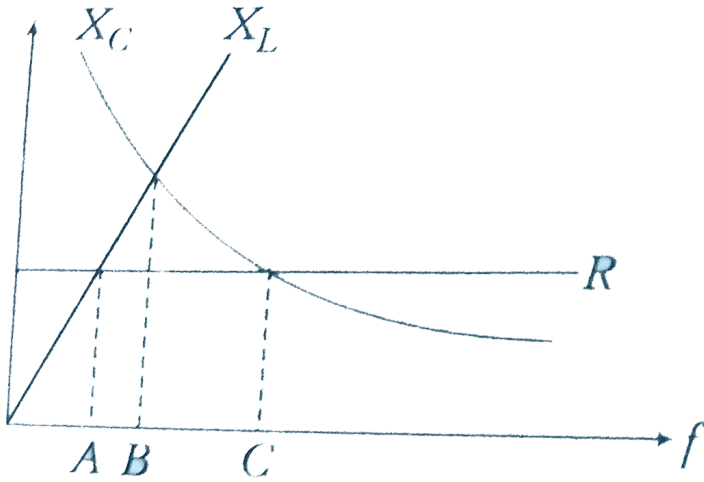

- A. A
- B. B
- C. C
- D. All points

Answer: C



Watch Video Solution

22. Same current is flowing in two alternating circuits. The first circuit contains only inductances and the other contains only a capacitor, if the frequency of the e.m.f of AC is increased, the effect on the value of the current will be


- A. increased in the first circuit and decreased in the other
- B. increased in both circuits
- C. decreased in both the circuits
- D. decreased in the first circuit and increased in the other

Answer: D

 [Watch Video Solution](#)

23. In the circuit shown, the AC source has voltage $V = 20\cos(\omega t)$ volt with $\omega = 200 \text{ rad s}^{-1}$ the amplitude of the current will be

nearest to

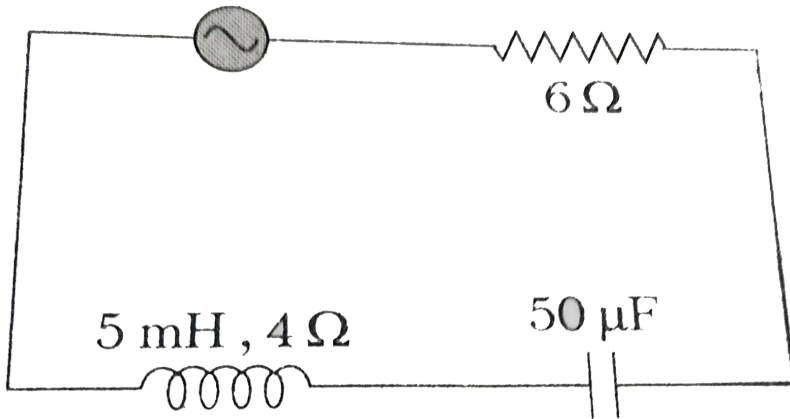

A. 2A

B. 3.3A

C. $2/\sqrt{5}\text{A}$

D. $\sqrt{5}\text{A}$

Answer: A



Watch Video Solution

24. In an LCR circuit $R=100$ ohm. When capacitance C is removed, the current lags behind the voltage by $\pi/3$. When inductor L is removed, the current leads the voltage by $\pi/3$. The impedance of the circuit is:


- A. 50Ω
- B. 100Ω
- C. 200Ω
- D. 400Ω

Answer: B

 [Watch Video Solution](#)

25. For the series L-C-R circuit shown in the figure, what is the resonance frequency and the current at the resonating

frequency?

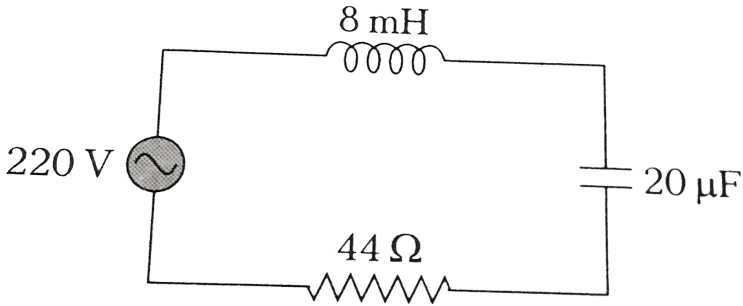

- A. 2500 rads^{-1} and $\sqrt{5} \text{ A}$
- B. 2500 rads^{-1} and 5 A
- C. 2500 rads^{-1} and $\frac{5}{\sqrt{2}} \text{ A}$
- D. 2500 rads^{-1} and $5\sqrt{2} \text{ A}$

Answer: B



Watch Video Solution

26. Following figure, as shown an an generator connected to a "block box" through a pair fo terminal. The box contains possible

R,L,C of their combination, whose elements and arrangements are not known to us. Measurements outside the box reveals that $e=75\sin(\omega t)$ volts, $i=1.5\sin(\omega t+45^\circ)$ amp then. the wrong statements is



- A. There must be a capacitor in the box.
- B. There must be an inductor in the box.
- C. There must be a resistance in the box.
- D. The power factor is 0.707.

Answer: B

 [Watch Video Solution](#)

27. A resistor R , an inductor L and a capacitor C are connected in series to an oscillator of frequency n . If the resonant frequency

is n_r , then the current lags behind voltage, when

A. $n=0$

B. $n < n_f$

C. $n < n_r$

D. $n > n_r$

Answer: D

 [Watch Video Solution](#)

Comphension Based

1. In a series L-R circuit, connected with a sinusoidal ac source, the maximum potential difference across L and R are respectively 3 volts and 4 volts.

At an instant the potential difference across resistor is 2 volts.

The potential difference in volt, across the inductor at the same instant will be:

A. $3\cos 30^\circ$

B. $3\cos 50^\circ$

C. $6\cos 45^\circ$

D. 6

Answer: A



[Watch Video Solution](#)

2. In a series $L - R$ circuit, connected with a sinusoidal ac source, the maximum potential difference across L and R are respectively 3 volts and 4 volts

At the same instant, the magnitude of the potential difference in volt, across the ac source will be

A. $3\cos 67^\circ$

B. $5\sin 37^\circ$

C. $6\cos 97^\circ$

D. 0

Answer: B



[Watch Video Solution](#)

3. In a series $L - R$ circuit, connected with a sinusoidal ac source, the maximum potential difference across L and R are respectively 3 volts and 4 volts

If the current at this instant is decreasing the magnitude of potential difference at that instant across the ac source is

A. Increasing

B. Decreasing


C. Constant

D. Cannot be said

Answer: A

 [Watch Video Solution](#)

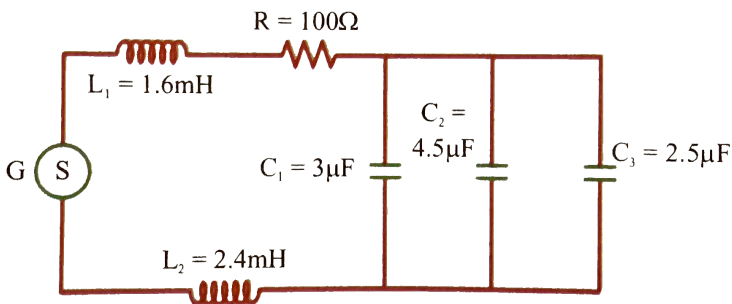4. An ac generator G with an adjustable frequency of oscillation is used in the circuit, as shown.



Current drawn from the ac source will be maximum if its angular frequency is

A. 10^5 rad/s

B. 10^4 rad/s


C. 5000 rad/s

D. 500 rad/s

Answer: C

 [Watch Video Solution](#)

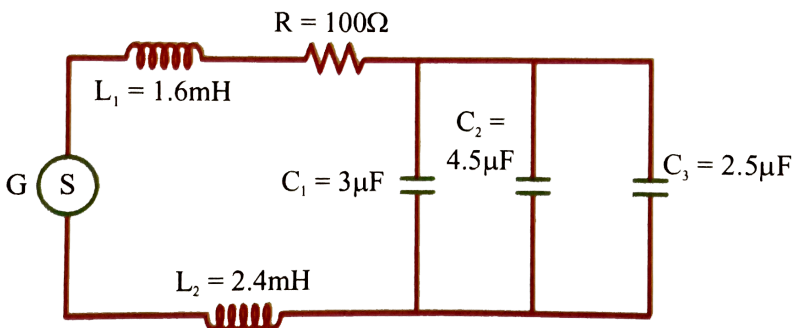5. An ac generator G with an adjustable frequency of oscillation is used in the circuit, as shown.



To increase resonant frequency of the circuit, some of the


changes in the circuit are carried out. Which changes would certainly result in the increase in resonant frequency ?

- A. R is increased.
- B. L_1 is increased and C_1 is decreased.
- C. L_2 is decreased and C_2 is increased
- D. C_3 is removed from the circuit.

Answer: D

 [Watch Video Solution](#)

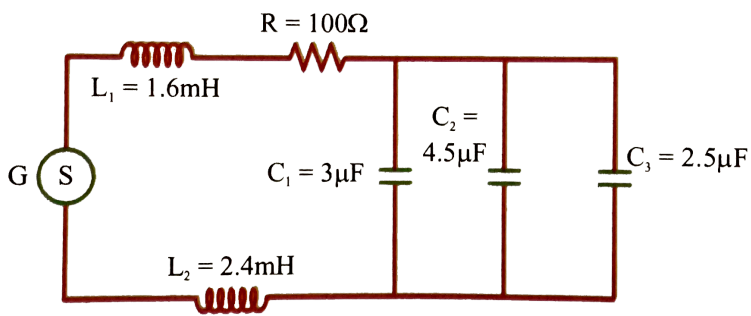6. An ac generator G with an adjustable frequency of oscillation is used in the circuit, as shown.




If the ac source G is 100V rating at resonant frequency of the circuit, then average power supplied by the source is

- A. 50W
- B. 100W
- C. 500W
- D. 1000W

Answer: B

[Watch Video Solution](#)

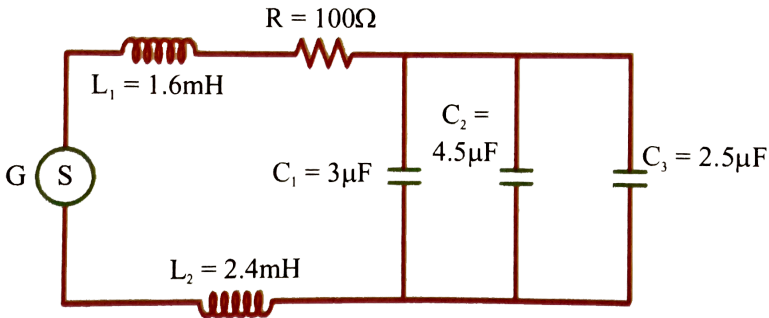7. An ac generator G with an adjustable frequency of oscillation is used in the circuit, as shown.



Average energy stored by the inductor L_2 (source is at resonance frequency) is equal to

- A. zero
- B. 1.2mj
- C. 2.4mj
- D. 4mj

Answer: B

 Watch Video Solution

8. Ratio of amplitude for two wave is 1:2 .Find the ratio of intensity?



Watch Video Solution

Single Correct

1. The rms current in an AC circuit is 2A. If the wattless current be $\sqrt{3}A$, what is the power factor of the circuit?

A. $\frac{1}{\sqrt{3}}$

B. $\frac{1}{\sqrt{2}}$

C. $\frac{1}{2}$

D. $\frac{1}{3}$

Answer: C

 [Watch Video Solution](#)

2. $\frac{2.5}{\pi} \mu F$ capacitor and 3000 – ohm resistance are joined in series to an AC source of 200volts and 50 sec^{-1} frequency. The power factor of the circuit and the power dissipated in it will respectively

A. 0.6, 0.06W

B. 0.06, 0.6W

C. 0.6, 4.8W

D. 4.8, 06W

Answer: C

 [Watch Video Solution](#)

3. The self inductance of a choke coil is 10 mH. When it is connected with a 10 V DC source, then the loss of power is 20 W. When its is connected with 10 V AC source loss of power is 10 W. The frequency of AC source will be

- A. 50Hz
- B. 60Hz
- C. 80Hz
- D. 100Hz

Answer: C



Watch Video Solution

4. A group of electric lamps having a total power rating of 1000 W is supplied by an AC voltage $E = 200 \sin(310t + 60^\circ)$, then the rms value of the circuit current is

A. $10A$

B. $10\sqrt{2}A$

C. $20A$

D. $20\sqrt{2}A$

Answer: B



[Watch Video Solution](#)

5. In an L-R circuit, the inductive reactance is equal to the resistance R of the circuit. An emf $E = E_0 \cos \omega t$ is applied to the circuit. The power consumed in the circuit is

A. $\frac{E_0^2}{R}$

B. $\frac{E_0^2}{R}$

C. $\frac{E_0^2}{4R}$

D. $\frac{E_0^2}{8R}$

Answer: C



[Watch Video Solution](#)


6. An L-C-R series circuit with a resistance of 100Ω connected to an AC source of 200V (rms) and angular frequency 300 rad/s . When only the capacitor is removed, the current lags behind the voltage by 60° . When only the inductor is removed the current leads the voltage by 60° . The average power dissipated in original L-C-R circuit (50x) Watt. Find the value of x.

- A. 50W
- B. 100W
- C. 200W
- D. 400W

Answer: D

 [Watch Video Solution](#)

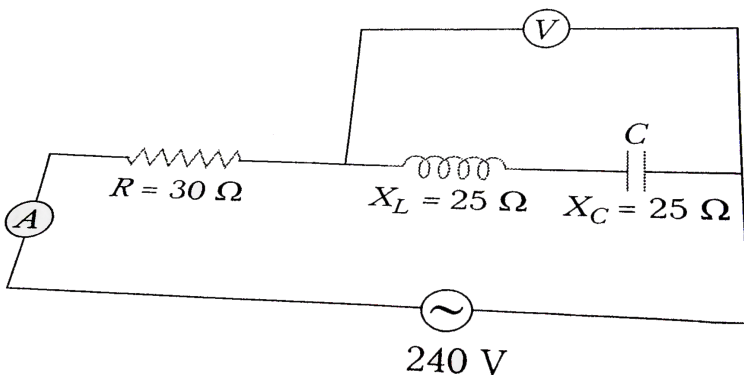7. In the circuit shown in figure neglecting source resistance, the voltmeter and ammeter readings will be respectively



A. 0V,3A

B. 150V,3A

C. 150V, 6A

D. 0V,8A


Answer: D



Watch Video Solution

8. In the circuit shown in the figure , the ac source gives a voltage $V = 20 \cos(200t)$. Neglecting source resistance , the voltmeter and

ammeter reading will be

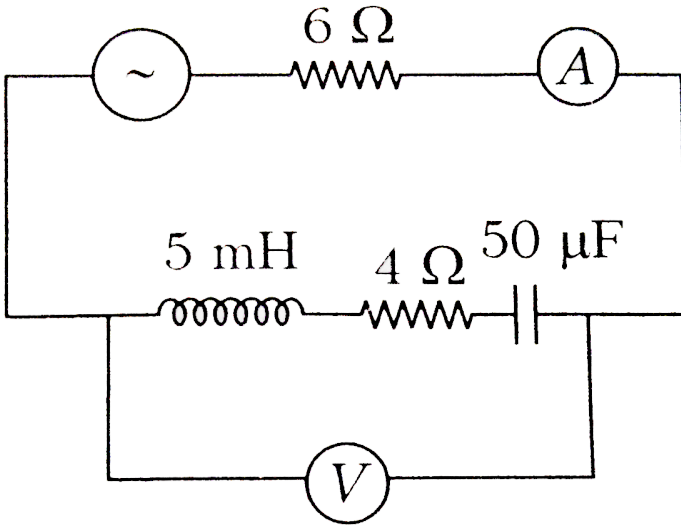

- A. 0V, 0.47A
- B. 1.68V, 0.47A
- C. 0V, 1.4A
- D. 5.6V, 1.4A

Answer: D

 [Watch Video Solution](#)

9. A series combination of resistor (R), capacitor (C) is connected to an AC source of angular frequency ω . Keeping the voltage same, If the frequency is changed to $\frac{\Omega}{3}$, the current becomes half of the original current. Then, the ratio of the capacitance reactance and resistance at the former frequency is

A. $\sqrt{\frac{3}{5}}$

B. $\sqrt{\frac{2}{5}}$

C. $\sqrt{\frac{1}{5}}$


D. $\sqrt{\frac{4}{5}}$

Answer: A



Watch Video Solution

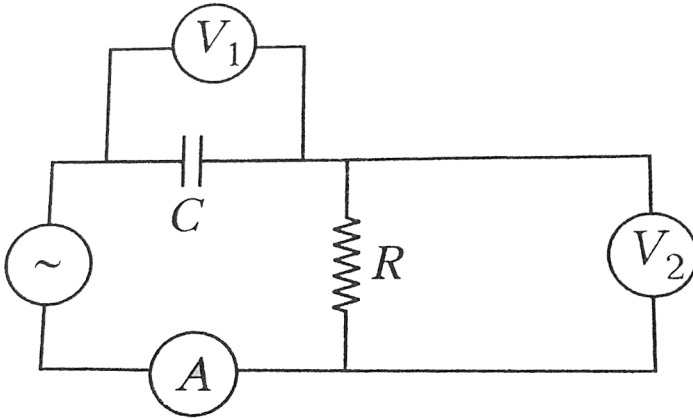10. The diagram shows a capacitor C and a variable resistor R connected in series to an AC source. V_1 and V_2 are voltmeters and A is an ammeter.



Consider the following statements

- I . Readings in A and V_2 are always in phase
- II . Reading in V_1 is ahead in phase with reading in V_2
- III . Reading in A and V_1 are always in phase. Which of these statements are/is correct

A. I only

B. II only

C. I and II only

D. II and III only

Answer: B



Watch Video Solution