



PHYSICS

BOOKS - CENGAGE PHYSICS (ENGLISH)

ELECTRIC CURRENT & CIRCUITS

Restivity And Drift Velocity

1. Is the motion of a charge across junction momentum conserving ? Why or why not ?




Watch Video Solution

2. The relaxation time τ is nearly independent of applied electric field E whereas it changes significantly with temperature T . First fact is (in part) responsible for Ohm's law whereas the second fact leads to variation of ρ with temperature. Elaborate why ?



[Watch Video Solution](#)

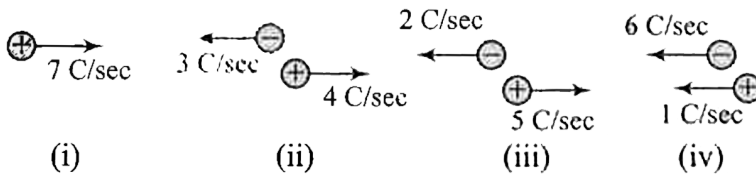3. Following figures show four situations in which positive and negative charges move horizontally through a region and give the rate at which each charge moves. Rank the situations according to the effective current through the region greatest first.



A. $i=ii=iii=iv$

B. $i>ii>iii>iv$

C. $i=ii=iii>iv$

D.


Answer: C



Watch Video Solution

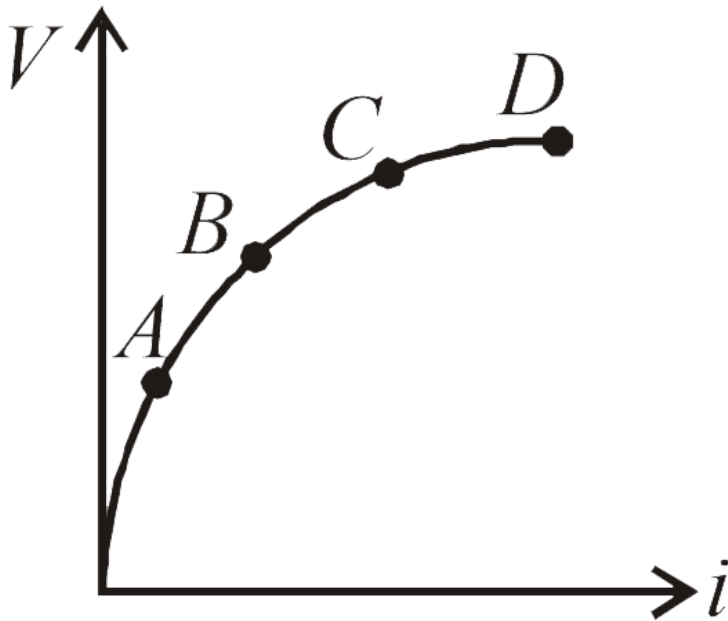4. Variation of current passing through a conductor as the voltage applied across its ends is varied as shown in the adjoining diagram. If the resistance (R) is determined at

the points A, B, C and D, we will find that



A. $R_C = R_D$

B. $R_B > R_A$

C. $R_C > R_B$

D. None of these


Answer: D



Watch Video Solution

5. $I - V$ characteristic of a copper wire of length L and area of cross-section A is shown

in Fig. The slope of the curve becomes

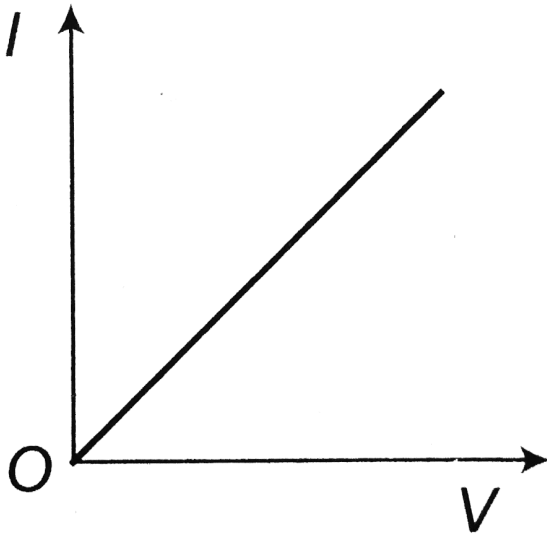

A. More if the experiment is performed at

higher temperature

B. More if a wire of steel of the same

direction is used

C. more if the length of the wire is increased

D. Less if the length of the wire is increased

Answer: D



Watch Video Solution

6. The resistance R of a conductor varies with temperature t as shown in the figure. If the variation is represented by

$$R_t = R_0 [1 + \alpha t + \beta t^2], \text{ then}$$




- A. α and β are both negative
- B. α and β are positive
- C. α is positive and β is negative
- D. α is negative and β is positive

Answer: B



Watch Video Solution

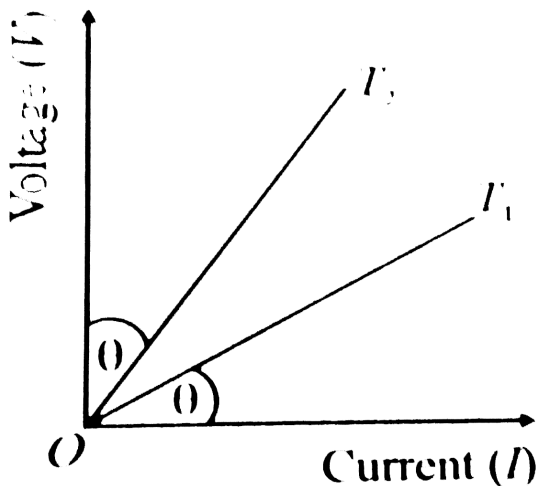7. The V-I graph for a conductor at temperature T_1 and T_2 are as shown in the figure. The term $(T_2 - T_1)$ is proportional to



A. $\cos 2\theta$

B. $\sin \theta$

C. $\cot 2\theta$

D. $\tan \theta$





Answer: C



Watch Video Solution

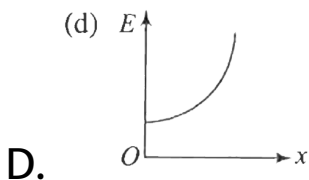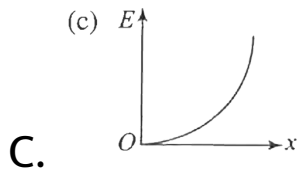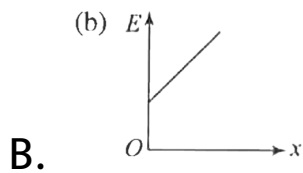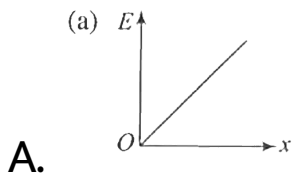8. A cylindrical conductor has uniform cross-section. Resistivity of its material increase linearly from left end to right end. If a

constant current is flowing through it and at a section distance x from left end, magnitude of electric field intensity is E , which of the following graphs is correct



Answer: B



Watch Video Solution

9. Dimensions of a block are $1\text{cm} \times 1\text{cm} \times 100\text{cm}$. If specific resistance of its material is $3 \times 10^{-7} \text{ohm} - \text{m}$, then the resistance between the opposite rectangular faces is

A. $3 \times 10^{-9} \Omega$

B. $3 \times 10^{-7} \Omega$

C. $3 \times 10^{-5} \Omega$

D. $3 \times 10^{-3} \Omega$

Answer: B



Watch Video Solution

10. Dimensions of a block are $1\text{cm} \times 1\text{cm} \times 100\text{cm}$. If specific resistance of its material is $3 \times 10^{-7} \text{ohm} - \text{m}$, then the resistance between the opposite square faces is

A. $3 \times 10^{-9} \Omega$

B. $3 \times 10^{-7} \Omega$

C. $3 \times 10^{-5} \Omega$

D. $3 \times 10^{-3} \Omega$

Answer: D



Watch Video Solution

11. A Steady current flows in a metallic conductor of non uniform cross section. The

quantity/quantities which remain constant along the length of the conductor is/are

- A. Current, electric field and drift speed
- B. Drift speed only
- C. Current and drift speed
- D. Current only

Answer: D



Watch Video Solution

12. A current I is passing through a wire having two sections P and Q of uniform diameters d and $d/2$ respectively. If the mean drift velocity of electrons in section P and Q is denoted by v_P and v_Q respectively, then

A. $v_P = v_Q$

B. $v_P = \frac{1}{2}v_Q$

C. $v_P = \left(\frac{1}{4}\right)v_Q$

D. $v_P = 2v_Q$

Answer: C



Watch Video Solution

13. The resistance of a wire is 10Ω . Its length is increased by 10% by stretching. The new resistance will now be

A. 0.1

B. 0.25

C. 0.21

D. 0.09

Answer: C



Watch Video Solution

14. Which of the following characteristics of electrons determines the current in a conductor?

- A. Drift velocity alone
- B. Thermal velocity alone
- C. Both drift velocity and thermal velocity
- D. Neither drift nor thermal velocity

Answer: A



Watch Video Solution

15. Temperature dependence of resistivity $\rho(T)$ of semiconductors, insulators and metals is significantly based on the following factors.

A. number of charge carriers can change with temperature T

B. time interval between two successive collisions can depend on T

C. length of material can be a function of T

D. mass of carriers is a function of T

Answer: A::B




Watch Video Solution

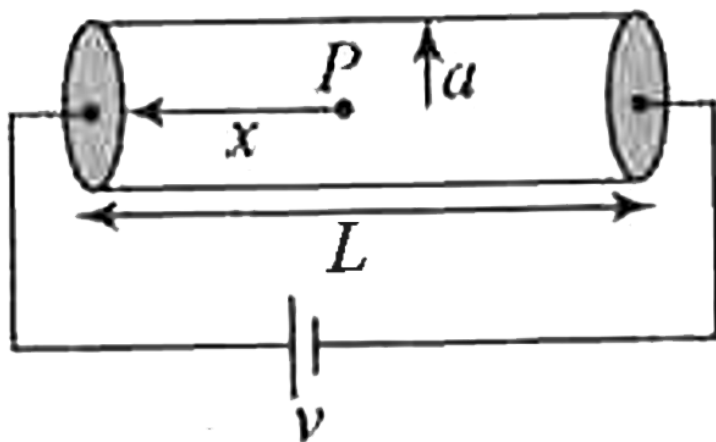16. A cylindrical solid of length L and radius a is connected across a source of emf V and negligible internal resistance shown in figure.

The resistivity of the rod at point P at a distance x from left end is given by $\rho = bx$

(where b is a positive constant). Find the electric field at point P .



[Watch Video Solution](#)

17. A common flashlight bulb is rated 0.30A and 2.7V (the values of the current and voltage under operating conditions.) If the resistance

of the tungsten bulb filament at room temperature $20^\circ C$ is 1.0Ω and its temperature coefficient of resistivity is $4.0 \times 10^{-3} C^{-1}$, then find the temperature in centigrade of the filament when the bulb is on. (Consider the variation of resistance to be linear with temperature.)



[Watch Video Solution](#)

18. Two wires of resistance R_1 and R_2 have temperature coefficient of resistance α_1 and

α_2 respectively. These are joined in series. The effective temperature coefficient of resistance is

A. $(\alpha_1 + \alpha_2)/2$

B. $(\sqrt{\alpha_1 \alpha_2})$

C. $\frac{\alpha_1 R_1 + \alpha_2 R_2}{R_1 + R_2}$

D. $\left(\frac{\sqrt{R_1 R_2 \alpha_1 \alpha_2}}{\sqrt{R_1^2 + R_2^2}} \right)$

Answer: C



Watch Video Solution

19. Two resistance R_1 and R_2 are made of different material. The temperature coefficient of the material of R_1 is α and of the material of R_2 is $-\beta$. Then resistance of the series combination of R_1 and R_2 will not change with temperature, if R_1 / R_2 will not change with temperature if R_1 / R_2 equals

A. $\frac{\alpha}{\beta}$

B. $\frac{\alpha + \beta}{\alpha - \beta}$

C. $\frac{\alpha^2 + \beta^2}{\alpha\beta}$

D. $\frac{\beta}{\alpha}$

Answer: D



Watch Video Solution

20. An ionization chamber with parallel conducting plates as anode and cathode has 5×10^7 electrons and the same number of singly-charged positive ions per cm^3 . The electrons are moving at $0.4m/s$. The current density from anode to cathodes $4\mu A/m^2$. The

velocity of positive ions moving towards cathode is

A. $0.4m / s$

B. $16m / s$

C. Zero

D. $0.1m / s$

Answer: D



Watch Video Solution

21. The current in conductor varies with time t as $I = 2t + 3t^2$ where I is in ampere and t in seconds. Electric charge flowing through a section of the conductor during $t = 2$ sec to $t = 3$ sec is

A. 10C

B. 24C

C. 33C

D. 44C

Answer: B



Watch Video Solution

22. The resistance of a wire of iron is 10ohm and temperature coefficient of resistivity is $5 \times 10^{-3} / .^{\circ} C$, At $20^{\circ} C$ it carries 30mA of current. Keeping constant potential difference between its ends. The temperature of the wire is raised to $120^{\circ} C$. The current in mA that flows in the wire now is.

A. 20

B. 15

C. 10

D. 40

Answer: A



Watch Video Solution

23. Length of a hollow tube is $5m$, its outer diameter is $10cm$ and thickness of its wall is 5 mm. If resistivity of the material of the tube is $1.7 \times 10^{-8} \Omega \times m$ then resistance of tube will be

A. $5.6 \times 10^{-5} \Omega$

B. $2 \times 10^{-5} \omega$

C. $4 \times 10^{-5} \Omega$

D. None of these

Answer: A



Watch Video Solution

24. In order to increase the resistance of a given wire of uniform cross section to four times its value, a fraction of its length is

stretched uniformly till the full length of the wire becoes $\frac{3}{2}$ times the original length. What is the value of this fraction?

A. $\frac{1}{8}$

B. $\frac{1}{6}$

C. $\frac{1}{10}$


D. $\frac{1}{4}$

Answer: A



Watch Video Solution

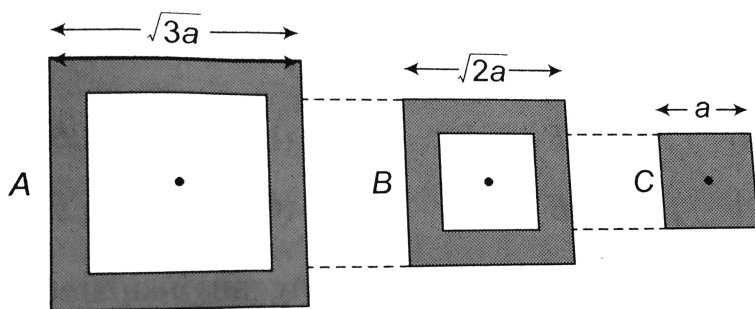25. Following figure shows cross-section through three long conductors of the same length and material, with square cross-section of edge lengths as shown. Conductor B will snugly within conductor A . Relationship between their end to end resistance is



A. $R_A = R_B = R_C$

B. $R_A > R_B > R_C$

C. $R_A < R_B < R$

D. Information is not sufficient.


Answer: A



Watch Video Solution

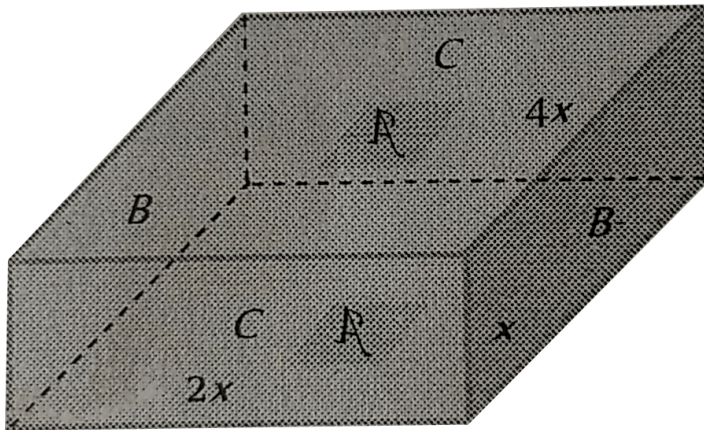26. In figure shows a rectangular block with dimensions x , $2x$ and $4x$. Electrical contacts can be made to the block between opposite pairs of faces (for example, between the faces labelled A - A , B - B and C - C). Between which

two faces would the maximum electrical resistance be obtained (A - A : Top and bottom faces, B - B : Left and right faces, C - C : Front and rear faces)



A. A-A

B. B-B

C. C-C

D. Same for all three pairs





Answer: C




Watch Video Solution

27. A battery is connected to a uniform resistance wire AB and B is earthed. Which one of the graphs below shows how the current

density J varies along AB

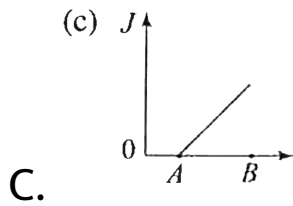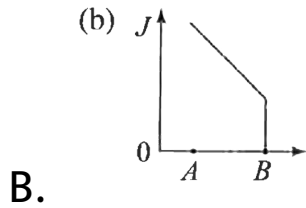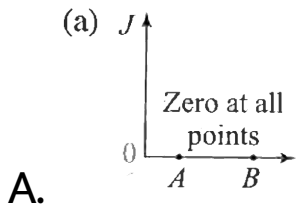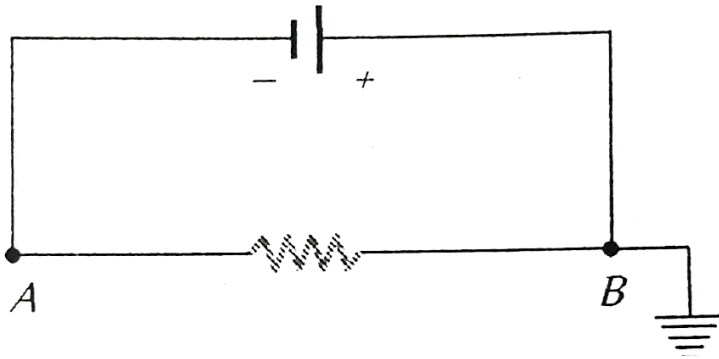

D.

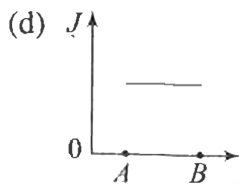

Answer: D



Watch Video Solution

28. Two wires each of radius of cross section r but of different materials are connected together end to end (in series). If the densities of charge carriers in the two wires are in the

ratio 1:4, the drift velocity of electrons in the two wires will be in the ratio:

A. 1:2

B. 2:1

C. 4:1


D. 1:4

Answer: C



Watch Video Solution

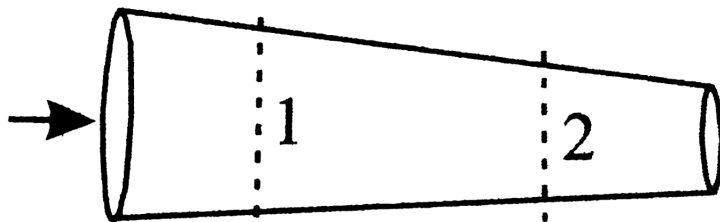29. Consider a conductor of variable cross section in which current is flowing from cross section 1 to 2. Then



A. current density at A = current density at

B

B. current density at A gt current density at

B

C. current density at A gt current density at

B

D. none of the above

Answer: B



Watch Video Solution

30. A 150 m long metal wire connects points A and B. The electric potential at point B is 50V less than that at point A. If the conductivity of

the metal is $60 \times 10^6 \text{ mho/m}$ then magnitude of the current density in the wire is equal to:

A. $11 \times 10^{-4} \text{ A/m}^2$

B. $5.5 \times 10^{-3} \text{ A/m}^2$

C. $4 \times 10^7 \text{ A/m}^2$

D. $20 \times 10^6 \text{ A/m}^2$

Answer: D



Watch Video Solution

1. First a set of n equal resistors of R each are connected in series to a battery of emf E and internal resistance R , A current I is observed to flow. Then, the n resistors are connected I parallel to the same battery.

It is observed that the current is increased 10 times. what is 'n'?



Watch Video Solution


2. Suppose there is a circuit consisting of only resistances and batteries suppose one is to double (or increase it to n -times) all voltages and all resistances. Show that currents are unaltered.



[Watch Video Solution](#)


3. Find the equivalent resistance between terminals A and B. Each resistor is of

resistance R.

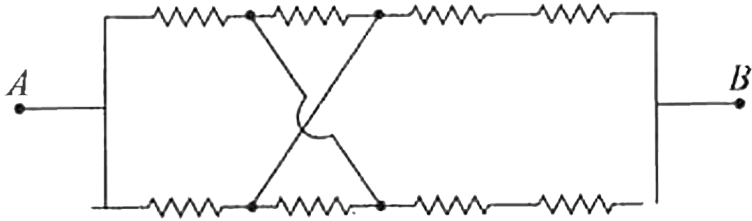

Watch Video Solution




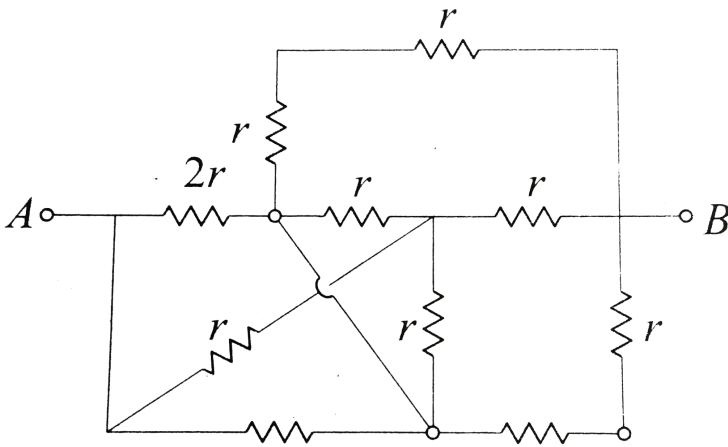
4. The equivalent resistance between A and B in the arrangement of resistance as shown is



Watch Video Solution

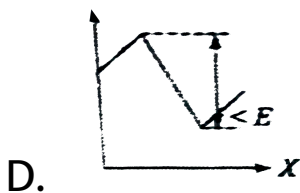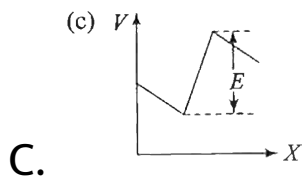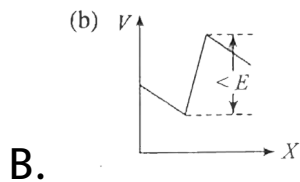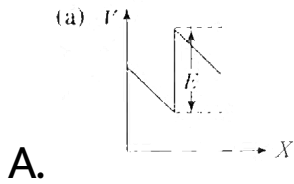5. The two ends of a uniform conductor are joined to a cell of e.m.f. E and some internal resistance. Starting from the midpoint P of the conductor, we move in the direction of current and return to P . The potential V at

every point on the path is plotted against the distance covered (x). which of the following graphs best represent the resulting curve ?




Answer: B



Watch Video Solution

6. V-I graph for parallel and series combination of two metallic resistors are shown in adjoining figure. Which graph represents

parallel combination ?

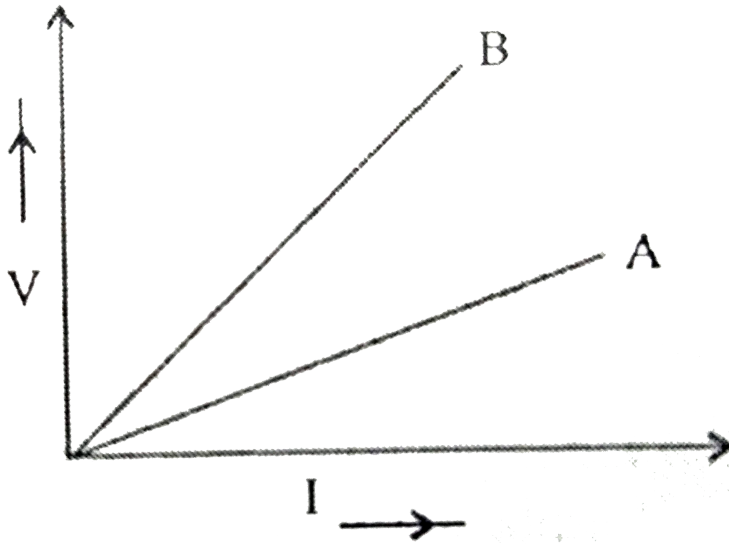

A. A

B. B

C. A and B both


D. Neither A nor B

Answer: A



Watch Video Solution

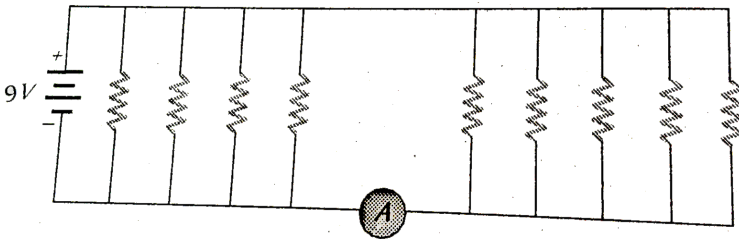7. If each resistance in the figure is of 9Ω then reading of ammeter is



Watch Video Solution

8. Two resistors of resistance R_1 and R_2 having $R_1 > R_2$ are connected in parallel. For equivalent resistance R , the correct statement is

A. $R > R_1 > R_2$

B. $R_1 < R < R_2$

C. $R_2 < R < (R_1 + R_2)$


D. $R < R_1$

Answer: D



Watch Video Solution

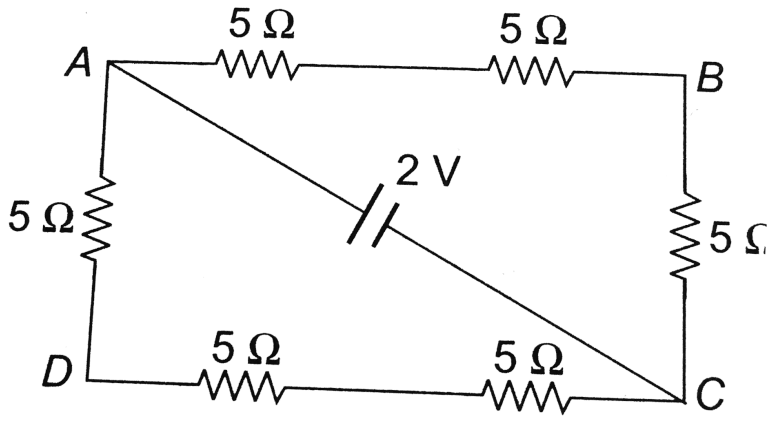9. The potential difference between points A and B adjoining figure is




- A. $2/3V$
- B. $8/9V$
- C. $4/3V$

D. 2V

Answer: C

 Watch Video Solution

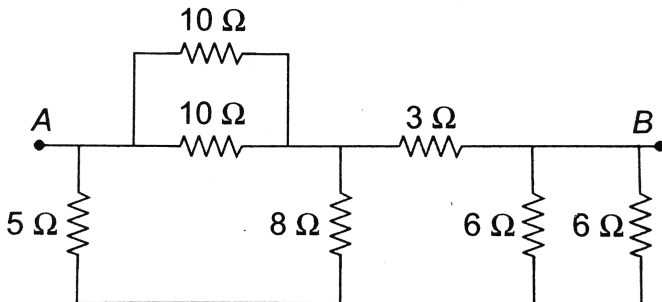10. Seven resistance are connected as shown in the figure. The equivalent resistance between A and B is approximately



A. 3Ω

B. 4Ω

C. 4.5Ω


D. 5Ω

Answer: A



Watch Video Solution

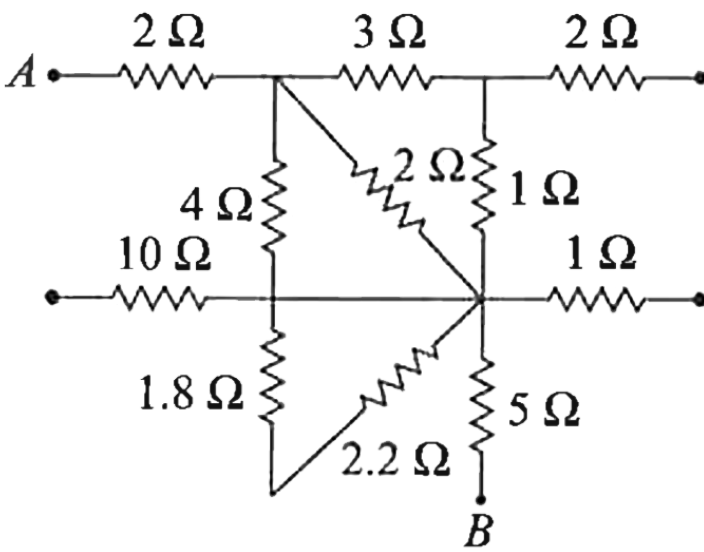11. What is the equivalent resistance between the points A and B of the network?



A. $\frac{57}{7} \Omega$

B. 8Ω

C. 6Ω

D. $\frac{57}{3} \Omega$

Answer: B



12. A uniform wire of resistance 9Ω is cut into 3 equal parts. They are connected in form of equilateral triangle ABC . A cell of e.m.f. $2V$ and negligible internal resistance is connected across B and C . Potential difference across AB is

A. $1V$

B. $2V$

C. $3V$


D. 0.5V

Answer: A



Watch Video Solution

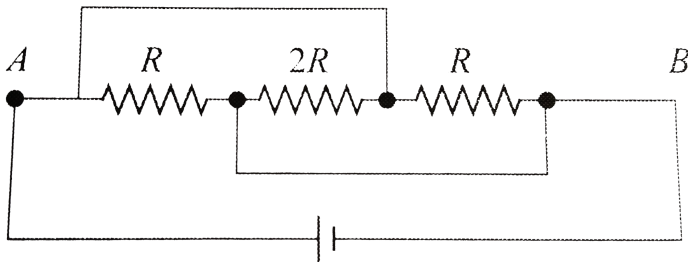13. In fig. the current flowing through $2R$ is



A. from left to right

B. from right to left

C. no current


D. none of these

Answer: B



Watch Video Solution

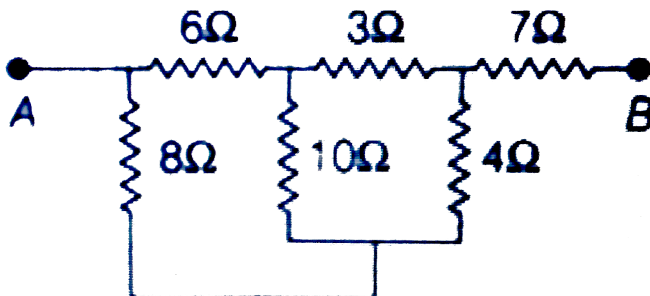14. The equivalent resistance between the points A and B is



A. $\frac{36}{7} \Omega$

B. 10Ω

C. $\frac{85}{7} \Omega$

D. none of these


Answer: C



Watch Video Solution

Combination Of Resistance 2

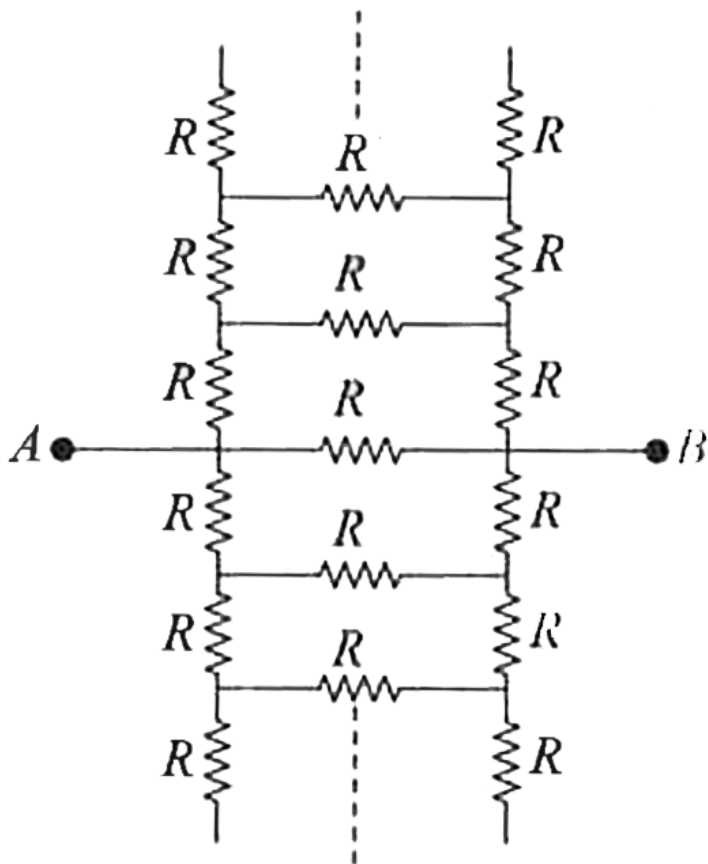
1. If each resistance $R = 100\sqrt{3}\Omega$, then find the equivalent resistance (in ohm) between A and B.



Watch Video Solution

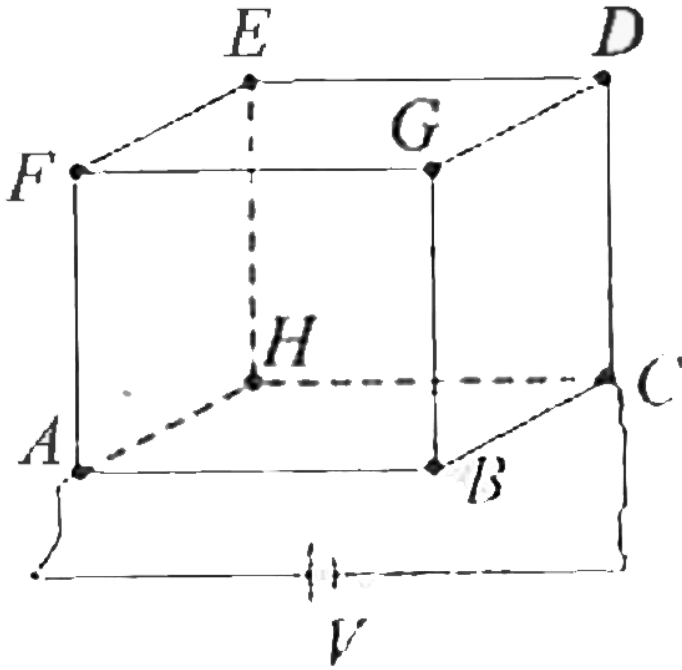
2. In the figure shown eight resistors each of resistance ' R ' are connected to form two squares ABCH and DEFG. Four resistors each of resistance ' $2R$ ' are connected in the vertical lines AF, BG, CD and EH. 'A' and 'C' are connected to a battery of internal resistance ' R '

and emf V . Find out the current in 'AB' and 'ED'.



[▶ Watch Video Solution](#)

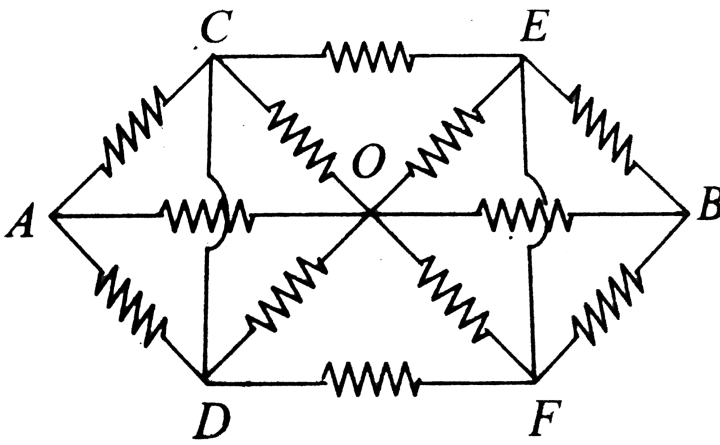
3. Find the equivalent resistance between A and B. Each resistor has same resistance R .



 [Watch Video Solution](#)

4. Thirteen resistors each of resistance R connected in the circuit as shown in figure.

Resistance between A and B is

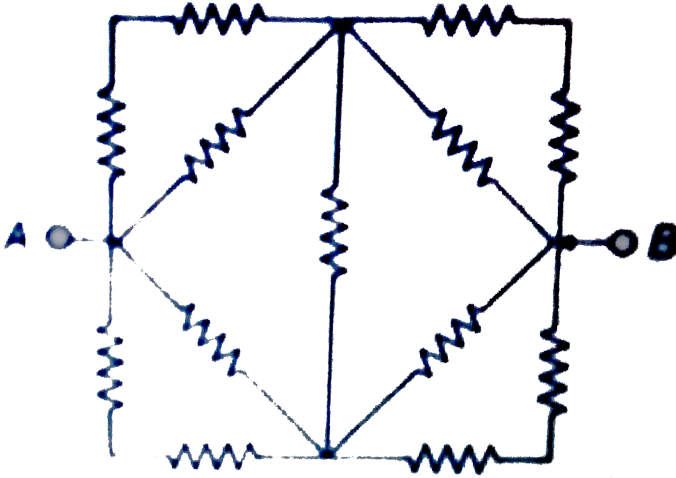

A. $2R\Omega$

B. $4\frac{R}{3}\Omega$

C. $2\frac{R}{3}\Omega$


D. $R\omega$

Answer: C



Watch Video Solution

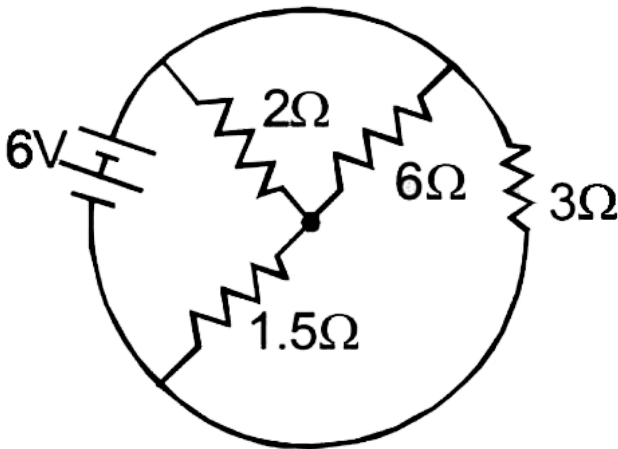5. The total current supplied to the circuit by the battery is



A. 1A

B. 2A

C. 4A

D. 6A


Answer: C



Watch Video Solution

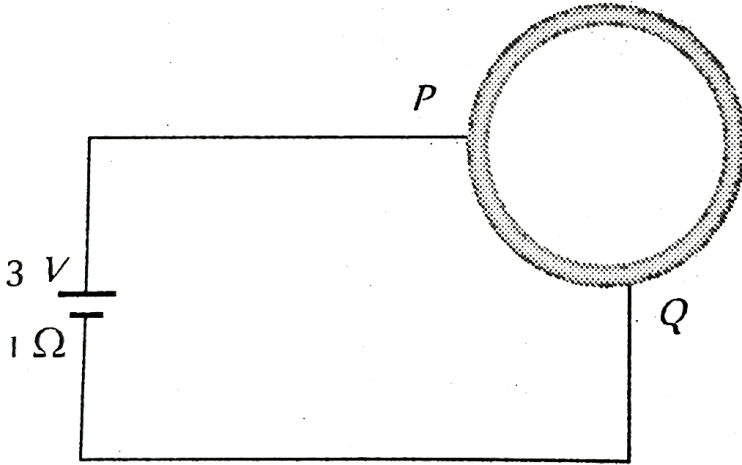6. A wire of resistance 10Ω is bent to form a circle. P and Q are points on the circumference of the circle dividing it into a quadrant and are connected to a Battery of 3 V and internal resistance 1Ω as shown in the figure. The

currents in the two parts of the circle are




- A. $\frac{6}{23} A$ and $\frac{18}{23} A$
- B. $\frac{5}{26} A$ and $\frac{15}{26} A$
- C. $\frac{4}{25} A$ and $\frac{12}{25} A$
- D. $\frac{3}{25} A$ and $\frac{9}{25} A$

Answer: A



Watch Video Solution

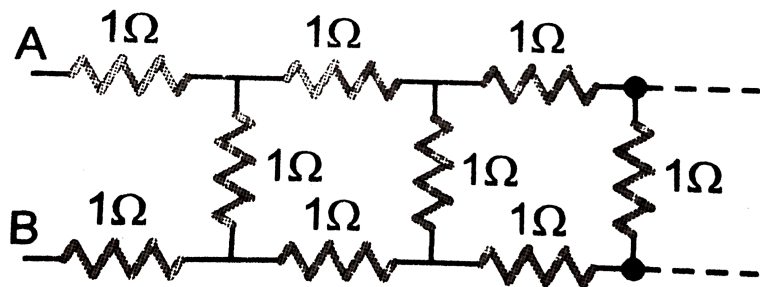7. The resistance between the terminal point A and B of the given infinitely long circuit will be



A. $(\sqrt{3} - 1)$

B. $(1 - \sqrt{3})$


C. $(1 + \sqrt{3})$

D. $(2 + \sqrt{3})$

Answer: C

 Watch Video Solution

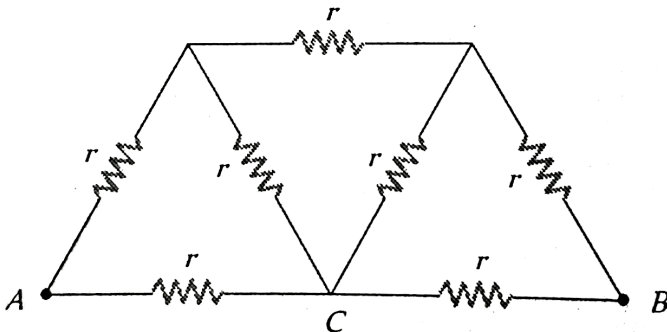8. In the circuit shown, the value of each resistance is r , then equivalent resistance of circuit between points A and B will be



A. $14/11 r$

B. $7/5 r$

C. $8/7 r$

D. $14/13 r$


Answer: D



Watch Video Solution

9. The potential difference across 8 ohm resistance is 48 volt as shown in the figure. The value of potential difference across X and Y

point will be

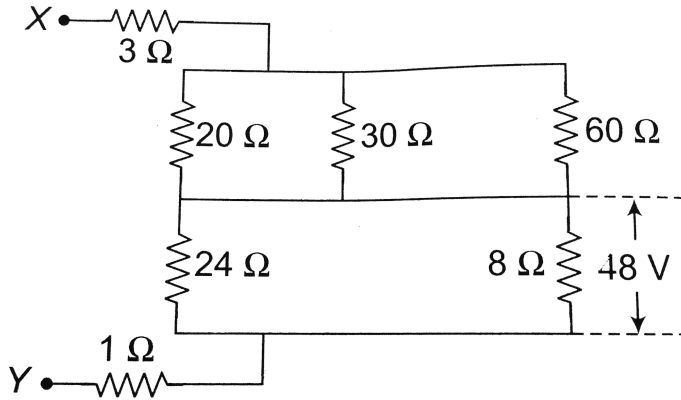

- A. 160 volt
- B. 128 volt
- C. 80volt
- D. 62volt

Answer: A



Watch Video Solution


10. The resistance of the series combination of two resistances is S . When they are joined in parallel the total resistance is P . If $S = nP$ then the minimum possible value of n is



Watch Video Solution

11. The equivalent resistance across the terminals of source of e.m.f. $24V$ for the circuit

shown in the figure is

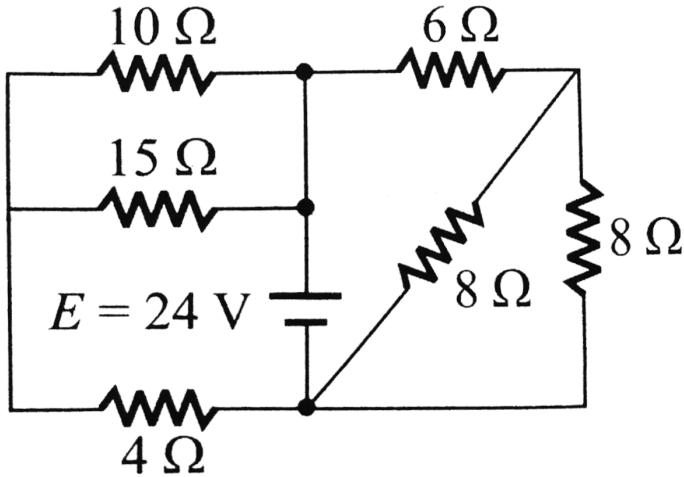

A. $15\ \Omega$

B. $10\ \Omega$

C. $5\ \Omega$


D. $4\ \Omega$

Answer: C



Watch Video Solution

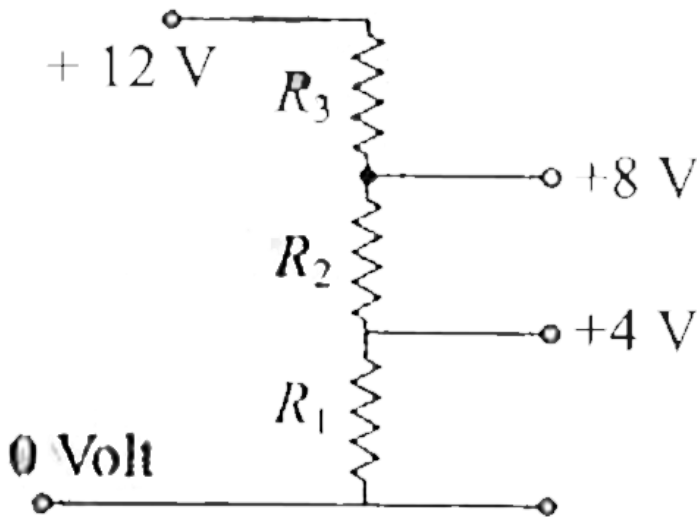12. A potential divider is used to give outputs of 4V and 8V from a 12V source. Which combination of resistance, (R_1, R_2, R_3) gives the correct voltages? ($R_1 : R_2 : R_3$)`



A. 2:1:2

B. 1:1:1

C. 2:2:1


D. 1:1:2

Answer: B



Watch Video Solution

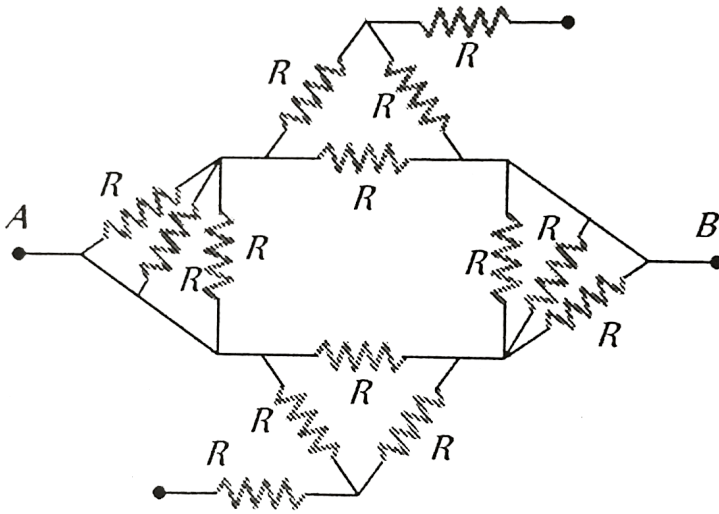13. Find equivalent resistance between A and B



A. R

B. $\frac{3R}{4}$

C. $\frac{R}{2}$


D. $2R$

Answer: C



Watch Video Solution

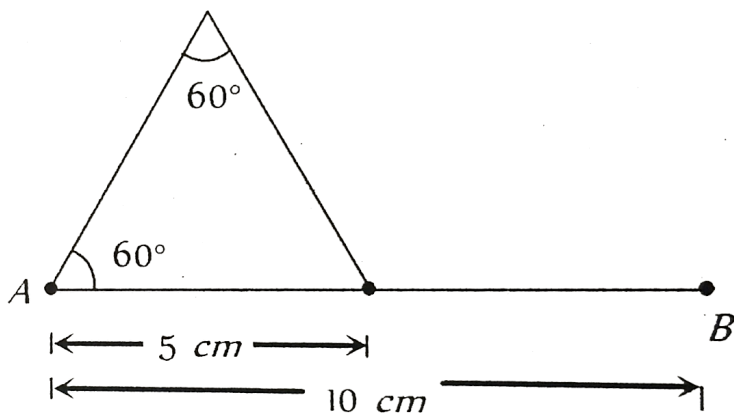14. A wire has resistance of 24Ω is bent in the following shape. The effective resistance between A and B is



A. 24Ω

B. 10Ω

C. $\frac{16}{3}\Omega$

D. None of these


Answer: B



Watch Video Solution

Kirchhoff S Law And Grouping Cells

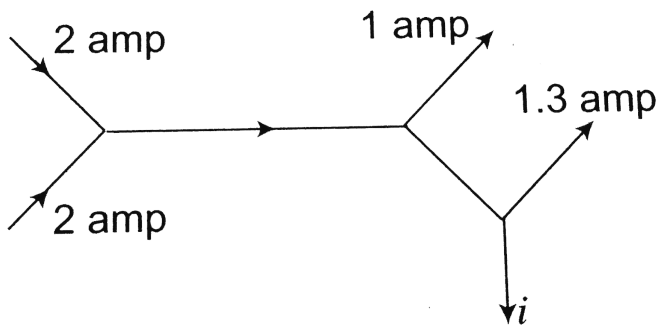1. The figure below shows current in a part of electric circuit. The current i is



A. 1.7amp

B. 3.7amp

C. 1.3amp


D. 1amp

Answer: A



Watch Video Solution

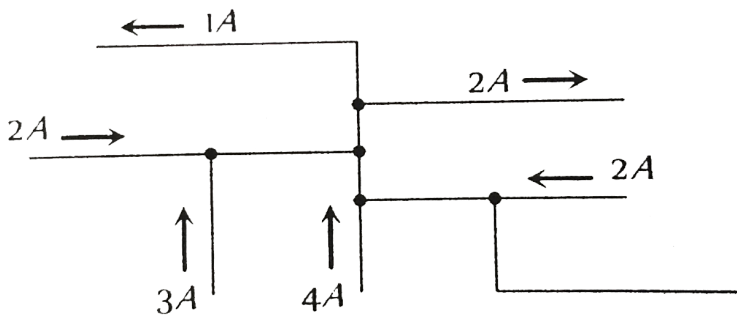2. The figure here shows a portion of a circuit. What are the magnitude and direction of the current i in the lower right-hand wire



A. $7A$

B. 8A


C. 6A

D. 2A

Answer: B



Watch Video Solution

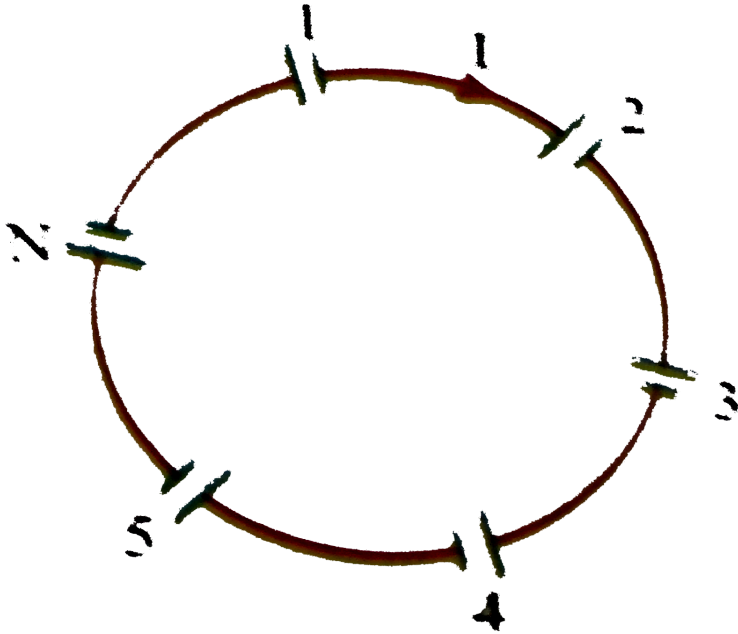

3.

A group of N cells where e.m.f. varies directly with the internal resistance as per the equation $E_N = 1.5r_N$ are connected as shown in the figure. The current I in the circuit is:

A. 0.51amp

B. 5.1amp

C. 0.15amp

D. 1.5amp


Answer: D



Watch Video Solution

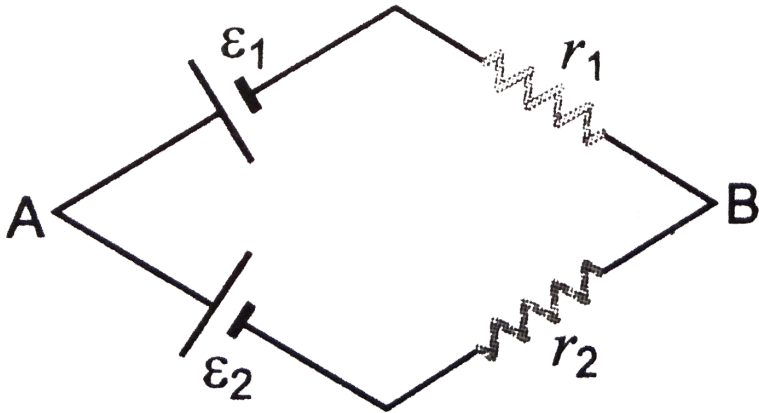4. Two batteries of emf ε_1 and ε_2 ($\varepsilon_2 > \varepsilon_1$ and internal resistances r_1 and r_2 respectively are

connected in parallel as shown in Fig. 2 (EP).1.



A. Two equivalent emf ϵ_{eq} of the two cells is

between ϵ_1 and ϵ_2 .ie. $\epsilon_1 < \epsilon_{eq} < \epsilon_2$

B. The equivalent emf e_{eq} is smaller than ϵ_1

C. The $\epsilon_{eq} = \epsilon_1 + \epsilon_2$ always

D. ϵ_{eq} is independent of internal resistance

r_1 and r_2

Answer: A



Watch Video Solution

5. Twelve cells each having the same e.m.f are connected in series and are kept to a closed box. Some of the cell are connected in reverse order .The battery is connected in series with an ammeter an external resistance R and two cells of the same type as an in the battery .The current when they and support each other is 3 ampere and current is 2 ampere when the two

oppose each other. How many cells are connected in reverse order ?

A. 4

B. 1

C. 3

D. 2

Answer: B



Watch Video Solution

6. A battery of 24 cells each of emf 1.5 V and internal resistance 2Ω is to be connected in order to send the maximum current through a 12Ω resistor. The correct arrangement of cells will be

- A. 2 rows of 12 cells connected in parallel
- B. 3 rows of 8 cells connected in parallel
- C. 4 rows of 6 cells connected in parallel
- D. All of these



Answer: A



Watch Video Solution

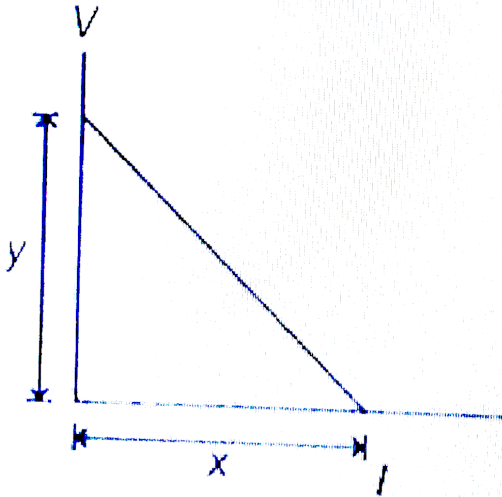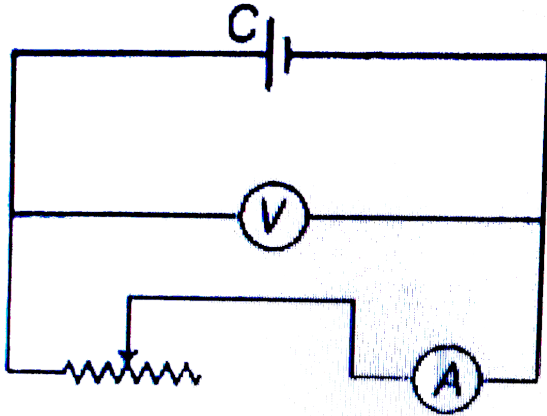7. The diagram shows a circuit used in an experiment to determine the emf and internal resistance of the cell C. A graph was plotted of the potential difference V between the terminals of the cell against the current I , which was varied by adjusting the rheostat.

What is the internal resistance of the cell?



A. xy

B. y/x

C. x/y

D. $(x-y)$


Answer: B



Watch Video Solution

8. In the circuit shown in fig. the magnitudes and the direction of the flow of current,

respectively, would be

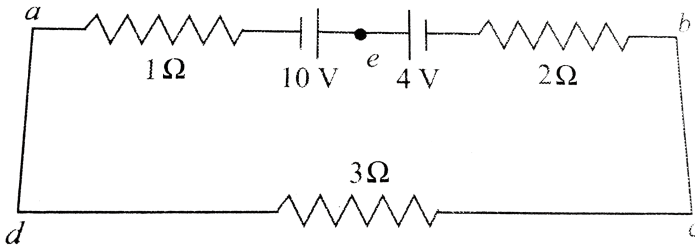


- A. $7/3$ A from a to b through c
- B. $7/3$ A from b to a through c
- C. 1 A from b to a through c
- D. 1A from a to b through c

Answer: B



Watch Video Solution

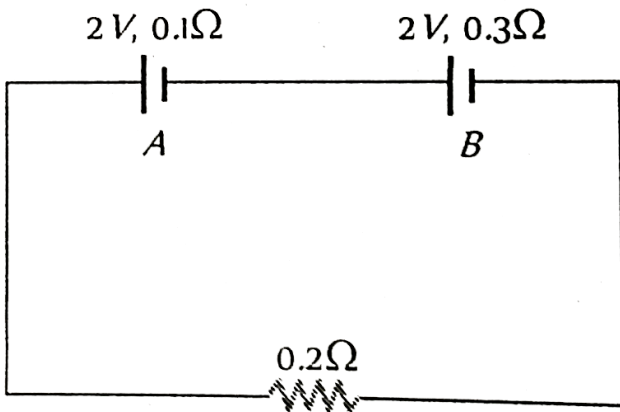9. The internal resistances of two cells shown are 0.1Ω and 0.3Ω . If $R = 0.2\Omega$, its potential difference across the cell



- A. B will be zero
- B. A will be zero
- C. A and B will be 2V

D. A will be gt 2V and B will be lt 2V

Answer: D



Watch Video Solution

10. Two cells, Having the same e.m.f., are connected in series through an external resistance R . Cell have internal resistances R_1 and R_2 ($R_1 > R_2$) respectively. When the circuit is closed, the potential difference across the first cell is zero. The value of R is:-

A. $r_1 + r_2$

B. $r_1 - r_2$

C. $\frac{r_1 + r_2}{2}$

D. $\frac{r - (1) - r_2}{2}$

Answer: A




Watch Video Solution

11. In the circuit shown here,

$$E_1 = E_2 = E_3 = 2V \text{ and } R_1 = R_2 = 4\text{ohms}$$

. The current flowing between point A and B

through battery E_2 is

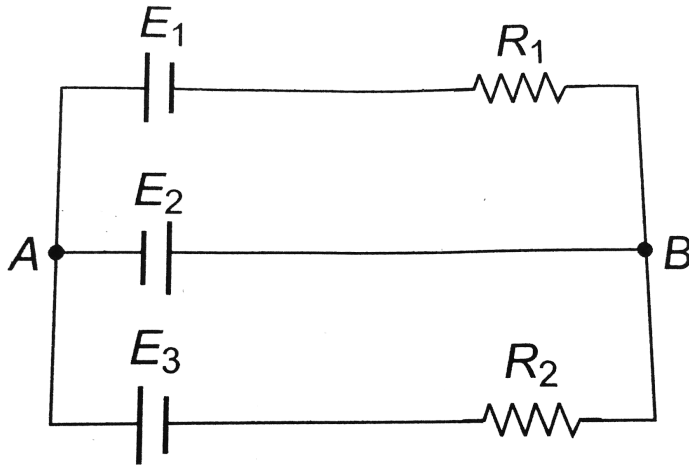

- A. zero
- B. 2A from A to B
- C. 2A from B to A
- D. None of the above


Answer: B



Watch Video Solution

12. Consider the circuit shown in the figure.

The current I_3 is equal to

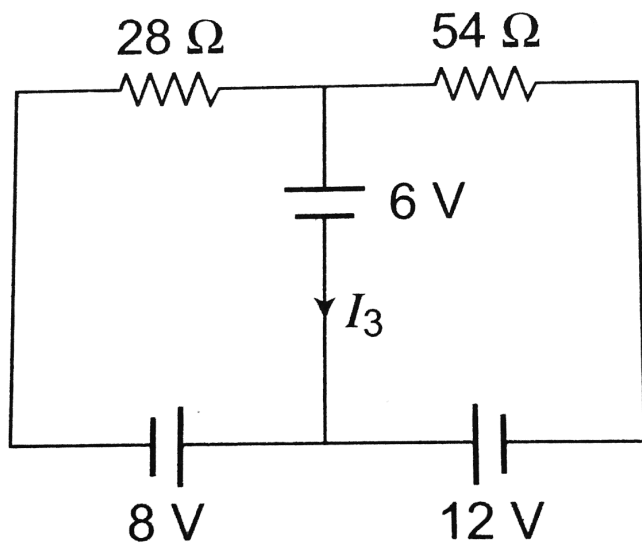

A. 5A

B. $3A$

C. $-3A$


D. $-\frac{5}{6}A$

Answer: D



Watch Video Solution

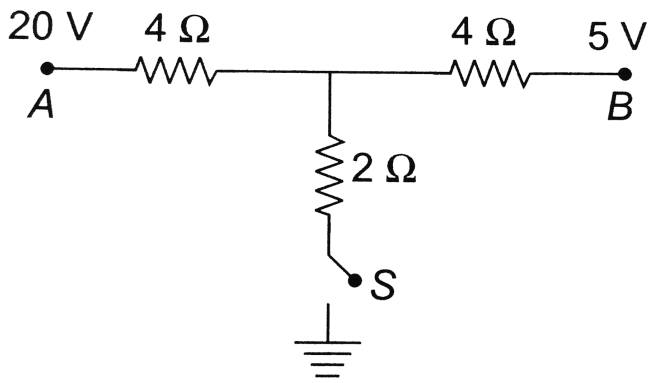13. As the switch S is closed in the circuit shown in figure, current passed through it is.



A. 4.5A

B. 6.0A

C. 3.0A


D. Zero

Answer: C



Watch Video Solution

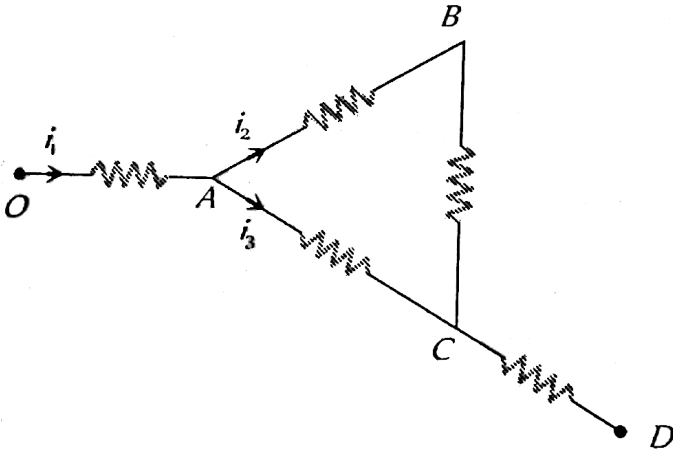14. The current in the arm CD of the circuit will be



A. i_1

B. $i_2 + i_3$

C. $I_1 + i_3$

D. $i_1 - i_2 + i_3$

Answer: A::B



Watch Video Solution

15. Kirchoff's junction rule is a reflection of

A. conservation of current density vector

B. conservation of charge

C. the fact that the momentum with which
a charged particle approaches a junction

is unchanged (as a vector) as the charged particle leaves the junction

D. the fact that there is no accumulation of charges at a junction


Answer: B::D



Watch Video Solution

Kirchhoff S Law And Simple Circuits

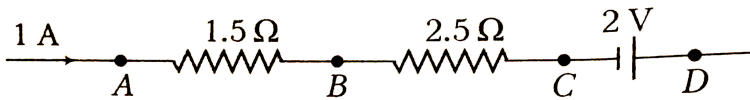1. In the circuit element given here, if the potential at point B, $V_B = 0$, then the potentials of A and D are given as



A. $V_A = -1.5V, V_D = +2.5V$


B. $V_A = +1.5V, V_D = +2.5V$

C. $V_A = +1.5V, V_D = +0.5V$

D. $V_A = +1.5V, V_D = -0.5V$

Answer: D

2. The magnitude in i in ampere unit is

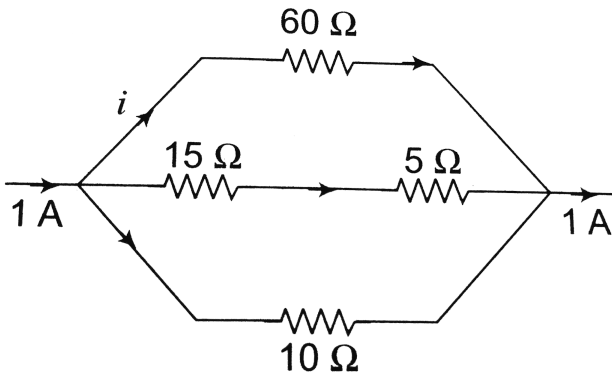

A. 0.1

B. 0.3

C. 0.6

D. None of these


Answer: A



Watch Video Solution

3. If in the circuit shown below, the internal resistance of the battery is 1.5Ω and V_P and V_Q are the potential at P and Q respectively, what is the potential difference between the

point P and Q ?

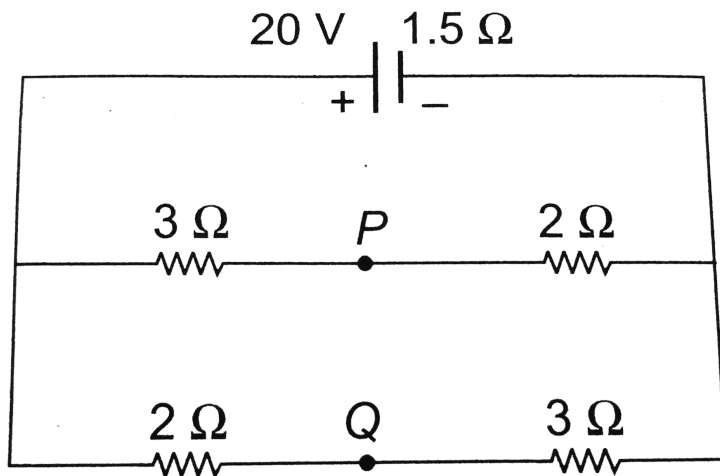


Watch Video Solution

4. In the circuit shown below

$$E_1 = 4.0V, R_1 = 2\Omega, E_2 = 6.0V, R_2 = 4\Omega$$

and $R_3 = 2\Omega$. The current I_1 is

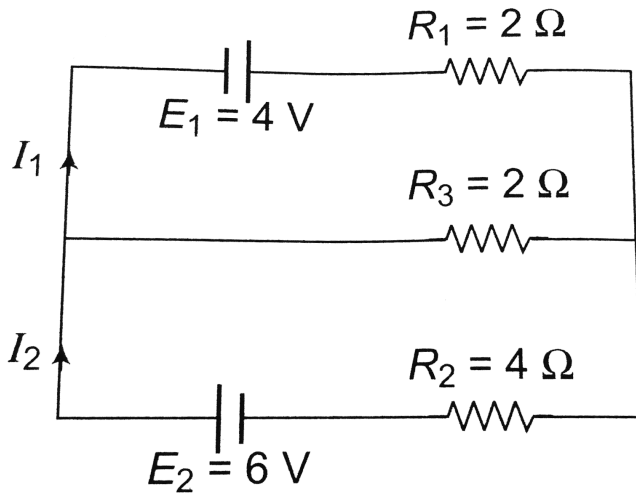


- A. 1.6A
- B. 1.8A
- C. 1.25A
- D. 1.0A

Answer: B




Watch Video Solution

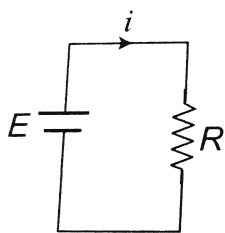5. Consider the circuit shown in the figure. Both the circuits are taking same current from battery but current through R in the second circuit is $\frac{1}{10}$ th of current through R in the first circuit. If R is 11Ω , the value of R_1



(a)

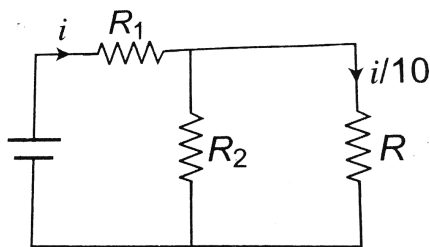

(b)

A. 9.9Ω

B. 11Ω

C. 8.8Ω


D. 7.7Ω

Answer: A



Watch Video Solution

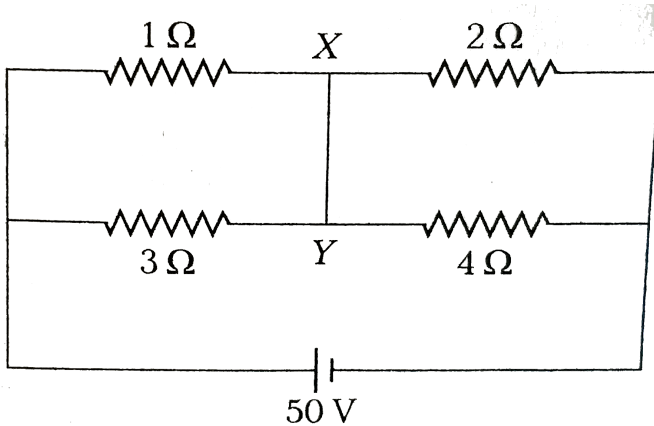6. Current through wire XY of circuit shown is



A. 1A

B. 4A

C. 2A from B to A


D. 3A

Answer: C



Watch Video Solution

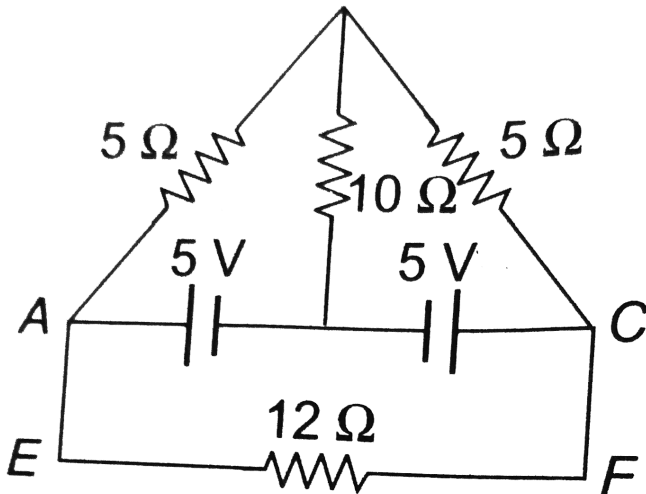7. In the circuit of adjoining figure the current through 12Ω resistor will be



A. 1 A

B. $1/5\text{ A}$

C. 2/5A

D. 0A

Answer: D



Watch Video Solution


8. The circuit is shown in the following figure.

The potential at points A, B, C, D and O are

given. The currents in the resistance R_1 , R_2

and R_3 are in the ratio of 4:2:1. What is the

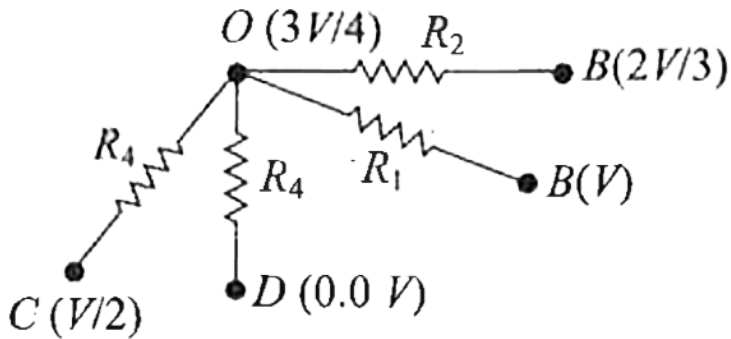ratio of resistance R_1 , R_2 , R_3 and R_4 ?



A. 3 : 2 : 12 : 16

B. 2 : 3 : 36 : 12

C. 4 : 3 : 12 : 32


D. 3 : 4 : 14 : 32

Answer: A



Watch Video Solution

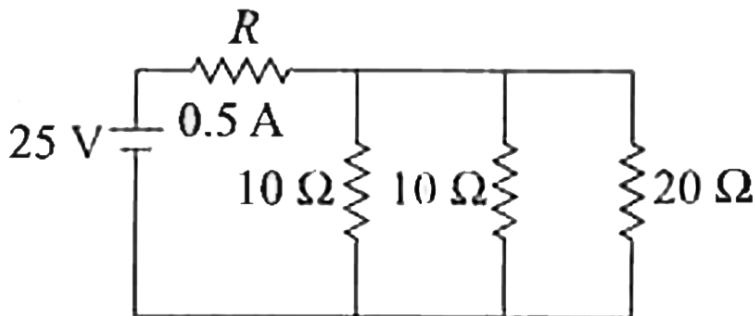9. In the circuit as shown if the current drawn through battery is 0.5 A . Then



A. Resistance $R = 46\ \Omega$

B. Current through $20\ \Omega$ resistance is 0.1 A


C. Potential difference across the middle resistance is 2 V

D. Potential difference across the 20Ω resistance is 4V

Answer: A::B::C



Watch Video Solution

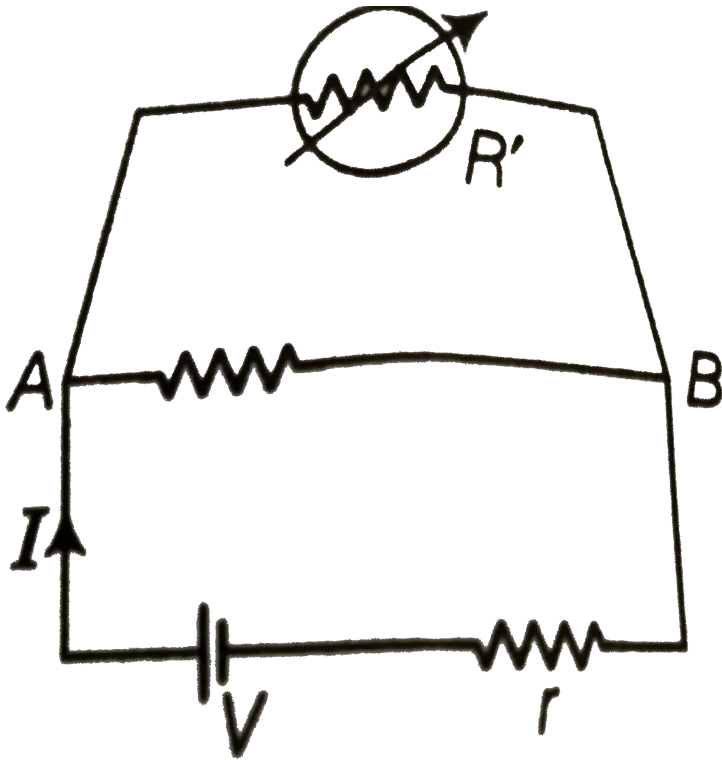

10.

Consider a simple circuit shown in figure stands for a variable resistance R' . R' can vary from R_0 to infinity. R is internal resistance of the battery ($r \ll R \ll R_0$).

A. Potential drop across AB is nearly constant as R' is varied

B. Current through R' is nearly a constant as R' is varied

C. Current I depends sensitivity on R'


D. $I \geq \left(\frac{V}{r + R} \right)$ always

Answer: A::D



Watch Video Solution

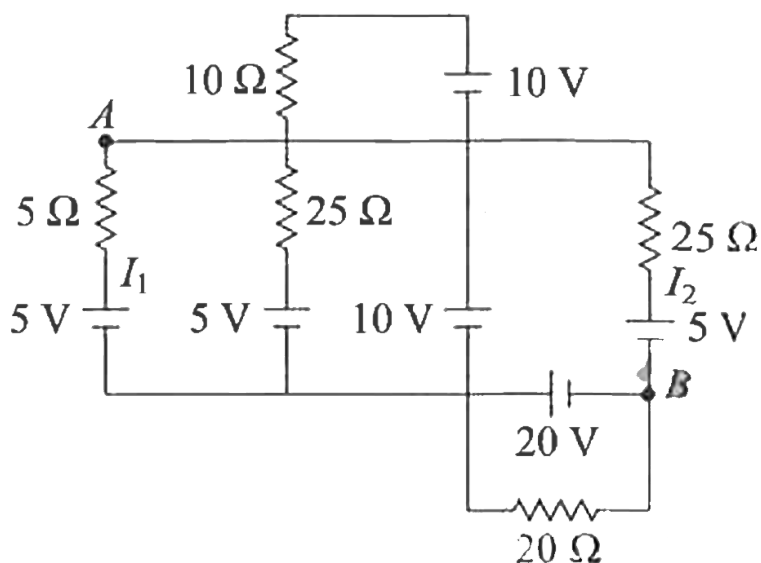11. The circuit consists of resistors and ideal cells. I_1 and I_2 are current through branches indicated in the figure, V_A and V_B is the potential at points A and B on the circuit



The value of $\frac{I_2}{I_1}$ is:

A. 1

B. 2

C. 3


D. 4

Answer: A



Watch Video Solution

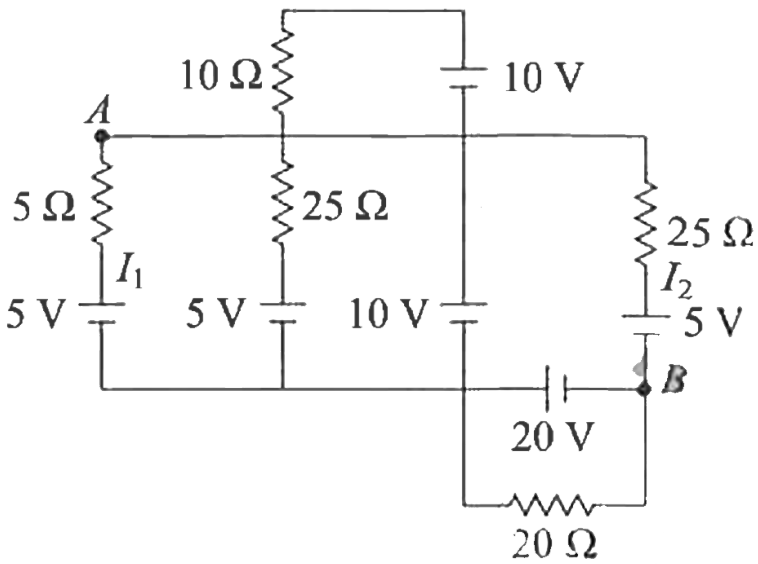12. The circuit consists of resistors and ideal cells. I_1 and I_2 are current through branches indicated in the figure, V_A and V_B is the potential at points A and B on the circuit



The value of $V_A - V_B$ in volts is:


- A. 5
- B. 10
- C. 15
- D. 30

Answer: D



Watch Video Solution

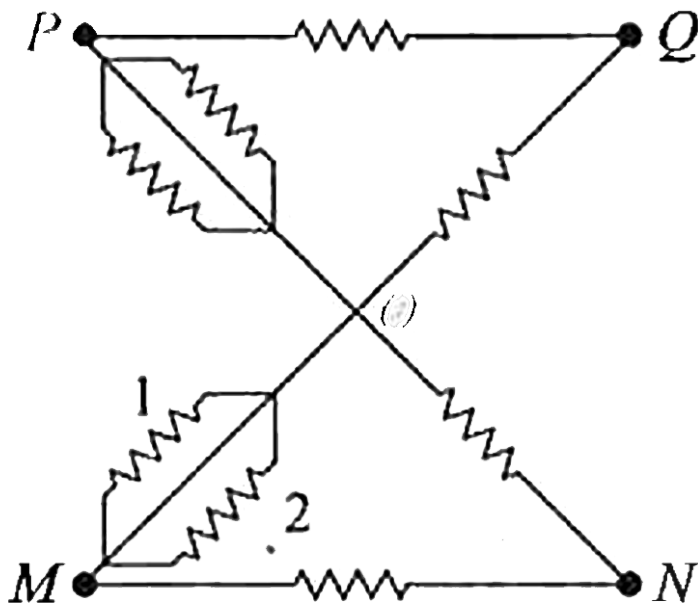13. In the given circuit, if resistance of each resistor is R :



Find the equivalent resistance between M and N,

A. $\frac{5}{2}R$

B. $5R$

C. $\left(\frac{31}{10}\right)R$


D. $\left(\frac{3}{5}\right)R$

Answer: D



Watch Video Solution

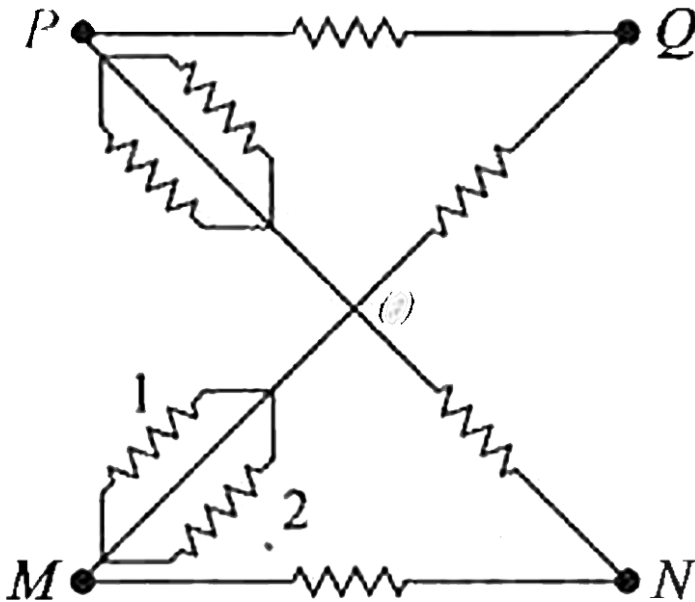14. In the given circuit, if resistance of each resistor is R :
resistor is R :



How much current will flow through resistor 1,
if current entered at M is I :

A. $\frac{I}{5}$

B. $2\frac{l}{5}$

C. $3\frac{I}{5}$


D. $4\frac{I}{5}$

Answer: A



Watch Video Solution

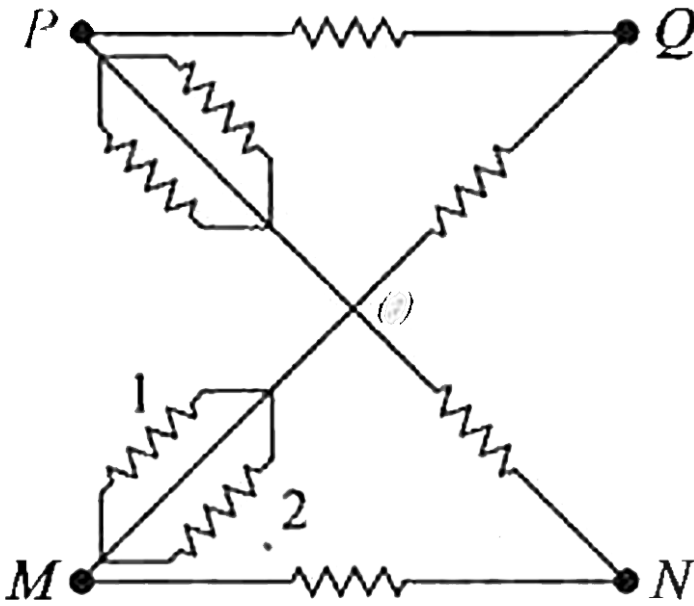15. In the given circuit, if resistance of each resistor is R:



The equivalent resistance between M and Q.

A. $\frac{R}{2}$

B. $\frac{R}{3}$

C. R

D. 2R

Answer: C



Watch Video Solution