



# PHYSICS

## BOOKS - CENGAGE PHYSICS (ENGLISH)

### INDUCTANCE

#### Illustration

1. A small square loop of wire of side  $l$  is placed inside a large square loop of wire of side  $L$  ( $L > l$ ). The loops are coplanar and their

centres coincide. What is the mutual inductance of the system?



[Watch Video Solution](#)

2. What is the mutual inductance of a system of coaxial cables carrying current in opposite directions as shown in Fig. 4.3. Their radii are  $a$  and  $b$ , respectively.



[Watch Video Solution](#)



3. The equivalent inductance of two inductors is 2.4 H when connected in parallel and 10 H when connected in series. What is the value of inductances of the individual inductors?



[Watch Video Solution](#)

4. What will happen to the inductance of a solenoid

a. when the number of turns and the length are double keeping the area of cross section

same?

b. when the air inside the solenoid is replaced by iron of relative permeability  $\mu_r$ ?



[Watch Video Solution](#)

5. In Fig. coil 1 and coil 2 are wound on a long cylindrical insulator. The ends  $A'$  and  $B$  are joined together and current  $I$  is passed. Self-inductance of the two coils are  $L_1$  and  $L_2$ , and their mutual inductance is  $M$ .

a. Show that this combination can be replaced


by a single coil of equivalent inductance given

by

$$L_{eq} = L_1 + L_2 + 2M.$$


b. How could the coils be reconnected by yielding an equivalent inductance of

$$L_{eq} = L_1 + L_2 - 2M.$$

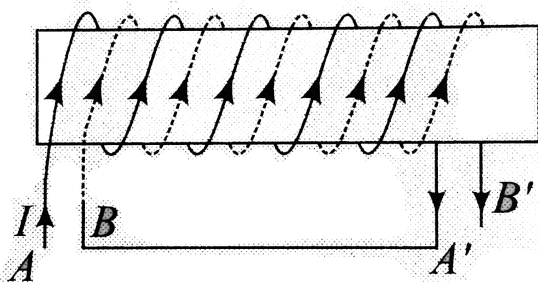

Watch Video Solution

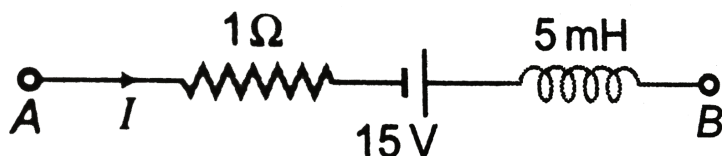
6. The network shown in the figure is a part of complete circuit. What is the potential difference  $V_B - V_A$  when the current  $I$  is  $5A$  and is decreasing at a rate of  $10^3 A / s$ ?



[Watch Video Solution](#)

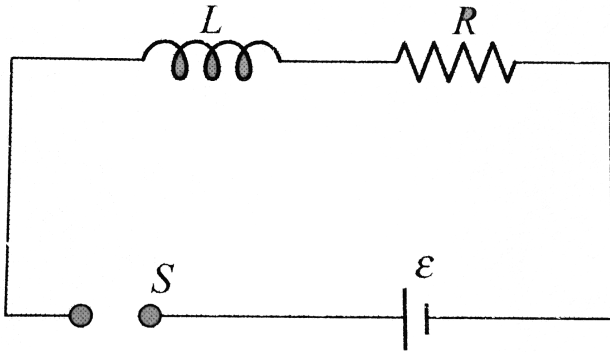7. In an  $LR$  circuit as shows in Fig.when the swtich is closed, how much time will it take for the current to grow to a value  $n$  times the

maximum value of current (where  $n < 1$ )?




[Watch Video Solution](#)

8. In the circuit shown in Fig. the initial current through the inductor at  $t = 0$  is  $I_0$ . After a time  $t = L/R$ , the switch is quickly shifted to position 2.

a. Plot a graph showing the variation of current with time.

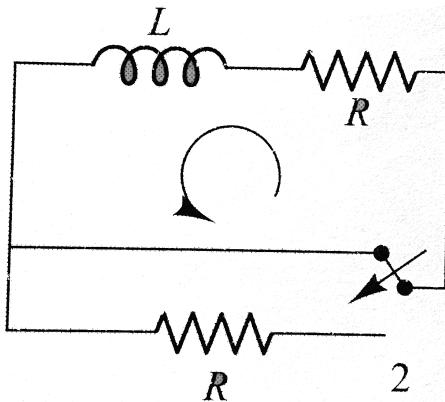b. Calculate the value of current in the

inductor at  $t = \frac{3}{2} \frac{L}{R}$ .



[Watch Video Solution](#)


9. During the decay of current in an  $LR$  circuit, if the current falls to  $\eta$  times the initial value in time  $T$ , then determine the value of time constant.



[Watch Video Solution](#)

10. In the following circuit (Fig.) the switch is closed at  $t = 0$ . Initially, there is no current in inductor. Find out the equation of current in

the inductor coil as a function of time.

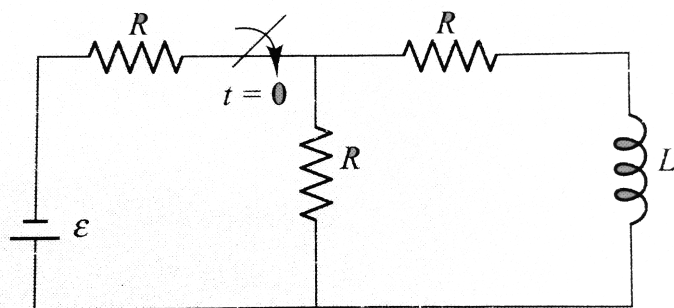


[Watch Video Solution](#)

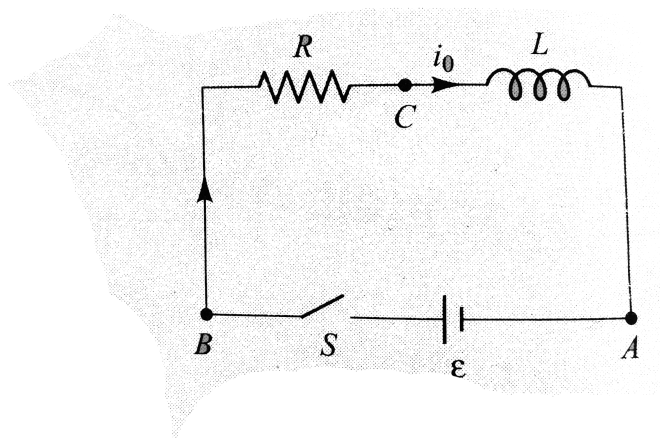**11.** Figure shows a circuit consisting of an ideal cell, an inductor  $L$ , and a resistor  $R$ , connected in series. Let switch  $S$  be closed at  $t = 0$ . Suppose at  $t = 0$ , the current in the




inductor is  $i_0$ , then find out the equation of current as a function of time.



[Watch Video Solution](#)

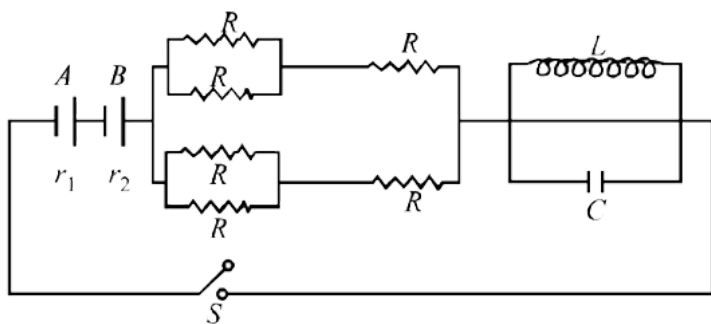**12.** In the figure both cells A and B are of equal emf. Find  $R$  for which potential difference across battery A will be zero, long time after

the switch is closed. Internal resistance of batteries A and B ( $r_1$ ) and ( $r_2$ ) respectively ( $r_1 > r_2$ ).



[Watch Video Solution](#)

**13.** Consider the  $RL$  circuit in Fig. When the switch is closed in position 1 and opens in

position 2, electrical work must be performed on the inductor and on the resistor. The energy stored in the inductor is for the resistor energy appears as heat.

a. What is the ratio of  $P_L / P_R$  of the rate at which energy is stored in the inductor to the rate at which energy is dissipated in the resistor?

b. Express the ratio  $P_L / P_R$  as a function of time.

c. If the time constant of circuit is  $t$ , what is the time at which  $P_L = P_R$ ?



**Watch Video Solution**

14. Derive an expression for the total magnetic energy stored in two coils with inductances  $L_1$  and  $L_2$  and mutual inductance  $M$ , when the currents in the coils are  $I_1$  and  $I_2$ , respectively.




[Watch Video Solution](#)

15. In an  $LC$  circuit as shows in Fig. the switch is closed at  $t = 0$ .  $Q_{\max} = 100\mu C$ ,  $L = 40mH$ ,  $C = 100\mu F$ .

a. Determine the equation for instantaneous change on the capacitor.

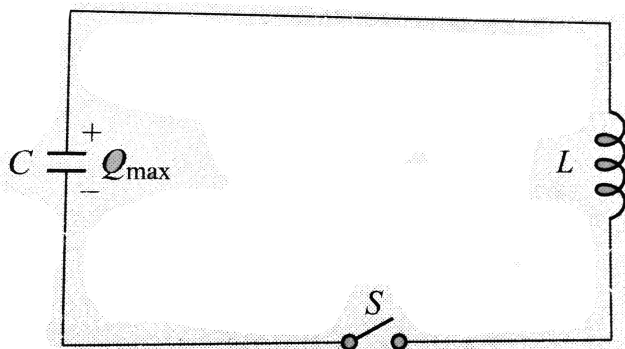
b. Determine the equation for instantaneous current in the circuit.



 [Watch Video Solution](#)

**16.** Initially the  $900\mu F$  capacitor is charged to  $100V$  and the  $100\mu F$  capacitor is uncharged in

Fig. Then switch  $S_2$  is closed for time  $t_1$ , after which it is opened and at the same instant switch  $S_1$  is closed for time  $t_2$  and then opened. It is now found that  $100\mu F$  capacitor is charged to  $300V$ . Find the minimum possible value of the time interval  $t_1$  and  $t_2$ .

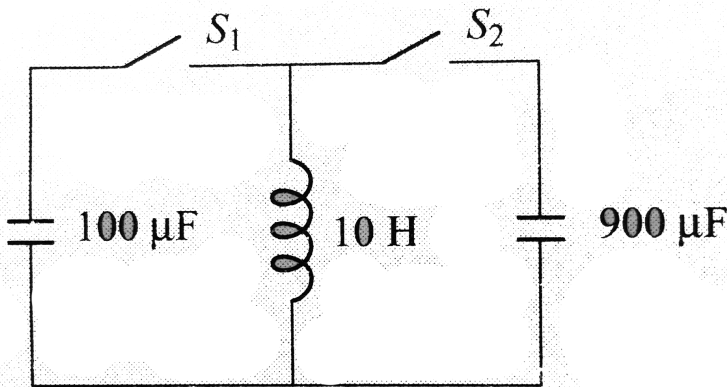


 [Watch Video Solution](#)

17. The circuit shown in Fig. is in the steady state with switch  $S_1$  closed. At  $t = 0$ ,  $S_1$  is opened and switch  $S_2$  is closed.

a. Derive an expression for the charge on capacitor  $C_2$  as a function of time.

b. Determine the first instant  $t$ , when the energy in the inductor becomes one-third of

that in the capacitor.

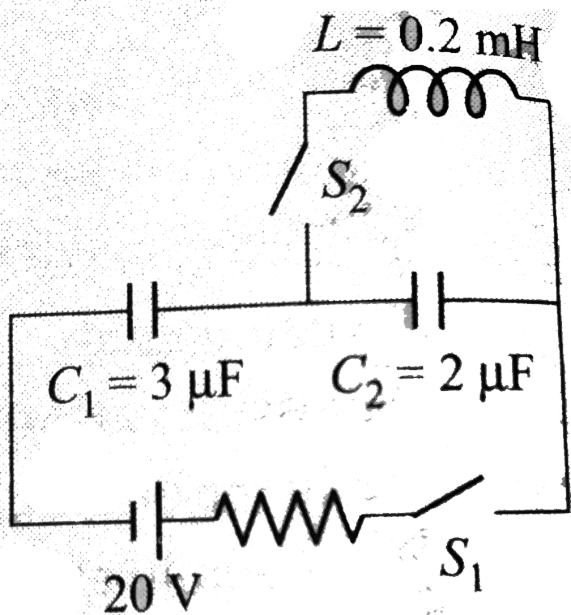


Watch Video Solution

**18.** In the circuit shows in Fig. the battery has negligible internal resistance. Show that the



current in the circuit through the battery rises instantly to its steady state value  $E/R$  when the switch is closed, provided that resistance

$R$  is  $\sqrt{L/C}$ .

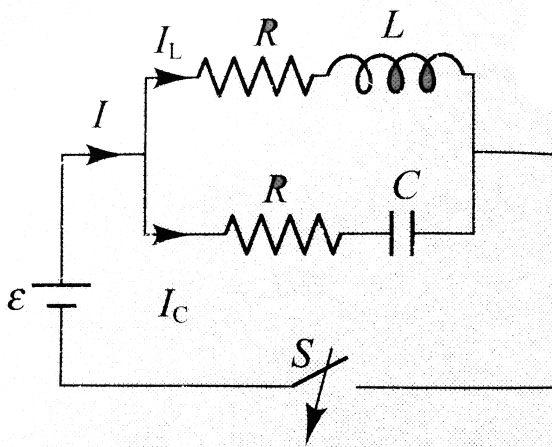

**Watch Video Solution**

19. An inductor of inductance  $2.0\text{mH}$  is connected across a charged capacitor of capacitance  $5.0\mu\text{F}$  and the resulting  $L - C$  circuit is set oscillating at its natural frequency. Let  $Q$  denotes the instantaneous charge on the capacitor and  $I$  the current in the circuit. It is found that the maximum value of  $Q$  is  $200\mu\text{C}$ .



[Watch Video Solution](#)

1. A metal bar AB can slide on two parallel thick metallic rails separated by a distance  $l$ . A resistance  $R$  and an inductance  $L$  are connected to the rails as shown in the figure. A long straight wire carrying a constant current  $I_0$  is placed in the plane of the rails and perpendicular to them as shown. The bar AB is held at rest at a distance  $x_0$  from the long wire. At  $t=0$ , it is made to slide on the rails away from wire. Answer the following questions.


(a) Find a relation among  $i$ ,  $\frac{di}{dt}$  and  $\frac{d\phi}{dt}$ ,

where  $i$  is the current in the circuit and  $\phi$  is the flux of the magnetic field due to the long wire through the circuit.

(b) It is observed that at time  $t=T$ , the metal bar AB is at a distance of  $2x_0$  from the long wire and the resistance  $R$  carries a current ( $i_1$ ). Obtain an expression for the net charge that has flown through resistance  $R$  from  $t=0$  to  $t=T$ .


(c) The bar is suddenly stopped at time  $T$ . The current through resistance  $R$  is found to be  $\frac{i_1}{4}$  at time  $2T$ . Find the value of  $\frac{L}{R}$  in terms of

the other given quantities.

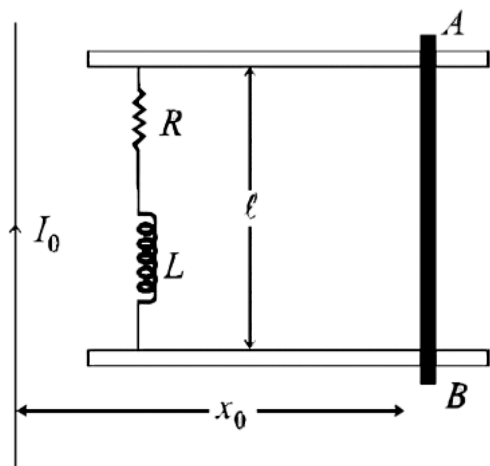

[Watch Video Solution](#)

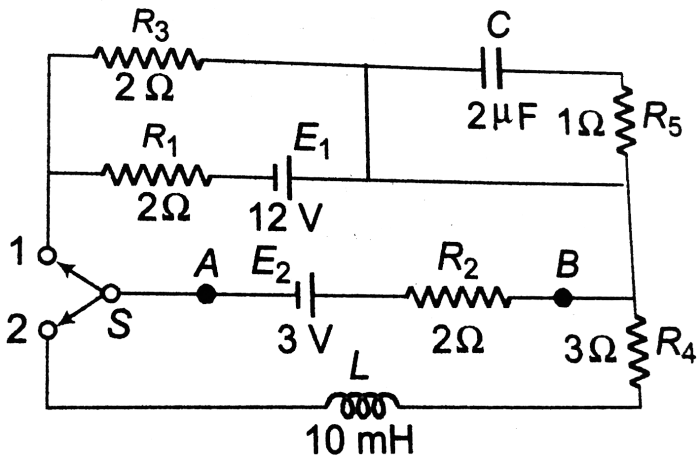
2. A circuit containing a two position switch  $S$  is shown in figure



- a. The switch  $S$  is in position 1. Find the potential difference  $V_A - V_B$  and the rate of production of joule heat in  $R_1$
- b. If now the switch  $S$  is put in position 2 at  $t = 0$ . Find  
 i) the steady current in  $R_4$  and  
 ii) the time when current in  $R_4$  is half the steady value. Also calculate the energy stored in the inductor  $L$  at that time.

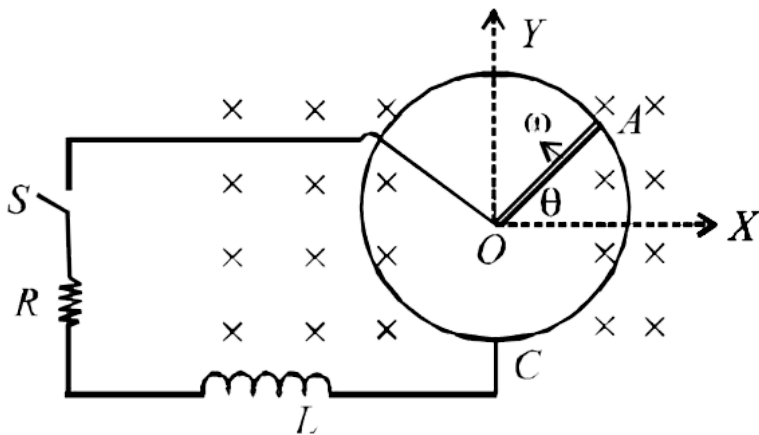3. A metal rod OA of mass 'm' and length 'r' is kept rotating with a constant angular speed  $\omega$  in a vertical plane about a horizontal axis at the end O. The free end A is arranged to slide without friction along fixed conduction circular ring in the same plane as that of rotation. A uniform and constant magnetic induction  $\vec{B}$  is applied perpendicular and into the plane of rotation as shown in the figure below. An inductor L and an external

resistance  $R$  are connected through a switch  $S$  between the point  $O$  and a point  $C$  on the ring to form an electrical circuit. Neglect the resistance of the ring and the rod. Initially, the switch is open.



- (a) What is the induced emf across the terminals of the switch?
- (b) The switch  $S$  is closed at time  $t=0$ .



(i) Obtain an expression for the current as a function of time.

(ii) In the steady state, obtain the time dependence of the torque required to maintain the constant angular speed, given that the rod OA was along the positive X-axis at  $t=0$ .




[Watch Video Solution](#)

## Exercise 4.1

1. The magnetic field  $B$  at all points within a circular region of the radius  $R$  is uniform space and directed into the plane of the page in figure. If the magnetic field is increasing at a rate  $dB/dt$  what are the magnitude and direction of the force on a stationary positive point charge  $q$  located at points  $a, b, c$ ? (Point  $a$  is a distance  $r$  above the centre of the region, point  $b$  is a distance  $r$  to the right to the centre and point  $c$  is at the centre of the


region).

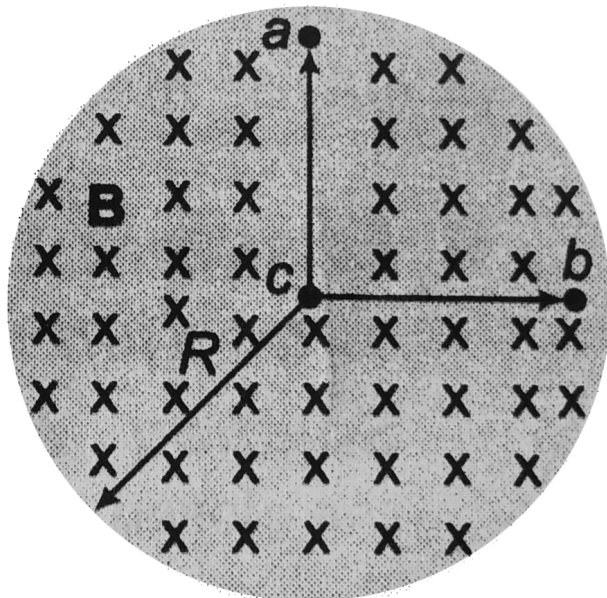

Watch Video Solution

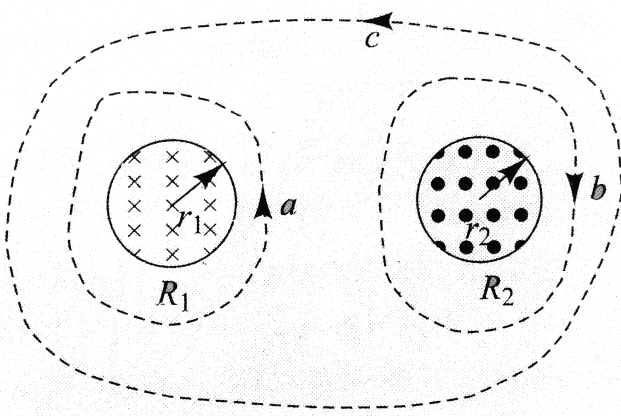
2. Figure shows two circular regions  $R_1$  and  $R_2$  with radii  $r_1 = 21.2\text{cm}$  and  $r_2 = 32.3\text{cm}$ ,

respectively. In  $R_1$  there is a uniform magnetic field  $B_1 = 48.6\text{mT}$  into the page and in  $R_2$  there is a uniform magnetic field  $B_2 = 77.2\text{mT}$  out of the page (ignore any fringing of these fields). Both fields are decreasing at the rate  $8.50\text{mT s}^{-1}$ . Calculate the integral  $\oint \vec{E} \cdot d\vec{l}$  for each of the three identical paths.



3. Figure shows five lettered regions in which a uniform magnetic field extends directly either out of the page (as in region  $a$ ) or into the page. The field is increasing in magnitude at the same steady rate in all five regions, the regions are identical in area. Also shown are four numbered paths along which  $\oint \vec{E} \cdot d\vec{l}$  has the magnitudes given below in terms of a quantity  $\text{mag.}$ . Determine whether the magnetic fields in regions  $b$  through  $e$  are

directed into or out of the page.

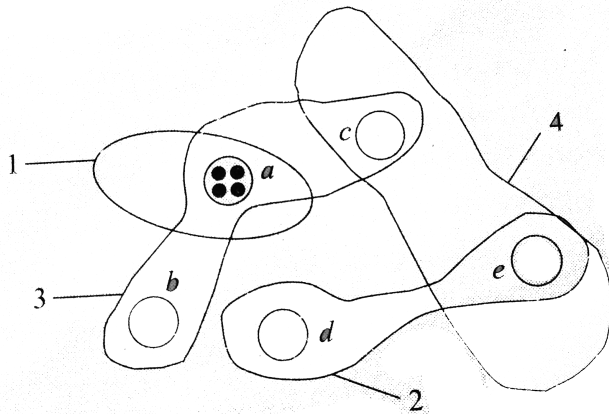

?

Path	1	2	3	4
$\oint \vec{E} \cdot d\vec{l}$	mag	2(mag)	3(mag)	0




**Watch Video Solution**

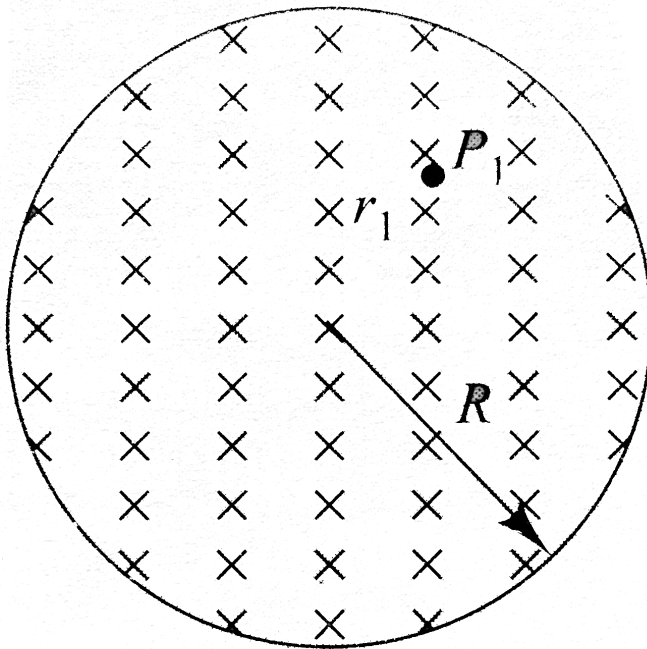4. A magnetic field directed into the page changes with time according to


$$B = (0.0300t^2 + 1.4.40)T, \text{ where } t \text{ is in}$$

seconds. The field has a circular cross section of radius  $R = 2.50\text{cm}$ . What are the magnitude and direction of the electric field at point  $P_1$  when  $t = 3.00\text{s}$  and  $r_1 = 0.0200\text{m}$ ?



[Watch Video Solution](#)

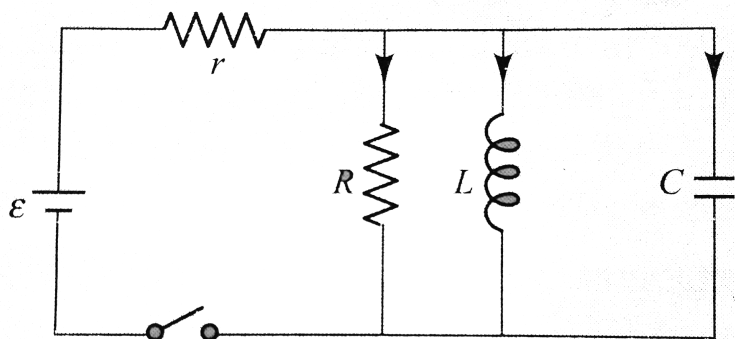5. Figure shows an  $LCR$  circuit. When the switch is closed, the currents through resistor  $R$ , inductor  $L$ , and capacitor  $C$  are  $I_1$ ,  $I_2$ , and  $I_3$ , respectively. Determine the values of  $I_1$ ,  $I_2$ , and  $I_3$ .



a. at  $t = 0$    b. at  $t = \infty$



**Watch Video Solution**



6. It has been proposed to use large inductors as energy storage devices.

a. How much electrical energy is converted to light and thermal energy by a  $200\text{ }\Omega$  light bulb in one day?

b. If the amount of energy calculated in part (a) is stored in an inductor in which the current is  $80.0\text{ A}$ , what is the inductance?



[Watch Video Solution](#)

7. A  $1 - k\Omega$  resistor is connected in series with a  $10 - mH$  inductor, a  $30V$  battery and an open switch. At time  $t = 0$ , the switch is suddenly closed.

a. What is the maximum current in this circuit and when does it occur?

b. What are the voltage drops across the inductor and across the resistor  $20\mu s$  after the switch is closed?

c. On a single set of axes, sketch the voltage across the resistor and the voltage across the inductor as functions of time. Also, sketch a

graph of the current in the circuit as a function of time.



[Watch Video Solution](#)

8. A capacitor with capacitance  $6 \times 10^{-5} F$  is charged by connecting it to a  $12 - V$  battery.

The capacitor is disconnected from the battery and connected across an inductor with  $L = 1.50H$ .

a. What are the angular frequency  $\omega$  of the electrical oscillations and the period of these

oscillations (the time for one oscillation)?

b. What is the initial charge on the capacitor?

c. How much energy is initially stored in the capacitor?

d. What is the charge on the capacitor  $0.0230$  s after the connecting to the inductor is made? Interpret the sign of the your answer.

e. At the times given in part (d), what is the current in the inductor? Interpret the sign of your answer.


f. At the time given in part (d), how much electrical energy is stored in the capacitor and how much is stored in the inductor?



Watch Video Solution

9. In the circuit shows in Fig. ,  $E = 10V$ ,  $R_1 = 5\Omega$ ,  $R_2 = 10\Omega$ , and  $L = 5H$ . For the two separate conditions, (i) switch  $S$  is just closed and (ii) switch  $S$  is closed for a long time, calculate
- current  $i_1$  through  $R_1$ ,
  - current  $i_2$  through  $R_2$ ,
  - current  $i$  through the switches,
  - the potential difference across  $R_2$ ,
  - the potential difference across  $L$ ,

f.  $di_2/dt$ .

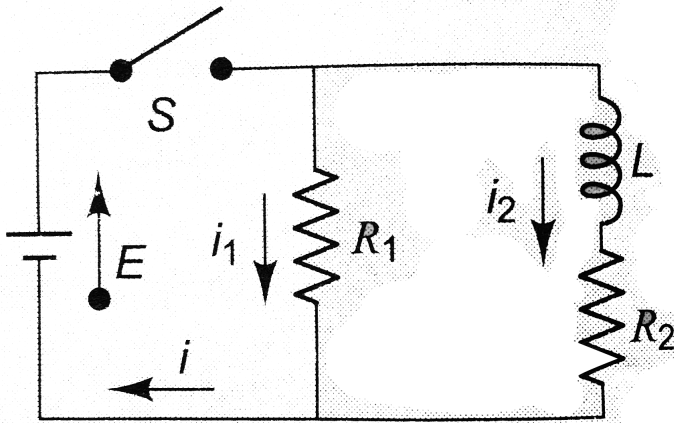

Watch Video Solution


**10.** In Fig. the switch is closed and steady-state conditions are established. The switch is thrown open at  $t = 0$ .

a. Find the initial voltage  $E_0$  across  $L$  just


after  $t = 0$ . Which end of the coil is at the higher potential :  $a$  or  $b$ ?

b. Make freehand graphs of the current in  $R_1$  and  $R_2$  as a function of time, treating the steady-state directions as positive. Show values before and after  $t = 0$ .

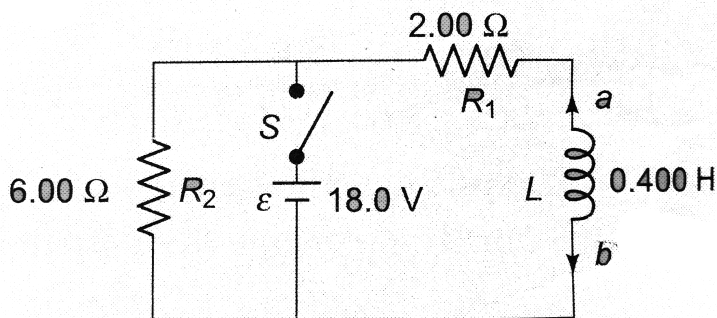c. How long after  $t = 0$  does the current in  $R_2$  have the value  $2\text{mA}$ ?



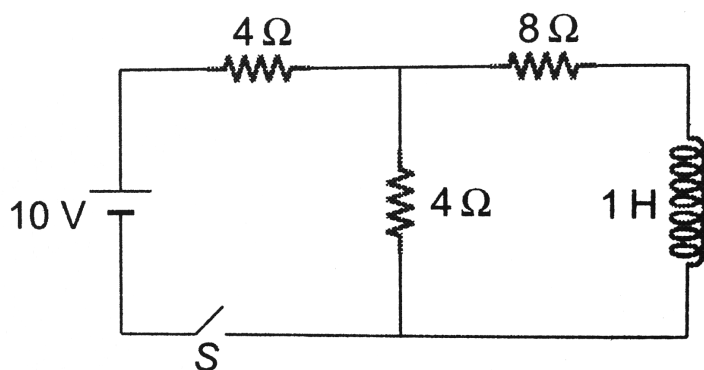11. The switch in figure is closed at time  $t = 0$ . Find the current in the inductor and the current through the switch as functions of time thereafter.



[Watch Video Solution](#)




12.  $AB$  is a part of circuit. Find the potential difference  $V_A - V_B$  if

a. current  $I = 2A$  and is constant,


b. current  $i = 2A$  and is increasing at the rate of  $1As^{-1}$ ,

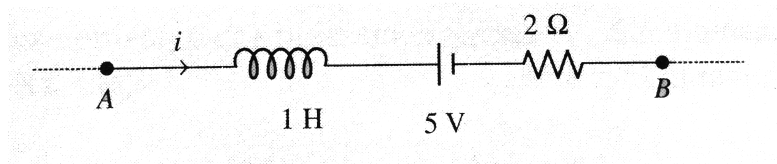c. current  $i = 2A$  and is decreasing at the rate  $1As^{-1}$ ,




[Watch Video Solution](#)

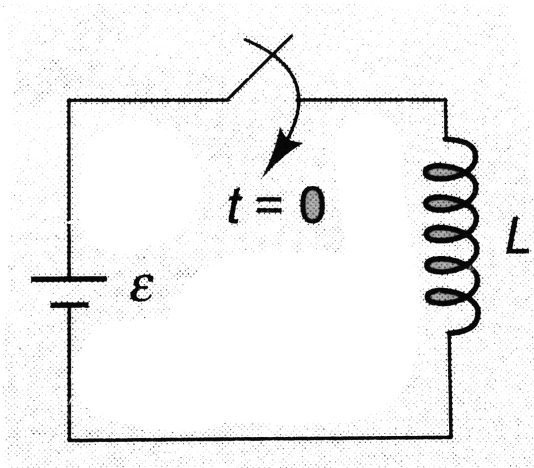**13.** A circuit contains an ideal cell and an inductor with a switch. Initially, the switch is open. It is closed at  $t = 0$ . Find the current as a function of time.




[Watch Video Solution](#)

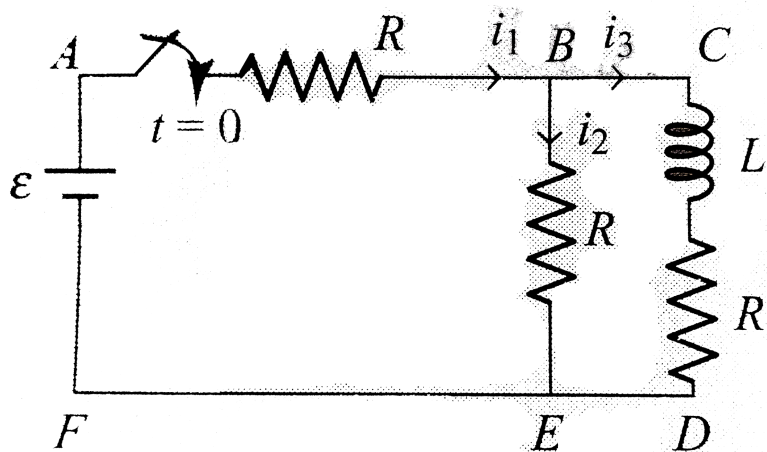14. In the following circuit (Fig.) the switch is closed at  $t = 0$ . Find the current  $i_1$ ,  $i_2$ ,  $i_3$  and  $di_3/dt$  at  $t = 0$  and at  $t = \infty$ . Initially, all current are zero.




Watch Video Solution

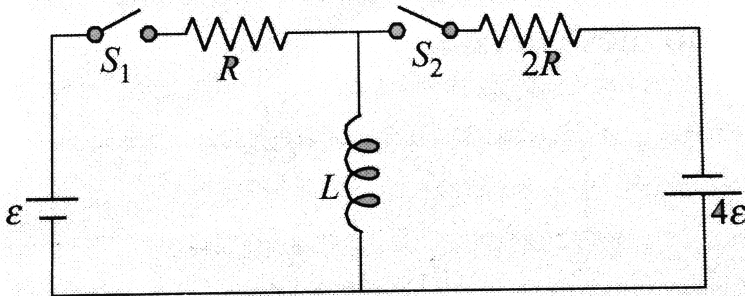15. In a circuit  $S_1$  remains closed for a long time and  $S_2$  remain open. Now  $S_2$  is closed and  $S_1$  is opened. Find out the  $di/dt$  in the right loop just after the moment.




**Watch Video Solution**

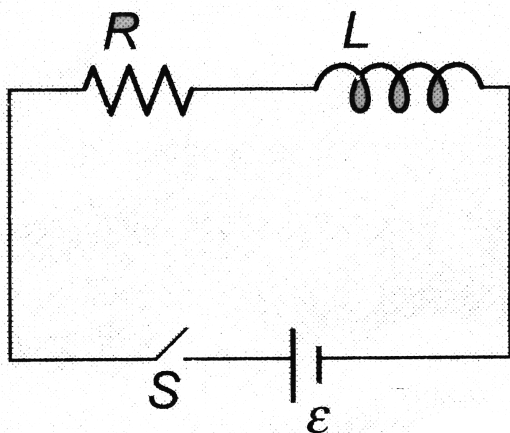16. At  $t = 0$ , switch  $S$  is closed (shown in Fig.). After a long time, suddenly the inductance of the inductor is made  $\eta$  times lesser ( $L/\eta$ ) than its initial value. Find out current just after the operation.



Watch Video Solution

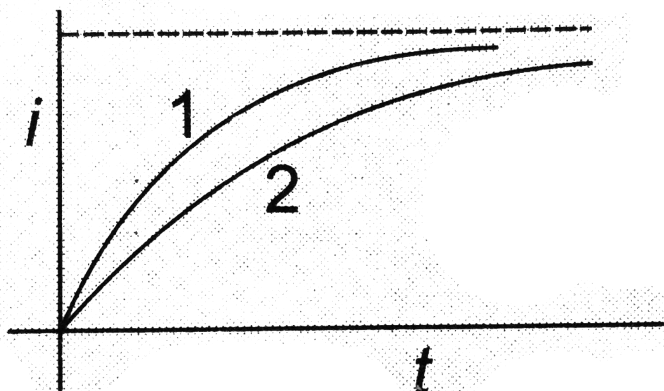17. Which of the two curves shows has lesser time constant.



Watch Video Solution

18. Two insulated wires are wound on the same hollow cylinder, so as to form two solenoids sharing a common air-filled core. Let  $l$  be the


length of the core,  $A$  the cross-sectional area of the core,  $N_1$  the number of times the first wire is wound around the core, and  $N_2$  the number of times the second wire is wound around the core. Find the mutual inductance of the two solenoids, neglecting the end effects.



[Watch Video Solution](#)

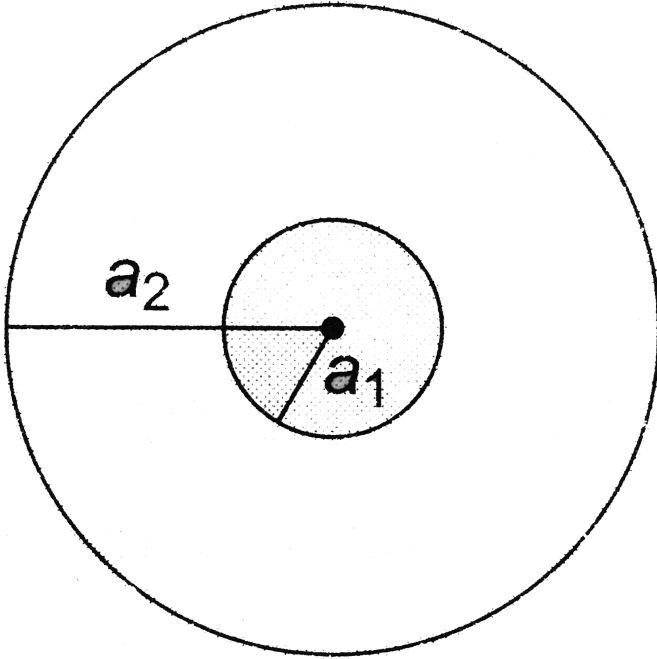**19.** Find the mutual inductance of two concentric coils of radii  $a_1$  and

$a_2 (a_1 < a_2)$  if the planes of the coils are same.



**Watch Video Solution**



**20.** Solve problem 19 if the planes of the coils are perpendicular.



**Watch Video Solution**

**21.** Find the mutual inductance of two concentric coils of radii  $a_1$  and  $a_2$  ( $a_1 < a_2$ ) if the planes of the coils are perpendicular.




**Watch Video Solution**

22. Figure. shows two concentric coplanar coils with radii  $a$  and  $b$  ( $a < b$ ). A current  $I = 2t$  flows in the smaller loop. Neglecting self-inductance of the larger loop,

- a. find the mutual inductance of the two coils,
- b. find the emf induced in the larger coil,
- c. if the resistance of the larger loop is  $R$ , find


the current in it as a function of time.

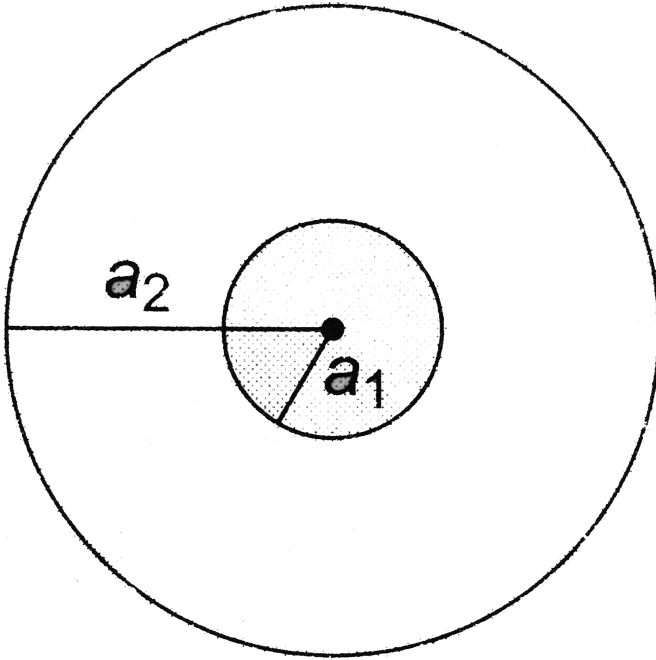

**Watch Video Solution**

**23.** Figure. shows two concentric coplanar coils with radii  $a$  and  $b$  ( $a < b$ ). A current  $I = 2t$  flows in the smaller loop. Neglecting self-inductance of the larger loop, if a capacitor of capacitance  $C$  is also connected in the larger loop as shows in Fig . , find the charge on the


capacitor as a function of time.

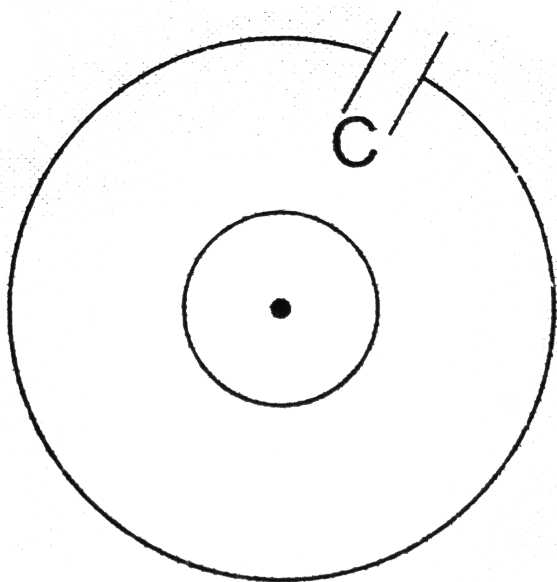

[Watch Video Solution](#)

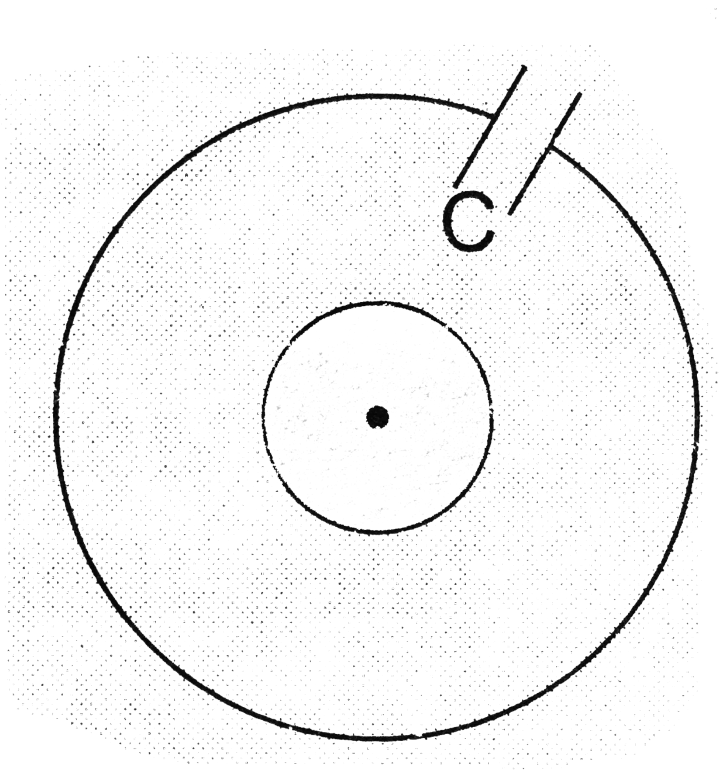24. If the current in the inner loop changes according to  $I = 2t^2$  (Fig .), then find the

current in the capacitor as a function of time.



[Watch Video Solution](#)


Exercises (subjective)

1. In Fig. a uniform magnetic field decrease at a constant rate  $\frac{dB}{dt} = K$ , where  $K$  is a positive constant. Circular loop of wire of radius  $a$  containing a resistance  $R$  and a capacitance  $C$  is placed with its plane normal to the field.

a. Find the charge  $Q$  on the capacitor when it is fully charged.

b. Which plate is at higher potential when it is

fully charged?

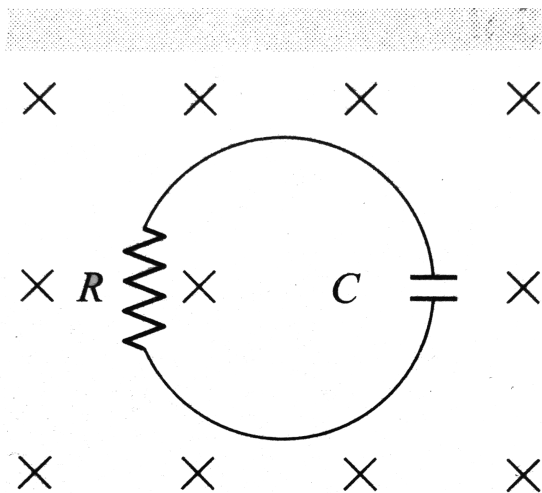


[Watch Video Solution](#)

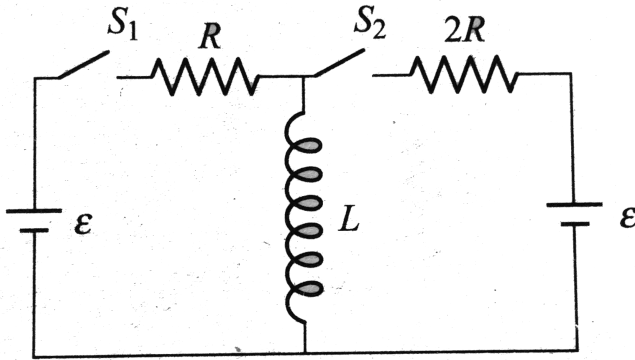2. In the circuits shows in  $S_1$  and  $S_2$  are switches.  $S_2$  remains closed for a long time and  $S_1$  is opened. Now  $S_1$  is also closed. Just after  $S_1$  is closed, find the potential difference




( $V$ ) across  $R$  and  $di/dt$  (with sign) in  $L$ .



[Watch Video Solution](#)

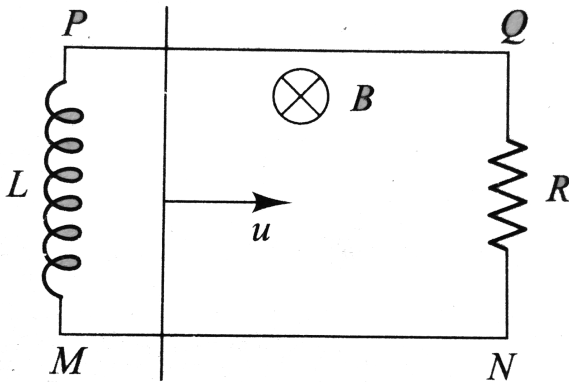3. In Fig a rod of length  $l$  and mass  $m$  moves with an initial velocity  $u$  on a fixed frame containing inductor  $L$  and resistance  $R$ .  $PQ$  and  $MN$  are smooth conducting wires. There

is a uniform magnetic field of strength  $B$ . Initially, there is no current in the inductor. Find the total charge flows through the inductor by the time, velocity of rod becomes  $v_f$  and the rod has travelled a distance  $x$ .



[Watch Video Solution](#)

4. A  $1.00\text{mH}$  inductor and a  $1.00\mu\text{F}$  capacitor are connected in series. The current in the circuit is described by  $i = 20t$ , where  $t$ , is in second and  $i$  is in ampere. The capacitor initially has no charge. Determine

(a) the voltage across the inductor as a function of time,


(b) the voltage across the capacitor as a function of time,

(c) the time when the energy stored in the capacitor first exceeds that in the inductor.



**Watch Video Solution**

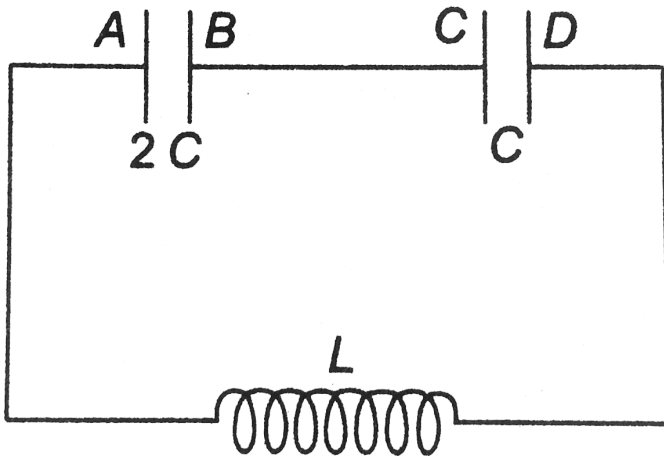5. Two capacitors of capacitances  $2C$  and  $C$  are connected in series with an inductor of inductance  $L$ . Initially, capacitors have charge such that  $V_B - V_A = 4V_0$  and  $V_C - V_D = V_0$ . Initial current in the circuit is zero. Find



(a) maximum current that will flow in the

circuit,

(b) potential difference across each capacitor at that instant,


(c) equation of current flowing towards left in the inductor.



[Watch Video Solution](#)

6. Switch  $S$  is closed in the circuit at time  $t = 0$ . Find the current through the capacitor

and the inductor at any time  $t$

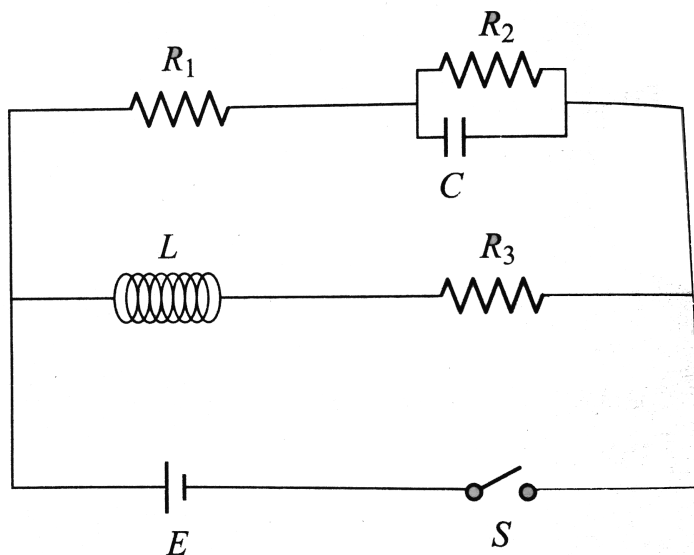


[Watch Video Solution](#)

7. In the circuit shows in Fig the capacitor is initially uncharged and the two - way switch is connected in the position  $BC$ . Find the

current through the resistance  $R$  as a function of time  $t$ . After time  $t = 4$  ms, the switch is connected in the position  $AC$ . Find the frequency of oscillation of the capacitor of the circuit in the position, and the maximum charge on the capacitor  $C$ . At what time will the energy stored in the capacitor be one-half of the total energy stored in the circuit? It is given

$$L = 2 \times 10^{-4} H, C = 5mF, R = \frac{In2}{10} \Omega \text{ and}$$

emf of the battery =  $1V$ .

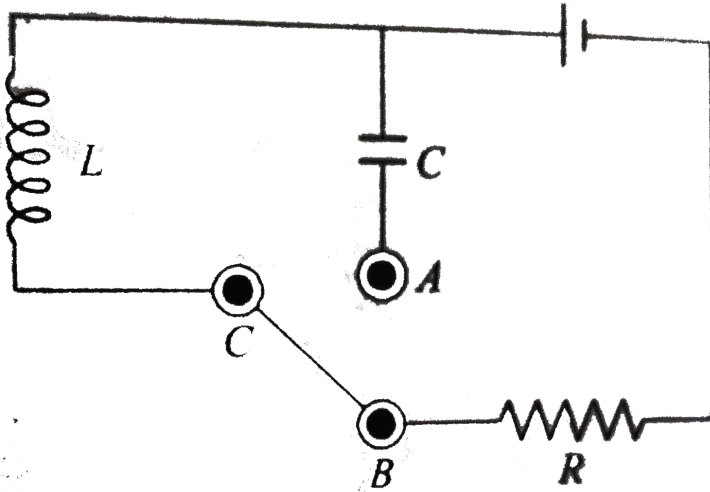

[Watch Video Solution](#)

Exercises (single Correct )



1. A mutual inductor consists of two coils  $X$  and  $Y$  as shown in Fig. in which one-quarter of the magnetic flux produced by  $X$  links with  $Y$ , giving a mutual inductance  $M$ . What will be the mutual inductance when  $Y$  is used as the primary?



A.  $M / 4$

B.  $M / 2$

C.  $M$

D.  $2M$





**Answer: C**




**Watch Video Solution**

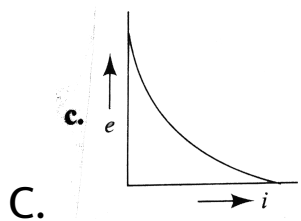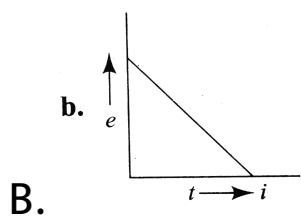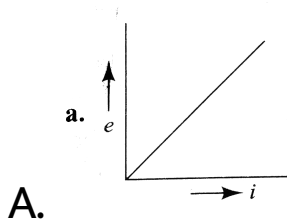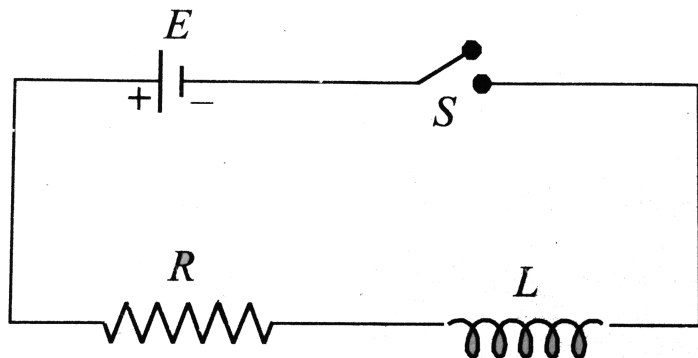2. Switch  $S$  of the circuit shows in Fig. is closed at  $t = 0$ . If  $e$  denotes the induced emf in  $L$  and  $i$  the current flowing through the circuit at time  $t$ , then which of the following graphs

correctly represents the variation of  $e$  with  $i$ ?



D.

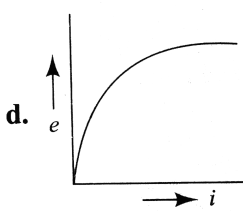

**Answer: B**



**Watch Video Solution**

3. A small coil of radius  $r$  is placed at the centre of a large coil of radius  $R$ , where  $R \gg r$ . The two coils are coplanar. The mutual inductance between the coils is proportional to

A.  $r / R$

B.  $r^2 / R$

C.  $r^2 / R^2$

D.  $r / R^2$

**Answer: B**



**Watch Video Solution**

4. A circuit contains two inductors of self-inductance  $L_1$  and  $L_2$  in series (Fig) If  $M$  is the mutual inductance, then the effective

inductance of the circuit shows will be



A.  $L_1 + L_2$

B.  $L_1 + L_2 - 2M$

C.  $L_1 + L_2 + M$


D.  $L_1 + L_2 + 2M$

**Answer: D**



**Watch Video Solution**

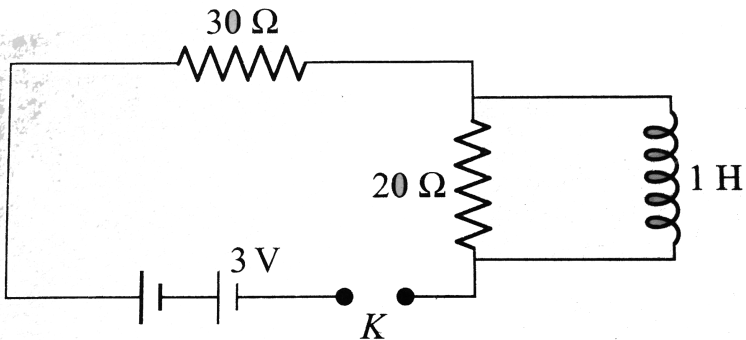5. In the circuit Fig the final current through  $30\Omega$  resistance when circuit is completed is



A.  $3\text{ A}$

B.  $0.1\text{ A}$

C.  $5\text{ A}$

D.  $0.5\text{ A}$

**Answer: B**



**Watch Video Solution**

6. The coefficient of mutual inductance of two circuits  $A$  and  $B$  is  $3mH$  and their respective resistances are  $10$  and  $4\Omega$ . How much current should change in  $0.02s$  in circuit  $A$ , so that the induced current in  $B$  should be  $0.0060A$ ?

A.  $0.24A$

B.  $1.6A$



C.  $0.18A$

D.  $0.16A$


**Answer: D**



**Watch Video Solution**

7. A long solenoid of length  $L$ , cross section  $A$  having  $N_1$  turns has about its center a small coil of  $N_2$  turns as shows in Fig The mutual

inductance of two circuits is

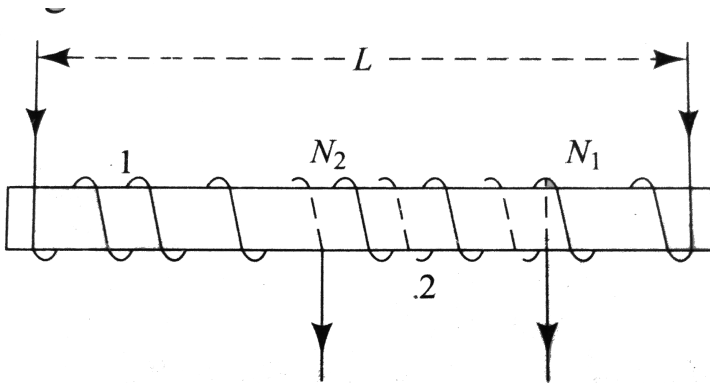

A.  $\frac{\mu_0 A (N_1 / N_2)}{L}$

B.  $\frac{\mu_0 A (N_1 N_2)}{L}$

C.  $\mu_0 A N_1 N_2 L$

D.  $\frac{\mu_0 A N_1^2 N_2}{L}$

**Answer: B**



8. An emf of 15 V is applied in a circuit coil containing 5 H inductance and  $10\Omega$  resistance. The ratio of the currents at time  $t = \infty$  and  $t = 1$  s is

A.  $\frac{e^{1/2}}{e^{1/2} - 1}$

B.  $\frac{e^2}{e^2 - 1}$

C.  $1 - e^{-1}$

D.  $e^{-1}$


**Answer: B**



**Watch Video Solution**

9. In Fig (a) and (b), two air-cored solenoids  $P$  and  $Q$  have been shown. They are placed near each other. In Fig (a), when  $I_P$ , the current in  $P$ , changes at the rate of  $5As^{-1}$ , an emf of  $2mV$  is induced in  $Q$ . The current in  $P$  is then switched off, and the current changing at  $2As^{-1}$  is fed through  $Q$  as shown in the

figure. What emf will be induced in  $P$ ?

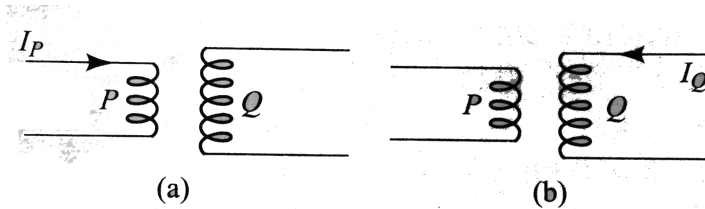

A.  $8 \times 10^{-4} V$

B.  $2 \times 10^{-3} V$

C.  $5 \times 10^{-3} V$

D.  $8 \times 10^{-2} V$

**Answer: A**



**Watch Video Solution**

10. A coil of inductance  $0.20H$  is connected in series with a switch and a cell of emf  $1.6V$ . The total resistance of the circuit is  $4.0\Omega$ . What is the initial rate of growth of the current when the switch is closed?

A.  $0.050As^{-1}$

B.  $0.40As^{-1}$

C.  $0.13As^{-1}$

D.  $8.0As^{-1}$

**Answer: D**



Watch Video Solution

11. The length of a wire required to manufacture a solenoid of length  $l$  and self-induction  $L$  is (cross-sectional area is negligible)

A.  $\sqrt{\frac{2\pi Ll}{\mu_0}}$

B.  $\sqrt{\frac{\mu_0 Ll}{4\pi}}$

C.  $\sqrt{\frac{4\pi Ll}{\mu_0}}$

D.  $\sqrt{\frac{\mu_0 Ll}{2\pi}}$

**Answer: C**



**Watch Video Solution**

**12.** The inductance  $L$  of a solenoid of length  $l$ , whose windings are made of material of density  $D$  and resistivity  $\rho$ , is (the winding resistance is  $R$ )

A.  $\frac{\mu_0}{4\pi l} \frac{Rm}{\rho D}$

B.  $\frac{\mu_0}{4\pi R} \frac{lm}{\rho D}$

C.  $\frac{\mu_0}{4\pi l} \frac{R^2 m}{\rho D}$



D.  $\frac{\mu_0}{2\pi R} \frac{lm}{\rho D}$


**Answer: A**



**Watch Video Solution**

**13.** A toroid is wound over a circular core. Radius of each turn is  $r$  and radius of toroid is  $R$  ( $R \gg r$ ). The coefficient of self-inductance

of the toroid is given by

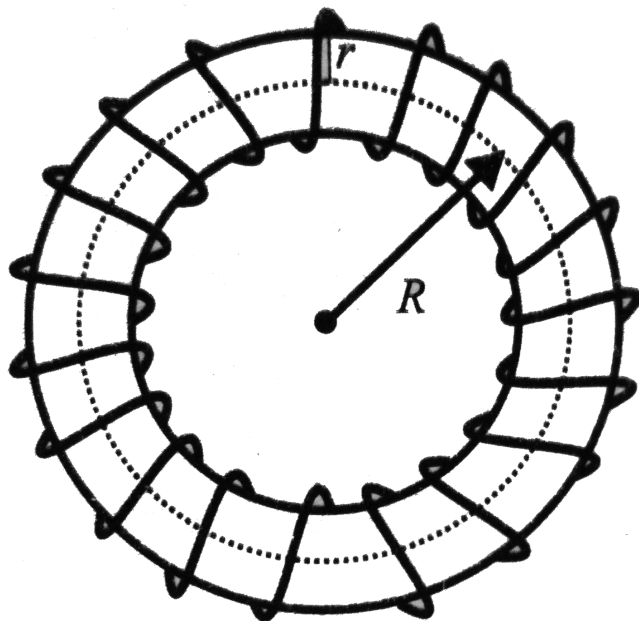

A.  $L = \frac{\mu_0 N r^2}{2R}$

B.  $L = \frac{\mu_0 N r}{2R}$

C.  $L = \frac{\mu_0 N r^2}{R}$

D.  $L = \frac{\mu_0 N^2 r^2}{2R}$

**Answer: D**



**Watch Video Solution**

**14.** A straight solenoid of length  $1m$  has 5000 turns in the primary and 200 turns in the secondary. If the area of cross section is  $4cm^2$ , the mutual inductance will be

A.  $503H$

B.  $503mH$

C.  $503\mu H$

D. 5.03H

**Answer: C**



**Watch Video Solution**

15. The approximate formula expressing the formula of mutual inductance of two coaxial loops of the same radius  $a$  when their centers are separated by a distance  $l$  with  $l \gg a$  is

A.  $\frac{1}{2} \frac{\mu_0 \pi a^4}{l^3}$

B.  $\frac{1}{2} \frac{\mu_0 a^4}{l^2}$

C.  $\frac{\mu_0}{4\pi} \frac{\pi a^4}{l^2}$

D.  $\frac{\mu_0}{\pi} \frac{a^4}{l^3}$

**Answer: A**



**Watch Video Solution**

**16.** The length of a thin wire required to manufacture a solenoid of length  $l = 100\text{cm}$  and inductance  $L = 1\text{mH}$ , if the solenoid's

cross-sectional diameter is considerably less than its length is

A.  $1\text{km}$

B.  $0.10\text{km}$

C.  $0.010\text{km}$

D.  $10\text{km}$

**Answer: B**



**Watch Video Solution**

17. Current in a coil of self-inductance  $2.0H$  is increasing as  $I = 2\sin t^2$ . The amount of energy spent during the period when the current changes from  $0$  to  $2A$  is

A.  $1J$

B.  $2J$

C.  $3J$


D.  $4J$

**Answer: D**



Watch Video Solution

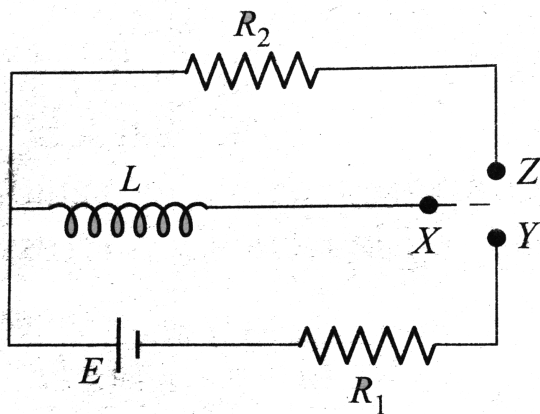18. In the circuit shown in Fig  $x$  is joined to  $Y$  for a long time and then  $X$  is joined to  $Z$ . The total heat produced in  $R_2$  is



- A.  $\frac{LE^2}{2R_1^2}$
- B.  $\frac{LE^2}{2R_2^2}$



C.  $\frac{LE^2}{2R_1R_2}$

D.  $\frac{LE^2R_2}{2R_1^3}$


**Answer: A**



**Watch Video Solution**

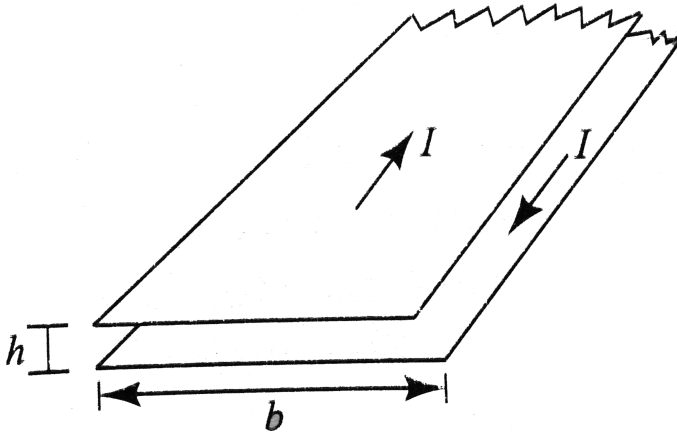**19.** Calculate the inductance of a unit length of a double tape line as shows in Fig if the tapes are separated by a distance  $h$  which is

considerably less than their width  $b$ .



- A.  $\frac{\mu_0 h}{b}$
- B.  $\frac{\mu_0 h}{2b}$
- C.  $\frac{2\mu_0 h}{b}$
- D.  $\frac{\sqrt{2}\mu_0 h}{b}$

**Answer: A**



20. Find the inductance of a unit length of two long parallel wires, each of radius  $a$ , whose centers are a distance  $d$  apart and carry equal currents in opposite directions. Neglect the flux within the wire.

A.  $\frac{\mu_0}{2\pi} I n \left( \frac{d - a}{a} \right)$

B.  $\frac{\mu_0}{\pi} I n \left( \frac{d - a}{a} \right)$

C.  $\frac{3\mu_0}{\pi} I n \left( \frac{d - a}{a} \right)$

D.  $\frac{\mu_0}{3\pi} I n \left( \frac{d - a}{a} \right)$


**Answer: B**



**Watch Video Solution**

**21.** Figure shows a rectangular coil near a long wire. The mutual inductance of the

combination is

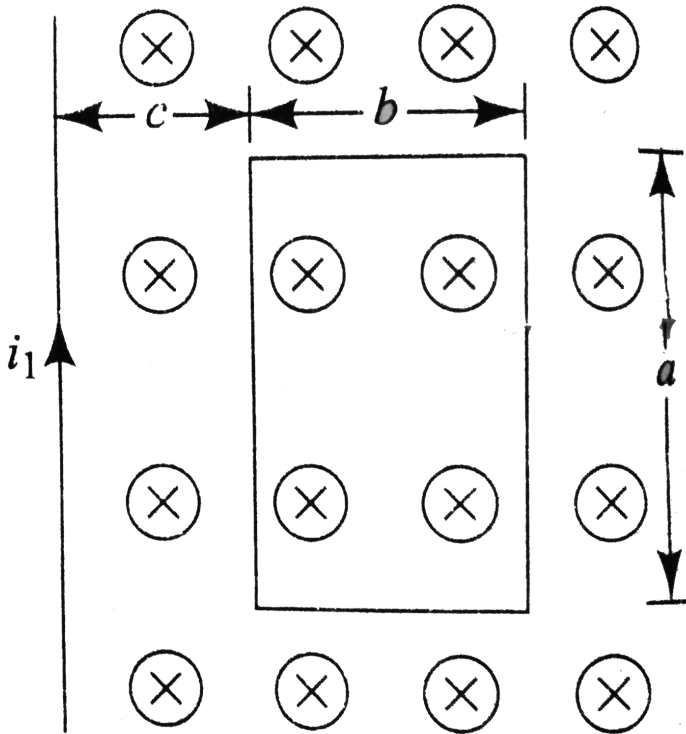

A.  $\frac{\mu_0 a}{2\pi} I n \left( 1 - \frac{b}{c} \right)$

B.  $\frac{\mu_0 a}{2\pi} I n \left( 1 + \frac{b}{c} \right)$

C.  $\frac{\mu_0 a}{\pi} I n \left( 1 + \frac{b}{c} \right)$


D.  $\frac{\mu_0 a}{\sqrt{2\pi}} \ln\left(1 + \frac{b}{c}\right)$

**Answer: B**



**Watch Video Solution**

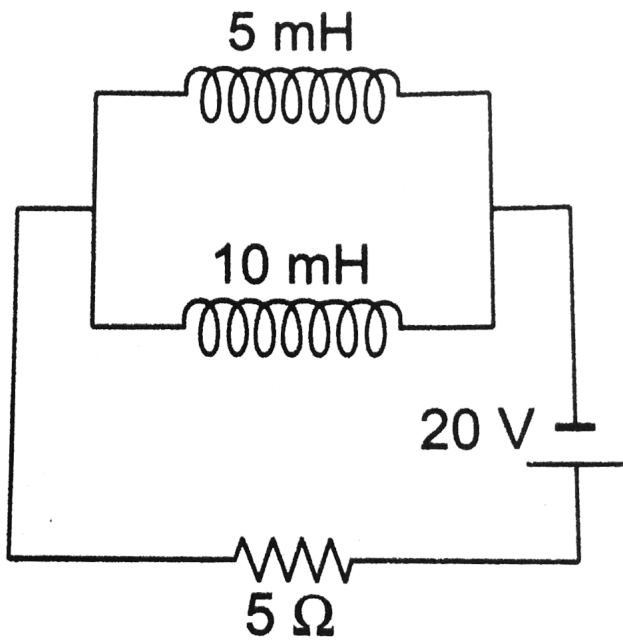**22.** In the given circuit, find the current through the  $5mH$  inductor in steady state.



A.  $\frac{2}{3} A$

B.  $\frac{8}{3} A$

C.  $\frac{1}{3} A$

D.  $\frac{2}{3} A$

**Answer: B**




**Watch Video Solution**

**23.** In the following electrical network at  $t = < 0$  Fig key is placed on (1) till the capacitor got fully charged. Key is placed on (2) at  $t = 0$ . Time when the energy in both the



same for the time is

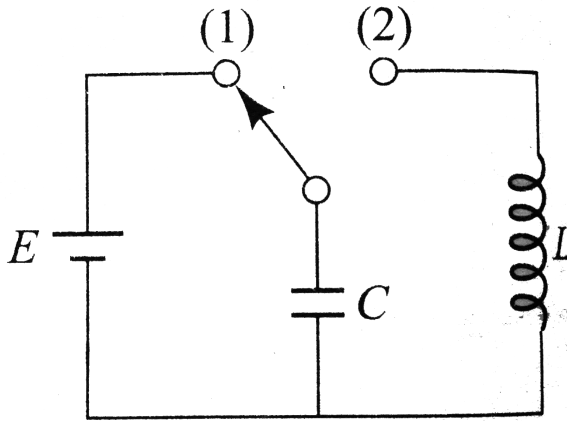

- A.  $\frac{\pi}{4} \sqrt{LC}$
- B.  $\frac{3\pi}{4} \sqrt{LC}$
- C.  $\frac{\pi}{3} \sqrt{LC}$
- D.  $\frac{2\pi}{3} \sqrt{LC}$

**Answer: A**



Watch Video Solution

24. The total heat produced in resistor  $r$  in an  $RL$  circuit when the current in the inductor decreases from  $I_0$  to 0 is

A.  $LI_0^2$

B.  $\frac{1}{2}LI_0^2$

C.  $\frac{3}{2}LI_0^2$


D.  $\frac{1}{3}LI_0^2$

**Answer: B**



Watch Video Solution

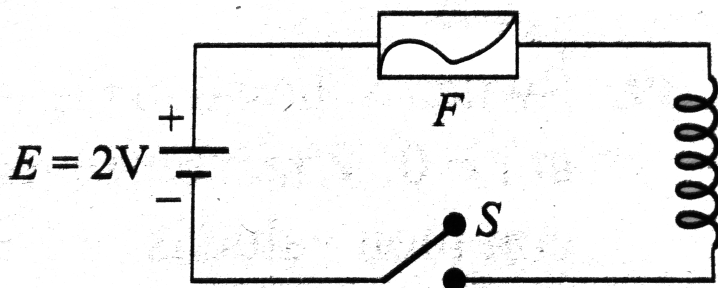25. In the circuit shown in Fig. the cell is ideal. The coil has an inductance of  $4H$  and zero resistance.  $F$  is a fuse of zero resistance and will blow when the current through it reaches  $5A$ . The switch is closed at  $t = 0$ . The fuse will blow



A. almost at once

B. after  $2s$

C. after  $5s$

D. after  $10s$


**Answer: D**



**Watch Video Solution**

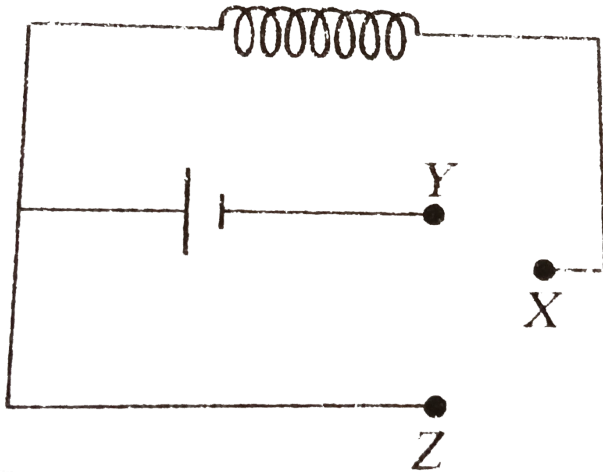**26.** In the circuit shown, the coil has inductance and resistance. When X is joined to Y, the time constant is  $\tau$  during growth of

current. When the steady state is reached, then heat is produced in the coil at a rate  $P$ . If  $X$  is now joined to  $Z$ , then choose the correct statement.



- A. the total heat produced in the coil is  $p\tau$
- B. The total heat produced in the coil is

$$\frac{1}{2}P\tau$$

C. The total heat produced in the coil is

$$2P\tau$$

D. The data given are not sufficient to reach a conclusion

**Answer: B**



**Watch Video Solution**

27. A long solenoid having 200 turns per centimeter carries a current of 1.5A. At the center of the solenoid is placed a coil of 100

turns of cross-sectional area  $3.14 \times 10^{-4} m^2$  having its axis parallel to the field produced by the solenoid. When the direction of current in the solenoid is reversed within  $0.05s$ , the induced emf in the coil is

A.  $0.48V$

B.  $0.048V$




C.  $0.0048V$

D.  $48V$


**Answer: B**



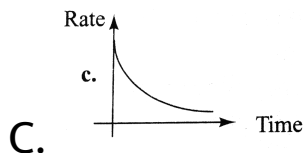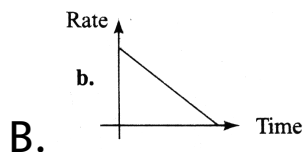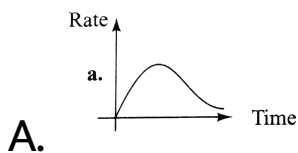28. In an L-R circuit connected to a battery at which energy is stored in the inductor is plotted against time during the growth of current in the circuit. Which of the following best represents the resulting curve?





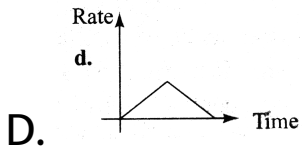

**Answer: A**



**Watch Video Solution**

**29.** Two coils are at fixed locations. When coil 1 has no current and the current in coil 2 increases at the rate of  $15.0\text{A/s}$  the emf in coil 1 is  $25.0\text{mV}$ , when coil 1 has no current and coil 2 has a current of  $3.6\text{A}$ , the flux linkage in coil 2 is

A.  $16mWb$

B.  $10mWb$

C.  $4.00mWb$

D.  $6.00mWb$


**Answer: D**



**Watch Video Solution**

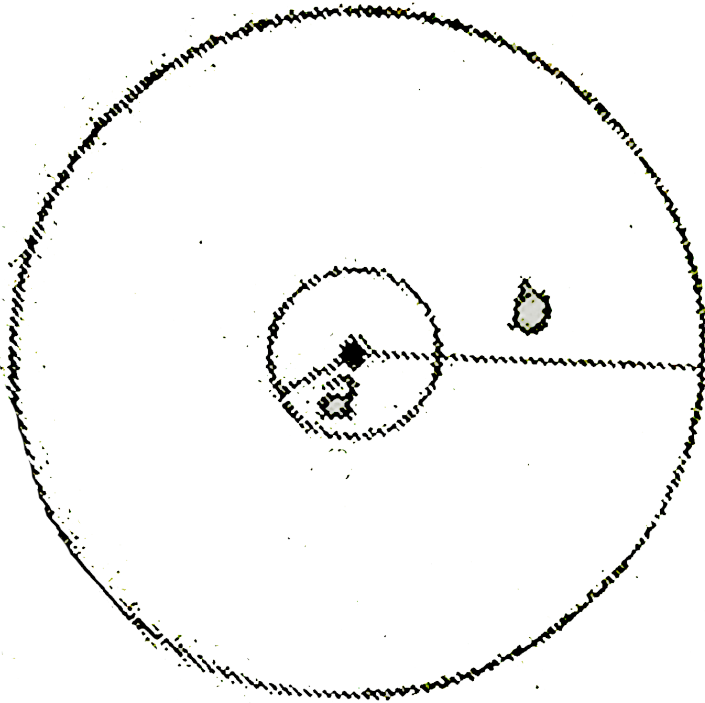**30.** Two concentric and coplanar circular coils have radii  $a$  and  $b$  ( $b > a$ ) as shown in the figure. Resistance of the inner coil is  $R$ . Current

in the outer coil is increased from 0 to  $I$ , then  
the total charge circulating the inner coil is



A.  $\frac{\mu_0 i a^2 \pi}{2Rb}$

B.  $\frac{\mu_0 i a b}{2R}$

C.  $\frac{\mu_0 i a b}{2a} \frac{\pi b^2}{R}$

D.  $\frac{\mu_0 i b}{2\pi R}$

**Answer: A**



**Watch Video Solution**

**31.** A current  $i_0$  is flowing through an L-R circuit of time constant  $t_0$ . The source of current is switched off at time  $t=0$ . Let  $r$  be the value of  $(-di/dt)$  at time  $t=0$ . Assuming this rate to be constant, the current will reduce to zero in a time interval of

A.  $t_0$

B.  $et_0$

C.  $\frac{t_0}{e}$

D.  $\left(1 - \frac{1}{e}\right)t_0$


**Answer: A**



**Watch Video Solution**

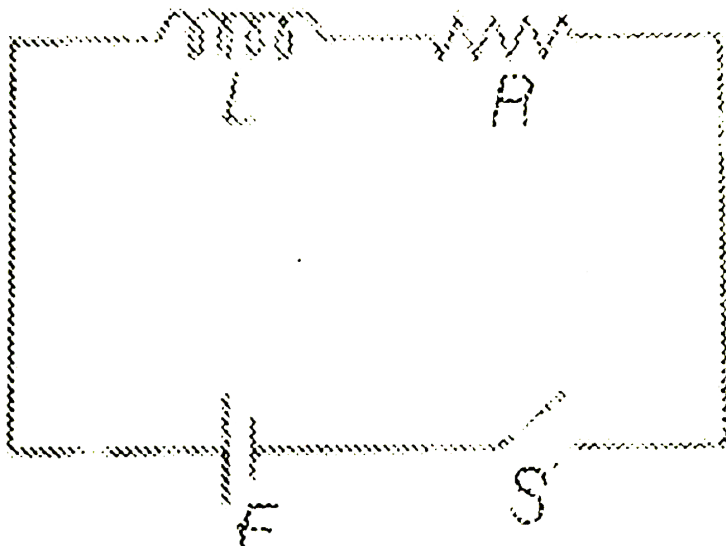**32.** In the circuit shown in figure switch S is closed at time  $t=0$ . The charge which passes

through the battery in one time constant is







- A.  $\frac{eR^2E}{L}$
- B.  $E\left(\frac{L}{R}\right)$
- C.  $\frac{EL}{eR^2}$
- D.  $\frac{eL}{ER}$

**Answer: C**



**Watch Video Solution**

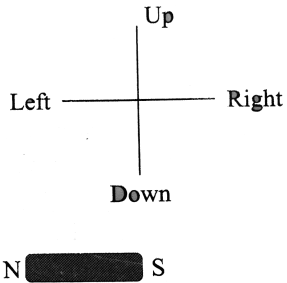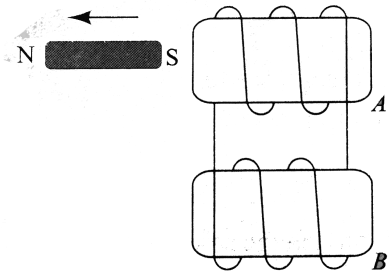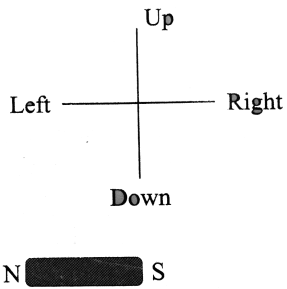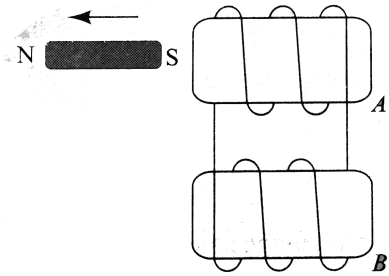**33.** A bar magnet was pulled away from a hollow coil  $A$  as shows in Fig As the south pole came out of the coil, the bar magnet next to hollow coil  $B$  experienced a magnetic force



A. to the right

B. to the left

C. upward

D. equal to zero




Answer: A



Watch Video Solution

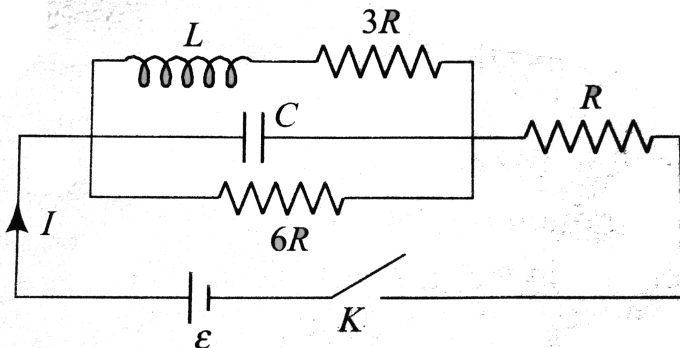34. In the given circuit (Fig), key  $K$  is witted on the at  $t = 0$ . The ratio of current  $i$  through the cell at  $t = 0$  to that at  $t = \infty$  will be



A. 3:1

B. 1:3

C. 1:2

D. 2:1

**Answer: A**




**Watch Video Solution**

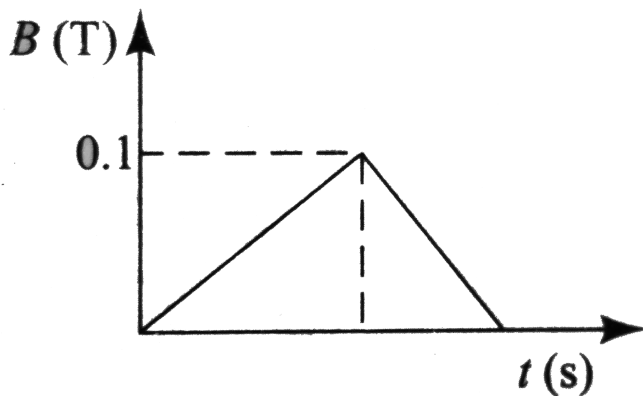**35.** A closed loop of cross-sectional area  $10^{-2}m^2$  which has inductance  $L = 10mH$  and negligible resistance is placed in a time-varying magnetic field. Figure shows the

variation of  $B$  with time for the interval  $4s$ .

The field is perpendicular to the plane of the loop (given at  $t = 0, B = 0, I = 0$ ). The value of the maximum current induced in the loop is



A.  $0.1mA$

B.  $10mA$

C.  $100mA$

D. Date insufficient


**Answer: C**



**Watch Video Solution**

**36.** In Fig. key  $K$  is closed at  $t = 0$ . After a long time, the potential difference between  $A$  and  $B$  is zero, the value of  $R$  will be  
[ $r_1 = r_2 = 1\Omega$ ,  $E_1 = 3V$  and  $E_2 = 7V$ ,  
 $C = 2\mu F$ ,  $L = 4mH$ , where  $r_1$  and  $r_2$  are the  
internal resistances of cells  $E_1$  and  $E_2$ ,

respectively].

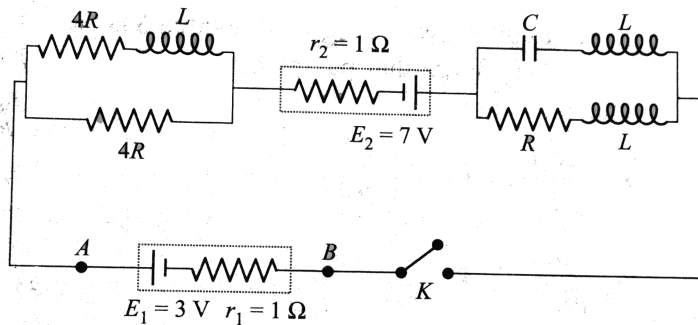

A.  $\frac{4}{3} \Omega$

B.  $\frac{4}{9} \Omega$

C.  $\frac{2}{3} \Omega$

D.  $4 \Omega$

**Answer: B**




**Watch Video Solution**

**37.** A solenoid of inductance  $L$  with resistance  $r$  is connected in parallel to a resistance  $R$ . A battery of emf  $E$  and of negligible internal resistance is connected across the parallel combination as shown in the figure. At time  $t = 0$ , switch  $S$  is opened, calculate

(a) current through the solenoid after the switch is opened.

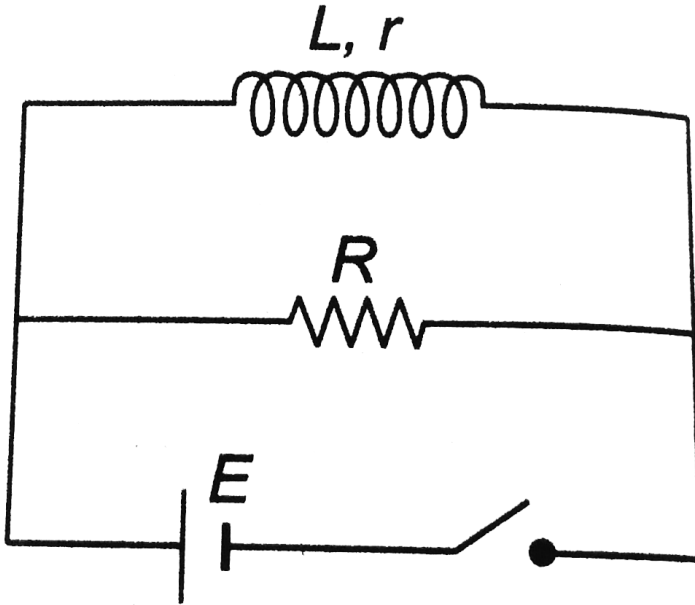(b) amount of heat generated in the solenoid.



A. Current in the inductor just after

removing the battery is  $\frac{E(r + R)}{rR}$

B. Total energy dissipated in the solenoid

and the resistor long time after removing

the battery is  $\frac{1}{2}L \frac{E^2(R+r)^2}{r^2 R^2}$

C. The amount of heat generated in the solenoid due to removing the battery is

$$\frac{E^2 L}{2r(r+R)}$$

D. The amount of heat generated in the solenoid due to removing the battery is

$$\frac{E^2 L}{2R(r+R)}$$


**Answer: C**



**Watch Video Solution**



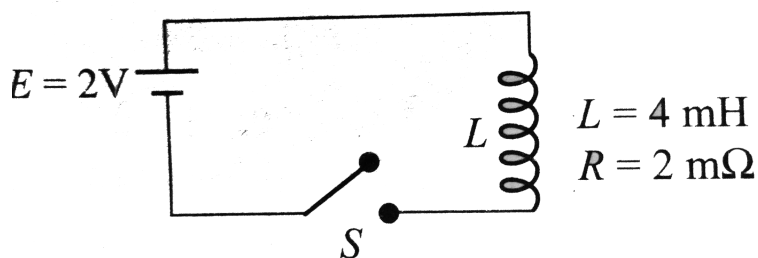38. The cell in the circuit shows in Fig is ideal. The coil has an inductance of  $4\text{mH}$  and a resistance of  $2\text{m}\Omega$ . The switch is closed at  $t = 0$ . The amount of energy stored in the inductor at  $t = 2\text{s}$  is (take  $e = 3$ )



A.  $\frac{4}{3}\text{ J}$

B.  $\frac{8}{9} \times 10^3\text{ J}$

C.  $\frac{8}{9} \times 10^3 J$

D.  $2 \times 10^3 J$


**Answer: B**



**Watch Video Solution**

**39.** Switch  $S$  shown in Fig. is closed for  $t < 0$  and is opened at  $t = 0$ . When currents through  $L_1$  and  $L_2$  are equal, their common

value is

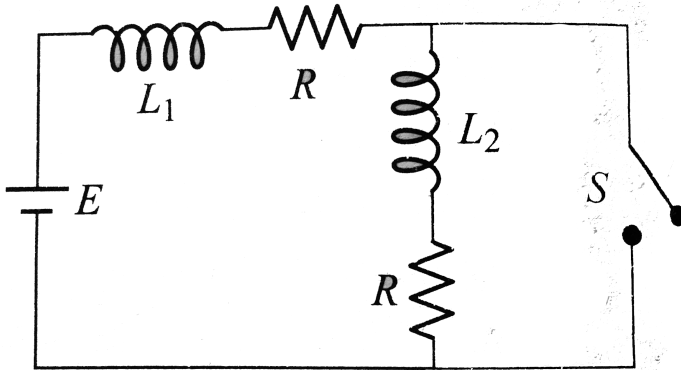

A.  $\frac{E}{R}$

B.  $\frac{E(L_2 + L_2)}{RL_1}$

C.  $\frac{EL_1}{R(L_1 + L_2)}$

D.  $\frac{E}{R} \frac{(L_1 + L_2)}{L_2}$


**Answer: C**



Watch Video Solution

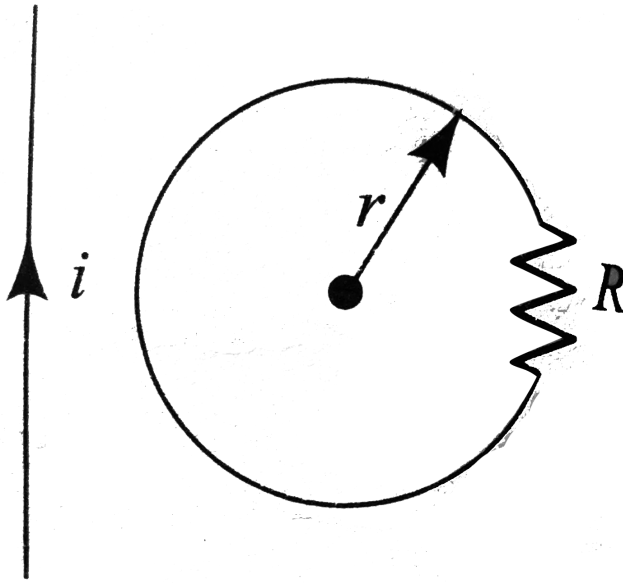**40.** In Fig, the mutual inductance of a coil and a very long straight wire is  $M$ , coil has resistance  $R$  and self-inductance  $L$ . The current in the wire varies according to the law  $I = at$ , where  $a$  is a constant and  $t$  is the time,

the time dependence of current in the coil is



A.  $\frac{M}{aR}$

B.  $maRe^{-Rt/L}$

C.  $\frac{M}{R}e^{-tR/L}$

$$D. \frac{Ma}{R} \left(1 - e^{-tR/L}\right)$$


**Answer: D**



**Watch Video Solution**

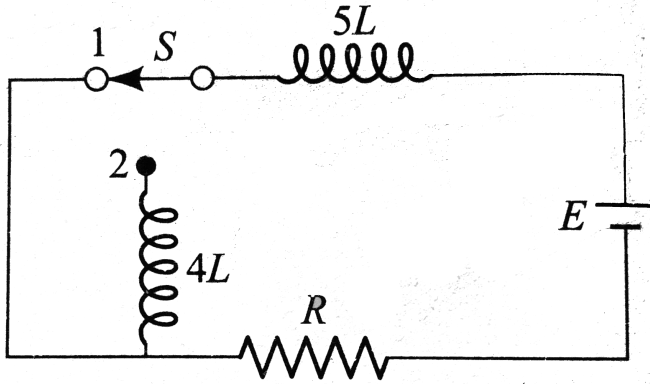**41.** In the circuit shows in Fig switch  $S$  is shifted to position 2 from position 1 at  $t = 0$ , having been on position 1 for a long time. The current in the circuit just after shifting of switch will

be (battery and both the inductors are ideal)



A.  $\frac{4}{5} \frac{E}{R}$

B.  $\frac{5}{4} \frac{E}{R}$

C.  $\frac{5}{9} \frac{E}{R}$

D.  $\frac{E}{R}$

**Answer: C**



Watch Video Solution

42. The capacitance in an oscillatory  $LC$  circuit is increased by  $1\%$ . The change in inductance required to restore its frequency of oscillation is to


- A. decrease it by  $0.5\%$
- B. increase it by  $1\%$
- C. decrease it by  $1\%$
- D. decrease it by  $2\%$



Answer: C

 Watch Video Solution

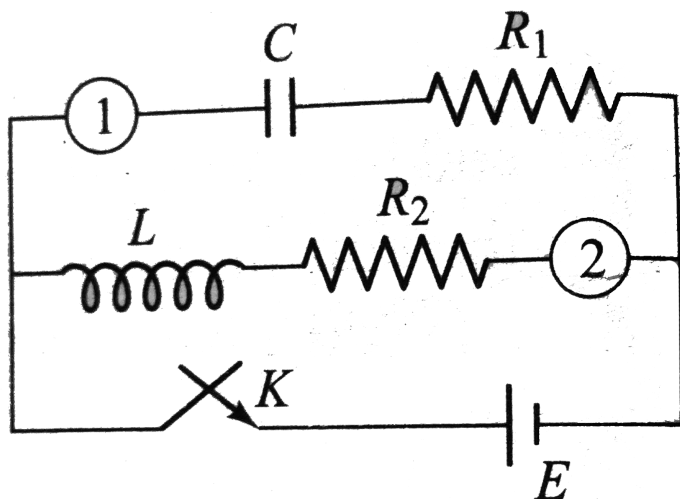43. In the circuit of Fig. (1) and (2) are ammeters. Just after circuit  $K$  is pressed to complete the circuit, the reading is



A. maximum in both 1 and 2

B. zero in both 1 and 2

C. zero in 1, minimum in 2

D. maximum in 1, zero in 2

**Answer: D**



**Watch Video Solution**

**44.** A wire of fixed length is wound on a solenoid of length ' $l$ ' and radius ' $r$ '. Its self inductance is found to be  $L$ . Now if same wire is

wound on a solenoid of length  $ad$  and radius  $\frac{r}{2}$   
then the self inductance will be

A.  $2L$

B.  $L$

C.  $4L$


D.  $8L$

**Answer: A**



**Watch Video Solution**

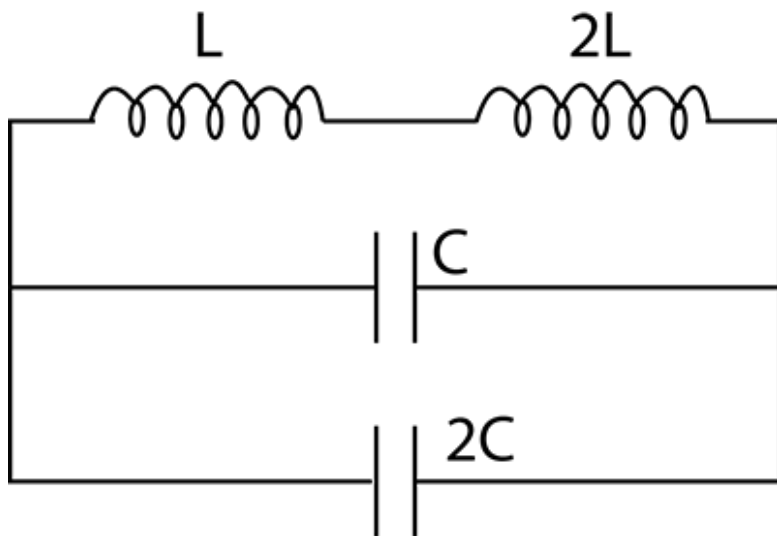45. The frequency of oscillation of current in the circuit is




- A.  $\frac{1}{3\sqrt{LC}}$
- B.  $\frac{1}{6\pi\sqrt{LC}}$
- C.  $\frac{1}{\sqrt{LC}}$
- D.  $\frac{1}{2\pi\sqrt{LC}}$

**Answer: B**



**Watch Video Solution**

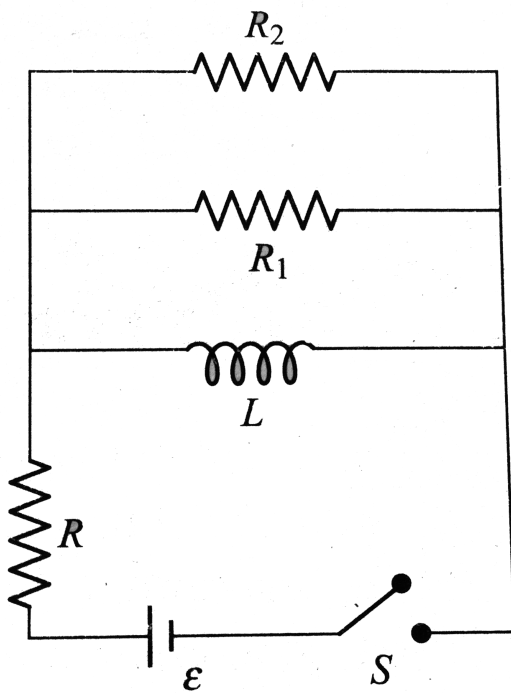**46.** In Fig. switch  $S$  is closed for a long time. At  $t = 0$ , if it is opened, then



A. total heat produced in resistor  $R$  after

opening the switch is  $\frac{1}{2} \frac{L\epsilon}{R^2}$

B. total heat produced in resistor  $R_1$  after

opening the switch is

$$\frac{1}{2} \frac{L\epsilon^2}{R^2} \left( \frac{R_1}{R_1 + R_2} \right)$$

C. heat produced in resistor  $R_1$  after

opening the switch is  $\frac{1}{2} \frac{R_2 L \epsilon^2}{(R_1 + R_2) R^2}$

D. no heat will be produced in  $R_1$

**Answer: C**



**Watch Video Solution**

**47.** A closed circuit of a resistor  $R$ , inductor of inductance  $L$  and a source of emf  $E$  are connected in series. If the inductance of the

coil is abruptly decreased to  $L/4$  (by removing its magnetic core), the new current immediately after this moment is (before decreasing the inductance the circuit is in steady state)

A. zero

B.  $\frac{E}{R}$

C.  $4\frac{E}{R}$




D.  $\frac{E}{4R}$

**Answer: C**





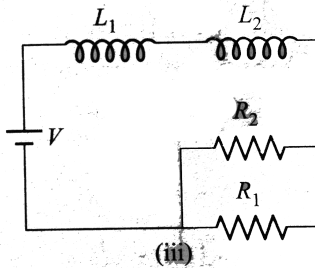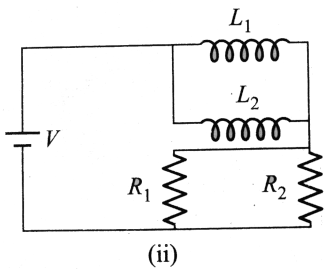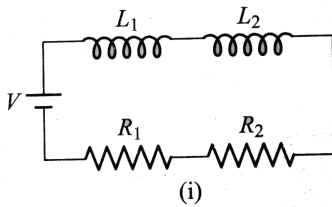48. Given  $L_1 = 1\text{mH}$ ,  $R_1 = 1\Omega$ ,  $L_2 = 2\text{mH}$ ,  
 $R_2 = 2\Omega$



Neglecting mutual inductance, the time

constants (in ms) for circuits (i), (ii), and (iii)

are

A.  $1, 1, \frac{9}{2}$

B.  $\frac{9}{4}, 1, 1$

C.  $1, 1, 1$

D.  $1, \frac{9}{4}, 1$

**Answer: A**



**Watch Video Solution**

49. A horizontal ring of radius  $r = \frac{1}{2}m$  is kept in a vertical constant magnetic field  $1T$ . The ring is collapsed from maximum area to zero area in  $1s$ . Then the emf induced in the ring is

A.  $1V$

B.  $(\pi/4)V$

C.  $(\pi/2)V$


D.  $\pi V$

**Answer: B**



Watch Video Solution

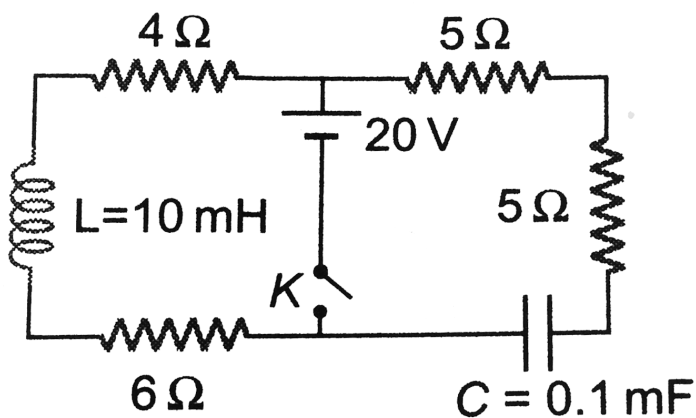50. In the circuit shown the key ( $K$ ) is closed at  $t = 0$ , the current through the key at the instant  $t = 10^{-3} \ln, 2$  is



A.  $2\ \text{A}$

B.  $3.5\ \text{A}$

C.  $2.5A$

D. 0






**Answer: C**



**Watch Video Solution**

**51.** In the circuit shown in Fig. switch  $k_2$  is open and switch  $k_1$  is closed at  $t = 0$ . At time  $t = t_0$ , switch  $k_1$  is opened and switch  $k_2$  is simultaneously closed. The variation of

inductor current with time is

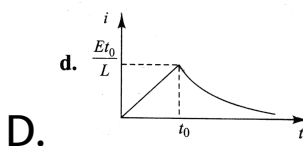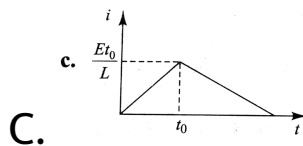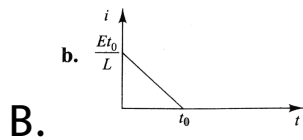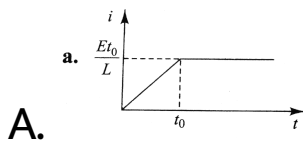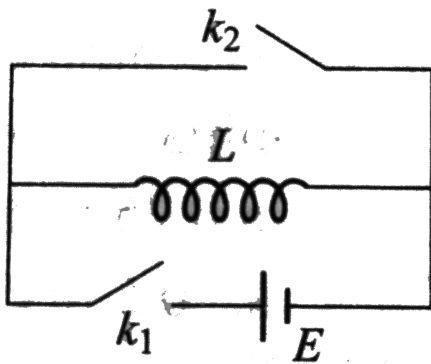

**Answer: A**




**Watch Video Solution**

**52.** In an L-C circuit shown in figure

$C=1\text{F}$ ,  $L=4\text{H}$

At time  $t=0$ , charge in the capacitor is  $4C$  and

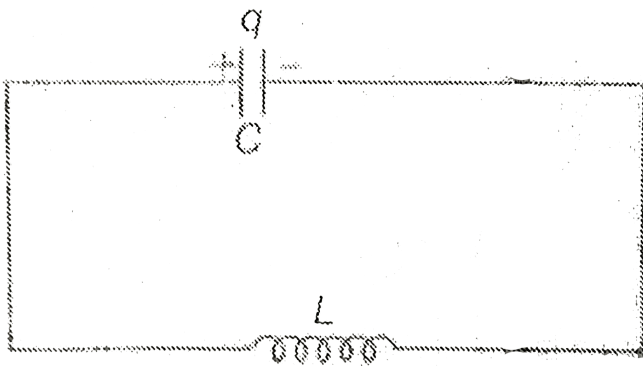it is decreasing at a rate of  $\sqrt{5}C / s$



Maximum charge in the capacitor can be

A. Maximum charge in the capacitor can be

$$6C$$

B. Maximum charge in the capacitor can be

$$8C$$

C. Charge in the capacitor will be maximum

$$\text{after time } 3 \sin^{-1}(2/3) s$$



D. None of these

**Answer: A**




**Watch Video Solution**

**53.** An aluminium ring hangs vertically from a thread with its axis pointing east-west. A coil is fixed near to the ring and coaxial with it.

What is the initial motion of the aluminium ring when the current in the coil is switched

on?

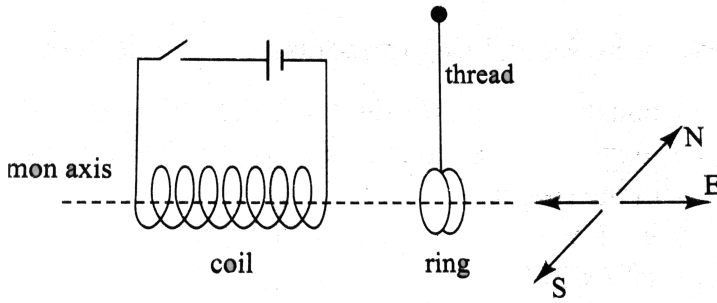

- A. moves toward  $E$
- B. moves toward  $W$
- C. moves toward  $N$
- D. moves toward  $S$

**Answer: A**



**Watch Video Solution**

54. A coil carrying a steady current is short-circuited. The current in it decreases  $\alpha$  times in time  $t_0$ . The time constant of the circuit is

A.  $\tau = t_0 \ln \alpha$

B.  $\tau = \frac{t_0}{\ln \alpha}$

C.  $\tau = \frac{t_0}{\alpha}$

D.  $\tau = \frac{t_0}{\alpha - 1}$

**Answer: B**



55. A solenoid has 2000 turns wound over a length of 0.30 m. The area of its cross-section is  $1.2 \times 10^{-3} \text{ m}^2$ . If an initial current of 2 A in the solenoid is reversed in 0.25 s, then the emf induced in the coil is

A.  $0.6 \text{ mV}$

B.  $60 \text{ mV}$

C.  $48 \text{ mV}$

D.  $0.48 \text{ mV}$

**Answer: C**



**Watch Video Solution**

**56.** Two coils  $X$  and  $Y$  are linked such that emf  $E$  is induced in  $Y$  when the current in  $x$  is changing at the rate  $I' (= dI/dt)$ . If a current  $I_0$  is now made to flow through  $Y$ , the flux linked with  $X$  will be

A.  $E I_0 I'$

B.  $\frac{I_0 I'}{E}$

C.  $(EI')I_0$

D.  $\left(\frac{E}{I'}\right)I_0$

**Answer: D**



**Watch Video Solution**

**57.** The time constant of an inductance coil is  $2.0 \times 10^{-3} \text{ s}$ . When a  $90\Omega$  resistance is joined in series, then the time constant becomes  $0.5 \times 10^{-3} \text{ s}$ . The inductance and resistance of the coil are

A.  $30mH, 30\Omega$

B.  $60mH, 30\Omega$

C.  $30mH, 60\Omega$

D.  $60mH, 60\Omega$


**Answer: B**



**Watch Video Solution**

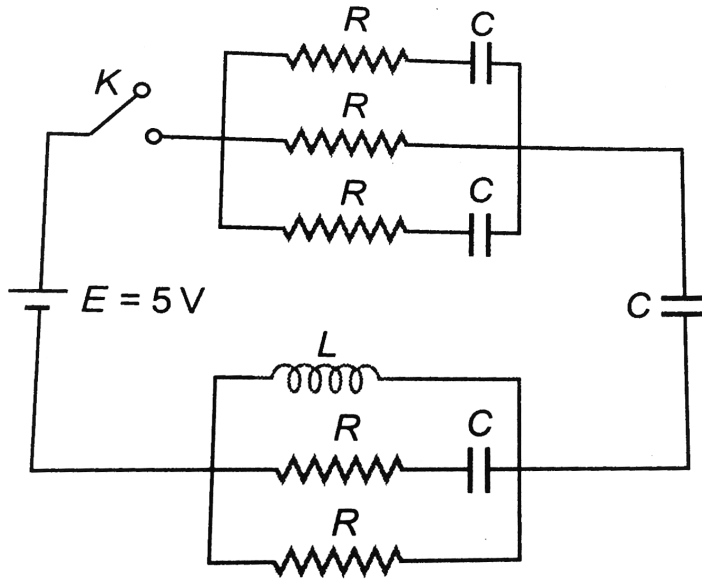**58.** Find the current passing through battery immediately after key ( $K$ ) is closed. It is given that initially all the capacitors are uncharged.

(Given that  $R = 6\Omega$  and  $C = 4\mu F$ )



A.  $1A$

B.  $5A$

C.  $3A$

D.  $2A$




**Answer: A**



**Watch Video Solution**

**59.** A pure inductor  $L$ , a capacitor  $C$  and a resistance  $R$  are connected across a battery of emf  $\varepsilon$  and internal resistance  $r$  as shown in the figure. The switch  $S_w$  is closed at  $t = 0$ , select

the correct alternative.

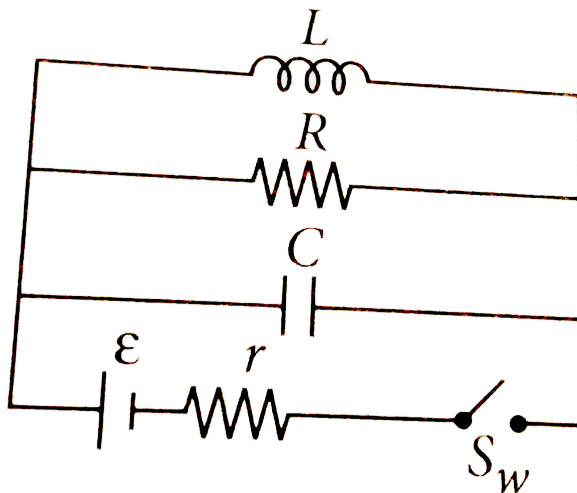

A. current through resistance  $R$  is zero all the time

B. current through resistance  $R$  is zero at  $t = 0$  and  $t \rightarrow \infty$

C. maximum charge stored in the capacitor

is  $CE$

D. maximum charge stored in the inductor

is equal to the maximum energy stored

in the capacitor

**Answer: B**




**Watch Video Solution**

60. A simple  $LR$  circuit is connected to a battery at time  $t = 0$ . The energy stored in the inductor reaches half its maximum value at time

- A.  $\frac{R}{L} \ln \left[ \frac{\sqrt{2}}{\sqrt{2} - 1} \right]$
- B.  $\frac{L}{R} \ln \left[ \frac{\sqrt{2} - 1}{\sqrt{2}} \right]$
- C.  $\frac{L}{R} \ln \left[ \frac{\sqrt{2}}{\sqrt{2} - 1} \right]$
- D.  $\frac{R}{L} \ln \left[ \frac{\sqrt{2} - 1}{\sqrt{2}} \right]$

**Answer: C**

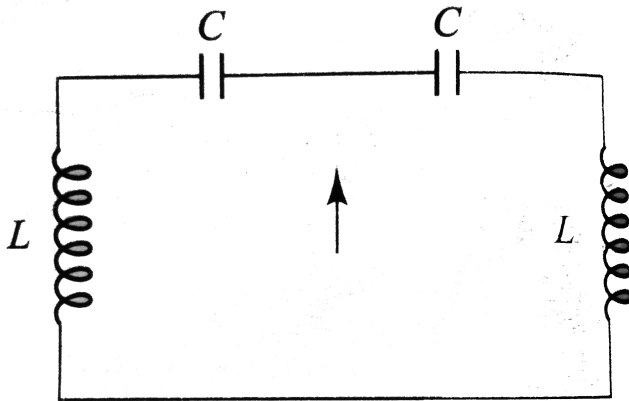61. The natural frequency of the circuit shows in Fig. is



A.  $\frac{1}{\sqrt{LC}}$

B.  $\frac{1}{\sqrt{2LC}}$

C.  $\frac{2}{\sqrt{LC}}$

D. None of these


**Answer: A**



**Watch Video Solution**

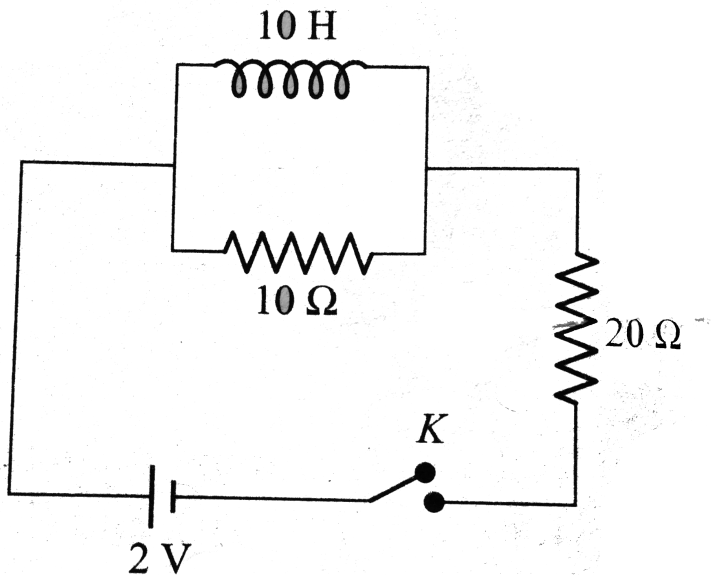**62.** Two resistors of  $10\Omega$  and  $20\Omega$  and an ideal inductor of  $10H$  are connected to a  $2V$  battery as shows in Fig. key  $K$  is inserted at time  $t = 0$ . The initial ( $t = 0$ ) and final

$(t \rightarrow \infty)$  currents through the battery are



A.  $\frac{1}{15} A, \frac{1}{10} A$

B.  $\frac{1}{10} A, \frac{1}{15} A$

C.  $\frac{2}{15} A, \frac{1}{10} A$

D.  $\frac{1}{15} A, \frac{2}{25} A$

**Answer: A**



**Watch Video Solution**

**63.** A square conducting loop of side  $L$  is situated in gravity free space. A small conducting circular loop of radius  $r$  ( $r \ll L$ ) is placed at the center of the square loop, with its plane perpendicular to the plane of the square loop. The mutual inductance of the two coils is



A.  $\frac{2\sqrt{2}\mu_0 I}{L} r^2$

B.  $\frac{\sqrt{2}\mu_0 I_0}{L} r^2$

C. 0

D. None of these

**Answer: C**



**Watch Video Solution**

**64.** There is a conducting ring of radius  $R$ . Another ring of radius  $r$  ( $r < R$ ) is kept on the axis of bigger ring such that its center

lies on the axis of bigger ring at a distance  $x$  from the center of bigger ring and its plane is perpendicular to the axis. The mutual inductance of the two rings is

- A.  $\frac{\mu_0 \pi R^2 r^2}{(R^2 + x^2)^{3/2}}$
- B.  $\frac{\mu_0 \pi R^2 r^2}{4(R^2 + x^2)^{3/2}}$
- C.  $\frac{\mu_0 \pi R^2 r^2}{16(R^2 + x^2)^{3/2}}$
- D.  $\frac{\mu_0 \pi R^2 r^2}{2(R^2 + x^2)^{3/2}}$

**Answer: D**



**Watch Video Solution**

**65.** The capacitor of an oscillatory circuit of frequency  $10000\text{Hz}$  is enclosed in a container. When the container is evacuated, the frequency changes by  $50\text{Hz}$ , the dielectric constant of the gas is

A. 1.1

B. 1.01

C. 1.001

D. 1.0001


**Answer: B**



**Watch Video Solution**

## Exercises (multiple Correct )

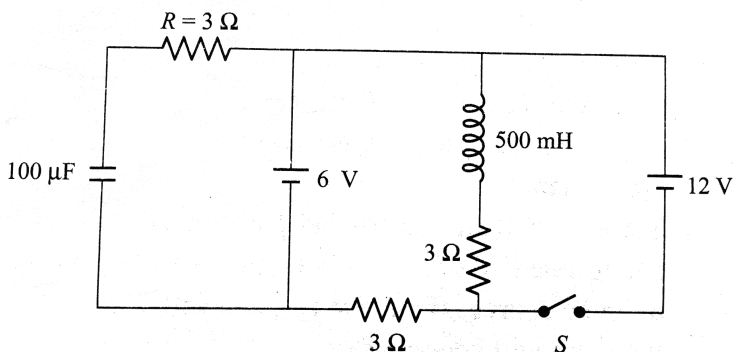1. In the given circuit Fig the switch is closed at  $t = 0$ . Choose the correct answers.



A. Current in the inductor when the circuit reaches the steady state is  $4A$ .

B. The net change in flux in the inductor is  $1.5Wb$ .

C. The time constant of the circuit after closing  $S$  is  $555.55s$

D. The charge stored in the capacitor in steady state is  $1.2mC$ .


**Answer: A::B**



**Watch Video Solution**

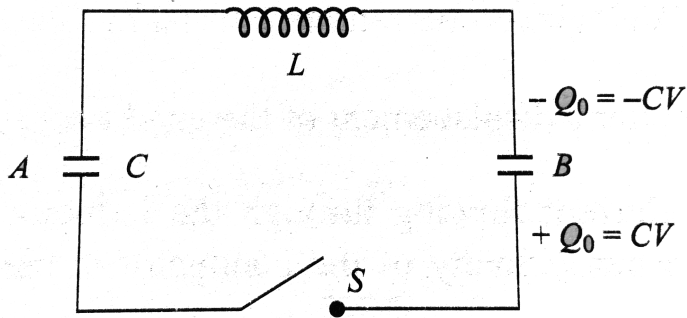2. An inductor and two capacitors are connected in the circuit as show in Fig Initially capacitor  $A$  has no charge and capacitor  $B$  has  $CV$  charge. Assume that the circuit has no resistance at all. At  $t = 0$ , switch  $S$  is closed, then [given

$$LC = \frac{2}{\pi^2 \times 10^4} S^2 \text{ and } Cv = 100mC]$$



A. when current in the circuit is maximum,  
charge on each capacitor is same

B. when current in the circuit is maximum,  
charge on capacitor  $A$  is twice the  
charge on capacitor  $B$

C.  $q = 50(1 + \cos 100\pi t)mC$ , where  $q$  is the charge on capacitor  $B$  at time  $t$

D.  $q = 50(1 - \cos 100\pi t)mC$ , where  $q$  is the charge on capacitor  $B$  at time  $t$


**Answer: A:C**



**Watch Video Solution**

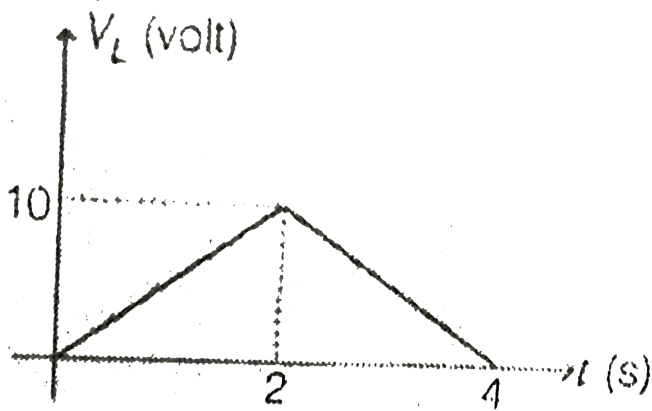3. The potential difference across a 2H inductor as a function of time is shown in the figure. At time  $t=0$ , current is zero.






Current at  $t = s$  is


A. Current at  $t = 2s$  is  $5A$

B. Current at  $t = 2s$  is  $10A$

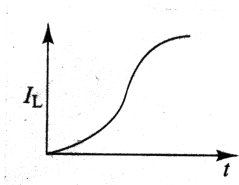C. Current versus time graph across the inductor will be Fig.



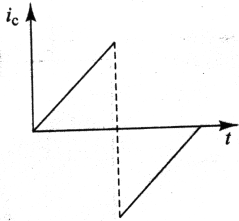D. Current versus time graph across the inductor will be Fig.




**Answer: A::C**



**Watch Video Solution**

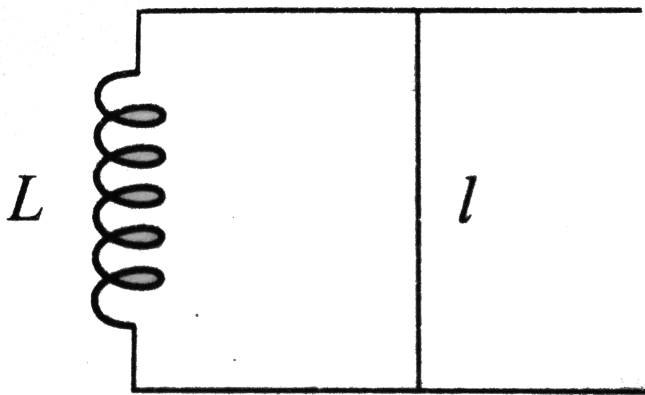4. Two parallel resistanceless rails are connected by an inductor of inductance  $L$  at one end as shows in Fig. A magnetic field  $B$

exists in the space which is perpendicular to the plane of the rails. Now a conductor of length  $l$  and mass  $m$  is placed transverse on the rail and given an impulse  $J$  toward the rightward direction. Then choose the correct option (S).



A. Velocity of the conductor is half of the initial velocity after a displacement of

the conductor  $d = \sqrt{\frac{3J^2L}{4B^2l^2m}}$

B. Current flowing through the inductor at the instant when velocity of the conductor is half of the initial velocity is

$$i = \sqrt{\frac{3J^2}{4Lm}}$$

C. Velocity of the conductor is half of the initial velocity after a displacement of

the conductor  $d = \sqrt{\frac{3J^2L}{B^2l^2m}}$

D. Current flowing through the inductor at the instant when velocity of the

conductor is half of the initial velocity is

$$i = \sqrt{\frac{3j^2}{mL}}$$

**Answer: A::B**



**Watch Video Solution**

5. Two inductors are connected in parallel and switch S is closed at  $t = 0$



A. At  $t = 0$ ,  $I_1 = I_2 = 0$

B. At any time  $t$ ,  $\frac{I_0}{I_2} = \frac{L_2}{L_1}$

C. At any time  $t$ ,  $I_1 + I_2 = \frac{\varepsilon}{R}$


D. At  $t = \infty$ ,  $I_1$  and  $I_2$  are independent of  $L_1$  and  $L_2$

**Answer: A:B**







**Watch Video Solution**

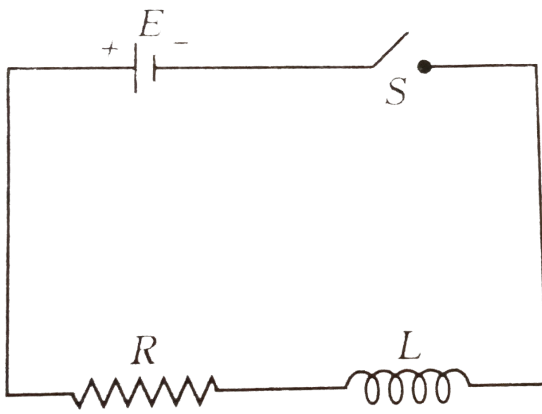6. Switch  $S$  of the circuit shown in figure is closed at  $t = 0$ .



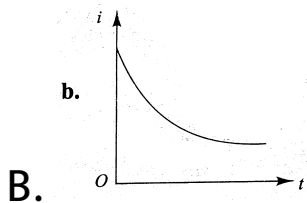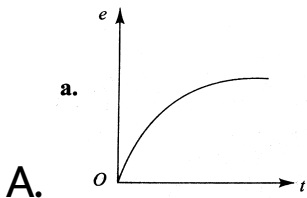If emf in  $L$  is  $e$  and  $i$  is the current flowing through the circuit at time  $t$ , which of the following graphs is correct?



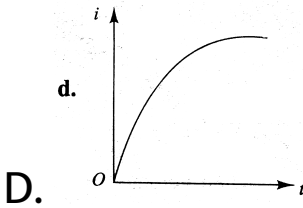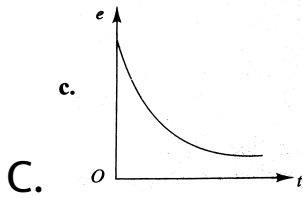


**Answer: C::D**



**Watch Video Solution**

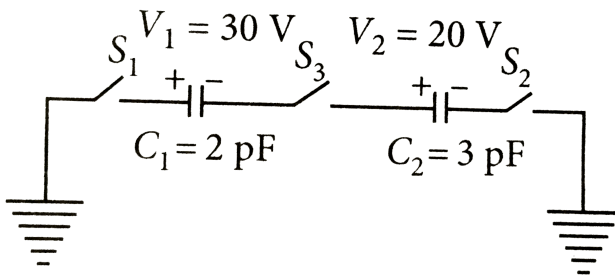7. For the circuit shown in figure, which of the following statements is true ?





- A. Its time constant is  $0.25s$
- B. In steady state, current through the inductance will be equal to zero
- C. In steady state, current through the battery will be equal to  $0.75A$
- D. None of these

**Answer: A::C**



Watch Video Solution

## Exercises (assertion-reasoning)

1. Assertion Two concentric conducting rings of different radii are placed in space. The mutual inductance of both the rings is maximum, if the rings are coplanar.

Reason For two co-axial conducting rings of different radii, the magnitude of magnetic flux in one ring due to current in other ring is maximum when both rings are coplanar.

A. Statement I is True, Statement II is True,  
Statement II is the correct explanation  
for Statement I.

B. Statement I is True, Statement II is True,  
Statement II is NOT the correct  
explanation for Statement I.

C. Statement I is True, Statement II is False.

D. Statement I is False, Statement II is True.

**Answer: A**



**Watch Video Solution**

2. Statement I: An electric lamp is connected in series with a long solenoid of copper with air core and then connected to an ac source. If an iron rod is inserted in the solenoid, the lamp will become dim.

Statement II: If an iron rod is inserted in the solenoid, the inductance of the solenoid increases.

A. Statement I is True, Statement II is True,

Statement II is the correct explanation

for Statement I.

B. Statement I is True, Statement II is True,

Statement II is NOT the correct

explanation for Statement I.

C. Statement I is True, Statement II is False.

D. Statement I is False, Statement II is True.


**Answer: A**



**Watch Video Solution**

## Exercises (linked Comprehension)

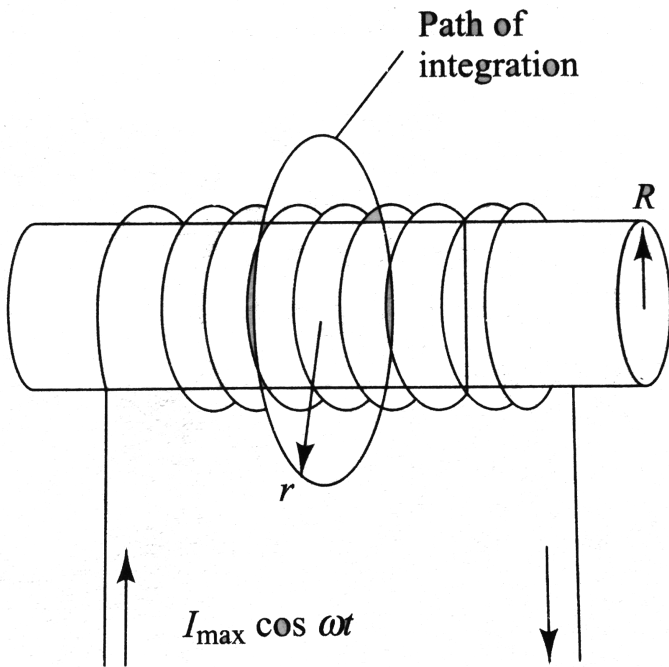1. A long solenoid of radius  $R$  has  $n$  turns of wire per unit length and carries a time-varying current that varies sinusoidally as  $I = I_{\max} \cos \omega t$ , where  $I_{\max}$  is the maximum current and  $\omega$  is the angular frequency of the alternating current source (shown in Fig.)



The magnitude of the induced electric field inside the solenoid, a distance  $r < R$  from its long central axis is

A.  $\frac{3\mu_0 n I_{\max} \omega}{2} r \sin \omega t$

B.  $\frac{\mu_0 n I_{\max} \omega}{2} r \cos \omega t$

C.  $\mu_0 n I_{\max} \omega r \sin \omega t$

D.  $\frac{\mu_0 n I_{\max} \omega}{2} r \sin \omega t$

**Answer: D**




**Watch Video Solution**

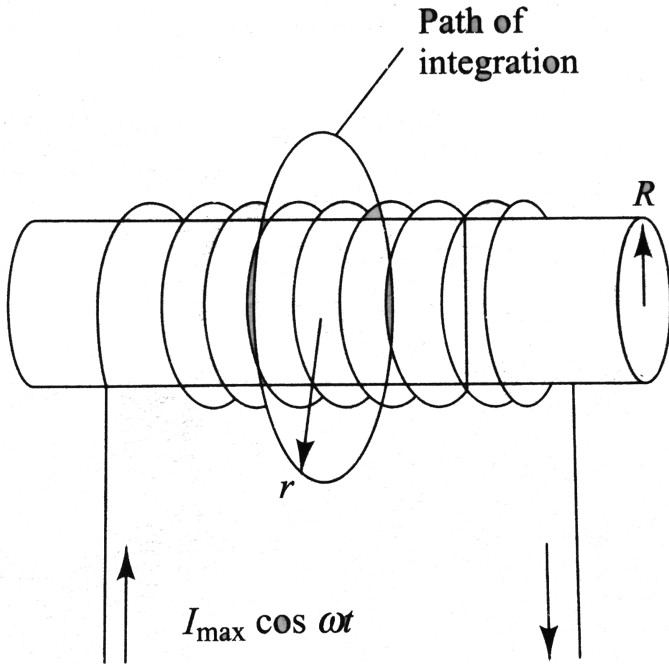2. A long solenoid of radius  $R$  has  $n$  turns of wire per unit length and carries a time-varying current that varies sinusoidally as  $I = I_{\max} \cos \omega t$ , where  $I_{\max}$  is the maximum current and  $\omega$  is the angular frequency of the



alternating current source (shows in Fig.)



The magnitude of electric field outside the solenoid at a distance  $r > R$  from its long central axis is

$$A. \frac{\mu_0 n I_{\max} \omega R^2}{2r} \sin \omega t$$

B.  $\frac{2\mu_0 n I_{\max} \omega R^2}{r} \sin \omega t$

C.  $\frac{\mu_0 n I_{\max} \omega R^2}{3r} \sin \omega t$

D.  $\frac{3\mu_0 n I_{\max} \omega R^2}{2r} \sin \omega t$


**Answer: A**



**Watch Video Solution**

**3.** In the Figure shown  $i_1 = 10e^{-2t} A$ ,  $i_2 = 4A$

and  $V_C = 3e^{-2t} V$ . Determine

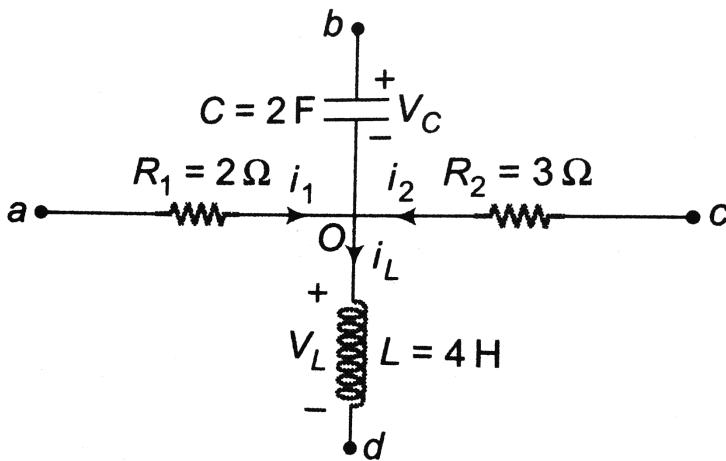

a.  $i_L$  and  $V_L$  b.  $V_{ac}$ ,  $V_{ab}$ ,  $V_{cd}$

A.  $[2 - 2(1 - e^{-2t})] A$

B.  $[2 + 2(1 - e^{-2t})] A$

C.  $[3 - 2(1 - e^{-2t})] A$


D.  $[2 + 3(1 - e^{-2t})] A$

**Answer: B**







Watch Video Solution

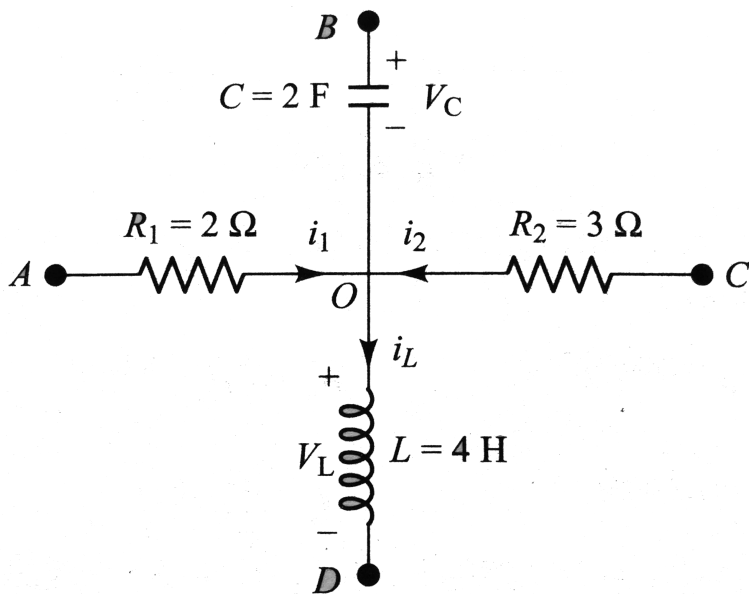4. In Fig  $i_1 = 10e^{-2t} A$ ,  $i_2 = 4A$ , and  $V_C = 3e^{-2t} V$ .



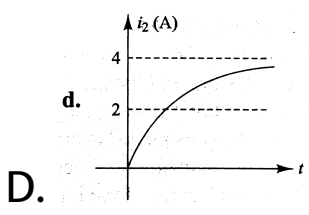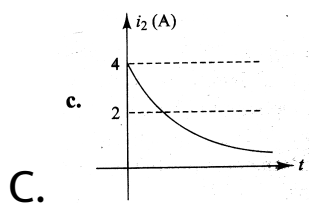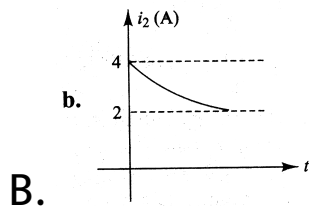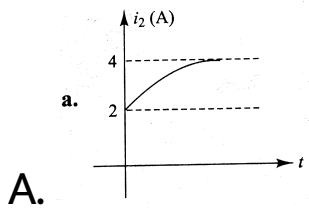
The variation of current in the inductor with time can be represented as



**Answer: A**

 [View Text Solution](#)

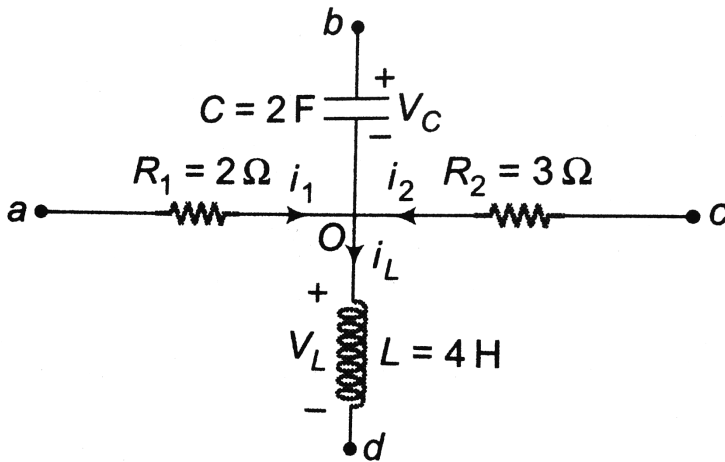5. In the Figure shown  $i_1 = 10e^{-2t} A$ ,  $i_2 = 4A$  and  $V_C = 3e^{-2t} V$ . Determine



a.  $i_L$  and  $V_L$  b.  $V_{ac}$ ,  $V_{ab}$ ,  $V_{cd}$

A.  $8e^{-2t} V$

B.  $9e^{-2t} V$

C.  $16e^{-2t} V$


$$D. 18e^{-2t}V$$

**Answer: C**





**Watch Video Solution**


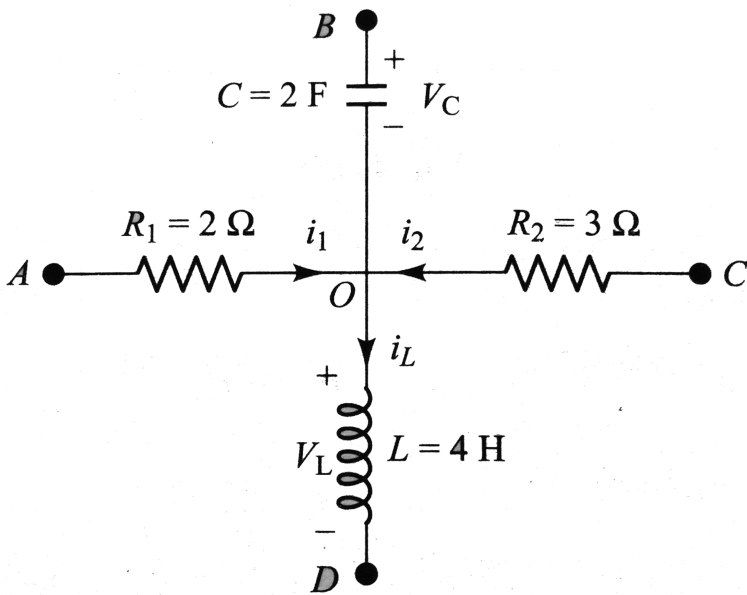
6. In Fig  $i_1 = 10e^{-2t}A$ ,  $i_2 = 4A$ , and  $V_C = 3e^{-2t}V$ .



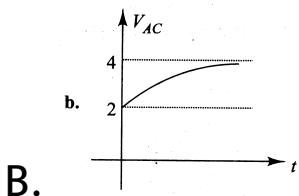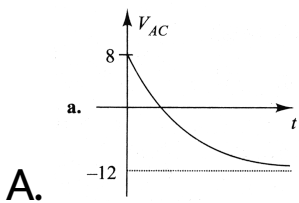the variation of potential difference across  $A$  and  $C$  ( $V_{AC}$ ) with time can be represented as





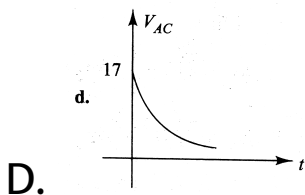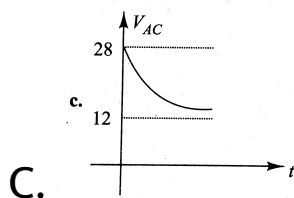


**Answer: A**



**Watch Video Solution**

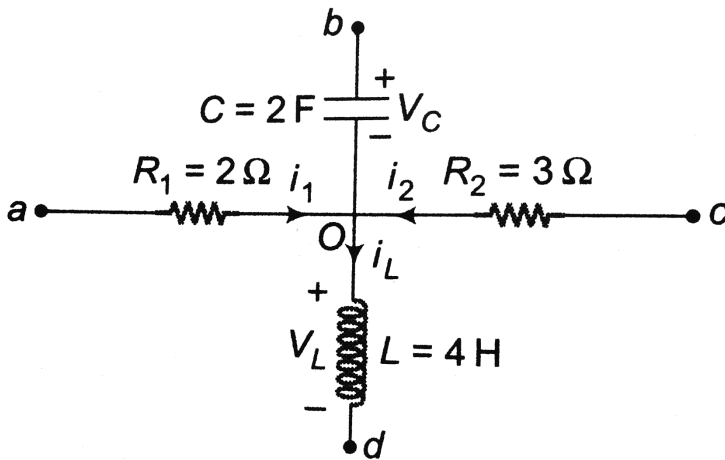7. In the Figure shown  $i_1 = 10e^{-2t} A$ ,  $i_2 = 4A$  and  $V_C = 3e^{-2t} V$ . Determine



a.  $i_L$  and  $V_L$  b.  $V_{ac}$ ,  $V_{ab}$ ,  $V_{cd}$

A.  $8e^{-2t}\text{V}$

B.  $\frac{1}{2}e^{-3t}\text{V}$

C.  $17e^{-2t}\text{V}$


D.  $16e^{-2t}\text{V}$

**Answer: C**







Watch Video Solution

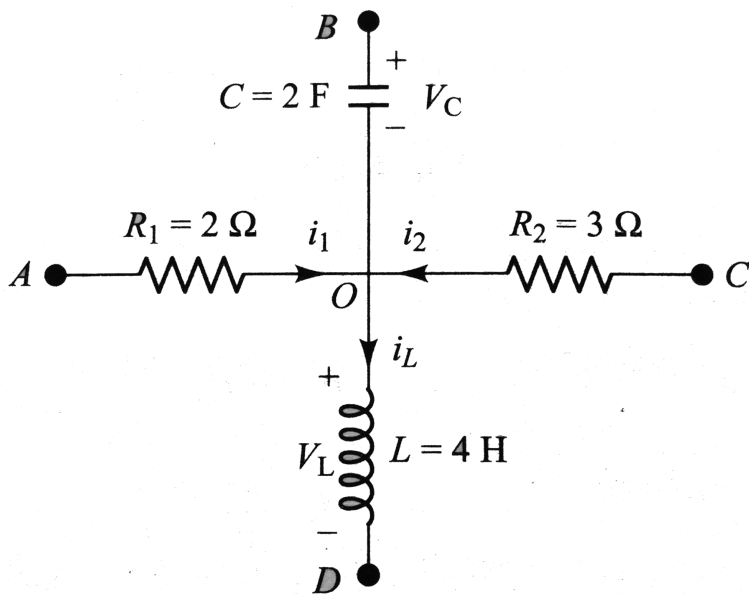8. In Fig  $i_1 = 10e^{-2t} A$ ,  $i_2 = 4A$ , and  $V_C = 3e^{-2t} V$ .



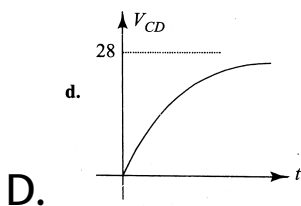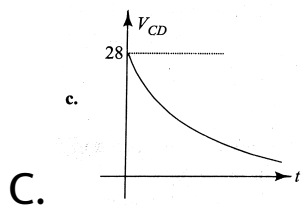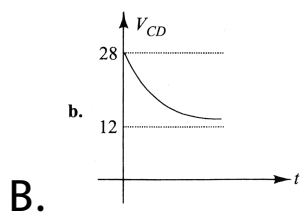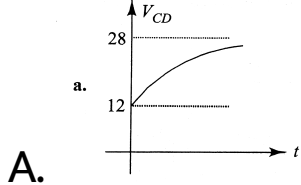The variation of potential difference across  $C$  and  $D(V_{CD})$  with time can be expressed as




**Answer: B**



**Watch Video Solution**

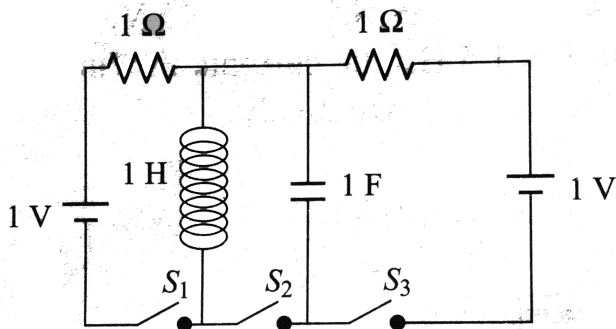9. In the circuit shows (Fig.) switches  $S_1$  and  $S_3$  have been closed for  $1s$  and  $S_2$  remained open. Just after  $1s$ , switch  $S_2$  is closed and  $S_1$  and  $S_3$  are opened. Find after that instant ( $t = 0$ ):



the maximum current in the circuit containing inductor and capacitor (only  $S_2$  is closed)

A.  $\sqrt{3} \left( 1 - \frac{1}{e} \right)$

B.  $\sqrt{2} \left( 1 - \frac{1}{e} \right)$

C.  $\sqrt{3} \left( 1 + \frac{1}{e} \right)$

D.  $\sqrt{2} \left( 1 + \frac{1}{e} \right)$

**Answer: B**




**Watch Video Solution**

**10.** In the circuit shows (Fig.) switches  $S_1$  and  $S_3$  have been closed for  $1s$  and  $S_2$  remained open. Just after  $1s$ , switch  $S_2$  is closed and  $S_1$

and  $S_3$  are opened. Find after that instant

( $t = 0$ ):

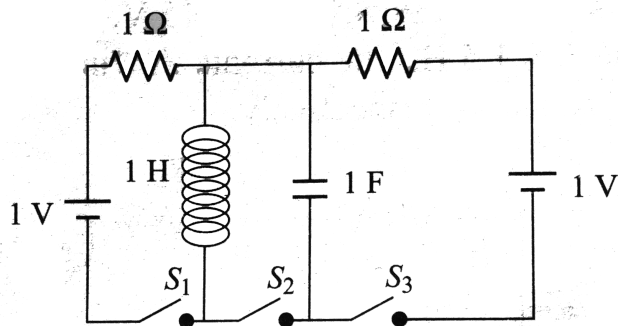

the maximum charge on the capacitor

A.  $\sqrt{3} \left( 1 + \frac{1}{e} \right)$

B.  $\sqrt{3} \left( 1 - \frac{1}{e} \right)$

C.  $\sqrt{2} \left( 1 + \frac{1}{e} \right)$

D.  $\sqrt{2} \left( 1 - \frac{1}{e} \right)$


**Answer: D**



**Watch Video Solution**

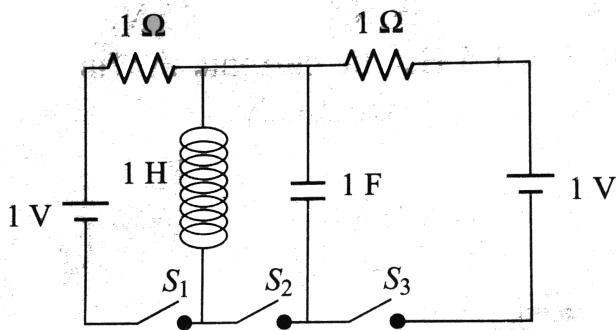**11.** In the circuit shows (Fig.) switches  $S_1$  and  $S_3$  have been closed for  $1s$  and  $S_2$  remained open. Just after  $1s$ , switch  $S_2$  is closed and  $S_1$  and  $S_3$  are opened. Find after that instant ( $t = 0$ ):





the charge on the upper plate of the capacitor  
as a function of time


- A.  $\sqrt{2} \left(1 - \frac{1}{e}\right) \sin\left(t + \frac{3\pi}{4}\right)$
- B.  $\sqrt{2} \left(1 - \frac{1}{e}\right) \sin\left(t + \frac{\pi}{4}\right)$
- C.  $\sqrt{3} \left(1 - \frac{1}{e}\right) \sin\left(t + \frac{\pi}{4}\right)$
- D.  $\sqrt{3} \left(1 + \frac{1}{e}\right) \sin\left(t + \frac{\pi}{4}\right)$

**Answer: A**



**Watch Video Solution**

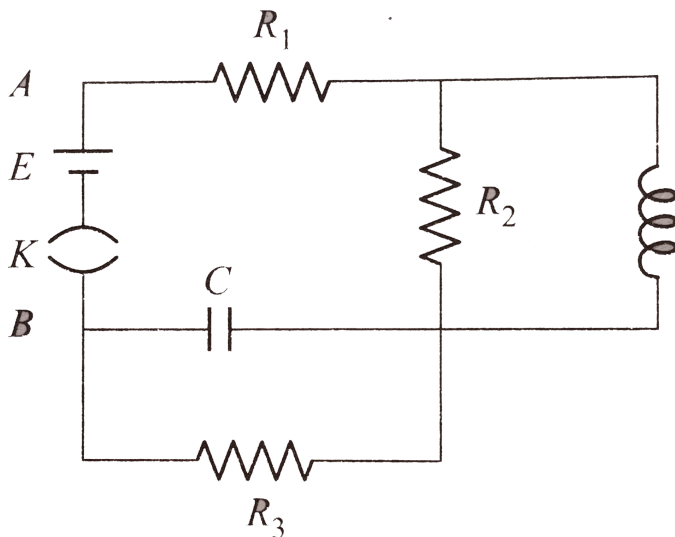**12.** In the given (Fig.) all the symbols have their usual meanings. At  $t = 0$ , key  $K$  is closed. Now answer the following questions.



At  $t = 0$ , the equivalent resistance between  $A$  and  $B$  is

A.  $R_1 + R_2 + R_3$

B.  $R_1 + R_2$

C.  $R_1 + R_3$


D. indeterminate

**Answer: B**



**Watch Video Solution**

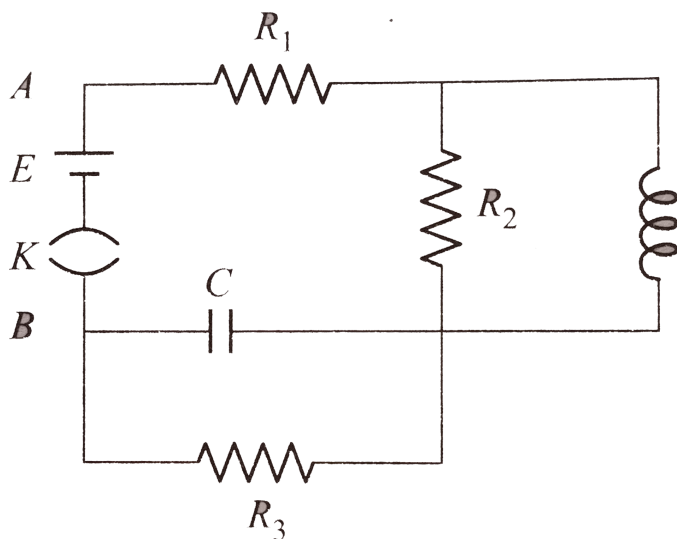13. In the given (Fig.) all the symbols have their usual meanings. At  $t = 0$ , key  $K$  is closed. Now answer the following questions.



At  $t \rightarrow \infty$ , the equivalent resistance between  $A$  and  $B$  is

A.  $R_1 + R_2 + R_3$

B.  $R_1 + R_2$

C.  $R_1 + R_3$

D. None of these

**Answer: C**




**Watch Video Solution**

**14.** In the circuit shows in Fig  $E = 15V$ ,

$R_1 = 1\Omega$ ,  $R_2 = 1\Omega$ ,  $R_3 = 2\Omega$ , and  $L = 1.5H$ .

The currents flowing through  $R_1$ ,  $R_2$ , and  $R_3$

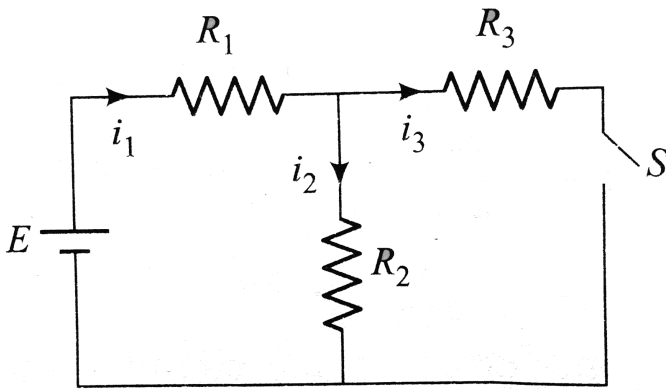are  $i_1$ ,  $i_2$ , and  $i_3$ , respectively.



Immediately after tuning switch  $S$  on,

- A.  $i_1 = i_2 = 7.5A, i_3 = 0A$
- B.  $i_1 = i_3 = 5A, i_2 = 0A$
- C.  $i_1 = i_2 = 9A, i_3 = 0A$
- D.  $i_1 = i_2 = i_3 = 0A$

**Answer: A**




Watch Video Solution

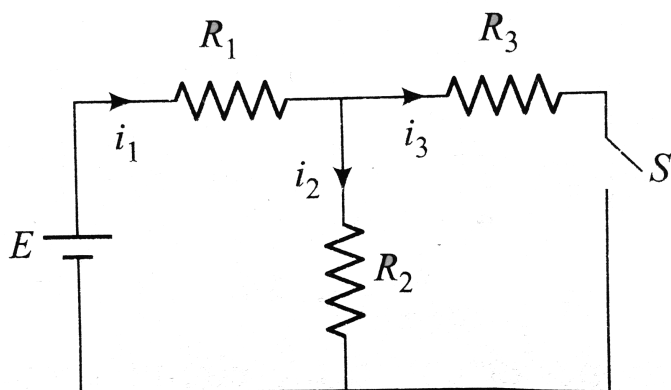15. In the circuit shows in Fig  $E = 15V$ ,  
 $R_1 = 1\Omega$ ,  $R_2 = 1\Omega$ ,  $R_3 = 2\Omega$ , and  $L = 1.5H$ .

The currents flowing through  $R_1$ ,  $R_2$ , and  $R_3$   
are  $i_1$ ,  $i_2$ , and  $i_3$ , respectively.

Immediately after turning switch  $S$  on,



A.  $i_1 = 9A, i_2 = 6A, i_3 = 3A$

B.  $i_1 = 9A, i_2 = 3A, i_3 = 6A$

C.  $i_1 = 6A, i_2 = 6A, i_3 = 0A$

D.  $i_1 = 0A, i_2 = 0A, i_3 = 0A$

**Answer: A**



**Watch Video Solution**


**16.** In the circuit shows in Fig  $E = 15V$ ,  
 $R_1 = 1\Omega, R_2 = 1\Omega, R_3 = 2\Omega$ , and  $L = 1.5H$ .

The currents flowing through  $R_1, R_2,$ and  $R_3$



are  $i_1$ ,  $i_2$ , and  $i_3$ , respectively.

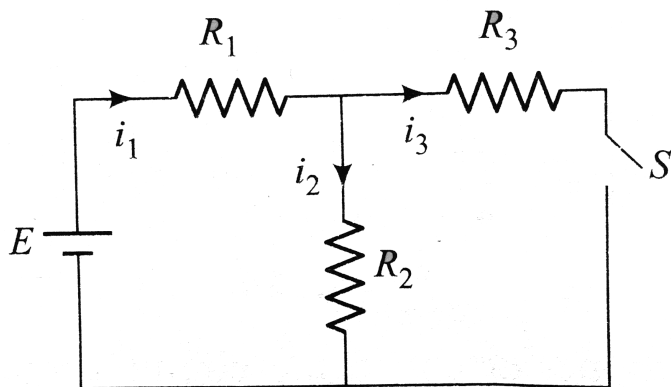Immediately after turning switch  $S$  on,



A.  $i_3 = 0A$  and  $\frac{di_3}{dt} = 0As^{-1}$

B.  $i_3 = 0A$  and  $\frac{di_3}{dt} \neq 0As^{-1}$

C.  $i_3 = 0A$  and the rate at which magnetic energy stored is not zero


D. None of these

**Answer: B**



**Watch Video Solution**

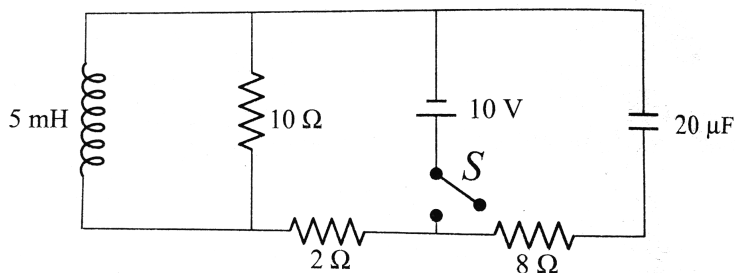17. In the given at  $t = 0$ , switch  $S$  is closed.



The current through the  $10\Omega$  resistor at any instant  $t(0 < t < \infty)$  will be

A.  $\frac{1}{6}e^{-(1000/3)t}$

B.  $\frac{5}{6}e^{-(1000/3)t}$

C.  $\frac{1}{6}e^{(1000/3)t}$


D.  $\frac{6}{5}e^{(1000/3)t}$

**Answer: B**



**Watch Video Solution**

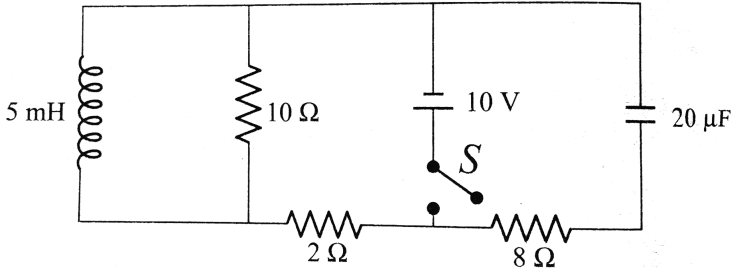18. In the given at  $t = 0$ , switch  $S$  is closed.



The energy stored in the inductor at any instant  $t(0 < t < \infty)$  will be


- A.  $\frac{1}{2} \left[ 5 - 5e^{- (1000/3)t} \right]^2 \text{ mJ}$
- B.  $\frac{125}{2} \left[ 1 - e^{- (1000/3)t} \right]^2 \text{ mJ}$
- C.  $\frac{25}{2} \left[ 1 - e^{- (1000/3)t} \right]^2 \text{ mJ}$
- D.  $\frac{5}{2} \left[ 1 - e^{- (1000/3)t} \right]^2 \text{ mJ}$

**Answer: B**



**Watch Video Solution**

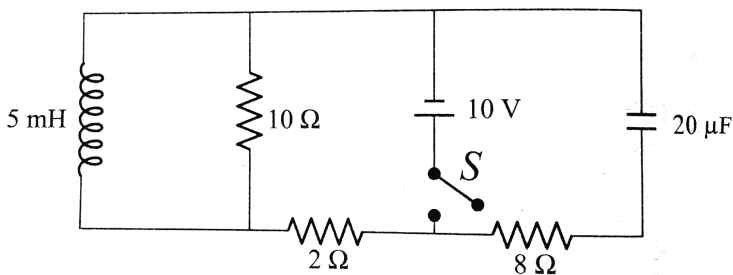**19.** In the given at  $t = 0$ , switch  $S$  is closed.



The energy stored in the capacitor and inductor, respectively, at  $t \rightarrow \infty$  will be

A.  $1mJ$  and  $62.5mJ$

B.  $62.5mJ$  and  $1mJ$

C.  $2mJ$  and  $62.5mJ$

D.  $1mJ$  and  $60mJ$

**Answer: A**



**Watch Video Solution**

**20.** In Fig. there is a frame consisting of two square loops having resistors and inductors as shown. This frame is placed in a uniform but time-varying magnetic field in such a way that


one of the loops is placed in crossed magnetic field and the other is placed in dot magnetic field. Both magnetic fields are perpendicular to the planes of the loops.

If the magnetic field is given by

$$B = (20 + 10t) \text{ Wbm}^{-2} \quad \text{in both regions}$$

$$[l = 20\text{cm}, b = 10\text{cm}, \quad \text{and} \quad R = 10\Omega,$$

$$L = 10\text{H}),$$

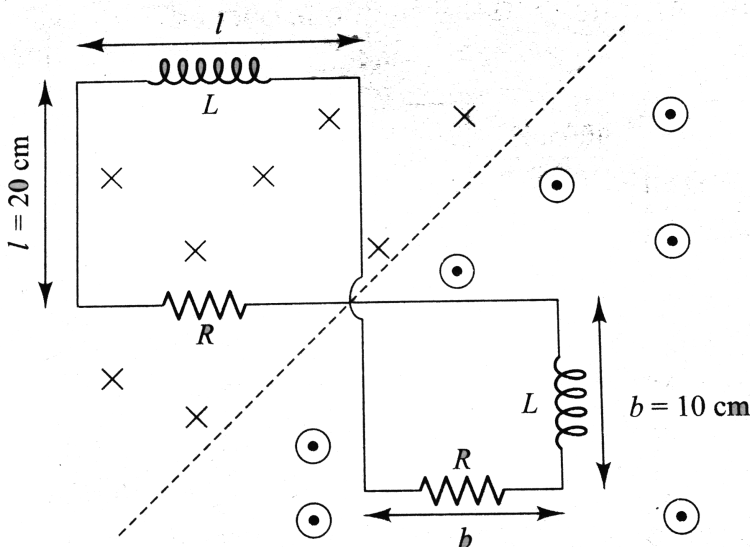

The direction in induced current in the bigger loop will be

A. clockwise

B. anticlockwise

C. first clockwise for some time, then anticlockwise, and so on

D. first clockwise for some time, then clockwise, and so on

**Answer: B**



**Watch Video Solution**




21. In Fig. there is a frame consisting of two square loops having resistors and inductors as shown. This frame is placed in a uniform but time-varying magnetic field in such a way that one of the loops is placed in crossed magnetic field and the other is placed in dot magnetic field. Both magnetic fields are perpendicular to the planes of the loops.

If the magnetic field is given by

$$B = (20 + 10t) \text{Wbm}^{-2} \quad \text{in both regions}$$

$$[l = 20\text{cm}, b = 10\text{cm}, \quad \text{and} \quad R = 10\Omega,$$

$L = 10H$ ),

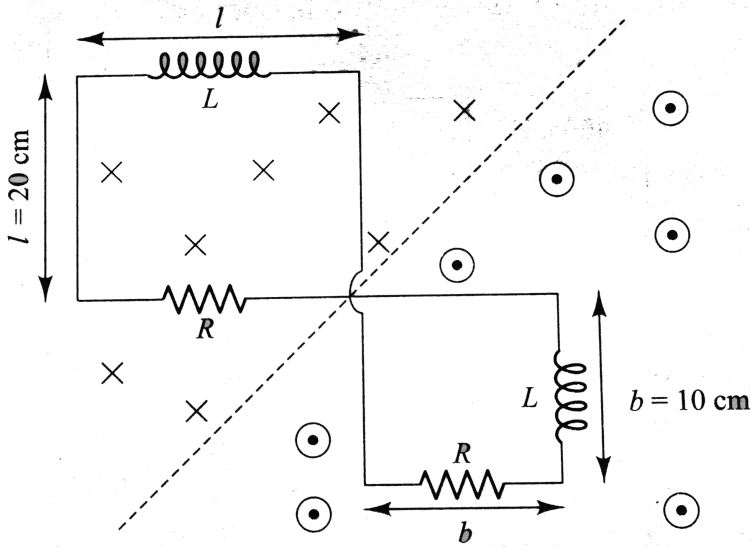

The induced emf in the frame only due to the variation of magnetic field will be

- A.  $0.3V$
- B.  $0.1V$
- C.  $0.5V$

D.  $0.4V$

**Answer: C**



**Watch Video Solution**

**22.** In Fig. there is a frame consisting of two square loops having resistors and inductors as shown. This frame is placed in a uniform but time-varying magnetic field in such a way that one of the loops is placed in crossed magnetic field and the other is placed in dot magnetic


field. Both magnetic fields are perpendicular to the planes of the loops.

If the magnetic field is given by

$$B = (20 + 10t) \text{ Wbm}^{-2} \quad \text{in both regions}$$

$$[l = 20\text{cm}, b = 10\text{cm}, \quad \text{and} \quad R = 10\Omega,$$

$$L = 10\text{H}),$$

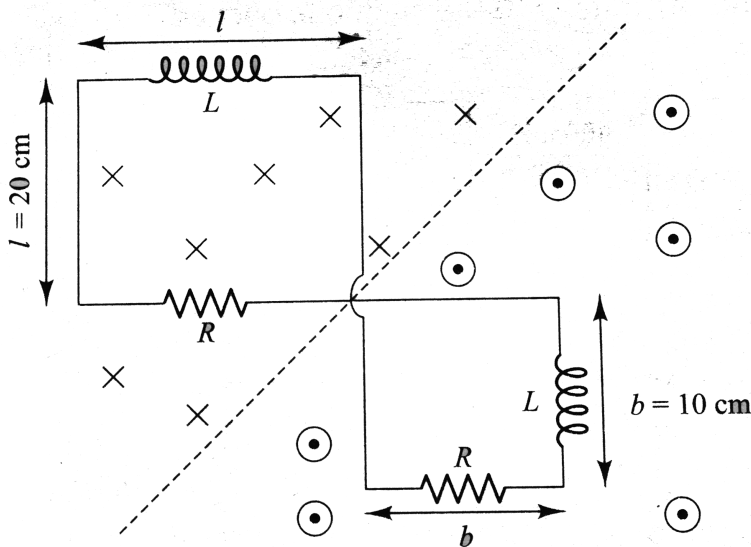

The current in the frame as a function of time will be

A.  $\frac{1}{20} (1 - e^{-t})$

B.  $\frac{1}{40} (1 - e^{-t})$

C.  $\frac{1}{20} e^{-t}$


D.  $\frac{1}{10} e^{-t}$

**Answer: B**



**Watch Video Solution**

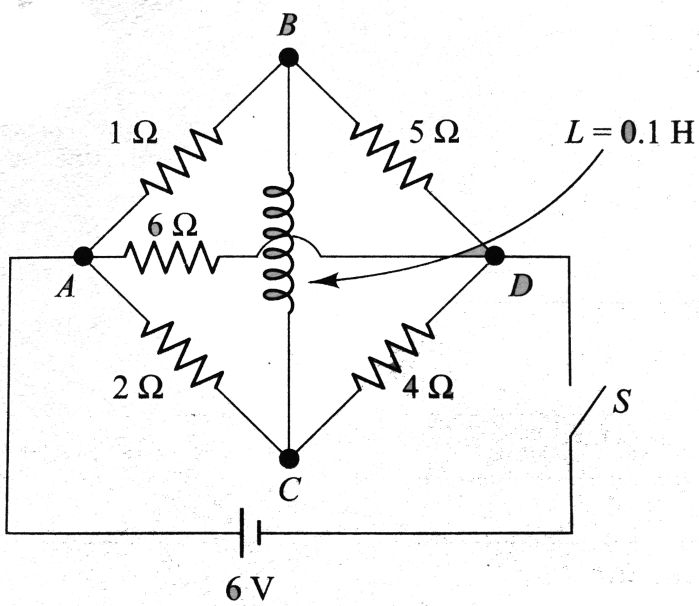**23.** there is no current part of this circuit for time  $t < 0$ . Switch  $S$  is closed at  $t = 0$ .



The rate at which the current through the inductor increases initially is


- A. zero
- B.  $10As^{-1}$
- C.  $1As^{-1}$
- D.  $5As^{-1}$

**Answer: B**



**Watch Video Solution**

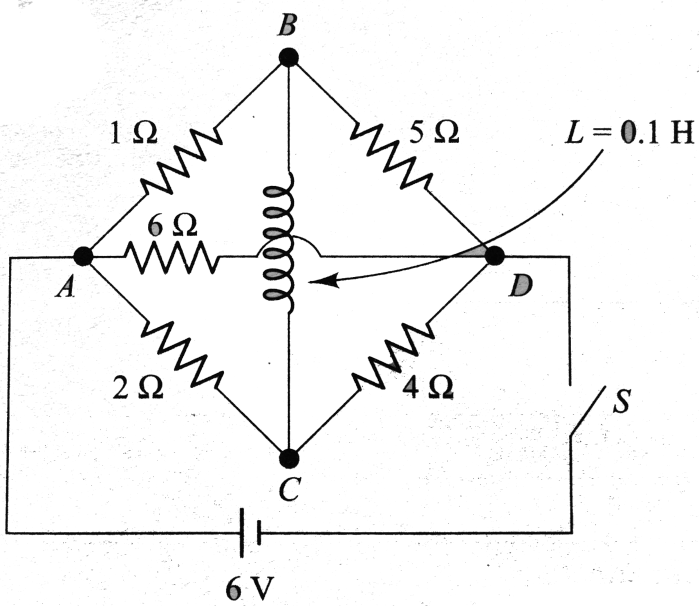**24.** there is no current part of this circuit for time  $t < 0$ . Switch  $S$  is closed at  $t = 0$ .



Current through the  $6\Omega$  resistor

- A. increases linearly with time
- B. increase non-linearly with time
- C. decreases non-linearly with time
- D. remains constant




**Answer: D**



**Watch Video Solution**

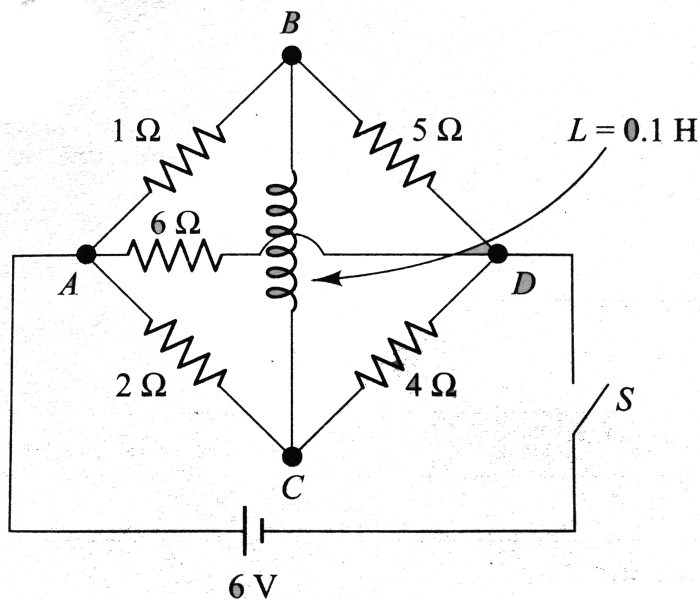25. there is no current part of this circuit for time  $t < 0$ . Switch  $S$  is closed at  $t = 0$ .



The current through the inductor after a long time will be

A. zero

B. infinite

C.  $\frac{6}{13} A$


D. None of these

**Answer: C**



**Watch Video Solution**

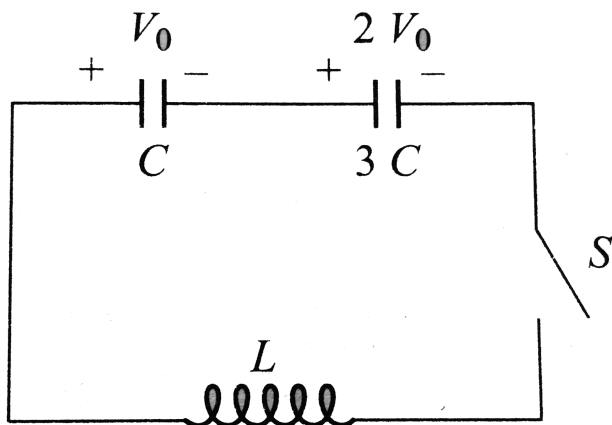26. Two capacitors of capacitance  $C$  and  $3C$  are charged to potential difference  $V_0$  and  $2V_0$ , respectively, and connected to an inductor of inductance  $L$  as shows in Fig. Initially, the current in the inductor is zero. Now, switch  $S$  is closed.



The maximum current in the inductor is

A.  $\frac{3V_0}{2} \sqrt{\frac{3C}{L}}$

B.  $V_0 \sqrt{\frac{3C}{L}}$

C.  $2V_0 \sqrt{\frac{3C}{L}}$

D.  $V_0 \sqrt{\frac{C}{L}}$


**Answer: A**



**Watch Video Solution**

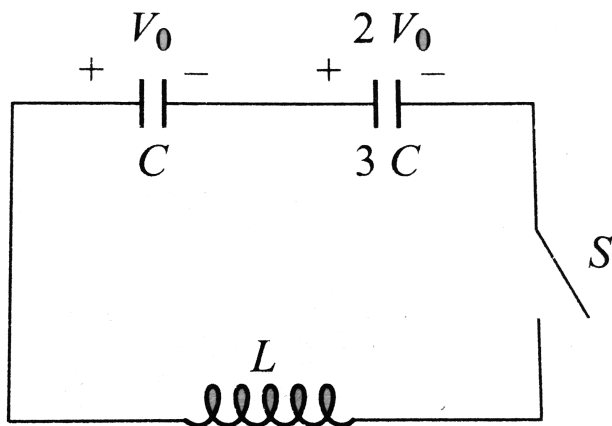**27.** Two capacitors of capacitance  $C$  and  $3C$  are charged to potential difference  $V_0$  and  $2V_0$ , respectively, and connected to an inductor of

inductance  $L$  as shows in Fig. Initially, the current in the inductor is zero. Now, switch  $S$  is closed.



Potential difference across capacitor of capacitance  $C$  when the current in the circuit is maximum is

A.  $\frac{V_0}{4}$

B.  $\frac{3V_0}{4}$

C.  $\frac{5V_0}{4}$

D. None of these


**Answer: C**



**Watch Video Solution**

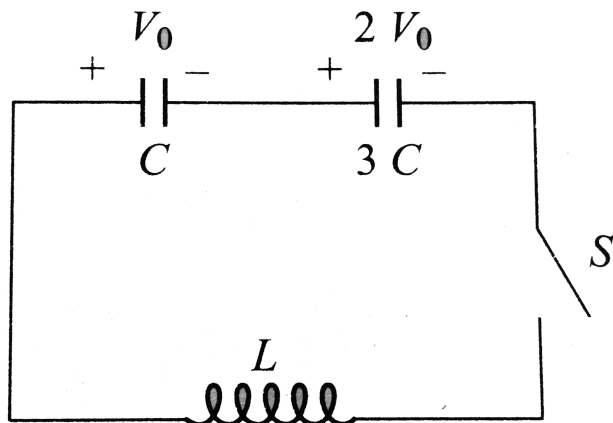**28.** Two capacitors of capacitance  $C$  and  $3C$  are charged to potential difference  $V_0$  and  $2V_0$ , respectively, and connected to an inductor of inductance  $L$  as shows in Fig. Initially, the

current in the inductor is zero. Now, switch  $S$  is closed.



Potential difference across capacitor of capacitance  $3C$  when the current in the circuit is maximum is

A.  $\frac{V_0}{4}$

B.  $\frac{V_0}{4}$

C.  $\frac{5V_0}{4}$

D. None of these

**Answer: C**




**Watch Video Solution**

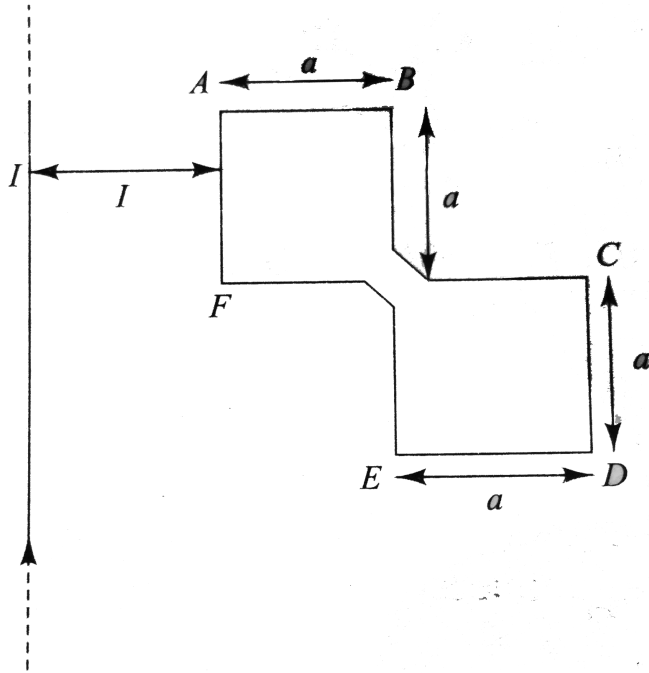**29.** In Fig. there is a conducting loop  $ABCDEF$  of resistance  $\lambda$  per unit length placed near a long straight current-carrying wire. The dimension are shows in the figure. The long wire lies in the plane of the loop. The



current in the long wire varies as  $I = I_0(t)$ .



The mutual inductance of the pair is

A.  $\frac{\mu_0 a}{2\pi} I n \left( \frac{2a + l}{l} \right)$

B.  $\frac{\mu_0 a}{2\pi} I n \left( \frac{2a - l}{l} \right)$

C.  $\frac{\mu_0 a}{\pi} I n \left( \frac{a + l}{l} \right)$


$$D. \frac{\mu_0 a}{\pi} \ln\left(\frac{a+l}{l}\right)$$

**Answer: A**



**Watch Video Solution**

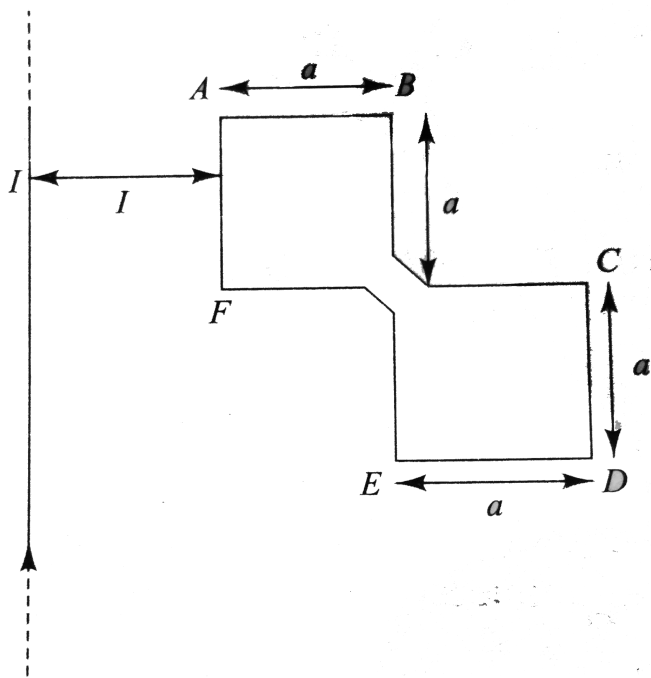**30.** In Fig. there is a conducting loop  $ABCDEF$  of resistance  $\lambda$  per unit length placed near a long straight current-carrying wire. The dimension are shows in the figure. The long wire lies in the plane of the loop. The current in the long wire varies as  $I = I_0(t)$ .



The emf induced in the closed loop is

A.  $\frac{\mu_0 I_0 a}{2\pi} I n \left( \frac{2a + l}{l} \right)$

B.  $\frac{\mu_0 I_0 a}{2\pi} I n \left( \frac{2a - l}{l} \right)$

C.  $\frac{\mu_0 I_0 a}{\pi} I n \left( \frac{a + l}{l} \right)$


D.  $\frac{\mu_0 a}{\pi} I n \left( \frac{a + l}{l} \right)$

**Answer: A**



**Watch Video Solution**

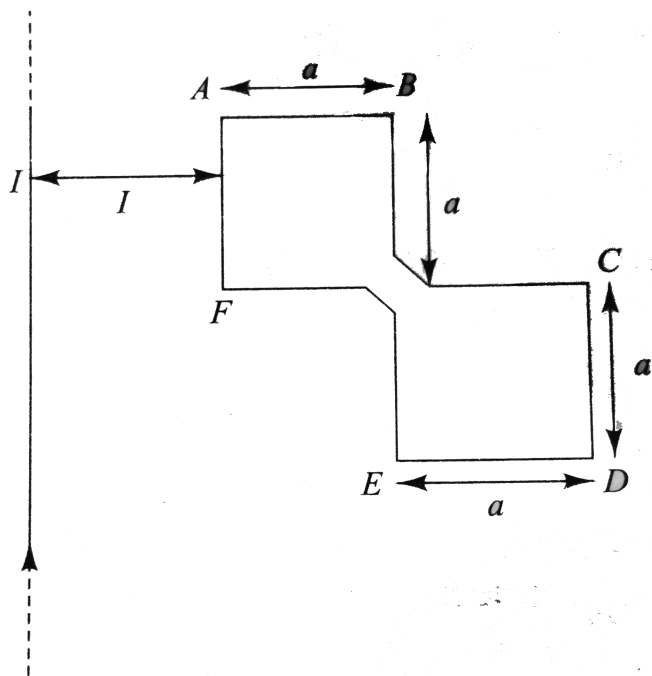**31.** In Fig. there is a conducting loop  $ABCDEF$  of resistance  $\lambda$  per unit length placed near a long straight current-carrying wire. The dimension are shows in the figure. The long wire lies in the plane of the loop. The current in the long wire varies as  $I = I_0(t)$ .



The heat produced in the loop in time  $t$  is

A. 
$$\frac{\left[ \frac{\mu_0 I_0}{2\pi} I n \left( \frac{a+l}{l} \right) \right]^2 at}{4\lambda}$$

B. 
$$\frac{\left[ \frac{\mu_0 I_0}{2\pi} I n \left( \frac{2a+l}{l} \right) \right]^2 at}{8\lambda}$$

C. 
$$\frac{\left[ \frac{\mu_0 I_0}{2\pi} I n \left( \frac{a+l}{l} \right) \right]^2 at}{3\lambda}$$


$$D. \frac{\left[ \frac{\mu_0 I_0}{2\pi} \ln\left(\frac{3a+l}{l}\right) \right]^2}{6\lambda} at$$

**Answer: B**



**Watch Video Solution**

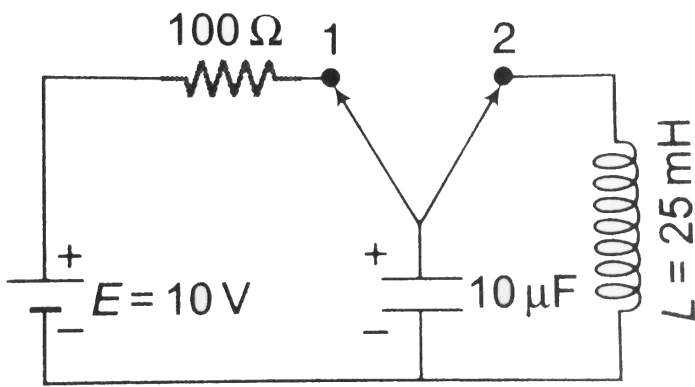**32.** Initially, the capacitor is charged to a potential of  $5V$  and then connected to position 1 with the shown polarity for  $1s$ . After  $1s$  it is connected across the inductor at position 2



(a) Find the potential across the capacitor after  $1\text{s}$  of its connection to position 1.

(b) Find the maximum current flowing in the  $L - C$  circuit when capacitor is connected across the inductor. Also, find the frequency of  $LC$  oscillations.

A.  $5 \times 10^3 \left( 2 + \frac{1}{e} \right) \text{V}$

B.  $5 \times 10^3 \left( 2 - \frac{1}{e} \right) \text{V}$

C.  $5 \times 10^3 \left(1 + \frac{2}{e}\right) V$

D. none of these


**Answer: B**



**Watch Video Solution**

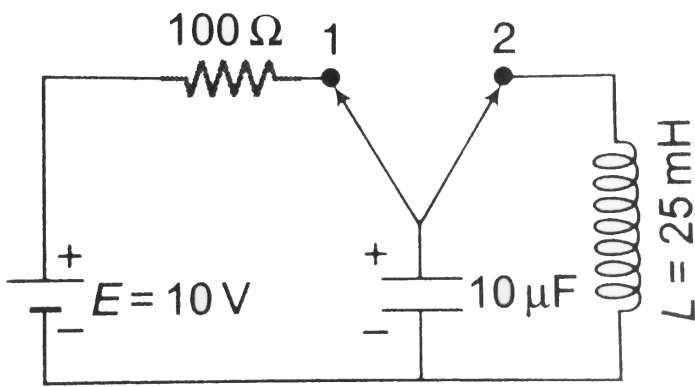**33.** Initially, the capacitor is charged to a potential of  $5V$  and then connected to position 1 with the shown polarity for  $1s$ . After  $1s$  it is connected across the inductor at position 2





(a) Find the potential across the capacitor after  $1\text{s}$  of its connection to position 1.

(b) Find the maximum current flowing in the  $L - C$  circuit when capacitor is connected across the inductor. Also, find the frequency of  $LC$  oscillations.

A.  $\left(2 - \frac{1}{e}\right) \times 10^4\text{A}$

B.  $\left(1 + \frac{2}{e}\right) \times 10^4\text{A}$

c.  $\left(1 - \frac{2}{e}\right) \times 10^4 A$


D. none of these

**Answer: A**



**Watch Video Solution**

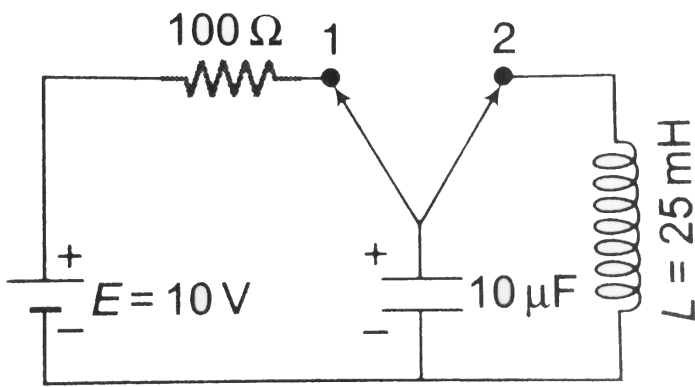**34.** Initially, the capacitor is charged to a potential of  $5V$  and then connected to position 1 with the shown polarity for  $1s$ . After  $1s$  it is connected across the inductor at position 2



(a) Find the potential across the capacitor after  $1\text{ s}$  of its connection to position 1.

(b) Find the maximum current flowing in the  $L - C$  circuit when capacitor is connected across the inductor. Also, find the frequency of  $LC$  oscillations.

A.  $(20 / \pi)\text{ Hz}$

B.  $(2 / \pi)\text{ Hz}$

C.  $(40 / \pi) Hz$


D.  $100 / \pi Hz$

**Answer: D**



**Watch Video Solution**

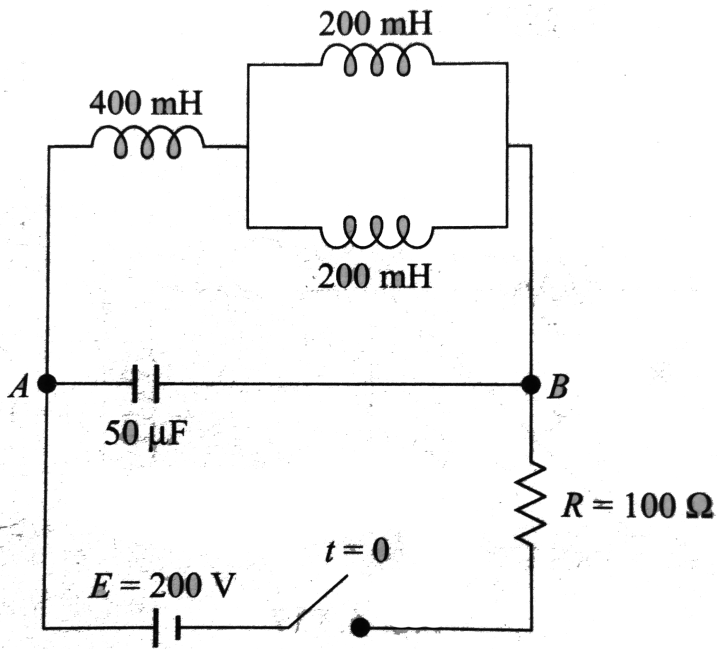**35.** In the circuit in Fig. switch  $S_1$  was closed for a long time . At time  $t = 0$  the switch is opened.



Find the maximum potential difference across the plates of the capacitor after the switch is opened.

A.  $100\text{ V}$

B.  $200\text{ V}$

C.  $300V$


D.  $400V$

**Answer: B**



**Watch Video Solution**

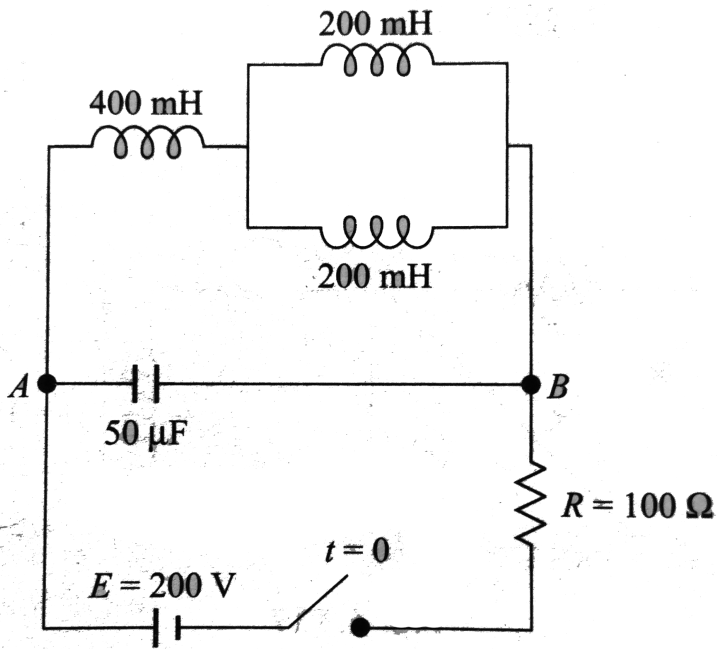**36.** In the circuit in Fig. switch  $S_1$  was closed for a long time . At time  $t = 0$  the switch is opened.



Find the angular frequency of oscillation of the charge on the capacitor.

- A.  $100 \text{ rad s}^{-1}$
- B.  $200 \text{ rad s}^{-1}$
- C.  $300 \text{ rad s}^{-1}$

$$D. 400 \text{rads}^{-1}$$

**Answer: B**



**Watch Video Solution**

## Exercises (integer)


1. Figure shows a part of a bigger circuit. The capacity of the capacitor is  $6mF$  and is decreasing at the constant rate  $0.5mFs^{-1}$ . The potential difference across the capacitor



at the shows moment is changing as follows:


$$\frac{dV}{dt} = 2Vs^{-1}, \quad \frac{d^2V}{dt^2} = \frac{1}{2}Vs^{-2}$$

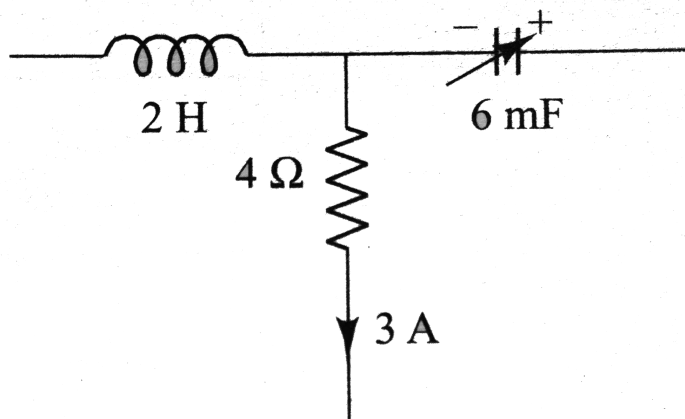The current in the  $4\Omega$  resistor is decreasing at the rate of  $1mA s^{-1}$ . What is the potential difference (in  $mV$ ) across the inductor at this moment?



[Watch Video Solution](#)

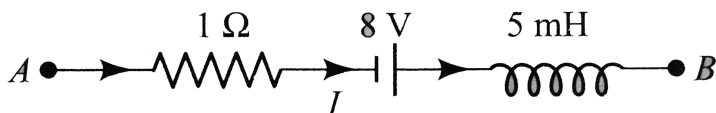2. In the circuit (Fig.) what is potential difference  $V_B - V_A$  (in  $V$ ) when current  $I$  is  $5A$  and is decreasing at the rate of  $10^3 A s^{-1}$



 [Watch Video Solution](#)


3. A current of  $2A$  is increasing at a rate of  $4A s^{-1}$  through a coil of inductance  $1H$ . Find

the energy stored in the inductor per unit time in the units of  $J_s^{-1}$ .



**Watch Video Solution**

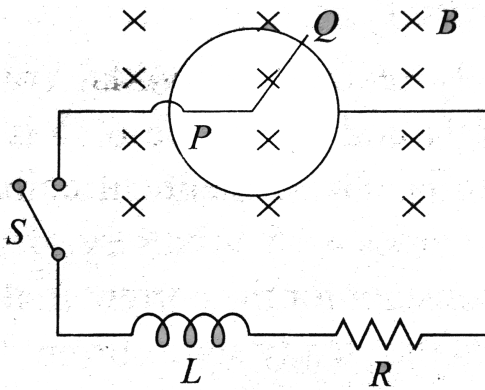4. Figure shows a circuit having a coil of resistance  $R = 2.5\Omega$  and inductance  $L$  connected to a conducting rod of radius  $10\text{cm}$  with its center at  $P$ .



Assume that friction and gravity are absent and a constant uniform magnetic field of  $5T$  exists as shown in figure. At  $t = 0$ , the circuit is switched on and simultaneously a time-varying external torque is applied on the rod so that it rotates about  $P$  with a constant angular velocity  $40\text{rads}^{-1}$ . Find the magnitude of this torque (in  $\text{mNm}$ ) when

current reaches half of its maximum value. Neglect the self inductance of the loop formed by the circuit.




[Watch Video Solution](#)

5. In the given circuit, initially switch  $S_1$  is closed, and  $S_2$  and  $S_3$  are open. After charging of capacitor, at  $t = 0$ ,  $S_1$  is opened and  $S_2$  and  $S_3$  are closed. If the relation between inductance, capacitance and resistance is  $L = 4CR^2$ , then find the time (in s) after

which current passing through capacitor and inductor will be same (given

$$R = 100\Omega, L = 2\text{mH})$$

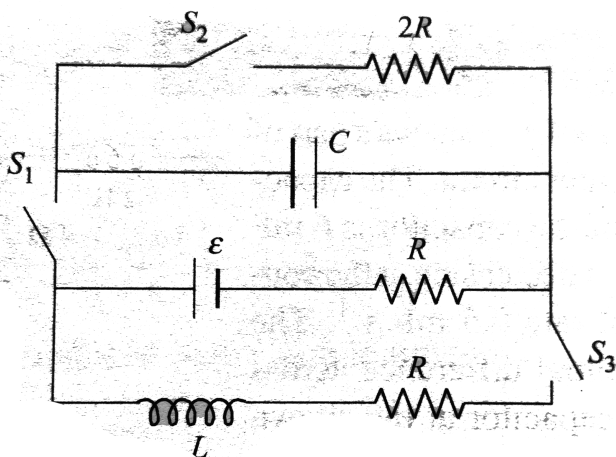

Watch Video Solution

6. Two coils, 1 and 2 have a mutual inductance

$M = 5\text{H}$  and resistance  $R = 10\Omega$  each. A

current flows in coil 1, which varies with time as:  $I_1 = 2t^2$ , where  $t$  is time. Find the total charge (in  $C$ ) that has flows through coil 2 between  $t = 0$  and  $t = 2s$ .



[Watch Video Solution](#)

7. A long solenoid of diameter  $0.1m$  has  $2 \times 10^4$  turns per metre. At the centre of the solenoid, a 100 – turns coil of radius  $0.01m$  is placed with its axis coinciding with the constant rate from  $+2A$  to  $2A$  in  $0.05s$ . Find

the total charge (in  $\mu C$ ) flowing through the coil during this time when the resistance of the coil is  $40 \sqrt{2} \Omega$ .



[Watch Video Solution](#)

**8.** A capacitor of capacitance  $2\mu F$  is charged to a potential difference of 12V. It is then connected across an inductor of inductance 0.6mH. The current in the circuit when the potential difference across the capacitor is 6V is





Watch Video Solution

## Archives (fills In The Blanks)

1. A uniform wound solenoidal coil of self inductance  $1.8 \times 10^{-4}$  henry and resistance 6 ohm is broken up into two identical coils. These identical coils are then connected in parallel across a 15-volt battery of negligible resistance. The time constant for the current in the circuit is.....seconds and the steady

state current through the battery is  
.....amperes.




[Watch Video Solution](#)

2. If  $\epsilon_0$  and  $\mu_0$  are, respectively, the electric permittivity and magnetic permeability of free space,  $\epsilon$  and  $\mu$  the corresponding quantities in a medium, the index of refraction of the medium in terms of the above parameters is \_\_\_\_\_.



[Watch Video Solution](#)

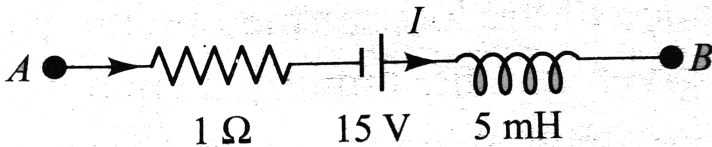3. The network shown in Fig is part of a complete circuit. If at a certain instant the current ( $I$ ) is  $5A$ , and is decreasing at a rate of  $10^5 A s^{-1}$  then  $V_B - V_A = -V$ .



[Watch Video Solution](#)

## Archives (single Correct )

1. A small square loop of wire of side  $l$  is placed inside a large square loop of wire of side  $L$  ( $L > l$ ). The loops are coplanar and their centres coincide. What is the mutual inductance of the system?

A.  $l/L$

B.  $l^2/L$

C.  $L/l$

D.  $L^2/l$

**Answer: B**



**Watch Video Solution**

2. A coil of inductance  $8.4 \text{ mH}$  and resistance  $6(\Omega)$  is connected to a  $12 \text{ V}$  battery. The current in the coil is  $1.0 \text{ A}$  at approximately the time

A.  $500s$

B.  $25s$

C.  $35ms$

D.  $1ms$


**Answer: D**



**Watch Video Solution**

**3.** A uniform but time-varying magnetic field  $B(t)$  exists in a cylindrical region of radius  $a$  and is directed into the plane of the paper as shown. The magnitude of the induced electric field at point P at a distance  $r$  from the centre

of the circular region

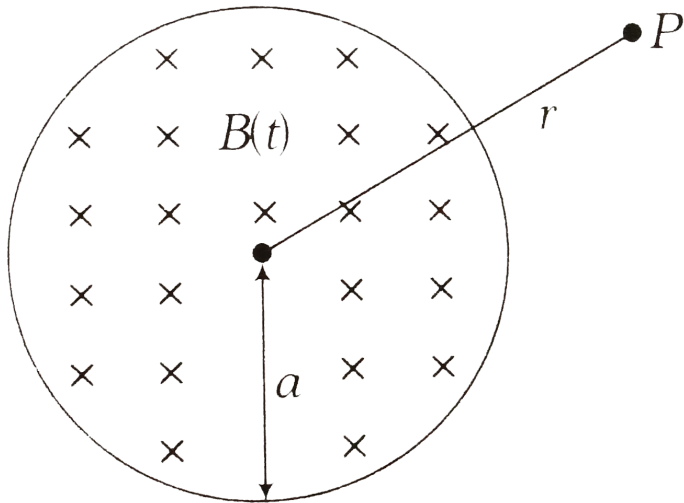

A. is zero

B. decreases as  $1/r$

C. increases as  $r$

D. decreases as  $1/r^2$

**Answer: B**



Watch Video Solution

4. A coil of wire having inductance and resistance has a conducting ring placed coaxially within it. The coil is connected to a battery at time  $t=0$ , so that a time-dependent current  $I_1(t)$  starts flowing through the coil. If  $I_2(t)$  is the current induced in the ring, and  $B(t)$  is the magnetic field at the axis of the coil due to  $I_1(t)$  then as a function of time ( $t > 0$ ), the product  $I_2(t)B(t)$



- A. increases with time
- B. decreases with time
- C. does not vary with time
- D. passes through a maximum


**Answer: D**



**Watch Video Solution**

5. Two circular coils can be arranged in any of the three situations shown in figure. Their

mutual inductance will be

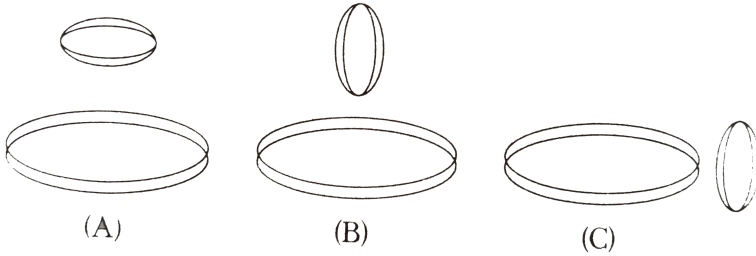

A. maximum in situation (i)

B. maximum in situation (ii)

C. maximum in situation (iii)

D. the same in all situations

**Answer: A**



**Watch Video Solution**

6. A short-circuited coil is placed in a time-varying magnetic field. Electrical power is dissipated due to the current induced in the coil. If the number of turns were to be quadrupled and the wire radius halved, then the electrical power dissipated would be

- A. halved
- B. the same
- C. doubled
- D. quadrupled





**Answer: B**




**Watch Video Solution**

7. A small bar magnet is being slowly inserted with constant velocity inside a solenoid as shown in figure. Which graph best represents the relationship between emf induced with

time

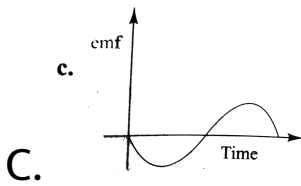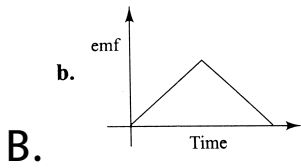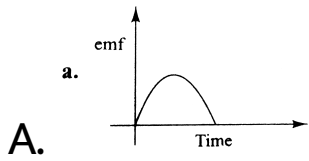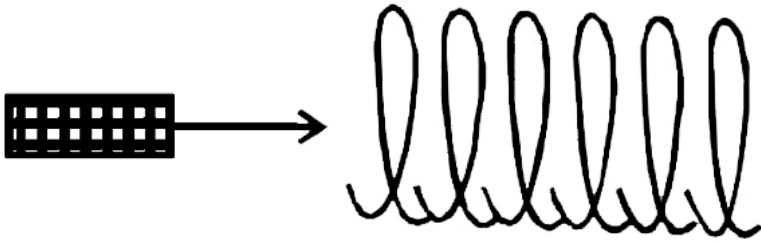

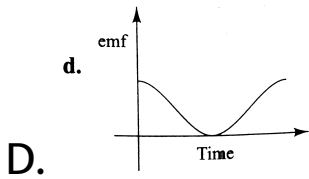

**Answer: C**



**Watch Video Solution**

8. Which of the field patterns given below is valid for electric field as well as for magnetic field?



**Watch Video Solution**

## Archives (multiple Correct)

1. Two different coils have self-inductance  $L_1 = 8mH$ ,  $L_2 = 2mH$ . The current in one coil is increased at a constant rate. The current in the second coil is also increased at the same rate. At a certain instant of time, the power given to the two coils is the same. At that time the current, the induced voltage and the energy stored in the first coil are  $i_1$ ,  $V_1$  and  $W_1$  respectively. Corresponding

values for the second coil at the same instant are  $i_2$ ,  $V_2$  and  $W_2$  respectively. Then,

A.  $\frac{i_1}{i_2} = \frac{1}{4}$

B.  $\frac{i_1}{i_2} = 4$

C.  $\frac{W_1}{W_2} = \frac{1}{4}$

D.  $\frac{V_1}{V_2} = 4$

**Answer: A::C::D**



**Watch Video Solution**



2. The SI unit of the inductance , the henry can  
by written as

A. weber//ampere

B. volt-second//ampere

C. joule//(ampere) <sup>^</sup> (2)


D. ohm-second

**Answer: A::B::C::D**



**Watch Video Solution**

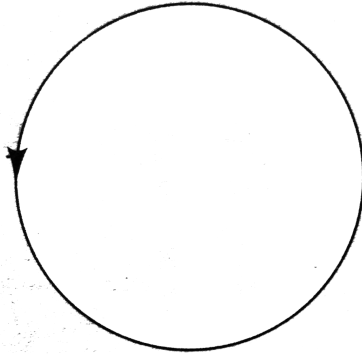3. A field line is shown in Fig. This field cannot represent



- A. Magnetic field
- B. Electrostatic field
- C. Induced electric field
- D. Gravitational field


**Answer: B::D**



**Watch Video Solution**

## Archives (linked Comprehension)

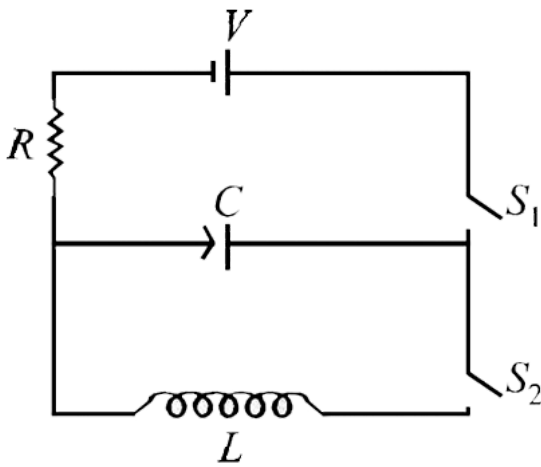1. In the given circuit the capacitor (C) may be charged through resistance R by a battery V by closing switch ( $S_1$ ). Also when ( $S_1$ ) is open and ( $S_2$ ) is closed the capacitor is connected in series with inductor (L).



At the start, the capacitor was uncharged. when switch ( $S_1$ ) is closed and ( $S_2$ ) is kept open, the time constant of this circuit is  $\tau$ . which of the following is correct

- A. After time interval  $\tau$ , charge on the capacitor is  $CV/2$


- B. After time interval  $2\tau$ , charge on the capacitor is  $CV(1 - e^{-2})$
- C. The work done by the voltage source will be half of the heat dissipated when the capacitor is fully charged
- D. After time interval  $2\tau$ , charge on the capacitor is  $CV(1 - e^{-1})$

**Answer: B**



**Watch Video Solution**

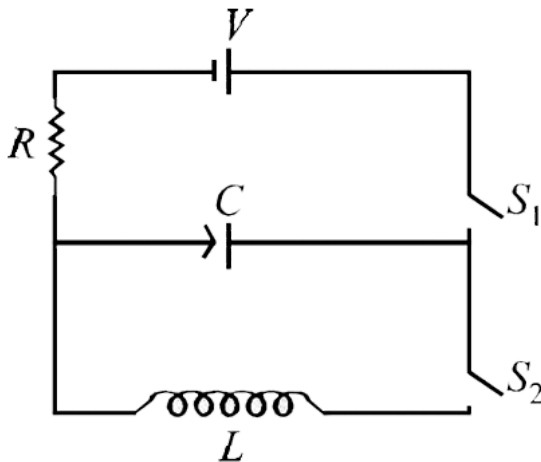2. In the given circuit the capacitor ( $C$ ) may be charged through resistance  $R$  by a battery  $V$  by closing switch ( $S_1$ ). Also when ( $S_1$ ) is open and ( $S_2$ ) is closed the capacitor is connected in series with inductor ( $L$ ).



When the capacitor gets charged completely, ( $S_1$ ) is opened and ( $S_2$ ) is closed, Then,

A. at  $t = 0$ , energy stored in the circuit is purely in the form of magnetic energy.

B. at any time  $t > 0$  current in the circuit is in the same direction.

C. at  $t > 0$ , there is no exchange of energy between the inductor and capacitor.

D. at any time  $t > 0$ , maximum instantaneous current in the circuit may


$$\text{be } V \sqrt{\frac{C}{L}} .$$

**Answer: D**



Watch Video Solution

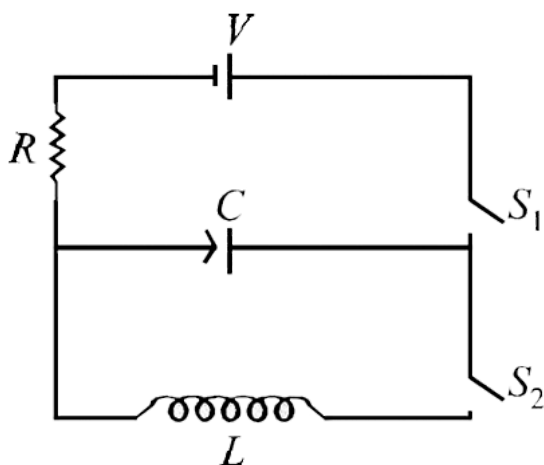3. In the given circuit the capacitor ( $C$ ) may be charged through resistance  $R$  by a battery  $V$  by closing switch ( $S_1$ ). Also when ( $S_1$ ) is open and ( $S_2$ ) is closed the capacitor is connected in series with inductor ( $L$ ).





Given that the total charge stored in the LC circuit is  $(Q_0)$ . for  $t \geq 0$ , the charge on the capacitor is

A.  $Q = Q_0 \cos \left( \frac{\pi}{2} + \frac{t}{\sqrt{LC}} \right)$

B.  $Q = Q_0 \cos \left( \frac{\pi}{2} - \frac{t}{\sqrt{LC}} \right)$

C.  $Q = -LC \frac{d^2Q}{dt^2}$

D.  $Q = -\frac{1}{\sqrt{LC}} \frac{d^2Q}{dt^2}$

**Answer: C**



**Watch Video Solution**

4. Modern train are based on maglev technology in which trains are magnetically levitated, which runs its *EDS* maglev system. There are coils on both sides of wheels. Due to motion of the train, current induces in the coil of track which levitate it. This is in accordance with Lenz's law. If train lowers down then due to Lenz's law, repulsive force increase due to which train gets uplifted and if it goes much higher then there is a net downward force due to gravity. The advantage of Maglev trains in that there is no friction between the train and

the track, thereby reducing power consumption and enabling the train to attain very high speeds. Disadvantage of Maglev train is that as it slows down, the electromagnetic forces decrease and it becomes difficult to keep it levitated and as it moves forward according to Lenz's law there is an electromagnetic drag force.

What is the advantage of this system?

A. No friction hence no power consumption

B. No electric power is zero

C. Graviatation force is zero

D. Electrostatic force draws the train

**Answer: A**



**Watch Video Solution**

5. Modern train are based on maglev technology in which trains are magntically levitated, which runs its *EDS* maglev system. There are coils on both sides of wheels. Due to motion of the train, current induces in the coil

of track which levitate it. This is in accordance with Lenz's law. If train lowers down then due to Lenz's law, repulsive force increase due to which train gets uplifted and if it goes much higher then there is a net downward force due to gravity. The advantage of Maglev trains is that there is no friction between the train and the track, thereby reducing power consumption and enabling the train to attain very high speeds. Disadvantage of Maglev train is that as it slows down, the electromagnetic forces decrease and it becomes difficult to keep it levitated and as it moves forward

according to Lenz's law there is an electromagnetic drag force.

What is the disadvantage of this system?

A. Train experiences upward force

according to Lenz's law

B. Friction force creates a drag on the train

C. Retardation

D. By Lenz's law, the train experiences a drag

**Answer: D**





Watch Video Solution

6. Modern train are based on maglev technology in which trains are magnetically levitated, which runs its *EDS* maglev system. There are coils on both sides of wheels. Due to motion of the train, current induces in the coil of track which levitate it. This is in accordance with Lenz's law. If train lowers down then due to Lenz's law, repulsive force increase due to which train gets uplifted and if it goes much higher then there is a net downward force due

to gravity. The advantage of Maglev trains is that there is no friction between the train and the track, thereby reducing power consumption and enabling the train to attain very high speeds. Disadvantage of Maglev train is that as it slows down, the electromagnetic forces decrease and it becomes difficult to keep it levitated and as it moves forward according to Lenz's law there is an electromagnetic drag force.

Which force causes the train to levitate up?

A. Electrostatic force



B. Time varying electric field

C. Magnetic force

D. Induced electric field

**Answer: C**



**Watch Video Solution**

7. A point charges  $Q$  is moving in a circular orbit of radius  $R$  in the  $x$ - $y$  plane with an angular velocity  $\omega$ . This can be considered as equivalent to a loop carrying a steady current

$\frac{Q\omega}{2\pi}$ . A uniform magnetic field along the positive z-axis is now switched on, which increases at a constant rate from 0 to B in one second. Assume that the radius of the orbit remains constant. The application of the magnetic field induces an emf in the orbit. The induced emf is defined as the work done by an induced electric field in moving a unit positive charge around a closed loop. It is known that, for an orbiting charge, the magnetic dipole moment is proportional to the angular momentum with a proportionality constant  $\lambda$ . The magnitude of the induced electric field in

the orbit at any instant of time during the time interval of the magnetic field change is

A.  $\frac{BR}{4}$

B.  $\frac{BR}{2}$

C.  $BR$

D.  $2BR$

**Answer: B**



**Watch Video Solution**

8. A point charges  $Q$  is moving in a circular orbit of radius  $R$  in the  $x$ - $y$  plane with an angular velocity  $\omega$ . This can be considered as equivalent to a loop carrying a steady current  $\frac{Q\omega}{2\pi}$ . A uniform magnetic field along the positive  $z$ -axis is now switched on, which increases at a constant rate from 0 to  $B$  in one second. Assume that the radius of the orbit remains constant. The application of the magnetic field induces an  $EMF$  in the orbit. The induced  $EMF$  is defined as the work done by an induced electric field in moving a

unit positive charge around a closed loop. It is known that, for an orbiting charge, the magnetic dipole moment is proportional to the angular momentum with a proportionality constant  $\lambda$ . The charge in the magnetic dipole moment associated with the orbit, at the end of the time interval of the magnetic field charge, is

A.  $\lambda BQR^2$

B.  $-\lambda \frac{BQR^2}{2}$

C.  $\lambda \frac{BQR^2}{2}$

$$D. -\lambda BQR^2$$

**Answer: B**




**Watch Video Solution**

## Archives (integer)

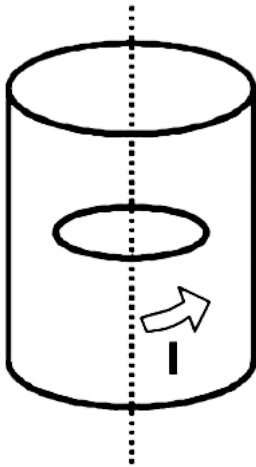1. A long circular tube of length  $10m$  and radius  $0.3m$  carries a current  $I$  along its curved surface as shown . A wire - loop of resistance  $0.005ohm$  and of radius  $0.1m$  is

placed inside the tube its axis coinciding with the axis of the tube . The current varies as  $I = I_0 \cos(300t)$  where  $I_0$  is constant. If the magnetic moment of the loop is  $N\mu_0 I_0 \sin(300t)$ , then 'N' is




**Watch Video Solution**

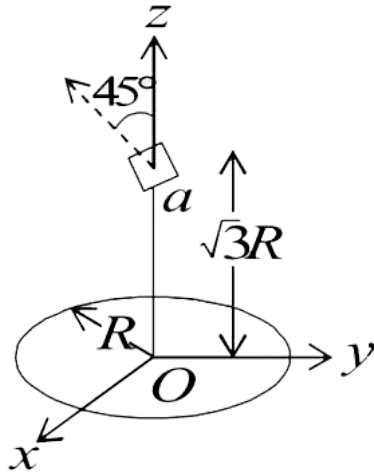2. A circular wire loop of radius  $R$  is placed in the  $x$ - $y$  plane centered at the origin  $O$ . A square loop of side  $a$  ( $a \ll R$ ) having two turns is placed with its centre at  $x = \sqrt{3}R$  along the  $x$ -axis of the circular wire loop, as shown in figure. The plane of the square loop makes an angle of  $45^\circ$  with respect to the  $z$ -axis. If the mutual inductance between the loops is given



bu  $\frac{\mu_0 a^2}{2^{p/2} R}$ , then the value of  $p$  is



[Watch Video Solution](#)

## Subjective Type

1. Two solenoids  $A$  and  $B$  spaced close to each other and sharing the same cylindrical axis

have 400 and 700 turns, respectively. A current of  $3.50\text{A}$  in coil  $A$  produced an average flux of  $300\mu\text{T} \cdot \text{m}^2$  through each turn of  $A$  and a flux of  $90.0\text{mT} \cdot \text{m}^2$  through each turn of  $B$ .

a. Calculate the mutual inductance of the two solenoids.

b. What is the self inductance of  $A$ ?

c. What emf is induced in  $B$  when the current in  $A$  increases at the rate of  $0.5\text{A} / \text{s}$ ?



**Watch Video Solution**

2. Solenoid  $S_1$  has  $N$  turns, radius  $R_1$  and length  $l$ . It is so long that its magnetic field is uniform nearly everywhere inside it and is nearly zero outside, Solenoid  $S_2$  has  $N_2$  turns, radius  $R_2 < R_1$ . and the same length as  $S_1$  It lies inside  $S_1$  with their axes parallel. (a) Assume  $S_1$  carries variable current  $i$ . Compute the mutual inductance characterizing the emf induced in  $S_2$ . (b) Now assume  $S_2$  carries current  $i$ . Compute the mutual inductance to which the emf in  $S_1$  is proportional. (c) State

how we results of parts (a) and (b) compare with each other.



[Watch Video Solution](#)

## Single correct Answer Type

1. A 2.00-H inductor carries a steady current of 0.500A. When the switch in the circuit is opened, the current is effectively zero after 10.0ms. What is the average induced emf in the inductor during this time interval?

A. 100V

B. 150V

C. 133V

D. 200V

**Answer: A**



**Watch Video Solution**

2. An emf of 25.0 mV is induced in a 500-turn coil when the current is changing is at the rate of 10.0A/s. What is the magnetic flux through

each turn of the coil at an instant when the current is 4.0A?

A.  $20\mu T \cdot m^2$

B.  $10\mu T \cdot m^2$

C.  $15\mu T \cdot m^2$

D.  $30\mu T \cdot m^2$

**Answer: A**



**Watch Video Solution**

3. The current in a coil changes from 3.50 A to 2.00 A in the same direction in 0.500s. If the average emf induced in the coil is 12.0mV. What is the inductance of the coil?

A. 2.00mH

B. 4.00mH

C. 3.00mH

D. 8.00mH

**Answer: B**



Watch Video Solution

4. A self-induced wmf in a solenoid of inductance  $L$  changes in time as  $\mathcal{E} = \epsilon_0 e^{-kt}$ . Assuming the charge is finite, find the total charge that passes a point in the wire of the solenoid.

A.  $\frac{\epsilon_0}{Lk^2}$

B.  $\frac{2\epsilon_0}{Lk^2}$

C.  $\frac{\epsilon_0}{2Lk^2}$

D.  $\frac{3\epsilon_0}{Lk^2}$



**Answer: A**



**Watch Video Solution**

5. Light of wavelength  $24000\text{\AA}$  is incident on a thin glass plate of refractive index 1.5 such that angle of refraction into plate is  $60^\circ$ . Calculate the thickness of plate which will make it appear dark by reflection?



**Watch Video Solution**

6. An emf 96.0mV is induced in the windings of a coil when the current in a nearby coil is increasing at the rate of 1.20A/s. The mutual inductance of the two coils is

A. 40mH

B. 20mH

C. 10mH

D. 80mH

**Answer: D**



Watch Video Solution

7. Two coils, held in fixed positions have a mutual inductance of  $100\mu\text{H}$ . what is the peak emf in one coil when the current in the other coil is  $10 \sin(1000t)$  where  $i$  is in amperes and  $t$  is in seconds?

A. 2.00V

B. 1.00V

C. 4.00V

D. 3.00V

**Answer: B**



**Watch Video Solution**

8. Two conducting circular loops of radii  $R_1$  and  $R_2$  are placed in the same plane with their centres coinciding. Find the mutual inductance between them assuming  $R_2 < R_1$ .

A.  $\frac{\mu_0 \pi r^2}{R}$

B.  $\frac{2\mu_0 \pi r^2}{R}$

C.  $\frac{\mu_0 \pi r^2}{2R}$

D.  $\frac{3\mu_0 \pi r^2}{3R}$

**Answer: C**



**Watch Video Solution**

9. A coil of *Cu* wire (radius  $r$ , self-inductance  $L$ ) is bent in two concentric turns each having radius  $\frac{r}{2}$ . The self-inductance now

A.  $2L$

B.  $L$

C.  $4L$

D.  $L/2$

**Answer: A**



**Watch Video Solution**

**10.** If in a coil rate of change of area is

$\frac{5 \text{ meter}^2}{\text{milli second}}$  and current become  $1 \text{ amp}$  from

$2 \text{ amp}$  in  $2 \times 10^{-3}$  sec. if magnetic field is 1

Tesla then self-inductance of the coil is

A.  $2H$

B.  $5H$

C.  $20H$

D.  $10H$


**Answer: D**



**Watch Video Solution**

**11.** The current through a  $4.6\text{ H}$  inductor is shown in the following graph. The induced emf during the time interval  $t = 5\text{ milli - sec}$  to

6 milli - sec will be

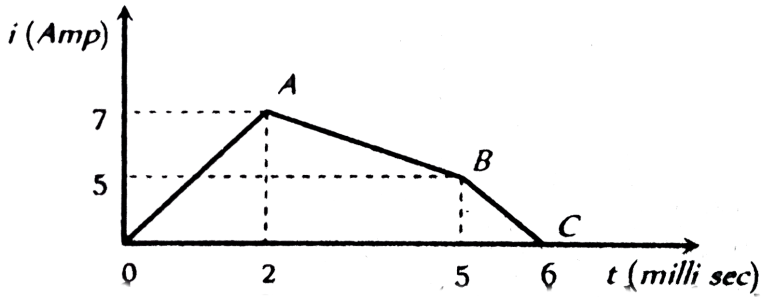

A.  $10^3 V$

B.  $-23 \times 10^3 V$

C.  $23 \times 10^3 V$

D. Zero

**Answer: C**



**Watch Video Solution**



12. An alternating current of frequency  $200\text{rad/sec}$  and peak value of  $1\text{A}$  as shown in the figure is applied to the primary of a transformer. If the coefficient of mutual induction between the primary and the secondary is  $1.5\text{H}$ , the voltage induced in the secondary will be

A.  $300\text{V}$

B.  $191\text{V}$

C.  $220\text{V}$


D. 471V

**Answer: B**



**Watch Video Solution**

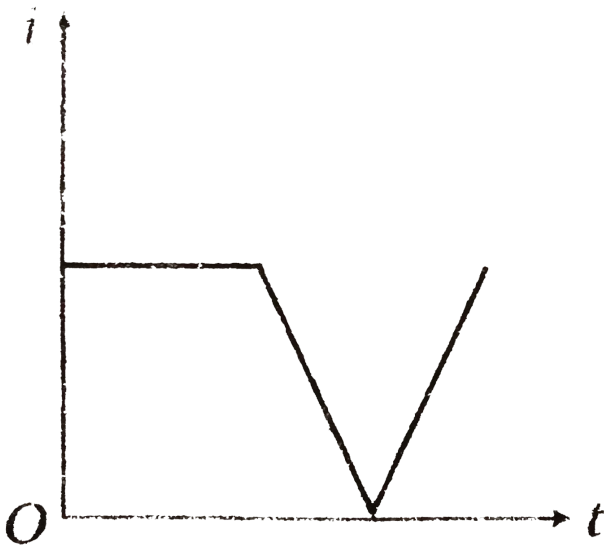**13.** The current  $i$  in an inducton coil varies with time  $t$  according to the graph shown in figure.



Which of the following graphs shows the induced emf ( $E$ ) in the coil with time?

A. 

B. 

C. 

D. 

**Answer: C**



**Watch Video Solution**

**14.** When a certain circuit consisting of a constant e.m.f.  $E$  an inductance  $L$  and a resistance  $R$  is closed, the current in it increases with time according to curve 1. After one parameter ( $E$ ,  $L$  or  $R$ ) is changed, the increase in current is closed second time. Which parameter was changed and in what

direction?



A. L is increased

B. L is decreased

C. R is increased


D. R is decreased

**Answer: A**



**Watch Video Solution**

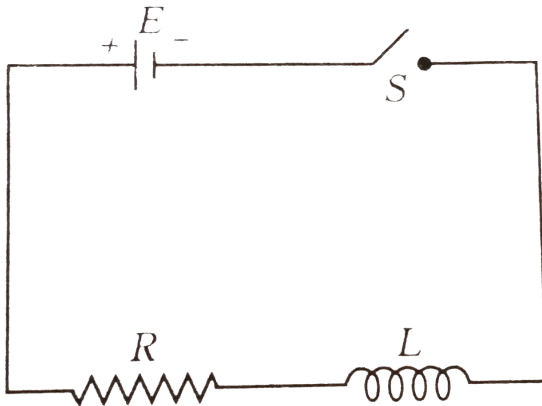15. Switch  $S$  of the circuit shown in figure is closed at  $t = 0$ .



If emf in  $L$  is  $e$  and  $i$  is the current flowing through the circuit at time  $t$ , which of the following graphs is correct?

A. 

B. 

C. 

D. 

**Answer: C**




**Watch Video Solution**

**16.** Light of wavelength  $12000\text{\AA}$  is incident on a thin glass plate of refractive index  $1$  such that angle of refraction into plate is  $60^\circ$ . Calculate the thickness of plate which will make it appear dark by reflection?



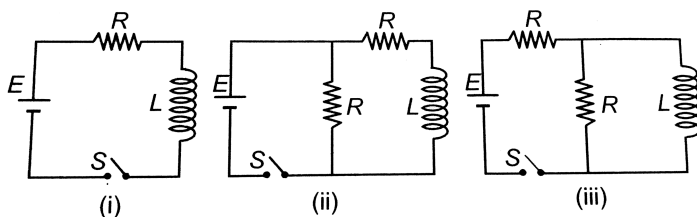17. In which of the following circuits is the current maximum just after the switch  $S$  is closed?



A. (i)

B. (ii)

C. (iii)



D. Both (ii) and (iii)

**Answer: B**

 [Watch Video Solution](#)

**18.** In an L-R circuit connected to a battery at which energy is stored in the inductor is plotted against time during the growth of current in the circuit. Which of the following best represents the resulting curve?

A. 

B. 

C. 

D. 

**Answer: A**



**Watch Video Solution**

**19.** In the circuit diagram shown,

$R = 10\omega$ ,  $L = 5mH$ ,  $E = 10\text{ V}$  and  $i = 1A$ .

The current is decreasing at the reate of

$10^3 \text{ A/S}$ . Then  $(V_A - V_B)$  at this instant is :



A.  $10V$

B.  $15V$

C.  $20V$

D.  $25V$

**Answer: B**




**Watch Video Solution**

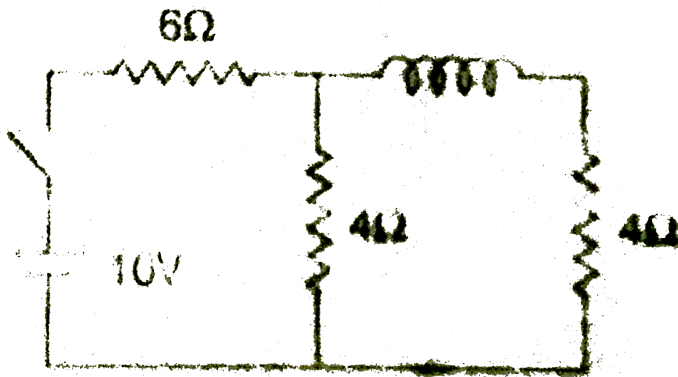20. In the given circuit find the ratio of  $i_1$  to  $i_2$ .

Where  $i_1$  is the initial (at  $t=0$ ) current, and  $i_2$  is

steady state (at  $t = \infty$ ) current the battery



A. 1.0

B. 0.8

C. 1.2

D. 1.5


**Answer: D**



**Watch Video Solution**

**21.** Consider the circuit shown in figure. The current through the battery a long time after

the switch  $S$  is closed is:

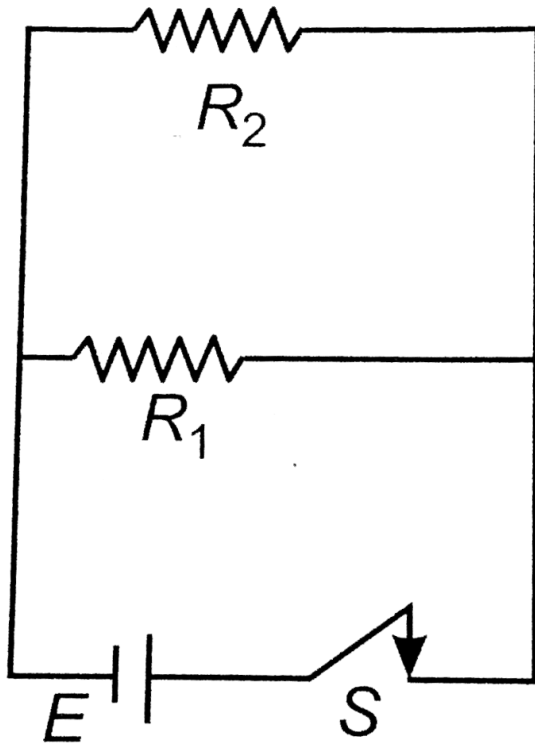

A.  $\frac{E}{R_1}$

B.  $\frac{E}{R_2}$

C.  $\frac{E}{R_1 + R_2}$

D.  $\frac{E(R_1 + R_2)}{R_1 R_2}$


**Answer: C**



**Watch Video Solution**

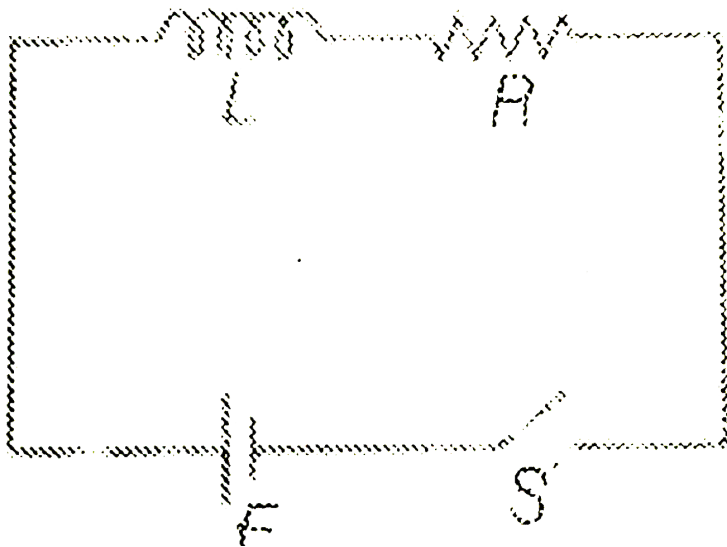**22.** In the circuit shown in figure switch S is closed at time  $t=0$ . The charge which passes

through the battery in one time constant is



- A.  $\frac{eR^2E}{L}$
- B.  $E\left(\frac{L}{R}\right)$
- C.  $\frac{EL}{eR^2}$
- D.  $\frac{eL}{ER}$



**Answer: A**



**Watch Video Solution**

## Multiple Correct Answer

1. The current in a 90mH inductor changes with time as  $i = 1.0t^2 - 6t$ , where  $i$  is in amperes and  $t$  is in seconds.

A. the magnitude of the induced emf at

$t=4.0s$  is 180 mV

B. the emf zero at time  $t=3.0\text{s}$

C. the magnitude of the induced emf at

$t=4.0\text{s}$  is  $360\text{ mV}$

D. the emf zero at time  $t=4.0\text{s}$

**Answer: A:B**



**Watch Video Solution**

2. A  $1 - k\Omega$  resistor is connected in series with a  $10 - mH$  inductor, a  $30V$  battery and an open switch. At time  $t = 0$ , the switch is

suddenly closed.

a. What is the maximum current in this circuit and when does it occur?

b. What are the voltage drops across the inductor and across the resistor  $20\mu s$  after the switch is closed?

c. On a single set of axes, sketch the voltage across the resistor and the voltage across the inductor as functions of time. Also, sketch a graph of the current in the circuit as a function of time.

- A. the power being supplied by the battery  
is  $20.0W$
- B. the power being delivered to the  
resistor is  $20.0W$
- C. the power being delivered to the inductor  
zero
- D. the energy stored in the magnetic field  
of the inductor is  $20.0J$

**Answer: A**



**Watch Video Solution**

3. The switch in figure 1 is connected to position a for a long time interval. At  $t = 0$ , the switch is thrown to position b. After this time, what are



A. the frequency of oscillation of the LC circuit

B. the maximum charge that appears on the capacitor

C. the maximum current in the inductor

D. the total energy the circuit possesses at

$$t = 3.00 \text{ s}$$



**Answer: A**



**Watch Video Solution**

**Comprehension Type**

1. A solenoid of radius 2.50cm has 400turns and a length of 20.0cm. The inductance (L) of this solenoid is \_\_\_\_\_.

A. 4mH

B. 5mH

C. 3mH

D. 2mH

**Answer: D**



**Watch Video Solution**

2. A solenoid of radius 2.50cm has 400turns and a length of 20.0cm. The current in the coil is changing with time such that an emf of  $75 \times 10^{-6}$  is produced.

The rate of change of current in the solenoid is

A. 38.0mA/s

B. 19.0mA/s

C. 21.0mA/s

D. 50.0mA/s



**Answer: A**



**Watch Video Solution**

3. A technician wraps wire around a tube of length  $4\pi^2$  cm having a diameter of 8.00cm. When the windings are evenly spread over the full length of the tube, the result is a solenoid containing 1000turns of wire. If the current in this solonoid increases at the rate of 4.00A/s. the inductance of this solenoid is

A. 32mH

B. 16mH

C. 48mH

D. 8mH

**Answer: B**



**Watch Video Solution**

4. A technician wraps wire around a tube of length  $4\pi^2$  cm having a diameter of 8.00cm. When the windings are evenly spread over the

full length of the tube, the result is a solenoid containing 1000 turns of wire. If the current in this solenoid increases at the rate of  $4.00\text{ A/s}$  the self-induced emf in the solenoid is

A.  $32\text{ mV}$

B.  $16\text{ mV}$

C.  $64\text{ mV}$

D.  $24\text{ mV}$

**Answer: C**



**Watch Video Solution**

5. Consider the circuit shown in figure.



When the switch is in position a, for what value of  $r$  will the circuit have a time constant of  $10\mu s$ ?

A.  $2.0k\Omega$

B.  $2.5k\Omega$

C.  $1.0k\Omega$

D. none of these

**Answer: A**



**Watch Video Solution**

6. Light of wavelength  $3000\text{\AA}$  is incident on a thin glass plate of refractive index  $n_1$  such that angle of refraction into plate is  $60^\circ$ . Calculate the thickness of plate which will make it appear dark by reflection?



**Watch Video Solution**

7. A circuit consists of a coil, a switch and a battery, all in series. The internal resistance of the battery is negligible compared with that of the coil. The switch is originally open. It is thrown closed, after a time interval  $\Delta t$ . The current in the circuit reaches 80.0% of its final value. The switch then remains closed for a time interval much longer than  $\Delta t$ . The wires connected to the terminals of the battery are then short circuited with another wire and removed from the battery, so that the current is uninterrupted.

At an instant that is a time interval  $\Delta t$ . After the short circuit, the current is what percentage of its maximum value? a)20% b) 8% c) 4% d)10 %

A. 20.0 %

B. 8.0 %

C. 4.0 %

D. 10.0 %

**Answer: A**



**Watch Video Solution**

8. what is the expression of work done for isobaric process?



[Watch Video Solution](#)

## Concept Based

1. Light is incident on a glass plate of refractive index 3.0 such that angle of refraction is  $60^\circ$ . Dark band is observed corresponding to the wavelength of  $12000 \text{ \AA}$ . If the thickness of



glass plate is  $1.2 \times 10^{-3}$  mm. Calculate the order of the interference band for reflected system.



[Watch Video Solution](#)

2. After switch is closed in the LC circuit shown in the figure, the charge on the capacitor is sometimes zero, but at such instants the current in the circuit is not zero. How is this behaviour possible ?





[Watch Video Solution](#)

3. Discuss the similarities between the energy stored in the electric field of charged capacitor and the energy stored in the magnetic field of a current-carrying coil.



[Watch Video Solution](#)

4. In the circuit of figure, the battery emf is  $\varepsilon$  the resistance is  $R$  and the capacitance is  $C$ . The switch  $S$  is closed for a long time interval,

and zero potential difference is measured across the capacitor



After the switch is opened, the potential difference across the capacitor reaches a maximum value of  $\Delta V$ . What is the value of the inductance?

A.  $\frac{C(\Delta V)^2}{2\epsilon^2}$

B.  $\frac{C(\Delta V)^2}{\epsilon^2}$

C.  $\frac{2C(\Delta V)^2}{\epsilon^2}$

D.  $\frac{C(\Delta V)^2}{4\epsilon^2}$

**Answer: A**



**Watch Video Solution**

5. A  $1.00\mu F$  capacitor is charged by a  $40.0V$  power supply. The fully charged capacitor is then discharged through a  $10.0mH$  inductor. Find the maximum current in the resulting oscillations.

A.  $400mA$

B.  $800mA$

C.  $600\text{mA}$

D.  $150\text{mA}$

**Answer: A**



**Watch Video Solution**

6. The frequency of oscillation of current in the inductor is



A.  $\frac{1}{3\sqrt{LC}}$

B.  $\frac{1}{6\pi\sqrt{LC}}$

C.  $\frac{1}{\sqrt{LC}}$

D.  $\frac{1}{2\pi\sqrt{LC}}$

**Answer: A**



**Watch Video Solution**

7. Light of wavelength  $24000\text{\AA}$  is incident on a thin glass plate of refractive index 1 such that angle of refraction into plate is  $60^\circ$ . Calculate

the thickness of plate which will make it appear dark by reflection?



[Watch Video Solution](#)

8. Two waves of intensity  $I$  and  $9I$  are superimposed in such a way that resultant Intensity is  $7I$ . Find the phase difference between them ?



[Watch Video Solution](#)