



PHYSICS

BOOKS - CHETANA PUBLICATION

AC CIRCUITS

Example

1. Which are the two types of supplies of electricity?



Watch Video Solution

2. Define DC supply of electricity



[Watch Video Solution](#)

3. Define AC supply of electricity .



[Watch Video Solution](#)

4. Name a device which converts AC to DC.



[Watch Video Solution](#)

5. Name some devices which use DC supply of electricity.



[Watch Video Solution](#)

6. Name domestic appliances which run on AC supply of electricity.



[Watch Video Solution](#)

7. State the expression for emf of an AC source.



[Watch Video Solution](#)

8. State the expression for current of AC source.



[Watch Video Solution](#)

9. What is peak value of AC.



[Watch Video Solution](#)

10. What is average or mean value of AC .



[Watch Video Solution](#)

11. What is the average value of full cycle of AC? Why.



[Watch Video Solution](#)

12. What is the relation between peak value and average value of AC .



Watch Video Solution

13. What does an ammeter or voltmeter measure? Average value or peak value.



Watch Video Solution

14. Why can moving coil instruments not be used to measure alternating currents voltages



Watch Video Solution

15. Which is more dangerous, AC or DC?



Watch Video Solution

16. An alternating current measuring instrument have linear or non-linear

scale.Why?



[Watch Video Solution](#)

17. What is the $v_0 < a \geq$ / *equency* cycle of AC supply India.



[Watch Video Solution](#)

18. What is peak value and r.m.s. value of alternating current?



[Watch Video Solution](#)

19. What is peak value and r.m.s. value of alternating e.m.f.in the electric circuit?



Watch Video Solution

20. Derive expression for heat produced by the AC source in time t .



Watch Video Solution

21. An alternating voltage is given by $e=6 \sin 314t$. Find:- the peak value



[Watch Video Solution](#)

22. An alternating voltage is given by $e=6 \sin 314t$. Find:- frequency



[Watch Video Solution](#)

23. An alternating voltage is given by $e=6 \sin 314t$. Find:- time period and



Watch Video Solution

24. An alternating voltage is given by $e=6 \sin 314t$. Find:-instantaneous value at time $t=2\text{ms}$



Watch Video Solution

25. An alternating voltage given by $e=140 \sin 3142t$ is connected across a pure resistor of 50Ω . Find:- the frequency of the source



[Watch Video Solution](#)

26. An alternating voltage given by $e=140 \sin 3142t$ is connected across a pure resistor of 50Ω . Find:- the rms current through the resistor.



[Watch Video Solution](#)

27. An alternating e.m.f. is given by $100 \sin 100\pi t$ o a pure resistance of 50Ω . calculate:- peak value of e.m.f



Watch Video Solution

28. An alternating e.m.f. is given by $100 \sin 100\pi t$ to a pure resistance of 50Ω . calculate:- frequency



Watch Video Solution

29. An alternating e.m.f. is given by $100 \sin 100\pi t$ to a pure resistance of 50Ω . calculate:-
r.m.s current through the circuit.



[Watch Video Solution](#)

30. The r.m.s. value of current is $(2)\sqrt{2}$
A. Calculate its peak value of current.



[Watch Video Solution](#)

31. An e.m.f. of peak value 100 V and frequency 60 r.p.s is supplied to the bulb. Write down the equation of supplied voltage.



Watch Video Solution

32. The A.C. current passing through 60Ω resistor causes a power loss of 6000 W. Find the r.m.s current and its maximum value .
What are maximum value and r.m.s value of

D.C? What is the value of D.C.current that produces same power loss as the A.C. current?



[Watch Video Solution](#)

33. If the effective current in a 50 cycle AC circuit is 5A, what is the peak value of current?

What is the current $1/600$ sec.after it was Zero?



[Watch Video Solution](#)

34. A light bulb is rated 100 W for 220V AC supply of 50 Hz. Calculate:- resistance of the bulb.



Watch Video Solution

35. A light bulb is rated 100 W for 220V AC supply of 50 Hz. Calculate:- the rms current through the bulb.



Watch Video Solution

36. What is a phasor ?What is phasor diagram?



Watch Video Solution

37. How is the phasor of alternating emf or current represented ?



Watch Video Solution

38. Explain the theory of an A.C.circuit with resistor. Draw the phasor diagram for it.





[Watch Video Solution](#)

39. An alternating e.m.f. is applied to a circuit containing resistance. Discuss the behaviour of current in the circuit. Also discuss the phase diagram for it.



[Watch Video Solution](#)

40. Explain the theory of A.C. circuit with pure inductor. Draw the phasor diagram for voltage and current in the circuit.



[Watch Video Solution](#)

41. Define inductive reactance and state its SI unit.



[Watch Video Solution](#)

42. How does inductive reactance vary with frequency f and inductance L ?



[Watch Video Solution](#)

43. Show graphically the variation of X_L with frequency f .



Watch Video Solution

44. What is SI unit and dimension of X_L .



Watch Video Solution

45. Why does a pure inductor pass DC and block AC of high frequency





[Watch Video Solution](#)

46. An inductor of inductance 200 mH is connected to an AC source of peak emf 210 V and frequency 50 Hz . Calculate the peak current. What is the instantaneous voltage of the source when the current is at its peak value?



[Watch Video Solution](#)

47. An AC circuit consists of only an inductor of inductance 2 H. If the current is represented by a sine wave of amplitude 0.25 A and frequency 60Hz, calculate the effective potential difference across the inductor



Watch Video Solution

48. Alternating emf of $e=220 \sin 100 \pi t$ is applied to a circuit containing an inductance of $\left(\frac{1}{\pi}\right)$ henry. Write an equation for

instantaneous current through the circuit.

What will be the reading of the AC galvanometer connected in the circuit?



[Watch Video Solution](#)

49. Find the reactance of a coil of inductance 100mH at a frequency 50 Hz and 1000 Hz .



[Watch Video Solution](#)

50. An inductor of 500 mH is connected across a 100 V, 50 Hz supply. Calculate its reactance.



Watch Video Solution

51. Explain the theory of an A.C. circuit in a purely capacitive circuit. Draw the Phasor diagram for voltage and current in it



Watch Video Solution

52. Define capacitive reactance X_C .



[Watch Video Solution](#)

53. How does capacitive reactance vary with frequency and capacitance?



[Watch Video Solution](#)

54. A device Y is connected across an AC source of emf $e = e_0 \sin \omega t$. the current through

y is given as $i = i_o \sin\left(\omega t + \left(\frac{\pi}{2}\right)\right)$:-Identify the device Y and write the expression for its reactance.



[Watch Video Solution](#)

55. A device Y is connected across an AC source of emf $e = e_o \sin \omega t$. the current through y is given as $i = i_o \sin\left(\omega t + \left(\frac{\pi}{2}\right)\right)$:-Draw graphs showing variation of emf and current with time over one cycle of AC for Y .



[Watch Video Solution](#)

56. A device Y is connected across an AC source of emf $e = e_0 \sin \omega t$. The current through y is given as $i = i_0 \sin\left(\omega t + \left(\frac{\pi}{2}\right)\right)$: -How does the reactance of the device Y vary with the frequency of the AC? Show graphically.



Watch Video Solution

57. A device Y is connected across an AC source of emf $e = e_0 \sin \omega t$. The current through y is

given as $i = i_o \sin\left(\omega t + \left(\frac{\pi}{2}\right)\right)$:-Draw the phasor diagram for the device Y.



[Watch Video Solution](#)

58. Draw the graph of capacitive reactance against frequency of a.c. source. Hence discuss its conclusion.



[Watch Video Solution](#)

59. State SI unit and dimensions of X_c .



[Watch Video Solution](#)

60. A capacitor of $2\mu F$ is connected to an AC source of emf $e = 250 \sin 100\pi t$. Write an equation for instantaneous current through the circuit and give reading of AC ammeter connected in the circuit.



[Watch Video Solution](#)

61. A capacitor draws 20 A current at 240 V, 50 Hz. Find the capacitive reactance and the capacitance of the capacitor.



Watch Video Solution

62. A $100\mu F$ capacitor is charged with a 50 V source supply. Then source supply is removed and the capacitor is connected across an inductance of reactance 10Ω , as a result of which 5A current flows through the

inductance. Calculate the value of the inductance.



[Watch Video Solution](#)

63. A $15.0\mu F$ capacitor is connected to a 220 V 50 Hz source. Find the capacitive reactance and the current (rms and peak) in the circuit. If the frequency is doubled, what will happen to the capacitive reactance and the current?



[Watch Video Solution](#)

64. Obtain an expression for impedance of resistor, pure inductor and capacitor connected in series across alternating e.m.f. State formula for phase difference.



Watch Video Solution

65. Define impedance. State its SI unit.



Watch Video Solution

66. State SI unit and dimensions of impedance.



Watch Video Solution

67. What do you mean by reactance and impedance?



Watch Video Solution

68. Define admittance, State its SI unit.



Watch Video Solution

69. What happens in LCR circuit when $X_L = X_C$
 $X_L > X_C$, X_L



[Watch Video Solution](#)

70. Draw and explain impedance triangle.



[Watch Video Solution](#)

71. A 100 mH inductor, a $25\mu F$ capacitor and a 15Ω resistor is connected in series to a 120 V, 50 Hz. AC source. Calculate:-impedance of the circuit at resonance



[Watch Video Solution](#)

72. A 100 mH inductor, a 25 pF capacitor and a 15 Ω resistor is connected in series to a 120 V, 50 Hz. AC source. Calculate:-current at resonance





[Watch Video Solution](#)

73. A 100 mH inductor, a 25 pF capacitor and a 15 Ω resistor is connected in series to a 120 V, 50 Hz AC source. Calculate: - Resonant frequency



[Watch Video Solution](#)

74. A coil of 0.01 H inductance and 1Ω resistance is connected to 200 V, 50 Hz AC supply. Find the impedance of the circuit and

time lag between maximum alternating voltage and current.



[Watch Video Solution](#)

75. In LCR circuit, inductance $L = \frac{2}{\pi} H$, capacitance $C = \frac{10}{\pi} F$ and resistance 10 Omega are connected in series to A.C. source of frequency = 50 Hz. Find:-inductive reactance



[Watch Video Solution](#)

76. In LCR circuit, inductance $L = \frac{2}{\pi} H$, capacitance $C = \frac{10}{\pi} F$ and resistance 10Ω are connected in series to A.C. source of frequency = 50 Hz. Find:-capacitive reactance



Watch Video Solution

77. In LCR circuit, inductance $L = \frac{2}{\pi} H$, capacitance $C = \frac{10}{\pi} F$ and resistance 10Ω are connected in series to A.C. source

of frequency = 50 Hz. Find:-impedance of the circuit.



[Watch Video Solution](#)

78. When 100 V D.C. is applied across a coil, a current of 1A flows through it. When 100 V A.C. of frequency 50 Hz is applied to the same coil only 0.5 A current flows through it. Calculate resistance, and self inductance of the coil



[Watch Video Solution](#)

79. A capacitor of $20\mu F$ is connected in series with a 25Ω resistance to peak e.m.f. 240 V, 50 Hz A.C. Calculate:-the capacitive reactance of the coil



[Watch Video Solution](#)

80. A capacitor of $20\mu F$ is connected in series with a 25Ω resistance to peak e.m.f. 240 V, 50 Hz A.C. Calculate:-impedance of the circuit



[Watch Video Solution](#)

81. A 100Ω resistor is connected to a 220 V, 50 Hz supply:-What is the rms value of current in the circuit?



[Watch Video Solution](#)

82. An alternating e.m.f. of peak value 110 V and frequency 50 Hz is connected across LCR series circuit with $R = 100\Omega$, $L = 10 \text{ mH}$, $C = 25\mu F$. Calculate the inductive reactance, capacitive reactance and impedance.





[Watch Video Solution](#)

83. A capacitor of $25\mu F$, inductor of 0.1 H and resistor of resistance 25Ω are connected in series with an A.C. source of e.m.f., $e = 310 \sin(314 t)$ volt. What is the :-reactance



[Watch Video Solution](#)

84. A capacitor of $25\mu F$, inductor of 0.1 H and resistor of resistance 25Ω are connected in series with an A.C. source of e.m.f., $e = 310 \sin$

(314 t) volt. What is the:- impedance and current of the circuit



[Watch Video Solution](#)

85. A capacitor of $25\mu F$, inductor of 0.1 H and resistor of resistance 25Ω are connected in series with an A.C. source of e.m.f., $e = 310 \sin(314 t)$ volt. What is the:-phase angle between current and applied e.m.f.



[Watch Video Solution](#)

86. A capacitor of $25\mu F$, inductor of 0.1 H and resistor of resistance 25Ω are connected in series with an A.C. source of e.m.f., $e = 310 \sin(314 t)$ volt. What is the :-reactance



Watch Video Solution

87. An A.C. supply of frequency 50 Hz is supplied to a series combination of $25\mu F$ condenser, 0.1 H inductor and 24Ω resistor. Calculate inductive and capacitive reactance. Also find impedance of the circuit.



[Watch Video Solution](#)

88. A capacitor of $100\mu F$, a coil of resistance 50Ω and an inductance 0.5 H are connected in series with a 110 V - 50 Hz source. Calculate the rms value of current in the circuit.



[Watch Video Solution](#)

89. A $10\mu F$ capacitor is charged to a 25 volt of potential. The battery is disconnected and a

pure 100 mH coil is connected across the capacitor so that LC oscillations are set up. Calculate the maximum current in the coil.



[Watch Video Solution](#)

90. An electric lamp is connected in series with a capacitor and an AC source is glowing with a certain brightness. How does the brightness of the lamp change on increasing the capacitance?



[Watch Video Solution](#)

91. The total impedance of a circuit decreases when a capacitor is added in series with L and R. Explain why?



Watch Video Solution

92. For very high frequency AC supply, a capacitor behaves like a pure conductor. Why?



Watch Video Solution

93. A $25\mu F$ capacitor, a 0.10 H inductor and a 25Ω resistor are connected in series with a AC source whose emf is given by $e = 310 \sin 314 t$ (volt). What is the frequency, reactance, impedance, current and phase angle of the circuit?



Watch Video Solution

94. Derive an expression for the average power associated with resistance in AC circuit.



Watch Video Solution

95. A 100Ω resistor is connected to a 220 V, 50 Hz supply:-What is the rms value of current in the circuit?



Watch Video Solution

96. A 100Ω resistor is connected to a 220 V, 50 Hz supply:- What is the net power consumed over a full cycle?



Watch Video Solution

97. Show that average power over a complete cycle of AC through an ideal inductor is zero.



Watch Video Solution

98. Show that the average power supplied to an ideal capacitor by the source over a complete cycle is zero.



Watch Video Solution

99. Find the capacity of a capacitor which when put in series with a 10Ω resistor makes the power factor equal to 0.5. Assume an 80 V -100 Hz AC supply.



[Watch Video Solution](#)

100. Obtain an expression for power consumed in a LCR series circuit. Hence obtain an expression for power factor of the circuit.



[Watch Video Solution](#)

101. Define power factor



Watch Video Solution

102. What is wattless current?



Watch Video Solution

103. In a series LR circuit $X_L = R$ and power factor of the circuit is P_1 . When capacitor with capacitance C such that $X_L = X_C$ is put in

series the power factor becomes P_2 . Calculate

$$P_1 / P_2.$$



[Watch Video Solution](#)

104. A sinusoidal voltage of peak value 283V and frequency 50 Hz is applied to a series LCR circuit in which $R = 3\Omega$, $L = 25.48 \text{ mH}$ and $C = 796\mu\text{f}$. Find:-The impedance of the circuit



[Watch Video Solution](#)

105. A sinusoidal voltage of peak value 283V and frequency 50 Hz is applied to a series LCR circuit in which $R = 3\Omega$, $L = 25.48 \text{ mH}$ and $C = 796\mu\text{f}$. Find:-The phase difference between the voltage across source and the currents



Watch Video Solution

106. A sinusoidal voltage of peak value 283V and frequency 50 Hz is applied to a series LCR

circuit in which $R = 3\Omega$, $L = 25.48 \text{ mH}$ and $C = 796\mu\text{f}$. Find:-The power factor



[Watch Video Solution](#)

107. A sinusoidal voltage of peak value 283V and frequency 50 Hz is applied to a series LCR circuit in which $R = 3\Omega$, $L = 25.48 \text{ mH}$ and $C = 796\mu\text{f}$. Find:-The power dissipated in the surface.



[Watch Video Solution](#)

108. An alternating voltage of 240V, 50 Hz is applied to 20H inductance coil and resistance 300Ω . Calculate, inductive reactance power factor and power absorbed.



Watch Video Solution

109. How oscillations are produced using an inductor and a capacitor?



Watch Video Solution

110. Why are LC oscillations usually damped?



Watch Video Solution

111. Calculate the value of capacity in picofarad, which will make 101.4 micro henry inductance to oscillate with frequency of one megahertz.



Watch Video Solution

112. What is natural frequency of oscillation of a system?



Watch Video Solution

113. What is electric resonance?



Watch Video Solution

114. What is resonant circuit?



Watch Video Solution

115. Which are the different types of electric resonance circuits?



Watch Video Solution

116. Explain series resonance in LCR circuit.



Watch Video Solution

117. Define series resonant frequency.



Watch Video Solution

118. State the applications of series resonant circuit.



Watch Video Solution

119. State the condition for series resonance. Obtain an expression for resonant frequency.



Watch Video Solution

120. Draw series resonance curve and discuss its importance.



Watch Video Solution

121. State the characteristics of series resonance circuit.



Watch Video Solution

122. What are acceptor circuits?



[Watch Video Solution](#)

123. What is parallel resonance circuit? Obtain condition for parallel resonance.



[Watch Video Solution](#)

124. Define resonance frequency in parallel resonance. Obtain an expression for resonance frequency in parallel LC circuit. Also

discuss the variation of current with frequency.



[Watch Video Solution](#)

125. What are rejector circuits?



[Watch Video Solution](#)

126. State the characteristics of parallel resonance circuit



[Watch Video Solution](#)

127. An A.C. voltage is applied to parallel combination of inductance 2 mH and a capacitor $3.2\mu F$. Calculate the resonant frequency.



Watch Video Solution

128. A series LCR circuit has capacitor of $0.2\mu F$ and inductor of 8 mH. Find its resonant frequency.



[Watch Video Solution](#)

129. In series LCR circuit, the inductor of inductance . 100 mH, a resistor of 10Ω , and a variable. capacitor are connected across 20 V, 50 Hz supply. At what capacitance will resonance occur? Find the corresponding current.



[Watch Video Solution](#)

130. An A.C. voltage of r.m.s. value 1 V is applied to a parallel combination of inductor $L = 10$ mH, and capacitor $4\mu F$. Calculate the resonant frequency and current through each branch and resonance.



Watch Video Solution

131. A coil of resistance 5μ and self inductance 0.2 H is connected in series with a variable capacitor across 30 V, 50 Hz supply. At what

value of capacitor resonance will occur? Find the corresponding current.



[Watch Video Solution](#)

132. In a resonant circuit, inductance of the coil is 3 mH and resonant frequency is 1000 kHz. What is the value of capacitor in the circuit?



[Watch Video Solution](#)

133. An A.C. circuit consists of a resistor of 5Ω and inductor of 10 mH connected in series with 50 V, 50 Hz supply. What capacitance should be connected in series with the circuit to obtain maximum current? What will be the maximum current?



Watch Video Solution

134. In LCR series combination $R = 10\Omega$, $L = 1$ mH, $C = 2\mu F$. Determine :- resonant frequency,





[Watch Video Solution](#)

135. In LCR series combination $R = 10\Omega$, $L = 1$ mH, $C = 2\mu F$. Determine :- the current in the circuit when an alternating voltage of 10 mV operating at the resonant frequency is applied to the series combination.



[Watch Video Solution](#)

136. An A.C. circuit consists of inductor of inductance 125 mH connected in parallel with

a capacitor of capacity $50\mu F$. Determine the resonant frequency.



[Watch Video Solution](#)

137. The LCR series circuit has an inductance 50 mH and a capacitor $0.1 \times 10^{-6} F$ and a resistance 200Ω . Find the impedance at resonance and resonant frequency



[Watch Video Solution](#)

138. What is half power frequency in series LCR circuit.



Watch Video Solution

139. Define Q factor of series resonant circuit and state formula



Watch Video Solution

140. Draw the sharpness resonance curve of series LCR circuit to explain the Q-factor.



Watch Video Solution

141. State the units and dimensions of Q factor



Watch Video Solution

142. What happens if Q factor of LCR circuit is large.



[Watch Video Solution](#)

143. What is a choke coil?



[Watch Video Solution](#)

144. Where is a choke coil used ?



[Watch Video Solution](#)

145. Write a short note on choke coil.



[Watch Video Solution](#)

146. Distinguish between Resistance and Reactance.



[Watch Video Solution](#)

147. Differences between series and parallel resonance.



[Watch Video Solution](#)

Exercise

1. A LCR series circuit has the impedance of 240 ohm. If $R = 120\Omega$, find the power factor of the circuit.



[Watch Video Solution](#)

2. In LCR series circuit a voltmeter is connected in turn across the ends of R, L and C, and the voltages are found to be 192 V, 200V and 56 V

respectively. Find the phase angle and hence the power factor of the circuit



[Watch Video Solution](#)

3. What inductive reactance will $a \frac{1}{\pi}$ H inductor have at the 50 Hz frequency?



[Watch Video Solution](#)

4. What is the period of a 50 Hz voltage wave?



[Watch Video Solution](#)

5. An inductor draws 5A of current at 230 V, 50 Hz. Find the value of inductive reactance and the inductance.



[Watch Video Solution](#)

6. A capacitor draws 10 A of current at 230 V, 50 Hz. Find the capacitive reactance and the capacitance of the capacitor.



[Watch Video Solution](#)

7. A circuit connected to a 200 V supply takes a current of 4.8 A. If the angle of lag is 25° , find the power absorbed.



[Watch Video Solution](#)

8. A voltage $e = 50\sqrt{2}\sin 314.0 t$ volt is applied across a 10 ohm resistor. Find:- peak value of emf



[Watch Video Solution](#)

9. A voltage $e = 50\sqrt{2}\sin 314.0 t$ volt is applied across a 10 ohm resistor. Find:-frequency



[Watch Video Solution](#)

10. A voltage $e = 50\sqrt{2}\sin 314.0 t$ volt is applied across a 10 ohm resistor. Find:-rms current (i.e. an ac ammeter reading) through the circuit.



[Watch Video Solution](#)

11. A 2H inductor of negligible resistance is connected to a 50 V, 50 Hz power line:- What is the inductive reactance?



Watch Video Solution

12. A 2H inductor of negligible resistance is connected to a 50 V, 50 Hz power line:- What is the current in the coil?



Watch Video Solution

13. A peak value of alternating voltage is 494.97 V. Find reading on voltmeter used to measure it?



Watch Video Solution

14. In a purely inductive ac circuit $L = 25 \text{ mH}$ and peak voltage of ac supply is 150 V. Find inductive reactance and maximum current if the frequency is 50 Hz.



Watch Video Solution

15. An inductor has a reactance of 125.6Ω at 200 Hz. What is the inductance?



Watch Video Solution

16. An alternating e.m.f. given by $e = 50 \sin 314t$ is applied to a pure resistance of 100 ohm. Find:-peak value of e.m.f.



Watch Video Solution

17. An alternating e.m.f. given by $e = 50 \sin 314t$ is applied to a pure resistance of 100 ohm.

Find:-frequency



Watch Video Solution

18. An alternating e.m.f. given by $e = 50 \sin 314t$ is applied to a pure resistance of 100 ohm.

Find:-r.m.s. current through the circuit



Watch Video Solution

19. An alternating e.m.f. given by $e = 50 \sin 314t$ is applied to a pure resistance of 100 ohm. Find:- power dissipated in the circuit.



Watch Video Solution

20. A 60 watt lamp is connected to an alternating e.m.f. of peak value 230 volt. Find the peak value of current flowing through the lamp.



Watch Video Solution

21. When an a.c. current passes through a 14Ω resistor, the power loss is 224 W. Find the r.m.s. values of current and voltage. Also find the maximum values of current and voltage. Find the steady value of current which when passed through this resistor will produce the same power loss as the a.c. current.



Watch Video Solution

22. Calculate the reactance of a 2H inductance in an a.c. circuit of frequency 50 Hz.



Watch Video Solution

23. Calculate the reactance of a $1\mu F$ capacitance in an a.c. circuit of frequency 50 Hz.



Watch Video Solution

24. A coil has an inductance of 0.5H. Calculate:-
its inductive reactance when connected to 240
V (peak), 50 Hz A.C.



Watch Video Solution

25. A coil has an inductance of 0.5H. Calculate:-
its impedance if the resistance of the circuit is
50 Ω and



Watch Video Solution

26. A coil has an inductance of 0.5H and a resistance of 100 ohm are connected in series to 240v , 50 Hz supply. Calculate:- the maximum current in the circuit.



Watch Video Solution

27. An a.c. e.m.f. of peak value 240 V and frequency 50 Hz is connected to a circuit with $R = 12\Omega$, $L = 2.5\text{ H}$ and a capacitor all in series. Find the capacitance for the current in the

circuit to be maximum. Find the maximum current.



[Watch Video Solution](#)

28. Find the current in a circuit consisting of a coil and a capacitor in series with an A.C. source of 110 V (r.m.s.), 60 Hz. The inductance of the coil is 0.80 H and its resistance is 50Ω . The capacitance of the capacitor is $8\mu F$.



[Watch Video Solution](#)

29. In a series LCR circuit, $R = 20\Omega$, $C = 10\mu F$ and $L = 25 \text{ mH}$. The frequency of applied a.c. e.m.f. of 240 volt (peak) is 50 Hz. Calculate :- impedance of the circuit



[Watch Video Solution](#)

30. In a series LCR circuit, $R = 20\Omega$, $C = 10\mu F$ and $L = 25 \text{ mH}$. The frequency of applied a.c. e.m.f. of 240 volt (peak) is 50 Hz. Calculate :- maximum current



[Watch Video Solution](#)

31. In a series LCR circuit, $R = 20\Omega$, $C = 10\mu F$ and $L = 25 \text{ mH}$. The frequency of applied a.c. e.m.f. of 240 volt (peak) is 50 Hz. Calculate :- phase angle between the current and the voltage



Watch Video Solution

32. In a series LCR circuit, $R = 20\Omega$, $C = 10\mu F$ and $L = 25 \text{ mH}$. The frequency of applied a.c.

e.m.f. of 240 volt (peak) is 50 Hz. Calculate :-
maximum current



[Watch Video Solution](#)

33. In a series LCR circuit, $R = 20\Omega$, $C = 10\mu F$
and $L = 25\text{ mH}$. The frequency of applied a.c.
e.m.f. of 240 volt (peak) is 50 Hz. Calculate :-
average power delivered to the circuit.



[Watch Video Solution](#)

34. In a series resonant circuit, the inductance coil is of 0.2 H and the resistance coil is of 50Ω . What is the value of capacitance in the circuit for resonance to occur at a frequency of 1500 kHz? The source has an e.m.f. of 100 V r.m.s.?



Watch Video Solution

35. Find the reactance of a 0.8H inductance coil on an A.C. line of frequency 50 Hz.



Watch Video Solution

36. Find the impedance of a LR circuit with $R = 50\Omega$ in series with an inductive reactance of 30Ω .



Watch Video Solution

37. An A.C. circuit of maximum e.m.f. 100 volt and of frequency 50 Hz contains an inductance of 0.2 mH. What is the inductive reactance of the circuit? What is the maximum current in the circuit?



[Watch Video Solution](#)

38. An A.C.source of r.m.s. value 85V and frequency 50Hz is connected in series with an inductance of 2H and a resistance of 10Ω . Find the maximum current in the circuit.



[Watch Video Solution](#)

39. A resistance of 160Ω is used in series with an inductance L and an a.c. of 230V , 50Hz . If

the current in the circuit is 0.25A, find L.



[Watch Video Solution](#)

40. An A.C. e.m.f. of peak 220 V, 50 Hz is connected to an inductance of 253 mH and a resistance of 9Ω series calculate the impedance of the circuit and the r.m.s. current in the circuit.



[Watch Video Solution](#)

41. A circuit has a resistance and a reactance each equal to 100Ω . Find its power factor. If the circuit draws a current of 1.5 A for an applied voltage of 200 V, what is the average power consumed in the circuit?



Watch Video Solution

42. An A.C. circuit of peak e.m.f. 200 V and of frequency 50 Hz contains an inductive of 0.1 H

and resistance 10Ω in series. Find the power factor and the power consumed in the circuit



[Watch Video Solution](#)

43. Find the capacitive reactance of a $100\mu F$ capacitor used on a A.C.source of 50 Hz.



[Watch Video Solution](#)

44. A capacitance of $0.4\mu F$ is connected to an alternating e.m.f. of frequency 100 Hz. What is

the capacitive reactance ?



[Watch Video Solution](#)

45. A capacitor of $50\mu F$ is connected across a 100 V, 50 Hz a.c. supply. Find the reactance and the r.m.s. current.



[Watch Video Solution](#)

46. An a.c. series circuit has a source of maximum e.m.f. 220 V at a frequency of 50 Hz

connected to a capacitor of 8pF , an inductor of 0.8 H and a non-inductive resistor of 50Ω .

What is the maximum current in the circuit?



[Watch Video Solution](#)

47. The resonant frequency of a parallel LC circuit is 1000 kHz . If $L = 3\text{mH}$, find the capacitance used.



[Watch Video Solution](#)

48. Find the capacitance to be connected in parallel with a 100 mH inductance to achieve a resonance frequency of 50 Hz.



Watch Video Solution

49. An A.C. voltage of r.m.s. value V is applied to a parallel combination of inductor $L = 10\text{mH}$ and capacitor $C = 4\mu\text{F}$. Calculate the resonant frequency and current through each branch at resonance.





[Watch Video Solution](#)

50. A capacitor is used with an A.C. source of 110 V and frequency 50 Hz. If the maximum current in the circuit is 4.89 A, calculate the capacitance



[Watch Video Solution](#)

51. An a.c. consists of a resistor of 10W, inductor of 0.1 H and capacitor of 50 mF in

series across a 50 V, 50 Hz supply. Determine power factor of the circuit.



[Watch Video Solution](#)

52. An A.C. circuit consists of inductor of inductance 125 mH connected in parallel with a capacitor of capacity $50\mu F$. Determine the resonant frequency.



[Watch Video Solution](#)

53. In an ac circuit, V and I are given by $V = 100 \sin(100t)$ volts, $I = 100 \sin\left(100t + \frac{\pi}{3}\right)$ mA. The power dissipated in circuit is

- A. 10^4 wa
- B. 10 watt
- C. 2.5 watt
- D. 5 watt

Answer:



Watch Video Solution

54. The frequency of ac mains in India is

A. 30c/s or Hz

B. 50c/s or Hz

C. 60c/s or Hz

D. 120c/s or Hz

Answer:



Watch Video Solution

55. The peak value of 220 volts of ac mains is

- A. 155.6 volts
- B. 220.0 volts
- C. 311.0 volts
- D. 440 volts

Answer:



Watch Video Solution

56. If a current I given by $I_o \sin\left(\omega t - \frac{\pi}{2}\right)$ flows in an ac circuit across which an potential of $e = e_o \sin \omega t$ has been applied, then the power consumption P in the circuit will be.

A. $P = \frac{e_o i_o}{\sqrt{2}}$

B. $P = \sqrt{2} e_o i_o$

C. $P = \frac{e_o i_o}{2}$

D. $P = 0$

Answer:



Watch Video Solution

57. In an ac circuit, the current is given by $I = 5 \sin\left(100t - \frac{\pi}{2}\right)$ and the ac potential is $V = 200 \sin(100t)$ volt. Then the power consumption is

- A. 20 watts
- B. 40 watts
- C. 1000 watts
- D. 0 watts

Answer:



Watch Video Solution

58. The frequency of an alternating voltage is 50 cycles//sec and its amplitude is 120V. Then the r.m.s. value of voltage is

A. 101.3 V

B. 84.8 V

C. 70.7V

D. 56.5 V

Answer:



Watch Video Solution

59. The ratio of peak value and r.m.s. value of an alternating current is

A. 1

B. $\frac{1}{2}$

C. $\sqrt{2}$

D. $\frac{1}{\sqrt{2}}$

Answer:



Watch Video Solution

60. The power factor of LCR circuit at resonance is

A. 0.707

B. 1

C. zero

D. 0.5

Answer:



Watch Video Solution

61. Power delivered by the source of the circuit becomes maximum, when

A. $\omega L - \omega C$

B. $\omega L = \frac{1}{\omega} C$

C. $\omega L = - \left(\frac{1}{\omega C} \right)^2$

D. $\omega L = \sqrt{\omega} C$

Answer:



Watch Video Solution

62. In a circuit containing an inductance of zero resistance, the e.m.f. of the applied ac voltage leads the current by

A. 90°

B. 45°

C. 30°

D. 0°

Answer:



Watch Video Solution

63. An alternating e.m.f. is applied to purely capacitive circuit. The phase relation between e.m.f. and current flowing in the circuit is

A. e.m.f. is ahead of current by $\frac{\pi}{2}$

B. current is ahead of e.m.f. by $\frac{\pi}{2}$

C. current is ahead of e.m.f. by π

D. current is ahead of e.m.f. by π

Answer:



Watch Video Solution

64. An alternating current of frequency 'f' is flowing in a circuit containing a resistance R and a choke L in series. The impedance of this circuit is

A. $R + 2\pi fL$

B. $\sqrt{R^2 + 4\pi^2 f^2 L^2}$

C. $\sqrt{R^2 + L^2}$

D. $\sqrt{R^2 + 2\pi fL}$

Answer:



Watch Video Solution

65. The average power dissipation in a pure capacitance in ac circuit is

A. $\frac{1}{2}CV^2$

B. CV^2

C. $\frac{1}{4}CV^2$

D. Zero

Answer:



Watch Video Solution

66. An alternating voltage $e = 200\sqrt{2} \sin (100 t)$ is connected to a 1microfarad capacitor through an ac ammeter. The reading of the ammetershall be

A. 10mA

B. 20 mA

C. 40 mA

D. 80 mA

Answer:



Watch Video Solution

67. L, C and R denote inductance, capacitance and resistance respectively. Pick out the combination which does not have the dimensions of frequency

A. $\frac{1}{R}C$

B. $\frac{R}{L}$

C. $\frac{1}{\sqrt{LC}}$

D. C/L

Answer:



Watch Video Solution

68. What will be the phase difference between virtual voltage and virtual current, when the current in the circuit is wattless

A. 90°

B. 45°

C. 180°

D. 60°

Answer:



Watch Video Solution

69. Power factor is maximum in an LCR circuit
when

A. $X_L = X_C$

B. $R=0$

C. $X_L = 0$

D. $X_C = 0$

Answer:



Watch Video Solution

70. The capacity of a pure capacitor is 1 Farad.

In DC circuits, its effective resistance will be

A. zero

B. infinite

C. 1 ohm

D. $\frac{1}{2} \text{ohm}$

Answer:



Watch Video Solution

71. A 220 V, 50 Hz ac source is connected to an inductance of 0.2 H and a resistance of 20 ohm in series. What is the current in the circuit.

A. 10 A

B. 5 A

C. 33.3 A

D. 3.33 A

Answer:



Watch Video Solution

72. For high frequency, a capacitor offers

A. More reactance

B. Less reactance

C. Zero reactance

D. Infinite reactance

Answer:



Watch Video Solution

73. In LCR circuit the pd between the terminals of the inductance is 60 V, between the terminals of the capacitor is 30 V and that

between the terminals of resistance is 40 V.

The supply voltage will be equal to

A. 50V

B. 70V

C. 130V

D. 10 V

Answer:



Watch Video Solution

74. In a LCR circuit capacitance is changed from C to $2C$. For the resonant frequency to remain unchanged, the inductance should be changed from L to

A. $4L$

B. $2L$

C. $L/2$

D. $L/4$

Answer:



Watch Video Solution

75. An oscillator circuit consists of an inductance of 0.5 mH and a capacitor of $20 \mu\text{F}$. The resonant frequency of the circuit is nearly

A. 15.92 Hz

B. 159.2 Hz

C. 1592 Hz

D. 15910 Hz

Answer:





Watch Video Solution

76. Which of the following components of an LCR circuit with ac supply, dissipates energy

A. L

B. R

C. C

D. All of these

Answer:



Watch Video Solution

77. The phase difference between the ac and emf is $\frac{\pi}{2}$. Which of the following cannot be the constituent of the circuit

A. LC

B. L alone

C. R alone

D. R,L

Answer:



Watch Video Solution

78. In an A.C. circuit the current

A. Always leads the voltage

B. Always lags behind the voltage

C. It is always in phase with the voltage

D. May lead or lag behind or be in phase
with the voltage

Answer:



Watch Video Solution

79. A coil of inductive reactance 31Ω has a resistance of 8Ω . It is placed in series with a condenser of capacitive reactance 25Ω . The combination is connected to an a.c. source of 110 volt. The power factor of the circuit is

A. 0.8

B. 0.33

C. 0.56

D. 0.64

Answer:



Watch Video Solution

80. A light bulb is rated 100 W for a 220 V supply. The resistance of the bulb and the peak voltage of the source respectively are

- A. 242Ω and 311V
- B. 484Ω and 311V
- C. 484Ω and 440 V
- D. 242Ω and 440 V

Answer:



Watch Video Solution

81. A 50 volt a.c. is applied across an RC (series) network. The rms voltage across the resistance is 40 volt, then the potential across the capacitance would be

A. 10 V

B. 20 V

C. 30 V

D. 40 V

Answer:



Watch Video Solution

82. A pure inductor of 25 mH is connected to a source of 220 V. Given the frequency of the source as 50 Hz, the rms current in the circuit is

A. 7 A

B. 14 A

C. 28 A

D. 42A

Answer:



Watch Video Solution

83. If the rms current in a 50 Hz AC rircuit is 5A
the value of the current $\frac{1}{300}$ seconds after its
value becomes zero is

A. $5(\sqrt{2})A$

B. $\frac{5(\sqrt{3})}{2}$

C. $\frac{5}{6}A$

D. $5/(\text{sqrt}2)A$

Answer:



Watch Video Solution

84. A resistor of 500Ω and an inductance of 0.5 H are in series with an AC source which is

given by $V = 100\sqrt{2} \sin (1000 t)$. The power factor of the combination is

A. $\frac{1}{\sqrt{2}}$

B. $\frac{1}{s} qtr3$

C. 0.5

D. 0.6

Answer:



Watch Video Solution

85. The displacement current is given by the expression

A. $\mu_0 \left(1 + \epsilon_0 \frac{d\phi_E}{dt} \right)$

B. $\epsilon_0 \frac{d\phi_E}{dt}$

C. $\mu_0 \epsilon_0 \frac{d\phi_E}{dt}$

D. $\mu_0 \epsilon_0$

Answer:



Watch Video Solution

86. An alternating e.m.f. is given by $e = 100 \sin 314 t$, the time within which the e.m.f. will half of its maximum value is

A. 0.16 sec.

B. 0.016 sec.

C. 0.0016 sec.

D. 1.6 sec.

Answer:



Watch Video Solution

87. A sinusoidal voltage $e = 200 \sin (100 t)$ is applied across a resistance of 100Ω then current measured by D.C. ammeter is

A. 2 A

B. 2.828 A

C. 0.2 A

D. 0

Answer:



Watch Video Solution

88. Relation between e_{rms} and e_o is

A. $\frac{e_{rms}}{e_o} = \frac{1}{\sqrt{2}}$

B. $e_{rms} = e_o\sqrt{2}$

C. $e_{rms} = 2e_o$

D. $e_o = e_{rms}\sqrt{2}$

Answer:



Watch Video Solution

89. A 6Ω resistance and 8Ω inductance are connected in series then power factor of the circuit is

A. 0.06

B. 0.6

C. 0.8

D. $\frac{1}{8}$

Answer:



Watch Video Solution

90. A current that does not perform any work is

- A. peak current
- B. r.m.s. current
- C. ideal current
- D. eddy currents

Answer:



Watch Video Solution

91. In LCR series circuit apparent power is

A. $e_{r.m.s.} \cdot i_{r.m.s.}$

B. $\frac{e_{r.m.s.}}{i_{r.m.s.}}$

C. $\frac{i_{r.m.s.}}{e_{r.m.s.}}$

D. $(e_{r.m.s.})^2 (i_{r.m.s.})$

Answer:



Watch Video Solution

92. Seled true statement for purely inductive circuit

A. current and voltage are in phase

B. current lags behind the e.m.f. by phase

of $\frac{\pi}{2}rad$

C. e.m.f. lags behind the current by phase

of $\frac{\pi}{2}rad$

D. current lags behind the e.m.f. by phase

of πrad

Answer:



Watch Video Solution

93. Resonance frequency for parallel LC circuit is given by

A. $\left(L \frac{C}{2\pi} \right)$

B. $\frac{1}{2\pi\sqrt{LC}}$

C. $\frac{2\pi}{LC}$

D. $\frac{\sqrt{LC}}{2\pi}$

Answer:



Watch Video Solution

94. In LCR series circuit, at resonance the applied e.m.f. and current

A. out of phase

B. differ by π radians

C. in phase

D. differ by $\frac{\pi}{2}$ rad

Answer:



Watch Video Solution

95. In series LCR circuit, at resonance impedance

A. maximum

B. minimum

C. zero

D. infinite

Answer:



Watch Video Solution

96. In series LCR circuit $R = 4\Omega$, $L = 0.2$ H and $C = 0.1$ F, at resonance impedance is

A. 4Ω

B. 15.99Ω

C. 0.2Ω

D. 19

Answer:



Watch Video Solution

97. The impedance of LCR circuit increases with frequency when

A. $L > C$

B. $C > L$

C. $X_L > X_C$

D. $X_C > X_L$

Answer:



Watch Video Solution

98. Which of the following depends upon frequency?

A. inductance

B. capacitance

C. resistance

D. C and B

Answer:



Watch Video Solution

99. In an R.C. circuit resistance = 4 Omega and $X_C = 3\Omega$, then power factor is

A. 0.8

B. 8

C. 0

D. 1

Answer:



Watch Video Solution

100. In a circuit L, C and R are connected in series with an alternating voltage of frequency f the current leads the voltage by 45° . The value of C is

A.
$$\frac{1}{\pi f(2fL - R)}$$

B.
$$\frac{1}{2\pi f(2\pi fL - R)}$$

C.
$$\frac{1}{\pi f(2\pi fL - R)}$$

$$D. \frac{1}{2\pi f(2\pi fL + R)}$$

Answer:



Watch Video Solution

101. In an AC circuit, e and i are given by $e = 150 \sin 150 t$ V and $i = 150 \sin \left(150t + \frac{\pi}{3} \right)$ A. The power dissipated in the circuit is

A. 106 W

B. 150 W

C. 5625 W

D. zero

Answer:



Watch Video Solution

102. In a series LCR circuit the phase difference between the voltage and the current is 45° .

Then the power factor will be

A. 0.607

B. 0.707

C. 0.808

D. 1

Answer:



Watch Video Solution

103. Select and write the most appropriate answer. The instantaneous current in an A.C. circuit is given by $i = 2 \sin (\omega t + \theta)$ ampere.

The r.m.s. value of the current is

- A. 2 ampere
- B. $2\sqrt{2}$ ampere
- C. $\sqrt{2}$ ampere
- D. $1/\sqrt{2}$ ampere

Answer:



Watch Video Solution

104. An L- C - R series circuit is joined to a source of alternating e.m.f. If $R = 9\Omega$, $X_L = 28\Omega$

, $X_c = 16 \Omega$, then the impedance of the circuit will be

A. 10Ω

B. 15Ω

C. 20Ω

D. 30Ω

Answer:



Watch Video Solution

105. In an A.C. circuit $I = 10 \cos (100t)$ ampere and $V = 20 \sin (100t)$. The power loss in the circuit will be

A. 20 watt

B. 200watt

C. 0 watt

D. 50 watt

Answer:



Watch Video Solution

106. An alternating e.m.f. is applied to a series L - C - R circuit. If the frequency of the applied e.m.f. is more than the resonant frequency of the circuit then the circuit will act as

- A. a resistive circuit
- B. an inductive circuit
- C. a capacitive circuit
- D. an oscillatory circuit

Answer:



Watch Video Solution

107. Answer the following in short. What is the power factor for a purely resistive circuit?



Watch Video Solution

108. State the condition for series resonance. Obtain an expression for resonant frequency.



Watch Video Solution

109. What is the phase difference between current and e.m.f. in a purely capacitive circuit?



Watch Video Solution

110. A alternating e.m.f. $e = 200 \sin (100\pi t)$ is connected across a resistor of resistance 10Ω . Calculate the r.m.s. current flowing through the circuit.



Watch Video Solution

111. Define: inductive reactance capacitive.



Watch Video Solution

112. Define peak and r.m.s. value of alternating signal.



Watch Video Solution

113. Distinguish between Resistance and Reactance.





[Watch Video Solution](#)

114. A radio can tune over a frequency range 400 kHz to 600 kHz of the medium wave band. If the L - C tuner circuit has an effective inductance of 0.2 mH, what must be the range of its variable capacitance of the capacitor?



[Watch Video Solution](#)

115. Distinguish between acceptor circuit and rejector circuit.



[Watch Video Solution](#)

116. An A.C. circuit consists of a resistor of 5Ω and inductor of 10 mH connected in series with 50 V, 50 Hz supply. What capacitance should be connected in series with the circuit to obtain maximum current? What will be the maximum current?



[Watch Video Solution](#)

117. Attempt the following . What is a series LCR resonant circuit? State the condition for series resonance and obtain an expression for the resonant frequency of the circuit.



[Watch Video Solution](#)

118. A capacitor of $25\mu F$, inductor of 0.1 H and resistor of resistance 25Ω are connected in series with an A.C. source of e.m.f., $e = 310 \sin(314 t)$ volt. What is the :-reactance





[Watch Video Solution](#)

119. A $25\mu F$ capacitor, 0.1 H inductor and 25W resistor are connected in series with an ac source of emf $e = 310 \sin 314 t$ volt. What is :- impedance



[Watch Video Solution](#)

120. A $25\mu F$ capacitor, 0.1 H inductor and 25W resistor are connected in series with an ac

source of emf $e = 310 \sin 314 t$ volt. What is:-
current in the circuit



[Watch Video Solution](#)

121. A capacitor of $25\mu F$, inductor of 0.1 H and resistor of resistance 25Ω are connected in series with an A.C. source of e.m.f., $e = 310 \sin (314 t)$ volt. What is the:-phase angle between current and applied e.m.f.



[Watch Video Solution](#)

122. A $25\mu F$ capacitor, 0.1 H inductor and 25W resistor are connected in series with an ac source of emf $e = 310 \sin 314 t$ volt. What is:-
current in the circuit



Watch Video Solution