



PHYSICS

BOOKS - MODERN PUBLICATION

ELECTRICAL MEASUREMENTS

Example

1. Two parallel resistors of 5 ohm and 20 ohm are connected in left arm of a metre bridge. If the null point is at 40 cm from left end of the wire, calculate the value of resistance connected in right arm.



[Watch Video Solution](#)

2. A cell of e.m.f. 4 V and of negligible internal resistance is connected in series with a potentiometer wire of length 400 cm. The e.m.f. of a

Leclanche cell is found to be balanced at 150 cm from the positive end of the potentiometer wire. What is the e.m.f. of the Leclanche cell ?

 [Watch Video Solution](#)

3. Two cells of emfs 1.5 V and 2.0V internal resistance 1Ω and 2Ω are connected in parallel so as to send current in the same direction through an external resistance of 5Ω .

Draw the circuit diagram.

 [Watch Video Solution](#)

4. Two cells of emfs 1.5 V and 2.0V internal resistance 1Ω and 2Ω are connected in parallel so as to send current in the same direction through an external resistance of 5Ω .

Draw the circuit diagram.

 [Watch Video Solution](#)

5. Two cells of emfs 1.5 V and 2.0V internal resistance 1Ω and 2Ω are connected in parallel so as to send current in the same direction through an external resistance of 5Ω .

Using Kirchhoff's rules, calculate.

potential difference across the 5Ω resistance.



[Watch Video Solution](#)

6. Three cells are connected in parallel with their like poles connected together with wires of negligible resistance. If the emfs of the cells are 2, 1 and 4 V respectively and their internal resistances are 4, 3 and 2Ω respectively, find the current through each cell.



[Watch Video Solution](#)

7. Two cells of emf 2V and 4V and internal resistance 1Ω and 2Ω respectively are connected in parallel so as to send the current in the

same direction through an external resistance of 10Ω . Find the potential difference across 10Ω resistor.

 [Watch Video Solution](#)

8. Twelve wire, each having resistance r , are joined to form a cube. Find the equivalent resistance between the end of a face diagonal such as a and c .

 [Watch Video Solution](#)

9. 12 wires each of resistance r ohm are connected in the form of a skelton cube. Find the equivalent resistance of the cube, when a cell is joined across any one of the 12 wires forming the cube.

 [Watch Video Solution](#)

10. Four resistors of 15ohm , 12ohm , 4ohm and 10ohm given in cyclic order to form a wheat stone bridge. What resistance (in ohm) should be

connected in parallel across the 10ohm resistor to balance the wheat stone bridge .

 [Watch Video Solution](#)

11. 4 resistance $P= 5\text{ohm}$, $Q= 6\text{ ohm}$, $R=50\text{ ohm}$ & $S= 60\text{ ohm}$ are connected in Four Arms of a wheatstone bridge. If a cell of EMF 1.5 v and negligible internal resistance is connected across the bridge, calculate the current in the arms of the Wheat stone bridge and the cell.

 [Watch Video Solution](#)

12. A wire connected in the left gap of a meter bridge balance a 10Ω resistance in the right gap to a point, which divides the bridge wire in the ratio 3:2. If the length of the wire is 1m. Calculate the length of one ohm wire.

 [Watch Video Solution](#)

13. In a metre bridge, the balance point is found to be at 39.5 cm from the end A, when the resistor Y is of 12.5Ω . Determine the resistance of X.

Made of thick copper strips? Determine the balance point of the bridge above if X and Y are interchanged. What happens if the galvanometer and cell are interchanged at the balance point of the bridge? Would the galvanometer show any current?

 [Watch Video Solution](#)

14. With two resistance R_1 and $R_2 (> R_1)$ in the two gaps of a metre bridge the balance was found to be $1/3$ m from the zero end. When a 6Ω resistance is connected in series with the smaller of the two resistance, the point is shifted to $2/3$ m from the same end, then R_1 and R_2 Find the resistance of the two wires.

 [Watch Video Solution](#)

15. A potentiometer wire of length 1 m has a resistance 10 ohm. It is connected to 6 V battery in series with a resistance of 5 ohm. Determine the emf of the primary cell which gives a balance point at 40 cm.



[Watch Video Solution](#)

16. The resistance of a potentiometer wire of length 10 m is 25Ω . A resistance box and a 2 volt accumulator are connected in series with it. What resistance should be introduced in the box to have a potential drop of one microvolt per millimetre of the potentiometer wire ?



[Watch Video Solution](#)

17. A 10 meter long wire of uniform cross section of 20Ω resistance is used as a potentiometer wire. This wire is connected in series with a battery of 5V along with an external resistance of 480 Ω if an unknown emf ϵ is balanced at 600 cm of this wire , calculate the potential gradient of the potentiometer wire.



[Watch Video Solution](#)

18. A 10 meter long wire of uniform cross section of 20Ω resistance is used as a potentiometer wire. This wire is connected in series with a battery of 5V along with an external resistance of 480 Ω if an unknown emf ϵ is balanced at 600 cm of this wire, calculate the value of the unknown emf.



[Watch Video Solution](#)

19. With a certain cell, the balance point is obtained at 65 cm from the zero end of a potentiometer wire. With another cell, whose e.m.f. is less than that of the first by 0.1 V, the balance point is obtained at 60 cm. What is the e.m.f. of the first cell ?



[Watch Video Solution](#)

20. A potentiometer has 10 wires each of 1 meter length and the total resistance is 20Ω . Find the resistance to be connected to the driving battery of emf 2 volts to produce a potential drop of $1\mu V$ per millimeter.



[Watch Video Solution](#)


21. Three resistors are connected to form the sides of a triangle ABC , the resistance of the sides AB, BC and CA are 40 ohms , 60 ohms and 100 ohms respectively. Find the effective resistance between the points A and B in ohms .



[Watch Video Solution](#)

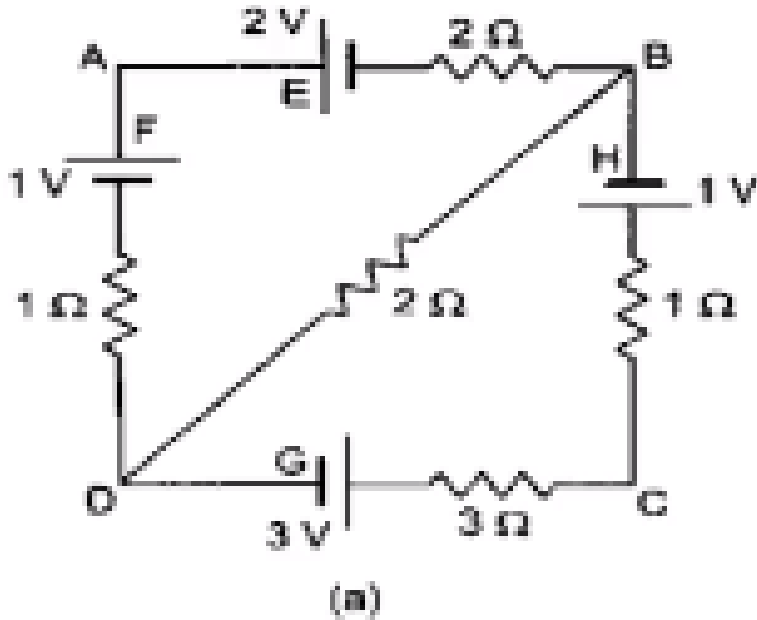22. In the circuit show in the figure E,F,G and H are cells of e.m.f. 2,1,3 and 1 V and their internal resistances are 2,1,3 and 1Ω respectively. Calculate the


potential difference across the terminals of each of the cells G and H.



[▶ Watch Video Solution](#)

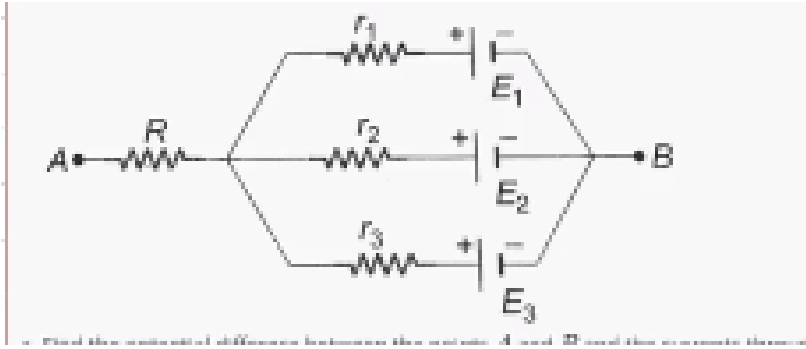
23. In the circuit shown in the figure $E_1 = 3V$, $E_2 = 2V$, $E_3 = 1V$ and the resistances $R = r_1 = r_2 = r_3 = 1\Omega$. Find the potential difference

between the points A and B and the current through each branch.




[▶ Watch Video Solution](#)

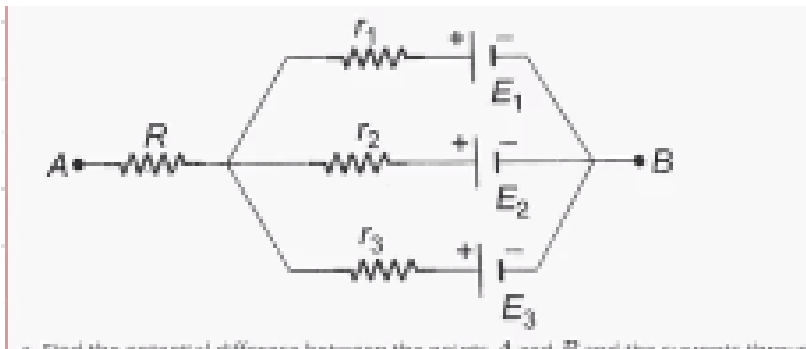24. In the circuit shown in the figure $E_1 = 3V$, $E_2 = 2V$, $E_3 = 1V$ and the resistances $R = r_1 = r_2 = r_3 = 1\Omega$. If r_2 is short circuited and the point A is connected to the point B, find the currents through E_1 , E_2 and E_3 and the resistor R



[▶ Watch Video Solution](#)

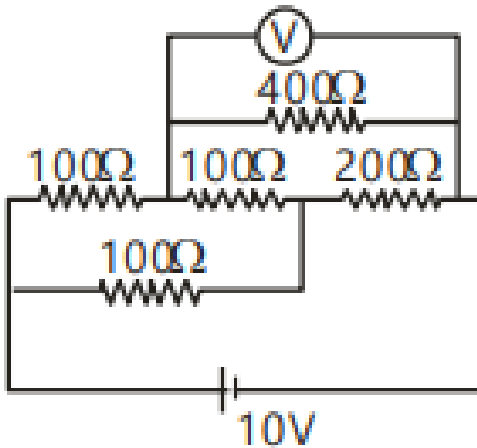
25. An electrical circuit is shown in the Fig. Calculate the potential difference across the resistance of 400 ohm, as will be measured by the voltmeter V of resistance 400 ohm, either by applying Kirchhoff's rules or otherwise.



[▶ Watch Video Solution](#)

26. A part of a circuit in steady state along with the currents flowing in the branches, the values of resistances, etc, is shown in figure. Calculate the

energy stored in the capacitor.

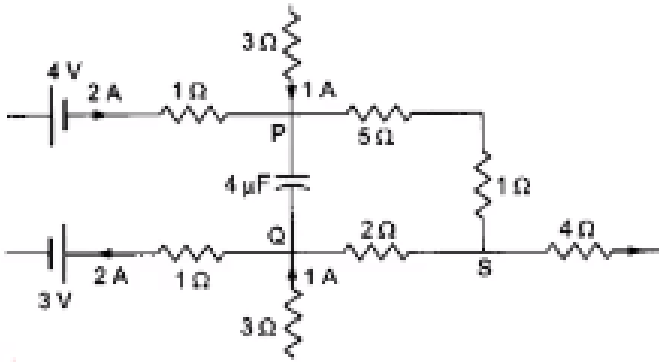


[Watch Video Solution](#)

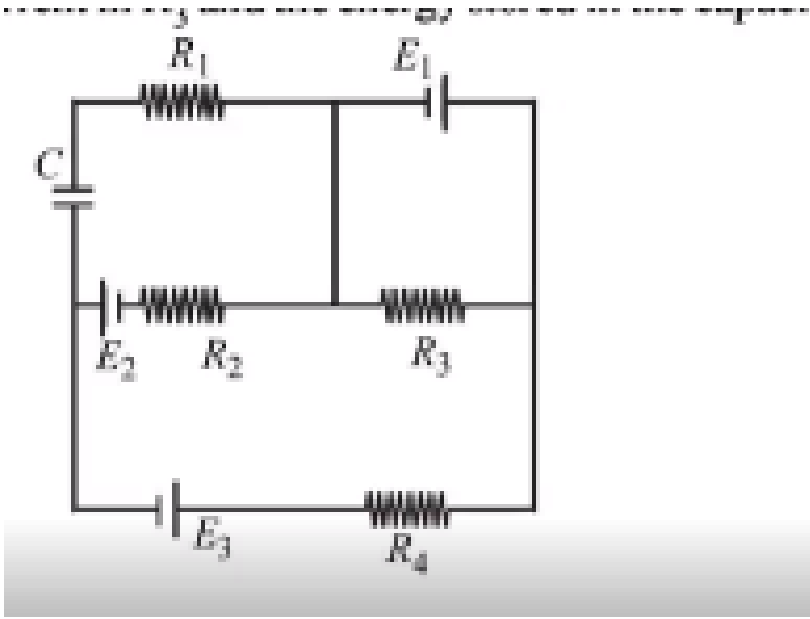27. In the circuit show in figure

$$E_2 = 2V, E_1 = 3E_3 = 6V, C = 5\mu F, R_1 = 2R_2 = 6\Omega, R_3 = 2R_4 = 4\Omega$$

. Find the current in R_3 and the energy stored in the capacitor.




Watch Video Solution

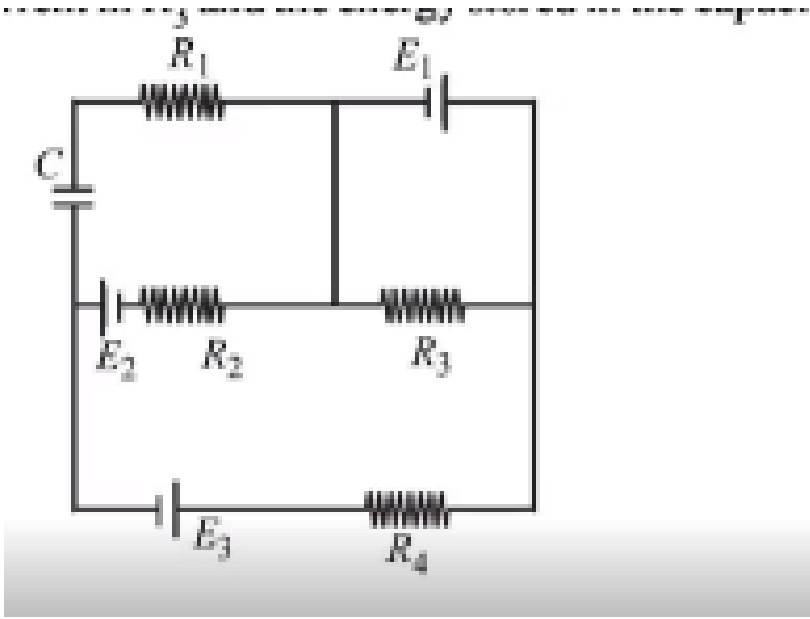28. In the circuit show in figure

$$E_2 = 2V, E_1 = 3E_3 = 6V, C = 5\mu F, R_1 = 2R_2 = 6\Omega, R_3 = 2R_4 = 4\Omega$$

. Find the current in R_3 and the energy stored in the capacitor.




Watch Video Solution

29. In a wheatstone bridge, the resistance of the arms of the bridge are $AB = 2\Omega$, $BC = 4\Omega$, $AD = 1\Omega$ and $DC = 3\Omega$. a cell of emf 2volt the terminals of negligible resistance to A and C is connected. If a galvanometer of resistance 10Ω is connected between B and D, find the current in the galvanometer.



Watch Video Solution

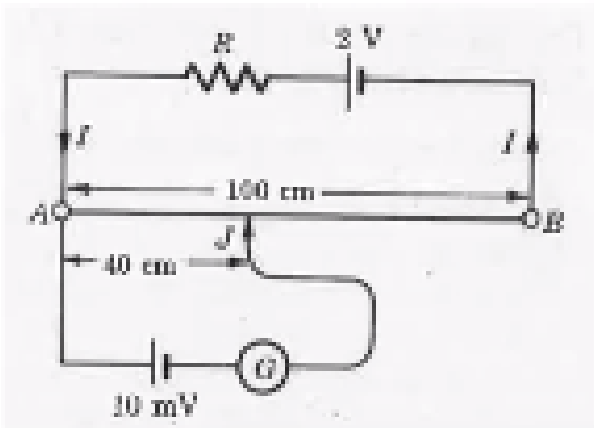30. A potentiometer wire of length 100 cm has a resistance of 10Ω . It is connected in series with a resistance and an accumulator of emf 2V and negligible internal resistance. A source of emf 10 mV is balanced against a length of 40 cm of the potentiometer wire. what is the value of the external resistance?



[▶ Watch Video Solution](#)

31. State the basic concept on which Kirchhoff's first law is based?

[▶ Watch Video Solution](#)

32. What is the loop rule?

 [Watch Video Solution](#)

33. Draw the circuit diagram of Wheatstone bridge. Under what condition, no current flows through its galvanometer (balanced condition)?

 [Watch Video Solution](#)

34. Name two practical applications of Wheatstone bridge?

 [Watch Video Solution](#)

35. What is principle of a metre bridge?

 [Watch Video Solution](#)

36. Why is a slide wire bridge also called a metre bridge?

 [Watch Video Solution](#)

37. Why are the connections between the resistors in a meter bridge made of thick copper strips?

 [Watch Video Solution](#)

38. In a meter bridge, two unknown resistances R and S when connected in two gaps, give a null point at 40 cm from one end. What is the ratio of R and S ?

 [Watch Video Solution](#)

39. The resistance in the left gap of a metre bridge is 10Ω and the balance point is 40 cm from the left end. Calculate the value of the unknown resistance.



[Watch Video Solution](#)

40. Name the device used for measuring the e.m.f. of a cell.



[Watch Video Solution](#)

41. Why is a potentiometer named as potentiometer?



[Watch Video Solution](#)

42. State the principle of a potentiometer.



[Watch Video Solution](#)

43. Why should the potentiometer wire be of uniform cross-section and composition?



[Watch Video Solution](#)

44. By which material is a potentiometer wire normally made and why?

 [Watch Video Solution](#)

45. Of which material is a potentiometer wire normally made and why?

 [Watch Video Solution](#)

46. What type of cell should be used in the main circuit of the potentiometer and why?

 [Watch Video Solution](#)

47. Why electric current should not be passed through potentiometer wire for a long time continuously?

 [Watch Video Solution](#)

48. Sometimes balance point may not be obtained on the potentiometer wire. Why?

 [Watch Video Solution](#)

49. The e.m.f. of the cell used in the main circuit of the potentiometer should be more than the potential difference to be measured. Why?

 [Watch Video Solution](#)

50. Name the device used for measuring the internal resistance of a secondary cell.

 [Watch Video Solution](#)

51. Write down the relation between the e.m.f. of a cell and its internal resistance.



[Watch Video Solution](#)

52. Define junction and loop. State Kirchoff's laws.



[Watch Video Solution](#)

53. Explain the significance of Kirchoff's law.




[Watch Video Solution](#)

54. Using meter bridge, it is advised to obtain the null point in the middle of the wire. why?




[Watch Video Solution](#)

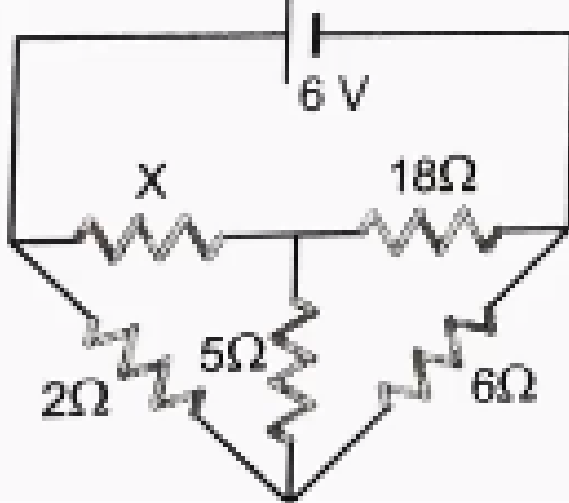55. Find out the magnitude of resistance X in the circuit shown in the figure, when no current flows through the 5Ω resistor.



 [Watch Video Solution](#)

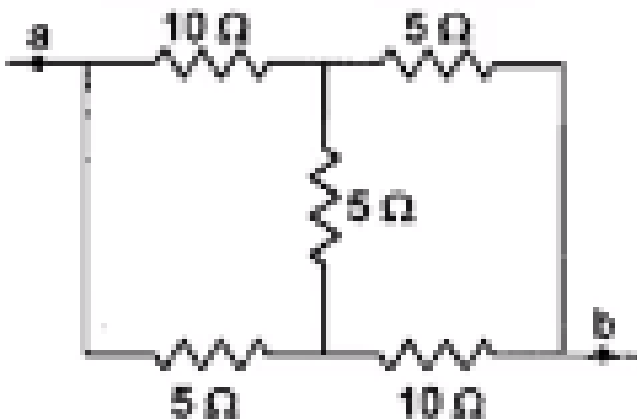
56. What is the resistance between points A and B in the circuit shown in the figure.





Watch Video Solution

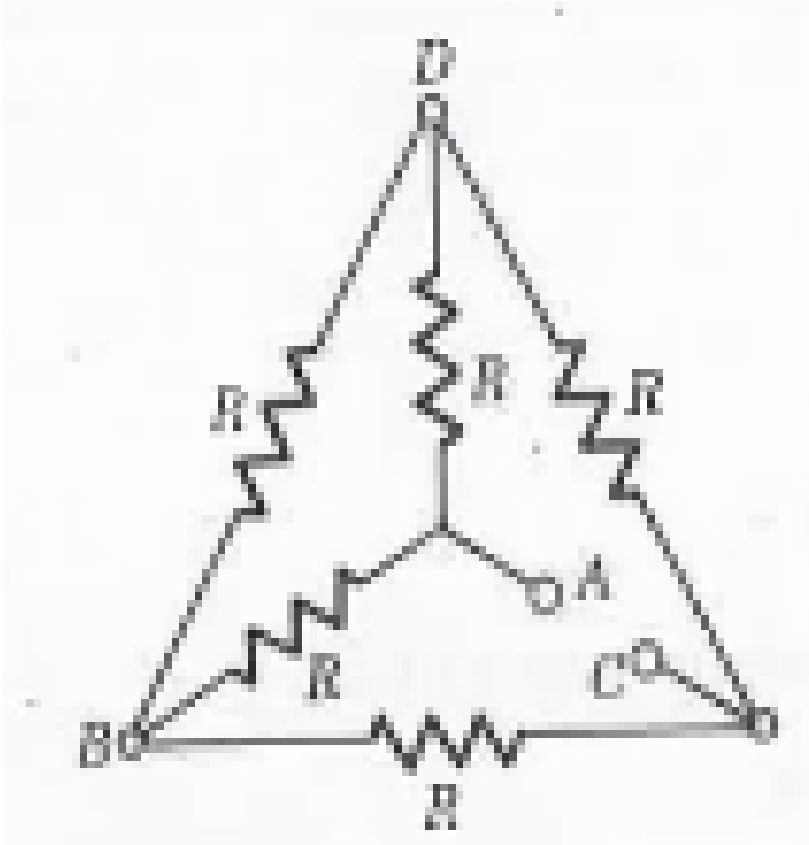57. If each of the resistances in network shown in the figure is R , what is the resistance between terminals A and C?



Watch Video Solution

58. Draw a circuit diagram for determining the unknown resistance R using meter bridge. Explain briefly its working, giving the necessary formula used.


 [Watch Video Solution](#)

59. Why is a potentiometer preferred over a voltmeter for determining the e.m.f. of a cell?

 [Watch Video Solution](#)

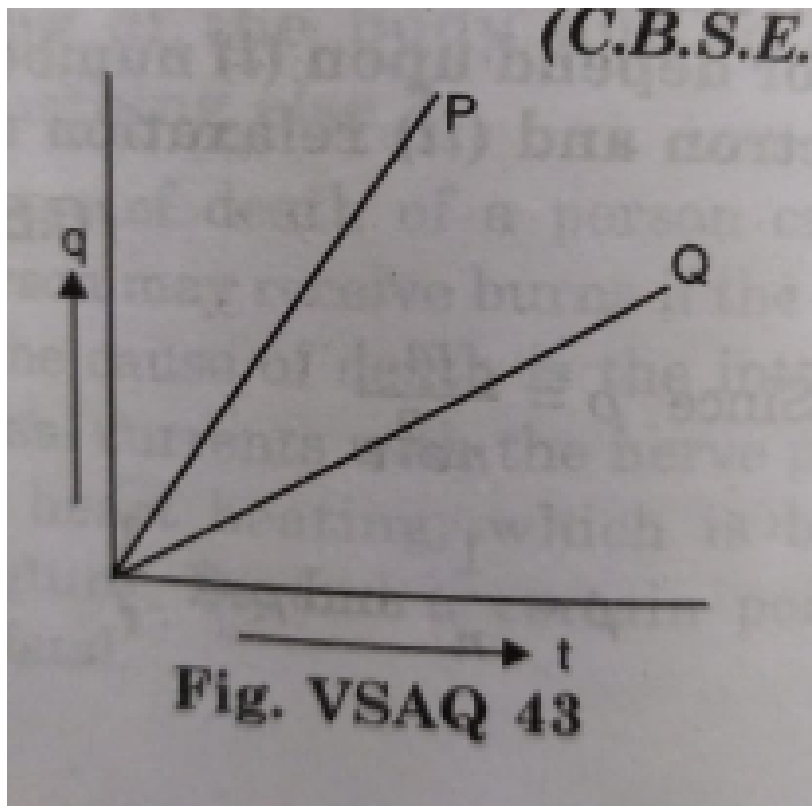60. The variation of potential difference V with length l in the case of two potentiometers, P and Q is as shown in the figure. Which of these two will

you prefer for comparing the emf's of the two primary cells?



[Watch Video Solution](#)

61. How can you make a potentiometer of given wire length more sensitive using resistance box?

[Watch Video Solution](#)

62. Draw circuit diagram for the comparison of e.m.fs of two cells with the help of a potentiometer.

 [Watch Video Solution](#)


63. How will you use potentiometer to determine internal resistances of a cell?

 [Watch Video Solution](#)

64. In a potentiometer experiment , the balancing with a cell is at length 240 cm. On shunting the cell with a resistance of 2Ω , the balancing length becomes 120 cm. Find the internal resistance of the cell.

 [Watch Video Solution](#)

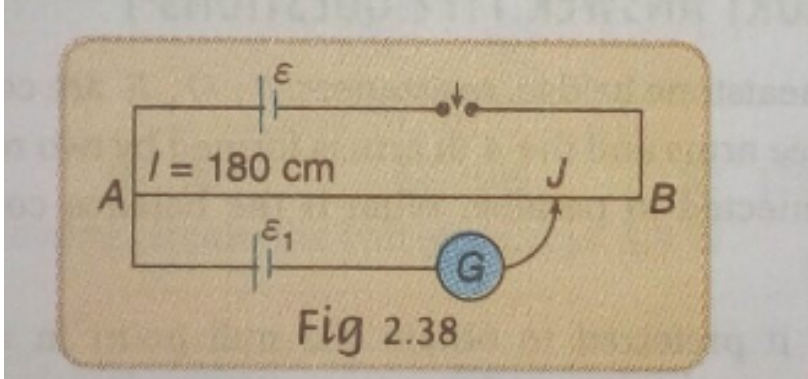
65. In the circuit shown in the figure, AB is a resistance wire of uniform cross-section in which a potential gradient of $0.01V^{-1}$ exists.



If the galvanometer G shows zero deflection what is the e.m.f. \mathcal{E}_1 of the cell used?

[▶ Watch Video Solution](#)

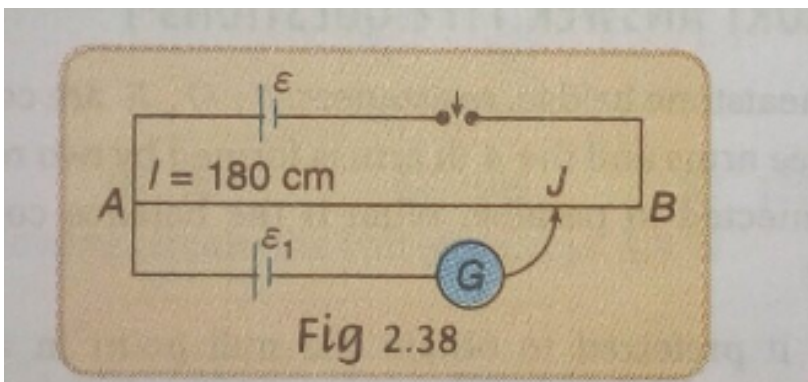66. In the circuit shown in the figure, AB is a resistance wire of uniform cross-section in which a potential gradient of $0.01Vcm^{-1}$ exists.



If the internal resistance of the driver cell increases on some account, how will it change the balance point in the experiment?



[Watch Video Solution](#)

67. A cell of e.m.f. 1 V gives a balance point at 40 cm length of a potentiometer wire. For another cell, the balance point shifts to 60 cm. Find the e.m.f. of the second cell.




[Watch Video Solution](#)

68. Two students X and Y performs an experiment on potentiometer separately using the circuit diagram shown in the fig keeping other things unchanged

X increases the value of resistance R.

How would these changes affect the position of null point in each case

and why?

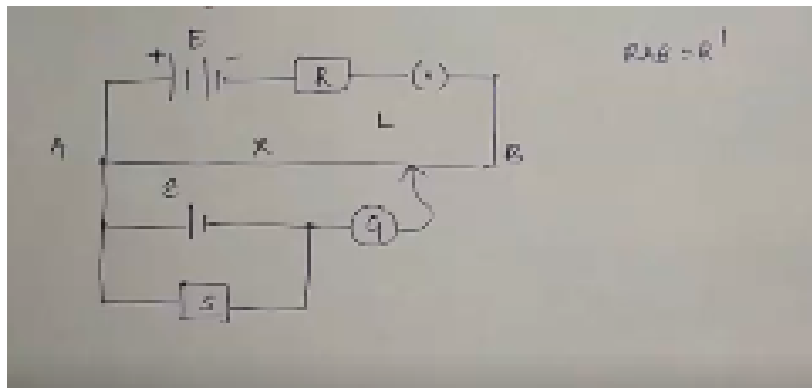


[Watch Video Solution](#)

69. Two students X and Y performs an experiment on potentiometer separately using the circuit diagram shown in the fig keeping other things unchanged

Y decreases the value of resistance S in the set up.

How would these changes affect the position of null point in each case

and why?

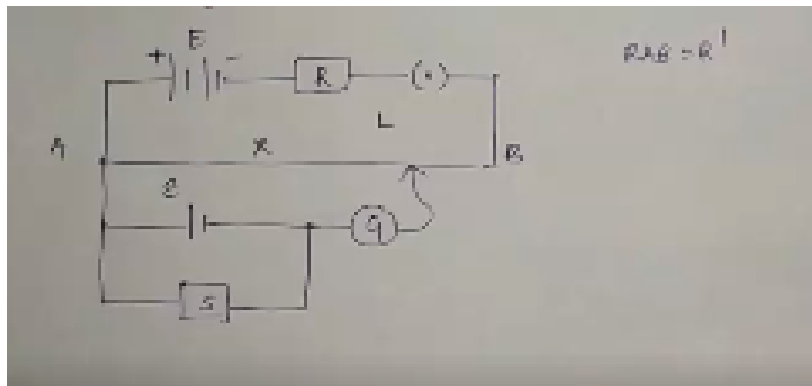

[▶ Watch Video Solution](#)

70. Why do we prefer potentiometer of longer length for sensitive measurements?

[▶ Watch Video Solution](#)


71. Explain the principle on which the working of a potentiometer is based. Why is the use of potentiometer preferred over that of a voltmeter for measuring the e.m.f. of a cell.

[▶ Watch Video Solution](#)

72. Why is a potentiometer preferred over a voltmeter for determining the e.m.f. of a cell?


[▶ Watch Video Solution](#)

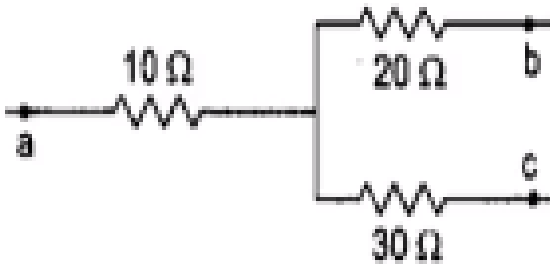73. Figure shows a part of an electric circuit. The potentials at the points a, b and c are 30V, 12V and 2V respectively. Find the currents through the three resistors.




[▶ Watch Video Solution](#)

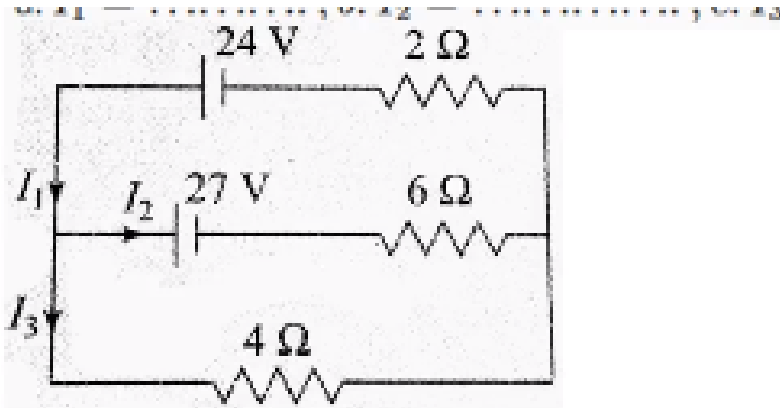74. Determine the values of currents I_1 , I_2 and I_3 in the network shown in the figure.



[Watch Video Solution](#)

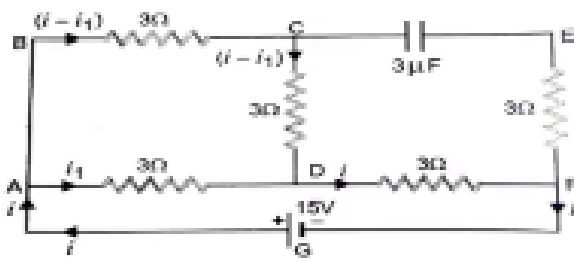
75. In the circuit shown in the figure, calculate the potential difference across the capacitor C.



Find the potential difference across capacitor.

[▶ Watch Video Solution](#)

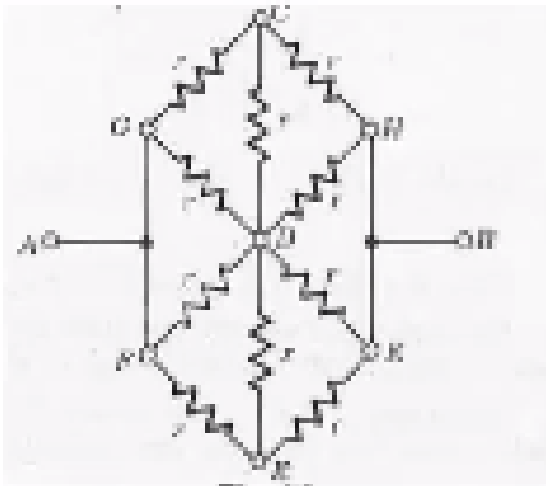76. Find the equivalent resistance between points A and B of the network of resistors shown in the figure. Each resistor is of resistance r .




[▶ Watch Video Solution](#)

77. Eight equal resistors, each of resistance r are connected along the edge of a pyramid OABCD having square base ABCD . Calculate the equivalent resistance of the network between the points A and D.

[▶ Watch Video Solution](#)

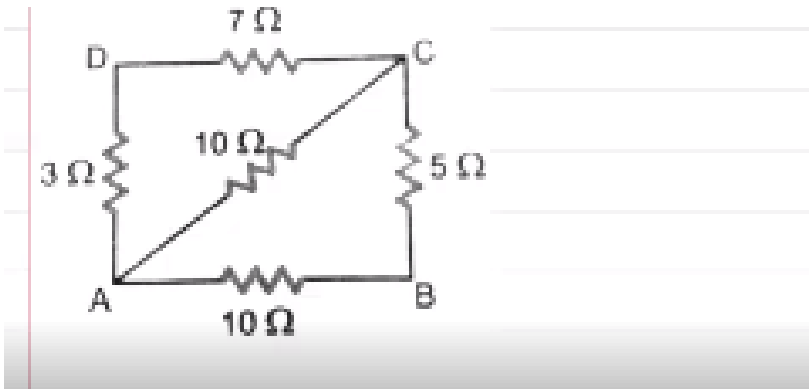78. Find the equivalent resistance of the network of resistors shown in the figure between the points A and B.



[▶ Watch Video Solution](#)

79. A short circuit occurs in a telephone cable having a resistance of $0.45\Omega m^{-1}$. The circuit is tested with a Wheat stone bridge network have values of 100Ω and $1,110\Omega$ respectively. A balance condition is found when the variable resistor has a value of 400Ω . Calculate the distance down the cable, where the short has occurred.

 [Watch Video Solution](#)

80. Two cells, E_1 and E_2 of emfs 4 V and 8 V having internal resistances 0.5Ω and 1.0Ω respectively are connected in opposition to each other. This combination is connected in opposition to with resistance of 4.5Ω and 3.0Ω . Another resistance of 6Ω is connected in parallel across the 3Ω resistor. Draw the circuit diagram

 [Watch Video Solution](#)

81. Two cells of e.m.f. 6V and 12V and internal resistances 1Ω and 2Ω respectively are connected in parallel so as to send current in the same

direction through an external resistance of 15ohm . Draw the circuit diagram.

 [Watch Video Solution](#)

82. Two cells of e.m.f. 6V and 12V and internal resistance 1ohm and 2ohm respectively are connected in parallel so as to send current in the same direction through an external resistance of 15ohm . Calculate current in each branch of the circuit (c) potential difference across the 15ohm resistor.

 [Watch Video Solution](#)


83. Two cells of e.m.f. of 1.6V and 2.4V have internal resistance 2 and 4 respectively. The two resistance wires positive poles are connected to resistance of 6 and negative poles connected to 8ohm . If another wire of 10 is connected between the mid-points of these wires, what is the potential difference across it.

 [Watch Video Solution](#)

84. A battery of 10V and negligible internal resistance is connected across the diagonally opposite corners of a cubical network consisting of 12 resistors each of resistance 1Ω . Determine equivalent resistance of the network and the current through the battery.

[Watch Video Solution](#)

85. Calculate the resistance between points X and Y in the circuit shown in the figure

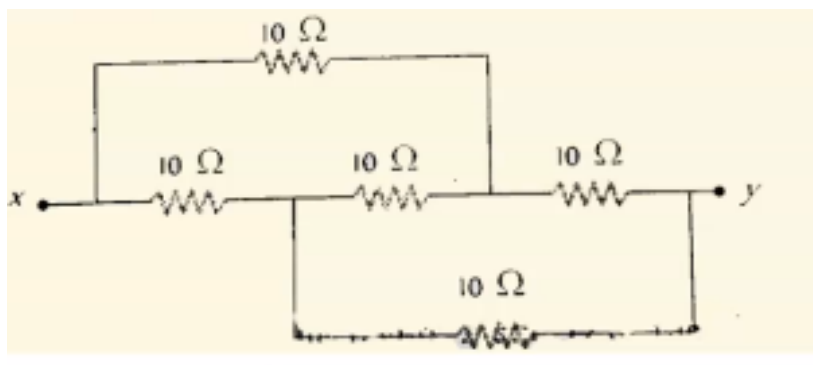[Watch Video Solution](#)

86. In a Wheatstone's network, $P = 2\Omega$, $Q = 2\Omega$, $R = 2\Omega$ and $S = 3\Omega$.

The resistance with which S is to be shunted in order that the bridge may be balanced .

 [Watch Video Solution](#)

87. In a meter bridge when the resistance in the left gap is 2Ω and an unknown resistance in the right gap the balance point is obtained at 40 cm from the zero end. On shunting the unknown resistance with 2Ω , find the shift of the balance point on the bridge wire

 [Watch Video Solution](#)

88. In a meter-bridge experiment with a resistance R_1 in left gap and a resistance X in a right gap. null point is obtained at 40 cm from the left end. With a resistance R_2 in the left gap, the null point is obtained at 50 cm from left hand. Find the position of the left gap is containing R_1 and R_2 in series.

 [Watch Video Solution](#)

89. In a meter-bridge experiment with a resistance R_1 in left gap and a resistance X in a right gap. null point is obtained at 40 cm from the left emf. With a resistance R_2 in the left gap, the null point is obtained at 50 cm from left hand. Find the position of the left gap is containing R_1 and R_2 in parallel.

 [Watch Video Solution](#)

90. In comparing the resistance of two cells P and Q with a sides wire bridge, a balance point is obtained when the sliding contact is 30 cm from the zero end of the wire. The resistances P and Q are interchanged and the balance is obtained at 120 cm from the same emf. Find the ratio of the resistance P and Q and the length of the bridge wire

 [Watch Video Solution](#)

91. A cell gives a balance with 85 cm of a potentiometer wire. When the terminals of the cell are shorted through a resistance of 7.5Ω , the balance is obtained at 75 cm. Find the internal resistance of the cell.

 [Watch Video Solution](#)

92. It is found that 125 cm length of a potentiometer wire is required to balance the e.m.f. of a Daniel cell but that only 100 cm of the wire is required for the balance, if the poles of the cell are joined to a resistance of 2 ohm. Calculate the internal resistance of the cell.

 [Watch Video Solution](#)

93. A cell can be balanced against 110 cm and 100 cm of potentiometer wire respectively, when open circuited and when short circuited through a resistance of 10 ohm. Find the internal resistance of the cell.

 [Watch Video Solution](#)

94. The potentiometer wire of length 100cm has a resistance of 10Ω . It is connected in series with a resistance of 5Ω and an accumulator of emf 3V having negligible resistance. A source 1.2V is balanced against a length 'L' of the potentiometer wire. Find the value of L.

 [Watch Video Solution](#)

95. In an experiment to determine the internal resistance of a cell, the null point is obtained at 2 cm, when the cell is shunted by a resistance of 5Ω . When the cell is shunted by a resistance of 20Ω , the null point is obtained at 3 cm. Find the internal resistance of the cell.

 [Watch Video Solution](#)

96. In a potentiometer, a standard cell of emf 5V and of negligible resistance maintains a steady current through the galvanometer wire of length 5 m. Two primary cells of emfs ε_1 and ε_2 are joined in series with (i) same polarity and (ii) opposite polarity. The combination is connected

through it galvanometer and a joined to the potentiometer. The balancing length is the two cases are found to be 350 cm and 50 cm respectively

Draw the necessary circuit diagram.

 [Watch Video Solution](#)


97. In a potentiometer, a standard cell of emf 5V and of negligible resistance maintains a steady current through the galvanometer wire of length 5 m. Two primary cells of emfs ε_1 and ε_2 are joined in series with (i) same polarity and (ii) opposite polarity. The combination is connected through it galvanometer and a joined to the potentiometer. The balancing length is the two cases are found to be 350 cm and 50 cm respectively

Find the value of emfs of the two cells

 [Watch Video Solution](#)

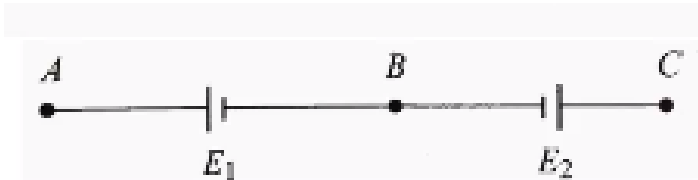98. Two cells of emfs E_1 and $(E_2 (E_1 > E_2))$ are connected as shows in figure

When a potentiometer is connected between A and B, the balancing length of the potentiometer wire is 300 cm. On connecting the same potentiometer between A and C, the balancing length is 100 cm. The ratio E_1 / E_2



[Watch Video Solution](#)

99. A cell of e.m.f. 2 V and negligible internal resistance is connected to a potentiometer wire of resistance 10 Ω and length 4 m. The potential difference per unit length (potential gradient) of the wire is



[Watch Video Solution](#)

100. A standard cell emf 1.08 V is balanced by the potential difference across 91 cm of a meter long wire applied by a cell of emf 2 V through a series resistor of resistance 2Ω . The internal resistance of the cell is zero. Find the resistance per unit length of the potentiometer wire.

 [Watch Video Solution](#)

101. A potentiometer wire carries current. The potential difference across 70 cm of it balances the potential difference across a 2 ohm coil supplied by a cell of e.m.f. 2 volt. When a 1 ohm coil is placed in parallel with the 2 ohm coil, a length equal to 50 cm of the potentiometer wire is required to balance the potential difference across the parallel combination. What is the internal resistance of the 2 V cell?

 [Watch Video Solution](#)

102. A certain unknown resistance is connected in the left gap and a resistance box in the right gap of a metre bridge. By introducing a

resistance of 10Ω with the help of resistance box, the balance point is determined. If the balance point shift by 20 cm on increasing the resistance from the resistance box by 12.5Ω Find the value of unknown resistance.

 [Watch Video Solution](#)

103. A standard cell emf 1.08 V is balanced by the potential difference across 91 cm of a meter long wire applied by a cell of emf 2 V through a series resistor of resistance 2Ω . The internal resistance of the cell is zero. Find the resistance per unit length of the potentiometer wire.

 [Watch Video Solution](#)

104. There is a potentiometer wire of length 1200 cm and 60 mA current is flowing in it. A battery of emf 5V and internal resistance of 20 ohm is balanced on potentiometer wire with balancing length 1000 cm. Find the resistance of the potentiometer wire



 [Watch Video Solution](#)

105. There is a potentiometer wire of length 1200 cm and 60 mA current is flowing in it. A battery of emf 5V and internal resistance of 20 ohm is balanced on potentiometer wire with balancing length 1000 cm. if a voltmeter is connected across the cell, the balancing length decreasing by 20 cm find reading of the voltmeter



[Watch Video Solution](#)

106. There is a potentiometer wire of length 1200 cm and 60 mA current is flowing in it. A battery of emf 5V and internal resistance of 20 ohm is balanced on potentiometer wire with balancing length 1000 cm. if a voltmeter is connected across the cell, the balancing length decreasing by 20 cm find reading of the voltmeter



[Watch Video Solution](#)

107. Derive the expression for internal resistance of a cell.



[Watch Video Solution](#)

108. What is the principle of a potentiometer? With the help of circuit diagram, explain the use of potentiometer to measure internal resistance of a given primary cell.



[Watch Video Solution](#)

109. Using Kirchoff's law, derive the condition for the balance of a Wheatstone bridge circuit.



[Watch Video Solution](#)

110. Using Kirchoff's law, derive the condition for the balance of a Wheatstone bridge circuit.



 [Watch Video Solution](#)

111. State and explain Kirchhoff's laws.

 [Watch Video Solution](#)

112. State Wheatstone bridge principle. Use kirchoff'slaws to obtain the relation btween the resistance in four arms of the Wheatstone bridge by drawing circuit diagram.

 [Watch Video Solution](#)

113. What is the principle of a metre bridge ? With a circuit diagram, explain how a metre bridge can be used to determine an unknown resistance of a given wire.

 [Watch Video Solution](#)

114. Deduce the conditions for balance in a wheatstone bridge. Using the principle of Wheatstone bridge, describe the method to determine the specific resistane of a wire in the laboratory. Draw the circuit diagram and write the formula used. Write any two important precautions you would observe, while performing the experiment.

 [Watch Video Solution](#)

115. What is Wheatstone bridge? Deduce the condition for which Wheatstone bridge is balanced.

 [Watch Video Solution](#)

Exercise

1. State and explain Kirchhoff's laws.

 [Watch Video Solution](#)

2. State and explain Kirchhoff's laws.

 [Watch Video Solution](#)

3. State and explain Kirchhoff's laws.

 [Watch Video Solution](#)

4. Derive condition of a balanced wheatstone's bridge.

 [Watch Video Solution](#)

5. Using Kirchhoff's law, derive the condition for the balance of a Wheatstone bridge circuit.

 [Watch Video Solution](#)

6. Using Kirchoff's law, derive the condition for the balance of a Wheatstone bridge circuit.

 [Watch Video Solution](#)

7. State Wheatstone bridge principle. Use kirchoff's laws to obtain the relation between the resistance in four arms of the Wheatstone bridge by drawing circuit diagram.

 [Watch Video Solution](#)

8. State Wheatstone bridge principle. Use kirchoff's laws to obtain the relation between the resistance in four arms of the Wheatstone bridge by drawing circuit diagram.

 [Watch Video Solution](#)

9. Draw the circuit diagram of Wheatstone bridge. Under what condition, no current flows through its galvanometer (balanced condition)?

 [Watch Video Solution](#)

10. Draw the circuit diagram of Wheatstone bridge. Under what condition, no current flows through its galvanometer (balanced condition)?

 [Watch Video Solution](#)

11. With help of circuit diagram, explain how a meter bridge can be used to find unknown resistance of a given wire.

 [Watch Video Solution](#)

12. Explain the principle of Wheatstone bridge for determining and unknown resistance. How is it realised in actual practice in the

laboratory?

 [Watch Video Solution](#)

13. What is a slide wire bridge? How can you find unknown resistance by it?

 [Watch Video Solution](#)

14. With help of circuit diagram, explain how a meter bridge can be used to find unknown resistance of a given wire.

 [Watch Video Solution](#)

15. Draw a circuit diagram for determining the unknown resistance R using meter bridge. Explain briefly its working, giving the necessary formula used.

 [Watch Video Solution](#)

16. Draw a circuit diagram of a meter bridge and write the necessary mathematical relation used to determine the value of unknown resistance. Why cannot such arrangement be used for measuring very low resistances?

 [Watch Video Solution](#)

17. Draw a circuit diagram of a metre bridge arranged to find the value of an unknown resistance. Write the formula used.

 [Watch Video Solution](#)

18. Draw a circuit diagram of a metre bridge arranged to find the value of an unknown resistance. Write the formula used.

 [Watch Video Solution](#)

19. Draw a neatly labelled diagram of a potentiometer and explain its principle.

 [Watch Video Solution](#)

20. Explain the principle on which the working of a potentiometer is based. Why is the use of potentiometer preferred over that of a voltmeter for measuring the e.m.f. of a cell.

 [Watch Video Solution](#)

21. What is potentiometer? With the help of circuit diagram, explain how a potentiometer can be used to compare the emf of two primary cells.

 [Watch Video Solution](#)

22. Define e.m.f of a cell. How can you compare the e.m.f of the cells using potentiometer.



[Watch Video Solution](#)

23. State the principle of a potentiometer.



[Watch Video Solution](#)

24. What is potentiometer? With the help of circuit diagram, explain how a potentiometer can be used to compare the emf of two primary cells.



[Watch Video Solution](#)

25. Explain the principle of a potentiometer. How will you compare the e.m.f. of two primary cells by using potentiometer? Explain with proper circuit diagram.



[Watch Video Solution](#)

26. Define e.m.f of a cell. How can you compare the e.m.f of the cells using potentiometer.

 [Watch Video Solution](#)

27. Define internal resistances of a cell. explain how the internal resistance of a primary cell can be determined using a Potentiometer.

 [Watch Video Solution](#)

28. What is the principle of a potentiometer? With the help of circuit diagram, explain the use of potentiometer to measure internal resistance of a given primary cell.

 [Watch Video Solution](#)

29. What is the principle of a potentiometer? With the help of circuit diagram, explain the use of potentiometer to measure internal resistance of a given primary cell.

 [Watch Video Solution](#)

30. How will you use potentiometer to determine internal resistances of a cell?

 [Watch Video Solution](#)

31. What is the principle of a potentiometer? With the help of circuit diagram, explain the use of potentiometer to measure internal resistance of a given primary cell.

 [Watch Video Solution](#)

32. Using Kirchoff's law, derive the condition for the balance of a Wheatstone bridge circuit.

 [Watch Video Solution](#)

33. Using Kirchoff's law, derive the condition for the balance of a Wheatstone bridge circuit.

 [Watch Video Solution](#)

34. Using Kirchoff's law, derive the condition for the balance of a Wheatstone bridge circuit.

 [Watch Video Solution](#)

35. Derieve condition of a balanced wheatstone's bridge.

 [Watch Video Solution](#)

36. With help of circuit diagram, explain how a meter bridge can be used to find unknown resistance of a given wire.

 [Watch Video Solution](#)

37. Explain the principle of Wheatstone bridge for determining and unknown resistance. How is it realised in actual practice in the laboratory?

 [Watch Video Solution](#)

38. What is Wheatstone bridge? Deduce the condition for which Wheatstone bridge is balanced.

 [Watch Video Solution](#)

39. What is potentiometer? With the help of circuit diagram, explain how a potentiometer can be used to compare the emf of two primary cells.

 [Watch Video Solution](#)

40. Explain the principle of a potentiometer. How will you compare the e.m.f. of two primary cells by using potentiometer? Explain with proper circuit diagram.

 [Watch Video Solution](#)

41. Explain the principle of a potentiometer. How will you compare the e.m.f. of two primary cells by using potentiometer? Explain with proper circuit diagram.

 [Watch Video Solution](#)

42. Draw circuit diagram for the comparison of e.m.fs of two cells with the help of a potentiometer.

 [Watch Video Solution](#)

43. How will you use potentiometer to determine internal resistances of a cell?

 [Watch Video Solution](#)

44. Explain the principle of a potentiometer. How will you compare the e.m.f. of two primary cells by using potentiometer? Explain with proper circuit diagram.

 [Watch Video Solution](#)