



# PHYSICS


## BOOKS - MODERN PUBLICATION

### SEMICONDUCTOR DEVICES

#### Example

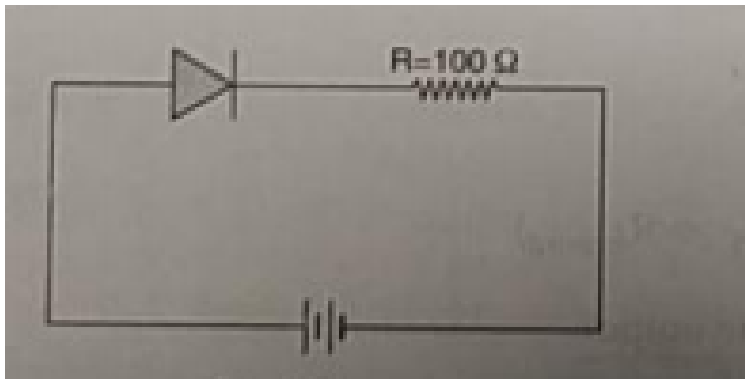1. Figure Shows a diode connected to an external resistance and an e.m.f. Assuming that the barrier potential developed in diode


is 0.5 V, obtain the value of current in the circuit in milliamperere.



[Watch Video Solution](#)

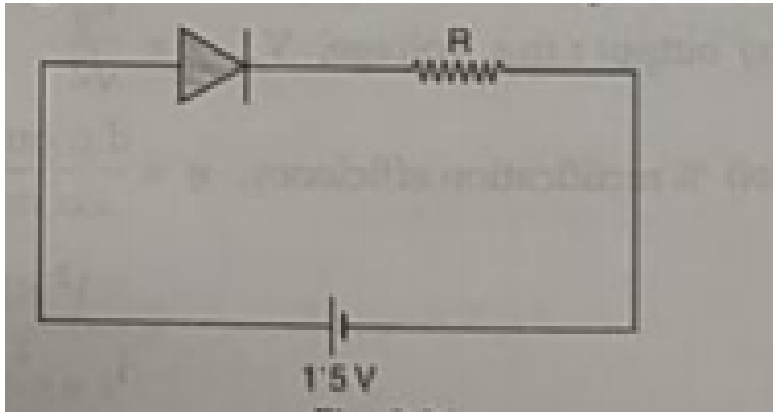2. The diode used in the circuit shown in the adjacent figure has a constant voltage drop of 0.5V at all currents and a maximum power rating of 100mW. What should be the value of

resistor  $R$  connected in series with the diode for obtaining maximum current?




[Watch Video Solution](#)

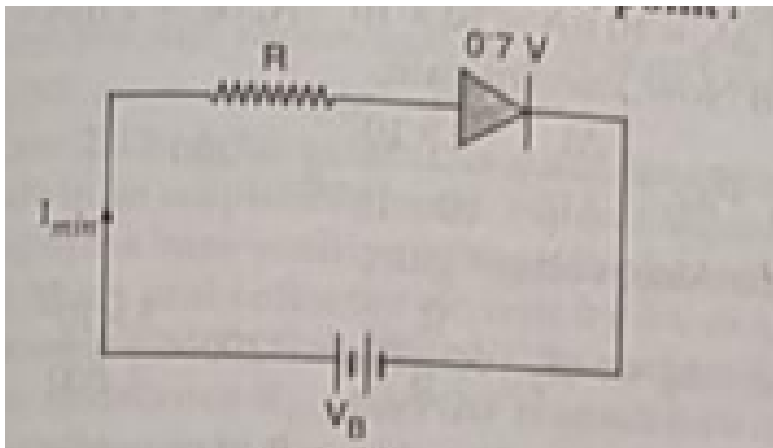3. Assume that the silicon diode in the circuit shown in fig. requires a minimum current of  $1\text{mA}$  to be above the knee point ( $0.7\text{V}$ ) of its I-V

characteristics. Also assume that the voltage across the diode is independent of current above the knee point.


If  $V_B = 5V$ , what should be the maximum value of  $R$  so that the voltage is above the knee point?



[Watch Video Solution](#)

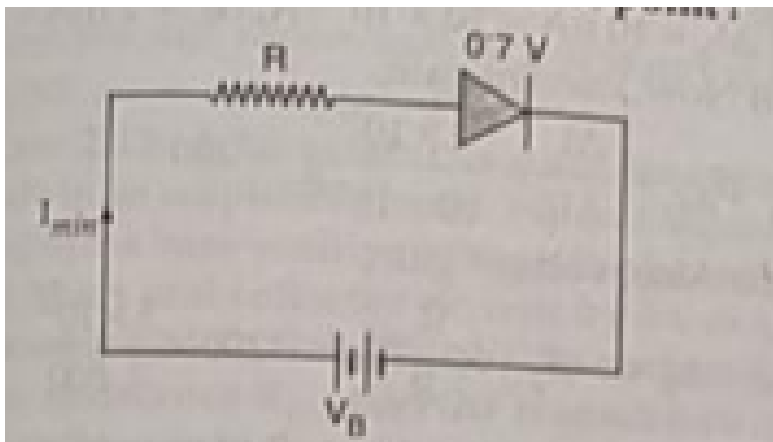4. Assume that the silicon diode in the circuit shown in fig. requires a minimum current of 1mA to be above the knee point (0.7V) of its I-V characteristics. Also assume that the voltage across the diode is independent of current above the knee point.

If  $V_B = 5V$ , what should be the value of R to establish the current of 5mA in the circuit?






5. Assume that the silicon diode in the circuit shown in fig. requires a minimum current of 1mA to be above the knee point (0.7V) of its I-V characteristics. Also assume that the voltage across the diode is independent of current above the knee point.

What is the power dissipated in the resistance  $R$  and in the diode, when a current of 5mA

flows in the circuit at  $V_B = 6V$ ?

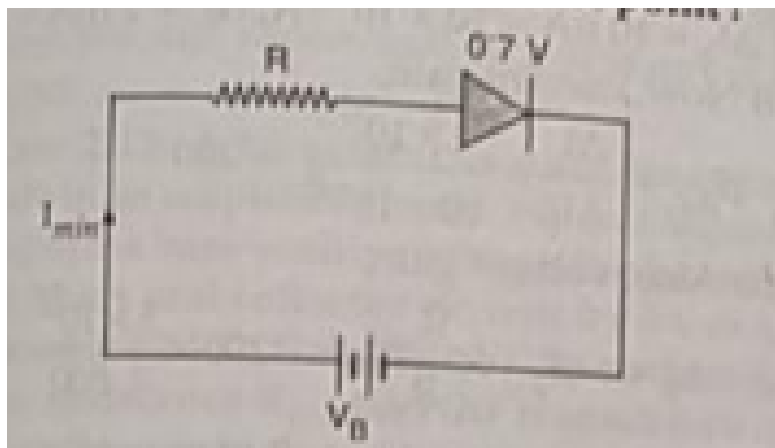


[Watch Video Solution](#)

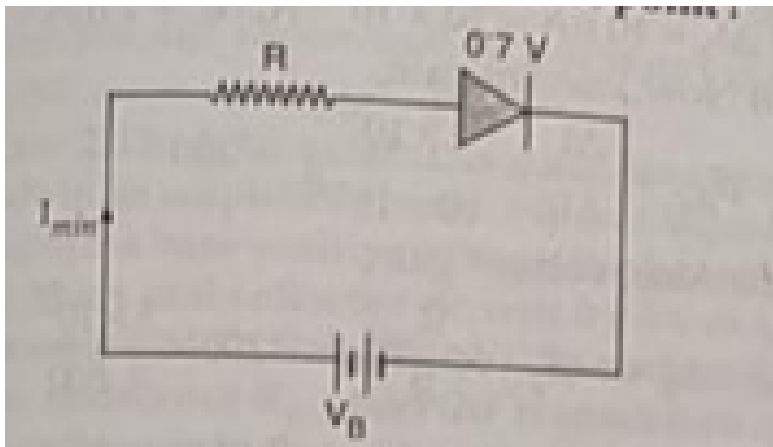6. Assume that the silicon diode in the circuit shown in fig. requires a minimum current of 1mA to be above the knee point (0.7V) of its I-V characteristics. Also assume that the voltage

across the diode is independent of current above the knee point.

If  $R = 1k\Omega$ , what is the minimum voltage  $V_B$  required to keep the diode above the knee point?



[Watch Video Solution](#)



7. In a half wave rectifier, a p-n junction diode with internal resistance 20 ohm is used. If the load resistance of 2 kilohm is used in the circuit, then find the efficiency of this half wave rectifier.



[Watch Video Solution](#)

8. For a transistor working as common base amplifier, current gain is 0.96. If the emitter current is 7.2 mA, calculate the base current.





[Watch Video Solution](#)

9. For a common emitter amplifier , current gain is 70 . If the emitter is 8.8 mA , calculate the collector and base current . Also calculate current gain , when transistor is worked on common base amplifier.



[Watch Video Solution](#)

10. The base current of a transistor is  $105\mu A$  and collector current is 2.05mA.

Determine the value of  $\beta$ ,  $I_e$  and  $\alpha$



[Watch Video Solution](#)

**11.** A change of  $20\mu A$  in the base current produces a change of  $0.5mA$  in the collector current. Calculate  $\beta_{ac}$



[Watch Video Solution](#)

**12.** In a silicon transistor, a change of  $7.79\text{ mA}$  in the emitter current produces a change of

7.7 mA in the collector current. What change in the base current is necessary to produce an equivalent change in the collector current?



[Watch Video Solution](#)

**13.** For a transistor amplifier, the collector load resistance  $R_L = 2k\Omega$  and the input resistance  $R_i = 1k\Omega$ . If the current gain is 50, calculate voltage gain of the amplifier.



[Watch Video Solution](#)

**14.** In a silicon transistor, the base current is changed by  $20\mu A$ . This results in a change of 0.02 V in base to emitter voltage and a change of 2mA in the collector current.

Find the input resistance,  $\beta_{ac}$  and transconductance of the transistor  $g_m$ .



**Watch Video Solution**

**15.** In a silicon transistor, the base current is changed by  $20\mu A$ . This results in a change of 0.02 V in base to emitter voltage and a change

of 2mA in the collector current.

This transistor is used as an amplifier in CE configuration with load resistance  $5k\Omega$ . What is the voltage gain of the amplifier.



[Watch Video Solution](#)

**16.** The input resistance of a silicon transistor is  $665\Omega$  when base current is changed by  $15\mu A$ , the collector current changes by 2mA. In a common emitter amplifier load resistance

is  $5k\Omega$ . Calculate transconductance ( $g_m$ ) & voltage gain ( $A_v$ ) of the amplifier.



**Watch Video Solution**

**17.** A transistor is used in common emitter mode in an amplifier circuit. When a signal of 24 mV (millivolt) is added to base emitter voltage, the base current changes by  $32\mu A$  (micro ampere) and collector current by 3.6 mA (milli ampere) and the load resistance is

4.8k $\Omega$  (kilo ohm). Calculate trans conductance

$g_m$



Watch Video Solution

**18.** A transistor is used in common emitter mode in an amplifier circuit. When a signal of 24 mV (millivolt) is added to base emitter voltage, the base current changes by 32 $\mu A$  (micro ampere) and collector current by 3.6 mA (milli ampere) and the load resistance is 4.8k $\Omega$  (kilo ohm). Calculate voltage gain.






Watch Video Solution

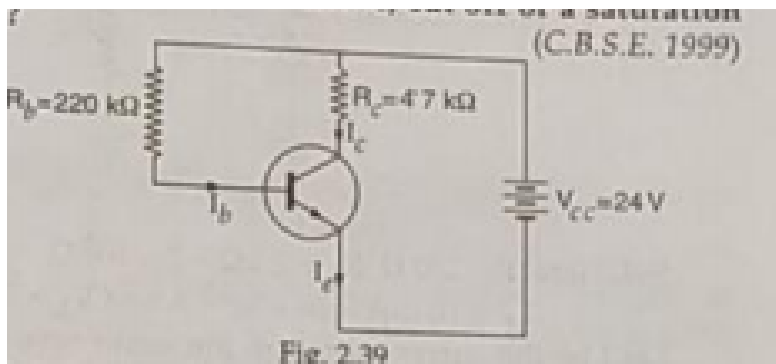19. In the circuit Fig. the value of beta is 200.

Find  $I_B$ ,  $V_{CE}$ ,  $V_{BE}$  and  $V_{BC}$ , when

$I_C = 2.5\text{mA}$ . The transistor is in active, cut off or saturation state.



Watch Video Solution

20. A potential barrier of 0.3 V exists across a P-N junction: If the depletion region is  $3 \times 10^{-7}$  m wide , what is the intensity of the electric field in this region?



[Watch Video Solution](#)

21. A potential barrier of 0.3 V exists across a P-N junction: If an electron with speed  $4 \times 10^5 \text{ m s}^{-1}$  approaches this P-N junction from the N-side, the find the speed with which

it will enter the P-side. Given mass of electron


$$9.1 \times 10^{-31} \text{ kg}$$



[Watch Video Solution](#)

**22.** In figure what is the voltage needed to maintain 15V across the load resistance  $R_L$  of 2K, assuming that the series resistance R is  $200\Omega$  and the zener requires a minimum current of 10mA to work satisfactorily? What is

the zener rating required?

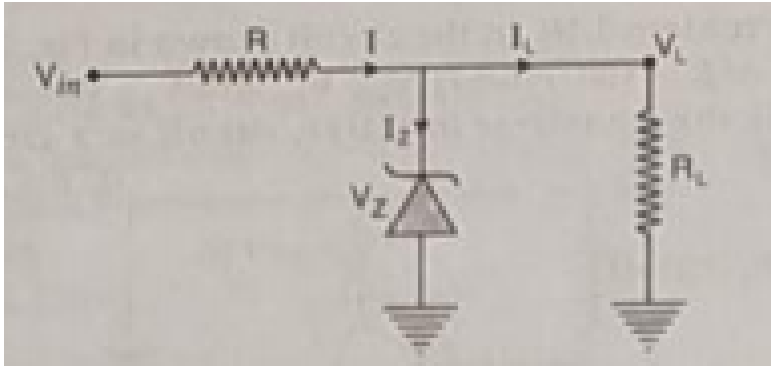

[▶ Watch Video Solution](#)

**23.** In a p-n-p transistor circuit, the collector current is 10mA , If 90% of the electrons emitted reach the collector , what is base current ?

[▶ Watch Video Solution](#)

24. A n-p-n transistor is connected in common emitter configuration in which collector supply is 9V and the voltage drop across the load resistance of  $700\Omega$  connected to the collector circuit is 0.7V. If the current amplification factor alpha is  $25/26$ , determine collector emitter voltage and base current. If the input resistance of the transistor is  $100\Omega$ , calculate the voltage gain and the power gain.




[Watch Video Solution](#)

25. An amplifier is represented by the circuit shown in Fig. Here  $r_i$  is the input resistance of the amplifier and the voltage  $V_i$  is appearing across it. This voltage is amplified by a factor  $A_V$  and appears across the load as voltage  $V_0$

An external voltage  $V_s(s)$  is applied at the input terminals of the amplifier via series resistance  $R_s(s)$ . What will be the apparent gain  $A_V( = V_0 / V_s)$  of the amplifier in terms

of  $A_V$ ,  $R_S$  and  $r_i$ .

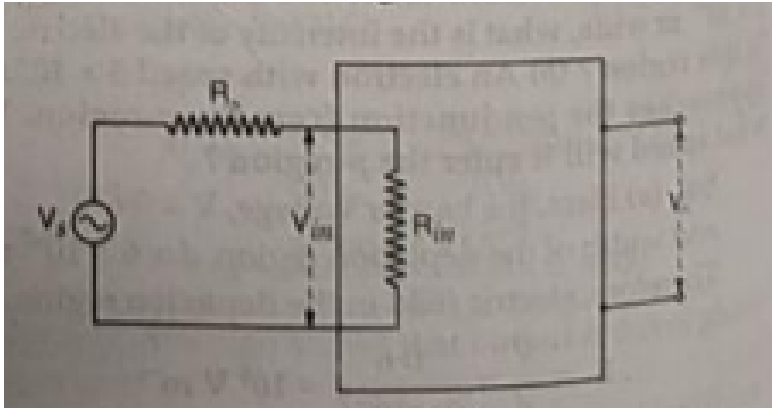

[▶ Watch Video Solution](#)

26. What do you understand by potential barrier?

[▶ Watch Video Solution](#)

**27.** Explain how the width of depletion layer in p-n junction diode changes when the junction is reverse biased.



**Watch Video Solution**

**28.** Can the potential barrier across a p-n junction be measured by simply connecting a voltmeter across the junction?



**Watch Video Solution**



**29.** What do you mean by depletion region in a p-n junction ?



**Watch Video Solution**

**30.** How does the junction width change when a p-n junction is forward biased?



**Watch Video Solution**

**31.** What is the effect of forward biasing on the resistance of a p-n junction?



**Watch Video Solution**

**32.** Which type of biasing gives a semiconductors diode vary high resistance?



**Watch Video Solution**

**33.** Fill in the blanks:

When a p -n junction is forward biased, then the motion of charge carriers across the barrier is due to ..... (drift, diffusion) and when it is reverse biased, then the motion of charge carriers is due to..... (drift, diffusion).



**Watch Video Solution**

**34.** Fill in the blanks:

An ideal p-n junction diode conducts, when

\_\_\_\_\_ biased and does not conduct, when  
..... Biased. (Forward, reverse)



[Watch Video Solution](#)

**35.** Draw a circuit diagram with a p-n junction in forward bias.



[Watch Video Solution](#)

**36.** Draw a circuit diagram with a p-n junction at reverse bias.



Watch Video Solution

37. In the figure is the diode D forward or reverse biased?



Watch Video Solution

38. In the figure is the diode D forward or reverse biased?



[Watch Video Solution](#)

**39.** Under what condition does a junction diode work as open switch?

[Watch Video Solution](#)

**40.** What is a zener diode? How is it symbolically represented? With the help of a

circuit diagram, explain the use of zener diode as a voltage stabilizer



[Watch Video Solution](#)

**41.** How reverse current suddenly increases at the break down voltage in case of a junction diode?



[Watch Video Solution](#)

**42.** What is Zener breakdown?



[Watch Video Solution](#)

**43.** Draw the

symbol and

the reverse bias I-V characteristics of a zener diode. Explain briefly, which property of the characteristics enables us to use zener diode as voltage regulator.



[Watch Video Solution](#)



**44.** Write in brief about Photo-diodes.



**Watch Video Solution**

**45.** How is the band gap  $E_g$  of a photodiode related to the maximum wavelength  $\lambda_m$  that can be detected by it?



**Watch Video Solution**

**46.** Draw a circuit diagram to show how a photodiode is biased.



**Watch Video Solution**

**47.** What is light emitting diode (LED)?



**Watch Video Solution**

**48.** State the factors, which controls wavelength of light, emitted by a LED.



[Watch Video Solution](#)

**49.** State the factors, which controls wavelength of light, emitted by a LED.



[Watch Video Solution](#)

**50.** Name the diode for which the output voltage is a regulated voltage.



[Watch Video Solution](#)

**51.** Name the diode that emits spontaneous radiation, when forward biased.



**Watch Video Solution**

**52.** What is a solar cell? What is its working principle? Write short note on the making of solar cells and also give its uses.



**Watch Video Solution**

**53.** Write the full form of transistor.



**Watch Video Solution**

**54.** Why transistor is so called?



**Watch Video Solution**

**55.** How P-N-P and N-P-N transistor are represented symbolically?




**Watch Video Solution**

**56.** Can two P-N junction diodes back to back works as P-N-P transistor?




**Watch Video Solution**

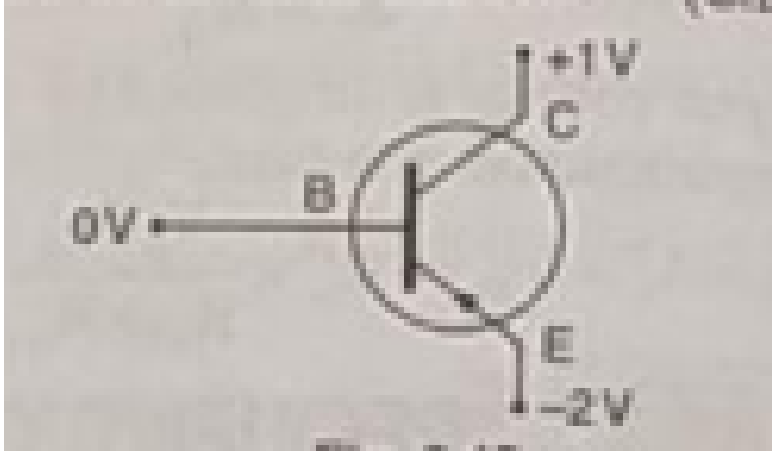**57.** In the figure the collector forward or reverse biased?



Watch Video Solution

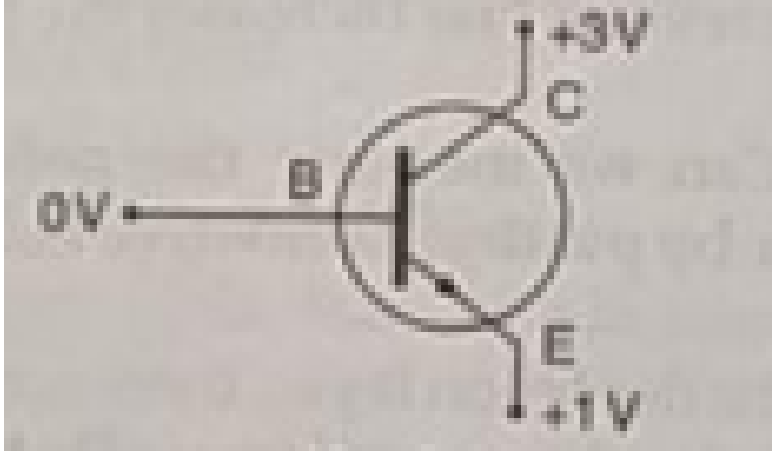
**58.** In the figure the emitter forward bias or reverse bias?



Watch Video Solution

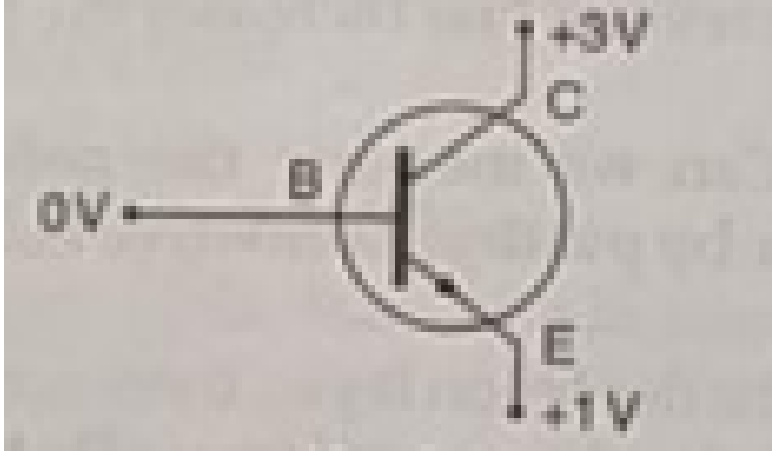**59.** In the figure the collector forward or reverse biased?





[▶ Watch Video Solution](#)

60. What is the relation among emitter current ( $I_E$ ) collector current ( $I_C$ ) and base current ( $I_B$ ) for a transistor circuit? Which one of the three has the smallest magnitude?

[▶ Watch Video Solution](#)

**61.** Fill in the blanks: The base of transistor is always ..... and ..... doped, compared to the emitter and collector. (thinner, thicker, lightly, heavily)



**Watch Video Solution**

**62.** Fill in the blanks: For using a transistor as an amplifier, the base emitter junction is ..... Biased and the base collector junction

is ..... biased. (forward, reverse, forward, reverse)



[Watch Video Solution](#)

**63.** Define input resistance of a transistor used in its common emitter configuration.



[Watch Video Solution](#)

**64.** Define d.c. current gain in common base and common emitter amplifier. Also find a

relation between them.



[Watch Video Solution](#)

**65.** Write the relation between current gains  $\alpha$  and  $\beta$



[Watch Video Solution](#)

**66.** define the trans-conductance of a transistor.



[Watch Video Solution](#)

**67.** What kinds of biasing are required to the collector and base of a transistor in a common emitter amplifier?



**Watch Video Solution**

**68.** Why is common emitter amplifier preferred over common base amplifier?



**Watch Video Solution**

**69.** Which one will you prefer, a common base or a common emitter amplifier?



**Watch Video Solution**

**70.** Portable radio receiver sets are generally not made with electron tube circuits. Why?



**Watch Video Solution**

71. Explain the advantages and disadvantages of semiconducting devices as compared to vacuum tube devices.



[Watch Video Solution](#)

72. State two disadvantages of semiconductor devices.



[Watch Video Solution](#)

**73.** What is an integrated circuit?



**Watch Video Solution**

**74.** Explain the two processes involved in the formation of a p-n junction diode. Hence define the term "barrier potential".



**Watch Video Solution**



75. Why can't we take one slab of p-type semiconductor and physically join it to another slab of n-type semiconductor to get a p-n junction?



[Watch Video Solution](#)

76. Explain the terms depletion layer and potential barrier for a junction diode.



[Watch Video Solution](#)

**77.** What do you mean by depletion region in a p-n junction ?



**Watch Video Solution**

**78.** In the depletion region of a diode



**Watch Video Solution**

**79.** Explain how the depletion layer and barrier potential are formed in pn junction diode ?





[Watch Video Solution](#)

**80.** How does the width of the depletion region of a p-n junction vary if the reverse bias applied to it decreases?



[Watch Video Solution](#)

**81.** The resistance of a p-n junction is low, when forward biased and is high, when reverse is biased. Explain.



[Watch Video Solution](#)

**82.** How is forward biasing different from reverse biasing in a p-n junction diode?




**Watch Video Solution**

**83.** Explain forward bias and reverse bias of the junction diode.



**Watch Video Solution**

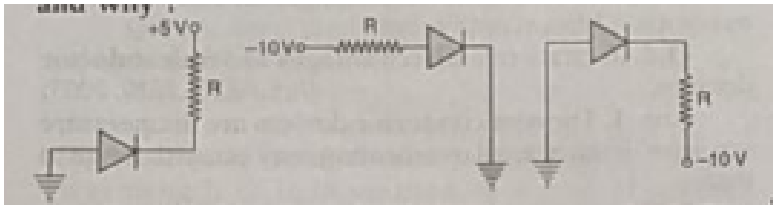
**84.** In the following circuits, which of the diodes is forward-biased and which is reverse-biased and why?



[Watch Video Solution](#)

**85.** In the following circuits, which of the diodes is forward-biased and which is reverse-

biased and why?

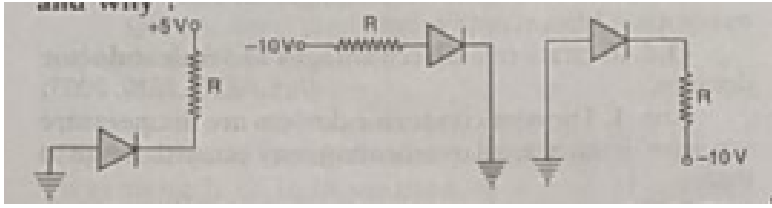


[Watch Video Solution](#)

**86.** Which type of biasing gives a semiconductor diode very high resistance?



[Watch Video Solution](#)

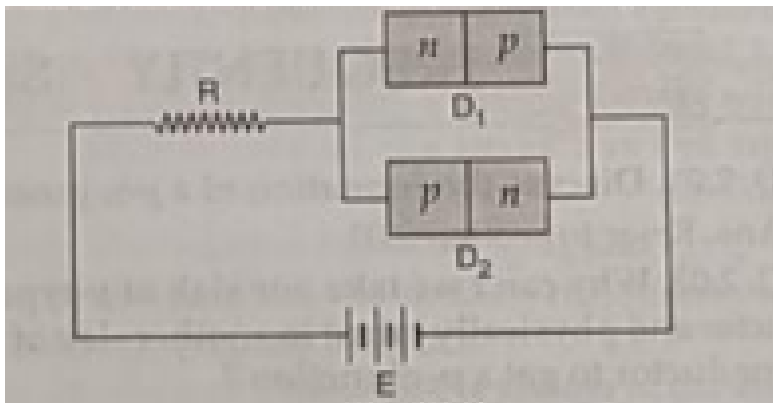**87.** Show in figure two p-n junction diodes along-with a resistanc  $R$  and a d.c. battery  $E$ . Indicate the path and direction of flow of appreciable current in the circuit.



**Watch Video Solution**

**88.** The following table provides the set of values, of  $V$  and  $I$ , obtained for a given diode. Assuming the characteristics to be nearly linear, over this range, calculate the forward and reverse bias resistance of the given diode.

Forward biasing		Reverse biasing	
$V$	$I$	$V$	$I$
2 V	60 mA	0 V	0 $\mu$ A
24 V	80 mA	-2 V	-0.25 $\mu$ A

 [Watch Video Solution](#)

**89.** Draw the graph showing the variation of current with voltage for a p-n junction diode.





[Watch Video Solution](#)


**90.** Draw the voltage current characteristics of a p-n junction bias?



[Watch Video Solution](#)

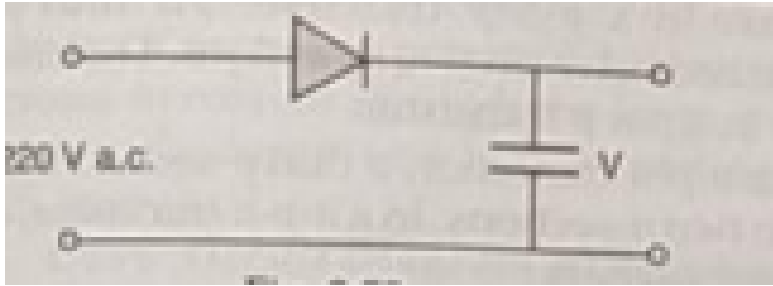**91.** A diode is connected to 220V (r.m.s) a.c. in series with a capacitor as shown in the figure.

What is the voltage  $V$  across the capacitor is



[Watch Video Solution](#)

**92.** Draw the circuit diagram of a half wave rectifier using a junction diode.



[Watch Video Solution](#)

**93.** Draw a labelled circuit diagram of a full wave rectifier using junction diodes.



**Watch Video Solution**

**94.** With the help of circuit diagram explain working of junction diode as full wave rectifier.



**Watch Video Solution**

**95.** State the function of a zener diode in a circuit.



**Watch Video Solution**

**96.** Which special type of diode can act as a voltage regulator? Give the symbol of this diode and draw the general shape of its V-I characteristics.



**Watch Video Solution**

**97.** Write briefly, how a Zener diode acts as voltage regulator.



**Watch Video Solution**

**98.** How do we choose the semiconductor, to be used in LED, if the emitted radiation is to be in the visible region?



**Watch Video Solution**

**99.** The current in the forward bias is known to be more ( $\sim mA$ ) than the current in the reverse bias ( $\sim \mu A$ ). What is the reason then to operate the photodiodes in reverse bias?



**Watch Video Solution**

**100.** What is light emitting diode (LED)?



**Watch Video Solution**

**101.** What the help of a diagram, show that biasing of a light emitting diode (LED). Give its two advantages over conventional incandescent lamps.



**Watch Video Solution**

**102.** With the help of an activity, explain the method of inducing an electric current in a coil with a moving magnet. Mention one

practical application of electromagnetic induction.



[Watch Video Solution](#)

**103.** Represent symbolically Zener diode, photodiode, n-p-n and p-n-p transistors.



[Watch Video Solution](#)

**104.** Write the function of base region of a transistor. Why is the region made thin and



slightly doped?



[Watch Video Solution](#)

**105.** How does the collector current change in a junction transistor, if the base region has larger width?



[Watch Video Solution](#)

**106.** In a transistor, forward bias is always small as compared to the reverse bias. Why?



[Watch Video Solution](#)

**107.** In a transistor, doping level in base is increased slightly. Now will it affect collector current?



[Watch Video Solution](#)

**108.** In a transistor, doping level in base is increased slightly. Now will it affect base current?



[Watch Video Solution](#)

**109.** Explain the following A transistor is a temperature - sensitive device.



[Watch Video Solution](#)

**110.** Explain the following A transistorised circuit starts working immediately after the circuit is switched on, whereas a vacuum tube circuit takes some time to start working.



[Watch Video Solution](#)

**111.** How will you test in a simple way whether the transistor is spoiled or in working order?



**Watch Video Solution**

**112.** What is transistor ? Give the symbols of n-p-n and p-n-p transistor.



**Watch Video Solution**

**113.** What is transistor? Give symbols of p-n-p and n-p-n transistor.



**Watch Video Solution**

**114.** Discuss the working of p-n-p transistor as an amplifier in common emitter mode.



**Watch Video Solution**

**115.** Why a transistor cannot be used as a rectifier ?




**Watch Video Solution**

**116.** Consider a npn transistor with its base-emitter junction forward biased and collector base junction reverse biased. Which of the following statements are true?



**Watch Video Solution**

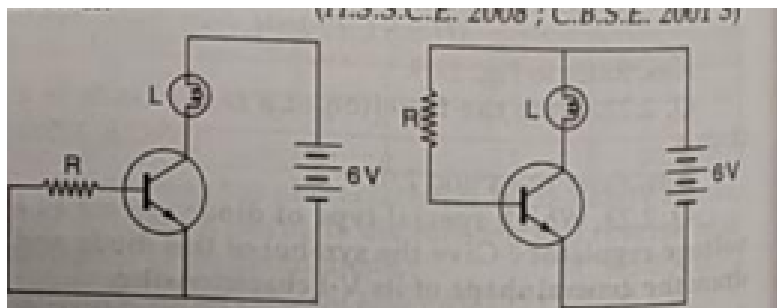
**117.** In only one of the circuits given below, the lamp L lights. Which circuit is it? Given reason for your answer.



[Watch Video Solution](#)

**118.** In the circuit shown in Fig.a voltage V is connected across lamp L. What changes would occur at lamp and the voltage V, if the

resistance R is reduced in value?

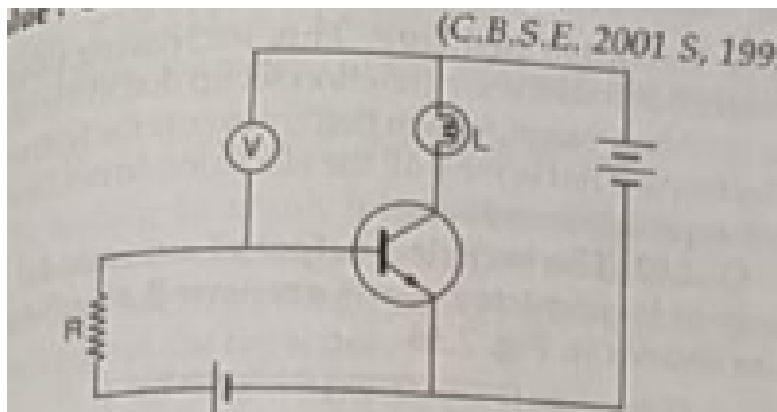

[▶ Watch Video Solution](#)

**119.** Draw circuit diagram of common base amplifier using p-n-p transistor.

[▶ Watch Video Solution](#)



**120.** Discuss the working of p-n-p transistor as an amplifier in common emitter mode.



**Watch Video Solution**

**121.** Discuss the working of p-n-p transistor as an amplifier in common emitter mode.



**Watch Video Solution**

**122.** Why the output voltage is out of phase with the input voltage in a common emitter

transistor amplifier?



[Watch Video Solution](#)

**123.** Draw the circuit of a transistor as an amplifier.



[Watch Video Solution](#)

**124.** Define current gains,  $\alpha$  and  $\beta$  of a transistor.



[Watch Video Solution](#)

**125.** Discuss the working of n-p-n transistor as an amplifier in common base mode.



**Watch Video Solution**

**126.** Write the relation between current gains  $\alpha$  and  $\beta$



**Watch Video Solution**

**127.** A transistor has a current gain of 30. If the collector resistance is  $6k\Omega$ , input resistance is  $1k\Omega$  calculate its voltage gain.



[Watch Video Solution](#)

**128.** AC current gain for transistor in common emitter amplifier is 20. If input and output resistances are  $2k\Omega$  and  $5K\Omega$  respectively, find: Voltage gain



[Watch Video Solution](#)

**129.** AC current gain for transistor in common emitter amplifier is 20. If input and output resistances are  $2k\Omega$  and  $5K\Omega$  respectively, find: Power gain



**Watch Video Solution**

**130.** What is an oscillator ? Draw a labelled circuit diagram for an oscillator using PNP transistor. What is the function of feed back coil in it ? Write an expression for the

frequency of waves produced by it. What is the use of waves produced by it ?



[Watch Video Solution](#)

**131.** What is an oscillator ? Draw a labelled circuit diagram for an oscillator using PNP transistor. What is the function of feed back coil in it ? Write an expression for the frequency of waves produced by it. What is the use of waves produced by it ?



[Watch Video Solution](#)

**132.** Explain the advantages and disadvantages of semiconducting devices as compared to vacuum tube devices.



**Watch Video Solution**

**133.** Explain the advantages and disadvantages of semiconducting devices as compared to vacuum tube devices.



**Watch Video Solution**

**134.** In a p-n junction diode, the current  $I$  can be expressed as  $I = I_0 \exp\left(\frac{eV}{2k_B T}\right)$  where  $I_0$  is called the reverse saturation current,  $V$  is the voltage across the diode and is positive for forward bias and negative for reverse bias, and  $I$  is the current through the diode,  $k_B$  is the Boltzmann constant  $\left(8.6 \times 10^{-5} \frac{eV}{K}\right)$  and  $T$  is the absolute temperature. If for a given diode  $I_0 = 5 \times 10^{-12} A$  and  $T = 300 K$ , then - What will be the increase in the current if the voltage across the diode is increased from  $0.6 V$  to  $0.7 V$ ?





Watch Video Solution

**135.** In a p-n junction diode, the current  $I$  can be expressed as  $I = I_0 \left( \exp\left(\frac{eV}{2k_B T}\right) - 1 \right)$  where  $I_0$  is called the reverse saturation current,  $V$  is the voltage across the diode and is positive for forward bias and negative for reverse bias, and  $I$  is the current through the diode,  $k_B$  is the Boltzmann constant ( $8.6 \times 10^{-5}$  eV/K) and  $T$  is the absolute temperature. If for a given diode  $I_0 = 5 \times 10^{-12}$  A and  $T =$

300 K, then - What will be the forward current at a forward voltage of 0.6 V?



[Watch Video Solution](#)

**136.** In a p-n junction diode, the current  $I$  can be expressed as  $I = I_0 \exp\left(\frac{eV}{2k_B T}\right)$  where  $I_0$  is called the reverse saturation current,  $V$  is the voltage across the diode and is positive for forward bias and negative for reverse bias, and  $I$  is the current through the diode,  $k_B$  is the Boltzmann constant  $\left(8.6 \times 10^{-5} \frac{eV}{K}\right)$  and  $T$

is the absolute temperature. If for a given diode  $I_0 = 5 \times 10^{-12} \text{ A}$  and  $T = 300 \text{ K}$ , then -  
What is the dynamic resistance when the voltage is increased to  $0.7 \text{ V}$  from  $0.6 \text{ V}$ ?



[Watch Video Solution](#)

**137.** In a p-n junction diode, the current  $I$  can be expressed as  $I = I_0 \left( \exp\left(\frac{eV}{2k_B T}\right) - 1 \right)$  where  $I_0$  is called the reverse saturation current,  $V$  is the voltage across the diode and is positive for forward bias and negative for

reverse bias, and  $I$  is the current through the diode,  $k_B$  is the Boltzmann constant ( $8.6 \times 10^{-5}$  eV/K) and  $T$  is the absolute temperature. If for a given diode  $I_0 = 5 \times 10^{-12}$  A and  $T = 300$  K, then - What will be the current if reverse bias voltage changes from 1 V to 2 V?



[Watch Video Solution](#)

**138.** An n-type semiconductor is the one which has excess of free electrons and p-type semiconductor is deficient in these. When a p-

n junction is formed, the electrons should flow from n to p region. But all the electrons do not do so. Explain, why.



[Watch Video Solution](#)

**139.** The output  $E$  of an alternating voltage supply of frequency 50 Hz is shown in Fig.


From this Fig, state

(i) value of time  $t_1$

(ii) peak voltage  $E_0$  (iii) root mean square

voltage  $E_v$

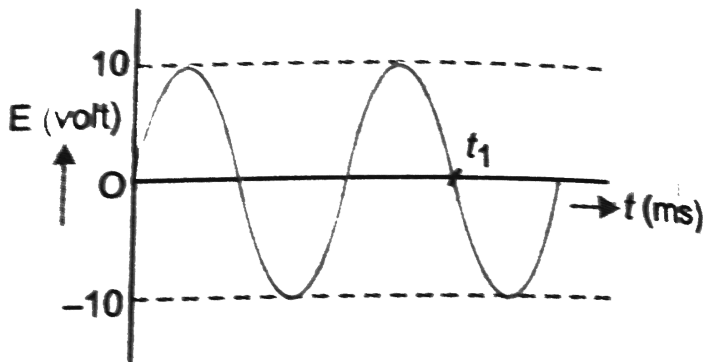(iv) mean supply is connected in series with a resistance of  $2.4\Omega$ , calculate the mean power dissipated in the resistor.




[Watch Video Solution](#)

140. The output  $E$  of an alternating voltage supply of frequency 50 Hz is shown in Fig.

From this Fig, state

root mean square voltage  $E_v$

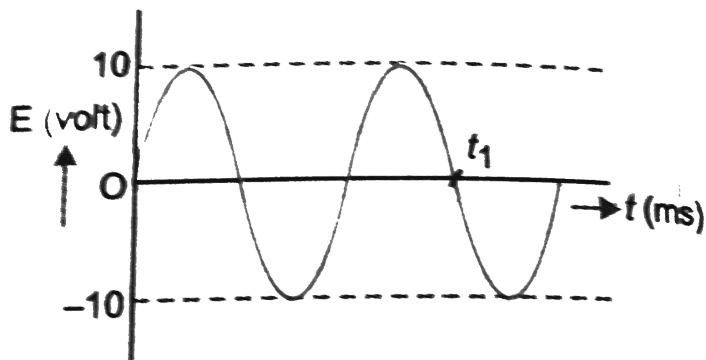

Watch Video Solution

**141.** The output  $E$  of an alternating voltage supply of frequency 50 Hz is shown in Fig.


From this Fig, state

(i) value of time  $t_1$

(ii) peak voltage  $E_0$  (iii) root mean square voltage  $E_v$

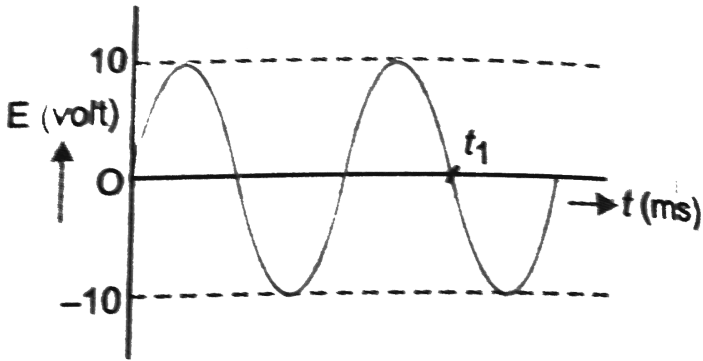(iv) mean supply is connected in series with a resistance of  $2.4\Omega$ , calculate the mean power dissipated in the resistor.





[Watch Video Solution](#)

**142.** A sinusoidal alternating voltage is to be rectified. Suggest one advantage of full-wave rectification as compared with half-wave rectification.




[Watch Video Solution](#)

**143.** An ideal transformer has 5,000 turns on its primary coil . It is to be used to convert a mains supply of 230 V.to an alternating voltage having a peak value of 9.0 V. Calculate the number of turns on the secondary coil.



[Watch Video Solution](#)

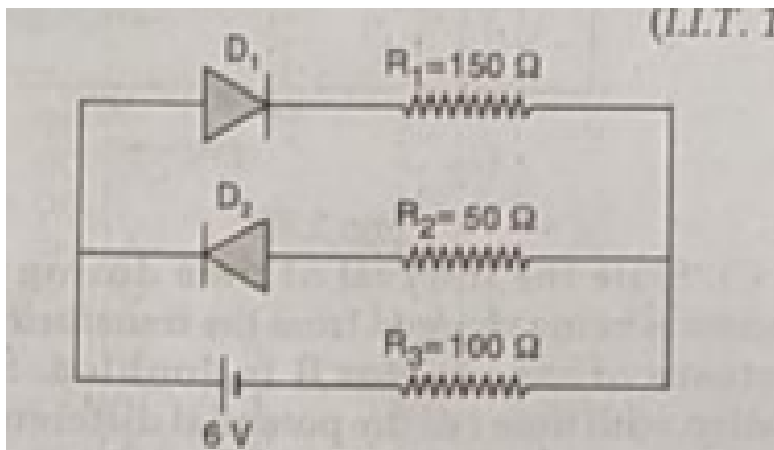**144.** The circuit shown in the figure contains two diodes each with a forward resistance of  $30\Omega$  and with infinite backward resistance. If the battery is  $3\text{ V}$ , the current through the  $100\Omega$  resistance (in ampere)



**Watch Video Solution**

**145.** A block diagram for an electronic sensor is shown in the figure



In figure name the boxes A and B.



[Watch Video Solution](#)

## Exercise

1. Explain the two processes involved in the formation of a p-n junction diode. Hence

define the term "barrier potential".



[Watch Video Solution](#)

2. Describe briefly, with the help of a diagram, the role of the two important processes involved in the formation of a p-n junction.



[Watch Video Solution](#)

3. What do you mean by depletion region in a p-n junction ?



**Watch Video Solution**

4. Explain the terms depletion layer and potential barrier for a junction diode.



**Watch Video Solution**

5. Explain the terms depletion layer and potential barrier for a junction diode.



**Watch Video Solution**

6. Explain the two processes involved in the formation of a p-n junction diode. Hence define the term "barrier potential".



[Watch Video Solution](#)

7. Explain forward bias and reverse bias of the junction diode.



[Watch Video Solution](#)

**8.** Explain forward bias and reverse bias of the junction diode.



**Watch Video Solution**

**9.** Explain forward bias and reverse bias of the junction diode.



**Watch Video Solution**



**10.** With the help of circuit diagram, explain the  $V-I$  characteristics of p-n junction diode in reverse biasing.



**Watch Video Solution**

**11.** Draw a circuit diagram with a p-n junction in forward bias.



**Watch Video Solution**

**12.** With the help of circuit diagram, explain the V-I characteristics of p-n junction diode in forward biasing.



**Watch Video Solution**

**13.** Draw a circuit diagram with a p-n junction in forward bias.



**Watch Video Solution**

**14.** Explain with the help of circuit diagram, how V-I characteristics of pn junction diode are obtained in forward biasing.



**Watch Video Solution**

**15.** With the help of circuit diagram, explain the V-I characteristics of p-n junction diode in reverse biasing.



**Watch Video Solution**

**16.** Define the term dynamic resistance of a p-n junction diode.



**Watch Video Solution**

**17.** Define Rectification. With the help a circuit diagram explain the working of p-n junction diode as a half wave rectifier.



**Watch Video Solution**

**18.** With the help of circuit diagram explain working of junction diode as full wave rectifier.



**Watch Video Solution**

**19.** Draw the circuit diagram of a half wave rectifier using a junction diode.



**Watch Video Solution**

**20.** Draw the circuit diagram of a half wave rectifier using a junction diode.



**Watch Video Solution**

**21.** What is rectifier ? Explain the working of junction diode as a full wave rectifier, with diagram.



**Watch Video Solution**

**22.** What is rectifier ? Explain the working of junction diode as a full wave rectifier, with diagram.



**Watch Video Solution**

**23.** With the help of suitable diagrams, explain the function of p-n junction diode as full wave rectifier.



**Watch Video Solution**

**24.** Draw a labelled circuit diagram of a full wave rectifier using junction diodes.



**Watch Video Solution**

**25.** With the help of circuit diagram explain working of junction diode as full wave rectifier.



**Watch Video Solution**



**26.** Draw a circuit diagram with a p-n junction in forward bias.



**Watch Video Solution**

**27.** Draw a circuit diagram with a p-n junction in reverse bias.



**Watch Video Solution**

**28.** What the help of a diagram, show that biasing of a light emitting diode (LED). Give its two advantages over conventional incandescent lamps.



**Watch Video Solution**

**29.** Name the semiconductor device that can be used to regulate an unregulated d.c. power supply. With the help of I-V characteristics of this device, explain its working principle.





[Watch Video Solution](#)

**30.** Name the device which is used as a voltage regulator. Draw the necessary circuit diagram and explain its working.



[Watch Video Solution](#)

**31.** What is a zener diode? How is it symbolically represented? With the help of a circuit diagram, explain the use of zener diode as a voltage stabilizer



**Watch Video Solution**

**32. What is Zener diode?**



**Watch Video Solution**

**33. Write briefly, how a Zener diode acts as voltage regulator.**




**Watch Video Solution**

**34.** What is the most common application of a zener diode?



**Watch Video Solution**

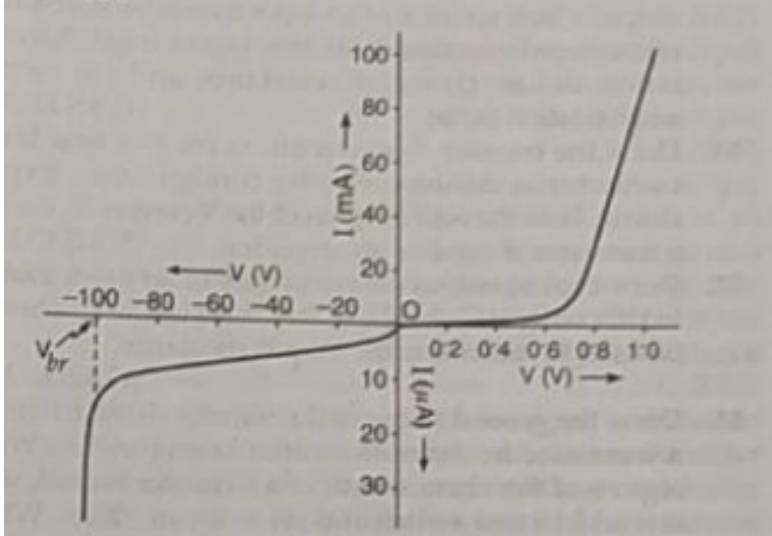**35.** In figure shows the V-I characteristics of semiconductor diode.



Identify


the semiconductor diode.



Watch Video Solution


**36.** In figure shows the V-I characteristics of semiconductor diode. Draw the circuit diagram to obtain the given characteristic of

this device.

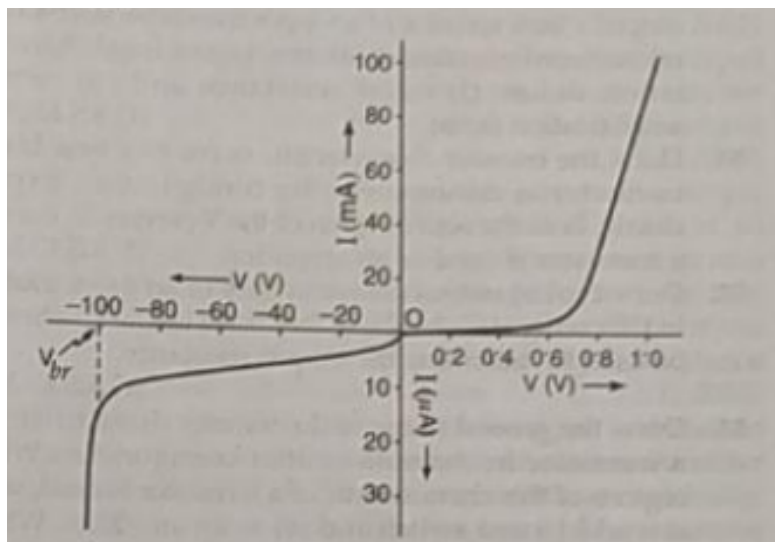

[Watch Video Solution](#)

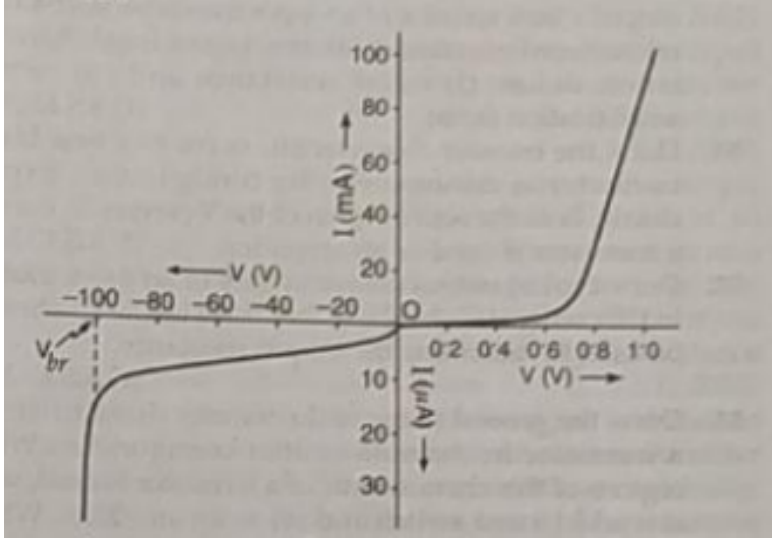37. In figure shows the V-I characteristics of semiconductor diode.



Briefly

explain, how this diode can be used as a voltage regulator.



[Watch Video Solution](#)

**38.** Draw the current versus voltage characteristics curve of a Zener diode. Indicate



the position of Zener voltage. Draw a labelled circuit diagram of a d.c. voltage regulator using a Zener diode.



[Watch Video Solution](#)

**39.** Write in brief about Photo-diodes.



[Watch Video Solution](#)

**40.** What is Zener diode?



[Watch Video Solution](#)

**41.** Draw a circuit diagram to show how a photodiode is biased.



**Watch Video Solution**

**42.** Distinguish between the light emitting diode and photo diode.



**Watch Video Solution**

**43.** What the help of a diagram, show that biasing of a light emitting diode (LED). Give its two advantages over conventional incandescent lamps.



**Watch Video Solution**

**44.** Explain, with the help of a schematic diagram, the principle and working of a Light Emitting Diode. What criterion is kept in mind while choosing the semiconductor material for

such a device ? Write any two advantages of light emitting diode over conventional incandescent lamps.



[Watch Video Solution](#)

**45.** Mention two types of junction transistor.  
How are they represented.



[Watch Video Solution](#)

**46.** Write the function of base region of a transistor. Why is the region made thin and slightly doped?



**Watch Video Solution**

**47.** What is transistor ? Give the symbols of n-p-n and p-n-p transistor.



**Watch Video Solution**

**48.** What is transistor? Give symbols of p-n-p and n-p-n transistor.



**Watch Video Solution**

**49.** With the help of circuit diagram, explain the working of transistor as a common emitter amplifier.



**Watch Video Solution**

**50.** With the help of a circuit diagram, explain the action of a N-P-N junction transistor.



**Watch Video Solution**

**51.** With the help of a circuit diagram, explain the action of a N-P-N junction transistor.



**Watch Video Solution**

**52.** What is transistor ? Give the symbols of n-p-n and p-n-p transistor.



**Watch Video Solution**

**53.** Draw the circuit arrangement for studying the output characteristics of n-p-n transistor in CE configuration. Explain how the output characteristics is obtained.



**Watch Video Solution**



**54.** Draw the circuit arrangement for studying the output characteristics of n-p-n transistor in CE configuration. Explain how the output characteristics is obtained.



**Watch Video Solution**

**55.** Draw the circuit arrangement for studying the output characteristics of n-p-n transistor in CE configuration. Explain how the output characteristics is obtained.



**Watch Video Solution**

**56.** Draw the circuit arrangement for studying the output characteristics of n-p-n transistor in CE configuration. Explain how the output characteristics is obtained.

 [Watch Video Solution](#)

**57.** Explain with diagram, the working of a transistor as a common-emitter amplifier.

 [Watch Video Solution](#)

**58.** Explain with diagram, the working of a transistor as a common-emitter amplifier.



**Watch Video Solution**

**59.** Explain , why the input resistance of a transistor is low and output resistance is high.



**Watch Video Solution**

**60.** If the emitter and base of n-p-n transistor have same doping concentration, explain, how will the collector and base currents be affected.



**Watch Video Solution**

**61.** Discuss the working of p-n-p transistor as an amplifier in common emitter mode.



**Watch Video Solution**

**62.** What is an amplifier?



**Watch Video Solution**

**63.** With the help of a circuit diagram, explain the action of a N-P-N junction transistor.



**Watch Video Solution**

**64.** Discuss the working of n-p-n transistor as an amplifier in common base mode.





[Watch Video Solution](#)

**65.** Discuss the working of p-n-p transistor as an amplifier in common emitter mode.



[Watch Video Solution](#)

**66.** Discuss the working of n-p-n transistor as an amplifier in common base mode.




[Watch Video Solution](#)

**67.** What is an amplifier ? Draw a circuit diagram for an amplifier with PNP transistor in common emitter configuration. Also define current gain, voltage gain and power gain for it.



**Watch Video Solution**

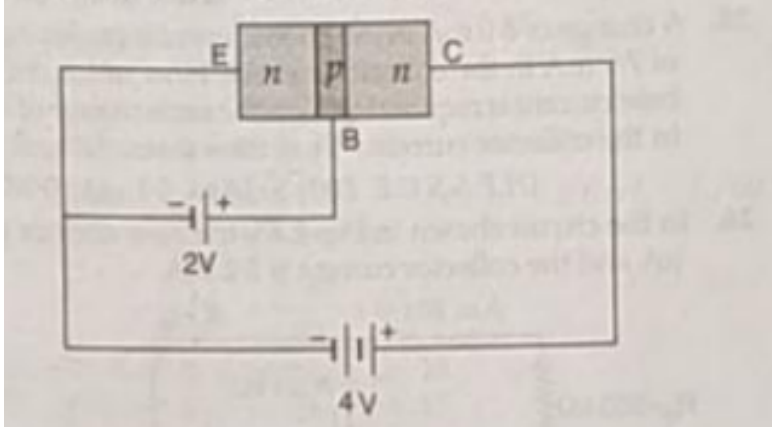**68.** In the n-p-n transistor circuit shown in the figure.



What is

the biasing. Between emitter base and collector-base junctions?



[Watch Video Solution](#)

**69.** What is an amplifier ? Draw a circuit diagram for an amplifier with PNP transistor in common emitter configuration. Also define



current gain, voltage gain and power gain for it.



[Watch Video Solution](#)

**70.** With the help of labelled circuit diagram, discuss the working of transistor as a common emitter amplifier. Find the phase relationship between input and output signals. Also define its voltage gain.



[Watch Video Solution](#)

**71.** With the help of labelled circuit diagram, discuss the working of transistor as a common emitter amplifier. Find the phase relationship between input and output signals. Also define its voltage gain.



**Watch Video Solution**

**72.** With the help of labelled circuit diagram, discuss the working of transistor as a common emitter amplifier. Find the phase relationship

between input and output signals. Also define its voltage gain.



[Watch Video Solution](#)

**73.** With the help of circuit diagram, explain the working of transistor as a common emitter amplifier.



[Watch Video Solution](#)

**74.** With the help of circuit diagram, explain the working of transistor as a common emitter amplifier.



**Watch Video Solution**

**75.** Discuss the working of n-p-n transistor as an amplifier in common base mode.



**Watch Video Solution**

**76.** Define d.c. current gain in common base and common emitter amplifier. Also find a relation between them.



**Watch Video Solution**

**77.** With the help of circuit diagram, explain the working of transistor as a oscillator.



**Watch Video Solution**

**78.** With the help of circuit diagram, explain the working of transistor as a oscillator.



**Watch Video Solution**

**79.** With the help of circuit diagram, explain the working of transistor as a oscillator.



**Watch Video Solution**

**80.** What is an electric oscillator ? With the help of labelled diagram, explain the use of junction transistor as an oscillator.



**Watch Video Solution**

**81.** Draw the circuit of a transistor as an amplifier.



**Watch Video Solution**

**82.** A transistor can be used as a switch by operating it in its cut off state or saturation state. (Yes/No)



**Watch Video Solution**

**83.** Explain the advantages and disadvantages of semiconducting devices as compared to vacuum tube devices.



**Watch Video Solution**



**84.** Explain the advantages and disadvantages of semiconducting devices as compared to vacuum tube devices.



**Watch Video Solution**

**85.** Give important uses of integrated circuits.



**Watch Video Solution**

**86.** Explain the terms depletion layer and potential barrier for a junction diode.



**Watch Video Solution**

**87.** Explain the terms depletion layer and potential barrier for a junction diode.



**Watch Video Solution**

**88.** How does the junction width change when a p-n junction is forward biased?



**Watch Video Solution**

**89.** What is a p-n junction ? Explain with the help of a diagram, how depletion layer is formed near the junction. Also explain what happens to this layer, when the junction is reversed biased.



**Watch Video Solution**

**90.** Explain how the depletion layer and barrier potential are formed in pn junction diode ?



**Watch Video Solution**

**91.** P-N junction is:



**Watch Video Solution**

**92.** What is junction diode ? How is depletion layer formed ? Draw its forward and reverse bias characteristics by showing biasing of diodes ?



**Watch Video Solution**

**93.** Answer the following questions: Why is the current under reverse bias independent to the applied potential up to a critical voltage?



**Watch Video Solution**

**94.** Answer the following questions: Why does the reverse current show a sudden increase at the critical voltage?



**Watch Video Solution**

**95.** Draw the voltage current characteristics of a p-n junction bias?



**Watch Video Solution**

**96.** The resistance of a p-n junction is low, when forward biased and is high, when reverse is biased. Explain.



**Watch Video Solution**

**97.** Explain with the help of circuit diagram, how V-I characteristics of pn junction diode are obtained in forward biasing.



**Watch Video Solution**

**98.** With the help of circuit diagram, explain the  $V-I$  characteristics of p-n junction diode in reverse biasing.



[Watch Video Solution](#)

**99.** Define Rectification. With the help a circuit diagram explain the working of p-n junction diode as a half wave rectifier.



[Watch Video Solution](#)



**100.** Define Rectification. With the help a circuit diagram explain the working of p-n junction diode as a half wave rectifier.



**Watch Video Solution**

**101.** Define Rectification. With the help a circuit diagram explain the working of p-n junction diode as a half wave rectifier.



**Watch Video Solution**

**102.** What is rectifier ? Explain the working of junction diode as a full wave rectifier, with diagram.



**Watch Video Solution**

**103.** State the principle of working of p-n-diode as a rectifier. Explain with the help of a circuit diagram, the use of p-n diode as a full wave rectifier. Draw a sketch of the input and output waveforms.



**Watch Video Solution**

**104.** Discuss the construction and working of diode as full wave rectifier



**Watch Video Solution**

**105.** Draw a labelled circuit diagram of a full wave rectifier using junction diodes.



**Watch Video Solution**

**106.** Draw a labelled circuit diagram of a full wave rectifier using junction diodes.



**Watch Video Solution**

**107.** With the help of a circuit diagram, explain the action of a N-P-N junction transistor.



**Watch Video Solution**

**108.** What is light emitting diode (LED)?



[Watch Video Solution](#)

**109.** What is transistor ? Give the symbols of n-p-n and p-n-p transistor.



[Watch Video Solution](#)

**110.** What is transistor? Give symbols of p-n-p and n-p-n transistor.



[Watch Video Solution](#)

**111.** With the help of a circuit diagram, explain the action of a N-P-N junction transistor.



**Watch Video Solution**

**112.** With the help of circuit diagram, explain the working of transistor as a common emitter amplifier.



**Watch Video Solution**

**113.** Draw circuit diagram of common base amplifier using p-n-p transistor.



**Watch Video Solution**

**114.** Draw the circuit arrangement for studying the output characteristics of n-p-n transistor in CE configuration. Explain how the output characteristics is obtained.



**Watch Video Solution**

**115.** For an n-p-n transistor in the common emitter configuration, draw a labelled circuit diagram of an arrangement for measuring the collector current as a function of collector emitter voltage for at least two different values of base current. Draw the shape of the curves obtained. Define the terms output resistance



**Watch Video Solution**

**116.** In a p-n-p transistor circuit, the collector current is 10mA , If 90% of the electrons



emitted reach the collector , what is base current ?



[Watch Video Solution](#)

**117.** With the help of circuit diagram, explain the working of transistor as a common emitter amplifier.



[Watch Video Solution](#)

**118.** Draw the circuit arrangement for studying the output characteristics of n-p-n transistor in CE configuration. Explain how the output characteristics is obtained.



**Watch Video Solution**

**119.** Define input resistance of a transistor used in its common emitter configuration.



**Watch Video Solution**

**120.** Define input resistance of a transistor used in its common emitter configuration.



**Watch Video Solution**

**121.** Define input resistance of a transistor used in its common emitter configuration.



**Watch Video Solution**

**122.** Discuss the working of n-p-n transistor as an amplifier in common base mode.



**Watch Video Solution**

**123.** Draw circuit diagram of common base amplifier using p-n-p transistor.



**Watch Video Solution**

**124.** If the emitter and base of n-p-n transistor have same doping concentration, explain, how will the collector and base currents be affected.



**Watch Video Solution**

**125.** With the help of labelled circuit diagram, explain the working of transistor as a switch.



**Watch Video Solution**

**126.** With the help of circuit diagram, explain the working of transistor as a common emitter amplifier.



**Watch Video Solution**

**127.** Draw a simple circuit of a CE transistor amplifier. Explain its working. Show that the

voltage gain,  $A_V$  of the amplifier is given by

$$A_v = - \frac{\beta_{ac} R_L}{r_i}$$

where  $\beta_{Ac}$  is the current gain,

$R_L$  is the load resistance and  $r_1$  is the input

resistance of the transistor. What is the

significance of the negative sign in the expression for the voltage gain?



[Watch Video Solution](#)

**128.** What is an amplifier ? Draw a circuit diagram for an amplifier with PNP transistor in common emitter configuration. Also define current gain, voltage gain and power gain for it.



[Watch Video Solution](#)

**129.** Discuss the working of p-n-p transistor as an amplifier in common emitter mode.

 [Watch Video Solution](#)

**130.** What is an amplifier ? Draw a circuit diagram for an amplifier with PNP transistor in common emitter configuration. Also define current gain, voltage gain and power gain for it.

 [Watch Video Solution](#)



**131.** Draw the circuit arrangement for studying the output characteristics of n-p-n transistor in CE configuration. Explain how the output characteristics is obtained.



**Watch Video Solution**

**132.** Explain with diagram, the working of a transistor as a common-emitter amplifier.



**Watch Video Solution**

**133.** Differentiate between three segments of a transistor on the basis of their size and level of doping.



**Watch Video Solution**

**134.** How is a transistor biased to be in active state?



**Watch Video Solution**

**135.** With the help of a circuit diagram, explain the action of a N-P-N junction transistor.



**Watch Video Solution**


**136.** How the common emitter n-p-n transistor is used as a switch? Explain with the help of a circuit diagram.



**Watch Video Solution**

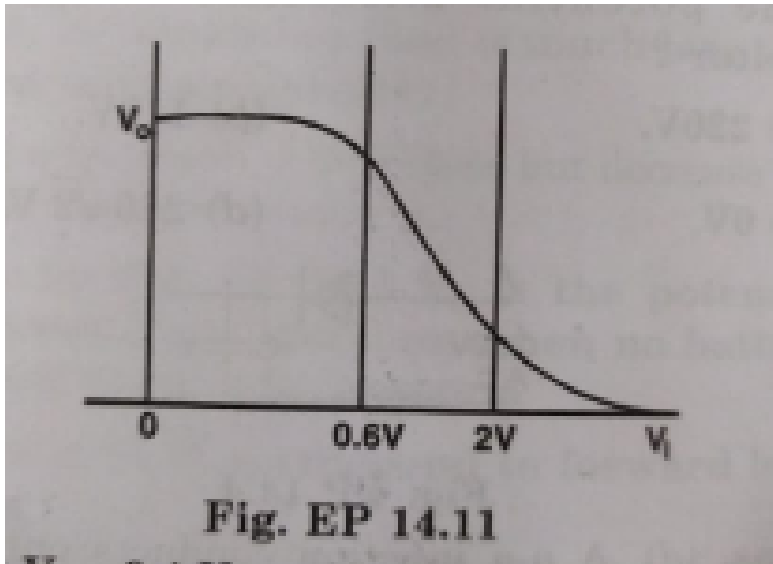137. Figure EP 14.11 shows the transfer characteristics of a base biased CE transistor.

Which of the following statements are true?



[Watch Video Solution](#)

**138.** What is an electric oscillator ? With the help of labelled diagram, explain the use of junction transistor as an oscillator.



**Watch Video Solution**

**139.** What is an electric oscillator ? With the help of labelled diagram, explain the use of junction transistor as an oscillator.



**Watch Video Solution**

**140.** With the help of circuit diagram, explain the working of transistor as a oscillator.



**Watch Video Solution**

**141.** With the help of circuit diagram, explain the working of transistor as a oscillator.



**Watch Video Solution**

**142.** What is an oscillator ? Draw a labelled circuit diagram for an oscillator using PNP transistor. What is the function of feed back coil in it ? Write an expression for the frequency of waves produced by it. What is the use of waves produced by it ?



**Watch Video Solution**

**143.** What is an oscillator ? Draw a labelled circuit diagram for an oscillator using PNP

transistor. What is the function of feed back coil in it ? Write an expression for the frequency of waves produced by it. What is the use of waves produced by it ?



[Watch Video Solution](#)

**144.** What is an oscillator ? Draw a labelled circuit diagram for an oscillator using PNP transistor. What is the function of feed back coil in it ? Write an expression for the



frequency of waves produced by it. What is the use of waves produced by it ?



[Watch Video Solution](#)

**145.** In a forward biased silicon diode, current occurs at close to 0.7 V and increase rapidly with very small further potential difference increase. What current will flow, when there is a 200 ohm resistor in series with the diode with a 10 V battery across the series combination?




[Watch Video Solution](#)

**146.** A PN junction diode when forward biased has a drop of 0.5 V which is assumed to be independent of current. The current in excess of 10 mA through the diode produces large joule heating which damages the diode. If we diode, the resistor used in series with the diode so that the maximum current does not exceed 5 mA



[Watch Video Solution](#)

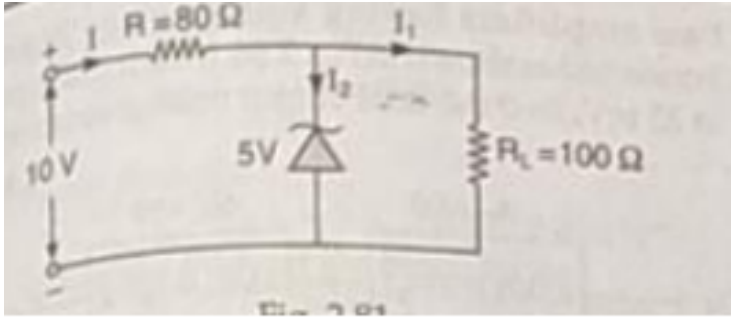**147.** In the circuit shown in the figure, find the current passing through  $r_L$  and zener diode.




**Watch Video Solution**

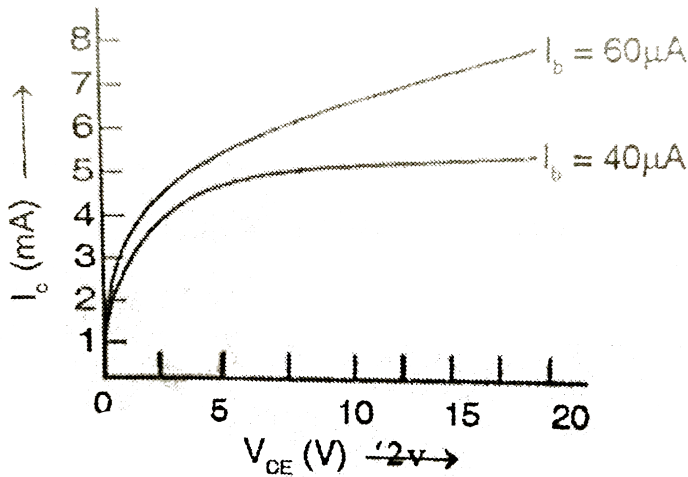**148.** A certain n-p-n transistor has the common emitter output characteristics as shown in the figure.

Find the emitter current at

$$V_{CE} = 12.5V \text{ and } I_b = 60\mu A,$$




Watch Video Solution

**149.** A certain n-p-n transistor has the common emitter output characteristics as shown in the figure.

Find the Current gain ' $\beta$ ' at  $V_{CE}=12.5$  V and

$I_b=60 \mu\text{A}$ .

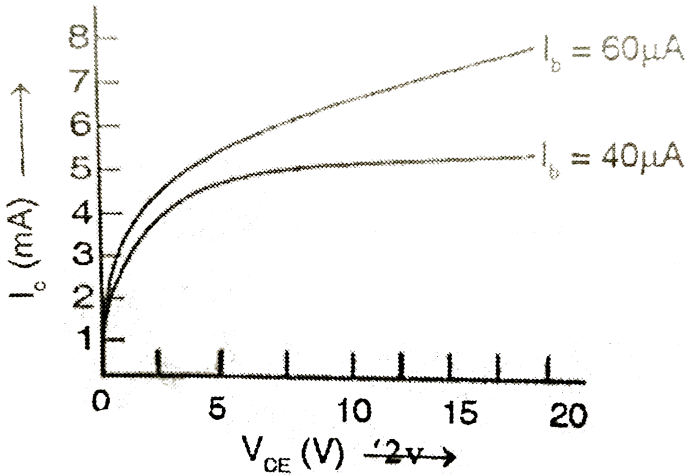

[Watch Video Solution](#)

**150.** For a common base amplifier, emitter current is 5.2 mA and base current is 0.22 mA.

Find the current gain of the amplifier.



[Watch Video Solution](#)

**151.** For a transistor working as common base amplifier, current gain is 0.97 and base current is 0.12 mA. Calculate the collector and emitter current.



[Watch Video Solution](#)

**152.** In a common base transistor amplifier, if the input resistance is 200 ohm and load

resistance is 20 kilohm, find Voltage gain

Given current gain of common base transistor

is 0.95



[Watch Video Solution](#)

**153.** In a common base transistor amplifier, if

the input resistance is 200 ohm and load

resistance is 20 kilohm, find power gain.


Given current gain of common base transistor

is 0.95



[Watch Video Solution](#)

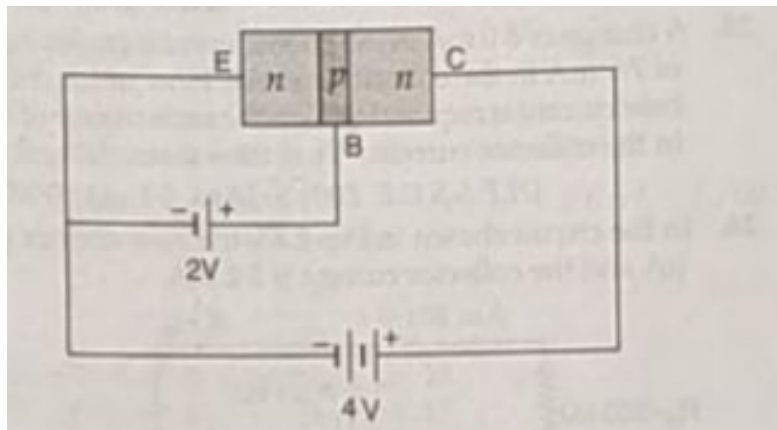**154.** In the n-p-n transistor circuit shown in the figure.




What is the potential difference between base and collector



**Watch Video Solution**



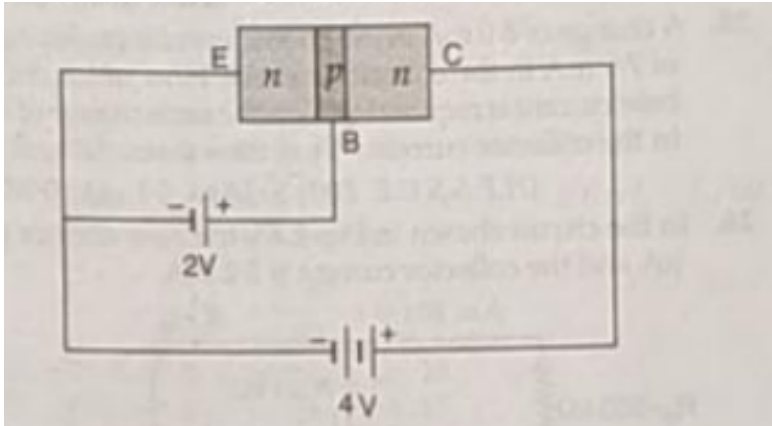155. In the n-p-n transistor circuit shown in the figure.



What is the biasing. Between emitter base and collector-base junctions?



[Watch Video Solution](#)

**156.** Calculate emitter current for which  $\beta = 100$  and base current  $I_b = 20\mu A$ .



**Watch Video Solution**

**157.** For a common emitter amplifier current gain = 50 if the emitter current is 6.6 mA. Calculate the collector and base current.



**Watch Video Solution**

**158.** In a common-emitter mode of transistor d.c. current gain is 20 and the emitter current is 7 mA. Calculate base current



**Watch Video Solution**

**159.** In a common-emitter mode of transistor d.c. current gain is 20 and the emitter current is 7 mA. Calculate base current



**Watch Video Solution**

**160.** The current gain of a transistor in a common base arrangement is 0.95. Find the voltage gain and power gain if the load resistance of output circuit is  $400k\Omega$  and the input resistance is  $200\Omega$ .



**Watch Video Solution**

**161.** A common-emitter circuit has an input resistance of  $0.6 k\Omega$  and output resistance of  $51k\Omega$  . If the current gain is 64, find voltage gain and power gain.



[Watch Video Solution](#)

**162.** In a common emitter amplifier, using output resistance of 5000 ohm and input resistance of 2000ohm, if the peak value of input signal voltage is 10 m V and  $\beta=50$ , then the peak value of output voltage ?



[Watch Video Solution](#)

**163.** A transistor connected in common emitter configuration has input resistance  $R_{in} = 2K\Omega$  and load resistance of  $5K\Omega$ . If  $\beta = 60$  and an input signal  $12\text{ mV}$  is applied, calculate the resistance gain.



**Watch Video Solution**

**164.** For a common emitter amplifier, current gain is  $70$ . If the emitter is  $8.8\text{ mA}$ , calculate the collector and base current. Also calculate

current gain , when transistor is worked on common base amplifier.



[Watch Video Solution](#)

**165.** A common-emitter circuit has an input resistance of  $0.6\text{ k}\Omega$  and output resistance of  $51\text{ k}\Omega$  . If the current gain is 64, find voltage gain and power gain.



[Watch Video Solution](#)

**166.** the input resistance of a comon-emitter amplifier is  $2k\Omega$  and a.c. current gain is 20. If the laod resistor used is  $5k\Omega$  calculate the voltage gain of the amplifier



**Watch Video Solution**

**167.** the input resistance of a comon-emitter amplifier is  $2k\Omega$  and a.c. current gain is 20. If the laod resistor used is  $5k\Omega$  calculate the transconductance of the transistor used.








[Watch Video Solution](#)

**168.** In a transistor, a change of 7.9 mA in emitter current produces a change of 7.8 mA in the collector current produces a change of 7.7 mA in the collector current. What change in the base current is necessary to produce an equivalent change in the collector current?



[Watch Video Solution](#)

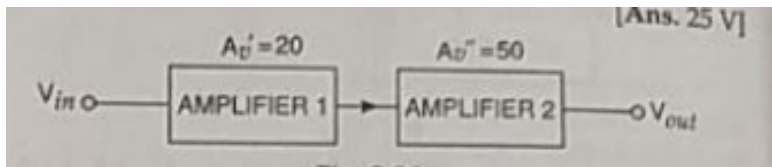**169.** Two amplifiers having voltage gains 20 and 50 are connected as shown in the figure. If the initial input voltage is 25 mV, find the final output voltage obtained.



**Watch Video Solution**

**170.** A crystal diode having internal resistance  $200\Omega$  is used as a half rectifier. If the applied voltage is  $V = 50 \sin \omega t$  volt and load

resistance is  $800\Omega$ , find maximum output current



[Watch Video Solution](#)

**171.** A crystal diode having internal resistance  $200\Omega$  is used as a half rectifier. If the applied voltage is  $V = 50 \sin \omega t$  volt and load resistance is  $800\Omega$ , find maximum output current



[Watch Video Solution](#)

**172.** A crystal diode having internal resistance  $200\Omega$  is used as a half rectifier. If the applied voltage is  $V = 50 \sin \omega t$  volt and load resistance is  $800\Omega$ , find maximum output current



**Watch Video Solution**

**173.** A crystal diode having internal resistance  $200\Omega$  is used as a half rectifier. If the applied voltage is  $V = 50 \sin \omega t$  volt and load

resistance is  $800\Omega$ , find maximum output current



[Watch Video Solution](#)

**174.** A p-n photodiode is fabricated from a semiconductor with band gap of 2.8 eV. Can it detect a wavelength of 6000 nm?



[Watch Video Solution](#)