



PHYSICS

BOOKS - BETTER CHOICE PUBLICATION

DIGITAL ELECTRONICS

Very Short Answer Type Questions

1. Write the truth table of OR gate.



Watch Video Solution

2. Write the truth table of AND gate.



[Watch Video Solution](#)

3. Write the truth table of 'NOT' logic gate .



[Watch Video Solution](#)

4. Write down the truth table of AND gate and also draw its logic symbol.



[Watch Video Solution](#)

5. Write down the truth table of OR gate and also draw the logic symbol.



[Watch Video Solution](#)

6. What is logic gate ?



[Watch Video Solution](#)

7. Draw the logic symbol of AND gate. Write its truth table also. How can one realise such a gate in actual practice by using junction diodes ?



[Watch Video Solution](#)

8. Draw the logic symbol of NOR gate.



[Watch Video Solution](#)

9. Draw the logic symbol of NAND gate.



Watch Video Solution

10. The following truth table represents .

<i>A</i>	<i>B</i>	<i>y</i>
<i>0</i>	<i>0</i>	<i>1</i>
<i>1</i>	<i>0</i>	<i>0</i>
<i>0</i>	<i>1</i>	<i>0</i>
<i>1</i>	<i>1</i>	<i>0</i>

A. AND gate

B. NOR gate

C. OR gate

D. NAND gate .

Answer: B



Watch Video Solution

11. The following truth table represents :

<i>A</i>	<i>B</i>	<i>y</i>
<i>0</i>	<i>0</i>	<i>1</i>
<i>1</i>	<i>0</i>	<i>1</i>
<i>0</i>	<i>1</i>	<i>1</i>
<i>1</i>	<i>1</i>	<i>0</i>

A. AND gate

B. NOR gate

C. OR gate

D. NAND gate .

Answer: D



Watch Video Solution

12. The output of OR gate is 1

A. if either input is zero

B. if both inputs are zero

C. only, if both inputs are 1

D. if either or both inputs are 1 .

Answer: d



Watch Video Solution

Short Answer Type Questions

1. Draw the logic symbol for 'OR' logic gate and write its truth tale .



Watch Video Solution

2. Draw the logic symbol for 'AND' logic gate and write its truth table .



[Watch Video Solution](#)

3. Draw the logic symbol for 'NOT' logic gate and write its truth table .



[Watch Video Solution](#)

4. Draw the logic symbol and write truth table of NAND logic gate



[Watch Video Solution](#)

5. Draw the logic symbol and write truth table of NOR logic gate



[Watch Video Solution](#)

6. How 'NAND' logic gate is obtained from basic gates ? Draw its logic symbol and write its truth table.



[Watch Video Solution](#)

7. How 'NAND' logic gate is obtained from basic gates ? Draw its logic symbol and write its truth table.




[Watch Video Solution](#)

8. Give the logic symbol, truth table and Boolean expression for NOR gate.


 [Watch Video Solution](#)

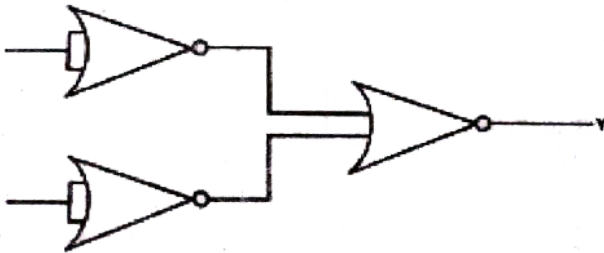9. Make the truth table for all possible inputs of the following circuit .



 [Watch Video Solution](#)

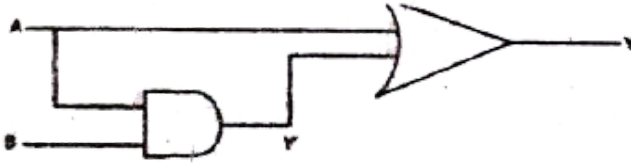10. Make the truth table for all possible inputs of the following gates .



[Watch Video Solution](#)

11. What is logic symbol and truth table for NAND gate ? Also give its Boolean expression.



[Watch Video Solution](#)

12. Write logic symbol, Boolean expression and truth table of AND and NOR gate.



Watch Video Solution

13. How would you set up a circuit to obtain NOT gate using a transistor?



Watch Video Solution

14. Write the truth table of NAND gate. Draw its symbol. Draw a circuit to obtain NOT gate using NAND gate only.



Watch Video Solution

15. Draw a circuit to obtain OR gate using NAND gate only .



Watch Video Solution

16. Write Boolean expression and the truth table of OR



Watch Video Solution

17. What is logic symbol and truth table for NAND gate ? Also give its Boolean expression.



Watch Video Solution

18. Give the logic symbol, truth table and Boolean expression for OR gate.



Watch Video Solution

19. Give the logic symbol, truth table and Boolean expression for NOR gate.



Watch Video Solution

20. Give the logic symbol, truth table and Boolean expression for AND gate.



[Watch Video Solution](#)

21. Draw the logic symbol of NAND gate.



[Watch Video Solution](#)

22. Write Boolean expression and the truth table of OR



[Watch Video Solution](#)

23. Write logic symbol, Boolean expression and truth table of NAND and OR gate.



[Watch Video Solution](#)

24. Write logic symbol, Boolean expression and truth table of NOT and OR gate.



[Watch Video Solution](#)

Long Answers Type Questions

1. Draw the logic symbol of NOT gate. Write its truth table. Explain, how this gate can be realized in actual practice by using transistor



[Watch Video Solution](#)

2. Draw the logic symbol of OR gate. Write its truth table. Explain how this gate can be realized in actual practice by using junction diodes.



[Watch Video Solution](#)

3. Draw the logic symbol of OR gate. Write its truth table. Explain how this gate can be realized in actual practice by using junction diodes.



[Watch Video Solution](#)